
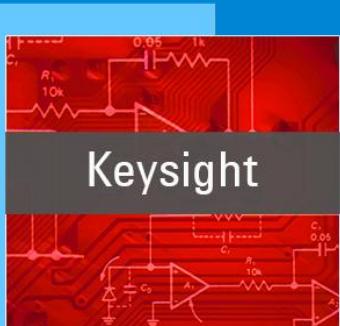


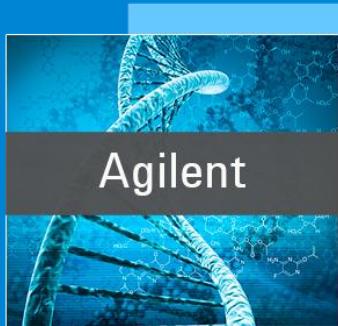Retos y Soluciones en Medidas de Impedancia



Adolfo Del Solar

Application Engineer
adolfo_del-solar@agilent.com

Agenda



Unlocking Measurement Insights for 75 Years

- **Introduction**
- **Impedance fundamentals**
- **Measurement methods**
- **Fixturing and cabling**
- **Calibration and compensation**
- **Solution selection process**

Agenda




Unlocking Measurement Insights for 75 Years

- **Introduction**
 - Impedance test environment
 - Challenges
 - Components tested

Industry Distribution



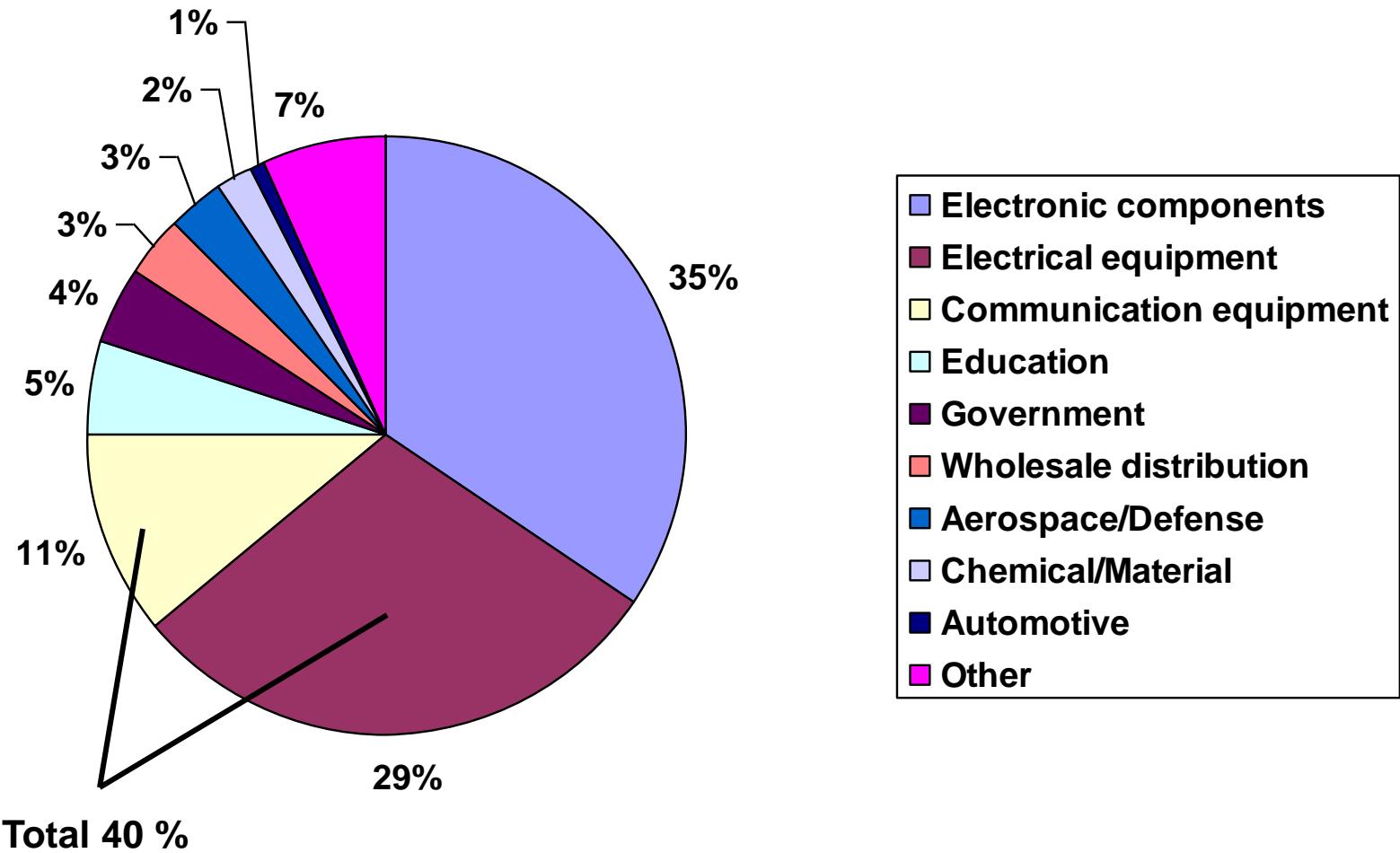
Unlocking Measurement Insights for 75 Years



Geographical Distribution



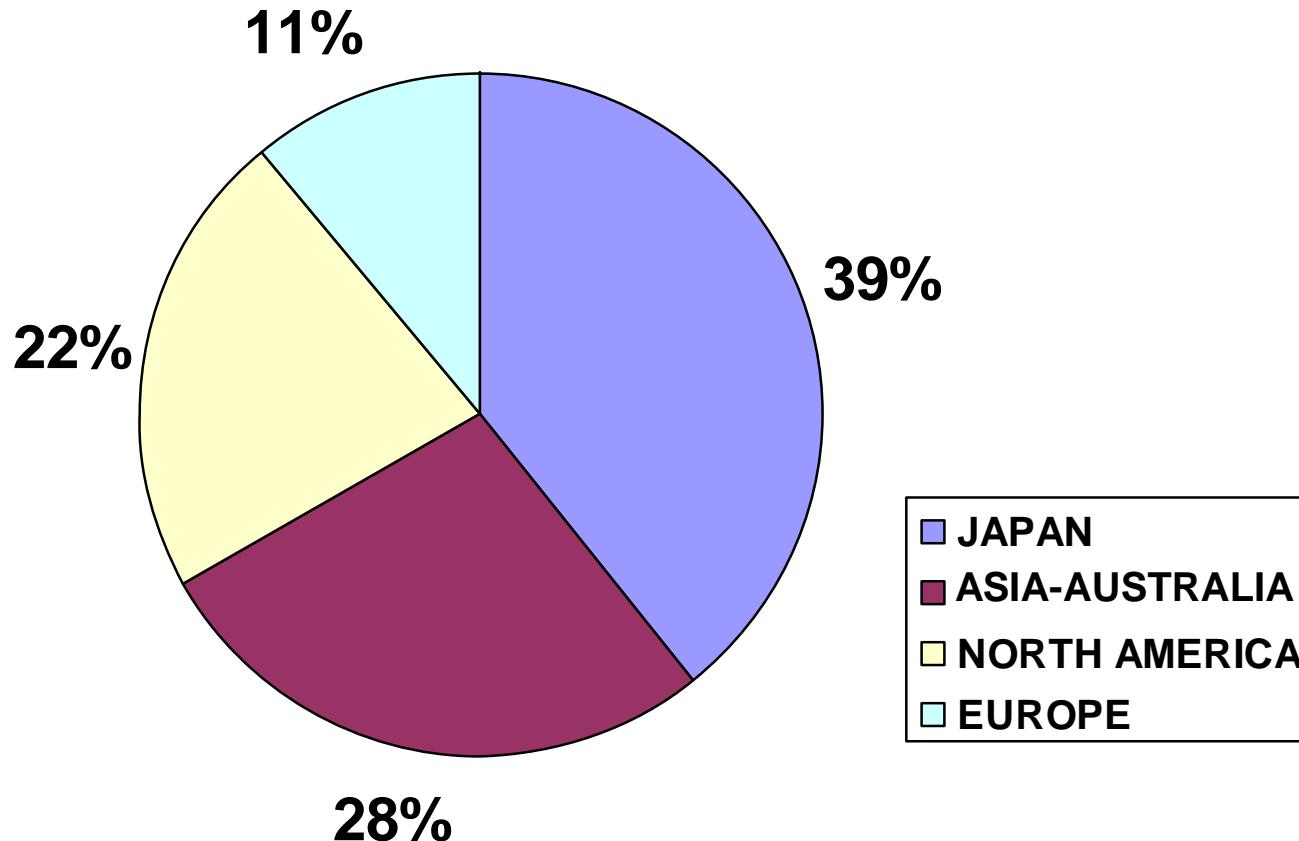Unlocking Measurement Insights for 75 Years



Profile: Component Manufacturers



Unlocking Measurement Insights for 75 Years

- **Impedance testing is done throughout the design and manufacturing processes**
- **Material evaluation (ceramics, inductor cores)**
 - Ensures component performance and quality
- **Production test**
 - Minimizes production failure rate
 - Ensures that specifications are met
- **Accuracy and speed requirements vary**



Profile: Equipment Manufacturers



Unlocking Measurement Insights for 75 Years

- **Incoming inspection**

- Find defective components before they are used
- Quality assurance departments may use several types of impedance measuring instruments

- **Circuit design**

- **Circuit evaluation**

- Check all components on the PC board
- Probing required



Profile: Education and Research



Unlocking Measurement Insights for 75 Years

- Measuring material and component behavior over a wide range of conditions
- Testing new and experimental materials
- Key instrument features:
 - Wide range of capabilities
 - PC connectivity for simplified data collection and analysis



Agenda



Unlocking Measurement Insights for 75 Years

- **Introduction**
 - Impedance test environment
 - Challenges
 - Components tested

Current Trends in Test Requirements



Unlocking Measurement Insights for 75 Years

- Higher frequencies
- High quality/low loss
- Smaller size
- Lower price
- Stable performance in various environments




Agilent Technologies

Agilent Technologies
February 2014



Higher Frequency / Lower Loss

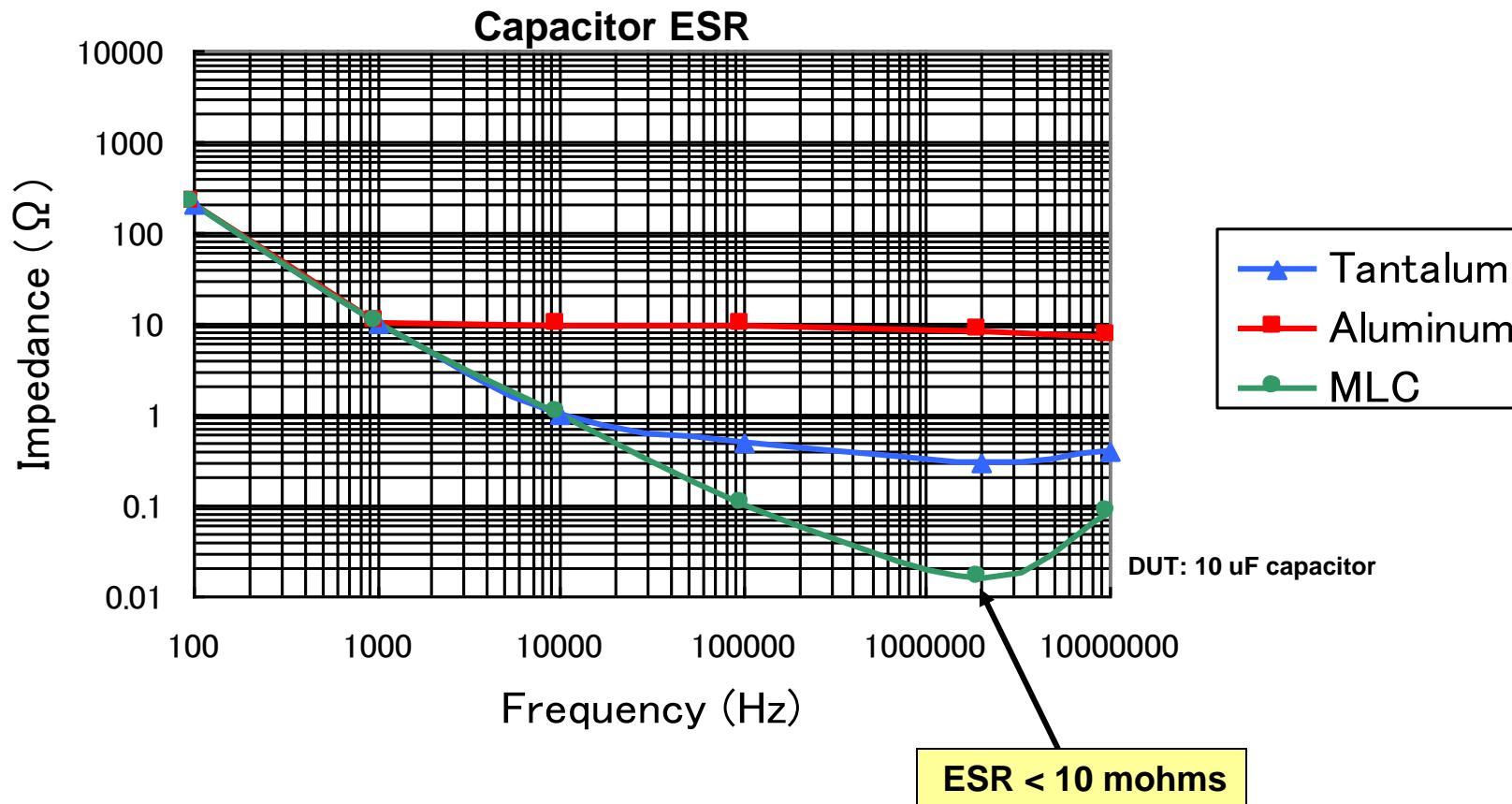- Equivalent series resistance (ESR) is a key parameter



Smaller SMDs

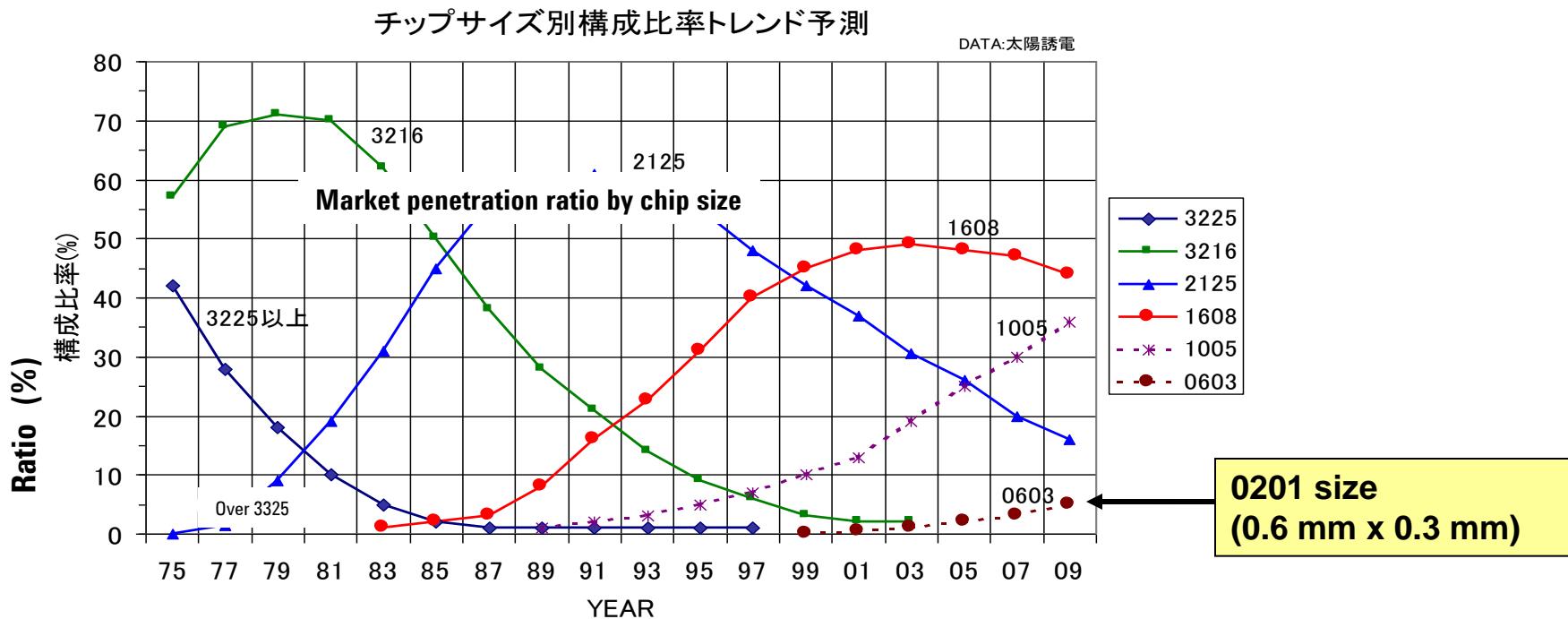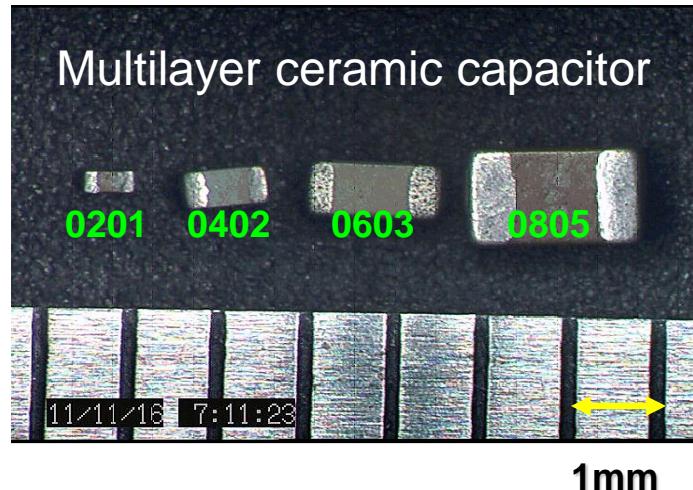- **Extremely small packages**
 - As small as 0.02 x 0.01 inches
 - Require special test fixture



Agenda



Unlocking Measurement Insights for 75 Years

- **Introduction**
 - Impedance test environment
 - Challenges
 - Components tested

Example DUT



Unlocking Measurement Insights for 75 Years



Amplifier Circuit

Antenna

Battery

Cable

Capacitor, Ceramic

Capacitor, Electrolytic

Capacitor, Film

Connector

Diode

IC Package

Inductor, IF/RF

Inductor, Ferrite Core

Inductor, Power

Inductor, Transformer



HDD Head, Magnetic

HDD Head, MR

Material, Dielectric

Material, Magnetic

PC board

Relay

Resistor

Resonator, Ceramic


Resonator, Crystal

RFID

Switch


Transistor



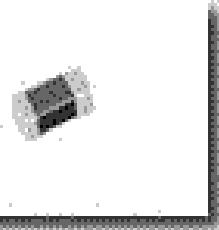

Ceramic (<10 μ F)

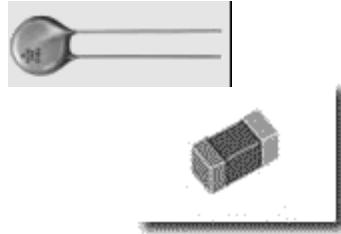- 0.1 pF to 10 μ F
- Low D/high Q
- Wide capacitance range



Ceramic (>10 μ F)

- 10 μ F to 200 μ F
- High capacitance



Electrolytic

- 0.1 μ F to 0.1 F
- High capacitance




Film

- 20 pF to 400 μ F
- Low D/high Q
- High stability
- High reliability



RF/IF

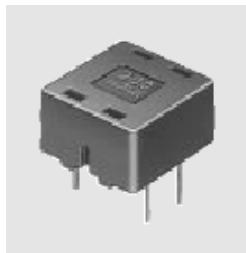- 100 kHz to 6 GHz
- Low D/high Q
- High SRF
- Small size



EMI

- 10 kHz to 1 GHz
- Noise suppression
 - Power line
 - Signal line



Power

- Switching freq.
- High current



Transformer

- Power trans. to 120 Hz
- Switching trans. to 1 MHz
- AC voltage conversion

Agenda




Unlocking Measurement Insights for 75 Years

- Introduction
- **Impedance fundamentals**
 - What is impedance?
 - Parasitics
 - Ideal, real and measured values
 - Component dependency factors

Definition of Impedance (Z)

- Total opposition a device or circuit offers to the flow of AC

Imaginary axis

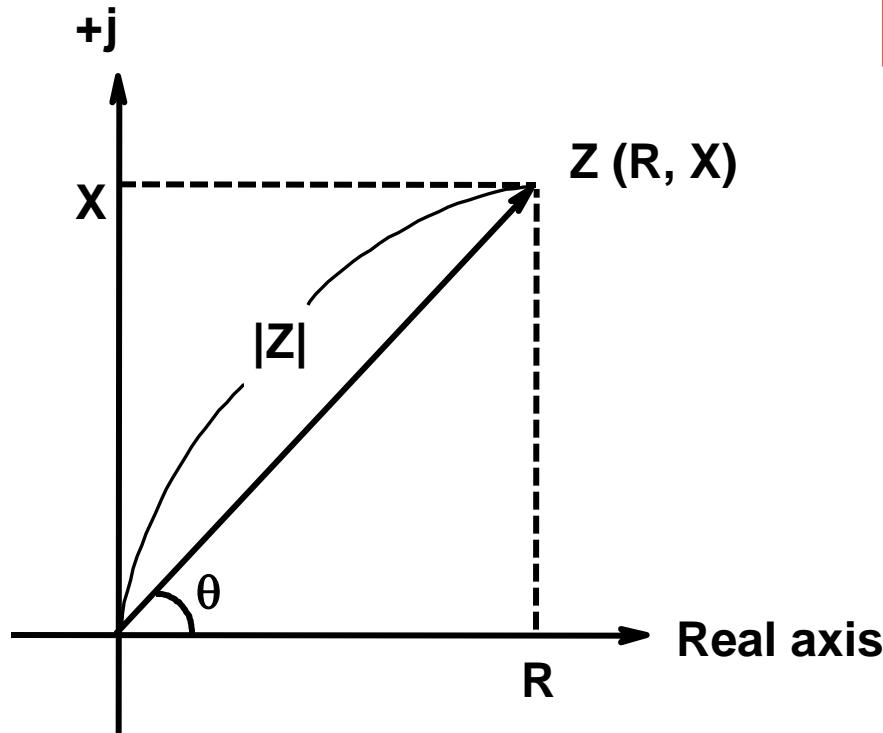

$$Z = R + jX = |Z| \angle \theta$$

$$R = |Z| \cos \theta$$
$$X = |Z| \sin \theta$$

$$|Z| = \sqrt{R^2 + X^2}$$

$$\theta = \tan^{-1}(X/R)$$



Series and Parallel Combinations


Real and imaginary components are connected in series



$$Z = R + jX$$

(Impedance is easier to express)

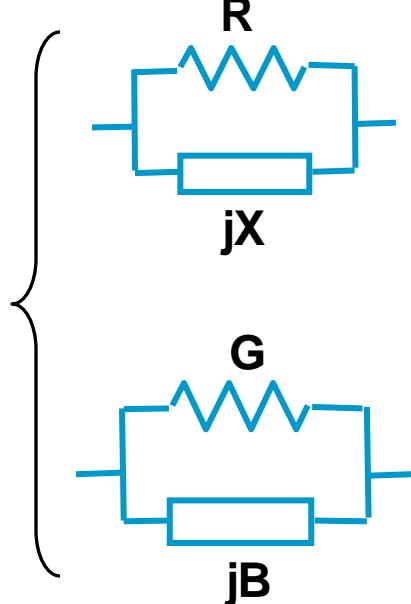Real and imaginary components are connected in parallel




$$Z = \frac{jRX}{R + jX} = \frac{RX^2}{R^2 + X^2} + j \frac{R^2X}{R^2 + X^2}$$

(Impedance is too complex)



$$Y = G + jB$$

(Admittance is easier)


Impedance Plane

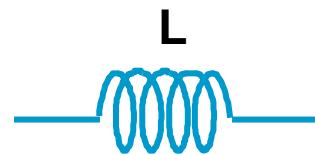


$$X_L = 2\pi fL = \omega L$$

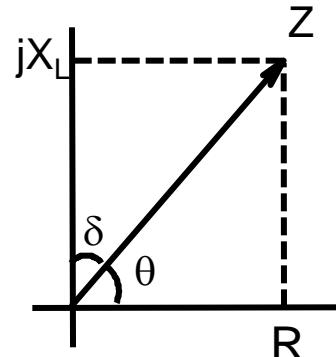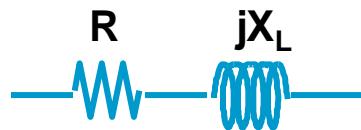

(a) Inductive vector
on impedance plane

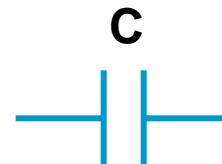
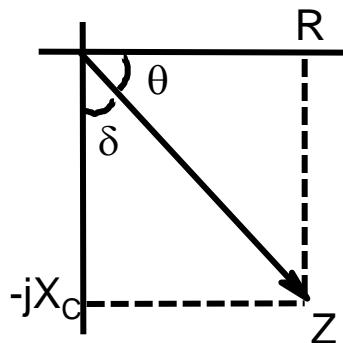
$$X_C = \frac{1}{2\pi fC} = \frac{1}{\omega C}$$





(b) Capacitive vector
on impedance plane



$$\begin{aligned} Q &= \text{quality factor} = \frac{X_L}{R} = \frac{-X_C}{R} \\ &= \tan \theta \end{aligned}$$

$$\begin{aligned} D &= \text{dissipation factor} = \frac{1}{Q} \\ &= \tan \delta \end{aligned}$$

Admittance Plane

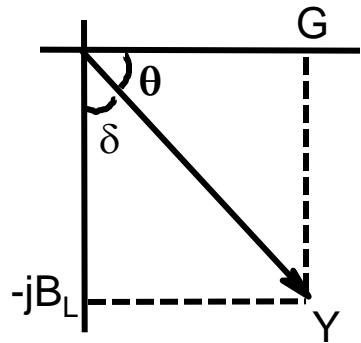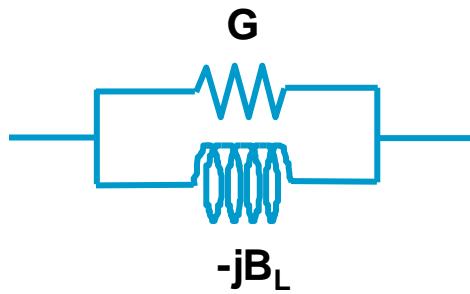

(c) Inductive vector
on admittance plane

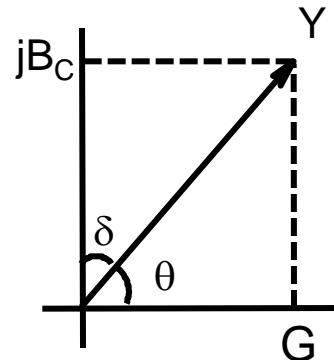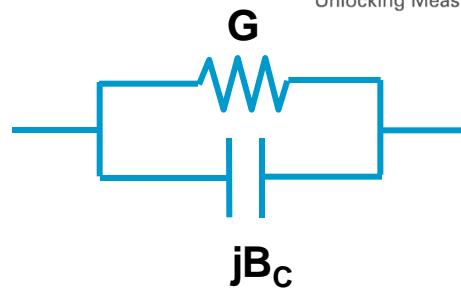

(d) Capacitive vector
on admittance plane

$$Q = \frac{-B_L}{G} = \frac{B_C}{G} = \tan \theta$$

$$D = \frac{1}{Q} = \tan \delta$$

Quality and Dissipation Factors



Unlocking Measurement Insights for 75 Years

- $Q = \frac{\text{Energy stored}}{\text{Energy lost}} = \frac{X_L}{R}$ (inductors)
- As $R \Rightarrow 0$, $Q \Rightarrow \infty$ (better component)
- $D = \frac{1}{Q} = \frac{R}{-X_C}$ (capacitors)
- As $R \Rightarrow 0$, $D \Rightarrow 0$ (better component)


Agenda



Unlocking Measurement Insights for 75 Years

- Introduction
- **Impedance fundamentals**
 - What is impedance?
 - Parasitics
 - Ideal, real and measured values
 - Component dependency factors

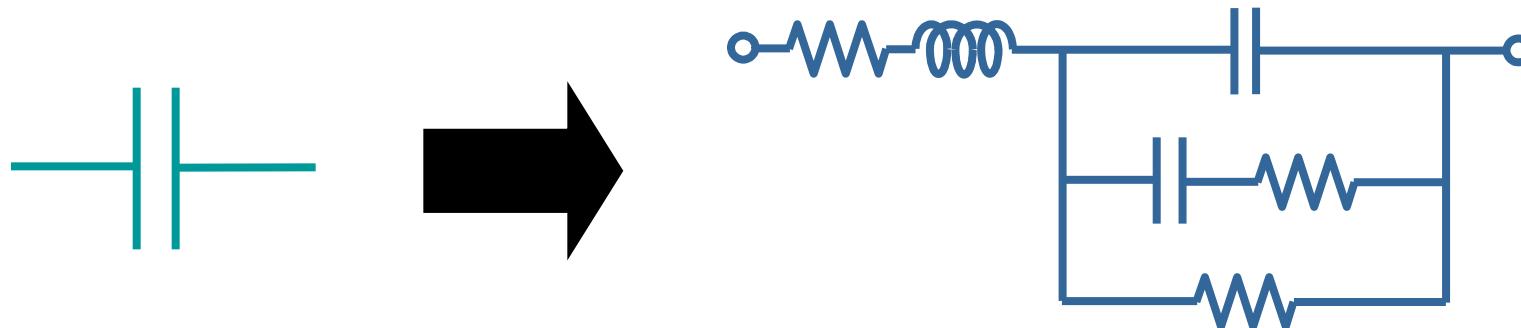
- No real components are purely resistive or reactive
 - Every component is a combination of R, C and L elements
 - The unwanted elements are called **parasitics**



Capacitor Equivalent Circuit

Series and Parallel Models

Capacitor Equivalent Circuit

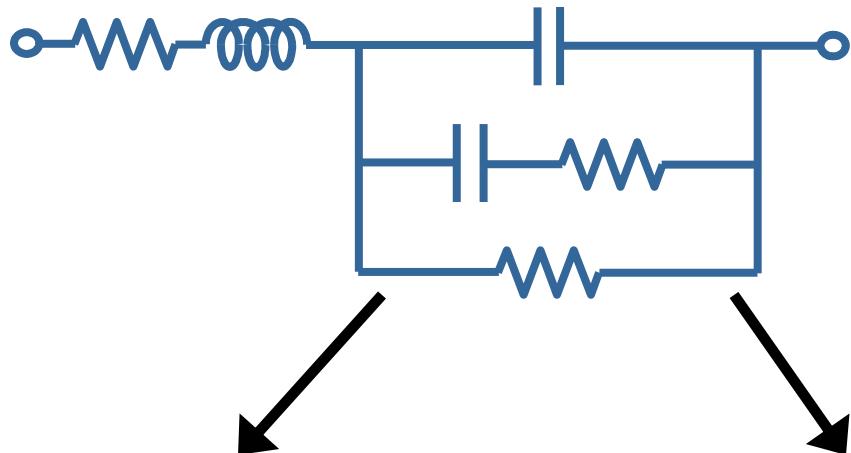


Series Model



Low-Impedance Device
(Large C, Small L)

Parallel Model

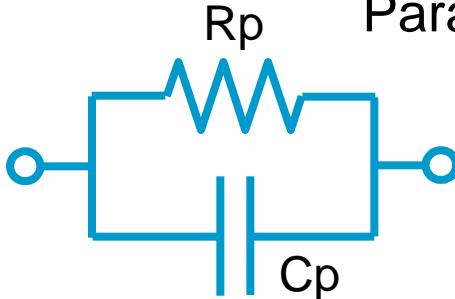


High-Impedance Device
(Small C, Large L)

Which Model is Correct?



Series model

?

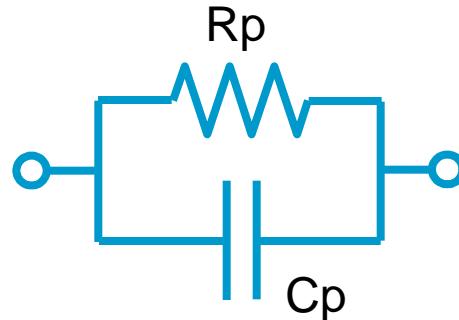

Parallel model

- Both are correct:

$$C_s = C_p (1 + D^2)$$

- For a low Q (high D) device, one model will be more accurate
- For a high Q (low D) device, $C_s \approx C_p$

Agenda




Unlocking Measurement Insights for 75 Years

- Introduction
- **Impedance fundamentals**
 - What is impedance?
 - Parasitics
 - Ideal, real and measured values
 - Component dependency factors

Ideal, Real, and Measured Values


- **Ideal value**

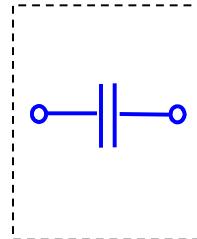- Excludes effects of parasitics
- Academic interest only




- **Real value**

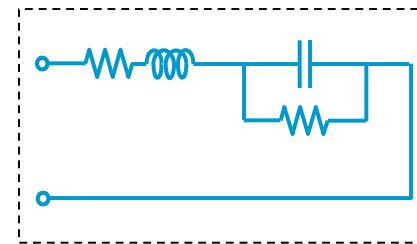- Takes into consideration the parasitics
- Frequency dependent




- **Measured value**

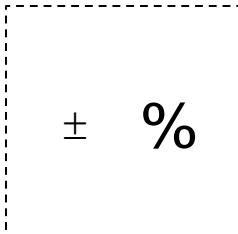
- The value obtained with and displayed by the measuring instrument.



Instrument

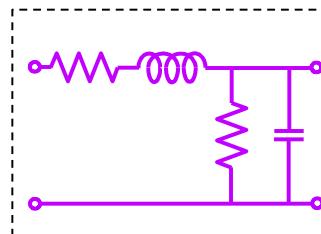

Test fixture

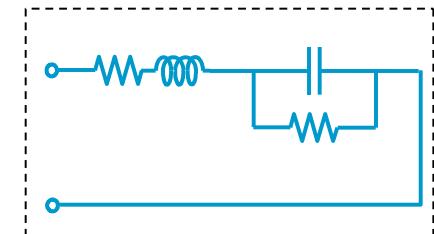

Real-world device

The goal of measurement: measured value very close to real value

Agenda




Unlocking Measurement Insights for 75 Years

- Introduction
- **Impedance fundamentals**
 - What is impedance?
 - Parasitics
 - Ideal, real and measured values
 - Component dependency factors


- **Measurement conditions that determine the measured impedance value**
- **Effects depend on component materials and manufacturing process**
- **Four major factors:**
 - Test signal frequency
 - Test signal level
 - DC voltage and current bias
 - Environment

X versus Test Signal Frequency

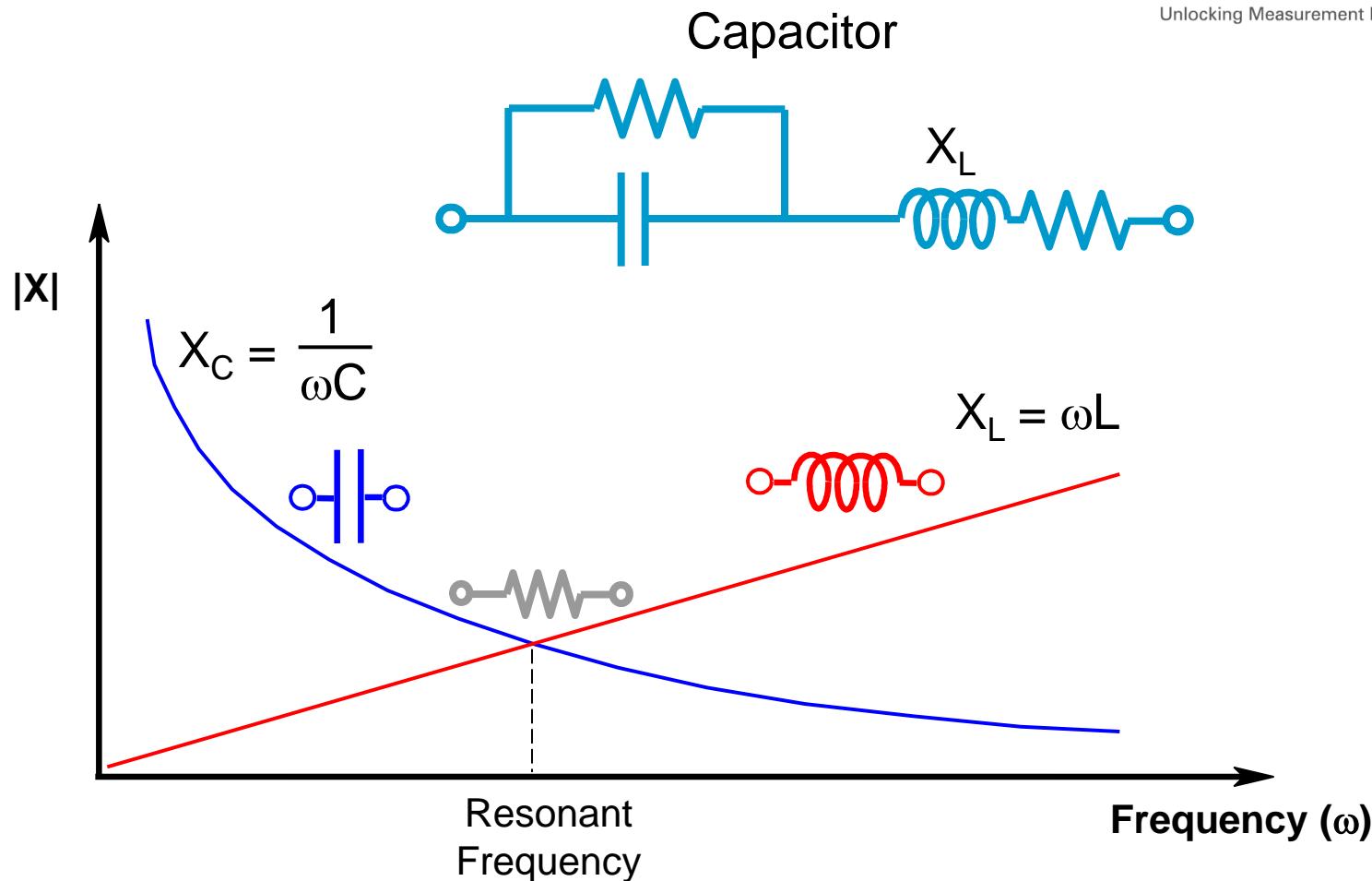


Example: Capacitor Resonance


Impedance versus Frequency

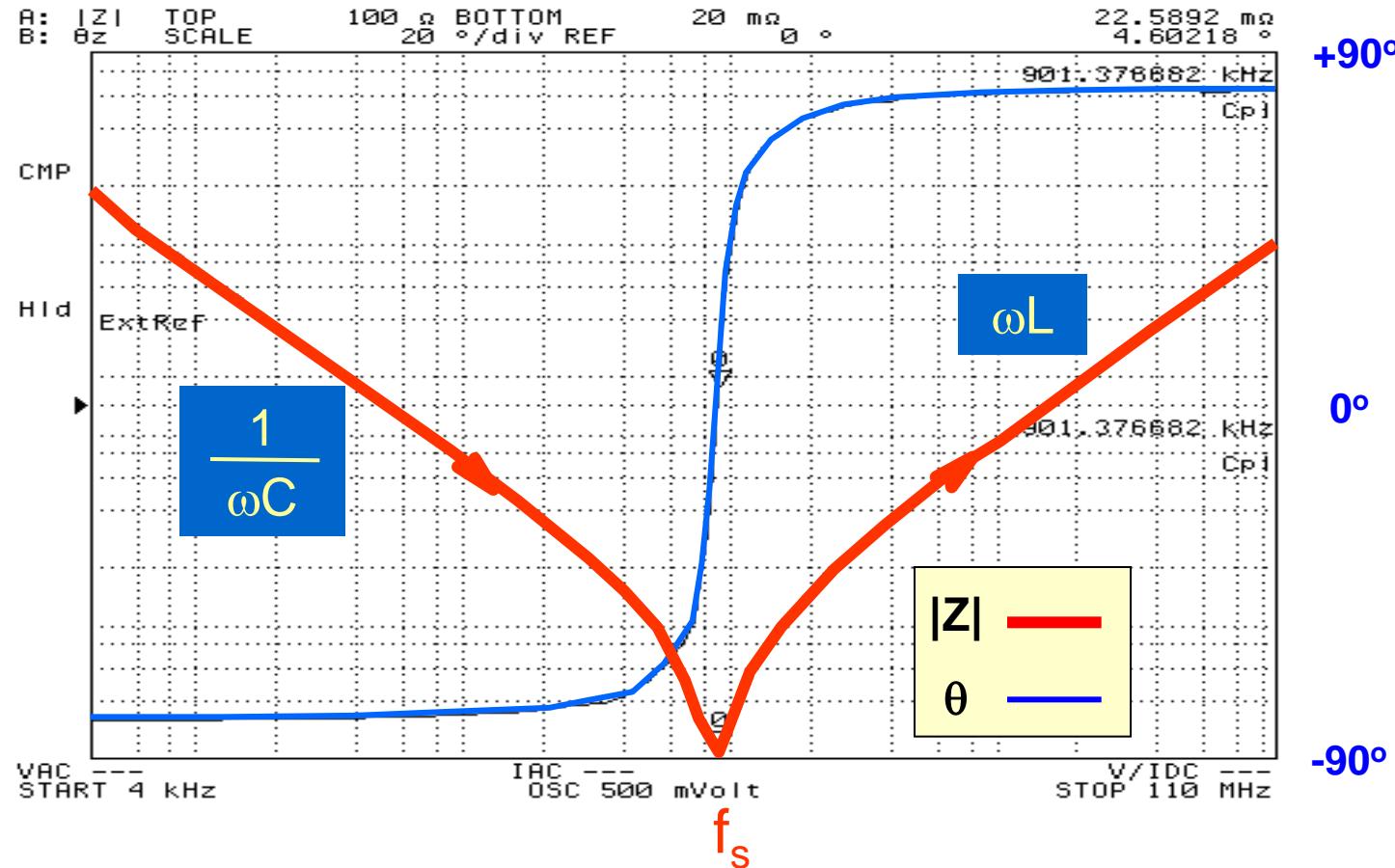

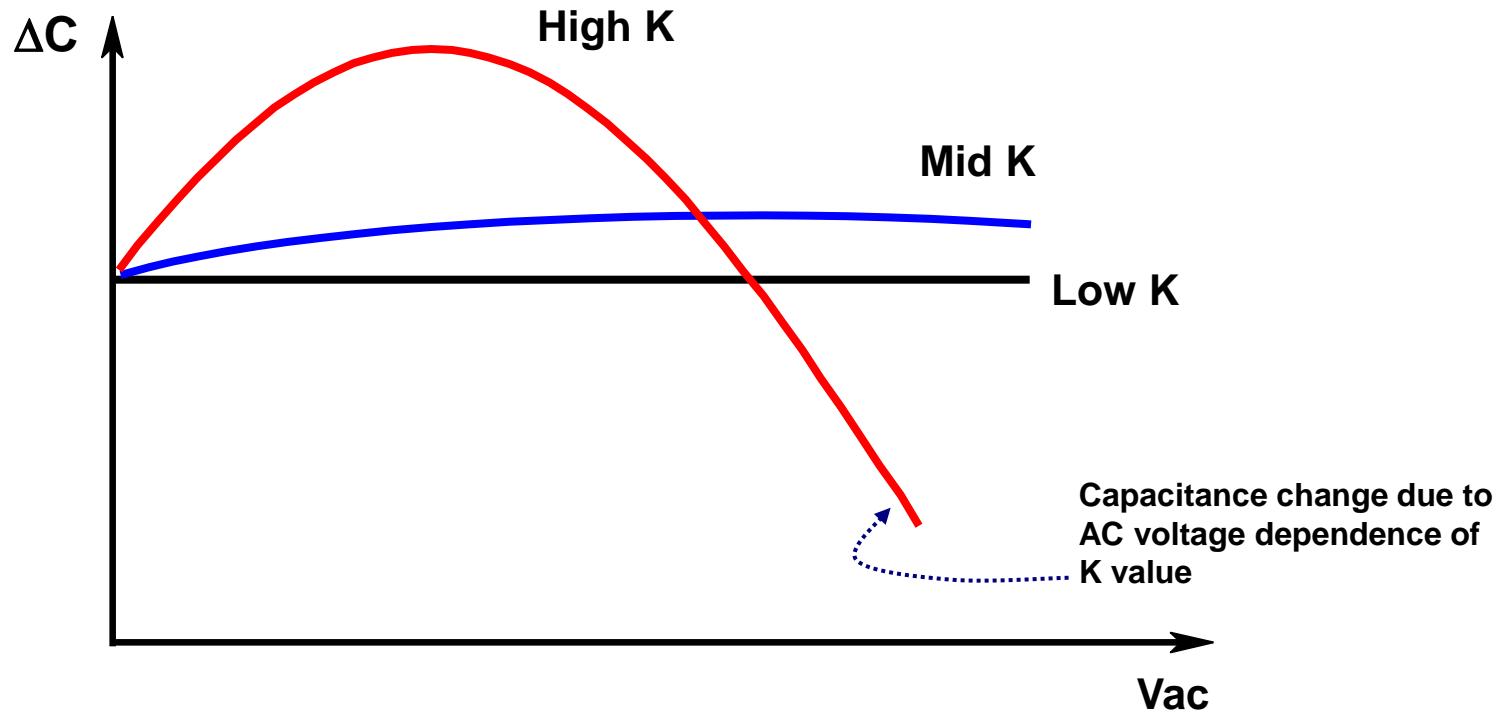
AC voltage dependency of ceramic SMD capacitors for various values of dielectric constant (K)



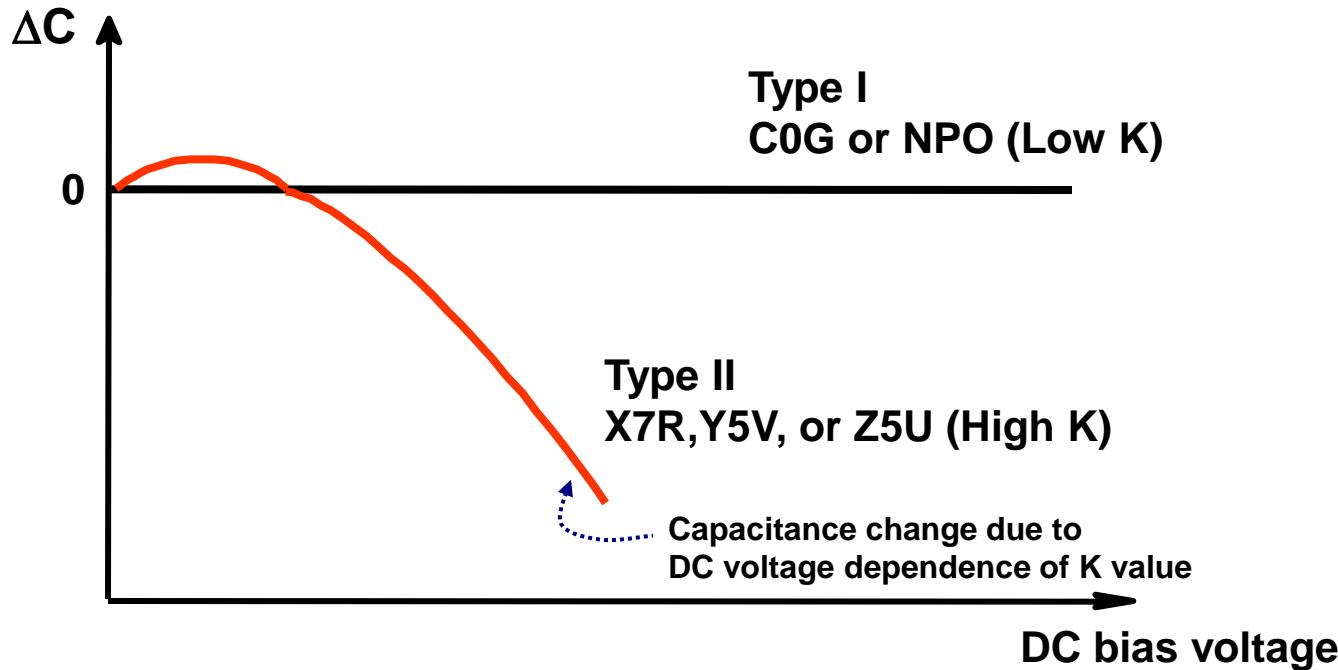
DC bias voltage dependency of type I and II SMD capacitors



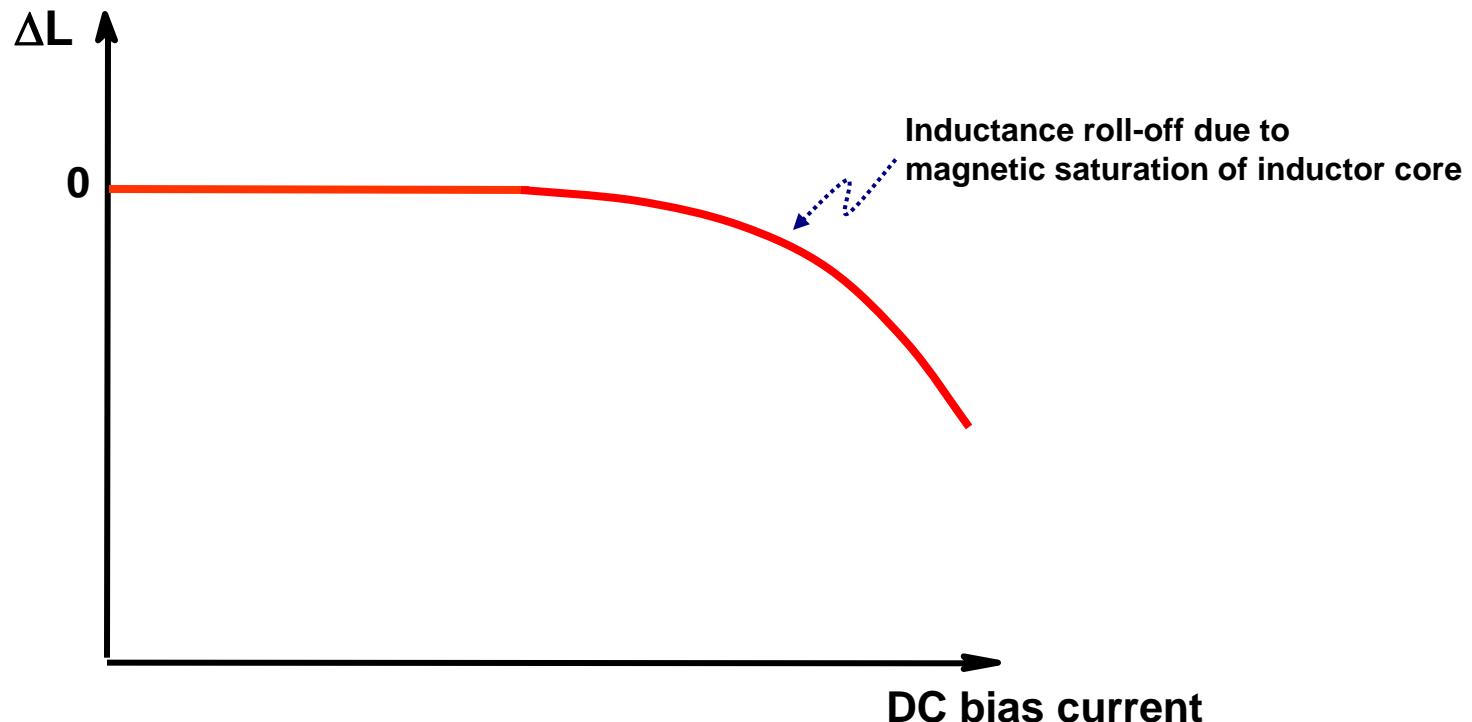DC bias current dependency of cored inductors



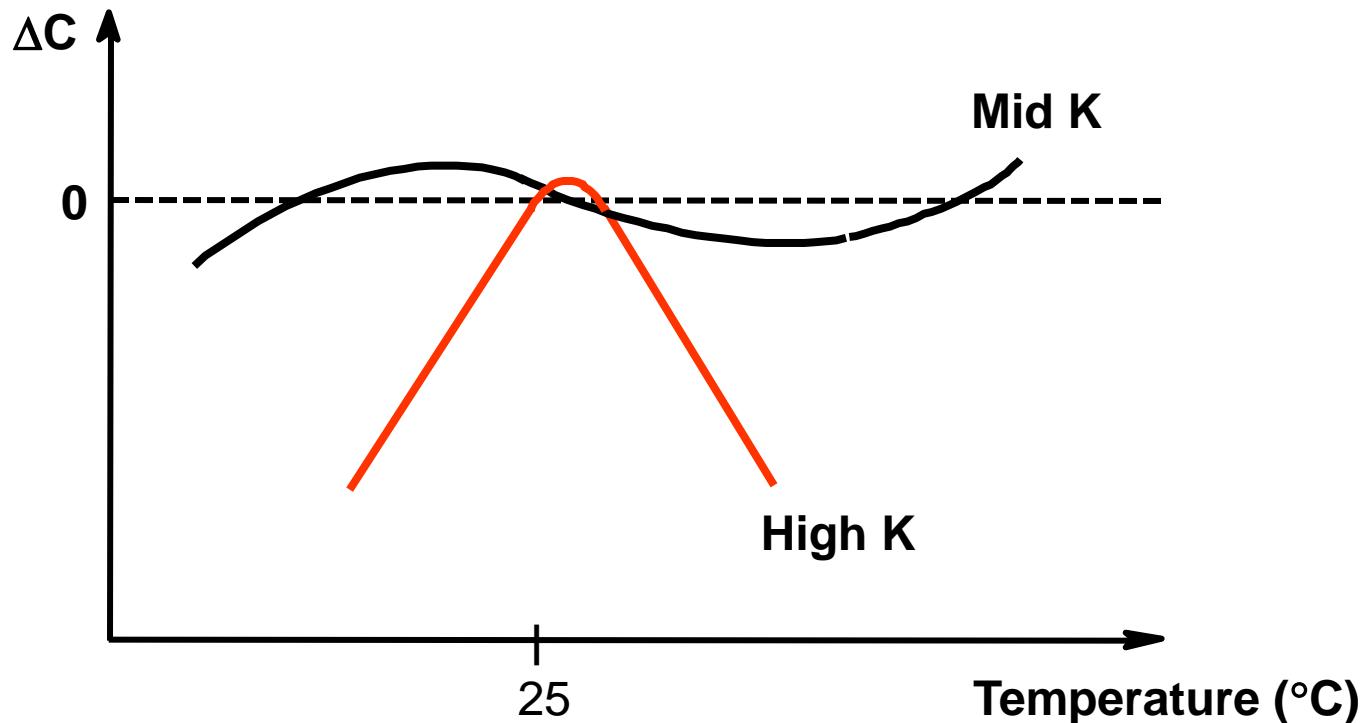Temperature dependency of ceramic capacitors for different K values



Agenda



Unlocking Measurement Insights for 75 Years

- Introduction
- Impedance fundamentals
- **Measurement methods**
 - Popular methods
 - Instrument functions

Popular Measurement Methods



Unlocking Measurement Insights for 75 Years

- Auto-balancing bridge
- RF I-V
- Network analysis (reflection coefficient)
- Less popular methods
 - Bridge
 - Resonant (Q meter)
 - I-V (probe)

- Method and instrument selection criteria
- Theory of operation
- Advantages and disadvantages

Method and Instrument Selection Criteria



Unlocking Measurement Insights for 75 Years

- 1) Frequency
- 2) DUT impedance
- 3) Required measurement accuracy
- 4) Electrical test conditions
- 5) Measurement parameters
- 6) Physical characteristics of DUT

These determine the most suitable method

These determine the proper instrument and test fixture




Finding Impedance from Frequency




Unlocking Measurement Insights for 75 Years

Reactance Chart

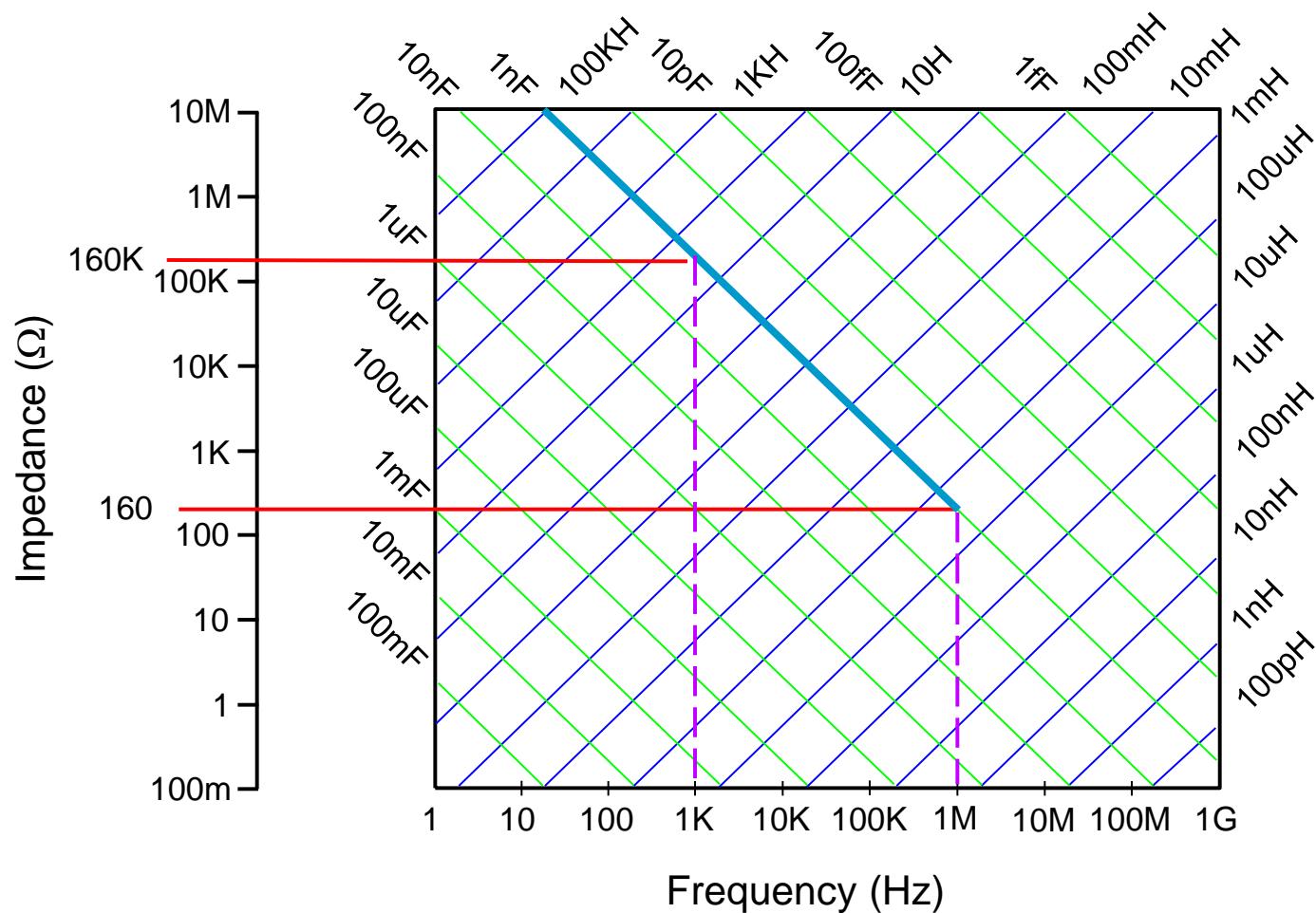

Frequency and DUT Impedance

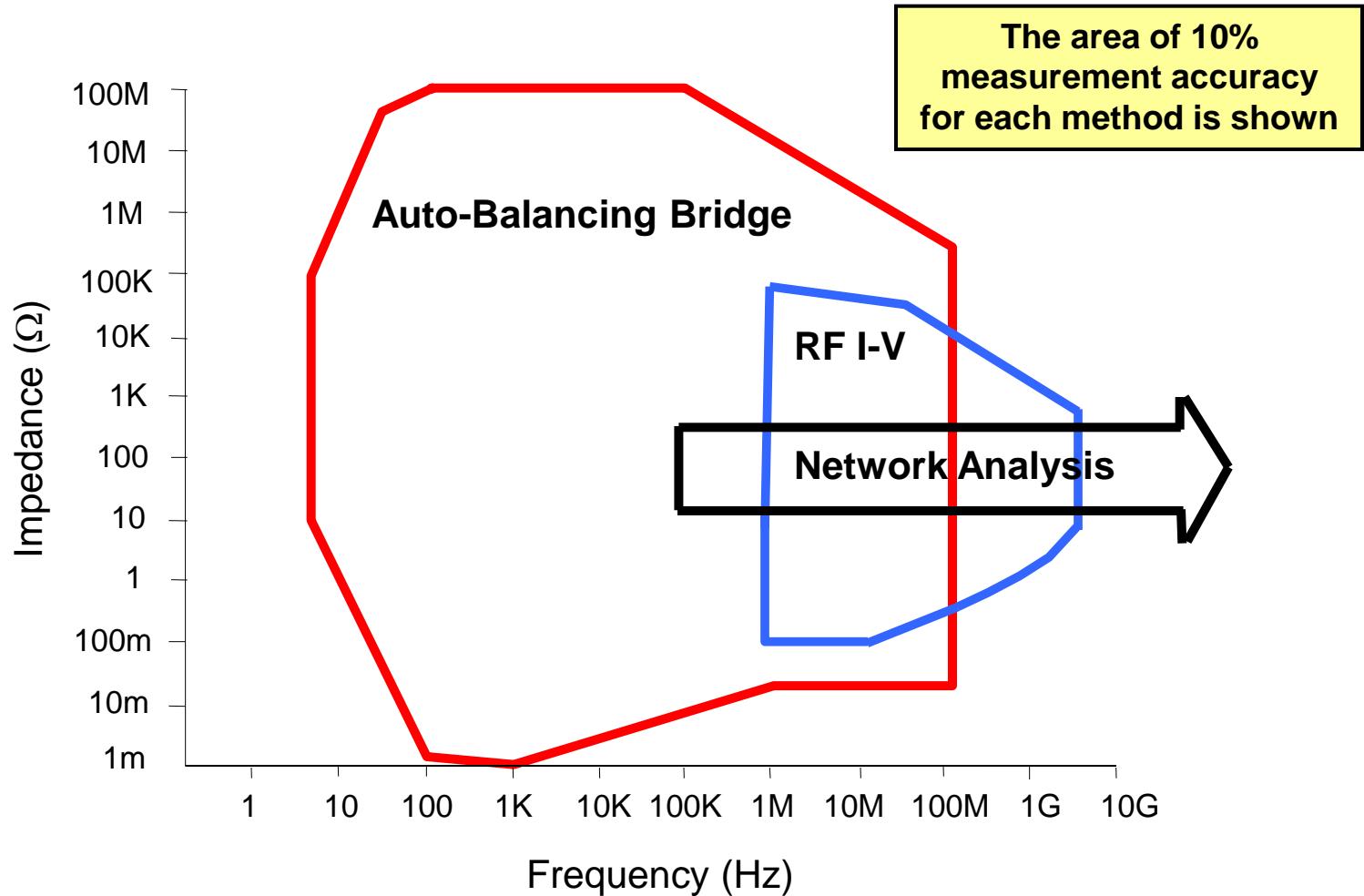

Measurement Method Considerations




Unlocking Measurement Insights for 75 Years

- Method and instrument selection criteria
- **Theory of operation**
- Advantages and disadvantages

Auto-Balancing Bridge Method (1 of 2)



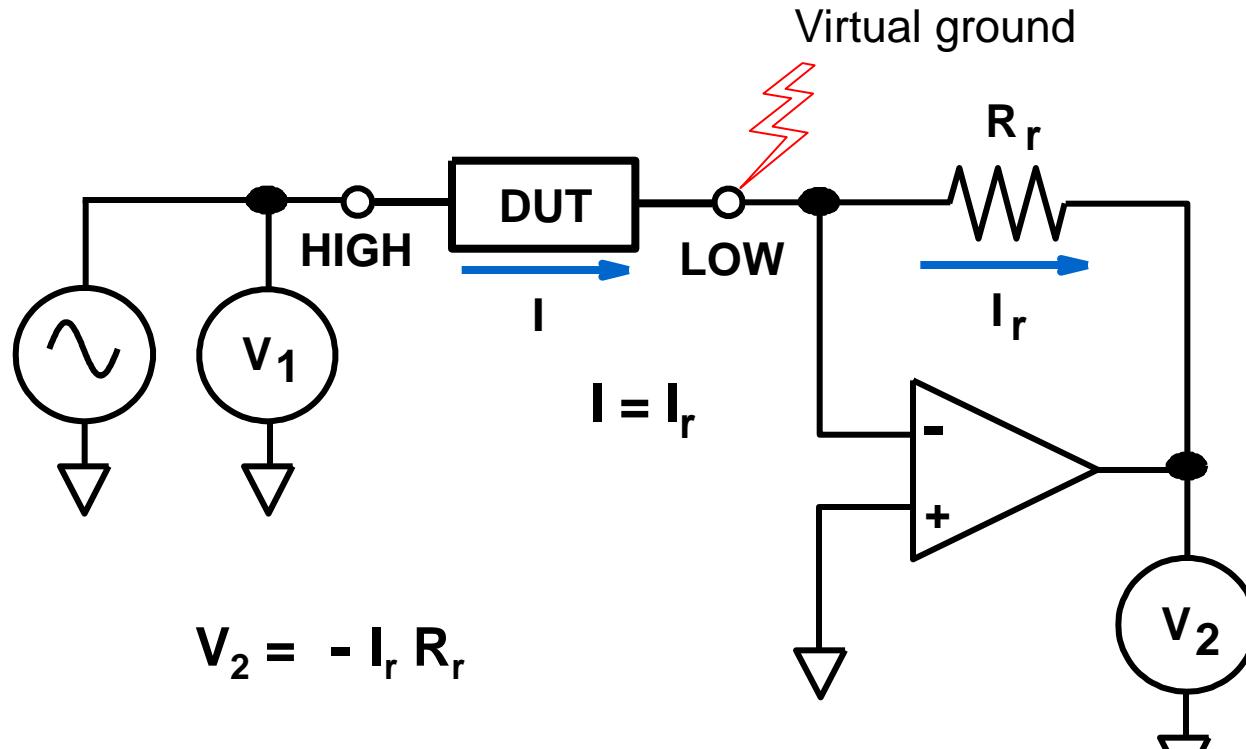
Unlocking Measurement Insights for 75 Years




$$V_2 = -I_r R_r$$

$$Z = \frac{V_1}{I_r} = \frac{-V_1 R_r}{V_2}$$

Auto-Balancing Bridge Method (2 of 2)

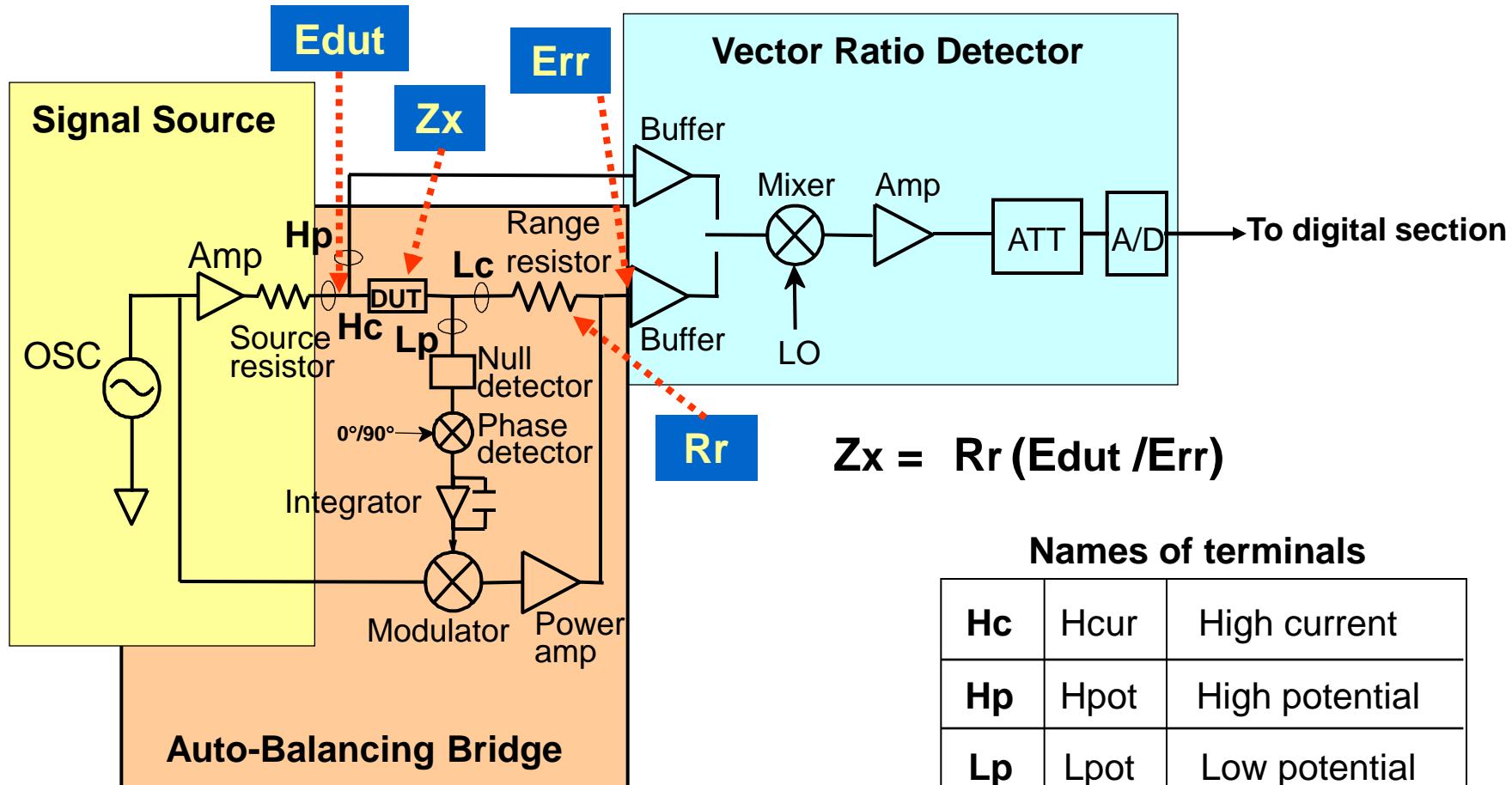


RF-IV Method (1 of 2)

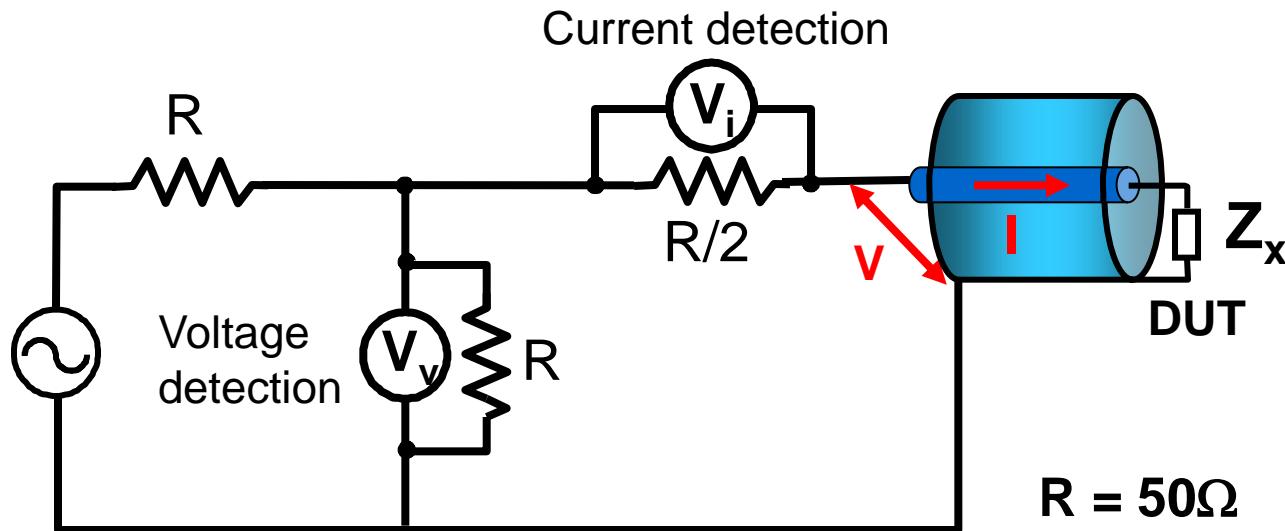

High-Impedance Test Head

$$Z_x = \frac{V}{I} = \frac{R}{2} \left(\frac{V_v}{V_i} - 1 \right)$$



RF I-V Method (2 of 2)

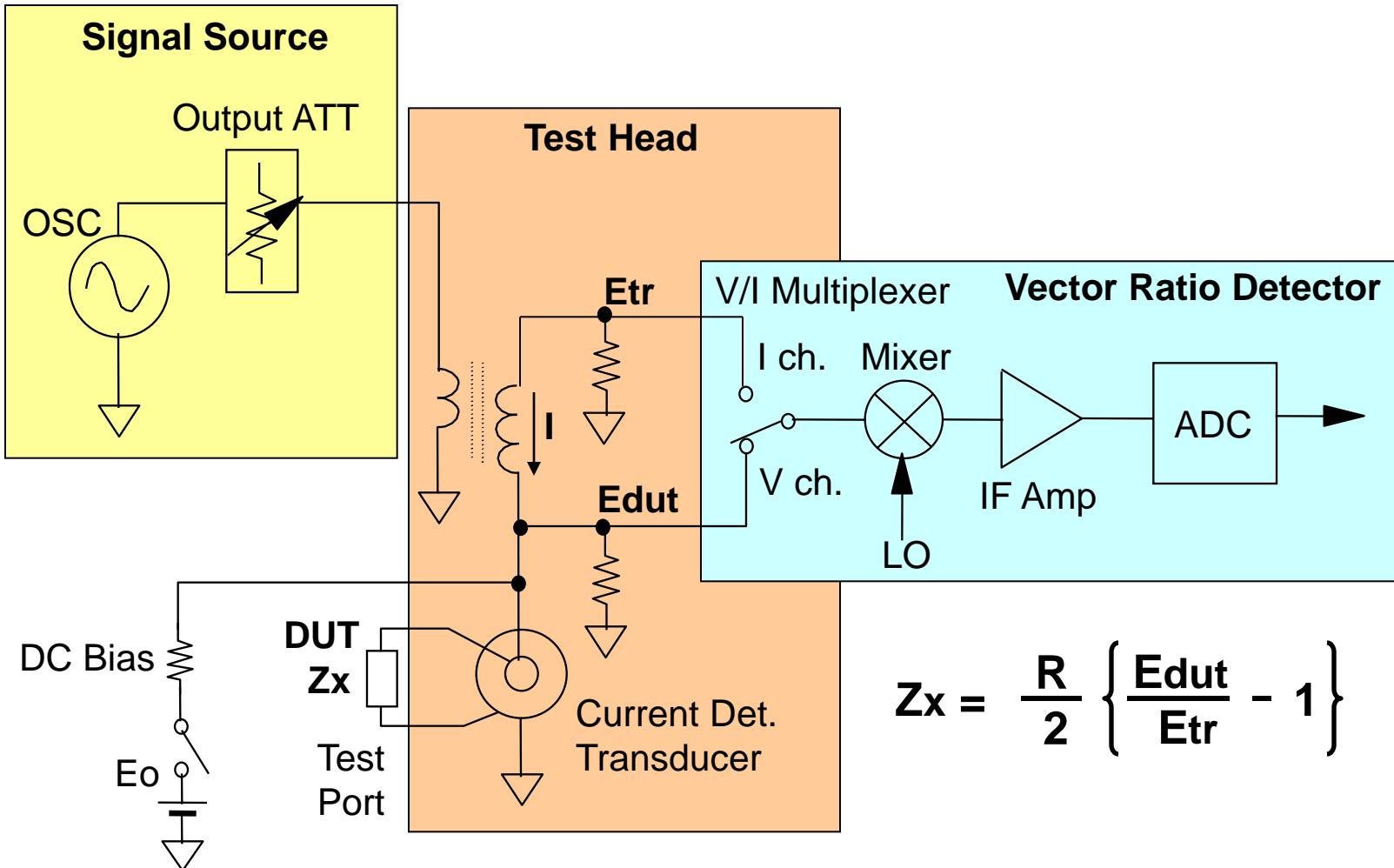

Network Analysis Method



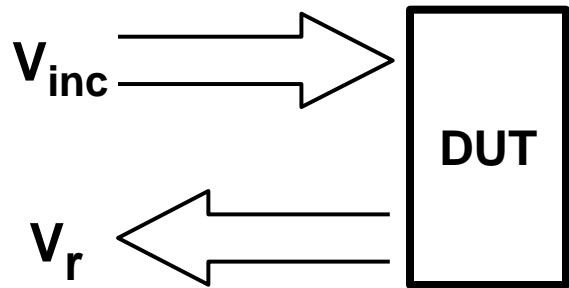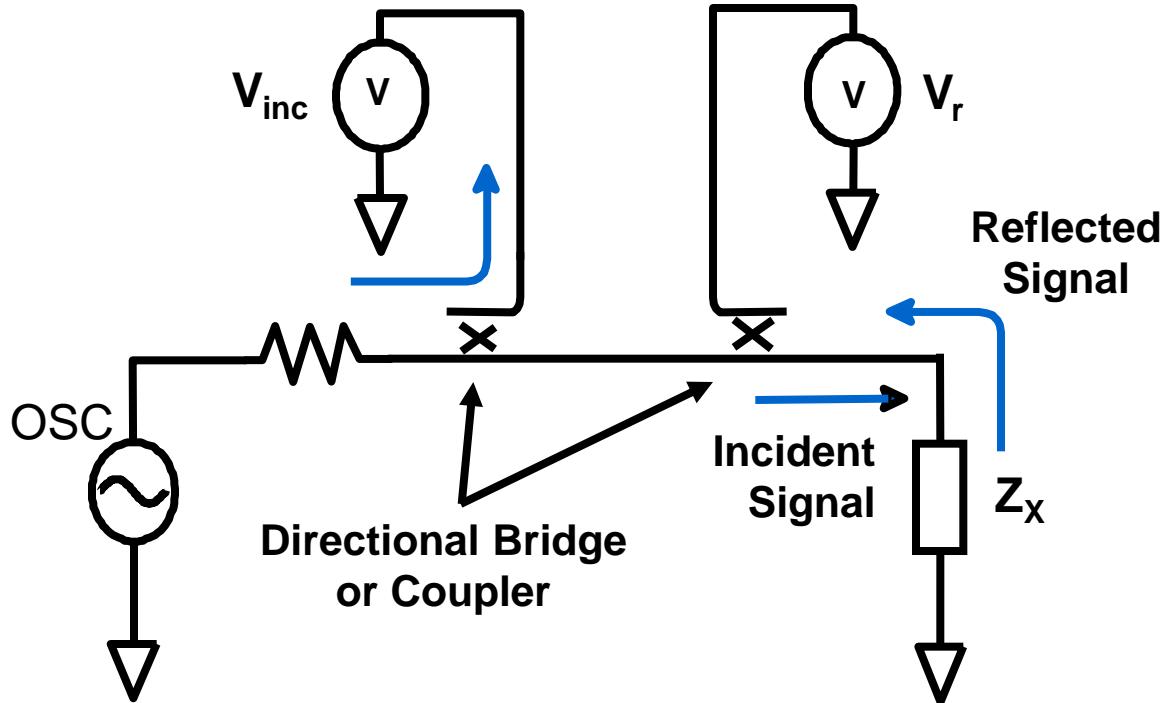Unlocking Measurement Insights for 75 Years



$$\Gamma = \frac{V_r}{V_{inc}} = \frac{Z_x - Z_0}{Z_x + Z_0}$$

Measurement Method Considerations



Unlocking Measurement Insights for 75 Years

- Method and instrument selection criteria
- Theory of operation
- **Advantages and disadvantages**


Auto-Balancing Bridge

- **Advantages**

- High accuracy over a wide impedance range
- Wide frequency coverage (LF to HF)
- Variety of fixture selections

- **Disadvantages**

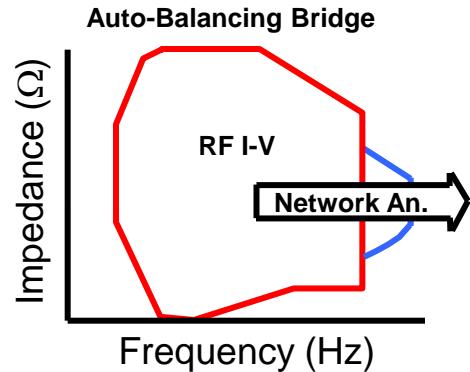- Higher frequency ranges (>110 MHz) not available




- **Advantages**

- Excellent HF and RF performance (≤ 3 GHz)
- High accuracy and wide impedance range
- Variety of fixture selections

- **Disadvantages**

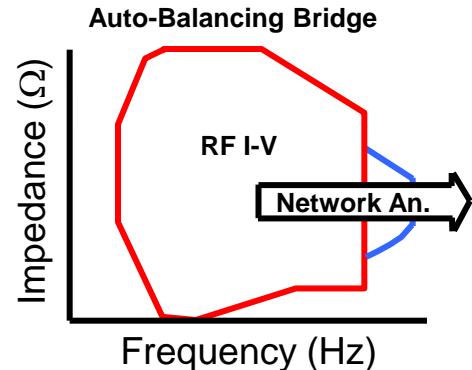- Lower frequency range is limited by the transformer used in the test head




Network Analysis

- **Advantages**


- Covers highest frequencies (≥ 3 GHz)
- High accuracy around the characteristic impedance of the analyzer (Z_0)
- Only method able to measure multiport devices

- **Disadvantages**

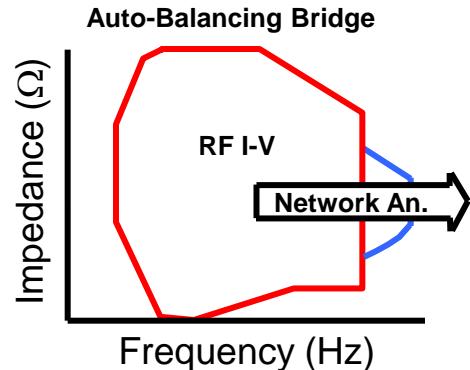- Recalibration required when measurement frequency is changed
- Narrow impedance measurement range



Summary of Measurement Methods

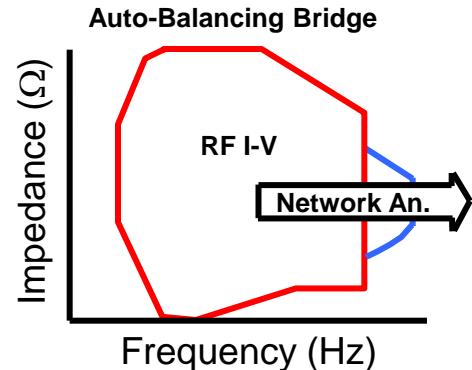

Method	Frequency Range	Impedance Range	Terminal Connections	# of Ports
Auto-Balancing Bridge	$20 \leq f \leq 110$ MHz	$1 \text{ m}\Omega \leq Z \leq 100 \text{ M}\Omega$ (10% acc)	4-terminal pair, BNC	1
RF I-V	$1 \text{ MHz} \leq f \leq 3 \text{ GHz}$	$0.2 \leq Z \leq 20 \text{ k}\Omega$ (10% acc)	7 mm	1
Network Analysis	$f \geq 300$ kHz	$Z \approx Z_0$	7 mm, N-type	$N \geq 1$

Measurement Methods and Agilent Products



Unlocking Measurement Insights for 75 Years


Measurement Method	Agilent Product	Frequency Range
Auto-Balancing Bridge	4263B LCR Meter E4981A C Meter E4980A Precision LCR Meter 4285A Precision LCR Meter 4294A Precision Impedance Analyzer	100 Hz to 100 kHz spot 120 Hz, 1kHz, 1 MHz spot 20 Hz to 2 MHz 75 kHz to 30 MHz 40 Hz to 110 MHz
RF I-V	E4982A RF LCR Meter E4991A Impedance/Material Analyzer	1 MHz to 3 GHz 1 MHz to 3 GHz
Network Analysis	ENA Series Vector Network Analyzers PNA Series Microwave Vector Network Analyzers	5 Hz to 20 GHz 300 kHz to 1.1 THz

Agenda




Unlocking Measurement Insights for 75 Years

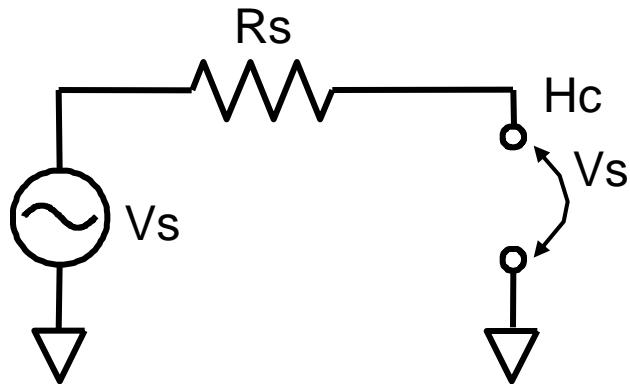- Introduction
- Impedance fundamentals
- **Measurement methods**
 - Popular methods
 - Instrument functions




(a) High terminal is open

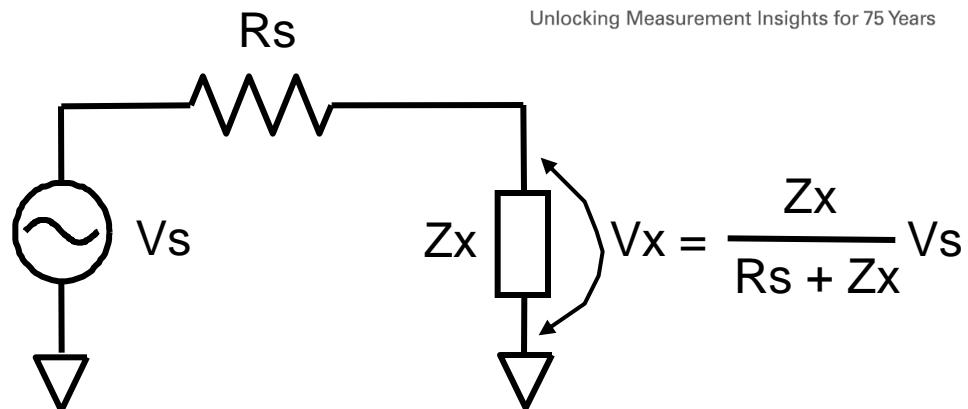


(b) DUT is connected to the high terminal

V_s = OSC level


R_s = source resistor

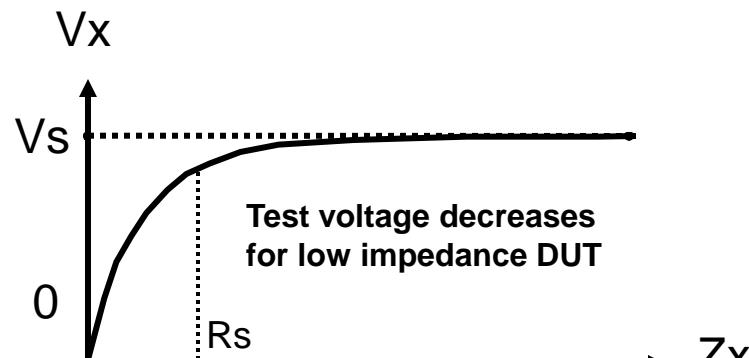

(c) V_x versus Z_x

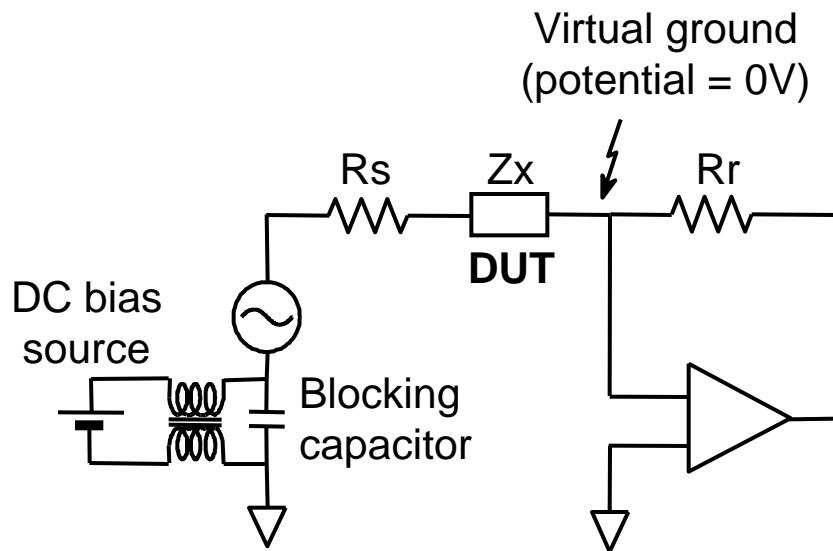

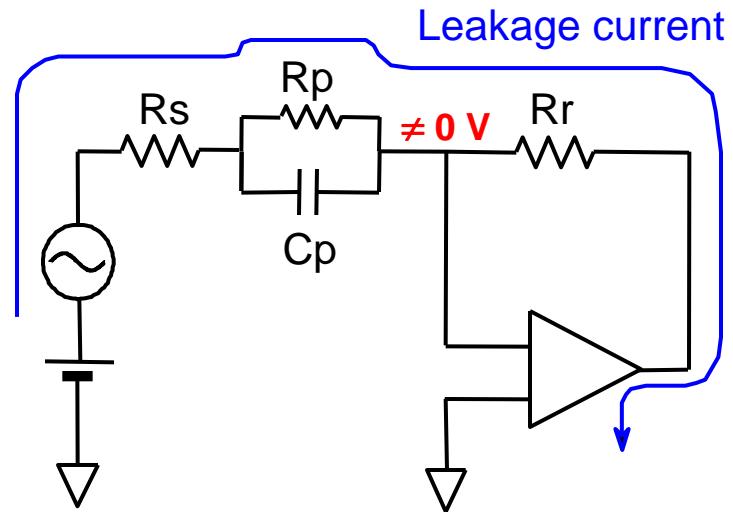
(a) Simplified diagram of measurement with DC bias




(b) When the DUT's R_p is low, leakage current decreases the DC voltage applied to the DUT

The 4294A and some impedance analyzers can automatically regulate DC bias voltage or current across DUT according to the monitored bias levels.

Ranging

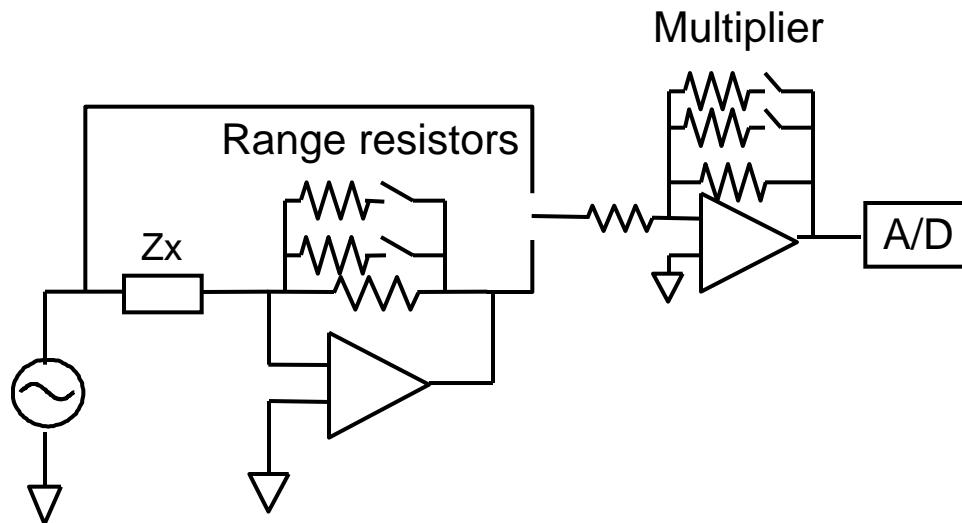

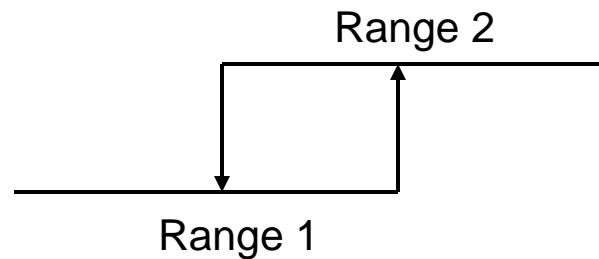(a) Ranging is done by changing the range resistor and multiplier of the vector ratio detector.



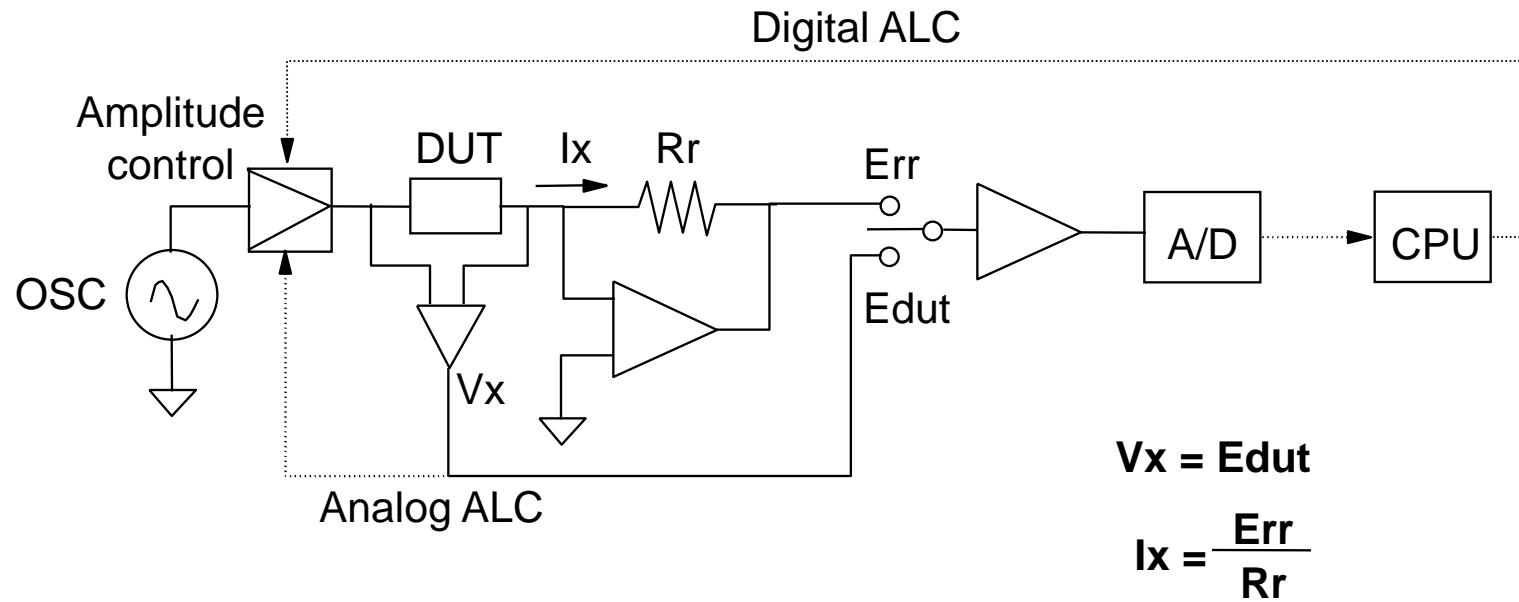
(b) Hysteresis in the range boundary prevents frequent range changes caused by noise



Level Monitor




Unlocking Measurement Insights for 75 Years



Measurement Time and Averaging



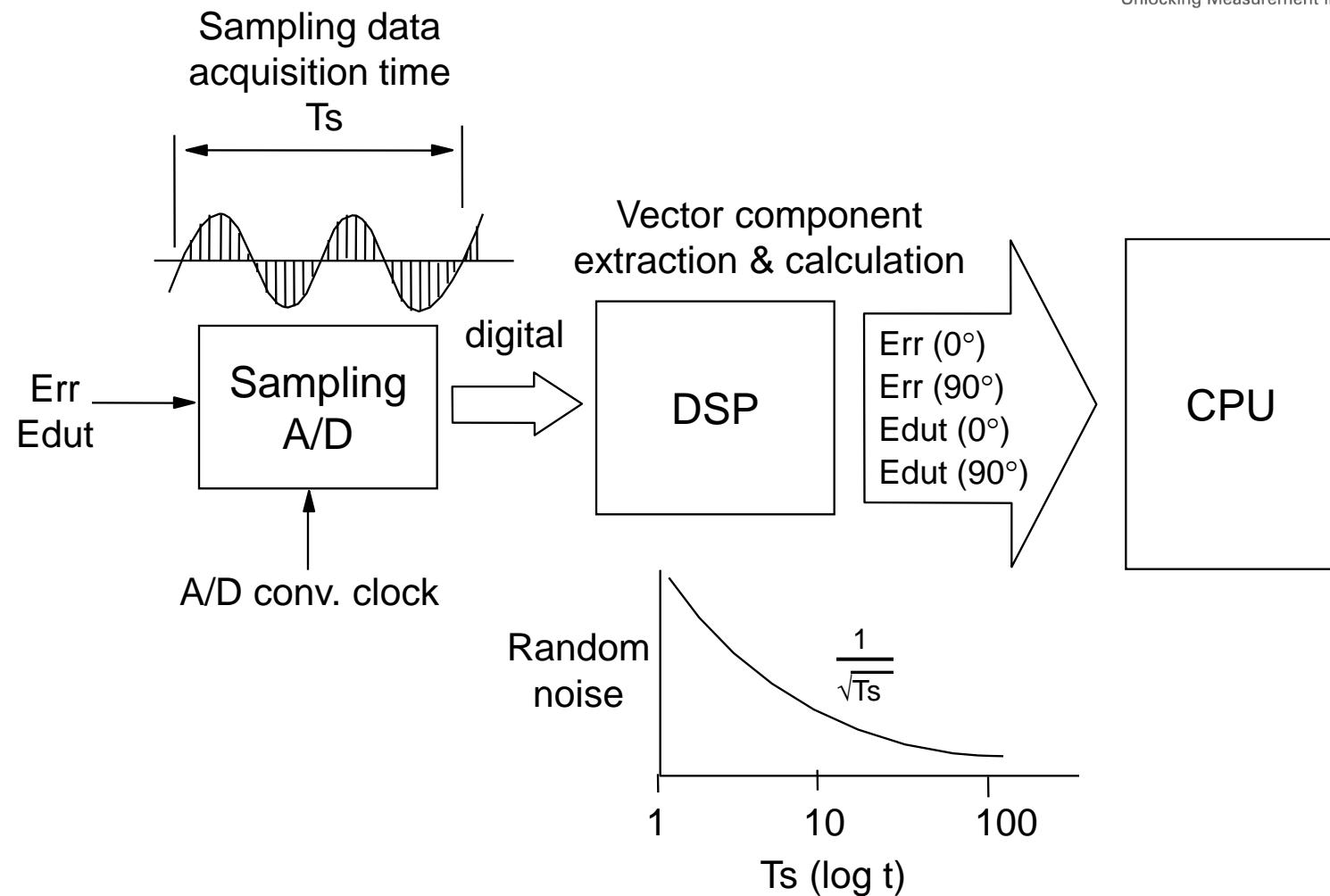Unlocking Measurement Insights for 75 Years



Agenda



Unlocking Measurement Insights for 75 Years

- Introduction
- Impedance fundamentals
- Measurement methods
- **Fixturing and cabling**
- Calibration and compensation
- Solution selection process

LF impedance measurement

- Terminal configuration
- Guarding

RF impedance measurement


- Terminal configuration in the RF range
- Test port extension in the RF range

Types of configuration

- Two-terminal (2T) configuration
- Three-terminal (3T) configuration
- Four-terminal (4T) configuration
- Five-terminal (5T) configuration
- Four-terminal pair (4TP) configuration


Terminal Configuration

Two-terminal (2T) method

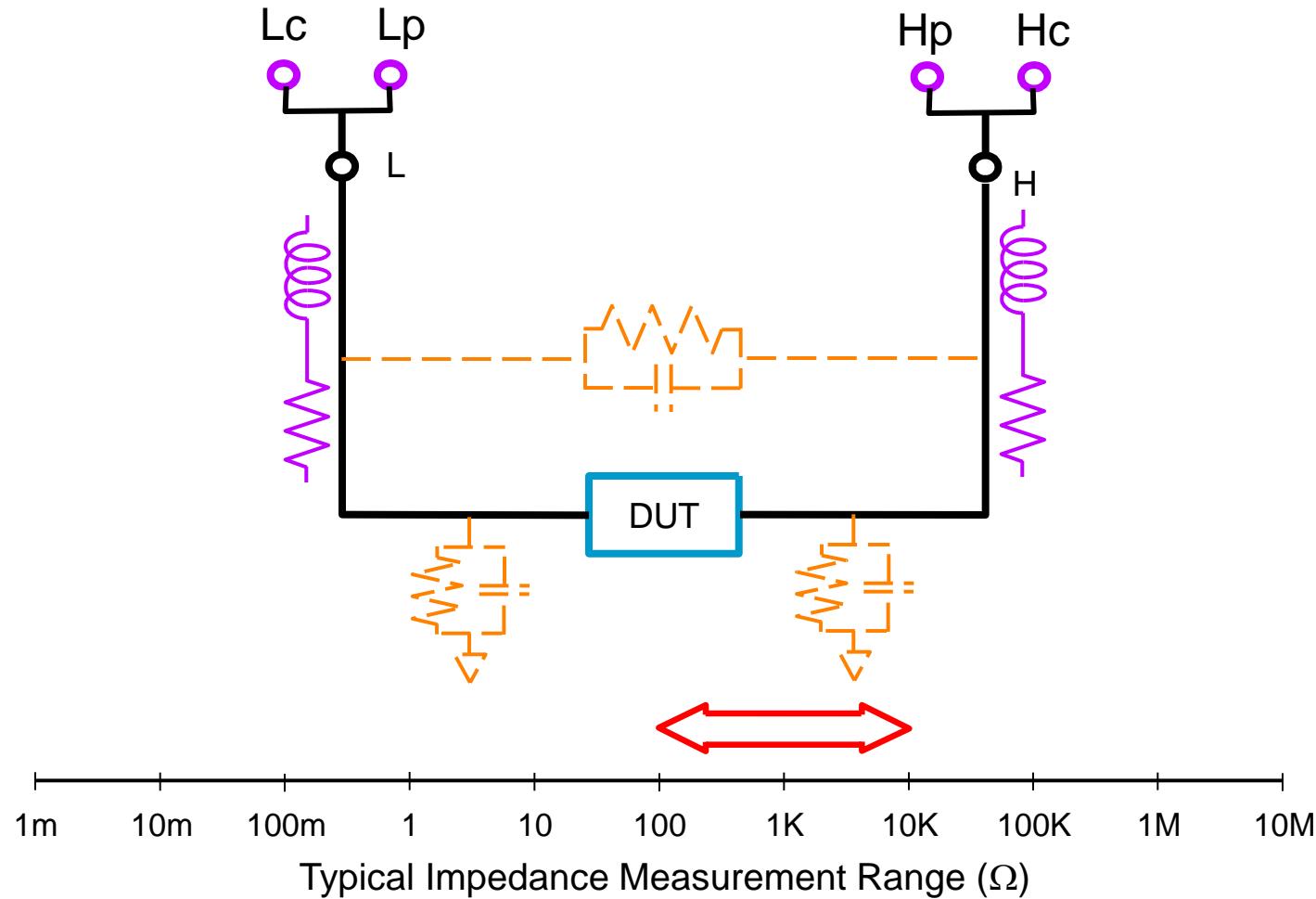

Terminal Configuration

Three-terminal (3T) method

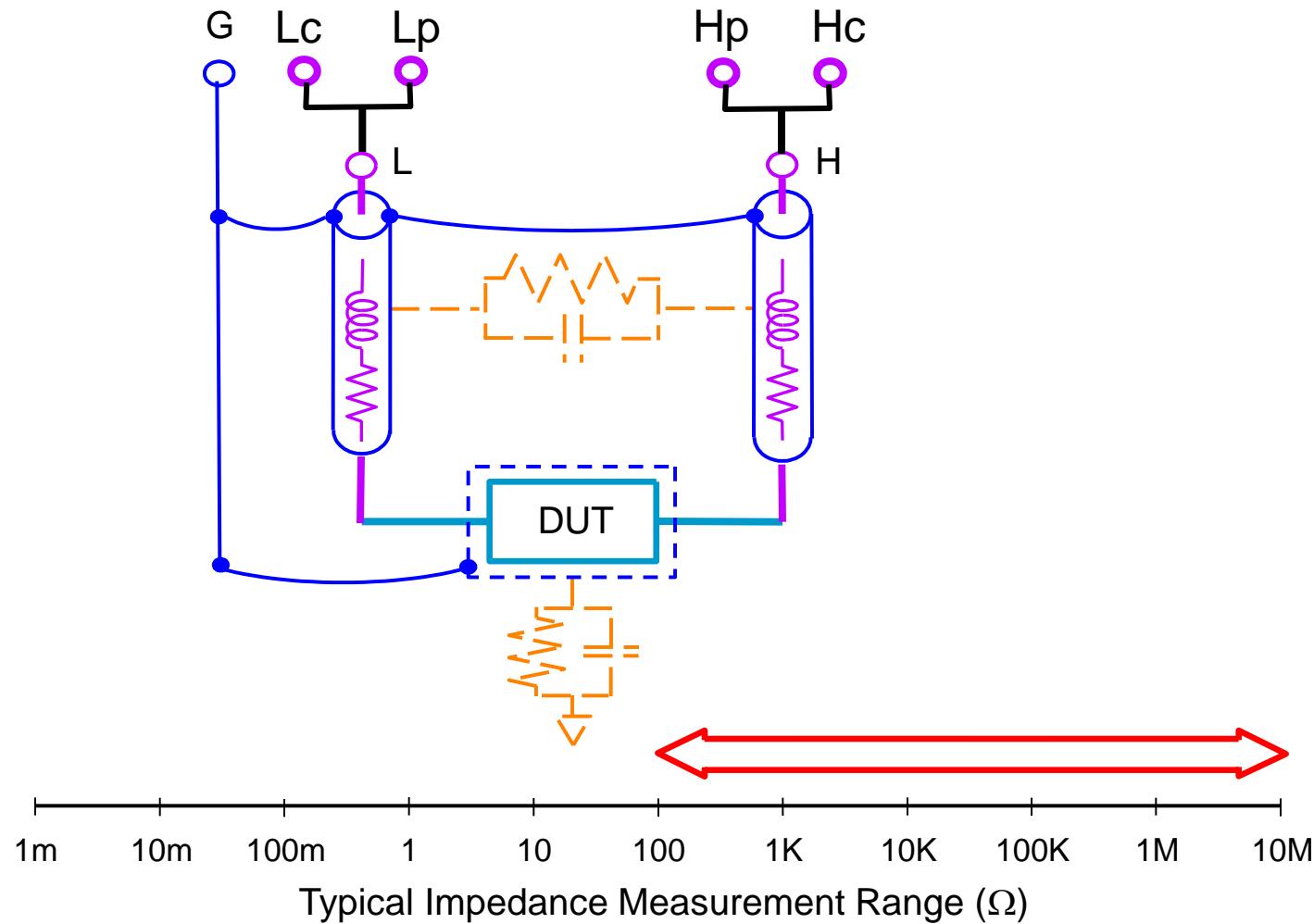


Terminal Configuration

Four-terminal (Kelvin, 4T) method




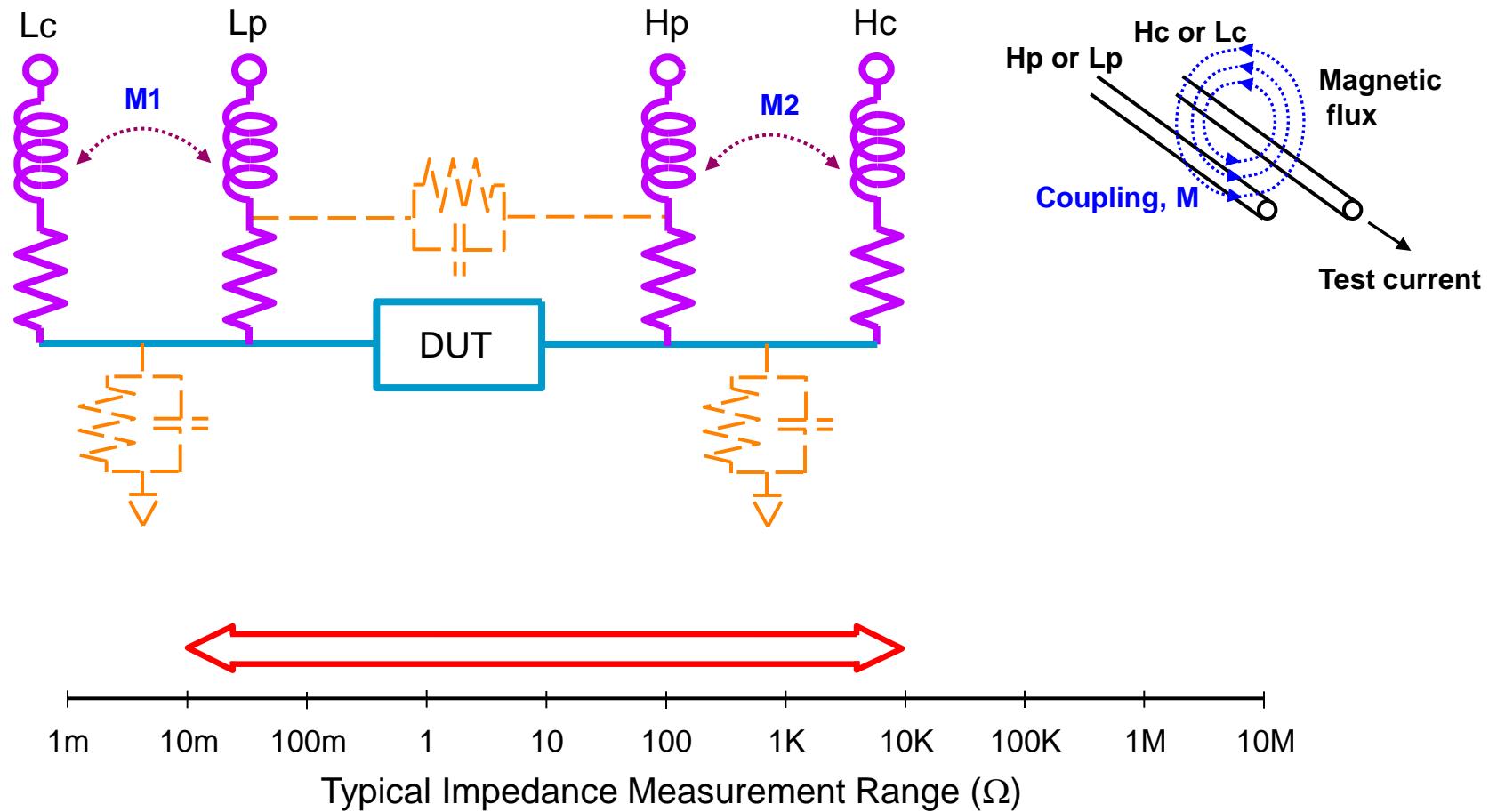Unlocking Measurement Insights for 75 Years



Terminal Configuration

Five-terminal (5T) method

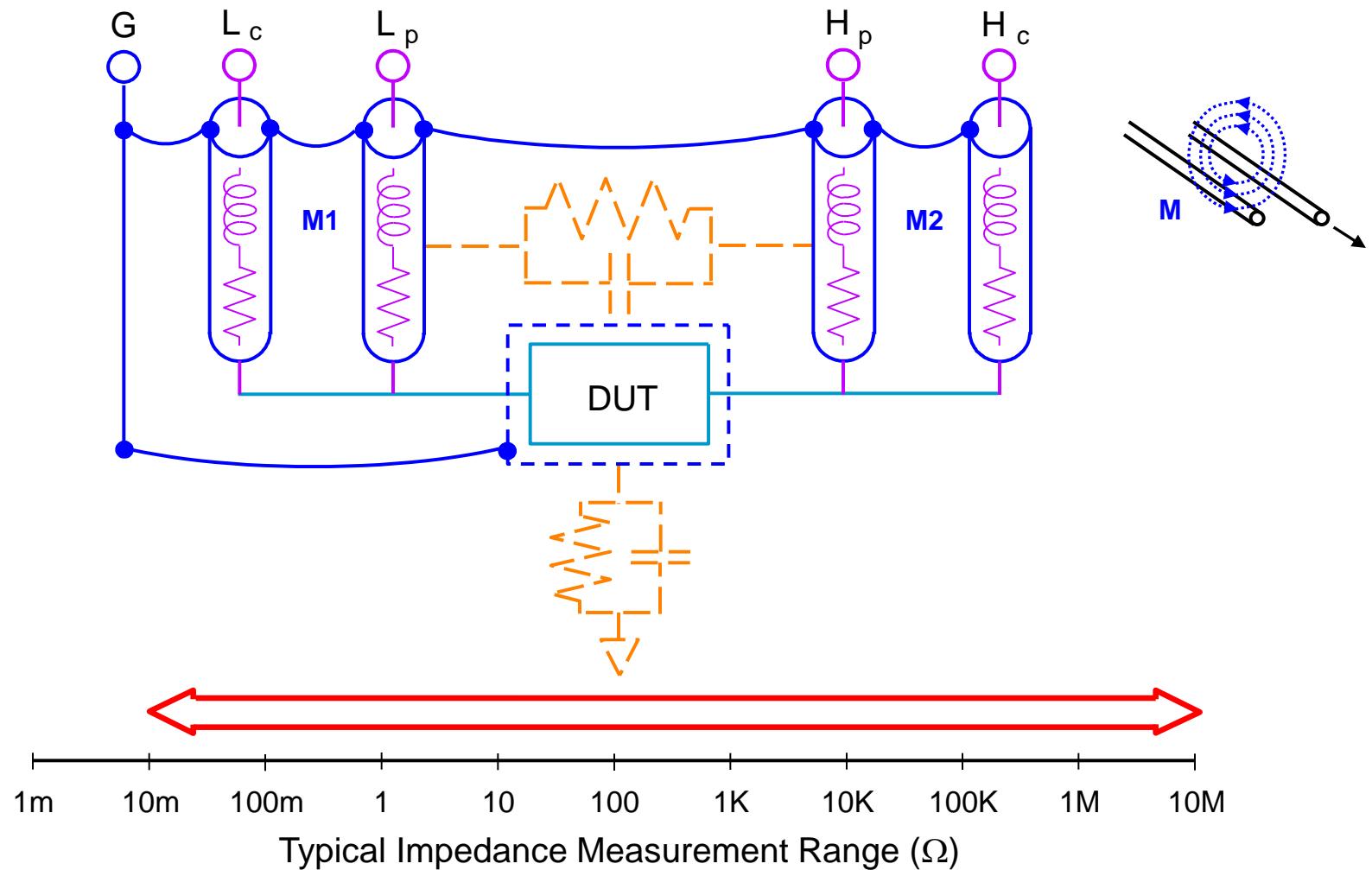


Terminal Configuration

Unlocking Measurement Insights for 75 Years


Mutual inductance error

For $m\Omega$ DUT

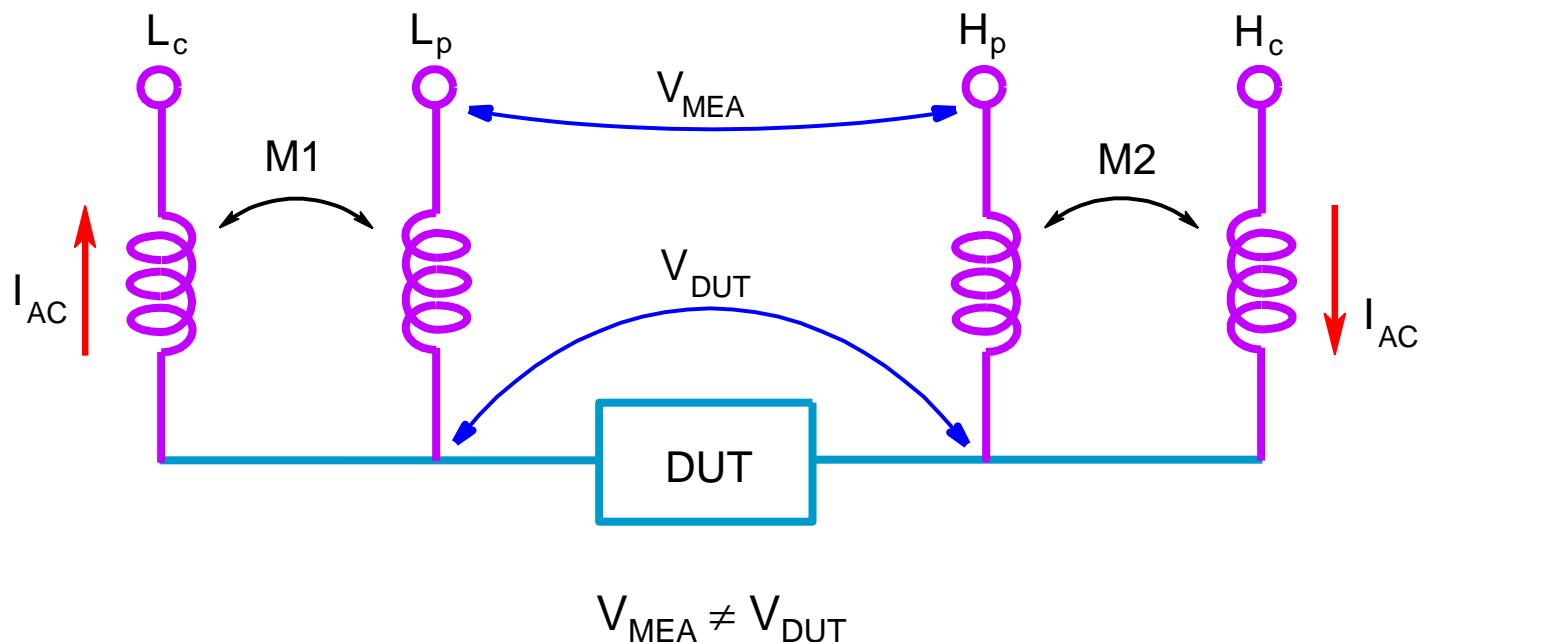


Terminal Configuration

Four-terminal pair (4TP) method

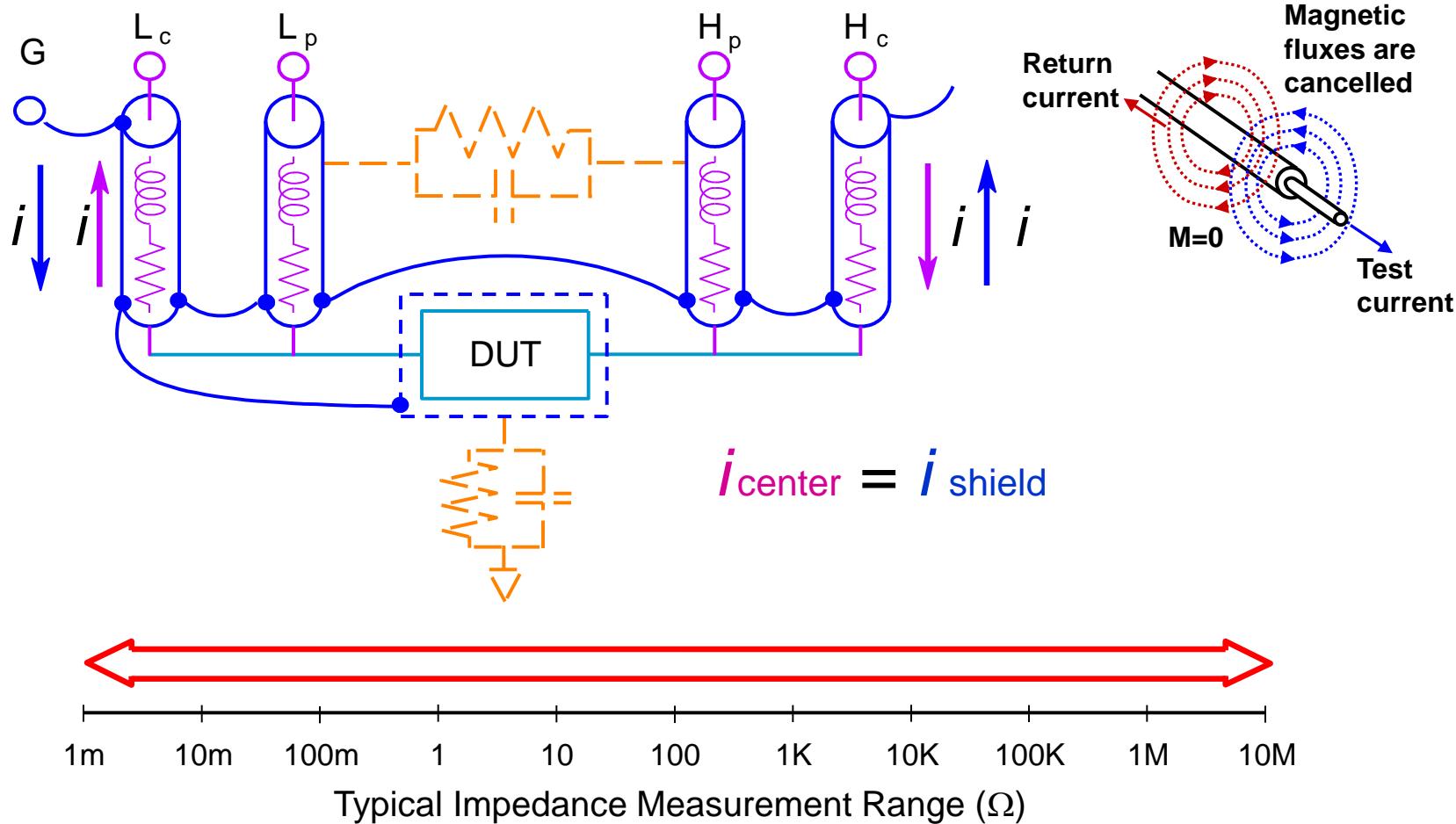

Terminal Configuration

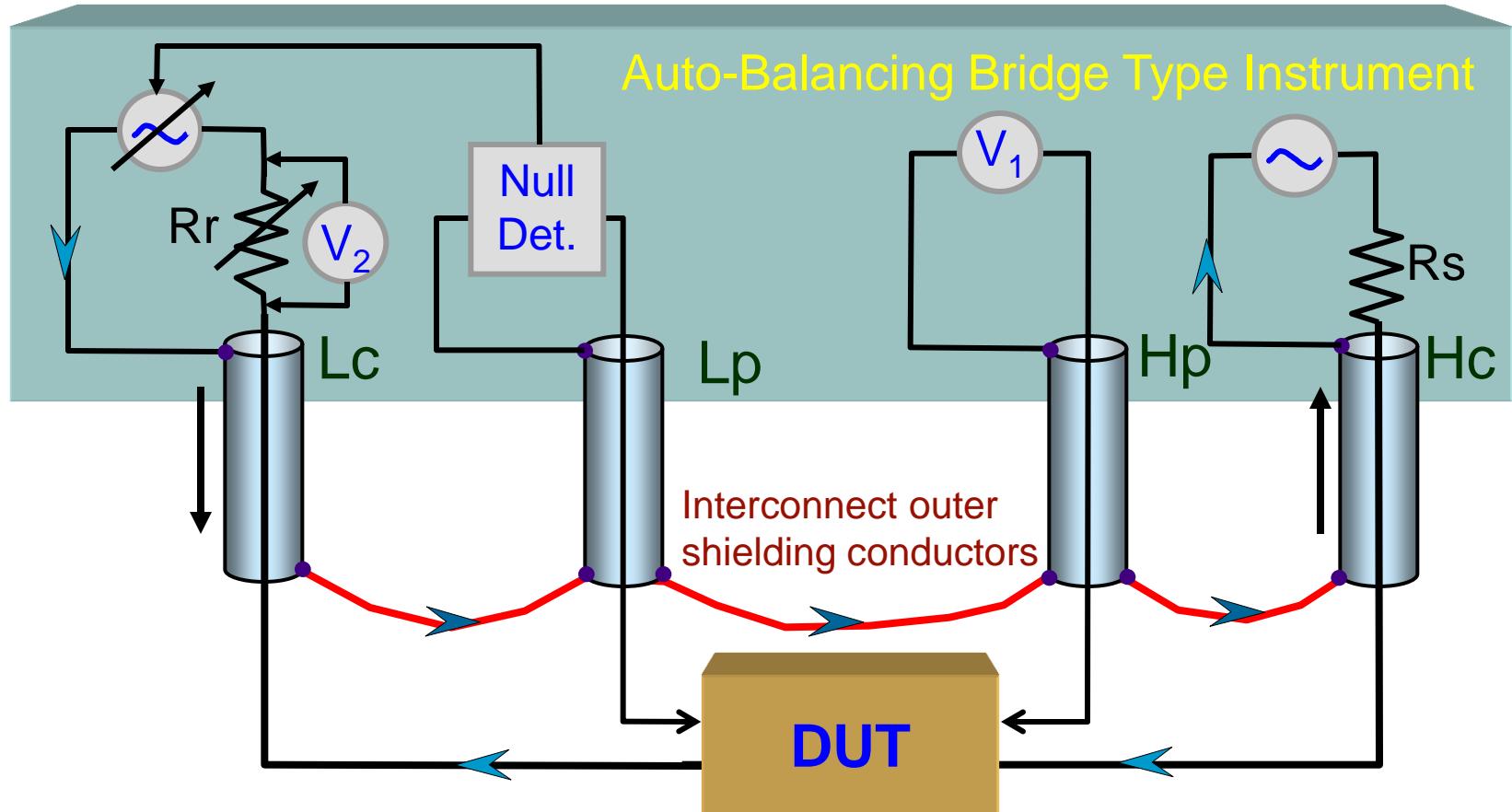Four-terminal pair (4TP) simplified schematic



LF impedance measurement


- Terminal configuration
- **Guarding**

RF impedance measurement

- Terminal configuration in the RF range
- Test port extension in the RF range

Stray capacitance and leakage current


Auto-Balancing Bridge Type Instrument

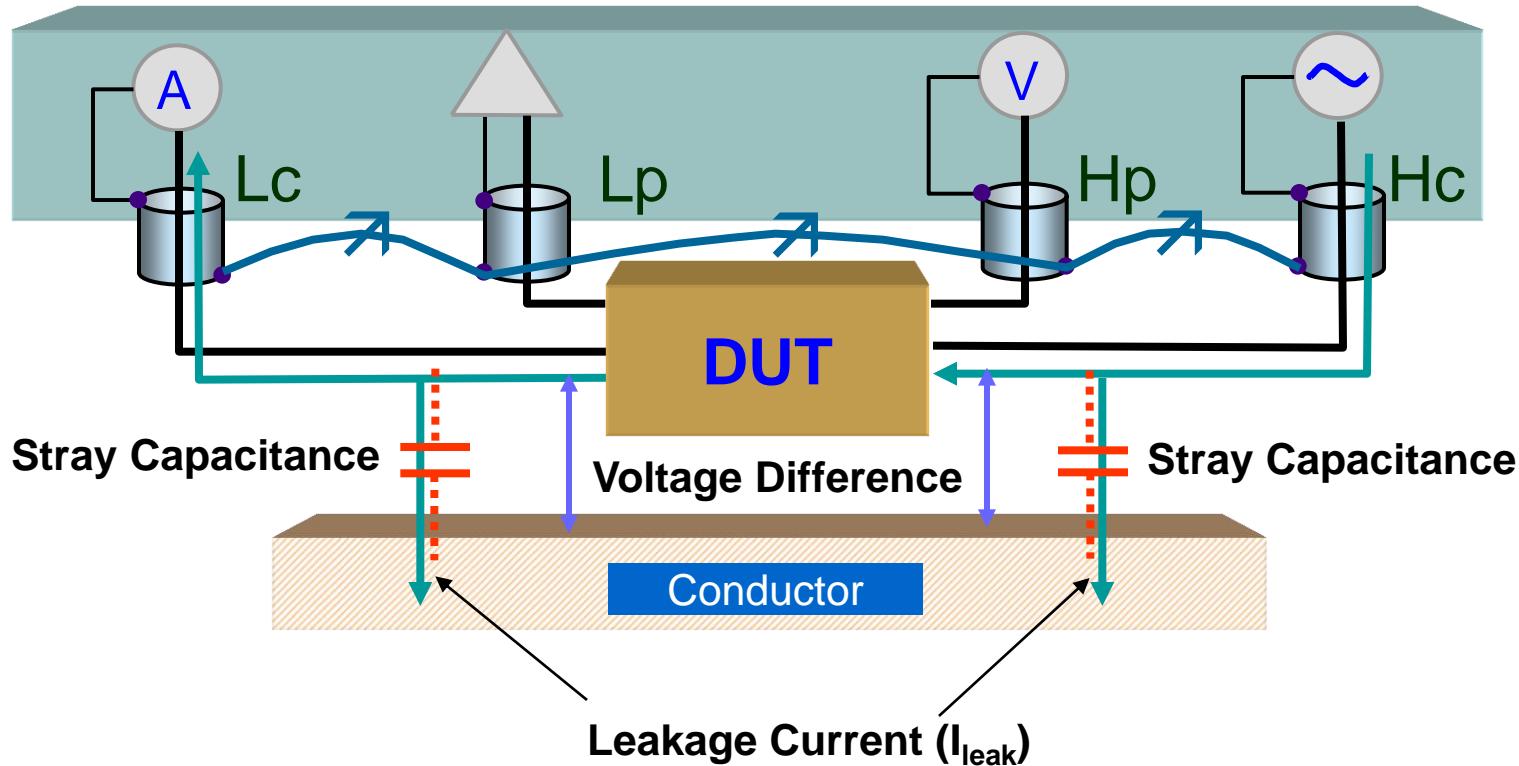

$$I_{dut} = I_{meas} + I_{leak}$$

Guard Mechanism and Solution


Auto-Balancing Bridge Type Instrument

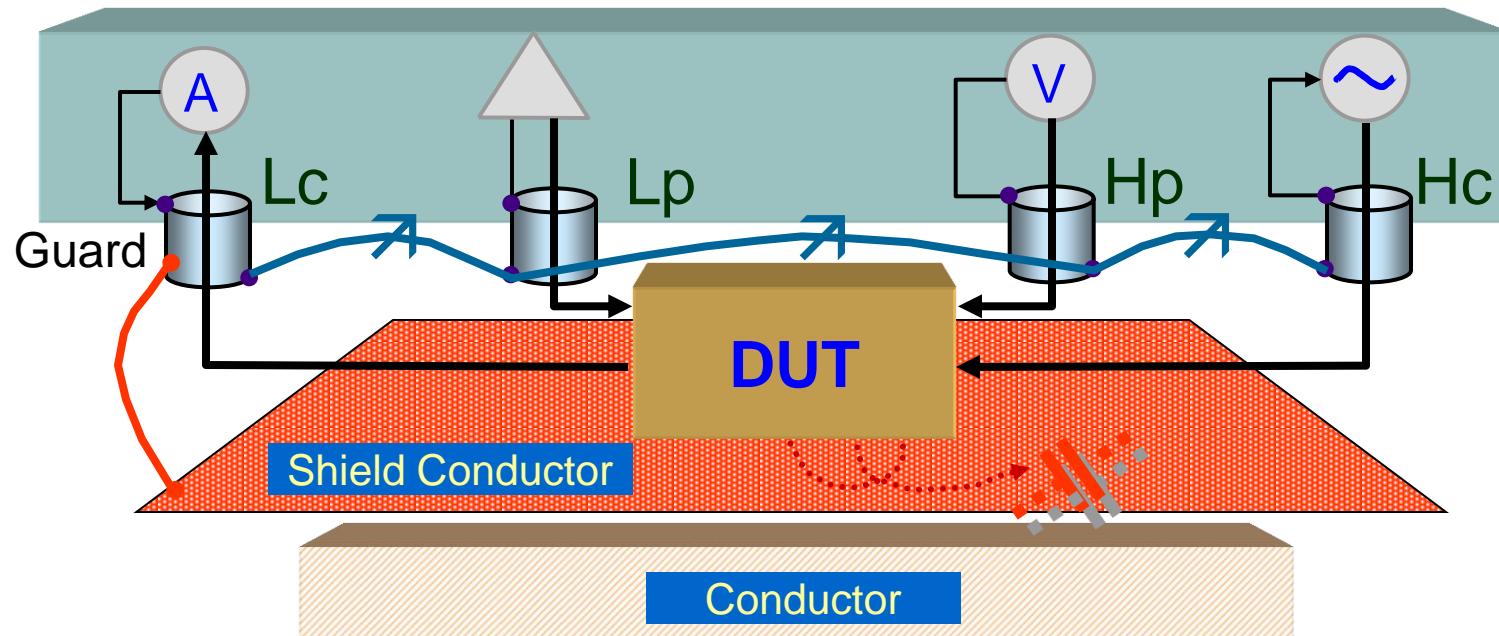


Guarding (3 of 3)

Key Points to Consider

(a) Minimize impedance of guard line.

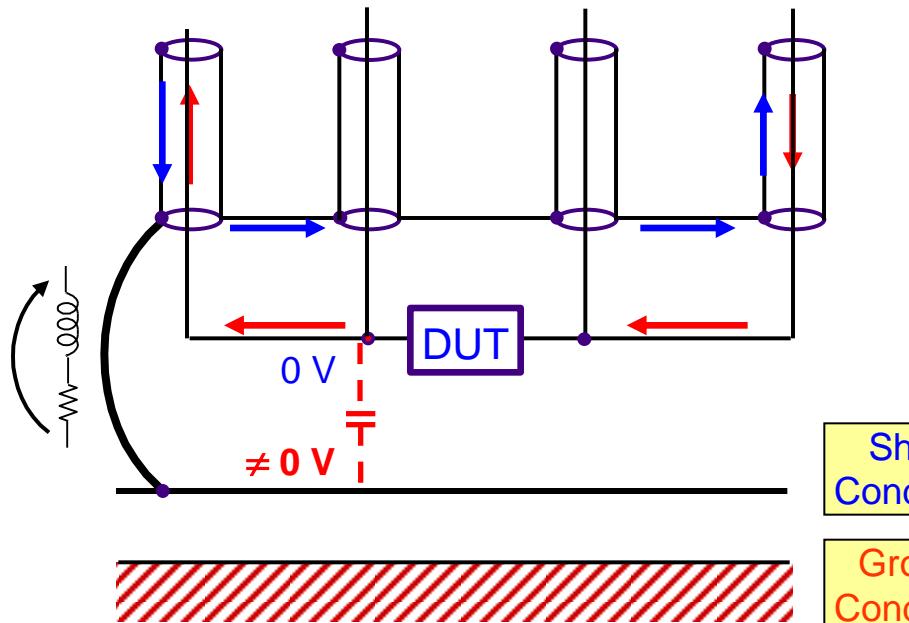

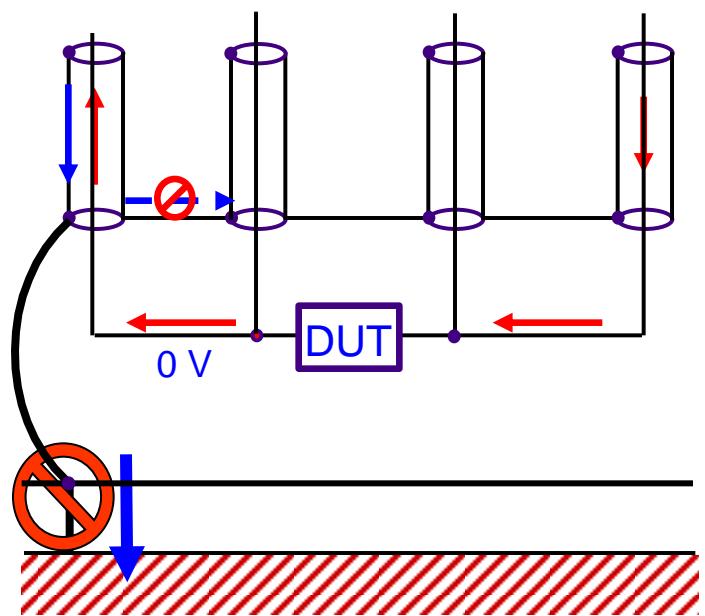(b) Do NOT connect the guard terminal directly to the ground conductor.



LF impedance measurement



- Terminal configuration
- Guarding

RF impedance measurement

- **Terminal configuration in the RF range**
- Test port extension in the RF range

Terminal Configuration in the RF Range

Coaxial One Port Measurement

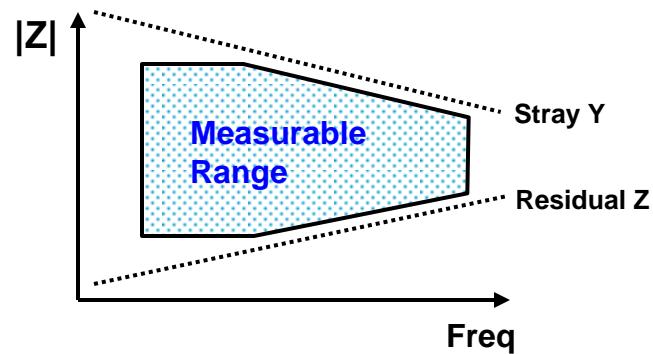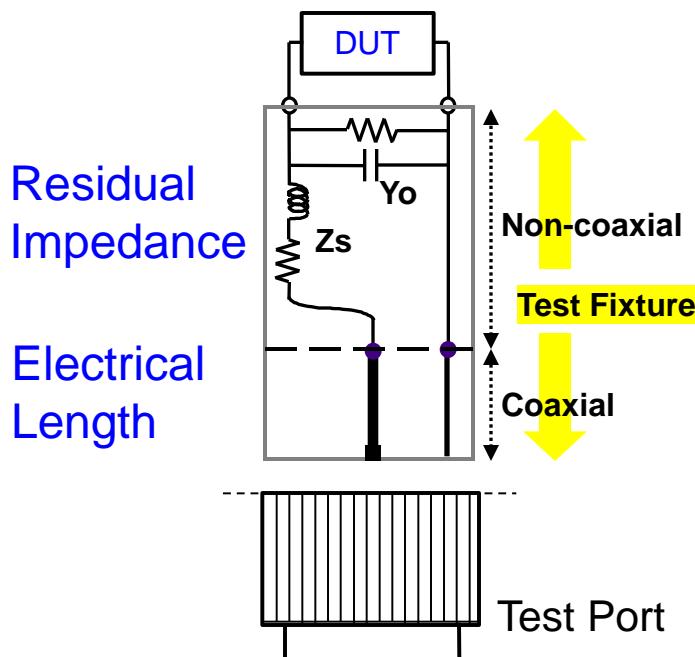

The measured value is also affected by a number of conditions surrounding the DUT:

- Ground plate
- Terminal layout
- Dielectric constant of the insulator
- Other conditions

LF impedance measurement

- Terminal configuration
- Guarding

RF impedance measurement


- Terminal configuration in the RF range
- **Test port extension in the RF range**

Test Port Extension in the RF Range




Unlocking Measurement Insights for 75 Years


Calibration plane extension

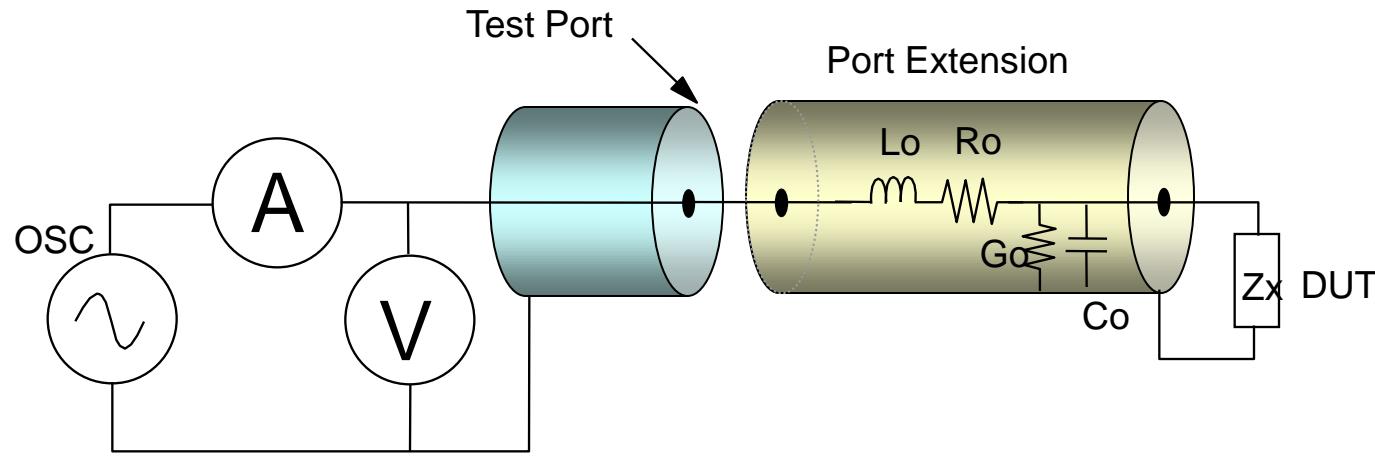

(a) Port Extension

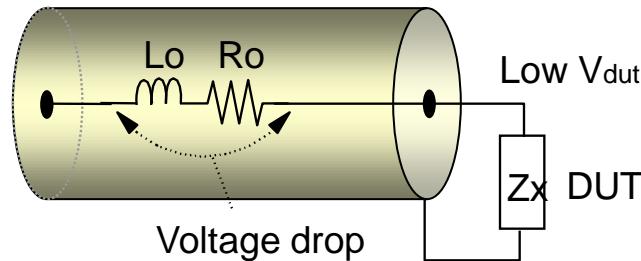

(b) Low impedance DUT

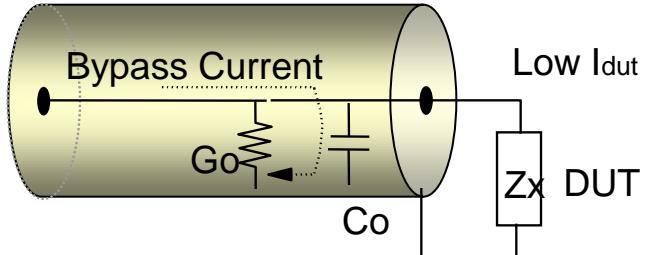

(c) High impedance DUT

Agenda




Unlocking Measurement Insights for 75 Years

- Introduction
- Impedance fundamentals
- Measurement methods
- Fixturing and cabling
- **Calibration and compensation**
- Solution selection process


Compensation \neq Calibration

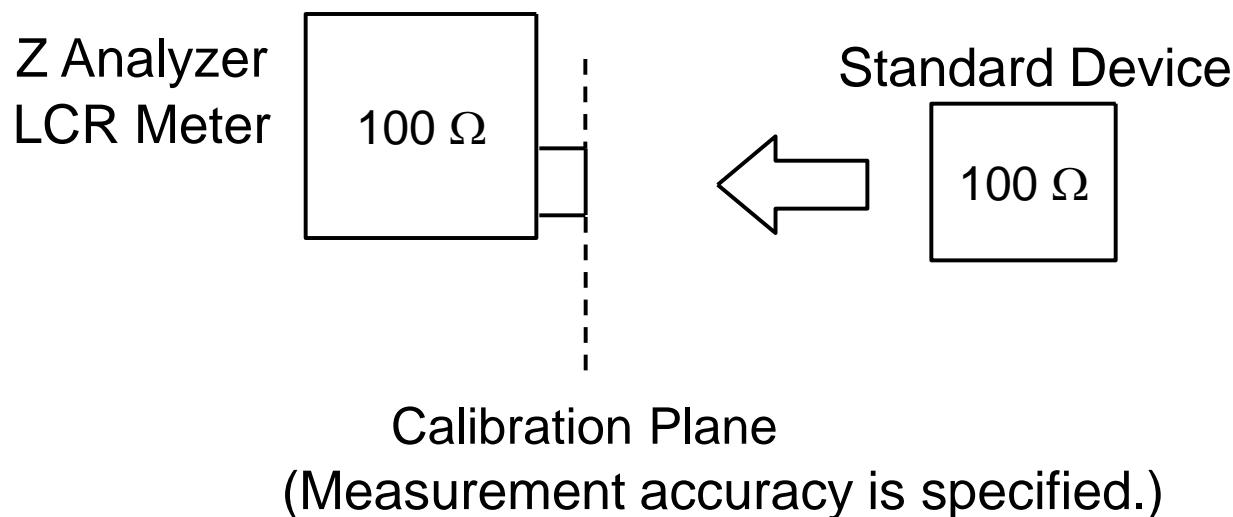Defining the "Calibration Plane" at which measurement accuracy is to be specified.




Cable Correction

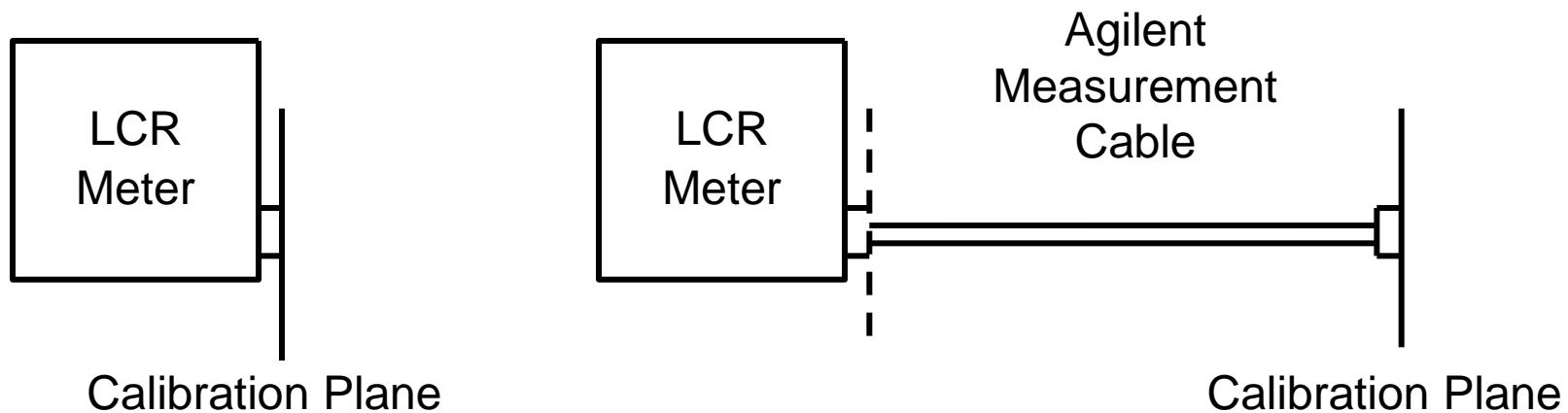Extending the Calibration Plane using specified Agilent cables. (Agilent 16048A/B/D/E)




Measurement Cable Extension Induced Error

Cable length correction

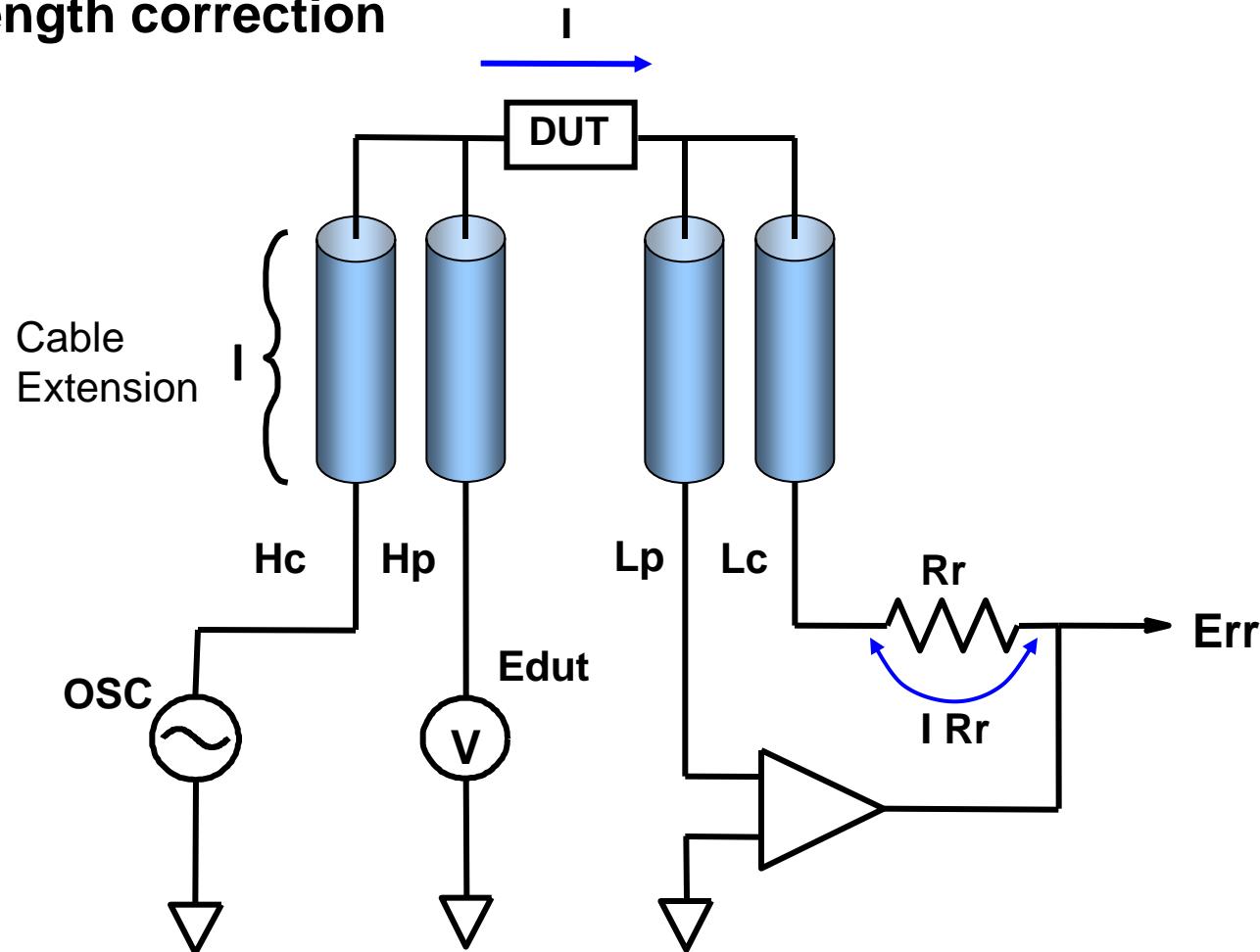


Measurement Cable Extension Induced Error

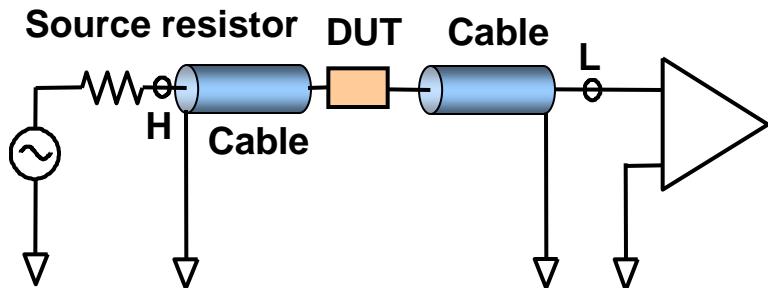Cable length extension in the low frequency range



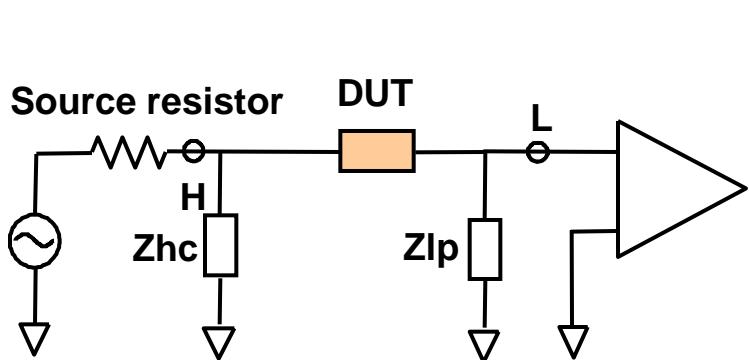(a) Extended cables connected to High and Low terminals




(b) Effects of cable extension

Z_{hc} : An impedance determined by the capacitance connected to the High terminal (H). This impedance decreases the test signal level and degrades accuracy.

Z_{lp} : An impedance determined by the cable connected to the Low terminal (L). This impedance decreases the input impedance of the amplifier and decreases the measurement accuracy.

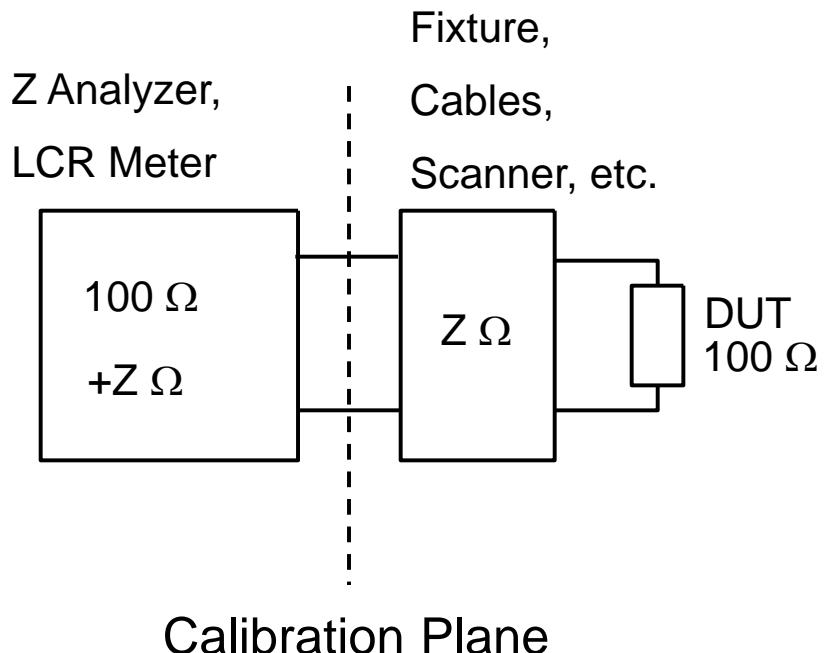Reducing the effects of error sources existing between the DUT and the instrument's "Calibration Plane".




- 2 types of compensation:
 - OPEN/SHORT compensation
 - OPEN/SHORT/LOAD compensation

Compensation


OPEN/SHORT Compensation

Basic Theory

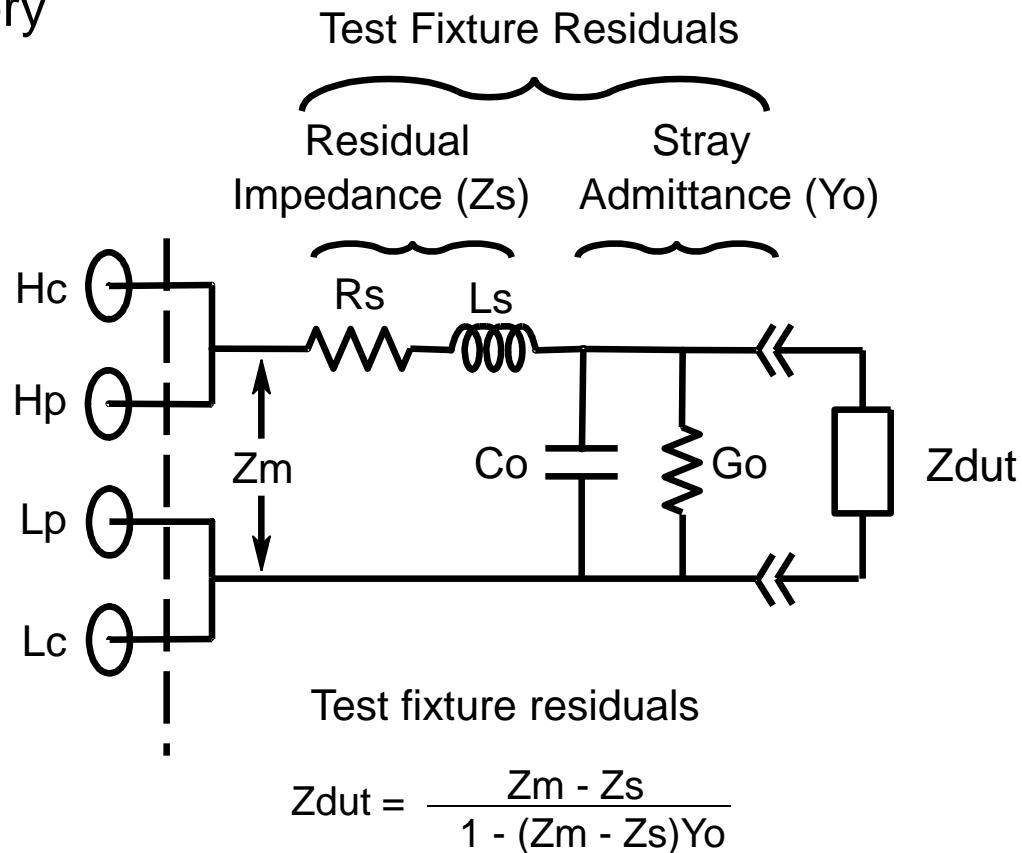


Compensation

OPEN/SHORT Compensation

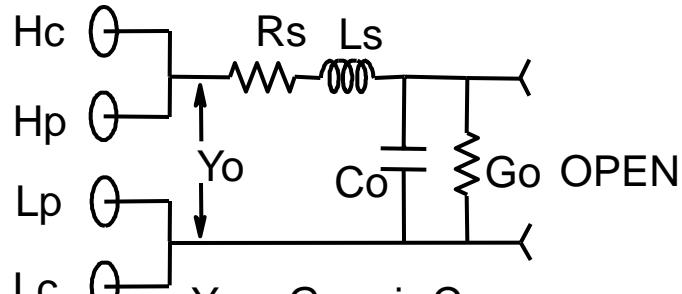

$$Y_o = G_o + j\omega C_o$$
$$(R_s + j\omega L_s \ll \frac{1}{G_o + j\omega C_o})$$


(a) OPEN measurement

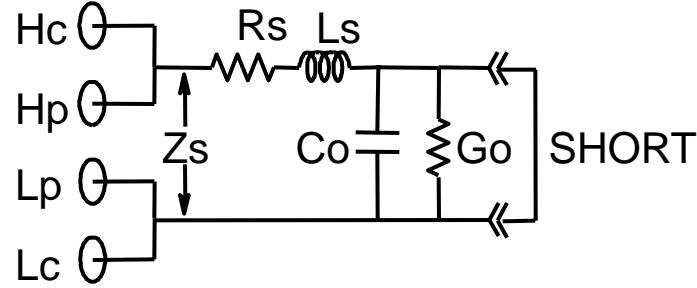

$$Z_s = R_s + j\omega L_s$$

SHORT Impedance $\ll R_s + j\omega L_s$

(b) SHORT measurement

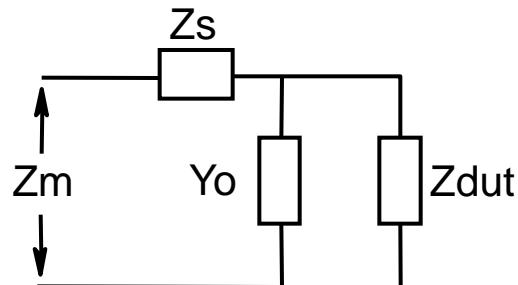


$$Z_{dut} = \frac{Z_m - Z_s}{1 - (Z_m - Z_s)Y_o}$$

(c) Compensation formula


Compensation

OPEN/SHORT Compensation Issues

Problem 1: Difficulty in eliminating complicated residuals

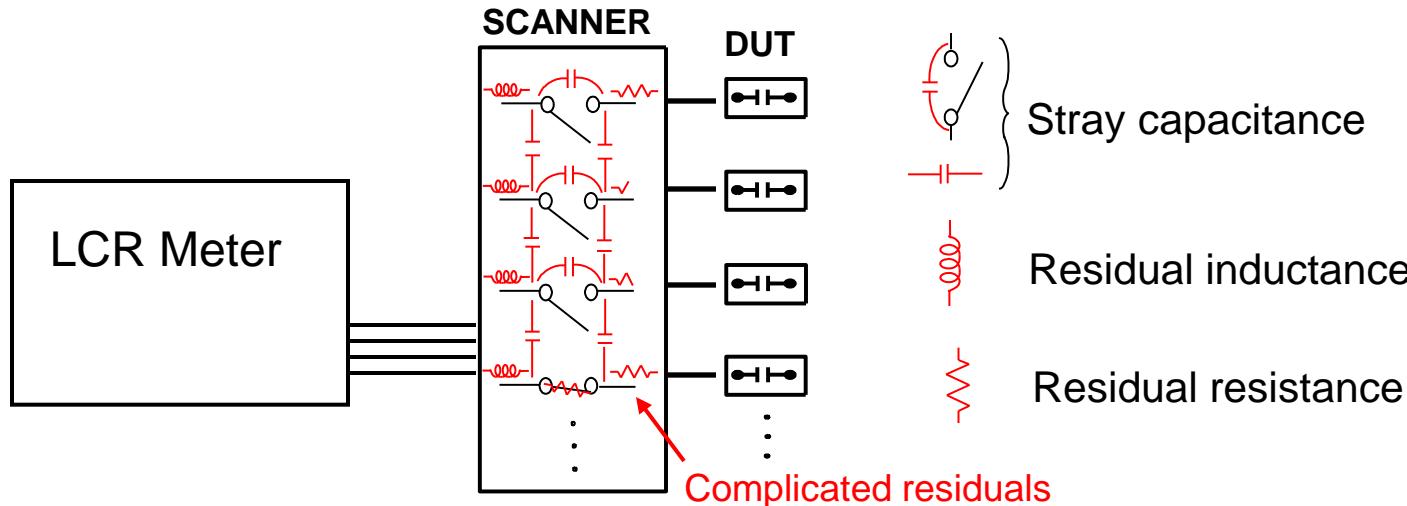

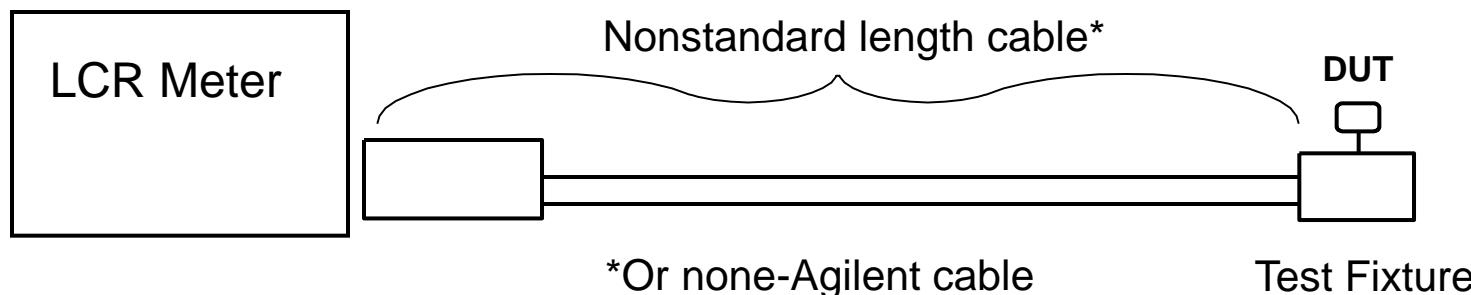Problem 2: Difficulty in eliminating Phase Shift Error




Compensation

OPEN/SHORT/LOAD Compensation



Unlocking Measurement Insights for 75 Years

Basic Theory

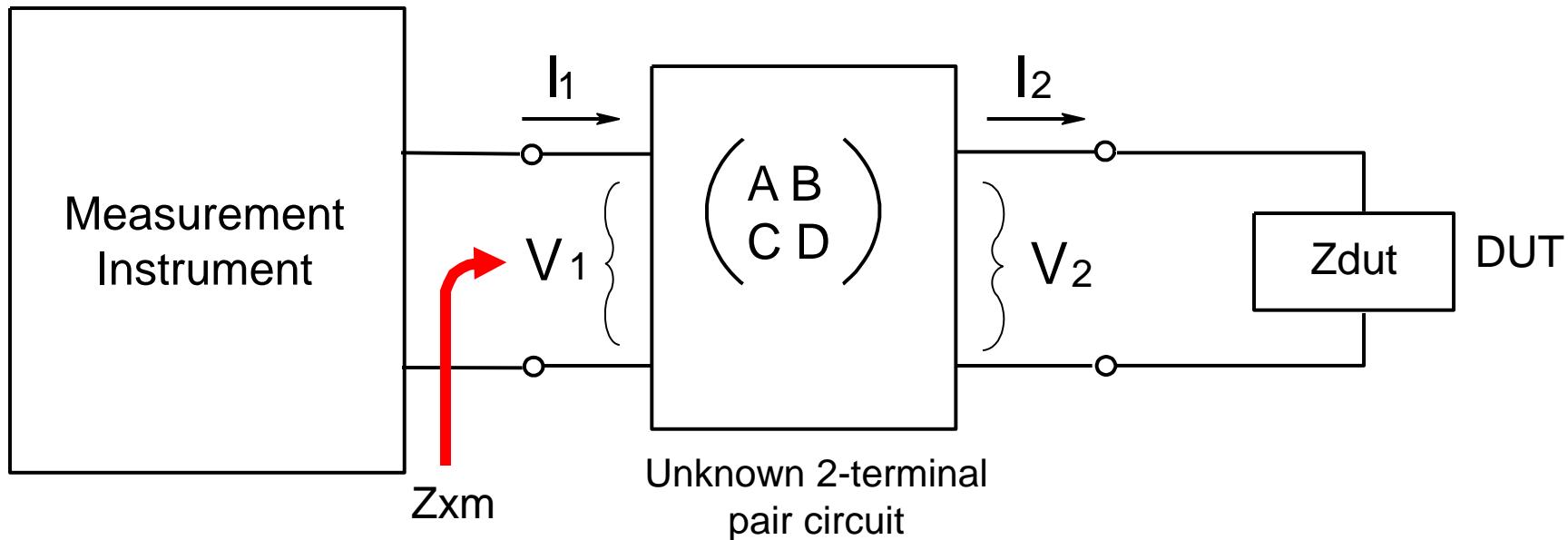

$$Z_{dut} = (A \times V_2 + B \times I_2) / (C \times V_2 + D \times I_2) = (A \times Z_{xm} + B) / (C \times Z_{xm} + D)$$

where $Z_{dut} = V_1/I_1$ and $Z_{xm} = V_2/I_2$

Basic Theory

$$Z_{dut} = \frac{Z_{std} (Z_o - Z_{sm}) (Z_{xm} - Z_s)^*}{(Z_{xm} - Z_s) (Z_o - Z_{xm})}$$

Z_o : OPEN measurement value

Z_s : SHORT measurement value

Z_{sm} : Measurement value of the LOAD device

Z_{std} : True value of the LOAD device

Z_{xm} : DUT Measurement value

Z_{dut} : DUT Corrected value

*These are complex vectors. Conversions to real and imaginary components are necessary




Practical Compensation Examples



Unlocking Measurement Insights for 75 Years

Practical Examples


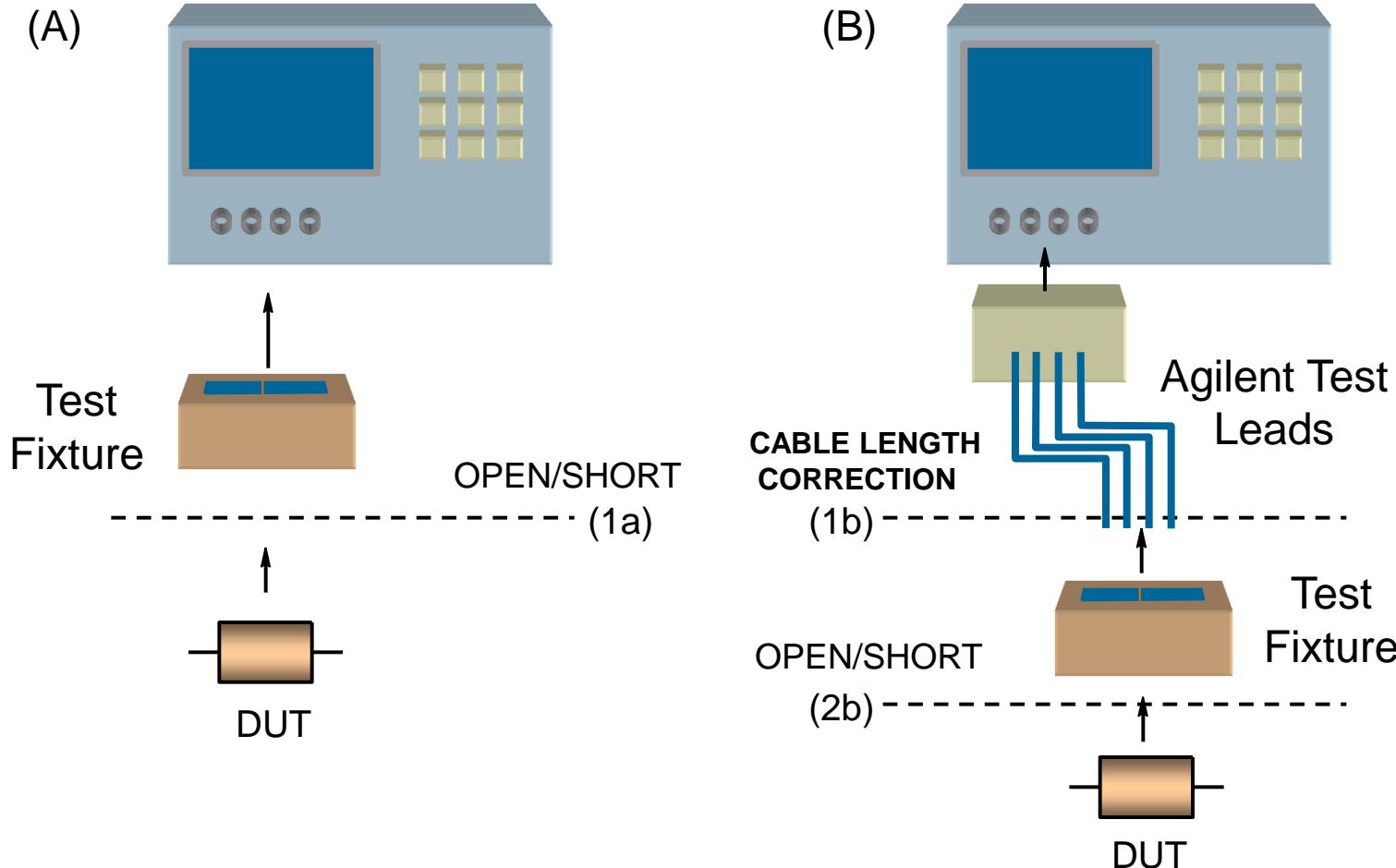


Practical Compensation Examples



Unlocking Measurement Insights for 75 Years

Practical Examples

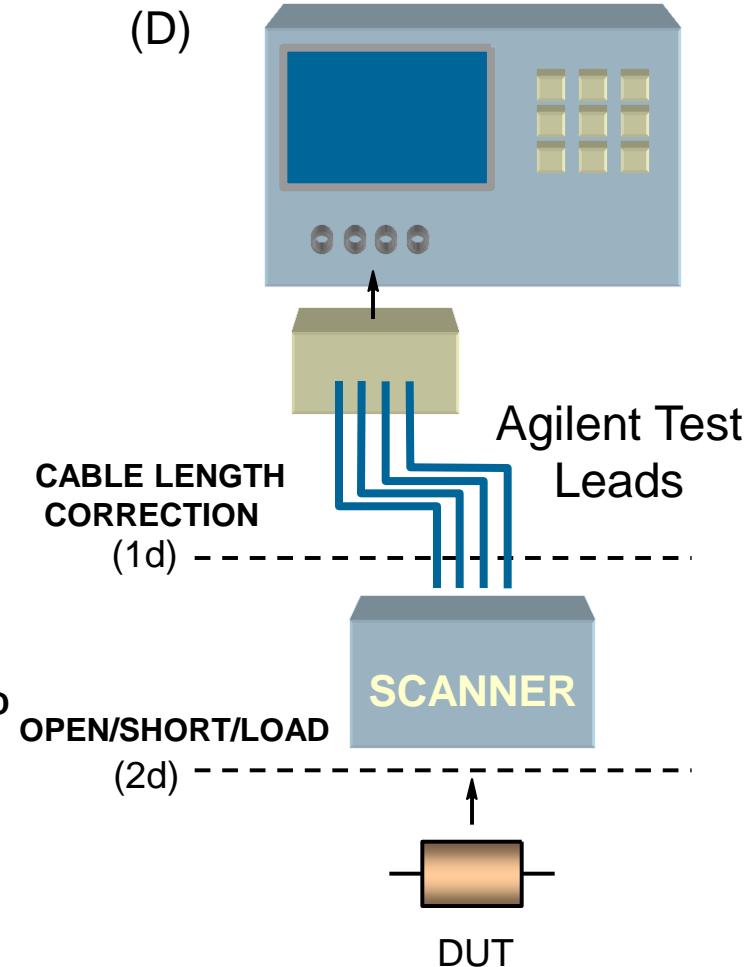
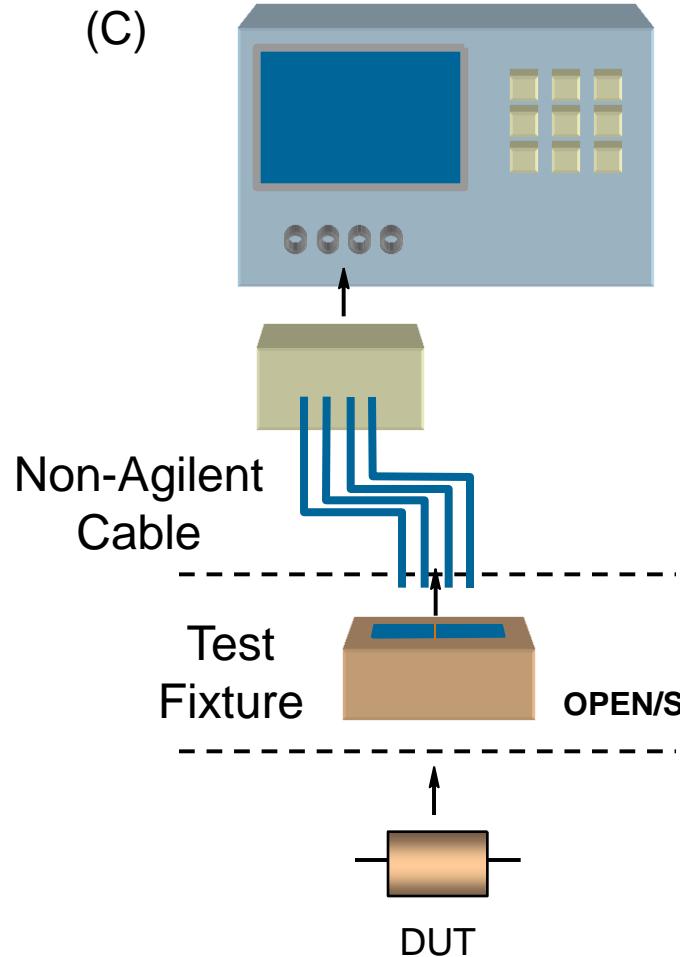


Compensation in RF Range



Unlocking Measurement Insights for 75 Years


Error Source Model

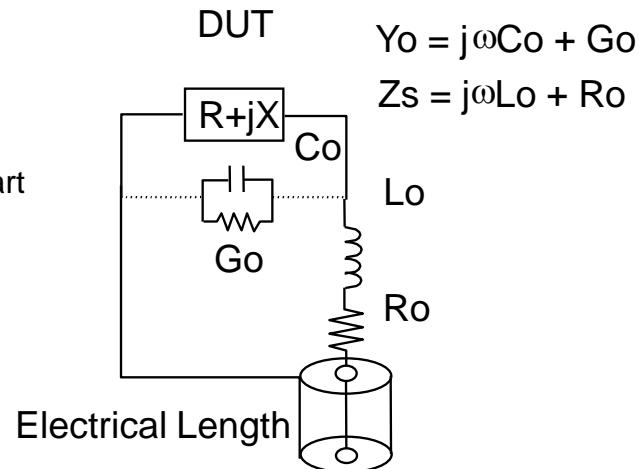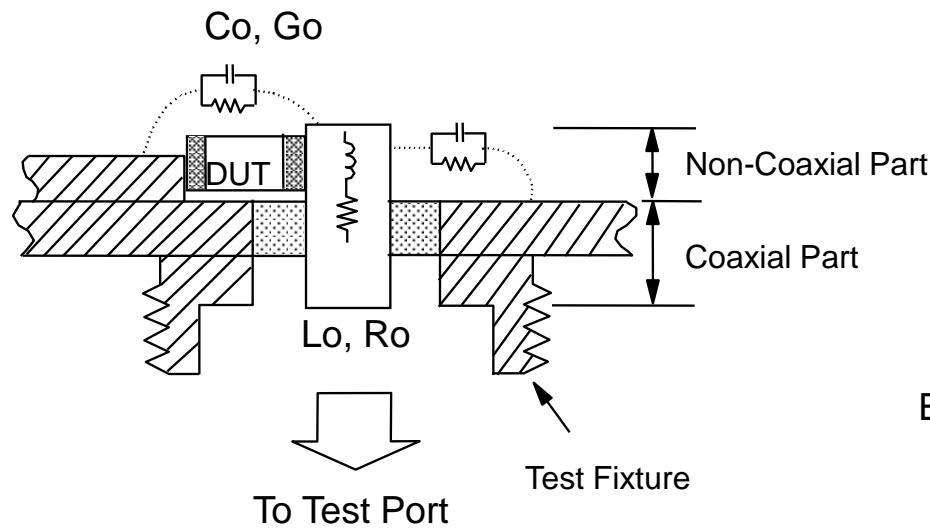

(a) Typical test fixture configuration

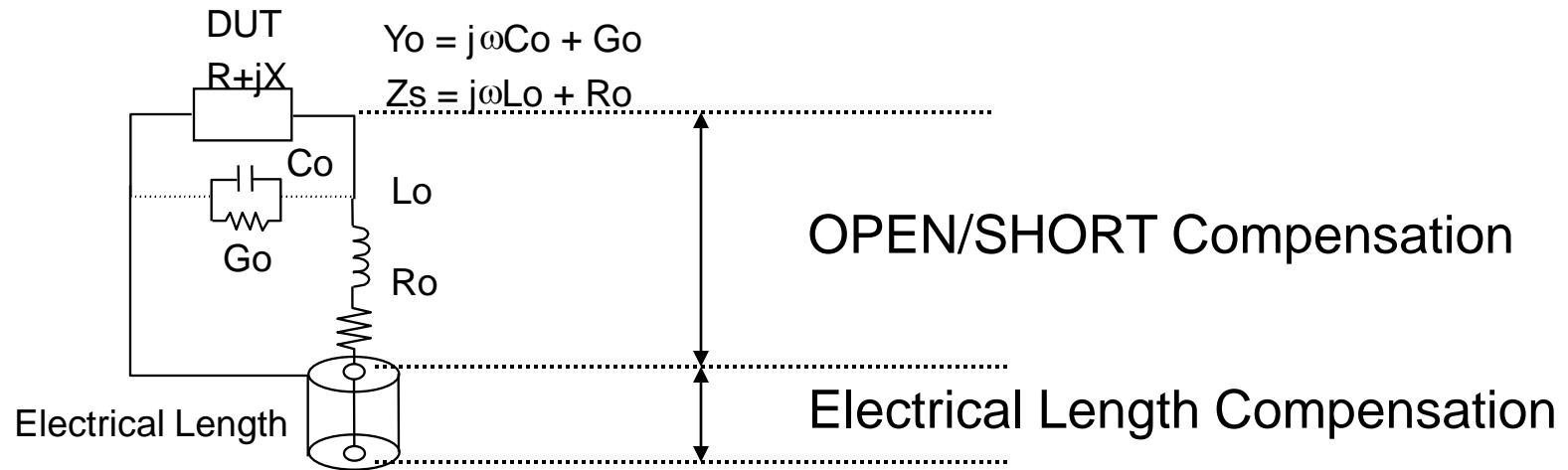(b) Simplified equivalent circuit model

Compensation for coaxial and non-coaxial portions




**Simplified Equivalent
Circuit Model**

Port Extension



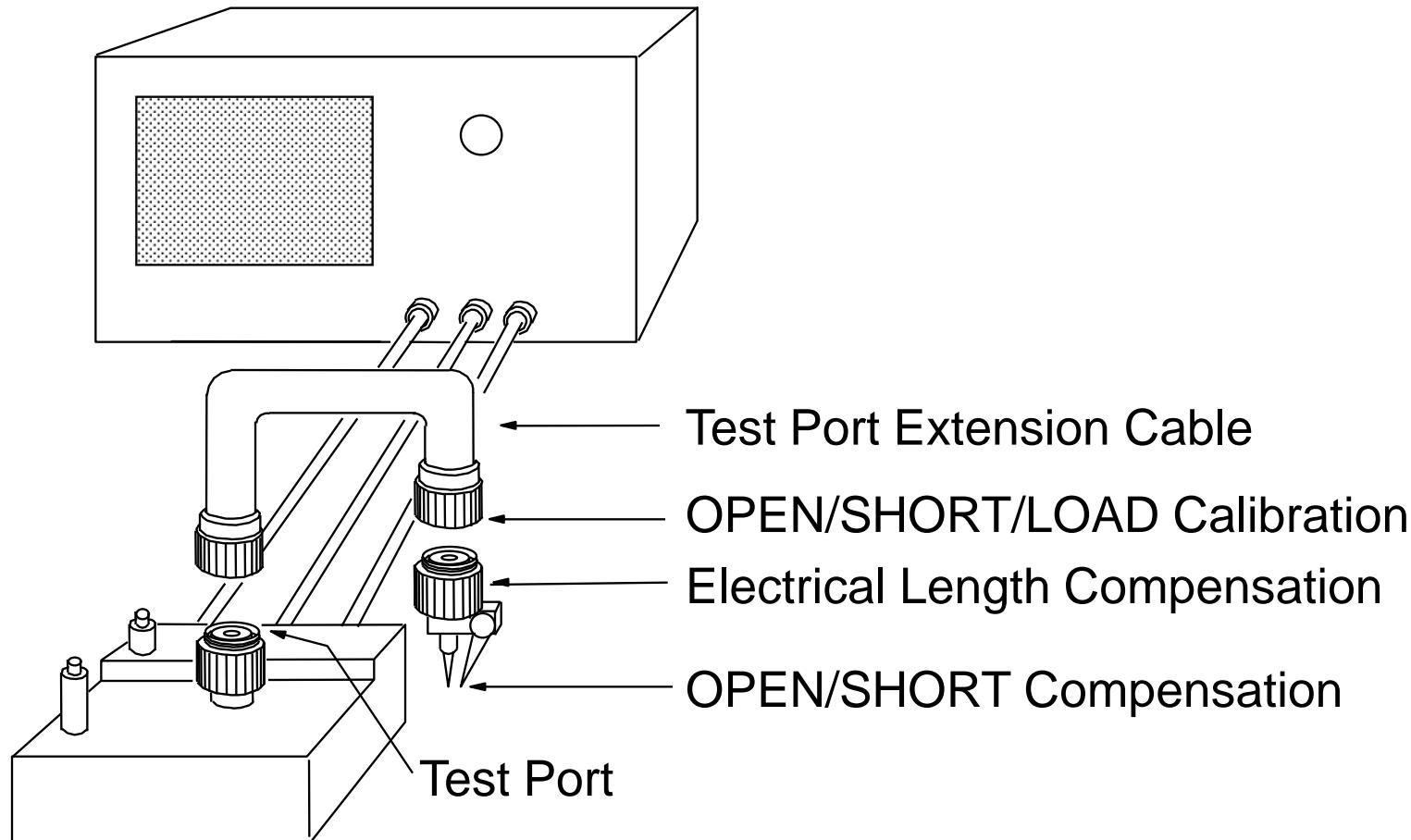Unlocking Measurement Insights for 75 Years



Agenda




Unlocking Measurement Insights for 75 Years

- Introduction
- Impedance fundamentals
- Measurement methods
- Fixturing and cabling
- Calibration and compensation
- **Solution selection process**



Step 1: Find Impedance (1 of 2)

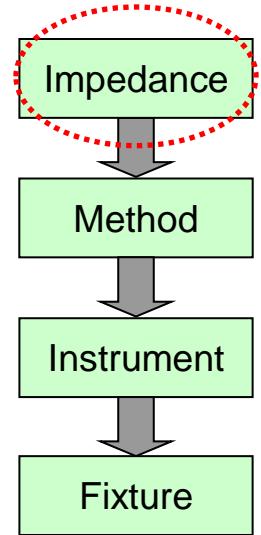- **Determine:**
 - Approximate C or L value of DUT
 - Typical measurement frequency
- **Find impedance using an admittance chart**




Step 1: Find Impedance (2 of 2)

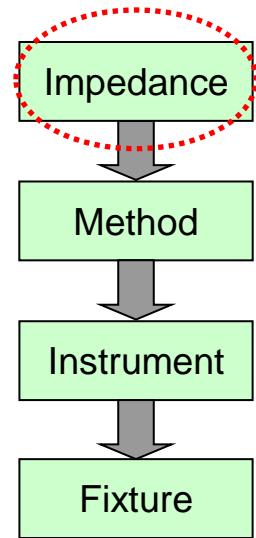
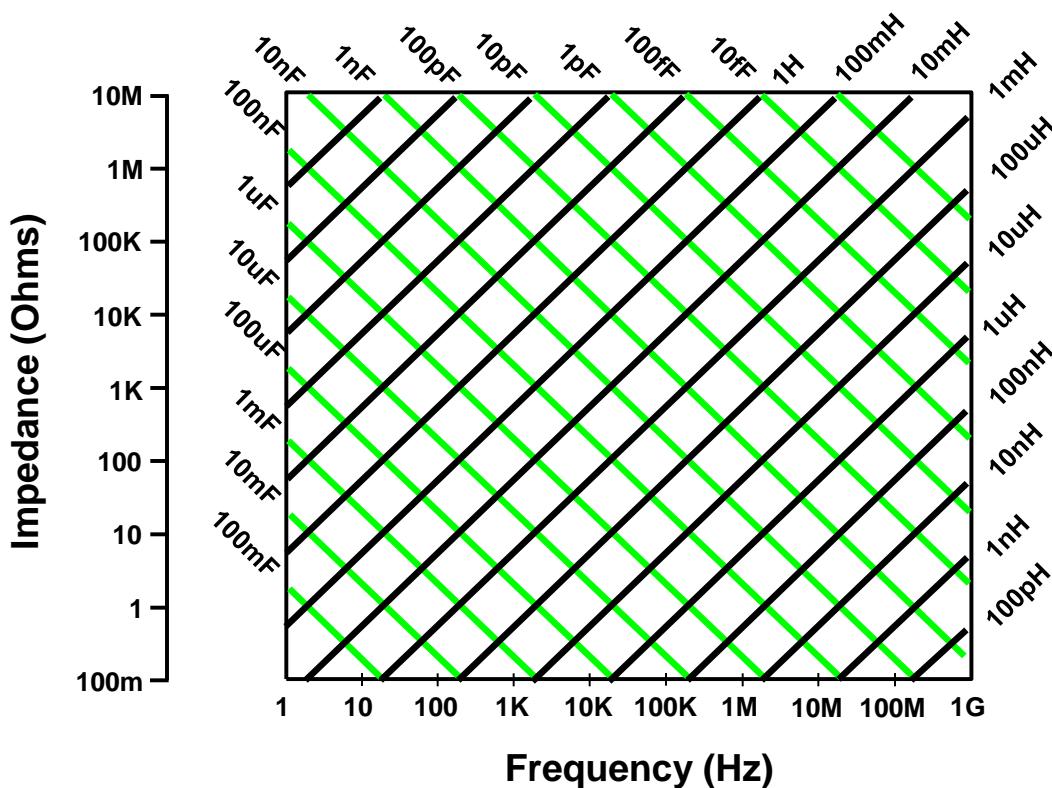
- Use this admittance chart to find impedance from capacitance or inductance value



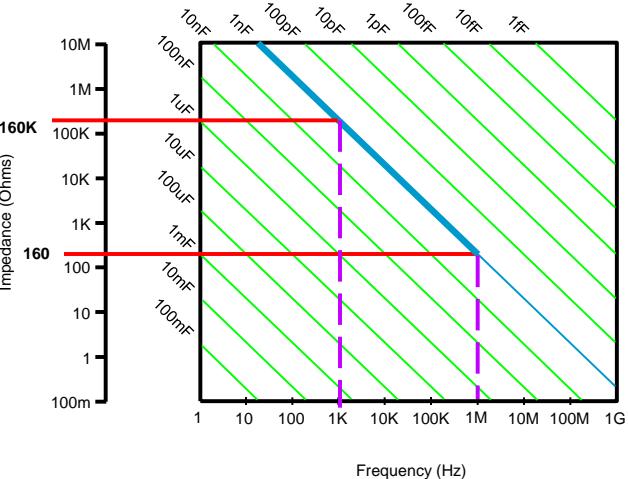Example: a 1 nF capacitor at 1 MHz has an impedance of about 160 ohms




Step 2: Choose Measurement Method

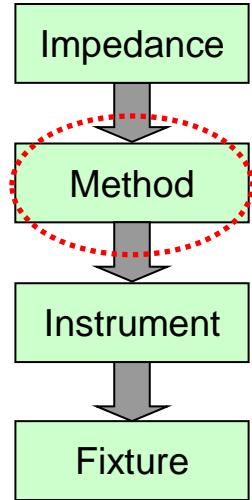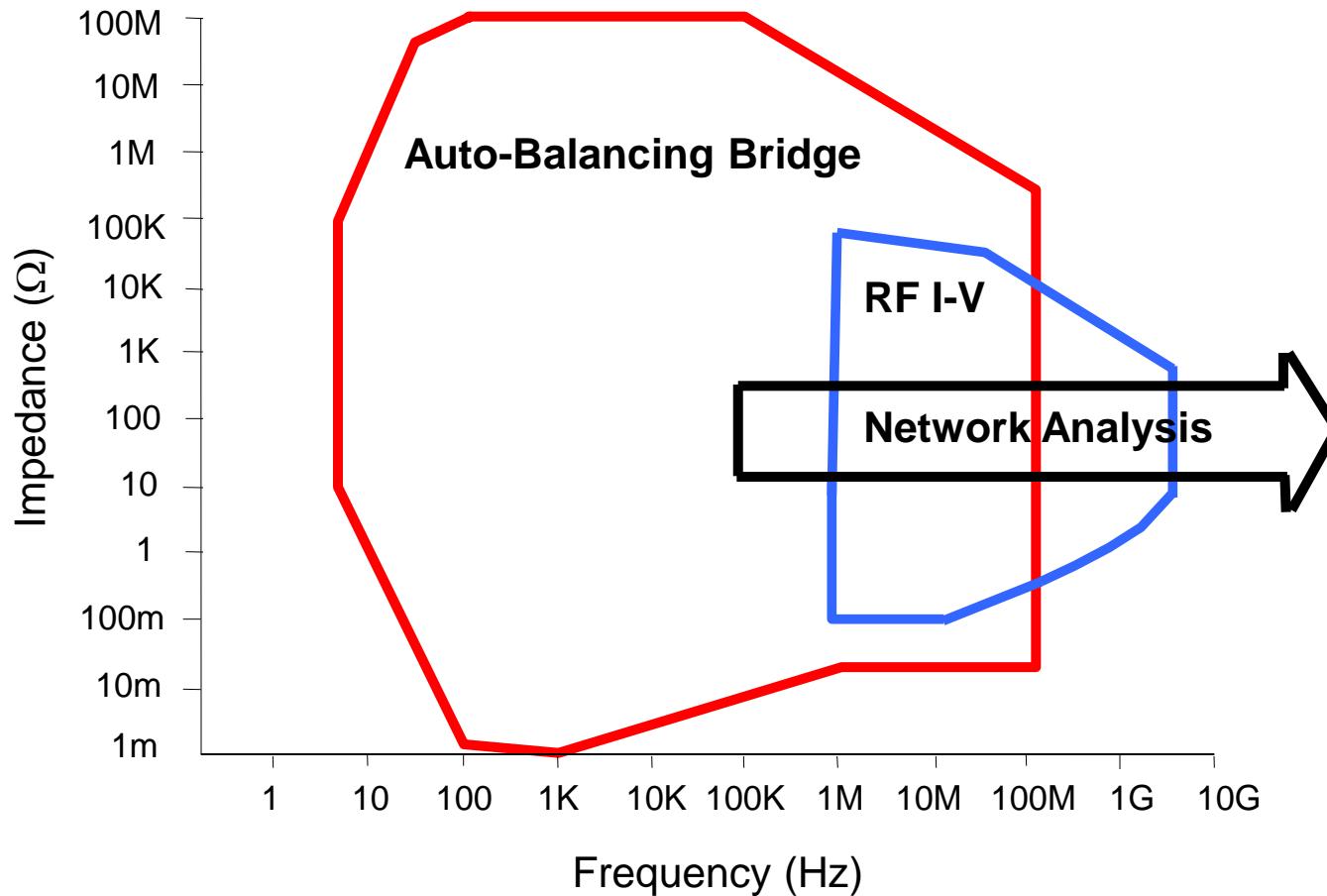

Step 3: Select Instrument


- **Determine test conditions:**
 - Measurement parameters (R, C, L, Z, D and Q)
 - Frequency (range, swept or fixed)
 - AC signal (voltage/current, range, swept or fixed)
 - DC bias (voltage/current, range, swept or fixed)
- **Identify desired display and analysis functions:**
 - Display: graph?
 - Analysis: market, limit lines, equivalent circuit analysis?
- **Identify other needs (speed, interface, price)**
- **Refer to selection guide to choose best instrument (*Agilent LCR Meters, Impedance Analyzers and Test Fixtures*, P/N 5952-1430E)**

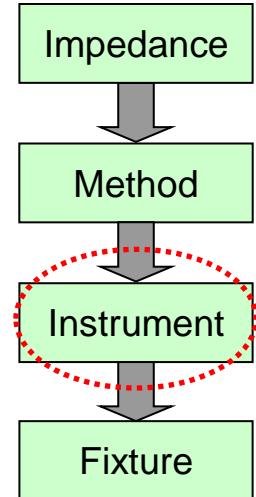

Step 4: Select Test Fixture (1 of 2)

- Determine fixture model number group by knowing DUT type and instrument connector type:

DUT Type	Instrument Connector Type	
	BNC (≤ 110 MHz)	7 mm (≤ 3 GHz)
Lead Component 	16047A/D/E, 16060A	16092A
SMD Component 	16034E/G/H, 16044A 16334A	16192A, 16194A, 16196A/B/C/D, 16197A
Other Shape or Size	16089A/B/C/D/E	None
Extension Cable 	16048A/D/E/G/H	None
DC Bias 	16065A/C, 42841A, 42842A/B/C, 42843A	16200B
Probe 	16095A, 42941A	16094-65000
Material 	16451B, 16452A	16453A, 16454A
Others	16314-60011 (Balun)	None

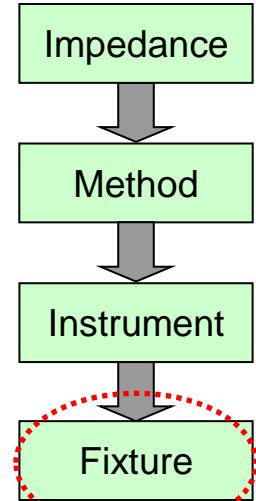


Step 4: Select Test Fixture (2 of 2)

- **Determine additional conditions:**

- Frequency range
- Impedance range
- DUT shape and size
- Location of electrodes
- DC bias
- Cable extension
- Temperature

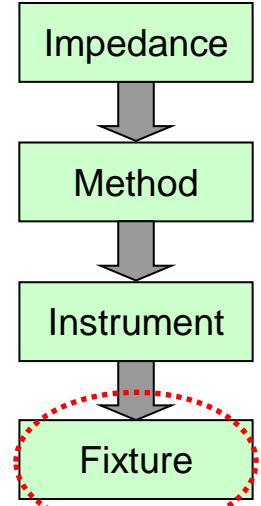- **Refer to selection guide to choose suitable fixture**
**([Accessories Selection Guide for Impedance Measurements](#),
P/N 5965-4792E)**



Product Selection Process Summary



Unlocking Measurement Insights for 75 Years

- **Step 1: Find impedance**

- Frequency
- DUT value

- **Step 2: Choose method**


- Frequency range
- Impedance range
- Accuracy

- **Step 3: Select instrument**

- Frequency range
- Impedance range
- Accuracy

- **Step 4: Select test fixture**

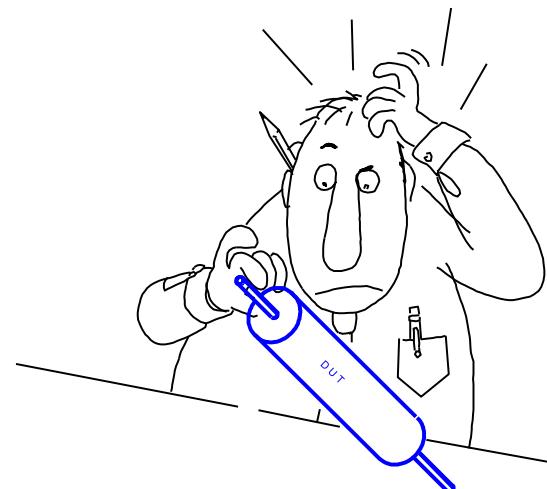- DUT and connector types
- Test conditions



For More Information



Unlocking Measurement Insights for 75 Years

- **Literature**

- *Impedance Measurement Handbook*, Lit. No. 5950-3000
- *Agilent Impedance Analyzers, LCR Meters and Test Fixtures*, Selection Guide, Lit. No. 5952-1430E
- *Accessories Selection Guide for Impedance Measurements*, Lit. No. 5965-4792E
- *8 Hints for Successful Impedance Measurements*, Lit. No. 5968-1947E
- *Solutions for Measuring Permittivity and Permeability with LCR Meters and Impedance Analyzers*, Lit. No. 5980-2862E

- **Internet**

- <http://www.agilent.com/find/impedance>
- <http://www.agilent.com/find/impedance-accessory>



Agilent Technologies

Agilent Technologies
February 2014



Thank you!



Adolfo Del Solar

Application Engineer
adolfo_del-solar@agilent.com