

LP3985 SOT23-5 Evaluation Board Instruction



National Semiconductor
Application Note 1223
Mary F Kao
May 2002



INTRODUCTION

This evaluation board is designed to enable independent evaluation of the LP3985 electrical performances. Each board is assembled and tested in the factory. This evaluation board instruction is for the SOT23-5 package.

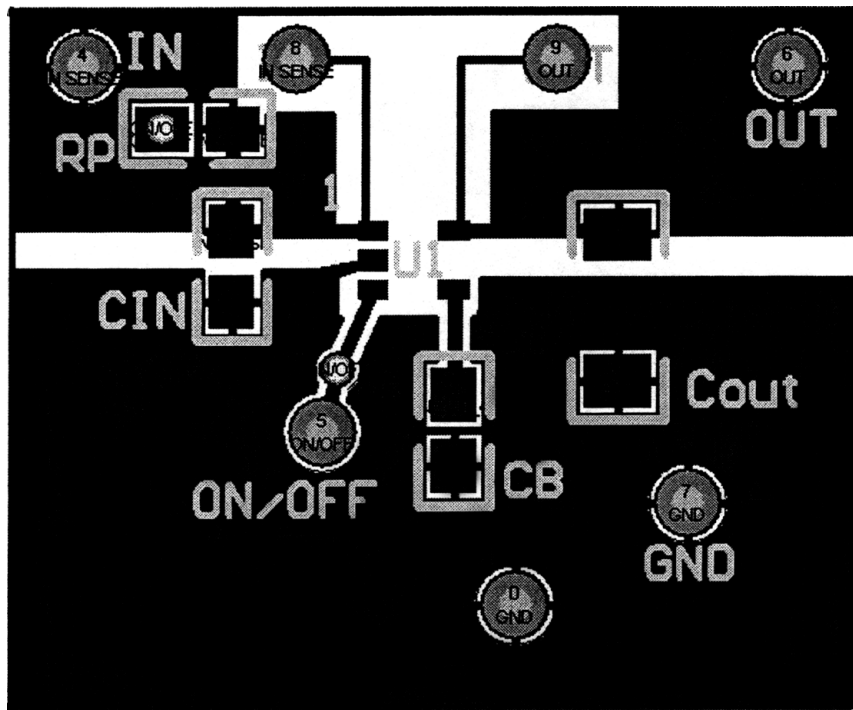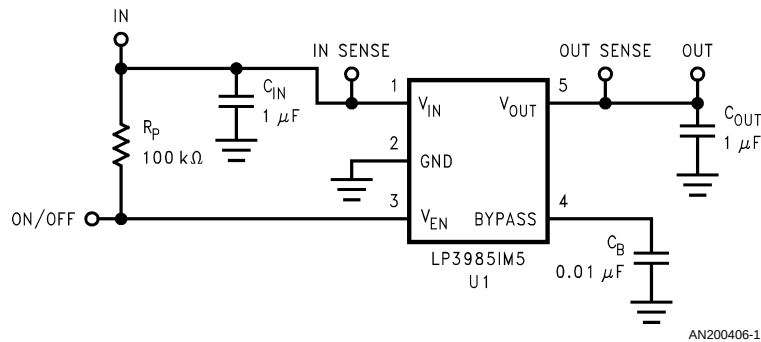The schematic and layout of the evaluation board are given below:



The LP3985 is a micropower CMOS voltage regulator that can provide up to 150 mA of output current. The 0.01 μF bypass capacitor is optional; but if used, it will reduce noise on the regulator output. The R_P resistor is tied to V_{IN} so that the regulator is on all the time. To control the V_{EN} pin externally, disconnect R_P resistor and use the ON/OFF connector on the evaluation board.

The input sense and output sense pins are used for more precise voltage measurements. These pins are connected to the LP3985 input and output via high impedance traces.

The LP3985 is also available in 5 bump large bump micro SMD and 5 bump small bump micro SMD. Evaluation boards for these two packages are available as well.

Below is the bill of material for the LP3985 SOT23-5 board.

Designator	Value	Amount	Footprint	Note
RP	100 k Ω	1	0805	
CB	0.01 μ F	1	0805	
C _{IN}	1 μ F	1	0805	X5R or X7R
C _{OUT}	1 μ F	1	1812	X5R or X7R
U1	LP3985IM5-xx	1	MF05A	The “xx” corresponds to the appropriate LDO output voltage option.
Test Pins		7		Keystone 1040

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.



National Semiconductor Corporation
Americas
Email: support@nsc.com

www.national.com

National Semiconductor Europe
Fax: +49 (0) 180-530 85 86
Email: europe.support@nsc.com
Deutsch Tel: +49 (0) 69 9508 6208
English Tel: +44 (0) 870 24 0 2171
Français Tel: +33 (0) 1 41 91 8790

National Semiconductor Asia Pacific Customer Response Group
Tel: 65-2544466
Fax: 65-2504466
Email: ap.support@nsc.com

National Semiconductor Japan Ltd.
Tel: 81-3-5639-7560
Fax: 81-3-5639-7507