

LM2642 Evaluation Board

National Semiconductor
Application Note 1239
Allan Fisher
July 2003



Introduction

The LM2642 evaluation board has been developed to aid in the design and evaluation of dc/dc converters based on the LM2642 controller IC. The board is intended to be a reusable tool on which several different circuit configurations meeting the requirements of different applications can be built. As shown in Figure 1, the evaluation board is configured to provide two outputs of 5V/3A and 3.3V/3A from an input range of 6V to 30V. The corresponding bill of materials is given in *Table 1*. *Figure 2*, *Figure 9* and *Figure 10* show the full evaluation board schematic and layout.

Board Configuration


The LM2642 Eval. Board can be easily configured for different current sensing schemes, as well as for parallel operation. *Table 1* gives the jumper and part settings for the current sensing. *Table 2* gives the jumper and circuit configurations for parallel and two-channel operation. The evalu-

ation board also includes several optional component pads for reducing switch node ringing and current sense noise, and for low input voltage applications.

TABLE 1. Jumper Settings for Current Sensing

Jumper/Part#	Connects To	Current Sense
KSx	VIN	Sense Resistor
RSNx	RSx	
KSx	DSx	R _{DS(ON)} Sense
RSNx	SWx	
C28, 29, 30, 31	Installed	Sense Resistor
C5, 32, 17, 33	Open	
C28, 29, 30, 31	Open	R _{DS(ON)} Sense
C5, 32, 17, 33	Installed	

Board Configuration (Continued)

 

20047401

FIGURE 1. Example Circuit

Parallel Operation

In applications with high output current demand, the two switching channels can be configured to operate as a two-180° out of phase converter to provide a single output voltage with current sharing between the two switching channels. This approach greatly reduces the stress and heat on the output stage components while lowering input ripple current. The sum of inductor ripple current is also reduced which results in lowering output ripple voltage. Because precision current sense is the primary design criteria to ensure accurate current sharing between the two channels, both channels must use external sense resistors for current sensing. To minimize the error between the error amplifiers of the two channels, tie the feedback pins FB1 and FB2 together using **J1** and **J2** and connect to one voltage divider for output voltage sensing. Also, tie pins COMP1 and COMP2 together with **R30** and connect to a single compensation network. ON/SS1 and ON/SS2 must be tied together with **R29** to enable and disable both channels simultaneously. Also, both output nodes must be connected.

TABLE 2. Parallel Configuration Settings

Jumper/Part#	2-Ch. Setting	Parallel Setting
J1	Open	Short
J2	Open	Short
R29	Open	Short
R30	Open	Short
R24	Installed	Open
R19	Installed	Open
R20	Installed	open

Optional Components


Optional resistor **R26**, must be installed with a 4.7ohm resistor when the input voltage is below 5.5V. This will ensure that VLIN5 does not fall below the UVLO threshold.

Power MOSFETs are very fast switching devices. In synchronous rectifier converters, the rapid increase of drain current in the top FET coupled with parasitic inductance will generate unwanted Ldi/dt noise spikes at the source node of the FET (SWx node) and also at the VIN node. The magnitude of this noise will increase as the output current increases. This parasitic spike noise may turn into electromagnetic interference (EMI), and can also cause problems in device performance. The LM2642 evaluation board provides several options for suppressing this noise.

R-C filters can be added to the current sense amplifier inputs as shown in *Figure 7*. These filters are comprised of **R2**, **C3**, **C4**, **R6**, and **R14**, **C14**, **R16**, **C15**, and are included in the example circuit. These filters will reduce the susceptibility to switching noise, especially during heavy load transients and short on-time conditions. Note that these filters should only be used when a current sense resistor is used.

The resistor in series with the SWx pin (**R31**, **R32**) slows down the gate drive (HDRVx), thus slowing the rise and fall time of the top FET, yielding a longer drain current transition time and reducing switch node ringing. Top FET switching losses will increase with higher resistance values. Small resistors (1-5 ohms) can also be placed in series with the HDRVx pin (**R8**, **R17**) or the CBOOTx pin (**R9**, **R18**) to effectively reduce switch node ringing. A CBOOT resistor will slow the rise time of the FET, whereas a resistor at HDRV will reduce both rise and fall times.

 To maintain stable regulation, the FBx pins should remain free of noise. The LM2642 evaluation board provides pads for **C10** and **C24**, which can be used to suppress noise that may be picked up by the FBx traces. Notice that both of these capacitors are placed close to the FBx nodes.



Note: * Optional resistor that is laid out as a copper trace on the board.
 ** Optional component that is not installed on the board.

20047402

FIGURE 2. Full Schematic of the LM2642 Evaluation Board

TABLE 3. Bill Of Materials

Code	Description	Manufacturer
C1	Cap-MLCC 1uF 50V UMK212F10560ZG	TaiyoYuden
C11	Cap-MLCC 10nF 50V VJ0805Y103KXA	Vishay
C12	Cap-MLCC 10nF 50V VJ0805Y103KXA	Vishay
C13	Cap-MLCC 10nF 50V VJ0805Y103KXA	Vishay
C18, C21	Cap-MLCC 470pF 50V VJ0805Y471KXAMT	Vishay
C19	Cap-MLCC 1nF 25V VJ0805Y102KXA	Vishay
C2	Cap-MLCC 10nF 50V VJ0805Y103KXA	Vishay
C20	Cap-MLCC 1nF 50V VJ0805Y102KXA	Vishay
C22	CAP-SP 150uF 6.3V +/-20% EEFUE0J151R	Panasonic
C25	Cap-MLCC 0.1uF 50V VJ0805Y104KXA	Vishay
C26	Cap-MLCC 4.7uF 10V LMK316475JML	TaiyoYuden
C27	Cap-MLCC 1uF 10V LMK212105FML	TaiyoYuden
C28, C29, C30, C31	Cap-MLCC 10uF 35V GMK 325 F106ZH-B	TaiyoYuden
C3, C4, C14, C15	Cap-MLCC 100pF 50V VJ0805Y101KXA	Vishay
C34	Cap-MLCC 0.1uF 50V VJ0805Y104KXA	Vishay
C7	Cap-MLCC 0.1uF 50V VJ0805Y104KXA	Vishay
C8	CAP-SP 150uF 6.3V +/-20% EEFUE0J151R	Panasonic
COM1&2, PGOOD1	Terminal Silver 0.094" Dia 40F6004	Newark
D3	Switching Diode-Dual 70V 200mA BAW56F	Fairchild
D4	Schottky Diode 40V MBRS140T31A	ON Semiconductor
D5	Schottky Diode 40V MBRS140T31A	ON Semiconductor
IC1	IC controller LM2642	National
L1	Inductor 8u2H CEP125-8R2MC	Sumida
L2	Inductor 6uH CEP125-6R0MC	Sumida
P1	HEADER- BREAKAWAY 2 POST PITCH = 0.156" 26-48-1025	Molex
P2	HEADER- BREAKAWAY 2 POST PITCH = 0.156" 26-48-1025	Molex
P3	HEADER- BREAKAWAY 2 POST PITCH = 0.156" 26-48-1025	Molex
Q1	N-MOSFET FDS6690A	Fairchild
Q2	N-MOSFET FDS6690A	Fairchild
Q3	N-MOSFET FDS6690A	Fairchild
Q4	N-MOSFET FDS6690A	Fairchild
R1	Resistor Chip 13K 0.1W 0.05 CRCW0805*J	Vishay
R10	Resistor Chip 60K4 0.1W 0.01 CRCW08056042F	Vishay
R11	Resistor Chip 20K 0.1W 0.01 CRCW08052002F	Vishay
R13	Resistor Chip 13K 0.1W 0.05 CRCW0805*J	Vishay
R15	Resistor Thick Film 20m 0.5W 0.01 WSL20100.020.01	Vishay
R19	Resistor Chip 33K2 0.1W 0.01 CRCW08053322F	Vishay
R2, R6, R14, R16	Resistor Chip 100R 0.1W 0.05 CRCW08051000J	Vishay
R20	Resistor Chip 20K 0.1W 0.01 CRCW08052002F	Vishay
R22, R25	Resistor Chip 0R0 0.1W ±5% CRCW08050RJ	Vishay
R23	Resistor Chip 20K 0.1W 0.05 CRCW0805203J	Vishay
R24	Resistor Chip 20K 0.1W 0.05 CRCW0805203J	Vishay
R27	Resistor Chip 4R7 0.1W 0.05 CRCW08054R7J	Vishay
R28	Resistor Chip 220K 0.1W 0.05 CRCW0805*J	Vishay
R31, R32	Resistor Chip 4R7 0.1W 0.05 CRCW08054R7J	Vishay
R7	Resistor Thick Film 20m 0.5W 0.01 WSL20100.020.01	Vishay
SW1, SW2	Switch SPST 0.4VA 28V AC/DC A12AB	NKK

TABLE 3. Bill Of Materials (Continued)

Code	Description	Manufacturer
KS1, RS1, KS2, RS2	Jumper Tinned Copper Wire AWG26 L=0.5" x 4pcs.	

Output Voltage Setting

The output voltage for each channel is set by the ratio of a voltage divider as shown in (R10, R11 and R19, R20) Figure 3. The resistor values can be determined by the following equation:

$$R_1 = \frac{R_2}{\left(\frac{V_{nom}}{V_{fb}} - 1\right)} \quad (1)$$

Where $V_{fb}=1.238V$. Although increasing the value of R1 and R2 will increase efficiency, this will also decrease accuracy. Therefore, a maximum value is recommended for R2 in order to keep the output within .3% of V_{nom} . This maximum R2 value should be calculated first with the following equation:

$$R_{2 \max} = \frac{.3\% \cdot V_{nom}}{200 \text{ nA}} \quad (2)$$

Where 200nA is the maximum current drawn by FBx pin.

 


FIGURE 3. Output Voltage Setting

Example: $V_{nom}=5V$, $V_{fb}=1.238V$, $I_{fbmax}=200nA$.

$$R_{2 \max} = \frac{.003 \cdot 5V}{200 \text{ nA}} = 75 \text{ k}\Omega \quad (3)$$

Choose 60K

$$R_1 = \frac{60k}{\left(\frac{5V}{1.238V} - 1\right)} = 19.75 \text{ k}\Omega \cong 20 \text{ k}\Omega \quad (4)$$

The output voltage is limited by the maximum duty cycle as well as the minimum on time. Figure 4 shows the limits for input and output voltages. The recommended maximum output voltage is approximately 1V less than the nominal input voltage. At 30V input, the minimum output is approximately 2.3V, and the maximum is approximately 27V.

For input voltages below 5.5V, V_{LIN5} must be connected to V_{in} through resistor R26 (approximately 4.7 ohm).

 


FIGURE 4. Available Output Voltage Range

Current Sensing and Limiting

As shown in Figure 5, the KSx and RSNSx pins are the inputs of the current sense amplifier. Current sensing is accomplished either by sensing the V_{ds} of the top FET or by sensing the voltage across a current sense resistor (R7 and R15) connected from V_{IN} to the drain of the top FET. The advantage of sensing current across the top FET are reduced parts count, cost and power loss, whereas using a current sense resistor improves the current sense accuracy. Keeping the differential current-sense voltage below 200mV ensures linear operation of the current sense amplifier. Therefore, the $R_{ds(on)}$ of the top FET or the current sense resistor must be small enough so that the current sense voltage does not exceed 200mV when the top FET is on. There is a leading edge blanking circuit that forces the top FET on for at least 166ns. Beyond this minimum on time, the output of the PWM comparator is used to turn off the top FET. Additionally, a minimum voltage of at least 50mV across R_{sns} is recommended to ensure a high SNR at the current sense amplifier.

Assuming a maximum of 200mV across R_{sns} , the current sense resistor can be calculated as follows:

$$R_{sns \max} = \frac{200 \text{ mV}}{I_{\max} + \frac{1}{2} I_{rip}} \quad (5)$$

where $I_{\max}$ is the maximum expected load current, including overload multiplier (ie:120%), and I_{rip} is the inductor ripple current (see Equation (14)). The above equation gives the maximum allowable value for R_{sns} . Switching losses will increase with R_{sns} , thus lowering efficiency.

The peak current limit is set by an external resistor (R1 and R13) connected between the ILIMx pin and the KSx pin. An internal 10μA current sink on the ILIMx pin produces a voltage across the resistor to set the current limit threshold which is compared to the current sense voltage. A 10nF

Current Sensing and Limiting

(Continued)

capacitor across this resistor is required to filter unwanted noise that could improperly trip the current limit comparator.

 


FIGURE 5. Current Sense and Current Limit

Current limit is activated when the inductor current is high enough to cause the voltage at the RSNSx pin to be lower than that of the LIMx pin. This toggles the comparator, thus turning off the top FET immediately. The comparator is disabled either when the top FET is turned off or during the leading edge blanking time. The equation for current limit resistor, R_{lim} , is as follows:

$$R_{lim} = \frac{(I_{lim} + \frac{1}{2} I_{rip}) R_{sns}}{10 \mu A} \quad (6)$$

Where I_{lim} is the load current at which the current limit comparator will be tripped.

When sensing current across the top FET, replace R_{sns} with the R_{dson} of the FET. This calculated R_{lim} value guarantees that the minimum current limit will not be less than I_{max} . It is recommended that a 1% tolerance resistor be used.

When sensing across the top FET, R_{dson} will show more variation than a current sense resistor, largely due to temperature. R_{dson} will increase proportional to temperature according to a specific temperature coefficient. Refer to the manufacturer's datasheet to determine the range of R_{dson} values over operating temperature or see the **COMPONENT SELECTION** section for a calculation of maximum R_{dson} . This will prevent R_{dson} variations from prematurely setting off the current limit comparator as the operating temperature increases.

Output Capacitor Selection (C8, C9, C22 and C23)

In applications that exhibit large and fast load current swings, the slew rate of such a load current transient may be beyond the response speed of the regulator. Therefore, to meet voltage transient requirements during worst-case load transients, special consideration should be given to output capacitor selection. The total combined ESR of the output capacitors must be lower than a certain value, while the total capacitance must be greater than a certain value. Also, in applications where the specification of output voltage regu-

lation is tight and ripple voltage must be low, starting from the required output voltage ripple will often result in fewer design iterations.

ALLOWED TRANSIENT VOLTAGE EXCURSION

The allowed output voltage excursion during a load transient (ΔV_{c_s}) is:

$$\Delta V_{c_s} = (\delta\% - \epsilon\%) \cdot V_{nom} - \frac{1}{2} V_{rip} \quad (7)$$

Where $\pm\delta\%$ is the output voltage regulation window and $\pm\epsilon\%$ is the output voltage initial accuracy.

Example: $V_{nom} = 5V$, $\delta\% = 7\%$, $\epsilon\% = 3.4\%$, $V_{rip} = 40mV$ peak to peak.

$$\begin{aligned} \Delta V_{c_s} &= (7\% - 3.4\%) \times 5V - \frac{40 mV}{2} \\ &= 160 mV. \end{aligned} \quad (8)$$

Since the ripple voltage is included in the calculation of ΔV_{c_s} , the inductor ripple current should not be included in the worst-case load current excursion. That is, the worst-case load current excursion should be simply maximum load current change specification, ΔI_{c_s} .

MAXIMUM ESR CALCULATION

Unless the rise and fall times of a load transient are slower than the response speed of the control loop, if the total combined ESR (R_e) is too high, the load transient requirement will not be met, no matter how large the capacitance.

The maximum allowed total combined ESR is:

$$R_{e_max} = \frac{\Delta V_{c_s}}{\Delta I_{c_s}} \quad (9)$$

Example: $\Delta V_{c_s} = 160mV$, $\Delta I_{c_s} = 3A$. Then $R_{e_max} = 53.3m\Omega$.

Maximum ESR criterion can be used when the associated capacitance is high enough, otherwise more capacitors than the number determined by this criterion should be used in parallel.

MINIMUM CAPACITANCE CALCULATION

In a switch mode power supply, the minimum output capacitance is typically dictated by the load transient requirement. If there is not enough capacitance, the output voltage excursion will exceed the maximum allowed value even if the maximum ESR requirement is met. The worst-case load transient is an unloading transient that happens when the input voltage is the highest and when the present switching cycle has just finished. The corresponding minimum capacitance is calculated as follows:

$$C_{min} = \frac{L \cdot [\Delta V_{c_s} - \sqrt{(\Delta V_{c_s})^2 - (\Delta I_{c_s} \cdot R_e)^2}]}{V_{nom} \cdot R_e^2} \quad (10)$$

Notice it is already assumed the total ESR, R_e , is no greater than R_{e_max} , otherwise the term under the square root will be a negative value. Also, it is assumed that L has already been selected, therefore the minimum L value should be

Output Capacitor Selection (C8, C9, C22 and C23) (Continued)

calculated before Cmin and after Re (see Inductor Selection below). Example: Re = 20mΩ, Vnom = 5V, ΔVc_s = 160mV, ΔIc_s = 3A, L = 8μH

$$C_{\min} = \frac{8 \mu\text{H} \cdot [160 \text{ mV} - \sqrt{(160 \text{ mV})^2 - (3\text{A} \times 20 \text{ m}\Omega)^2}]}{5 \times (20 \text{ m}\Omega)^2}$$

$$= 47 \mu\text{F}.$$
(11)

Generally speaking, Cmin decreases with decreasing Re, ΔIc_s, and L, but with increasing Vnom and ΔVc_s.

Inductor Selection

The size of the output inductor (L1 and L2) can be determined from the desired output ripple voltage, Vrip, and the impedance of the output capacitors at the switching frequency. The equation to determine the minimum inductance value is as follows:

$$L_{\min} = \frac{V_{\text{in}} - V_{\text{nom}}}{f \cdot V_{\text{in}}} \cdot \frac{V_{\text{nom}} \cdot R_e}{V_{\text{rip}}}$$
(12)

In the above equation, Re is used in place of the impedance of the output capacitors. This is because in most cases, the impedance of the output capacitors at the switching frequency is very close to Re. In the case of ceramic capacitors, replace Re with the true impedance.

Example: Vin (max) = 30V, Vnom = 5.0V, Vrip = 40mV, Re = 20mΩ, f = 300kHz

$$L_{\min} = \frac{30\text{V} - 5.0\text{V}}{300 \text{ kHz} \cdot 30\text{V}} \cdot \frac{5.0\text{V} \cdot 20 \text{ m}\Omega}{40 \text{ mV}}$$

$$L_{\min} = 7 \mu\text{H}$$
(13)

Lmin = 7μH

The actual selection process usually involves several iterations of all of the above steps, from ripple voltage selection, to capacitor selection, to inductance calculations. Both the highest and the lowest input and output voltages and load transient requirements should be considered. If an inductance value larger than Lmin is selected, make sure that the Cmin requirement is not violated.

Priority should be given to parameters that are not flexible or more costly. For example, if there are very few types of capacitors to choose from, it may be a good idea to adjust the inductance value so that a requirement of 3.2 capacitors can be reduced to 3 capacitors.

Since inductor ripple current is often the criterion for selecting an output inductor, it is a good idea to double-check this value. The equation is:

$$I_{\text{rip}} = \frac{(V_{\text{in}} - V_{\text{nom}})}{f \cdot L} \cdot D$$
(14)

Also important is the ripple content, which is defined by Irip /Inom. Generally speaking, a ripple content of less than 50% is ok. Larger ripple content will cause too much loss in the inductor.

Example: Vin = 12V, Vnom = 5.0V, f = 300kHz, L = 8μH

$$I_{\text{rip}} = \frac{12\text{V} - 5.0\text{V}}{300 \text{ kHz} \cdot 8 \mu\text{H}} \cdot \frac{5.0\text{V}}{12\text{V}} = 1.22\text{A}$$
(15)

Given a maximum load current of 3A, the ripple content is 1.2A / 3A = 40%.

When choosing the inductor, the saturation current should be higher than the maximum peak inductor current and the RMS current rating should be higher than the maximum load current.

Input Capacitor Selection

The LM2642 eval. board provides 5 input capacitor options for each channel (C5, C6, C28, C29, C32 and C16, C17, C30, C31, C33). Referring to Table 2, two capacitors are used on each channel and their placement depends on the method of current sensing. C6 and C16 can be installed when higher input capacitances are necessary.

The fact that the two switching channels of the LM2642 are 180° out of phase will reduce the RMS value of the ripple current seen by the input capacitors. This will help extend input capacitor life span and result in a more efficient system. Input capacitors must be selected that can handle both the maximum ripple RMS current at highest ambient temperature as well as the maximum input voltage. In applications in which output voltages are less than half of the input voltage, the corresponding duty cycles will be less than 50%. This means there will be no overlap between the two channels' input current pulses. The equation for calculating the maximum total input ripple RMS current for duty cycles under 50% is:

$$I_{\text{irrm}} = \sqrt{I_1^2 D_1 (1 - D_1) + I_2^2 D_2 (1 - D_2) - 2 I_1 I_2 D_1 D_2}$$
(16)

where I1 is maximum load current of Channel 1, I2 is the maximum load current of Channel 2, D1 is the duty cycle of Channel 1, and D2 is the duty cycle of Channel 2.

Example: Imax_1 = 3.6A, Imax_2 = 3.6A, D1 = 0.42, and D2 = 0.275

$$I_{\text{irrm}} = \left[(3.6\text{A})^2 \cdot 0.42 \cdot (1 - 0.42) + (3.6\text{A})^2 \cdot 0.275 \cdot (1 - 0.275) - 2 \cdot 3.6\text{A} \cdot 3.6\text{A} \cdot 0.42 \cdot 0.275 \right]^{.5}$$

$$= 2.75\text{A}.$$
(17)

Choose input capacitors that can handle 2.75A ripple RMS current at highest ambient temperature. In applications where output voltages are greater than half the input voltage, the corresponding duty cycles will be greater than 50%, and there will be overlapping input current pulses. Input ripple current will be highest under these circumstances. The input RMS current in this case is given by:

$$I_{\text{irrm}} = \left[\left[I_1 (1 - D_1) + I_2 (1 - D_2) \right]^2 (D_1 + D_2 - 1) + \left[I_1 (1 - D_1) - I_2 (D_2) \right]^2 (1 - D_2) + \left[I_2 (1 - D_2) - I_1 (D_1) \right]^2 (1 - D_1) \right]^{.5}$$
(18)

Where, again, I1 and I2 are the maximum load currents of channel 1 and 2, and D1 and D2 are the duty cycles. This equation should be used when both duty cycles are expected to be higher than 50%.

Input Capacitor Selection (Continued)

Input capacitors must meet the minimum requirements of voltage and ripple current capacity. The size of the capacitor should then be selected based on hold up time requirements. Bench testing for individual applications is still the best way to determine a reliable input capacitor value. The input capacitor should always be placed as close as possible to the current sense resistor or the drain of the top FET.

MOSFET Selection

BOTTOM FET SELECTION (Q2 AND Q4)

During normal operation, the bottom FET is switching on and off at almost zero voltage. Therefore, only conduction losses are present in the bottom FET. The most important parameter when selecting the bottom FET is the on resistance ($R_{ds(on)}$). The lower the on resistance, the lower the power loss. The bottom FET power loss peaks at maximum input voltage and load current. The equation for the maximum allowed on resistance at room temperature for a given FET package, is:

$$R_{ds(on)_{max}} = \frac{1}{I_{max}^2 \cdot \left(1 - \frac{V_{nom}}{V_{in_{max}}}\right)} \times \frac{T_{j_{max}} - T_{a_{max}}}{\left[1 + TC \cdot (T_{j_{max}} - 25^{\circ}C/W)\right] \cdot R_{\theta ja}} \quad (19)$$

where $T_{j_{max}}$ is the maximum allowed junction temperature in the FET, $T_{a_{max}}$ is the maximum ambient temperature, $R_{\theta ja}$ is the junction-to-ambient thermal resistance of the FET, and TC is the temperature coefficient of the on resistance which is typically in the range of 10,000ppm/°C.

If the calculated $R_{ds(on)_{max}}$ is smaller than the lowest value available, multiple FETs can be used in parallel. This effectively reduces the I_{max} term in the above equation, thus reducing $R_{ds(on)}$. When using two FETs in parallel, multiply the calculated $R_{ds(on)_{max}}$ by 4 to obtain the $R_{ds(on)_{max}}$ for each FET. In the case of three FETs, multiply by 9.

$$R_{ds_{max}} = \frac{1}{(3.6A)^2 \cdot \left(1 - \frac{5V}{30V}\right)} \times \frac{100^{\circ}C - 60^{\circ}C}{\left[1 + 0.01/^{\circ}C \cdot (100^{\circ}C - 25^{\circ}C)\right] \cdot 60^{\circ}C/W} = 35.3 m\Omega \quad (20)$$

If the selected FET has an R_{ds} value higher than 35.3Ω, then two FETs with an $R_{ds(on)}$ less than 141mΩ (4 x 35.3mΩ) can be used in parallel. In this case, the temperature rise on each FET will not go to $T_{j_{max}}$ because each FET is now dissipating only half of the total power.

TOP FET SELECTION (Q1 AND Q3)

The top FET has two types of losses: switching loss and conduction loss. The switching losses mainly consist of crossover loss and bottom diode reverse recovery loss. Since it is rather difficult to estimate the switching loss, a general starting point is to allot 60% of the top FET thermal

capacity to switching losses. The best way to precisely determine switching losses is through bench testing. The equation for calculating the on resistance of the top FET is thus:

$$R_{ds_{max}} = \frac{V_{in_{min}} \cdot .4}{I_{max}^2 \cdot V_{nom}} \times \frac{T_{j_{max}} - T_{a_{max}}}{\left[1 + TC \cdot (T_{j_{max}} - 25^{\circ}C/W)\right] \cdot R_{\theta ja}} \quad (21)$$

Example: $T_{j_{max}} = 100^{\circ}C$, $T_{a_{max}} = 60^{\circ}C$, $R_{\theta ja} = 60^{\circ}C/W$, $V_{in_{min}} = 4.5V$, $V_{nom} = 5V$, and $I_{load_{max}} = 3.6A$.


$$R_{ds_{max}} = \frac{5.5V \times .4}{(3.6A)^2 \times 5V} \times \frac{100^{\circ}C - 60^{\circ}C}{\left[1 + 0.01/^{\circ}C \cdot (100^{\circ}C - 25^{\circ}C)\right] \cdot 60^{\circ}C/W} = 13 m\Omega \quad (22)$$

When using FETs in parallel, the same guidelines apply to the top FET as apply to the bottom FET.

Loop Compensation

The general purpose of loop compensation is to meet static and dynamic performance requirements while maintaining stability. Loop gain is what is usually checked to determine small-signal performance. Loop gain is equal to the product of control-output transfer function and the output-control transfer function (the compensation network transfer function). Generally speaking it is a good idea to have a loop gain slope that is -20dB/decade from a very low frequency to well beyond the crossover frequency. The crossover frequency should not exceed one-fifth of the switching frequency, i.e. 60kHz in the case of LM2642. The higher the bandwidth is, the faster the load transient response speed will potentially be. However, if the duty cycle saturates during a load transient, further increasing the small signal bandwidth will not help. Since the control-output transfer function usually has very limited low frequency gain, it is a good idea to place a pole in the compensation at zero frequency, so that the low frequency gain will be relatively large. A large DC gain means high DC regulation accuracy (i.e. DC voltage changes little with load or line variations). The rest of the compensation scheme depends highly on the shape of the control-output plot.


Loop Compensation (Continued)

 

20047430

FIGURE 6. Control-Output Transfer Function

As shown in *Figure 6*, the control-output transfer function consists of one pole (f_p), one zero (f_z), and a double pole at f_n (half the switching frequency). The following can be done to create a -20dB/decade roll-off of the loop gain: Place the first pole at 0Hz, the first zero at f_p , the second pole at f_z , and the second zero at f_n . The resulting output-control transfer function is shown in *Figure 7*.

 

20047431

FIGURE 7. Output-Control Transfer Function

The control-output corner frequencies, and thus the desired compensation corner frequencies, can be determined approximately by the following equations:

$$f_z = \frac{1}{2\pi R_o C_o} \quad (23)$$

$$f_p = \frac{1}{2\pi R_o C_o} + \frac{.5}{2\pi L f C_o} \quad (24)$$

Since f_p is determined by the output network, it will shift with loading (R_o). It is best to use a minimum load value of approximately 100mA when determining the maximum R_o value.

Example: $R_e=20\text{m}\Omega$, $C_o=100\mu\text{F}$, $R_{\text{omax}}=5\text{V}/100\text{mA}=50\Omega$:

$$f_z = \frac{1}{2\pi \cdot 20\text{m}\Omega \cdot 100\mu\text{F}} = 80\text{kHz} \quad (25)$$

$$f_{p\text{ min}} = \frac{1}{2\pi \cdot 50\Omega \cdot 100\mu\text{F}} + \frac{.5}{2\pi \cdot 300\text{k} \cdot 8\mu \cdot 100\mu\text{F}} = 363\text{Hz} \quad (26)$$

First determine the minimum frequency ($f_{p\text{min}}$) of the pole across the expected load range, then place the first compensation zero at or below that value. Once $f_{p\text{min}}$ is determined, R_{c1} (**R23** and **R24**) should be calculated using:

$$R_{c1} = \frac{B}{g_m} \left(\frac{R_1 + R_2}{R_1} \right) \quad (27)$$

Where B is the desired gain in V/V at f_p (f_{z1}), g_m is the transconductance of the error amplifier, and R_1 and R_2 are the feedback resistors. A gain value around 10dB (3.3v/v) is generally a good starting point.

Example: $B=3.3\text{v/v}$, $g_m=650\text{m}$, $R_1=20\text{k}\Omega$, $R_2=60.4\text{k}\Omega$:

$$R_{c1} = \frac{3.3}{650\mu} \left(\frac{20\text{k} + 60.4\text{k}}{20\text{k}} \right) = 20.4\text{k}\Omega \cong 20\text{k}\Omega \quad (28)$$

Bandwidth will vary proportional to the value of R_{c1} . Next, C_{c1} (**C19** and **C20**) can be determined with the following equation:

$$C_{c1} = \frac{1}{2\pi \cdot f_{p\text{ min}} \cdot R_{c1}} \quad (29)$$

Example: $f_{p\text{min}}=363\text{Hz}$, $R_{c1}=20\text{k}\Omega$:

$$C_{c1} = \frac{1}{2\pi \cdot 363\text{Hz} \cdot 20\text{k}\Omega} \cong 22\text{nF} \quad (30)$$

The compensation network (*Figure 8*) will also introduce a low frequency pole which will be close to 0Hz.

A second pole should also be placed at f_z . This pole can be created with a single capacitor C_{c2} (**C18** and **C21**) and a shorted R_{c2} (see *Figure 8*). The minimum value for this capacitor can be calculated by:

$$C_{c2\text{ min}} = \frac{1}{2\pi \cdot f_z \cdot R_{c1}} \quad (31)$$

C_{c2} may not be necessary, however it does create a more stable control loop. This is especially important with high load currents and in current sharing mode.

Example: $f_z=80\text{kHz}$, $R_{c1}=20\text{k}\Omega$:

$$C_{c2\text{ min}} = \frac{1}{2\pi \cdot 80\text{kHz} \cdot 20\text{k}\Omega} \cong 100\text{pF} \quad (32)$$

A second zero can also be added with a resistor in series with C_{c2} (**R22** and **R25**). If used, this zero should be placed at f_n , where the control to output gain rolls off at -40dB/dec. Generally, f_n will be well below the 0dB level and thus will have little effect on stability. R_{c2} can be calculated with the following equation:

Loop Compensation (Continued)

$$R_{c2} = \frac{1}{2\pi \cdot f_n \cdot C_{c2}} \quad (33)$$



 


FIGURE 8. Compensation Network

 

Top Layer

FIGURE 9.

 

20047404

Bottom Layer

FIGURE 10.

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.



National Semiconductor
Americas Customer
Support Center
Email: new.feedback@nsc.com
Tel: 1-800-272-9959

www.national.com

National Semiconductor
Europe Customer Support Center
Fax: +49 (0) 180-530 85 86
Email: europe.support@nsc.com
Deutsch Tel: +49 (0) 69 9508 6208
English Tel: +44 (0) 870 24 0 2171
Français Tel: +33 (0) 1 41 91 8790

National Semiconductor
Asia Pacific Customer
Support Center
Email: ap.support@nsc.com

National Semiconductor
Japan Customer Support Center
Fax: 81-3-5639-7507
Email: jpn.feedback@nsc.com
Tel: 81-3-5639-7560