

LM2623 Evaluation Board

National Semiconductor
Application Note 1274
January 2004




The LM2623 is a general purpose, gated oscillator based, DC/DC boost converter that can run from low input voltage and produce a regulated output voltage with low ripple. The LM2623 evaluation board is programmed for a 5V output running off a two-cell power supply. For more information

regarding the LM2623, please refer to the data sheet, Application Note AN-1258, as well as the cookbook (AN-1221) for more application configurations. A bill of material and a schematic follow:


TABLE 1. Bill of Materials

Designator	Description	Manufacturer	Model Number
U1	LM2623 DC-DC Converter MSOP-8	National Semiconductor	LM2623
L1	Inductor (4.7µH 20% 2A)	Coilcraft	DO1813P-472HC
C1	Input Capacitor (220µF Tantalum Capacitor (20% 6.3V))	Vishay - Sprague	595D227X06R3C2
C2	Output Capacitor (100µF Tantalum Capacitor (10%, 6.3V))	Vishay - Sprague	293D107X96R3C2T
D1	Output Diode (40V 3A Schottky)	OnSemi	MBRS340T3
RF2	100 kΩ Feedback Resistor	Vishay - Dale	CRCW06031003F
RF1	300 kΩ Feedback Resistor	Vishay - Dale	CRCW06033003F
R3	150 kΩ Frequency Set Resistor	Vishay - Dale	CRCW06031503F
C3	4.7pF Ceramic Capacitor	TDK	C1608C0G1H4R7C

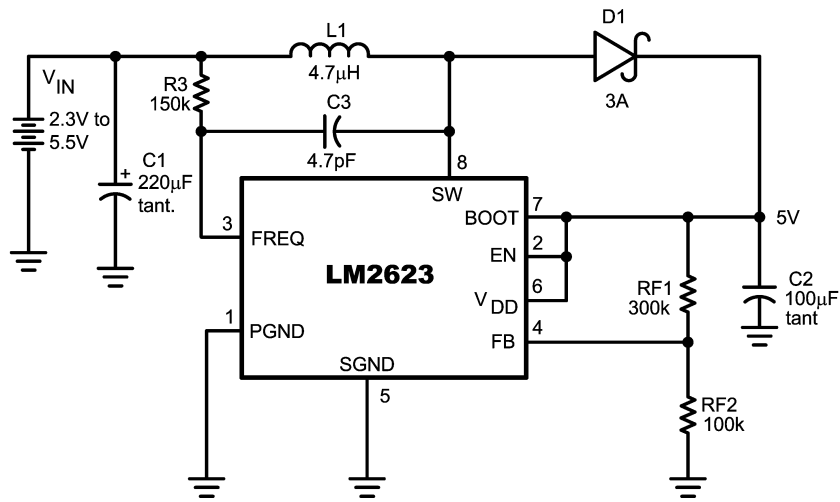

Two Cell to 5V Converter

20065204

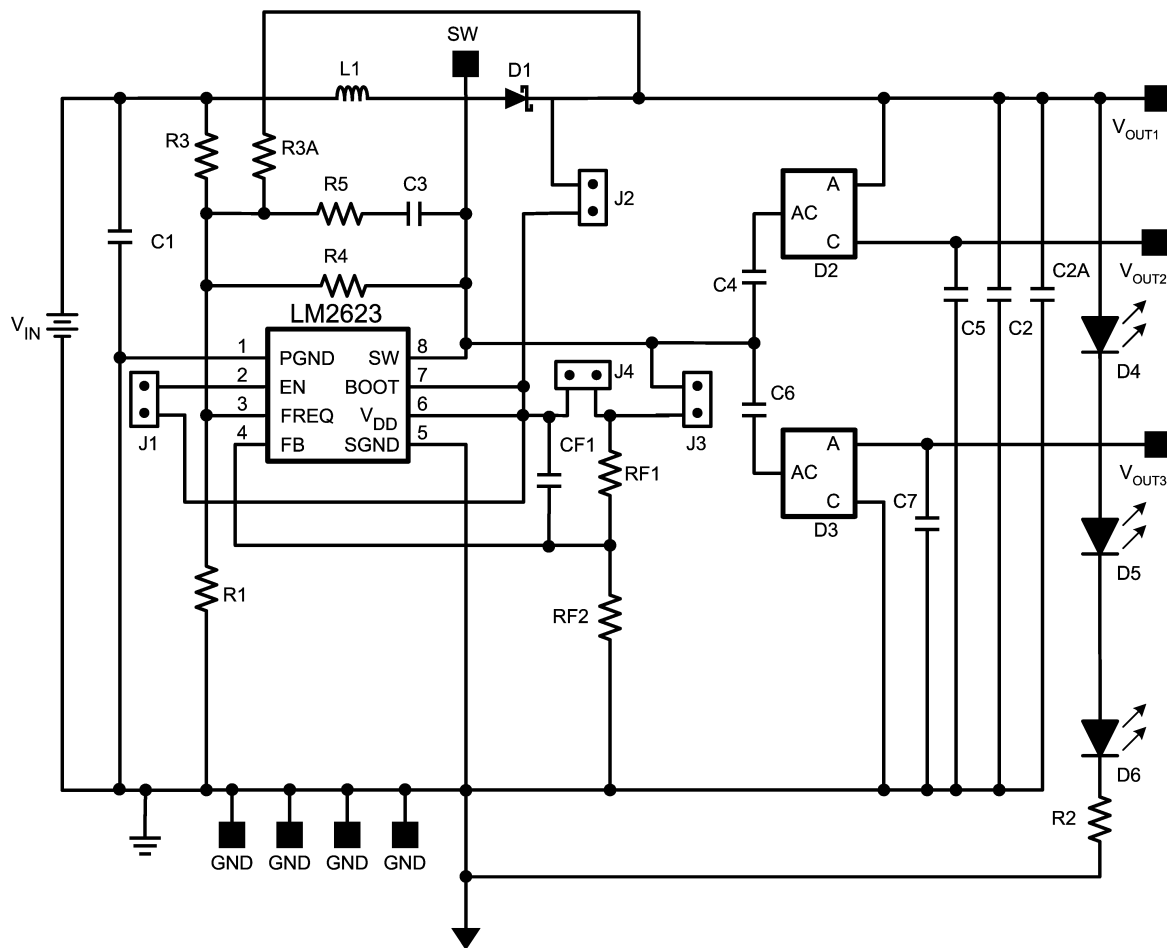


Application Board Circuit Diagram

20065201


Within the Application Board Circuit Diagram there are many components shown that are not populated on the 5V output evaluation board. These component footprints are used in

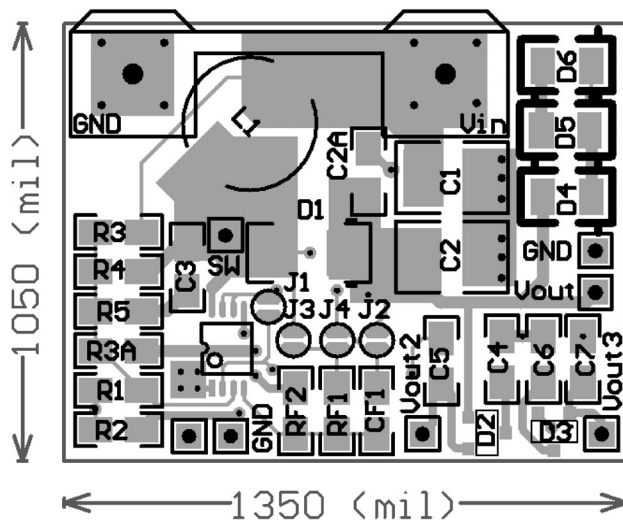numerous other applications found in application note AN-1221. In addition, jumpers J1, J2, and J4 are closed on the two-cell input to 5V output application board.



Typical Layout, Top View

20065202

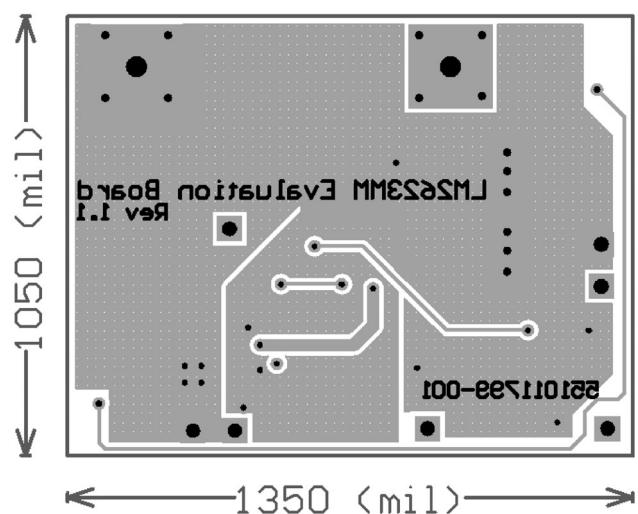

Bottom View Unmirrored

20065203

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

BANNED SUBSTANCE COMPLIANCE

National Semiconductor certifies that the products and packing materials meet the provisions of the Customer Products Stewardship Specification (CSP-9-111C2) and the Banned Substances and Materials of Interest Specification (CSP-9-111S2) and contain no "Banned Substances" as defined in CSP-9-111S2.



National Semiconductor
Americas Customer
Support Center
Email: new.feedback@nsc.com
Tel: 1-800-272-9959

www.national.com

National Semiconductor
Europe Customer Support Center
Fax: +49 (0) 180-530 85 86
Email: europe.support@nsc.com
Deutsch Tel: +49 (0) 69 9508 6208
English Tel: +44 (0) 870 24 0 2171
Français Tel: +33 (0) 1 41 91 8790

National Semiconductor
Asia Pacific Customer
Support Center
Email: ap.support@nsc.com

National Semiconductor
Japan Customer Support Center
Fax: 81-3-5639-7507
Email: jpn.feedback@nsc.com
Tel: 81-3-5639-7560