

NUTS & VOLTS

MAGAZINE



\$3.50
VOL. 18 NO. 1
JANUARY 1997

Exploring Electronics And Technology For The Hobbyist And Professional

**How
Much
Scope Is
Enough?**

**The DC Volt
Quick Tracey
Solar Workshop
Family Radio Service
RS-232 Digital Input/Output
Industrial Strength Motor Controller
H/Q Linear Power Supply For Automotive Electronics**



PicStic™

The New Standard in Component Computers

TAKE THIS HARDWARE:

- EEPROM-programmable PIC processor
- 19 bits of parallel I/O
- 16 Kb expanded data memory
- 4-channel, 8-bit ADC
- 2-channel, 12-bit ADC
- Real-time clock
- 2-channel, 12-bit DAC

ADD THESE FIRMWARE FUNCTIONS:

- ADC, DAC, clock, and expanded memory management
- 4 x 6 keypad scanning
- Frequency measurement
- Vinst, Vmax, Vmin, and Vavg monitoring
- Parallel printer output
- Parallel expansion via shift register
- Dallas Semiconductor iButton™ S/N reader
- 4 x 20 LCD display control
- Event counter
- PWM output (continuous)

AND YOU GET OUR ALL NEW



[shown actual size]

PicStic4 takes "component computers" to a new dimension. Packaged as an enclosed 32-pin DIP, PicStic4 combines the speed and economy of our original PicStics with sophisticated functions normally only available on our high-end SBC controllers. PicStic4 joins a user-programmable PIC and a powerful I/O coprocessor in one package. Program PicStic4 with our PicBasic compiler and you get BASIC Stamp compatibility with a 15 times increase in execution speed. Whatever the programming language, PicStic4 still gives you more digital I/O, both 8- and 12-bit analog, more data memory, a real-time clock, and a powerful set of firmware functions, all intended to provide the easiest control solution.

ORDER NOW:

PS4-P	includes all firmware functions, extra data memory, parallel I/O, and 8-bit analog inputs	\$59
PS4-Q	includes all functions in -P device, plus real-time clock and 2-channel, 12-bit ADC	\$69
PS4-X	includes all functions in -P and -Q devices, plus 2-channel, 12-bit DAC	\$79
PS4-DEV	Developer package. Includes PicBasic compiler, PicBasic programmer's manual, PicStic4 programmer w/ZIF socket, and power supply. (PicStic1-3 development systems can be upgraded for a nominal charge)	\$179

WHAT ARE PicStics?

PicStics (PS1-PS3) are component-sized BASIC Stamp™ 1 pin-compatible computers. They are primarily designed to run with PicBasic, but you can also use C or PIC assembly. They have 8 to 10 I/O lines and optional real-time clock or 2-channel, 12-bit ADC. Using a comfortable language like BASIC, program development simply involves typing a program into a PC and downloading the compiled code into PicStic's nonvolatile memory. Programs remain indefinitely, unless changed. PicStic 1 is \$29. PicStic 2 and 3 are \$39.

The PicStic4 is the next evolutionary step. It has more memory, parallel and analog I/O, and preprogrammed functions.

VISIT OUR WEB SITE FOR A COMPLETE DATA SHEET CALL 1-800-635-3355 TO ORDER



MICROMINT, INC.

4 Park Street • Vernon, CT 06066 • Tel: (860) 871-6170 • Fax: (860) 872-2204 • <http://www.micromint.com/>

in Europe: (44) 1285-658122 • in Canada: (514) 336-9426 • **Distributor Inquiries Welcome!**

BASIC Stamp® is a trademark of Parallax Inc. iButton is a trademark of Dallas Semiconductor Corp. PicStic™ is a trademark of Micromint Inc.

HSC Electronic Supply

Serving
Silicon Valley
since 1964!

...brings you a potpourri of high-tech goodies for the techno-tinkerer!
For thirty years we have been your source for Silicon Valley exotica!

Save with Monitor Miser!

- Monitor Miser turns your monitor off when not in use!
- Plugs into keyboard port to detect activity
- User selectable time interval, from 10 to 42 minutes
- Get EPA "Energy Star" compliance for older monitors
- Measures 4.5" x 3" x 1.5" with generous cables, adaptor
- New in box, ninety day warranty

HSC#16278

\$17.50

Orchid MPEG + Video!

- Orchid Technology Kelvin MPEG Video Card
- 64-bit graphics with MPEG Video on one card!
- Full screen 30 Frames/sec MPEG video plus audio
- 1MB version will display up to 800 x 600, 64K colors, or 1024 x 768, 256 colors
- Manual, audio cable & driver software included
- Note, the MPEG portion is not Win95 compatible, but the video portion is. Everything works fine with Windows 3.1
- OEM pack (plain white box) Ninety day HSC warranty

HSC# 16124

\$69.00

104-key Win95 Keyboard

- Superior quality in a Win95 compatible keyboard!
- Hewlett Packard part #5182-5521
- 104-key keyboard has special Win95 keys
- Attractive grey-beige finish,
- PS/2 style connector (mini-DIN)
- New, no box, 90-day warranty
- Similar to illustration

HSC#16275

\$19.95.

Peltier Cooler at a Price!

- Made for cooling ceramic Pentium Processors (not metal)
- Heatsink is 2" x 2.875", .5" thick
- Mounted 12VDC fan
- Peltier device is 1.125" square, has copper plate for thermal mounting on CPU
- Unit is new, and much cheaper than the separate parts!
- Perfect for Peltier experiments!

HSC# 16106

\$24.95

Rock-Bottom Reno!

- This is the Last Stock of Media Vision Reno:
- Consists of new external Reno CD-ROM drive, docking bay with SCSI2 port, AC Adapter, cables
- Uses NiCad battery pack(s), not included
- Double-speed 180MS drive is lightning fast!
- Drive detaches from docking bay, use with headphones as a portable personal audio CD player
- Great for Mac or IBM (adaptor bracket included)
- Mac software included
- SCSI Controller & software required for IBM use
- Brand new, 90-day warranty

Media Vision Reno Kit HSC#15586 includes:
Reno Cable Kit (SCSI2 - DB25 cable, 50p. ribbon cable, internal & external audio patch cables), padded travel pouch, headphones, Mac software, IBM Adapter bracket.



\$69.00

Available Separately:

- A. Rechargeable Battery Pack (for early-style Reno, will not recharge in late-model Reno) HSC#15587 \$14.95
- B. Macintosh Powerbook SCSI Adapter (HDI-30 to 25-pin D connector) HSC#15704 \$12.50 if purchased alone, or with purchase of Reno Kit, \$5.00

Yet Another Incredible 486 Motherboard Deal!

- The last deal sold out in record time, so we scoured the Valley for another 486 Motherboard bargain!
- Brand-new Micronics 486 VLB Motherboard (no CPU)
- Accepts up to a 486DX4-100 microprocessor
- On-board 2-port IDE / Floppy controller, 2 SIO, 1 PIO
- Three sixteen-bit ISA, one eight-bit, two VLB slots
- Three 72-pin SIMM memory sockets
- Phoenix BIOS with "Green" certification
- Sockets for cache RAM, no RAM chips included
- OEM white box with manual, serial/parallel brackets
- Mini size: 8.5" x 10" -- Ninety day warranty
- The last ones went fast -- Hurry before these are gone!

HSC#16255

\$34.95

486 Microprocessor Chip

- Intel 486DX33 chip -- usable in motherboard above
- HSC#16214 \$19.95 ea., or \$14.95 with 486 board above

Hand-Scanner Special!

- Logitech ScanMan 256-Bit Grayscale hand-scanner
- 100 - 400 dpi resolution, hardware (switch) selectable
- Factory Refurbished, 90-day warranty
- Includes Fototouch image acquiring & editing software, Omnipage OCR software
- Latest Windows 95 drivers included
- Comes with manuals, power supply, 16-bit interface card

HSC#15986

\$34.95

PCMCIA Card Reader

- IBM Compatible Reader/Writer for PCMCIA Cards
- SwapBox by SCM Microsystems with 16-bit ISA Bus card
- Convenient front access for slots (not in rear of system)
- Fits in 3.5" drive bay, or use included 5.25" bracket
- Dual slot, Type I, II or III, hot swappable
- Perfect for transferring data or hardware from laptops, notebooks or Kodak Cameras to desktop PCs
- Includes driver disk, manuals, cable, internal card, bracket
- New in OEM package (white box), 90-day warranty

HSC#15954

\$79.95

PCMCIA SCSI Card

- Mediavision PCMCIA SCSI II Card for Laptops
- Use with CD-ROM Drives, WORM Drives, Hard Drives, Scanners, any SCSI I or II device
- Bundled with Corel SCSI (ver. 2.04) software
- Cable, installation software, manual included
- Would make excellent laptop connection to Reno, above
- New in box with software, 90-day warranty

HSC# 15893

\$79.00

Hobby Parts Potpourri!

- Copper Foil Tape - .5" x 18 yd. roll, adhesive is conductive
- HSC#16189 \$4.95
- Karaoke-style microphone, good quality, black & gold
- HSC#16156 \$2.95
- Small flexy solar panel - 1.6VDC @ 350mA - 6" x 1.75"
- HSC#16133 \$5.95
- Desk stand microphone, multimedia-type, beige
- HSC#16157 \$5.95
- Nidec 12VDC tiny squirrel-cage blower, 3" x 3" x 1.125"
- HSC#16166 \$9.95
- Genuine IBM PS/2-style keyboard, 101 key
- HSC#16218 \$14.95
- Arcade game joystick (not for computers), 4 switches, Heavy duty! Choose red, blue, green, or black handle
- HSC#15227 \$6.95
- Coiled cigarette lighter extension cord, plug to jack
- HSC#15640 \$2.95

Give Your Computer Built-in Speakers!

- Save desk space, eliminate tangled wires!
- Suncom FX-2000, new in box, unbelievable value!
- Built-in 4-watt amplifiers punch up sound
- Compatible with any sound card
- Independent volume controls for left & right speaker
- Front-mounted jacks for microphone, headphones



HSC#16277

\$14.95

Joystick Extravaganza!

- Just in - joysticks for computer games!
- Suncom FX-2000, new in box, unbelievable value!
- Form fitting joysticks work with either hand
- Suction-cup feet anchor them for lightning fast action!
- New in box - 30 day warranty
- Hurry, they are going fast!

HSC#16212

Suncom FX-2000 Joystick \$3.95

Computer Remote Control - Click on this Special Price!



- Infrared Remote operates your computer from 50 feet
- Perfect for sales presentations, training, demonstrations
- Serial Interface (IBM version) or ADB (Mac version)
- Handheld remote is 7" x 2.5" x .5"
- Included software provides screen pointer for emphasis
- Keystroke mapping table can be customized, saved
- Room the room, make eye contact with your audience
- Like using a TV set remote control (easy to set-up, use)

HSC# 15240 IBM Remote Keyboard \$14.95

HSC# 15241 Mac Remote Keyboard \$14.95

3-D SCSI-2 Sound Card

- Mediavision Premium 3-D high-quality sound card
- 16-bit audio, 44.1KHz digitized stereo sound
- MPU 401 MIDI, Soundblaster compat., SRS 3-D circuitry
- Internal SCSI 2-CD-ROM port, microphone jack (mike not included), line-in, speaker jack, joystick port
- Includes driver disks, photocopied book
- OEM package (no box), 90-day warranty
- We had these and ran out...New Stock at Lower Price!

HSC#16164

\$39.95

House that Equipment!

- Beautiful, brand-new 19" rack cabinet!
- 29.5" tall, with room for 21" of vertical instrument height
- 23.25" wide, and 30" front-to-back, textured black finish
- Made by AMCO Engineering
- Units are new in box, strapped to skids, ready for truck shipment (cannot go UPS)
- Also available: Slide-out rail sets for convenient access to equipment (HSC# 16116, \$9.95)

HSC# 80398

\$149.00

FaxBoy for paperless FAX!

- High performance fax machine, saves space and paper!
- D2 FAX by Seponix with FaxBoy software uses 3.5" floppy disks rather than paper for input/output
- May be used as back-up to existing fax machine, or as a stand-alone fax (no need to leave computer on-line)
- Units are new in box with software, power supply, manuals
- Measures only 5" x 8" x 3.5"
- View and compose faxes on your computer, use top keypad to program unit and send faxes
- DOS, Windows 3.XX or Windows 95 compatible
- 90-day Warranty



HSC# 80400

\$59.95

SCSI Drive Case Deal!

- Low-profile case for 5.25" drives
- Perfect for CD-ROM drive
- 9.75" x 2.25" x 11" overall size
- 50-pin SCSI daisy-chain connectors
- Internal 50-pin cable, SCSI ID switch
- 30-watt power supply, DC Fan cooled
- New case is attractive grey color, has 90-day warranty

HSC# 16185 Low-Profile 5.25" Drive Case \$29.95

Tricky Tuned Mag-Switches!

- Ordinary magnetic switches used on doors and windows in security systems can be defeated by secretly placing another magnet next to the switch on the frame, where it doesn't move
- These government-spec. magnetic switches are carefully biased so that they only respond to their matched magnet.
- Box is 4.75" x 2.5" x 1.75", magnet is 4.75" x .5" x 1.75"
- Rugged die-cast box is gasketed, and has tamper switch
- New in box, buy six and save! Retail is over \$25 each!

HSC#16056

\$9.95 ea., or 6/\$50.00

Tape Backup Bargain!

- Irwin AccuTrak tape drives -- holds 250 Megabytes
- Brand new in box with 90-day warranty
- "Backup Exec" software for DOS/Windows 3.XX included
- Hooks to floppy controller with included insertion cable
- Comes with brackets and 5.25" faceplate for mounting in regular half-height drive bay, but can be mounted in 3.5" bay with optional faceplate below
- Made for IBM so you know it's rugged!
- Includes new 250MB unformatted tape (allow approx. 2 hours to format)

HSC#15805

\$39.95



-- Irwin Tape Backup Accessories --

3.5" Faceplate, Dark Gray HSC# 15808 \$2.95

HALTED
specialties co.

HSC

Electronic
Supply

Toll Free (Orders Only) 1-800-4 HALTED
Internet World Wide Web:
3500 Ryder St., Santa Clara, CA 95051
4837 Amber Ln., Sacramento, CA 95841
6819 Redwood Dr., Cotati, CA 94931

(1-800-442-5833)

http://www.halted.com

(408) 732-1573

(916) 338-2545

(707) 792-2277

FAX your orders to:

(408) 732-6428

Visit HSC's Website!

- HSC has a new presence on the Internet World Wide Web!
- Simply point your browser to http://www.halted.com
- Site is constantly being revised, please visit often!
- Specials and one-of-a-kind items not in our ads!

You can still subscribe to our e-mail "Mailing list", just send a posting to HSC-server@hsc.cue.com with the single line message: SUBSCRIBE HSCmail <full name>
You will get future unsolicited mailings. You can "Unsubscribe" at any time in the same manner.

http://www.halted.com

Terms: Some quantities limited; all items subject to prior sale. Minimum order: \$10.00 plus shipping. Orders under \$20.00 subject to \$2.00 handling fee, in addition to shipping. All orders shipped FOB Santa Clara, CA (this means you pay freight) by UPS Surface (no P.O. Boxes) unless otherwise specified, in which case prevailing carrier rate plus \$5.00 handling fee applies. Prepaid orders that don't include shipping charges will be shipped freight COD. There is a \$4.75 UPS charge added to shipping charges for COD shipments. If you have questions about your order, please call Customer Service at (408) 732-1854 M-F 9AM to 5PM PST.

NUTS & VOLTS MAGAZINE

Published Monthly By
T & L Publications, Inc.
430 Princeland Court
Corona, CA 91719
(909) 371-8497
FAX (909) 371-3052

E-Mail
editor@nutsvolts.com
URL
http://www.nutsvolts.com

Subscription
Order ONLY Line
1-800-783-4624

Publisher
Jack Lemieux
N6ZTD

Editor
Larry Lemieux
KD6UWV

Managing Editor
Robin Nelson
KD6UWS

On-The-Road Exhibit
Coordinator
Audrey Lemieux
N6VXW

Subscriptions
Abby Madain

Classified Ads
Lisa Wharton

Copyright 1997
by T & L Publications, Inc.
All Rights Reserved

NOTICE TO ADVERTISERS

All advertising is subject to publisher's approval. We are not responsible for mistakes, misprints or typographical errors. Nuts & Volts Magazine assumes no responsibility for the availability or condition of advertised items or for the honesty of the advertiser. The publisher makes no claims for the legality of any item advertised in Nuts & Volts. This is the sole responsibility of the advertiser. Advertisers and their agencies agree to indemnify and protect the publisher from any and all claims, action or expense arising from advertising placed in Nuts & Volts.

Please send all subscription orders, correspondence, UPS, overnight mail and artwork to: 430 Princeland Court, Corona, CA 91719.

The closing date for each issue is the 10th of the prior month, e.g., the closing date for the June issue is May 10th. Ad copy to be typeset by Nuts & Volts should be received one week prior to the closing date.

Call or write for current advertising rates.

CONTENTS

VOLUME 18 NO. 1 JANUARY 1997

ARTICLES

- A HIGH-QUALITY DESKTOP LINEAR POWER SUPPLY FOR AUTOMOTIVE ELECTRONICS** William C. Hendry IV 12
Construct this high-quality power supply for a fraction of the cost of those on the market.
- THE DC VOLT** Ron Tipton 20
Just what is a volt and how is it maintained? Discover answers to these questions, plus take a look at the search for more accurate methods of building a "standard volt."
- HOW MUCH SCOPE IS ENOUGH? — PART 2** Jeffrey Mazur 52
This series concludes with a discussion on digital storage scopes and information on a few specialty scopes.
- RS-232 DIGITAL INPUT/OUTPUT** Terry Weeder 63
Unlock your own programming potential via your serial port and this I/O module.
- BUILDING AN INDUSTRIAL STRENGTH MOTOR CONTROLLER ON A HOBBYIST BUDGET** Jeffrey Kerr 78
Get down to the brass tacks of building a servo motor control system at a reasonable price.
- QUICK TRACEY — SEMICONDUCTOR SLEUTH** Fred Blechman 95
Take the mystery out of determining if bargain semiconductors are good or bad with the help of your oscilloscope and "Quick Tracey."
- FAMILY RADIO SERVICE ON THE AIR!** Gordon West 113
"Tune in" to how you can utilize and enjoy this new personal radio service.

COLUMNS

- AMATEUR ROBOTICS** Karl Lunt 26
The best in robot soccer.
- OPEN CHANNEL** Joseph J. Carr K4IPV 107
Doing the numbers — or distributing saltwater taffy?
- RESOURCE BIN** Don Lancaster 89
Finding answers on the web.
- STAMP APPLICATIONS** Scott Edwards 71
Electronic control for DC motors using discrete bridge circuits.
- SOFTWARE WIZARDRY** Harry Helms 99
All about ActiveX components.
- THE NUTS & VOLTS SOLAR WORKSHOP** T.J. Byers 40
Building a small solar power plant, plus answers to frequently-asked questions.

DEPARTMENTS

- ADVERTISER'S INDEX** 116
- CLASSIFIED AD INFO** 116
- DEALER DIRECTORY** 87
- EVENTS CALENDAR** 35
- NEW PRODUCT NEWS** 34
- NV ADMART** 110
- ELECTRONICS Q & A** 48
- READER FEEDBACK** 6
- TECH FORUM** 84

To Subscribe to NUTS & VOLTS

Send payment to the address below or call 1-800-783-4624
and use your Visa or MasterCard.

USA ONLY

\$19.00 — One Year

\$35.00 — Two Years

MAILED FIRST CLASS — FOREIGN ONLY

\$37.00 — Canada/Mexico

\$100.00 — Foreign/Air Mail

\$50.00 — Foreign/Surface

Nuts & Volts Magazine, 430 Princeland Court, Corona, CA 91719

EDITORIAL CONTRIBUTIONS

Nuts & Volts Magazine encourages article submissions and queries. Send a SASE for a copy of our writer's guidelines.

All submissions should be on 5-1/4 or 3-1/2 inch diskettes and include hard copy as well. If return of materials is requested, include a SASE with your submission.

Deadlines should be discussed in advance with the editor, but generally all material should be submitted by the 1st of the month for the next month's issue.

CHANGE OF ADDRESS

If you are moving, notify us AS SOON AS POSSIBLE so we can continue your subscription without interruption.

Your magazine WILL NOT automatically be forwarded to you by the post office, so it's important to submit your change of address directly to Nuts & Volts.

We will not be able to replace missed issues of the magazine due to unreported address changes.

When you send in your new address, include a current mailing label from the magazine with your account number on it. If you do not have a mailing label, be sure to include your old address and the name(s) under which the subscription was submitted.

INDEX TO CLASSIFIED ADS

- 10. Ham Gear for Sale 5
- 20. Ham Gear Wanted 8
- 30. CB/Scanners 9
- 40. Music & Accessories 11
- 50. Computer Hardware 11
- 60. Computer Software 23
- 70. Computer Equip. Wanted 24
- 80. Test Equipment 25
- 85. Security 51
- 90. Satellite Equipment 56
- 95. Military Surplus Electronics 57
- 100. Audio/Video/Lasers 57
- 110. Cable TV 57
- 115. Telephone/Fax 59
- 120. Components 68
- 125. Microcontrollers 75
- 130. Antique Electronics 76
- 135. Aviation Electronics 76
- 140. Publications 82
- 145. Robotics 112
- 150. Plans/Kits/Schematics 82
- 155. Manuals/Schematics
Wanted 86
- 160. Misc. Electronics For Sale 86
- 170. Misc. Electronics Wanted 92
- 175. BBS & Online Services 104
- 180. Education 104
- 190. Business Opportunities 105
- 200. Repairs/Services 112

Nuts & Volts Magazine is published monthly for \$19.00 per year by T&L Publications, Inc., 430 Princeland Court, Corona, CA. Application to mail at 2nd class postage rates is pending at Corona and San Diego. POSTMASTER: Send address changes to Nuts & Volts Magazine, 430 Princeland Court, Corona, CA 91719.

HAM GEAR FOR SALE

ICOM 27H 2-mtr mobile "talking feature" \$185. Motorola Syntor X UHF 100 watt 420MHz \$200. GE Executive II 6-mtrs 65 watt \$75, 110 watt \$100. Motorola Micro VHF 45-60 watt \$50. Motorola Paging Bear 500 watt complete low band 6 mtrs \$1,000. Motorola Syntor X 860 trunking \$175. Regency VHF w/ program 16 ch., 15 watt \$85. PO Box 207, Bradenton, FL 34206. 813-238-4830. Call after Jan. 1, 1997.

NEW CATALOG, RF parts, shortwave kits, transceiver kits, iron powder and ferrite cores, hard to find parts, more. Two stamps to Dan's Small Parts, Box 3634, Missoula, MT 59806. Ph/Fax 406-258-2782. Online catalog <http://www.fix.net/dans.html>



LOW COST WSHFAX WEATHER FAX FOR PC/CLONES. This unit is featured in Chapter 5 of the Fifth Edition of the **WEATHER SATELLITE HANDBOOK**. It will process both HF and satellite weather FAX. For KIT order #200-KIT for \$159.95. For assembled unit order #200-ASY for \$189.95. Add \$6.50 S/H per order. Software is included. Tuning indicator available for \$30, compatible with JV FAX 7.0. Visa & MC accepted. For more information, send LSASE (55¢) to: A&A Engineering, 2521 W. La Palma #K, Anaheim, CA 92801. To order call, 714-952-2114. Fax 714-952-3280.

MILITARY COMPONENTS wanted. Capacitors, resistors, diodes, transistors, semiconductors, ICs. Electronic Material Industries, 818-842-5953, FAX: 818-845-3613.

When Visiting Disney World And Sea World... Come To The World Of Electronic Surplus!

SKYCRAFT

PARTS & SURPLUS, INC.
ORLANDO, FLORIDA



Located At The Intersection Of I-4
And Fairbanks Avenue.

A Self-Service Retail Outlet Featuring Commercial
And Government Electronic Surplus Including:

- ★ WIRE
- ★ SWITCHES
- ★ RESISTORS
- ★ TRANSISTORS
- ★ TRANSFORMERS
- ★ TEST EQUIPMENT
- ★ NI-CAD BATTERIES
- ★ COAX
- ★ RELAYS
- ★ HARDWARE
- ★ CAPACITORS
- ★ PANEL METERS
- ★ CIRCUIT BOARDS
- ★ INTEGRATED CIRCUITS

HOURS:

Monday - Friday 8:30-6:00
Saturday 8:30-5:00

★★★★★★★★

We Buy Surplus
Electronic Parts —
FAX your list.

FAX 407/647-4831

PH 407/628-5634

P.O. BOX 536186

ORLANDO, FLA. 32853-6186



WANTED: ROCKWELL HF-80 family equipment and accessories (i.e. 8020, 8054A, 8070A, 851S-1, etc.). Also need Rockwell 237A-3 or 237B-3, or antenna products LPH-1 or LPH-89, or higan #5000, 5001, 5002, or 5004 rotatable log periodic. Also looking for Collins or Rockwell literature. Jim Stitzinger 805-259-2011. bfi-jfs@smartlink.net

MORSE CODE computer interfaces \$49.95 with CW filter \$69.95 plus \$3 shipping. New DP-1 multiband antenna covers all ham bands from 80-2 meters \$129 + \$6 shipping. Free ham and IBM shareware catalog. Dynamic Electronics, Box 896, Hartselle, AL 35640, E-Mail dei@whnt19.com 205-773-2758, FAX 205-773-7295.

FACTORY NEW Wavetek RF portable power meter, complete system, 1990 price \$2,860. Our price \$575. 4 units available. Psitech Plus 707-745-4804, Fax 707-747-5277.

QUALITY PARTS at surplus prices. All new, never used distributor and OEM overstocks. Call IME, 817-561-2999 or write PO Box 170415, Arlington, TX 76003.

Accept Credit Cards and Increase Your Sales!

MasterCard, Visa, American Express, Discover

All Types of Businesses Considered

Why limit yourself to only customers with cash in their pocket or checking account? Accept credit cards and you open the door to the rest of the buying public!

Axin Financial Services, Inc.
will waive your sign-up fee!
(Limited time offer)

No sign-up fees if you act now!

Call or Fax for Free Info:

Jim Krause, Axin Financial Services, Inc.
Voice (800) 318-8304 Fax: (310) 690-5849

Axin Financial Services, Inc. A Registered ISO/MSP
of AmericanMidwest Bank & Trust, Rosemont, IL

Check Guarantee, ATM / Debit Card also available!
*American Express & Discover subject separate approval

Write in 73 on Reader Service Card.

COUNTERSURVEILLANCE MANUFACTURER

AI-6600

PHONE TAP DETECTOR

DETECTS:

- Radio Frequency Taps
- Series and Parallel Taps
- Line Impedance Taps
- Extension Phone Listeners



\$149⁹⁵

AI-2100

VIBRATING TRANSMITTER DETECTOR

DETECTS:

- Body Wires
- FM Wireless Mics
- AM Transmitters
- UHF Transmitters



\$189⁹⁵

AI-5500 COMPLETE SAFETY SYSTEM

DETECTS:

- All Phone Taps and Extension Phone Listeners
- All Body Wires, Wireless Mics, AM/FM and UHF Transmitters

DEFEATS:

- All Body Wires, Transmitters and Distance Microphones with its built-in white noise generator

\$379⁹⁵



TRVD-900 TRANSMITTER / TAPE RECORDER & VIDEO DETECTION SYSTEM

DETECTS:

- Body Wires • FM Wireless Mics
- AM Transmitters • UHF Transmitters
- Tape Recorders • Video Equipment

Alerts User By Vibrating and/or Illuminated LEDs



\$495⁰⁰

WSS-100 WIRELESS SURVEILLANCE SYSTEM SEES & HEARS EVERYTHING!

FEATURES:

- 2.4 GHz Video / Audio Transmitter
- 4 Channel Receiver • 300' Transmission Range
- Black & White CCD w/ Auto-Iris Lens • 410(H) TV Line Resolution
- FCC Approved Frequency



\$649⁹⁵

Send \$6.00
for 32-Page
Catalog
(FREE w/ Purchase)

Items May Be Purchased by Certified Check, Money Order or C.O.D.
AMERICAN INNOVATIONS, INC.

113 ROCKLAND CENTER - SUITE 315 - NANUET, NY 10954

VOICE: (914) 735-6127 • FAX: (914) 735-3560

HTTP://WWW.SPYSITE.COM • E-Mail: AMERICAN@SPYSITE.COM

Quantity
Discounts
Available

MO-TECH DISTRIBUTORS YOUR MIDWEST PANASONIC CONVERTER WHOLESALE

PANASONIC

10 PC 20 PC 50 PC

TZPC1453G2 \$63- \$61- \$59-

"Top of the line converter" featuring sleep timer, parental lock, standard/HRC switchable, last channel recall, favorite channel memory, and 83 channel capable.

TZPC1003 \$49- \$44- \$42-

One of our best selling converters featuring sleep timer, parental lock, last channel recall, favorite channel memory, and 80 channel capability.

TZPC175DG2 \$89- \$85- \$82-

Our "Top of the line" converter with volume control. Featuring sleep timer standard/HRC switchable, parental lock, last channel recall, favorite channel memory, and 83 channel capable.

PHONE (810) 566-7262
FAX (810) 566-7253

PIC Programmer Development Tools

- Programmer for PIC 16C5X, 16C6X, 16C7X, 16C84, and 17C4X in DIP packages.
- Conditional Assembler and Simulator.
- Emulates program memory, registers, and I/O for the PIC 16C5X.
- Instruction-level emulation for the PIC 16C71 and 16C84.
- Programmer only \$155. Complete package \$245. 15 day money-back guarantee.

Low cost Microcontroller Development Systems

80C552, 80C31, and 68HC11 development systems include single board computer, assembler, disassembler, real-time execution and debugging, monitor program, and examples.

ROMY-16 EPROM EMULATOR

Emulates ROM or RAM in 8- and 16-bit systems. \$195 (2716-27256) or \$245 (2716-27010). Window/menu driven interface. 15 day money-back guarantee.

J&M Microtek, Inc.

83 Seaman Road, W Orange, NJ 07052
Tel: (201) 325-1892 Fax: (201) 736-4567

Write in 217 on Reader Service Card.

EASY PIC'n MICROCONTROLLER BOOK

How to get started using PIC16CXX microcontrollers

- Programming techniques
 - Program design
 - Flow charts
 - Instruction set
 - Addressing modes
 - Bit manipulation
 - Subroutines
 - Sequencing
 - Lookup tables
 - Interrupts
- Writing source code using a text editor
- Using an assembler
- Interfacing
 - Circuits
 - I/O conversion
- Timing and counting
- Using a PIC16/17 programmer
- Experiments
- Lots of examples

PIC is a trademark of Microchip Technology Inc. in USA

\$29.95 + \$3 mail in US VISA, MC, MO, Check
CA residents please add 7.25% CA sales tax

SQUARE 1
ELECTRONICS

P.O. Box 501, Kelseyville, CA 95451
Voice (707) 279-8881
FAX (707) 279-8883
http://www.zapcom.net/~squareone

reader FeedBack

Dear Nuts & Volts:

First, I would like to say thanks for a super magazine, I look forward to reading it every month!

I would like to respond to the NC sidebar. I think Harry is way off his mark on how the NC can compare to the PC, in reality, there is NO comparison; the NC is NOT a personal computer, nor will it ever be. In the short, it is a web browser in a box, and in the long run it is a dumb terminal. It is not geared for the home user. It will work there, but it is not meant for there. It was thought out as a replacement to the desktop computer located in the offices of the world.

Consider this, 95% of all support problems are software related (i.e., Microsoft, for the simple fact that it has 90% of the market). If you remove this problem (software from MS) 90% of the problems will magically go away!

Take this one step farther, you remove the remaining 5% of the problems (hardware and compatibility) and you are left with a VERY solid computing environment. With drop-in replacement of hardware, you are looking at a 95% reliable system, with a VERY low down time, maybe 10 minutes to replace the tube with another tube.

Now multiply these factors by 1,000. The average number of computers in a large corporate structure, and the savings are staggering. Combine this with personnel reduction (I know that sucks, but a dollar is a dollar), software unification, and the most important aspect, single point of failure. And from the large com-

puter companies (i.e., IBM, Unisys, and Fujitsu) this is a wonderful time to swing in, tell the companies "We'll remove all your PCs, replace them with NCs, run new cables to handle voice, data, and video, ability to connect each desk with the Internet, and give you a new mainframe computers or minis (as/400) and a very small team of our techs (three-five) and all you have to do is pay X number of dollars a year, and you will have a guaranteed 24x7x365 system." Any company would be a fool not to take this offer.

By the numbers, the mainframe/mini solution is the best and most cost effective; after all, do you own your car or do you lease?

Thanks for a great mag, and see you next month!

Tony Farrell
tony_farrell@ibm.net

Dear Nuts & Volts:

Regarding Harry Helms' Nov. '96 "Software Wizardry" column: Sure, it's easy to trash the Network Computer, if you don't understand what it is.

The primary application for the Network Computer (NC) is a replacement for desktop systems wired on corporate LANs, not home machines. The business motivation: reducing the huge support costs for Intel PCs, variously estimated to be between \$5,000.00 and \$13,000.00 PER MACHINE, PER YEAR. The problem: PCs have local hard disks and system software that users can customize at will, causing big maintenance headaches for network managers.

Thus, the network computer resembles NOT a dumb terminal (with no local processing capability), but rather the diskless workstation that is commonplace in the Unix world. By loading up system software over the net (the high-speed, internal corporate LAN, NOT a slow 28.8K baud modem link), every time a machine boots, it gets the latest revision of system software as configured by system administrators.

The true promise of Java and Network Computers is simplifying and standardizing the PC software architecture, so people can actually get useful work done on their machines, rather than spending all of their time tracking down software conflicts.

Fred Martin
fredm@media.mit.edu

Dear Nuts & Volts:

John Iovine's article on NiCad Batteries (Dec. '96) incorrectly stated that battery power was measured in amp-hours. In actuality, this is a measure of battery capacity not power. The capacity of a battery is the amount of stored charge (measured in coulombs Q) that the battery can effectively deliver to a load before its voltage drops below some useful threshold. Since charge is equal to current times time ($Q=IT$) for a constant or slowly varying current, we obtain the familiar amp-hour or milliamp-hour rating. Note that this should not be confused with the common kilowatt-hour (KWh) rating that is used to measure energy consumption (power X time = energy). The power company thus charges us for the total energy that we use (KWh), not the rate at which we use it (watts). Power, as usual, is found by multiplying the current times the voltage ($P=IV$) for constant or slowly varying currents and voltages. For an AC circuit, the average power (for in-phase, sinusoidal waveforms) is found by multiplying the rms current by the rms voltage ($P_{av} = I_{rms} \times V_{rms}$). For out-of-phase sinusoidal waveforms, a $\cos(\theta)$ term must be included (the power factor). All of these are derived from the fundamental equation that instantaneous power is equal to the instantaneous current times the instantaneous voltage $P_i(t) = i(t) \cdot v(t)$.

Jay Rabkin
Pasadena, CA

Response:

I stand corrected; amp-hour is capacity, not power. Good catch!

John Iovine

Dear Nuts & Volts:

Don Lancaster's Resource Bin

Looking for someone to take care of your CABLE needs?

I.S.E. has all your cable needs

Call us at

1-800-667-8361

Call for best price.

I.S.E., INC.

Open Mon.-Fri. 9:30 AM-6:00 PM

No Florida Sales

Write in 178 on Reader Service Card.

reader FeedBack

#58 (on page 83 of the Nov. '96 issue) talks about batteries.

In his opening remarks about batteries, he says "An electrochemical cell consists of ... an anode at the positive terminal and a cathode at the negative terminal," and a paragraph later says "a chemical reaction forces electrons from the (-) cathode over to the (+) anode."

Whoaahh! I've been taught chemistry for years, and now teach chemistry to undergraduates. I believe this is backwards.

I grabbed my Webster's Collegiate Dictionary, 5th edition, and found it defined an anode as "the positive electrode of an electrolytic cell."

This seemed to match Don's description. When I got to work I pulled out a few references, and found in the Random House Unabridged dictionary, 2nd edition, the following definition of an anode: "The negative terminal of a battery."

One says positive, one says negative. What's going on?

At this point, Don succeeded in sending me back to some fundamental studies!

Well, the answer revolves around confusion of perspective. Someone charging a battery sends electrons one way, while someone using a battery allows electrons the other way around the loop. We can talk about electron flow vs. current flow, and charging vs. using. But as soon as the terms "anode" and "cathode" come up, there is no freedom to switch around the other terms.

In ALL cases, chemical "oxidation" of some species occurs at the anode, and reduction of some chemical species occurs at the cathode. It's easy to remember because "vowels go together." In other words, "O"xidation at the "A"node, and "R"eduction at the "C"athode.


In order to reduce the charge on a chemical atom, it needs to gain electrons (negatively charged). Reduction occurs at the cathode, so electrons must "go in" the cell at the cathode. This is the positive side of a garden variety household battery.

Here's how I think Don got confused. When charging the battery, electrons (-) are taken out of the anode. This makes sense, because when you charge the battery, you provide a higher voltage and put current (+) into the positive terminal. Putting current in means taking electrons out.

Now, when using the battery, the (+) terminal accepts electrons. The electrons cause chemical reduction in atom charges inside the battery at this electrode, so

The Ultimate Battery Monitor

E-Meter™



Here's why the E-Meter is the world's most popular DC energy monitor: Multi-color bar graph shows battery status at a glance. Big digital display reports Volts, Amps, Amp-hours, Time Remaining, - even Kilowatt-hours. Reports historical information including battery Charge Efficiency, number of discharge cycles, deepest depth of discharge and average depth of discharge. Optional RS-232 and low battery alarm contact available, too!

Actual Size Fits 2" hole

Up to 1000 Amps @500 Volts!

Cruising Equipment Co.
5245 Shilshole Ave. NW, Seattle, WA 98107
(206) 782-8100 Fax: (206) 782-4336
<http://cruisingequip.com>

OEM's: Call for free applications assistance.

Write in 181 on Reader Service Card.

the electrode is now the cathode.

Using the "anode"/"cathode" terminology, the electrodes switch depending on whether you're charging or using the cell!

The dictionary quote above properly claims the anode is the positive side of an electrolytic cell. An "electrolytic cell" stores energy, or gets charged. But Don makes the subtle slip to "electrochemical cell," which now implies it's being used as a source of energy. The anode and cathode reverse!

By equating the terms electrolytic cell, electrochemical cell, and battery, Don arrived at the wrong conclusion.

For almost all readers of the Nuts & Volts article (who think of using D-cells, C-cells, etc), the anode is the negative side of the battery — the side with the "-" printed on the battery case.

Brian J. Mork
Juniper, CO

Dear Nuts & Volts:
Keep up the good work. Lots

of great articles and advertising. Please keep the electronic advertising coming. I find stuff here I cannot find anywhere else.

Charles Martin
Stockbridge, GA

Dear Nuts & Volts:

Best electronics variety store ever. Add that to a wonderful smorgasbord of articles, it's a family policy not to bug me when Nuts & Volts is in my lap!

One small voice in the back row, though — either run some informational series on program language, AND how to hook-up to a computer, or stop frustrating me with yummy PIC and CPU-link projects! Please!

J. Burgmann
Sarasota, FL

Dear Nuts & Volts:

Please, more information on antennas, decoders, video capture, and cameras. Satellite TV would also be nice.


Dan Salgado
Rowland Heights, CA

PORTABLE DATA ACQUISITION FOR WINDOWS



- NO External Pwr Required, Uses Parallel Port
- 8 Analog Inputs, 8 Dig. 6 Dig Out
- Fully Featured Analysis S/W Includes: Graphical Interface, Math Post-Processing, Direct Disk Logging, Programmable Event Controller and Much More...
- Acquisition Module Available Separately or With Kit Including Break-Out Adapter
- 10 Bit DACQ-25/10 Only \$99.95
- 12 Bit DACQ-25/12 Only \$129.95
- See Us on the Internet at:

<http://www.loop.com/~base2>

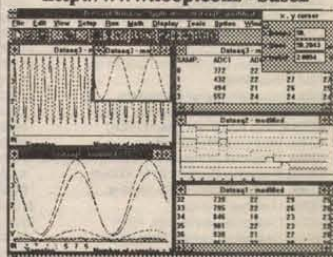

Base2 Computer Corp.

P.O. Box 950, Pasadena, CA 91102

818-583-5525

(CA Res Pls add 8.25% Sales Tax)

Write in 187 on Reader Service Card.

SPECIAL NEW PCMCIA SRAM & FLASH CARDS

Grid made by Fuji Elec. 1 Meg SRAM cards. Will work with most PDA & Laptops with PCMCIA socket. All sizes are uncompressed. Sample compatibility list: HP 100LX & 200LX, Tandy Zoomer, Zaurus 5XXX, Apple Newton, Etc.

★ 1 Meg SRAM \$34.95 Ea. ★

Flash Cards For HP 100/200LX & Kodak DC50 Digital Camera

New! 5 Meg, 10 Meg, 20 Meg PCMCIA Flash Cards. All Flash Cards have industry standard ATA interface.
(Note: Quantities Limited)

5 Meg Flash Card
5V Write & Read (40G3166) \$79.95 Ea.

10 Meg Flash Card
5V Write & Read (SDP5-10) \$199.95 Ea.

20 Meg Flash Card
5V Write & Read (40G3168) \$319.95 Ea.

30-Day Guarantee on all items

Reboot Electronics, Inc.

P.O. Box 1065

Maywood, NJ 07607

Phone/Fax **201-457-1980**

E-MAIL: reboot@carroll.com



Write in 140 on Reader Service Card.

WANTED

All Types of Test Equipment

WE BUY & SELL

Attn: Richard
3802 North 27th Ave., Phoenix, Arizona 85017



ELECTRONICS INC.

602-278-4062 • 602-269-1737 Fax

SURPLUS TEST EQUIPMENT

HEWLETT PACKARD

11664C, Detector	\$150
11683A, Range Calibrator	\$700
1827/8755C, Swept Amplitude Analyzer	\$850
214A, Pulse Generator, 0.08V to 100V	\$250
214B, Pulse Generator, 200 Watt	\$1200
3200B, VHF Oscillator	\$300
3310A, Function Generator	\$250
3310B, Function Generator, .0001Hz-5MHz	\$250
3311A, Function Generator, .01Hz-1MHz	\$225
3325A, Synthesizer/Function Generator, 10Hz-20.999MHz	\$2300
3325A, Synthesizer/Func. Generator w/opt. 002	\$2550
334A, Distortion Analyzer	\$350
339A, Distortion Analyzer	\$1750
3437A, Voltmeter	\$200
3455A, Digital Voltmeter	\$400
3456A, Digital Multimeter, 6.5 Digits	\$800
3562A, Dynamic Signal Analyzer	\$12,000
3577A, S-Parameter Test Set	\$2700
3575A, Phase Gain Meter 1Hz-13MHz	\$1000
3581A, Wave Analyzer	\$500
3581C, Selective Voltmeter	\$500
3582A, Spectrum Analyzer, .02Hz-25.5KHz	\$2800
4192A, LF Impedance Analyzer	\$11,500
4282A, LCR Meter	\$1750
4342A, Q-Meter, Opt. 001, 10KHz-32MHz	\$1750
435B, Power Meter	\$500
436A, Power Meter w/HP-IB Interface	\$1300
4428B, Output Actuator Assembly (New)	\$250
44709A, Data Acquisition Boards (New)	\$500
4800A, Vector Impedance Meter	\$800
4945A, Transmission Impairment Measurement Set	\$3000
5314A, Frequency Counter, 10Hz-100MHz	\$200
5328A, Universal Counter, DC-100MHz	\$225
5328B, Universal Counter	\$1250
5335A, Frequency Counter, opt. 1020	\$1200
5340A, Frequency Counter, 10Hz-18GHz	\$800
5345A, Universal Counter	\$750
5354A, Frequency Converter	\$800
5355A, Frequency Converter	\$1000
5356A, Converter Head	\$950
5359A, Time Synthesizer	\$1600
5370A, Universal Time Interval Counter	\$1500
54201A, Digitizing Oscilloscope, 300MHz	\$3000
54201D, Digitizing Oscilloscope	\$3500
6002A, Opt. 01, Power Supply, HP-IB, 0-50V/10A	\$800
6011A, DC Power Supply 0-20V, 0-0.120A	\$1250
6177C, DC Current Source	\$700
6186C, DC Power Source, 0-300V, 0.100 MA	\$850
6227B, Dual Power Supply, 0-25V/0-2A	\$600
7090A, Graphics Plotter	\$2500
71200A w/70310A, Spectrum Analyzer, 50KHz-22GHz w/ Precision Frequency Reference	\$18,000
8007B, Pulse Generator, 100MHz	\$550
8012B, Pulse Generator	\$750
8013B, Pulse Generator	\$750
8165A/O102, Signal Source	\$2750
83545A, Oscillator Plug-in, 5.9-12.4GHz	\$2500
8410B, Network Analyzer System w/8412A, 8743A & 8411A	\$600
8411A/O18, Frequency Converter .11 to 18GHz	\$500
8445B, Automatic Prefeeder	\$450
8447A, Amplifier, 0.1-400MHz	\$300
85020A, Bridge, 10MHz-4.3GHz	\$500
85050B, 7MM Calibration Kit	\$1750
85051A, 7MM Verification Kit	\$650
85051B, 7MM Verification Kit	\$1500
8505A, Network Analyzer	\$2500
8505A/8503A/8501A, Network Analyzer System w/S-Parameter Test Set & Storage Normalizer	\$4750
8508A, Vector Voltmeter w/85081A Plug-in	\$4750
8552B, IF Section Plug-in	\$500
8552B & 8553B, Spectrum Analyzer w/1411 Mainframe	\$1200
8552B & 8555A, Spectrum Analyzer w/1411 Mainframe	\$1450
8557A/182T, Spectrum Analyzer .01-350MHz	\$1300
8558B, Spectrum Analyzer, 100KHz-1500MHz, w/182T	\$2200
8565A, 10MHz-22GHz Spectrum Analyzer	\$4000
8568A, Spectrum Analyzer, .01-22GHz	\$6500
8568B, Spectrum Analyzer, .01-22GHz	\$7500
86290A, RF Plug-in, 2-18GHz	\$1500
86290B, RF Plug-in, 2-18.6GHz	\$1600
8640B, Signal Generator, Opt. 002, 5-1024MHz	\$2100
8640B, Signal Generator, Opt. 1, 2, 3	\$2200
8640B, Signal Generator, Opt. 1, 2, 3	\$2350
8660C/100, Synth. Signal Generator	\$1350
86601A, RF Plug-in, .01MHz-10MHz	\$350
86602B, RF Plug-in, 1-1300MHz	\$650
86603A, RF Plug-in, 1-2600MHz	\$1500
8660C Opt. 100, Signal Generator, 1-1800MHz w/86602B RF Plug-in & 86632A Mod. Plug-in	\$3000
8711A, Network Analyzer, Opt. 1E1, 1C2	\$6500
8745A, S-Parameter Test Set, 100MHz-2.0GHz	\$700
8753A w/85046A, Network Analyzer, 300KHz-3.0GHz w/S-Parameter Test Set	\$16,000
8756A, Network Analyzer	\$2500
8801B, Modulation Analyzer	\$10,000

TEKTRONIX

2236, 100MHz Oscilloscope w/Counter/Timer/DMM	\$1550
2337, 100MHz Oscilloscope w/DMM	\$1650
2440M, 300MHz Digitizing Oscilloscope	\$7500
2445B, 150MHz Four Channel Oscilloscope	\$4500
475, 200MHz Oscilloscope	\$650
475A, 250MHz Oscilloscope	\$800
485, Oscilloscope, 350MHz	\$900
494AP, Programmable Spectrum Analyzer, 10KHz-21GHz	\$18,500
577/D1, Curve Tracer w/Storage	\$1850
577/D2, Curve Tracer w/177 Fixture	\$1700
7104, 1GHz Mainframe w/(2) T429, T810, T815	\$3500
7A42, Four Channel Amplifier Plug-in	\$650
7B92A, Delaying Dual Time Base to 500MHz	\$250
7D20, Programmable Digitizer	\$500
7L18, Spectrum Analyzer Plug-in, 1.5-18GHz Capable of 60GHz with Mixers	\$2500
AF501, Band Pass Filter Plug-in	\$300
AM503, Current Probe Amplifier	\$450
DC5009, Counter Plug-in	\$575
FG502, 11MHz Function Generator	\$300
FG504, Function Generator Plug-in, .001Hz-40MHz	\$850
FG507, 2MHz Function Generator	\$975
I241, Color Logic Analyzer w/(4) I240D1 Cards	\$1250
OF150, Fiber Optic Cable Tester	\$2000
PG501, Pulse Generator	\$275
PG508, Pulse Generator Plug-in, 50MHz	\$600
PS5010, Programmable Triple Power Supply Plug-in	\$700
PS503A, Tracking Power Supply Plug-in	\$175
RTD710, Digitizer	\$5000
SC503, 10MHz Storage Oscilloscope Plug-in	\$650
SC504, 80MHz Oscilloscope Plug-in	\$500
SG505, Precision Audio Oscillator Plug-in	\$450
TR503, Tracking Generator for 492/4/5/6	\$850

MISCELLANEOUS

Boonton 102F, AM/FM Signal Generator, DC-1040MHz	\$2000
Fluke 332D, Voltage Standard	\$650
Fluke 3330B, DC Voltage Calibrator	\$750
Fluke 335D, DC Voltage Standard	\$1000
Fluke 5100B/03/05, Multifunction Calibrator	\$6000
Fluke 5100B/05, Multifunction Calibrator	\$6000
Fluke 5101B/03, Calibrator	\$5000
Fluke 515A, Calibrator	\$1200
Fluke 5200A, AC Voltage Calibrator	\$2000
Fluke 5200A/5215A, AC Voltage Calibrator w/Power Amp	\$3850
Fluke 5440B, Precision DC Voltage Calibrator	\$5500
Fluke 5450A, Resistance Calibrator (New)	\$2000
Fluke 6160B, Synthesizer, Opt. 09	\$1000
Fluke 7220, Frequency Counter, 10Hz-1300MHz	\$350
Fluke 8454B, Null Detector	\$800
Fluke 8502A, Digital Multimeter	\$300
Fluke 8505A, 6.5 Digit Digital Multimeter	\$400
Fluke SR1030, Resistance Standard Set (New)	\$2650
Fluke SR1060, Resistance Standard Set (New)	\$3200
Gigatronics 605, Signal Generator, 6-18GHz	\$3000
Hughes, Amplifier 18-26.5GHz, 1 Watt	\$2500
Keithley 195A, System DMM w/Temp.	\$700
Krohn-Hite 3100R, Tunable Filter	\$150
Krohn-Hite 3103/R3103, Tunable Filter/Rack Version	\$275/\$225
Krohn-Hite 3202/R3202, Tunable Filter/Rack Version	\$500/\$350
Krohn-Hite 3342, Tunable Filter	\$1000
Phillips PM3070, 100MHz Oscilloscope	\$1500
Phillips PM5715/11, 50MHz Pulse Generator (New)	\$1500
Sorenson QRD 30-1, Power Supply, 30V-1A	\$100
Sorenson QRD 40-2, Power Supply, 40V-2A	\$150
Wan, & Golt DA30, Protocol Analyzer	\$5000
Wavetek 166, Pulse Function Generator	\$1000
Wavetek 178, Automatic Synthesizer	\$1850
Wavetek 186, Phase Lock Generator, 5MHz	\$400
Wavetek 2002, Signal Generator, 1-2500MHz	\$1750
Wavetek 2002A, Signal Generator, 1-2500MHz	\$1500
Wavetek 3000, Signal Generator, 1-520MHz	\$900
Wavetek 3000-200, Signal Generator	\$900
Wavetek 3001, Signal Generator 1-520MHz	\$1000
Wavetek 801, Pulse Generator, 5Hz-50MHz	\$800
Wavetek 802, Pulse Generator, 5Hz-50MHz w/Delay	\$600
Wavetek 907A, Signal Generator, 7-12.4GHz	\$850
Wayne/Kerr 3220, 20A Bias Unit	\$2000
Wilton 560A, Scalar Network Analyzer	\$1350
Valhalla 2701C/TL-3, Programmable Direct Voltage/Current Standard	\$1450
Valhalla 2705, AC Voltage Standard	\$3000

VISIT OUR INTERNET SITE AT:

<http://home.earthlink.net/~rsurplus/rsurplus.html>

HAM GEAR FOR SALE cont.

MILITARY RADIOS: Easily made battery adapters for military radios & other electronics. Get "Power Up," big new 96 page manual of instructions, diagrams. Use readily available commercial batteries in PRC-6, -8, -9, -10, -28, -25, -47, -74, -77, TRC-77, AN/PRR-9, AN/PRT-4, RT-77, URC-68, more, also mine detectors, night scopes, radiacs, field telephones, etc. Only \$14.95, plus \$5 S/H (\$6 Canada). NYS residents add \$1.66 tax. CRB Research, Box 56-NVV, Commack, NY 11725. Visa/MasterCard welcome. Phone: 516-543-9169.



THE SMART BATTERY CHARGER for lead acid or gel cell batteries. Can be left connected to the battery INDEFINITELY, will not overcharge! Standard kit is 12V @ 1 amp. This kit is 100% complete, including a custom-made, pre-punched, painted and lettered enclosure. For the kit order #150-KIT at \$59.95. For an assembled and tested unit, order #150-ASY at \$79.95. CA residents add 7.75% sales tax. Add \$6.50 per unit shipping. MC/VISA accepted. A&A Engineering, 2521 W. La Palma #K, Anaheim, CA 92801. 714-952-2114, FAX 714-952-3280.

GE MASTER Executive II Comb# SX56KKP66A VHF, 40W, 8 ch., w/access. \$150. Aerotron MPAC-2 VHF, 10 ch., 60W, w/scale head and access. \$75. D. Smith 916-626-6952. desmith@spider.lylloyd.com



\$60 PACKET: BAYCOM software-based packet for PC/clone that does not require a TNC. Software requires a modem which connects to standard serial port. Watchdog timer and read relay keying are included. Power required is 8 to 14 VDC @ 100mA, wall power supply is included. Circuit uses crystal controlled 7910 chip, no tone alignment required. Three position switch allows HF or VHF operation. Order board KIT #190 for \$59.95, enclosure included. Order assembled in enclosure for \$79.95, both include free disk. Add \$5 S/H. A&A Engineering, 2521 W. La Palma #K, Anaheim, CA 92801. 714-952-2114, FAX 714-952-3280. MC or VISA accepted. CA residents add 7.75% tax.


LOW PRICED, new & used scanners & ham gear & commercial equipment. Free catalog. Call 909-873-1319 or fax on demand 909-820-1885. E-Mail: HRH6@aol.com or write: LML, 424 E. Shamrock, Rialto, CA 92376.



ELECTRONICS BOOKS. Thousands of titles. Electronics meet. Aviation at Marine, Manhattan Beach 7-11am, last Saturday each month. We also buy. Lee and Margaret Johnson, 805-525-8955.

LEARN THE SECRET. How to silently activate any phone/line and monitor. And without ID detection. For info, send \$5 refunded with first order to: ILIADIS, PO Box 350562, Jacksonville, FL 32235-0562.

NEW PRODUCTS FROM S&S: UPGRADE YOUR OLD RIGS! Digital Dial has 10Hz resolution HF, 100Hz VHF and frequency range 50KHz to 230MHz; kit \$99.95; assembled \$149.95. Digital VFO with 1Hz resolution; kit \$139.95; assembled \$189.95. S&H \$7.50 (continental US). GUARANTEED TO WORK. For info send SASE; call/write to order: S&S Engineering, 14102 Brown Road, Smithsburg, MD 21783; 301-416-0661; E-Mail: N3SAD@aol.com or see <http://www.xmetric.com/sseng>

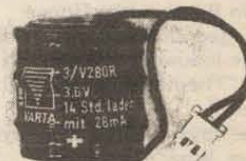

NEW NICAD \$2 S&H included. PO Box 207, Bradenton, FL 34206. KE4VOJ.

RCI-2950/2970 Modification Manual. Tune-up, audio, receiver, noise-blanker & clarifier modifications. Microphone wiring & more. \$20 ppd w/money order, \$25.50 COD. Scott, PO Box 225, St. Clair, MO 63077. 314-629-4294.

HAM GEAR WANTED

MILITARY COMPONENTS wanted. Capacitors, resistors, diodes, transistors, semiconductors, ICs. Electronic Material Industries, 818-842-5953, FAX: 818-845-3613.

Subscribe To Nuts & Volts
Call 1-800-783-4624

REMOTES

Remote Control for Any Application

NEW NEW NEW NEW NEW

3.5" x 2.75"

- 3 Channel Receiver
- Channel 1 - 5 amp Relay, N/O, N/C
- Channel 2 and 3 Digital Outputs
- Compatible with 2 Button or 4 Button Remote
- Code Hopping Receiver at 434 Mhz
- Compatible with All Garage Doors and Some Car Alarms

\$69⁹⁵

2.75" x 2.75"

- 6 Channel Receiver with Digital Outputs
- All Channels are Programmable for Momentary, Latched, Latched with Condition 30-60-90 Sec. Timed Outputs
- Code Hopping Receiver at 434 Mhz
- Compatible with 2 Button or 4 Button Remote
- Compatible with Some Car Alarms

\$99⁹⁵

1.25" x 1.75"

- 2 Button - 3 Channel Remote
- Extra Long Range 434 Mhz with S.A.W. Resonator
- Push Both Buttons together for Channel 3
- Compatible with three and Six Channel Receivers

\$29⁹⁵

1.25" x 1.75"

- 4 Button - 15 Channel
- Extra Long Range 434 Mhz S.A.W. Resonator
- Push Combination of Buttons together for Channel 5 through 15, i.e. Push Button 1 and 2 together for Channel 5
- Compatible with three and Six Channel Receivers

\$39⁹⁵

R & S Surplus

1050 E. CYPRESS STREET, COVINA, CA 91724

(818) 967-0846 • FAX (818) 967-1999



Cellular Extensions

from
"THE CELLULAR EXPERTS"

Motorola 3 Watt Bag Phone from \$199
Nec P120 12oz. Portable \$299
Motorola PT 550 10oz. "Flip" Phone from \$299

Others available, buy new from us, or send us your phone.
Get a second or third phone with no additional monthly charges!
Motorola, NEC, Panasonic, Audiovox and many others.

Fax Back Hotline For 24hr info. call from your FAX
(714) 581-7460 or call 1-800-457-4556 9 to 5 PST
CA Grapevine. Worldwide inquiries welcome.

Write in 139 on Reader Service Card.

WANTED: ICOM IC-03AT 220MHz handhelds. Will consider non-functional radios. **Top dollar offered.** Contact Alan Sanders, Communications Specialists, Inc., 426 West Taft Avenue, Orange, CA 92665-4296. 1-800-854-0547, FAX 1-800-850-0547.

I WANT it and I want it now. I want all of your SIMM memory. IBM, Mac, new, used, even defective. I want it all. Highest \$ paid. Now selling memory. We can beat any printed price in Nuts & Volts. Call 1-800-4-MEMORY now! Voice/FAX.

CB/SCANNERS

TOMCAT'S BIG CB Handbook, by Tom Kneitel 221 pages, illustrated. Everything they never told you about AM, SSB, DX, Freeband, legal and otherwise. Only \$15.95 (+\$5 postage, \$6 to Canada). CRB Research, Box 56, Commack, NY 11725. (NYS residents add \$1.73 tax). MC/Visa OK. Phone orders 516-543-9169.



NEW UPDATED/MORE INFO ULTIMATE MODIFICATION BIBLE VOL 6 1000 mike wiring CB and ham, 500 CB modulation boost, 200 CB PLLs, 200 ham radios, 30 scanner modifications, over 200 pages. KDC SOUND, PO BOX 8622, GRANGERLAND, TX 77302. Send \$29.95 (SORRY NO CODs) to order: VISA, MC, DISC. 1-800-256-9895. OTHER CALLS 409-231-3753.

CB RADIO Hacker's Guide! Wow! Big 150 pages; pictorials, diagrams, text. Peaking, tweaking & modifying 200 AM & SSB CB radios. Improved performance, extra capabilities! Which screws to turn, which wires to cut, what components to add: Cobra, Courier, GE, Midland, Realistic, SBE, Sears, Uniden/President. \$19.95 plus \$5 shipping (\$6 Canada). NY State residents add \$2.06 tax. CRB Research, Box 56-NV, Commack, NY 11725. Visa/ MasterCard accepted. Phone order M-Tu-Th-F, 10-2 Eastern Time, 516-543-9169.

FEDERAL FREQUENCY Directory! Kneitel's "Top Secret" Registry of government Frequencies, New 8th Edition. 268 Pages! FBI, DEA, Customs, Secret Service, BATF, Immigration, Border Patrol, IRS, FCC, State Dept., Treasury, CIA, etc. & surveillance, bugs, bumper beepers, worldwide US military, 225 to 400 MHz UHF aero band, Canadian listings, & more. Ultimate "insider's" directory! Standard reference of law enforcement, news media, private security, communications industry & scanner owners. \$22.95 + \$5 shipping (\$6 to Canada). NY State residents add \$2.31 tax. CRB Research Books, Box 56-NVT, Commack, NY 11725. Visa/MC welcome. Phone orders 516-543-9169 weekdays (ex-Wed.) 10 to 2 Eastern.

BILL'S CB & 2-Way Radio Service: CB/ham/scanners, AM/FM/SSB/CW export/domestic radios by Galaxy, Mirage, Palomar, Connex, Cobra, Superstar, RCI, Uniden Midland, Maxon, and more. Linear amps, antennas, books, manuals, mics, meters, sound toys, frequency expansion and modulation kits. \$3 for list of products, refundable on first order. Technical advice is free. Call: 408-782-0064. Write: PO Box 306, Morgan Hill, CA 95038-0306 MC/VISA.

ROGER BEEPS/keyup tones superior quality high reliability professional grade devices. Single and multitone. \$19.95 to \$29.95. For more information, faxed or mailed literature and orders please call **Daltronix**, 908-493-1658.

FREE CB EXPORT CATALOG 24 HOURS A DAY by our **INTERACTIVE VOICE MAIL SYSTEM, FAX ON-DEMAND. LISTEN** to or **FAX DOWN** the **ABSOLUTELY LOWEST PRICES** on CBs, Scanners, Modifications, Kits, Technical Books, Accessories and more. **LORD/WYATT COMMUNICATIONS** 718-789-7329, press Ext. 1 for the CB department. No FAX machine. Please send \$3 for catalog to LWC, PO Box 030128NVJL, Brooklyn, NY 11203-0001.

DEVICE PROGRAMMERS

OVER 50 MODELS
QUALITY PRODUCTS * FREE TECHNICAL SUPPORT * AND NEVER UNDERSOLD

ADVANTECH EETOOLS NEEDHAMS DATA I/O SYSTEM GENERAL MODULAR CIRCUIT TECHNOLOGY ICE TECHNOLOGY CHROMA HILO STAG XELTEK

PROMAX	MEGAMAX	MEGAMAX4	ALLMAX PLUS	SUPERPRO II	MICROMASTER-IV	LABTOOL-48	SA-20
\$CALL	Advantech Labtool-48 Universal	\$ 369	Xeltek SuperPro II Universal (ISA Card)				
\$ 650	EETOOLS Allmax Plus Universal (Printer Port)	\$ 409	Xeltek SuperPro IIP Universal (Printer Port)				
\$ 409	EETOOLS MegaMax 1 Gang Universal (PP)	\$ 249	Xeltek SuperPro Lite Universal (Printer Port)				
\$ 509	EETOOLS MegaMax 4 Gang Universal (PP)	\$ 165	Xeltek Rommaster II Universal (Printer Port)				
\$ 419	Needhams EMP-20 Universal (Printer Port)	\$ 479	MOD-EMUPA Universal (New Sale Price)				
\$ 679	Needhams SA-20 8 Gang Stand Alone	\$ 629	ICE Technology MicroMaster LV (Printer Port)				
\$ 739	Stag Orbit-32 E[Eprom Stand Alone		Please Call For Refurb Demo & Used Programmers				

General Device Instruments

Sales 408-241-7376 Fax 241-6375 BBS 983-1234
Web www.generaldevice.com E-Mail icdevice@best.com

MCT-EMUPA
\$479

ROMMASTERII
\$165

Write in 147 on Reader Service Card.

EPROM+

A DEVICE PROGRAMMER FOR BENCH AND FIELD

THE ORIGINAL PARALLEL PORT PROGRAMMING SYSTEM!

EPROMS (UV & FLASH) (24, 28, 32, 40* PIN PLUS 27C, 29C, 28F & 29F)
1702*, 2708, TMS2716*, 2716, 32, 32A, 64, 64A, 128, 128A, 256, 512, 513, 011, 010, 101, 1001, 1000, 1024, 210, 020, 2001, 220, 2048, 4001, 040, 080, 240, 4096, 2516, 32, 64, 68764

EEPROMS AND NVRAMS (1R, 24 & 28 PIN PLUS CXXX) X2210, 2212, 2804, 2816, 2816A, 2817, 2864, 2865, 28C256, 28C010, DS12XX

SERIAL EEPROMS* (8 & 14 PIN PLUS CXX) ER1400, MS8657, 2401, 02, 04, 08, 16, 32, 44, 64, 65, 59C11, 80011A, 8572, 82, 92, 9306, 46, 56, 66, 16811, 16911

BIPOLAR PROMS* (16 THROUGH 24 PIN) 74SXXX, 82SXXX FAMILY

MICROCONTROLLERS* (UV, EE AND FLASH) 8741, 42, 48, 48H, 49, 49H, 8751, 87C51, 52, 87C5XXX, 87C75X, 89C51, 52, 89C1051, 2051, 68705, 68HC705, 68HC711, 6871, PIC16C54, 55, 56, 57, 58, 61, 64, 620, 621, 622, 71, 74, 84, TMS742

*ADAPTER REQUIRED - DIAGRAMS INCLUDED IN MANUAL

- SOFTWARE - READ, VERIFY, PROGRAM, COPY, DISK FILE LOAD & SAVE, CHECKSUM, FULL SCREEN BUFFER EDITOR W/20 CMDS
- READS INTEL HEX, MOTOROLA S-RECORD AND BINARY FILES
- FAST-MOST DEVICES PROGRAM IN UNDER 20 SECONDS
- RUGGED (9" X 6" X 3") PORTABLE ENCLOSURE W/CARRY HANDLE
- MADE IN THE USA - 30 DAY MONEY BACK GUARANTEE
- SYSTEM INCLUDES: PROGRAMMING UNIT, PRINTED MANUAL, PRINTER PORT CABLE, POWER PACK AND SOFTWARE

\$289

ADD \$5.00 SHIPPING
\$5.00 COD
VISA / MASTERCARD

ANDROMEDA RESEARCH, P.O. BOX 222, MILFORD, OHIO 45150
(513) 831-9708 FAX (513) 831-7562

HOME PAGE: www.hamboree.org



37th ANNUAL TROPICAL HAMBOREE®

AMATEUR RADIO & COMPUTER SHOW
ARRL SOUTHEASTERN DIVISION CONVENTION
FEBRUARY 1 - 2, 1997

DADE COUNTY YOUTH FAIR & EXPOSITION CENTER
S.W. 112 AVENUE & CORAL WAY (S.W. 24 ST.)
MIAMI, FLORIDA

E-MAIL: edg@elink.net

• Sponsored by Dade Radio Club of Miami, Inc.

TALK IN: 146.925

INTRODUCTION TO AMATEUR RADIO DISPLAY • FORUM ON BACK TO BASICS IN THE WIDE WORLD OF AMATEUR RADIO • PANEL DISCUSSION ON INTERNATIONAL SPECTRUM PLANS & THE FUTURE OF AMATEUR RADIO • FORUM ON THE FCC AND THE AMATEUR RADIO SERVICE • 200+ EXHIBIT BOOTHS • 800+ INDOOR SWAP TABLES • TWO ON-SITE LICENSE EXAM SESSIONS • FIELD CHECKING FOR DXCC AND CQ AWARDS

• PROGRAMS BY AMSAT, ARRL, QCWA, DXPEDITIONS, ANTENNAS, PACKET, TRAFFIC, ARES
• ALTERNATIVE INTEREST PROGRAMS ON CRAFTS, PERSONAL APPEARANCE, HEALTH & NUTRITION

AIR CONDITIONED FACILITY • ON-SITE CAMPING FOR 300 RVs • FREE PARKING FOR 15,000 VEHICLES

Registration: \$5.00 Advance (deadline Jan. 21st) - Door: \$7.00
Campsites: 3 days (Fri., Sat., Sun.) \$45.00, 4 days (Thur., Fri., Sat., Sun.) \$60.00
Swap Tables: \$28.00 each plus reg. ticket • Power: \$10.00 per user.
(Prices quoted for tickets, tables & camping include Fla. & Dade Co. tax)

Headquarters Hotel: Miami Airport Fairfield Inn South in the Marriott Lodging Complex at 1201 N.W. LeJuene Road (N.W. 42 Ave.), Rates: \$65.00 Single or Double. Tel: (305) 643-0055 - Speak Only to Reservation Department and MUST mention "Tropical Hamboree" to get special rate. Deadline Jan. 19, 1997.

TICKET, CAMP, TABLE PAYMENTS PAYABLE TO: **DADE RADIO CLUB OF MIAMI, INC.**
Mail to: Evelyn Gauzens, W4WYR, 9780 N.W. 3 St., Miami, FL 33125-5059
BOOTH & TABLE INQUIRIES: email: edg@elink.net, Tel: 305-642-4139, Fax: 305-642-1648
HOMEPAGE: www.hamboree.org

100% Satisfaction & Every day Low Price Leader

ALL Motherboards w/CPU:
 486 DX2 66 MHZ VLB 1w/256k \$129
 486 DX4 100 MHZ w/256 \$139
 586 DX133 MHZ VLBw/256k \$145
 586 DX 133 MHZ PCI 256K \$145

486 100MHz
 System \$345
 16 speed CD Call

Orders & PRICE
 7 * 800-899-6430
 7 * 209-538-3940
 Free Tech Support
 800 899 6430

All Pentium
686 & 586 Mother Boards
Memory & Drives
at Super Low Price

12x Sp Bundle
\$199
 12x Speed CD
 16 Bit Sound Card
 CD Titles
 Amplified Speakers

Floppy Drives:

1.44 MITSU
 1.44 TEAC
 1.2/1.44 COMBO

Member of
 Better
 Business
 Bureau

8X Speed CD \$99
 10X Speed CD \$104
 12X Speed CD \$129

Monitors:

14" MONO.VGA
 14" 28 108 NH, LOW-R
 15" 28 1024x768 NH, LOW
 17" 28 1280x1024 NH, LOW

\$21
 \$23
 \$65

All Kinds Drives, Sound Cards
Speakers and CD Titles: Please Call

HARD DRIVES SPECIAL
 540MB \$135 850MB \$159
 1.27GB \$189 1.6GB \$219
 2.1GB \$249 2.5GB \$289

Keyboards:

101 KEYBOARD \$12
 KEYTRONIC \$23
 FOCUS 2000/2000 \$CALL

686DX

Cyrix P166+
 \$289
 Motherboard
 & CPU

Modem/Fax Modem:

28.8 PCMCIA \$169
 Fax/Mod. 14.4 \$33
 33.6 Voice M /Fax /Mod \$104
 US ROBOTIC 33.6 Int \$119
 ISDN \$CALL

VGA Cards:

VGA256K \$27
 SVGA 512K \$35
 SVGA 1MB \$39
 VESA/PCI 1MB EXP 2MB \$42
 PCI / VESA VGA 2MB \$59
 SVGA CARDS WITH VRAM CALL
 ANY OTHER VGA CARDS PL CALL

Simm Memory
 Will beat any price
LOW \$\$\$

Cases with P.SUPLIES

MINI TOWER PREMIUM \$35
 DESK TOP CASE PREMIUM \$45
 MED TOWER CASE PREMIUM \$55
 FULL TOWER CASE PREMIUM \$75

Controller Cards:

IDE CARD (2FD/2HD) \$11
 I/O (2S, 1P & 1G) \$11
 SUPER IDE-I/O \$12
 VESA EIDE-FAST-I/O \$19

IBM 686DX
P166+
 Faster than pentium
 166Mhz
\$289

Credit Cards Ok
 Govt P.O. • C.O.D.
 "Triton" Intel Mother Boards
 Pentium 100 Mhz w/CPU \$269
 Pentium 133 Mhz w/CPU \$349
 Pentium 166 Mhz w/cpu \$495
 Pentium 200 Mhz w/CPU \$CALL

Buy with
 Confidence
 Risk Free
 30 days Money
 Back

WE DO
CARRY
COMPLETE
SYSTEMS
 *
Printer
Memory.
 *

ONE YEAR
 WARRANTY
 ON PARTS
 LIFE TIME
 Labor
 Warranty

Resellers
Dealers
Welcome
 Terms:
 No minimum Charge
 No Hidden Charge
 Prices change w/o Notice
 15% Restock fee for Non Defective
 Orders of \$500 or more
 ground shipping free.
 Except Case, Monitor, Keyboard & F. Drives

Bismar Computer, Inc 1443 Angie Ave, Suite C, Modesto, CA 95351

Write in 179 on Reader Service Card.

CABLE TV CONVERTERS ★AS LOW AS \$25.00 WITH REMOTE★ TIMELESS PRODUCTS

550-PC
THE HOTTEST
CONVERTER
EVERYONE'S
AFTER!



WORKS
PERFECT
WITH
DECODERS
DOES NOT
DECODE

THE BEST CONVERTER ON THE MARKET. PERIOD!!!

PANASONIC

TZPC145 3G2
THE OLD
STAND-BY
NOW BACK IN
STOCK



ALSO:
 TZPC175
 DG2
VOLUME
CONTROL

NEW REPLACEMENT REMOTES — MOST CABLE MODELS
NEW WITH FULL WARRANTY!
 ★ REFURBISHED CONVERTERS ALSO AVAILABLE! ★
 WE'RE THE LARGEST STOCKING DISTRIBUTOR
 OF TPI CONVERTERS BECAUSE WE ARE...

TIMELESS PRODUCTS
(218) 346-6665

DEALERS ONLY — BEST PRICES — CALL! NO DECODER SALES

Write in 47 on Reader Service Card.

Electronic Components

ISD Voice Chip Module, 10 sec. #VM-1110A, \$4.00 each/10 piece min.

Crydom Relay #D2425 \$6.00 each, any quantity, regularly \$13.25 !!

Examples: Carbon Film, Carbon Composition, Metal Film Resistors, Capacitors, Diodes, and Much More!

Some price examples: 1/4W 5% Carbon film \$3.15/K, 1/4W 1% Metal film \$5.85/K**

1N4001 - 1N4007 1AMP Diodes \$10.50/K, 1N4148 Switching Diodes \$8.50/K

These examples are first grade, not surplus!!

CALL FOR A FREE SURPLUS CATALOG

**Some restrictions apply. Call for details

Visa and Master Card Accepted. Toll Free 1-800-323-8962 (c/o Edmar)

THE M.O.O. Corp. 809 W. Estes Schaumburg, Illinois 60193

FAX: 847-923-9112

VINTAGE TUBE CBs. LSASE list. RR3 Box 2075, Fort Kent, ME 04743. 207-834-6273, evenings/weekends.

"CB MODIFICATION SECRETS," new 200-page guide by author of "CB Radio Hacker's Guide." More easy AM/SSB CB upgrades & enhancements: Cobra, Realistic, Uniden, President, etc. Freq. expansion, VFO, clarifier unlock, VOX, Roger Beep, anti-theft device, receive preamp, more. Only \$21.95, plus \$5 S/H (\$6 to Canada). CRB Research, Box 56, Commack, NY 11725. NYS res. add \$2.22 tax. Visa/MC orders call: 1-800-656-0056. Canada/AK/HI: 516-543-9169.

SALES, SERVICE: CB equipment, radios, antennas, mics, connex echo boards, hard to find items. Send \$2. for list. **SUNDANCE ELECTRONICS, 1051 EVA RD., EVA, AL 35621. 205-482-2983**

RED BOOK CB MODIFICATION. Antennas, audio, modulation, PLL/VCO, synthesis, mixer crystals, sliders. \$25. **KEN'S, 2825 Lake, Kalamazoo, MI 49001. 616-345-4609.**

240+ CHANNEL CB/HAM radios AM/FM/SSB/CW export/domestic: RCI, Uniden, Galaxy, Cobra, Superstar, mics, antennas, linears, meters, manuals, night scopes, and tons more stuff! Catalog \$3. **MAXTECH, Box 8086, New York, NY 10150. 718-547-8244.**

PAGERS. TONE only starting \$3. Numeric pagers starting at \$5. Alpha starting at \$20. We also buy/sell new and used pagers. Credit cards okay. Fax/message: 501-223-9406. Internet: pager@aristotle.net **Surplus City, Box 23016, Little Rock, AR 72221.**

A Simple Solution. FBASIC TICKIT™

Starting as low as \$49

Run FBASIC programs without the delays and difficulty of assembly coding.

Simple to use, easy to learn, complete small projects quickly with the FBASIC TICKIT™. Suitable for both beginners and experienced engineers.


Internal RAM: 48 bytes
Max EEprom: 65535 bytes
Signed 32bit Math
300% faster than Stamp I
I²C Peripheral Buss

Interactive Debugging
EEprom Arrays and Structure
44780 LCD Module Routines
9600 Baud Serial Routines
16 Multi-purpose I/O Lines

Ask us about the new **I²C X-Tender Peripheral!**

Buffered RS232 Serial Hardware PWM & Stepping Real Time Clock
8 Additional I/O Lines 5 Channel A/D 128 Bytes SRAM

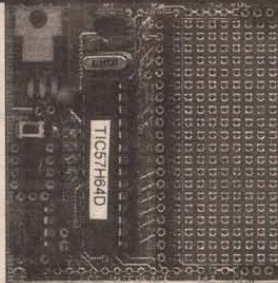QUESTIONS? Call us at (303) 440-5590 or visit our home page at www.csn.net/versatech



To Order Call:

Phone: (303) 440-5590

fax: (303) 440-9467

bbs: (303) 440-7828

e.mail: versatech@csn.net

VersaTech
Electronics

P.O. Box 18476, Boulder, CO 80308

SALES, SERVICE: CB equipment, radios, modifications, power mics, echo-reverb boxes, kits, meters, filters, antennas, noise toys, mounts, hard-to-find items. Partial list \$1, complete list \$4. D&R Electronics, 10 Park St., Thomaston, CT 06787. 860-283-9492.

CBs, ACCESSORIES, SCANNERS, ANTENNAS, MICROPHONES, COAX. Best prices! Call 1-800-821-2769 for current flyer. **THOMAS DISTRIBUTING**, 128 Eastwood, Paris, IL 61944.

VINTAGE TUBE CBs: Browning, Tram, Lafayette, Courier, Heathkit, Polycomm, Stoner, many others. For sale by former collector. Also: tube table radios. List (specify) LSASE. Fisher K10 Spacexander tube reverb (mint) \$100. C. Zafonte, RR 3 Box 2075, Fort Kent, ME 04743. 207-834-6273 evenings/weekends.

SCOPEBOOSTER KITS close out. Nov. '96 issue, \$39.95, S&H \$4.50. Technology Systems, PO Box 1401, Torrington, CT 06790-1401.

ORANGE BOOK SCANNER REPAIR. Modifications, repair information, 450+ models: Alaron to Yupiteri. \$25. KEN'S, 2825 Lake, Kalamazoo, MI 49001. 616-345-4609.

SCANNER MODIFICATION HANDBOOK. Big! 160 pages! More than 20 performance enhancements for PRO-2004 and PRO-2005. Restore cellular, increase scanning speed, add 6,400 memory channels, etc. Step by step instructions, photos, diagrams. Only \$18.95, +\$5 shipping (\$6 Canada). (NYS residents add \$1.98 tax.) CRB Research, Box 56, Commack, NY 11725. Visa/MC welcome. Tel. 516-543-9169.

THE MOST EXTRAORDINARY hacking catalog in the world! www.spectre-press.com

MUSIC & ACCESSORIES

COMPUTER HARDWARE

1.44 FLOPPIES beige Panasonic or black Teac, new \$20. IDE 540MB 2.5" new \$99. 44MB Syquest in external SCSI case, used \$25. 1-800-899-7677.

ZSORT. SORT huge files fast. Disk \$5. Manual \$10. Box 12238, Lexington, KY 40581-2238.

SURPLUS DEALS & BLOWOUTS. Windows NT: full ver 3.1 w/book, registration & CD (use it to upgrade to 4.0) \$55 or 5 at \$49 each. Disks: 100 3.5" 1.44M for \$19 or 100 3.5" 720K for \$13. SCSI cables from \$4 each. Extra long IDE cables from \$6. All the hard to find cables, adapters, & connectors! For stock list E-Mail: C-E-S@Juno.Com or send SASE to Computer & Electronic Solutions, PO Box 40302NV10, Redford, MI 48240. VISA/MC/AX ACCEPTED. 313-532-4291.

CHEAP IBM PC PARTS! Disk controllers, cases and power supplies, floppy drives, CD-ROMs, motherboards, coprocessors, cables, video cards, fax modems, and more! Examples combo 16-bit sound card (Sound Blaster and Adlib compatible) and 14.4 fax modem all in one card from Diamond \$55. Call Under the Wire Electronics (UTWE) 818-930-1121 (10am-5pm PST) or fax 818-930-1123 UTWE, 235 E. Colorado Blvd. #211, Pasadena, CA 91101.

IMSAI 8080 wanted. Pete Roemer, PO Box 1000, Manitowish Waters, WI 54545. 715-543-8451 days.

NEW APPLE IIc/e/gs peripherals. Factory direct prices! Complete list available. Price Breakers 360-837-3042. Fax 360-837-2057.

CHEEK3 There's only one BEST!

The Ultimate Scanner

The King of Scanners takes this step-by-step, richly illustrated, bench manual far beyond everything ever printed on scanner mods. Bill will help you convert your scanner into precisely what you've always wanted! 244pp, large format, \$29.95

Scanners & Secret Frequencies

Henry Eisenson's best seller. Novice to pro, it's *MUST* reading. Praised by the experts as truly outstanding, comprehensive. 320pp, \$19.95

Emergency Radio! Norm Schrein

FUN! 214pp, \$14.95 "Mr. Scanner"

COPS! ...in print

Television GRAY Market

How they steal cable programming, with vendor lists, parts, the law, much more! Henry Eisenson, 160pp, \$23.75

Cheating* at Blackjack

*and Advantage Play "Dangerous!" Snyder

D Marks, 230pp, \$19.95 "Exceptional" Dalton

Underground Database

Everything that's sort of legal. "Fascinating" ASG 100pp, large format, \$23.75

NEW for 1997

A selection of the McGraw-Hill Electronics Book Club

Radio Monitoring

The How-To Guide T.J. "Skip" Arey

The complete hands-on guide to the world of radio communication, including mediumwave, shortwave, VHF/UHF scanning, and more!

Equipment selection, antennas, accessories, clubs, techniques, logging, listening posts, etc. etc.

"This complete how-to guide should grace the shelf of anyone in the radio hobby."

Richard D'Angelo, Chairman Association of North American Radio Clubs

"Skip covers it all, from DC to daylight..."

A comprehensive course on intercepting and documenting radio signals.

Highly recommended! Bill Cheek

"The most complete and useful book of monitoring information available."

Paul Swearingen, Publisher, DX News

ISBN 1-56866-101-0 344 pages, \$19.95

www.electroniccity.com/~ipgbooks

INDEX Publishing Group, Inc. s/h 1st book: \$4

3368 Governor Dr. Ste 273N Add'l: \$2 ea

San Diego, CA 92122 CA: add


7.75% tax

1-800-546-6707 - credit cards

Write in 76 on Reader Service Card.

CALL 1-888-426-9787

ONE STOP SUPPLIER

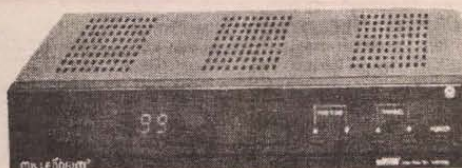

MILLENNIUM CONVERTER

\$69.00

NO
F
S
A
L
E
S
I
D
A



NOVAVISION CONVERTER

\$199.00 CALL FOR QUANTITY

**WE STOCK A FULL LINE OF CABLE EQUIPMENT
CALL US FOR QUOTES**

DOZENS OF OTHER CONVERTERS AVAILABLE

CALL FOR QUANTITY PRICING

OPEN MONDAY - SATURDAY FROM 9:00AM TO 5:00PM

WE SHIP THE SAME DAY

90 DAY LIMITED WARRANTY

Write in 86 on Reader Service Card.

Nuts & Volts Magazine/January 1997 11

CALL 1-888-426-9787

by William C. Hendry IV

A HIGH-QUALITY DESKTOP LINEAR POWER SUPPLY FOR AUTOMOTIVE ELECTRONICS

Our goal is to construct a high-quality supply that costs less than those on the market, and to completely describe the design.

Abstract

A linear power supply was chosen over a switching supply due to its relative simplicity, low noise, low-ripple voltage, and fast response.

A suitable filter capacitor was difficult to find that was not grossly above the calculated value, and the center-tapped transformer was not available from my "standard" catalogs. The solution seemed to improve with an inexpensive "12V" converter."

We observed that all kinds of voltage requirements are given for automotive equipment — from 12V to 13.8V — therefore, a variable supply was needed. We also felt that a voltmeter would be a desirable feature. Additionally, the ability to dial voltages down to 5V would prove useful.

Selecting a Regulator

A practical starting point for a power supply design is to identify a regulator. Surveying the data books shows that an LM138K is a suitable device, and is an adjustable regulator in a TO-3 package. The LM138K was priced at over \$40.00, but we found the LM338K for under \$5.00. The significant difference is that the LM138K maximum junction temperature is 25°C greater, at 150°C.

Features of the LM338K

- 8A typical output current (5A guaranteed, 12A peak)
- 50 watts max. power dissipation (for the device)
- Current and power limiting
- Short circuit protected

The power dissipation is calculated by:

$$(V_{in} - V_{out}) \times I_{out} = \text{power dissipated,}$$

$$(16.55 - 13.8) \times 8A = 22 \text{ watts.}$$

V_{in} = Input voltage to the regulator ($V_{out} + 2.75V$)

V_{out} = Maximum DC regulated output voltage

I_{out} = Maximum DC output current

As a point of interest, the maximum continuous current for the regulator set at 5V (TTL) would be 4.329A. Keeping the regulator cool would improve the current output at the lower voltages. Heatsinking of the device will be discussed later.

A disc capacitor of 0.1 μF (C5) should be used to bypass the input, and be installed at the regulator. This will improve transient response and stability. A 10 μF solid tantalum output capacitor (C7) should be used to improve transient response, prevent feedback ringing, and improve the output impedance. The capacitor should be located at the regulator with short leads to reduce the effect of lead inductance. The adjustment terminal should also be bypassed with a 10 μF solid tantalum capacitor (C6). This improves ripple rejection from about 50 dB to 75 dB.

The current set resistor (R2) should be installed directly to the regulator socket, as this will

improve the load regulation. If the current set resistor was placed at the load, with say only 0.05 ohms between the regulator and the load, the effective series loss would be increased 11.5 times to over 1/2 ohm. The parasitic loss resistance of 16GA wire translates to 20 mV/ft at 5A load current, so it is important to locate the regulator near the load. The adjust resistor (R1) should be located at the load ground to improve remote ground sensing and load regulation.

The Transformer

The proper transformer must be able to supply sufficient voltage to prevent the regulator from dropping out of regulation, yet if the voltage is too high, the excess causes unwanted heat and wastes power. When using a fullwave center tap transformer, the equation shown in Formula 1 is used to determine the transformer voltage requirement.

Remember:

V_{reg} = Minimum input-output voltage of the regulator

V_{rect} = Rectifier forward drop at 3x DC output current

V_{ripple} = 10% of $V_{in} = 1.655 V_{pp}$

V_{nom} = Nominal line voltage in ACrms (usually 115 VAC)¹

V_{low} = Low-line voltage in ACrms, 10% below nominal

* The 1.1 value is a correction factor that accounts for the load regulation of the transformer. A 1.2V diode drop is a good starting point before a diode is identified. Schottky diodes improve the drop to approximately 0.5V. See Formula 2.

When a center-tapped transformer is used, correct I_{out} by a factor of 1.2, shown as:

$$I_{rms} = I_{out} \times 1.2 = 8A \times 1.2 = 9.6A$$

Selecting a Rectifier

With our 8A supply, the diodes operate at 4A (center-tapped arrangement). The diodes must survive a shorted output, where the LM338K will provide 12A until it shuts down (6A per diode). Since the diodes conduct current in about 3.5mS pulses, the long term heating effect of the pulsing is roughly equivalent to 8A DC current. This gives rise to the need for a diode that will handle about 14A average current.

When the power supply is first turned on, the filter capacitor appears as a short circuit. The diodes must dissipate all of the initial current

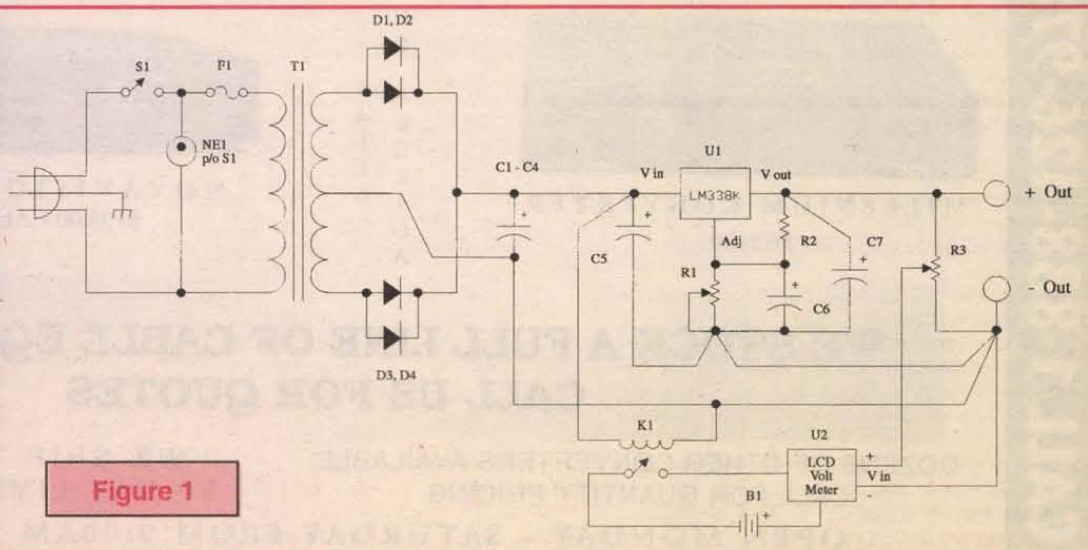


Figure 1

FORMULA 1

$$V_{rms} = \frac{(V_{out} + V_{reg} + V_{rect} + V_{ripple}) \times V_{nom} \times 1.1^*}{\sqrt{2} \quad V_{low}}$$

FORMULA 2

$$V_{rms} = \frac{(13.8 + 2.75 + 1.2 + 1.65) \times 115 \times 1.1^*}{\sqrt{2} \quad 103.5} = 16.7706$$

FORMULA 3

$$I_{surge} = \frac{(V_{sec} \times \sqrt{2}) - V_{rect}}{\text{Transformer Resistance}} = \frac{(16.55 \times \sqrt{2}) - 1.2}{(0.1 \text{ to } 1^*)}$$

FORMULA 4

$$C = \frac{(\text{Period} \times I_{out})}{\text{Ripple}} = \frac{8.3\text{ms} \times 8A}{1.655V} = 0.0401F \text{ or } 40,100\mu F$$

(surge current) with the exception of the loss due to the resistance of the transformer secondary winding. The surge current found is shown in Formula 3.

*A good transformer has a secondary resistance on the order of 0.1 ohm, and a poor one about 1 ohm. The lower secondary resistance of a good transformer requires extra care in selecting a rectifier, as it can develop 222A of surge current. The lower resistance is desirable when you consider I²R loss. Our transformer measured at 0.14 ohms, therefore the I_{surge} value is 158.6088A.

The minimum peak reverse voltage should include cases where the line voltage exceeds nominal, say +10% = 18.2050V_{rms}. The peak of this for a fullwave center-tap configuration is then:

$$2 \times 18.2050V_{rms} \times 2 = 51.4916 V_{peak}$$

The V_{peak} rating should again be increased to allow for line transients. So far, we would like to ensure that our diodes have the following minimum characteristics:

- 1.2V or less forward bias drop
- 14A rms minimum average current
- 159A or better surge current capacity
- 103V minimum peak reverse voltage rating

Searching the typical catalogs show that the economical way to achieve high prv and a large average current rating is to parallel two diodes. A suitable device is found in the Diodes Incorporated series, FR805, which has the following features when operated in parallel:

- Average forward current = 8A x 2 = 16A
- Peak reverse voltage = 600V
- Forward voltage drop = 1.3V
- Maximum surge current = 300A x 2 = 600A

Notice that we violated our 1.2V maximum forward bias voltage drop rule. The effect is to increase our transformer voltage requirement by 0.2V, and to dissipate slightly more heat at the diode. The FR805 is found in a TO-220 case, which will help to eliminate waste heat of about 5W each at full power by enabling us to heatsink the rectifiers to the chassis. It is always good practice to verify the diode polarity with an ohmmeter before installing it. The diodes we received had the anode marked (-).

The Filter Capacitor

It is preferable to calculate for a capacitor conduction time equal to the entire rectifier supply period (8.3 ms). This simplifies the calculations and builds in a conservative value for the filter to compensate for the wide filter tolerances, ranging from -10 to +50%. Formula 4 shows how the capacitor value can be found.

The 8A value is used since the regulator is capable of providing 8A continuously, and the ripple current rating should be two-three times the output current from the filter (16-24A). Another important characteristic is the Equivalent Series Resistance (ESR), which will cause I²R heating and shorten the capacitor's life. Lower ESR is better, and significant reliability improvement is achieved with derating.

A way to provide substantial ripple current economically is to use inexpensive capacitors in parallel. For our supply, four Panasonic TSUP series (pn# P6913) 10,000 uF units are used. The combined effect is:

Capacity: 10,000 uF x 4 = 40,000 uF ±20%
Ripple current: 4.42 x 4 = 17.68A rms
Working Voltage: 35V, 44V surge
Temperature rating: -40 - +85°C

Selecting a Heatsink

The LM338K will dissipate up to 50W continuously, as long as the maximum junction temperature of 125°C (257°F) is not exceeded. The short circuit heating need not be considered as the regulator will go into shutdown in this condition. Heatsink ratings and heat transfer are stated in terms of °C/W, and the principle factors are related as:

$$P_d = \frac{T_j - T_a}{R_{jc} + R_{cs} + R_{sa}}$$

P_d = Power dissipated in the regulator (W)
T_j = maximum junction temperature (°C)
T_a = ambient temperature (°C)
R_{jc} = thermal resistance: junction to case of regulator (°C/W)
R_{cs} = thermal resistance: case of regulator to heatsink (°C/W)
R_{sa} = thermal resistance: heatsink to ambient air (°C/W)

For our regulator, P_d = 50W, and we solve for R_{sa} as follows:

$$\begin{aligned} T_j &= 125^\circ\text{C maximum} \\ T_a &= 40^\circ\text{C (104}^\circ\text{F) (this is a typical design value)} \\ R_{jc} &= 1^\circ\text{C/W} \\ R_{cs} &= 1.2^\circ\text{C/W using dry 2-mil mica insulator} \\ &\quad 0.35^\circ\text{C/W using greased 2-mil mica insulator} \\ R_{sa} &= \frac{125 - 40}{50 - (1 + 0.35)} = 0.35^\circ\text{C/W} \end{aligned}$$

The heatsink thermal resistance must be less than 0.35°C/W to operate the regulator at the extreme limit. The existing unit is very similar to an ECG440B, which has a thermal resistance of 1.8°C/W. A better device is an EG&G Wakefield Engineering pn# 433K, which has a thermal

resistance of 0.37°C/W. That means that our 50W regulator case dissipation will elevate the 433K heatsink 0.37°C/W x 50W = 18.5°C over ambient (58.5°C).

Operating the power supply at room temperature (76°F = 24.4°C) with 13.8V at 8A continuous output develops a heatsink temperature of about 32.58°C (90.65°F).

One might think that a fan should have been

TABLE 1

Power Converter	High-Quality Unit
13.8 VDC ±0.3V	5-13.8 VDC variable
10A constant, 12A surge	8A constant (typ), 12A surge
150 mV rms ripple	0.3 mV rms ripple
2.5% load regulation	0.3% load regulation

installed to the existing 1.8°C/W heatsink. A 200 fpm fan would bring it into the 1.0°C/W range, which is still not quite good enough.

Voltmeter

A good analog panel meter has an accuracy of ±2% and costs in the \$40.00 range. A digital LCD panel meter (voltmeter) has accuracy on the order of ±0.5% and can be found for \$20.00.

We would have used a NJM78L09A +9V regulator, but our voltmeter would not permit a common ground between the supply and the negative input terminal. We thought about using a switched capacitor to isolate the supply ground, but felt it was unnecessarily complicated compared to a 9V D cell battery. Since the unit requires 1 mA to operate, we decided to operate the meter via a relay.

A voltage divider is required for input voltages above 200 mV. The vendor recommends installing 100K and a 9.9M 0.5% metal film resistor. An alternative to 0.5% resistors is to operate the voltmeter in the 200 mV mode, and use more commonly available 1% resistors to provide the appropriate sample voltage. A divider of 2K and 198K can be made up from the standard values of 2K, 178K, and 20K. The worse case and monte carlo voltages across the 2K resistor using a perfect 13.8 VDC source would be:

Worse Case	Monte Carlo (500 Trials)
0.13800V nominal	0.13801V mean
0.14076V maximum	0.14055V maximum
0.13529V minimum	0.13562V minimum

This means that even with 1% resistors, the voltmeter could read from 14.07V to 13.52V due to the resistor tolerance alone, which is an error we can't permit. The way to solve this is to use a trimmer pot with the wiper feeding the voltmeter. The trimmer could be calibrated to produce the exact sample voltage (the more turns, the better). This voltage divider method also avoids a calibration step requiring an accurate +10VDC source.

Install a jumper at P2 for the proper decimal point on the 20V scale. The meter could also be used to measure current if a sample resistor were

TABLE 2

Items to conserve	Items to remove	New Items
Enclosure	Regulator PCB	LM338K + support
Power Switch	Heatsink	Filter capacitor
Fuse Holder	Binding posts	Binding posts
Transformer	Power cord	3 wire power cord
		Voltmeter + support
		Potentiometer
		Heatsink

installed. The problem is that 0.01 ohms would be required to produce 50 mV at 5A and this would contribute to an unacceptable error.

The Power Converter

The supplied schematic revealed that we had, in fact, purchased a regulated supply. In simplified terms, a KA723 regulator was used to drive two parallel 2N3055 transistors. The following specifications were provided, and are compared to the expected project results as shown in Table 1.

The ripple is reduced by a factor of 500 and the load regulation is improved by a factor of 8.3. See Table 2.

Modifications

Install R1 to the enclosure. Install C6 to R1, and connect the R1/C6 ground directly to the (-) output terminal. Install the TO-3 socket to the heat-sink and mount U1 via the mica using heatsink grease on both sides of the mica. Install

R2 between the adjustment pin of U1 and the case connection. Install C5 between the Vin pin and the heatsink ground lug located near U1. Install C7 between the case and the ground lug. The ground lug may be attached directly to the heatsink via a nut and bolt.

Mount the heatsink so that a natural airflow will develop due to convection. Conveniently mount R3 between the (+) and (-) output terminals. Take advantage of the case as a heat sink when mounting D1-D4. Located T1 as far from the output terminals as possible, but watch the balance of the unit (center of gravity).

Use 16GA or larger wire between C1-C4(+) and U1 (Vin), between C1-C4(+) and the rectifiers, and between U1 (Out) and the (+) output terminal. Use a separate 16GA or larger conductor from C1-4(-) to the transformer center tap, and to the (-) output terminal. Keep all of these leads as short as possible. **NV**

Parts List

U1	LM338K
U2	3.5 Digit LCD Voltmeter
T1	115 VAC primary, 16.5Vrms, 10A secondary *
S1	115 VAC switch *
F1	2A slow blow fuse *
F1H	Fuse Holder *
D1-D4	FR805 rectifier
C1-4	10,000 uF, 35V, 4.42A rms ripple current minimum
C5	0.1 uF 25V
C6, C7	10 uF Tantalum 25V
R1	5K ohm linear taper
R2	220 ohm, 1/4 watt
R3	200K, trim pot
J1, J2	Binding terminals
P1	Three wire AC plug and strain relief
HS1	Heatsink, EG&G model 433K
SKT	TO-3 mounting kit and socket for U1
KIT	TO-220 mounting kit for D1-D4
GRS	Heatsink grease
K1	24 VDC relay
B1	9V D cell battery
H1	D cell battery holder
misc	hook-up wire, case, hardware

* part of power converter

WHITE-STAR ELECTRONICS

TEL: 405-631-5153 FAX: 405-631-4788

CONVERTERS:	20	50	100+
Regal CR-83.....	45	39	35
* New, Panasonic TZPC 145.....	75	69	65
DQN-5 (2 or 3) (unmodified).....	45	39	35
DRZ-3 PJ (unmodified) 70 Channel Plain.....	35	32	29
DRX-3 PJ (unmodified) 60 Channel Plain.....	32	30	27

Call for FREE catalog.
405-631-5153



REMOTE CONTROL

HAND UNITS:	20	50	100+
Jerrold Replaces: 400/450/550.....	4.95	4.50	4.25
Scientific Atlanta: 075/175/475.....	4.95	4.50	4.25
8600: On screen display.....	7.50	7.00	6.50
Pioneer: BR 81, 82.....	4.95	4.50	4.25
Panasonic: Call for model #.....	7.50	7.00	6.50
Zenith: All.....	4.95	4.50	4.25
Tocom: 5503-VIP, 5503-A.....	7.00	6.50	6.25
Universal: 4 in 1 R/M.....	7.50	7.00	6.50

Call for Oak, Hamlin, Regal-83, Regency, Texscan, and all others.

Tamper-Bit tools: (10-lot)

Jerrold compatible bits:	
1/4" Stacom Bit.....	\$8.00
Oval Round D.....	\$20.00
Torx Bit:	
Tocom T-8.....	\$8.00
Zenith T-10, T-15.....	\$8.00
Pioneer T-20.....	\$8.00
Scientific Atlanta T-20.....	\$8.00
Pio 63XX Oval.....	\$20.00
Bit Driver Handle.....	\$4.00

We carry most remote hand units. If you don't find the one you're looking for, we can locate for you.

Specializing in large quantities.

HOURS: Monday thru Friday 9 am to 5 pm Central Time.

Call for FREE catalog.

COMPUTER HARDWARE cont.

CONTROLLER CARDS: Vision 330 by #9 2MB PCI new w/drivers & manuals \$50. Stealth 32 2MB VLB graphics \$40. PCI SCSI with S/W new \$50. 1-800-899-7677.



2.5" SCSI case w/pwr cable MAC/IBM (specify) \$29.95. Price Breakers 360-837-3042. Fax 360-837-2057.

20 LEADING Edge XT PCs with dual floppies, keyboard, and monitor. \$60 per complete system. Tandy 1000 HX with color monitor, keyboard. \$65 per system. Credit cards okay. Fax: 501-223-9406. Internet: pager@aristotle.net **Surplus City**, Box 23016, Little Rock, AR 72221.

CRTs CHEAP. Buy direct from the manufacturer. Save money. Mfg. all CRT types since 1950. 3 year warranty. Reg-Res 19" tubes \$75; 25" \$100; hi-res 13" tubes from \$80. We specialize in hi-resolution video/computer CRTs. T.M.C. 215-226-0749/215-223-0388.

MACINTOSH/APPLE Repairs, Parts and Peripherals. Low prices on Macintosh, Apple II and peripheral repairs. Repairs of whole units or repair or exchange of parts. Sales of new third party peripherals. Used equipment available. Mac Shack 716-377-9230, FAX 716-377-9573.

www.usedcomputer.com - The Used Computer Mall™ at <http://www.usedcomputer.com> on the world wide web lists nearly 1000 dealers who buy, sell, and trade used computer equipment, and supply parts and service, too. They are well indexed by brand and type of equipment, so that you can quickly find the dealers you need. Visit the mall today to fill all of your used computer equipment needs.

INTEL I1430VX TRITON MOTHERBOARD WITH 686 CPU, PCI IDE I/O 686 P120+ & MB \$225, 686 P150+ & MB \$275. **COMPUTERS WHOLESALE** 501-259-3386.

FLOPPY DRIVE REPAIRS \$1-\$25. PCs, PS2, Mac, Apple II, 8". Since 1983. 6 month warranty. 1-800-458-6778. ISR, 2217 Downing Ln., Leander, TX 78641.

ZENITH COMPUTER PARTS SupersPort 286/386 keyboards, new, \$25 each. Power supplies \$30 each. Many other parts for Zenith computers. Call Surplus Trading Corp., 616-849-1800. We ship UPS COD.

Weeder Technologies Pro-Kit

PO Box 421, Batavia, OH 45103 weedtech@iglou.com 513-752-0279

Telephone Call Restrictor

Connects to telephone wall jack. Disables all phones on the line if attempting to either: dial a number that has been stored in memory "Block Group" mode or, dial a number that has not been stored in memory "Allow Group" mode. Use touch-tone phone to enter telephone numbers (or prefix) into non-volatile memory, and choose mode. Program or disable from any phone on the line using your private 4-digit password. \$35.00

Caller ID / Computer Interface

Connects between a telephone wall jack and an RS-232 serial port. Decodes the caller ID data sent over the phone line and sends it to your PC/Mac in a pre-formatted ASCII character string. Create your own program to log the name, number, date, and time of all incoming calls. Block out unwanted callers to your BBS/modem. \$34.50

50 MHz Frequency Counter

Reads frequency from 1Hz to 50MHz and displays up to 7 digits on a 16x1 character LCD display. Auto-range feature provides floating decimal point and automatic placement of suffix (Hz, KHz, or MHz). Microcontroller based; allows for highly stable readout and very small parts count, board only 2" x 3" big. \$46.50

IR Remote Control Receiver

Learns and records the data patterns emitted by standard infrared remote controls used by TVs, VCRs, Stereos, etc. Lets you control all your electronic projects with your TV remote. Seven individual I/O pins can be assigned to any button on your remote, and can be configured for either "toggle" or "momentary" action. Re-program over and over for use with different remote transmitters or configurations. \$32.00

DTMF Decoder/Logger

Keep track of all numbers dialed or entered from any phone on your line. Connects to your telephone wall jack. Decodes all 16 touch-tones and displays them on a 16-character LCD display. Holds the last 240 digits in a non-volatile memory. Scroll through and view all telephone numbers dialed, credit card numbers entered, etc. Can also be connected directly to radio receiver's speaker jack. \$54.50

RS-232 Digital Input/Output

Give your home-brewed PC/Mac programs a link to the outside world! 12 I/O pins can be configured individually for input or output. Turn on/off relays, triacs, etc. Respond to button presses, switch changes, 4x4 matrix decoding with auto-debounce. Stack up to 16 units on the same serial port for a total of 192 I/O points. \$32.00

UNDETECTABLE PHONE TAP

- SOPHISTICATED ULTRA HIGH IMPEDANCE CIRCUITRY AS USED BY CIA AND KGB
- NOT DETECTABLE BY EVEN THE MOST ADVANCED TAP SWEEPING EQUIPMENT
- MONITOR CONVERSATIONS, FAXES AND DATA WITHOUT FEAR OF DETECTION
- PLUG INTO ANY TELEPHONE LINE WITH NO CLICK, HUM, NOISE OR VOLTAGE CHANGE
- UNIVERSAL DESIGN ALLOWS MONITORING WITH HEADPHONES, TELEPHONE OR TAPE RECORDER
- VOICE ACTIVATED TAPE RECORDER CONTROL
- DISGUISED AS "TELEPHONE LINE TESTER"
- COMPACT SIZE - BATTERY POWERED



\$109.95 VISA MC COD



Ar² Communications Products

Box 1242 Burlington CT 06013

(203) 485-0310

Write in 180 on Reader Service Card.

SATELLITE TV - HACKERS 'BIBLE'!

The SECRETS are REVEALED!

- The principles of security
- Descrambler building blocks
- Smart cards, information wars & stupid mistakes
- Cracking codes (includes DirecTV source code)
- Installing and hooking up descramblers
- Video manipulative systems...and much more...

CALL 800-483-2423

TO ORDER - Send \$60 plus \$4 s/h to:
Baylin Publications, 1905 Mariposa, Boulder, CO 80302

MASTER, VISA & AMEX /COD orders accepted

Telephone: 303-449-4551

FAX: 303-939-8720

E-Mail: fbaylin@entertain.com



576 pages, 6" x 8-1/2"

FREE CATALOG - books, videos and software on Satellite Television, MMDS & SMATV

Write in 154 on Reader Service Card.

DON'T MISS THIS ONE!

THE GREATER BALTIMORE HAMBOREE AND COMPUTERFEST
HOST TO THE
ARRL MARYLAND STATE CONVENTION
APRIL 5 & 6, 1997
Timonium Fair Grounds • Timonium, Maryland

Saturday 8 A.M. - 5 P.M. and Sunday 8 A.M. - 4 P.M.
Over 17,000 attended in 1996

ARRL Forum & Programs • Banquet • FCC Exams • 3 Buildings
Indoor Fleamarket • Outdoor Tailgate • Acres of Parking
10 Acres of Indoor and Outdoor Sales • 1,100 Indoor Spaces
All spaces by advance sale! • Discount weekend passes in advance only!

For More Information: E-Mail - gbhc@concentric.net, Internet Home Page:
www.concentric.net/~gbhc, Write To: G.B.H. & C., P.O. Box 95, Timonium, MD
21094-0095, Voice or Fax: 1-410-HAM-FEST or Outside of MD 1-800-HAM-FEST

Sponsored by: The Baltimore Amateur Radio Club, Inc.

EXTERNAL SCSI cases with power supply for CD-ROM, tape, hard drive, etc. Includes 2 Centronics 50-pin connectors and internal cables, power LED, power cord, etc. Used but in good condition single device case \$30, 4 device case \$50. New external hard drive case with power supply \$30. Call UTWE 818-930-1121 (10am-5pm PST) or fax 818-930-1123.

COMPUTER BOOKS, parts, cables, and misc. below wholesale. Great for Computer Swap meets, hamfests, flea markets. For free catalog write: Computer News, PO Box 50127, Casper, WY 82605.

KITS 3.5" 200MB SCSI w/Adaptec 16 bit H/F & cable \$75. Colorado Tracker 250MB external parallel port back-up \$50. Colorado Jumbo internal floppy based back-up, 120MB & up, \$25 & up. 1-800-899-7677.

DEC EQUIPMENT WANTED!!! We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), DSD, Datability, Dialog, other DEC compatibles, and Computer Output Microfilm (COM) units. Please call for a quote or fax us your equipment list. We buy, sell, and trade. **KEYWAYS, INC.**, 513-847-2300 OR fax 513-847-2350.

TEST LAB CO.



SPECIALS

COUNTERS

HP 5315A, 100MHZ, GENERAL PURPOSE	\$ 600.00
RACAL DANA 1991, 120MHZ, UNIVERSAL	\$ 800.00
FLUKE 1900A, 120MHZ, ECONOMY	\$ 225.00
HP 5370A, UNIVERSAL COUNTER	\$ 2500.00
EIP 545A, 10HZ-18GHZ COUNTER	\$ 2000.00

SIGNAL SOURCES

GIGATRONICS 600&900 SERIES	CALL
EIP 924, SYNTHESIZER 3-12GHZ	\$ 1800.00
PHILIPS PM5715 PULSE GENERATOR 50MHZ	\$ 800.00
WAVETEK 2002, 1-2500MHZ SIGNAL GENERATOR	\$ 1850.00
HP 8640B, 1,2,3 SIGNAL GENERATOR, COVERS TO 1024MHZ	\$ 2495.00
TEKSG503 LVL SINE WAVE GENERATOR 250KHZ-250MHZ	\$ 850.00
HP 651B TEST OSCILLATOR 10HZ-10MHZ	\$ 495.00
HP 3310A/B FUNCTION GENERATOR, 5MHZ, A VERSION-\$ 450. B VERSION \$ 525.00	

SIGNAL MEASUREMENT

MARCONI 2957B COMM ANALYZER	\$ 6000.00
HP 1980B OSCILLOSCOPE	\$ 675.00
HP 435A POWER METER W/O SENSOR	\$ 495.00
FLU 8920A TRMS VOLTMETER	\$ 1000.00
HP 3577A/35677A 200MHZ NETWORK ANALYZER	\$ 16000.00
TEK 7L5/L3 AUDIO ANALYZER COVERS TO 5MHZ, REQUIRES MF	\$ 2500.00
HP 339A DISTORTION ANALYZER	\$ 1800.00
BOONTON 82AD MODULATION METER	\$ 1600.00
ANRITSU ML522F 300-1000MHZ RECEIVER	\$ 1795.00

POWER SUPPLIES

B-K PPS100, 30V, 3.5A GPIB, 200 SETUPS IN MEMORY	\$ 600.00
B-K PPS300, 40V, 7.5A GPIB, 200 SETUPS IN MEMORY	\$ 800.00
B-KPPS600, 60V, 10A GPIB, 200 SETUPS IN MEMORY	\$ 1400.00
B-KPPS1000, 60V, 17A GPIB, 200 SETUPS IN MEMORY	\$ 1800.00
HP 6264B 20V, 20A 120VAC INPUT	\$ 600.00
HP 6033A 200W AUTORANGING POWER SUPPLY	\$ 1950.00
KIKISUI PAL35-20, 35V, 20A	\$ 700.00
HP 6266B 40V/5A DC POWER SUPPLY	\$ 550.00
SOR SRL40-50, 40V/50A	\$ 1100.00

MISC.

GR 1658 LCR METER	\$ 1500.00
FLU 2280B DATA LOGGER	\$ 800.00
HP 2225A GPIB PRINTER	\$ 99.00
HONEYWELL 1858 VISICORDER	\$ 4000.00
HP 4342A Q METER	\$ 2400.00
STANFORD RESEARCH SR510 LOCK IN	\$ 1000.00
TEKTRONIX OF150 OTDR	\$ 4500.00
TEKTRONIX TM504 OR TM503	\$ 200.00
HP 3497A DATA ACQ. MAINFRAME	\$ 1200.00
HP 44421A 20CH MUX FOR 3497A	\$ 300.00
HP 44428A 16CH ACTUATOR	\$ 300.00
TEK 577D2/177 CURVE TRACER WITH STANDARD INPUT	\$ 2200.00
AC/DC EL750B ELECTRONIC LOAD, 750 WATT	\$ 995.00

THESE INSTRUMENTS ARE IN EXCELLENT CONDITION. WE GUARANTEE THEY WILL MEET MFRS SPECIFICATIONS, AND ARE SUPPLIED WITH A MANUAL, POWER CORD AND 90 DAY WARRANTY

PHONE 800-442-5835 OR 415-969-1142
FAX 415-969-0334
EMAIL TESTLAB2@IX.NETCOM.COM
WEB http://www.testlabco.com

TEST LAB COMPANY

1066 LINDA VISTA AVENUE
MOUNTAIN VIEW, CA 94043



Write in 182 on Reader Service Card.




Digicom Communications, Inc.

Happy New Year
Dealers New Year Special
Don't Miss Out
Call for the best
Cable Prices

Sales: (800)250-3187

Customer service (305)638-8242

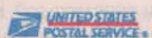

<http://www.a1digicom.com>
<http://members.aol.com/digicominc.html>
 E-mail: digicominc@aol.com

Sorry,
 no Florida
 or California sales

Write in 176 on Reader Service Card.

CRYSTAL CONTROLLED FM TRANSMITTER W/ RECEIVER & RECORDER



TRANSMITTER

Size - 2"x 3"
 2000' range (line of sight)
 170 MHZ - range
 Sens.: 85 db spl @ ±7khz FM
 8 Channels available
 Freq. Response: 100-10,000 hz
 Battery life: 9V Alkaline=12 hrs.
 9V Lithium=20 hrs.

FCC APPROVED

Transmitter: \$150.00 +\$7 shipping
 MicroRecorder, 4hr. Voice Activated: \$150.00 +\$7 shipping
 Programmable Scanner: \$150.00 +\$7 shipping
 Comprehensive 50 page catalog - \$3.00

Voice Changers, Transmitters, Micro Videos, Long Play
 recorders, Surveillance, Counter-surveillance & much more!
 For more information call 407-725-1000. COD ok.

USI CORP

P.O. Box 2052 - Melbourne, FL 32902

Write in 69 on Reader Service Card.



CUNARD ASSOCIATES

R D 6 Box 104, BEDFORD, PA 15522
 TEL / FAX 814 623 7000

THE POWER PRO

IF YOU NEED NEW BATTERIES FOR YOUR ELECTRONIC EQUIPMENT
 DON'T PITCH EM! SEND THEM TO US FOR REBUILDING!

- WE INSTALL NEW Ni-CAD BATTERIES INTO YOUR ORIGINAL CASE.
- WE IMPROVE CAPACITY TO BETTER THAN ORIGINAL.
- WE FIX WHAT CAN'T BE FOUND. (OR AFFORDED)
- WE PROVIDE QUICK SERVICE. / EXTENDED LIFE FOR OLDER EQUIPMENT.
- WE PROVIDE FREE QUOTES. / FREE RETURN IF QUOTE IS REFUSED.
- WE PROPERLY DISPOSE OF YOUR OLD CELLS BY RECYCLING.
- WE GIVE YOU A 12 MONTH WARRANTY.
- WE WILL BE HERE WHEN YOU NEED US. / 10 YEARS IN BUSINESS.
- WE SAVE YOU \$\$\$ MONEY !!!



ALL MAKES
 & MODELS

NO JOB IS TOO LARGE OR TOO SMALL WE OFFER VOLUME DISCOUNTS
 TO LAW ENFORCEMENT / COMPANIES / FIRE DEPARTMENTS / UNIVERSITIES
 FOR MORE INFORMATION ABOUT YOUR PARTICULAR NEEDS, WE CAN BE CONTACTED
 VIA PHONE OR FAX AT (814) 623-7000 OR VIA E-MAIL TO: ZAPREM@AOL.COM
 OR SEND YOUR PACKS FOR QUOTATION VIA UPS OR PRIORITY MAIL TO ADDRESS ABOVE.

GENERAL ELECTRIC	STANDARD	BENDIX KING
MPD/PLS - MPRMPS/MPX	CNB111/HWA110 \$ 29.95	KR105/LAA125 \$ 34.95
19A704850P(1200mAH) \$ 34.95	CNB120/HWA120 \$ 34.95	KENWOOD
19A704860P(1800mAH) \$ 39.95	CNB121/152/153 \$ 39.95	PB2 / KNB3 \$ 29.95
PL19D429763(777)G1/3 \$ 37.95	UNIDEN	PB21/21H \$ 14.95
MAXON SA-1155 \$ 39.95	APX650 \$ 34.95	PB25/H26 \$ 24.95
MOTOROLA	APX1100/1200 \$ 39.95	YAESU
P200/H7600/MT1000	BP100/200/205 \$ 19.95	FN34/12/27 \$ 32.95
NTN5521/4585/4824/5414 \$ 37.95	ICOM	FN31/14/16/26S \$ 32.95
MIDLAND	BP2 / BP3 /BP22 \$ 18.95	FN317/25 \$ 23.95
70-B32 / 70-B36 \$ 39.95	BP5 / BP23 / 24 \$ 24.95	COMPUTERS
70-B10 / B16 / B19 / B21 \$ 39.95	BP7 / CM7 / BP8 \$ 34.95	SEND PACK FOR QUOTE

BATTERY REBUILD SERVICE

MANY OTHERS AVAILABLE WRITE OR CALL



FREE CATALOG

ADD \$ 4.50 SHIPPING & HANDLING PER ORDER



Write in 102 on Reader Service Card.

MIDWEST ELECTRONICS

124 12TH AVE. SOUTH, MINNEAPOLIS, MN 55415

PHONE: (612) 339-9533 FAX: (612) 305-0964

WWW.MIDWEST-ELECTRONICS.COM

COMPUTERS

PENTIUM 90, SLIMLINE DESKTOP, 8MB RAM, 256K CACHE,
 528 MB HD, 1.44 FD, 4XCD, SOUND, PCI 64 BIT 1MB VIDEO,
 2S1P, KB, MOUSE, SPKRS, 14" SVGA MONITOR **\$900**

MONITORS: 15" AT&T SVGA \$290 14" ADI SVGA \$199

IDE DRIVES: 540MB \$139 40MB \$35 4XCD \$65

MULTIMEDIA: GALLANT 16 BIT SOUND CARD \$50
 28.8 MODEM WITH VOICE \$99

VIDEO MEMORY: 512K BYTE OF 4X256K 80NS DIP \$5
 1M BYTE OF 16X256K 70NS J-LEAD \$25

MOTHERBOARDS: 486DX2 VL BUS, 8-30 PIN SIMM,
 SOCKETED FOR CACHE, AMI BIOS, WITHOUT CPU \$25
 WITH SX 25 \$30 SX 33 \$32 SX 2/50 \$45

P5 PCI BUS, 3 PCI, 4 ISA, 4-72 PIN SIMM, 2 IDE, FDC, 2S1P,
 256K PIPELINE CACHE, 3V REG., WITH CYRIX P150+ \$275

CPUS: 486DX33 \$30 486SX33 \$7 486SX2/50 \$20

CONTROLLERS: IDE ISA 2 IDE, 2FD, CABLES \$12
 IDE CACHING ISA 4 IDE, 2FD, 4-30 PIN SIMM \$29
 I/O AT 2S1P1G 16550 UART \$19
 I/O VLB 2IDE,FD,2S1P 16450 \$15
 I/O AT 2S1P1G \$12

MEMORY: 30 PIN 1MB X 9 80NS \$12
 72 PIN 1 X 32 \$30, 2 X 32 \$60

MANY OLDER AND SURPLUS COMPUTER PARTS AND
 SYSTEMS VISIT OUR WEB PAGE OR CALL.
 QUANTITY DISCOUNTS AVAILABLE.

Write in 138 on Reader Service Card.

TANDY/RADIO SHACK Model 1/3/4,1000
 Support. Monthly magazine, software, parts,
 repair. Computer News, POB 50127, Casper,
 WY 82605-0127. 307-265-6483.

ZENITH COMPUTER parts, boards, periph-
 erals, keyboards, new and used computers.
 Call Les or Mike at: Surplus Trading Corp.,
 Benton Harbor, MI. 616-849-1800.



WANTED: EXCESS ELECTRONIC INVEN-
 TORIES, ICs, MEMORY, EPROMs, PALs,
 LEDs, CIRCUIT BOARDS, DIODES, AND
 TRANSISTORS. CALL ACTIVE MICRO,
 310-494-4851 OR FAX 310-494-4913.

THE MOST EXTRAORDINARY hacking
 catalog in the world! www.spectre-press.com

V.35 BREAKOUT box and activity monitor;
 new with case. Black box #TS291A, list price
 \$625, yours for \$300 or BO. Also, four 1
 Mbyte 40-pin SIMMs for Toshiba T5200
 portable computer, \$60. Call evenings 617-
 327-9025.

START YOUR OWN TECHNICAL VEN-
 TURE! Don Lancaster's newly updated
 INCREDIBLE SECRET MONEY MACHINE II
 tells how. We now have autographed copies
 of the Guru's underground classic for \$18.50.
 Synergetics Press, Box 809-K, Thatcher, AZ
 85552. 520-428-4073. VISAMC.

WANTED!

WE PURCHASE SURPLUS LASERS, LASER RELATED EQUIPMENT AND OPTICAL EQUIPMENT

We also sell LASER's for researchers, industrial applications, educational purposes, entertainment and hobbyists.



e-mail mkenny1989@aol.com
FAX (909) 278-4887

1269 W. Pomona, Corona, California 91720

CALL FOR FREE CATALOG!

(909) 278-0563

See our catalog on the internet!
<http://www.mwkindustries.com>

Write in 32 on Reader Service Card.

EPSON DFX5000 dot matrix printer, excellent condition. High speed, front and rear tractor feeds. \$350. Hewlett Packard Jet Direct 2552 BNC, Ethernet, Appletalk \$150. 847-394-1656 aft. 6pm. E-Mail: Teslacoil@AOL.Com



BEEP BEEP? Repair IBM compatible PCs with the "POST CODE MASTER" plug-in card. Shows result of Power On Self Test performed by all major BIOSs. Manual reveals their meaning and also explains those cryptic beep codes. \$59. MSD, 4100 Moorpark Ave. #104, San Jose, CA 95117. 408-296-4000, Fax: 408-296-5877.

MONITOR ADAPTERS. Convert OEM. (incl. PGA) 31.5KHz & above monitors with BNC connectors to PC use. Model VA10 VGA to RGB+ Sync \$45. Model VA11 VGA to RG/Sync-B \$55. VA12 VGA to PGA (DB9) \$45. Rich, Pikul & Assoc., 101 Glenfield Dr., Festus, MO 63028. 314-937-0335.

TRS-80 MODELS 1, 3, 4, 100 Pocket Computer, COCO. Hardware, software, repair/replacement parts, accessories. #10 SASE for list. Pete Bumgardner, 100-D W. Falls St., Kings Mountain, NC 28086. 704-730-0893.

MONITOR TECHNICIANS! 10 step program for successful analysis; diagnosis, and repair of high voltage and power supply problems in computer monitors. Booklet available for \$20 from Computer Vision, 6905 Indian Bay Rd., Montague, MI 49437.

INTEL ZAPPA Pentium motherboards, P75 to 133, w/IDE, hi-speed I/O on board, w/cables, mini AT size, w/docs, \$75, \$210/3. Closeout DEC 486DX33 PC pizza box WS, bare bones, case, PS 2M VRAM, SVGA, 2S, 1P, & MP, IDE, H&F cont., Token Ring, ext. SCSI-2, new bulk packed size: 15"x15"x2.5", 17" SVGA monitor 1280x1024, .27dpi, mouse, 101 keyboard, software, \$319. Have CPUs, motherboards, 486 & Pent. computers. Video cards also at super prices. See last cat'l SASE. BNFE, Rte 1S, Peabody, MA 01960. WWW.BNFE.COM V508-536-2000, F508-536-7400. Estab. 1964.

MONITORS REPAIRED. "Computer Vision" has flat fee repair of monitors; 14", \$70; 17", \$90. E-Mail to philip833@aol.com

LIQUIDATING WAY Below Distributor Cost NOW, They're Affordable! #1 Choices of America's Top Professionals EITD Electronics Yellow Pages



\$25!
* As Low As
\$110 From Publisher
* If Purchased with ANY other item
Only \$35 When purchased alone

You've never had a Directory Anything like this one. Generic phone books on a CD DO NOT contain the **Wealth of Contacts** you will find here. In just seconds, locate Distributors, Manufacturers and Service providers for **Products, Services or ANY Component Parts** you can possibly imagine! The EITD allows you to scan by Product Description and also contains a separate White Pages for **Half a Million Industrial Business Listings**. Ads in the Yellow Pages allow you to locate the Co's with Product Lines that best suit your needs. The Complete 2 Volume 4.5 lb Set is a Reference you'll find yourself using Constantly and Wonder how you ever did without it!



The "REFERENCE"
Semiconductor Crossreference & Consumer Electronics White Pages
* As Low As \$79!
* If Purchased with ANY other item
Only \$99 When purchased alone

The "REFERENCE" is the Most Comprehensive Cross REFERENCE Software on the market Today. Just under a Half Million Devices Listed! Swells to over 14 Meg. Extremely easy to use. You'll be Navigating your way around in just minutes. Three Databases are Included for Cross-referencing: Transistors, IC's & Diodes. Practically any device selected yields a wide variety of potential replacements. Case Style Drawings, Lead Configuration and Pin-out are available for many devices. Coverage of Replacement Numbers is very impressive. Many helpful extras are also included such as Conversion Utilities, Formulas, Resistor Library, Wire Gauge & More. NOW, with the Consumer Electronics "White Pages" there is a Directory specifically Designed to meet the needs of Service. When customers walk in with "Off the Wall Brands", where do you get parts? Four Directory Databases are Included: [Consumer Electronics Parts Sources], [Consumer Electronics Manufacturers/ Distributors & Importers for Equipment, Accessories and Services], [Computer Manufacturers/ Integrators/ Accessories & Related Services], [Semiconductor Manufacturers]. When combined with the Commercial Listings of the EITD you'll Finally have all the Directory Power you need.

\$55! ICM "The Bible" of the IC Industry

\$195 From Publisher
\$55 When purchased with ANY other item. Back Issue covering most Current Production IC's. Perfect for Service & Moderate Design Work (quantity limited)

Above Only \$69 If purchased alone

\$159! 97 ICM Books (for Advanced Design work) \$195 From Publisher

\$189! 97 ICM on CD \$235 From Publisher

\$88!! 97 EEM on CD only Limited Supply at this Price



The 3 Volume ICM is the Best & Most Comprehensive IC Reference Ever Published. The depth of your NEW ability to search will blow you away. There is NOTHING else like it in the world! 100,000 IC's of EVERY KIND from Every Manufacturer. Specifications, Selected Data Sheets, Every known Cross-reference, Alternate Sources, Manufacturer Profiles & Distributors. Perfect for Sales, Service, Engineering & Experimenters. Thousands have gladly paid \$195 (and at 9 lbs it's well worth it). If you're still squeezing an ICM from the 80's, you already know their power. With Prices like these, NOW is the time to move up! The EEM is the Largest Component Parts Directory available. All the Major Parts Manufacturers display Entire Product Lines with Pictures & Data sheets. Cabinets, Transformers, Pots, Semi's, Resistors, Capacitors, Crystals, Coils, Connectors, Wire, Heat sinks, Switches, Fuses, Speakers, Displays, an Endless list! This Extraordinary Library is perfect for Service, Designers, Distributors & Experimenters. The 4 Volume (18 Lb) EEM Set shown is now available on CD ONLY.

Netcom 800-881-6247 ext 6300 516-826-1808 x 6300 10am-10pm EST 7Days

Write in 101 on Reader Service Card.

Nuts & Volts Magazine/January 1997 17

MOTOROLA® UHF DATA TRANSCEIVERS




\$69.00 pr.
Plus S&H

Limited Quantity Offer!

NEW!

\$74.95 ca.
Plus S&H

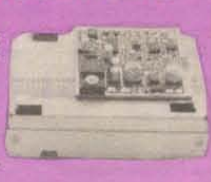

MODEL PI-10 INTERFACE MODULE FOR UHF Data Transceiver

A newly designed interface for the UHF data transceiver provides a simple straightforward circuit which interfaces most popular functions directly.

- Built-in voltage regulation... a 12 vdc power source will run the transceiver and interface board.
- 2 adjustable audio inputs: one for direct transmit modulation and another for PL or other input.
- Receiver audio out and speaker output with squelch action.
- Carrier detect for C.O.S. operation as well as unfiltered receiver detector output.
- Push-To Talk transmitter control.
- Compact size: 1.62 X 1.75 plug-in board (see photo directly above). Plug it in, connect it up, and it works!

Motorola (P-10) HLE9018 - 1 watt crystal controlled UHF 450-470 mhz. transceiver (presently on 467.850 or 467.925). Removed from data service in metal housing shown. 2 freq capable. Dim. 3"x 2 3/8" x 5/8". Wt 4.25 oz. Requires 7.5 vdc. Direct FM. Excellent for packet data, radio control, etc. With documentation. Pair for \$69.00 (NOTE: Motorola is the registered trademark of Motorola, Inc.)

SPECIAL PACKAGE DEAL!
One data transceiver with PI-10 interface for \$99.00

MDM Radio, Ltd.

7112 W Roosevelt Rd.
Oak Park, IL 60304



(708)848-4210

(708)848-0230 FAX

Write in 63 on Reader Service Card.

The Wireless Solution!

RF Link Wavecom Jr.

Accepts Output From... Video Camera / VCR / Camcorder / Satellite Video Output Etc. Receiver
Puts Out Channel 3 or 4 or Base Band Audio Video Recommended CCD Camera: w/audio 2-1/4" x 3-1/4" x 1-1/4" WHD CVC-300 \$199.95

Panasonic 550 MHz Cable Converter

The Best!
Goes To Channel 99
model #TZPC145-3G 69.00

OSCILLOSCOPES

B&K 20 MHz Dual Trace

- 1 mV/div sensitivity
- AUTO/NORM triggered sweep operation
- AC, TVH, TVV and line coupling
- Calibrated 19 step time-base with x10 magnifier
- Compact low-profile design

model #2120 2 year warranty... 385.00
model #2125 with delayed sweep... 529.95

Pinhole Camera

- Requires 1/16" opening size
- 1-1/2" x 1-1/2" x 7/8"
- Power 7.5-12VDC n.a. 8 lux
- 3.8mm lens included
- 380 lines resolution
- 12V DC Power Supply 9.95

model #CVC50PH 139.95

NTSC to PAL Video System Converter


\$289.95
Converts any NTSC video system to PAL format
Easily connects between your VCR, Satellite Receiver, or Camcorder and your TV to view PAL video systems

Call For FREE Catalog & Technical Assistance
Add \$8.95 Shipping/Handling, NYS Add Tax, Visa/MC/Discover/Amex
MAIL ORDERS TO: 70 CAIN DR. BRENTWOOD, NY 11717

1-800-945-0909
FAX: 516-435-7494

Write in 126 on Reader Service Card.

VGA LCD's Served Here

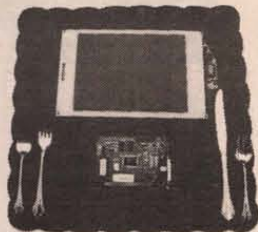

ROCK BOTTOM PRICES!

VGA LCD Controllers for PC ISA Bus
EarthLCD/M Monochrome LCD Controller \$160
EarthVision/ISA Color LCD Controller \$280
EarthVGA Analog Input Ctrl. (VGA to LCD) \$599

NEW! Touch Screen Kits

Analog resistive touch screen with controller \$249
VGA Display Kits Include LCD, Controller, & Backlight
7.4", 9.4", 10.4", 11.3" Starting at \$220
Mono, Dual Scan & Active Matrix in Stock

Displays Only

Both new and surplus color displays from \$99
Digital LCD Monitors Desktop LCD & ISA Controller
Monochrome Monitors Starting at \$400
Color Monitors Starting at \$600

See Earth on the Worldwide Web! <http://www.flat-panel.com>



EARTH
Computer Technologies

Ph. (714) 448-9368
Fax: (714) 448-9316

Write in 179 on Reader Service Card.

STEPPER DRIVERS & CAM SOFTWARE: microstepping full, 2, 3, 4, 5, 6, 7, 8, 3, & 6 amp starting at \$117. Software: Plotcam motion \$149; Z-trace isolation (PCB Gerber file toolpath) \$299. heater@digital.net MSG/FAX 407-452-7197, 407-459-2729.

HAM RADIO 2000 CD-ROM contains over 10,000 files in 934 directories of the latest HAM RADIO programs. Categories include antenna, BBS, exam tutors, FAX/SSTV, frequency lists, HF, logs, Morse Code, packet, QEX, control, satellite, scanner, TCP/IP, & VHF. Win3.1/Win95 interface lets you search through entire disk for any text. Only \$24.95 + \$5 S/H. Also available **VISUAL BASIC 2000 CD-ROM** with over 15,000 files and 1,200 directories of VB custom controls, source code, utilities and more! Search through the entire CD including forms for any text. Double-click any form to load into editor. Double-click on MAK files to load up to two copies of VB! Only \$29.95 + \$5 S/H. 30-day money back guarantee! ByteSize CD-ROM 714-650-3401, fax 714-650-3420. E-Mail: byteszcd@ix.netcom.com

PC VIDEO cards. Orchid Kelvin VLB or ISA new with DOS Win31X, Win95, WinNT, and OS/2 drivers, 1 meg/2 meg \$45/\$55. NEW Trident VLB 9440 AGI graphics accelerator, DOS, Win311, WinNT, and 95 drivers included, 1 meg/2 meg \$25/\$35. ISA 512K VGA cards NEW \$25 QUANTITY DISCOUNTS! Call UTWE 818-930-1121 (10am-5pm PST) or fax 818-930-1123.

PENTIUM MOTHERBOARDS 75/100/120/133/150/166/200, Triton I-VX chipset, Plug-N-Play BIOS, Pipeline cache, 3 ISA/4 PCI, cache module socket, 256K cache \$109, Triton II-HX boards with 512K cache \$139, Pentium CPUs @ \$109/155/168/245/330/399/599. IBM/Cyrix 686 P120/150/166 @ \$106/139/199. 12-speed CD-ROM, audio button \$139, 72-pin SIMMs, 60ns EDO, 16MB \$89, 8MB \$49. Call for current pricing, other parts and illustrated catalog. 1 year warranty, FOB tech-specialties, Inc., 5703 Heffernan, Houston, TX 77087-4113. 1-800-864-5391 for orders and tech support, fax: 713-307-0314.

DISCOUNT COMPUTER HARDWARE. All brand new. No refurbished merchandise. Motherboards w/CPU, cases, modems, and much more. For information please send request to **GTH3 COMPUTERS**, Dept. NV, 1726 Avenida Sevilla, Oceanside, CA 92056-6204.



19" RACKMOUNT PC chassis: Heavy duty, 4U, 8 slots expandable to 12, two (one hidden) 3.5"/two 5.25" drive bays, front panel fan, mini tower power supply not included, \$229 with this ad! Monitor chassis \$285, keyboard chassis \$145. We do business COD, cashier's check only. Computronics Technology, 972-242-8087.



LA PAZ

Electronics International

COMPUTER PARTS

DRAM SIMM

1Mx90 SIMM \$18
4Mx90 SIMM \$39
1Mx32/36-70 72-pin SIMM (4MB) \$24/32
2Mx32/36-70 72-pin SIMM (8MB) \$39/69
4Mx32/36-70 72-pin SIMM (16MB) \$95/112
256Kx4 DIP DRAM \$4.00
1Mx1- DIP DRAM \$3.00
1Mx4-80 DIP/ZIP DRAM \$18/15
256Kx8-60 VIDEO SOJ DRAM \$18.50
256Kx16-70 VIDEO SOJ (2CAS/2VE) \$20/24
256Kx16-70 VIDEO SOJ (2CAS) \$10

CPU & CO-PROCESSORS

386DX-33 INTEL CPU \$20
486DX-33 INTEL CPU \$25
486DX2-66 INTEL (SV) CPU \$65
486DX4-100 INTEL (SV) CPU \$39/119
PENTIUM 90/100 CPU \$130/139
80287-12 CO-PROCESSOR \$19
80387SX/DX CO-PROCESSOR \$32
68882RC33 FPU \$35

MISC.

PENTIUM (MMT) MHz CPU MOTHERBOARDS FOR ALL PACKARD BELL CASES \$395
MOTHERBOARD BIOS UPGRADES CALL
486 CPU 5V to 3V ADAPTER SOCKETS \$35
EPROM PROGRAMMERS \$129.95/139.95
16550 40-PIN UART \$10.50
EPROMS & FLASH:
27C512-150NS \$3.95
27F010-150NS \$5.25
27F020-150NS \$19.50

CACHE SRAM

64Kx1-15ns 22-DIP \$7.95
8Kx8-15/20ns 28-DIP \$3.50/3.00
32Kx8-15/20ns 28-DIP \$2.50/2.00
64Kx8-15ns 32-DIP \$8.00
128Kx8-15/20ns 32-DIP 3mil \$19/18
128Kx8-25/20ns 32-DIP 4mil \$18/16

* OTHER PARTS AVAILABLE, CALL FOR QUOTE * VOLUME DISCOUNTS OFFERED
* PRICES SUBJECT TO CHANGE WITHOUT NOTICE * TERMS: COD (CASH), VISA/MC
MINIMUM ORDER: \$20 SHIPPING & HANDLING: \$6 MIN
ORDER (800) 586-4199

LA PAZ ELECTRONICS INT'L
P.O. BOX 261095, San Diego CA 92196
TEL (619) 586-7610 FAX (619) 586-1482

Write in 186 on Reader Service Card.

Converters ★ Remotes ★ Converters ★ Remotes ★ Converters ★ Remotes

Modern Communications • (405) 691-0594 TEL & FAX

Converters:

	10	50	100+
Panasonic: TZPC145	\$75.00	\$69.00	\$65.00
DQN-7	\$45.00	\$40.00	\$35.00
DRZ-3 or DRX-3-105	\$29.00	\$25.00	\$20.00

Remotes:

Jerrold: 400, 450, 550	\$4.50	\$4.00	\$3.75
CFT: 2XXX	\$4.95	\$4.50	\$4.25
S/A: 075, 175, 475, 8600	\$4.95	\$4.50	\$4.25
Zenith:	\$4.95	\$4.50	\$4.25
Tocom: VIP	\$4.95	\$4.50	\$4.25
Tocom: 03-A	\$6.95	\$6.00	\$5.75
Pioneer:	\$4.95	\$4.50	\$4.25



Parts, Parts, Parts

	50	200	500
18 VAC, 300 MA P/S	\$3.00	\$2.50	\$2.00
68 MHz Saw Filters	\$2.50	\$2.35	\$2.10
Pic 16C54	\$2.20	\$2.10	\$2.00
Pic 16C56	\$2.35	\$2.30	\$2.25
E-PROM 2764	\$0.95	\$0.85	\$0.75
4 MHz (Crystal Resonance 2 pins)	\$0.45	\$0.40	\$0.35

Call for FREE CATALOG
(405) 691-0594


Converters ★ Remotes ★ Converters ★ Remotes ★ Converters ★ Remotes

BUILD YOUR OWN IBM COMPATIBLE COMPUTER for as little as \$399 with help of an easy-to-view 75 minute video tape that shows you how. This award winning VHS tape will show you how to save time and money by assembling any 286, 386, 486 or Pentium computer from available parts in a step-by-step easy to follow procedure. It's easy when you know how. Order your personal tape today while the limited supplies last for only \$29 (reg. \$59.95) plus \$2.95 P&H. Free bonus gift. Send check to: **EVP, PO Box 2201, Northlake, IL 60164-0201** or call: 1-800-754-5096 now!



800MB TAPE BACKUP WITH TAPE FOR ONLY \$49. Colorado DJ-20 includes 250MB tape and software. Works in any PC from existing floppy controller. Directly supported by Win95. Fast! Transfers 120MB in 13 min. 800MB tapes \$22. **The best insurance from disk crashes, viruses, theft, accidental erasure and easiest way to transfer files.** Money back guarantee. Equiptek, 415-244-9438, M-F 9-5 PST. E-Mail: equiptek@pacbell.net

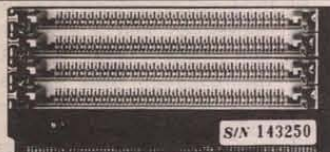
486 COMPUTER motherboard \$700, 686 motherboard \$275, 686 computer, monitor \$1,700. SVA monitor \$100, EGA, CGA monitor \$50, \$30. HP plotter 7475 \$100, HP 7395B D size plotter \$500. HP plotter 7550A \$175. 386 computer \$200, 286 computer \$50, Epson printer \$30. XT computer \$30. HP Think Jet printer \$40. Much more. Call 714-827-7345.



IBM SIMM converters. 4x30P/1x72P \$9.95. 2x72P/1x72P \$14.95. 4x30P/1x30P \$19.95. Price Breakers 360-837-3042. Fax 360-837-2057.

FROM SOURCE: motherboards with IDE-I/O controller on board, CPUs, mice, CD-ROMs, video controller, and other parts. Call NAME-TECHS: 312-395-1142, Fax: 312-395-1042.

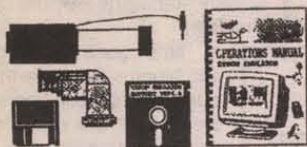
SONY/AMEGA MULTISCANS 15", 0.26DP 15.7 thru 36KHz CGA thru SVGA (1024 x 768 I). \$175. Generic VGA color monitors from \$125. Expert Sony repair, parts available. **Dealer discounts.** Refurbished guaranteed. Pikul & Assoc., 101 Glenfield Dr., Festus, MO 63028. 314-937-0335.



EPROM EMULATORS. Test your code without disconnecting equipment. All ICs mounted in sockets. MODEL-32 (2764-27256) \$109. MODEL-64 (2764-27512) \$129. **PRO-SERIES.** Includes battery back-up and real time link for single byte changes. PRO-128 (2764-27010) only \$199. PRO-512 (2764-27040) for \$259. \$5 shipping. Visa. Logical Design Tools, Inc. 512-888-4535. Internet: <http://www2.interconnect.net/dti/hom.htm>

BRAND NEW w/warranty! Motherboards w/CPU + 256K cache P 150+ \$195, P90+ \$145 586-100 \$125. SVGA monitors 14" \$150, 17" Multisync \$395. 810 2.5 gigabyte hard drive \$145-250. SCSI controller cards floppy/hard drives \$25. 1.2 & 1.44 floppy drives \$25. Windows NT software ver. 3.51 file-server \$350. Workstation \$175. Ver. 4.0 w/10 user license \$395. Windows 95 full version \$95. Corel Word Perfect Suite (includes 5 programs) \$79. Ink jet printers \$100. Hewlett Packard laser printer \$295. Call for complete list and monthly specials. Call CCI 714-778-0450.

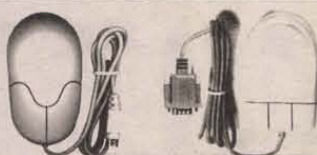CHAFFIN ELECTRONICS INC. Call us for all your IC needs. Let us save you \$\$\$\$. Call Sales 614-574-4456, Sales 614-574-6906, FAX 614-574-2124.




MACINTOSH ADB mouse \$18.95. IBM serial mouse w/sfwr \$7.99. Mouse pads \$1.95. Price Breakers 360-837-3042. Fax 360-837-2057.



DATA*LNK EASILY connects shortwave radio to PC serial port. Receive satellite photos, weather charts, & code on screen. Price reduction! Send ONLY \$25 + \$2 S&H, for 25-pin DATA*LNK (kits \$19). 9-pin DATA*LNK \$35 + \$2 S&H. INFO, SASE. Send check or MO: Howard Olsen, 5411 Atlantic View, St. Augustine, FL 32084.

PLOTTERS: HP 7580B drafting plotter (sizes A-D) \$1,300. HP 7586B (sizes A-E) \$1,850. HP 7595A DraftMaster I (sizes A-E) \$2,000. HP 7475A \$220. HP 7550A \$350. Excellent condition, warranty. Pepper Systems, 214-353-0257 (FAX 214-902-9511).

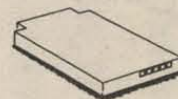I WANT it and I want it now. I want all of your SIMM memory. IBM, Mac, new, used, even defective. I want it all. Highest \$ paid. Now selling memory. We can beat any printed price in Nuts & Volts. Call 1-800-4-MEMORY now! Voice/FAX.



ZENITH LAPTOP BATTERIES. Mastersport ZA-4-1 "NEW" \$50. Supersport 2.5 amp-hour for ZWL 184 "NEW" \$25. Surplus Trading Corp., Benton Harbor, MI. 616-849-1800.



Eliminate single-chip burner drudgery, and increase Zilog Z8 chip burning productivity without universal programmer expense.

NTZ-818 combines economy with productivity for Zilog Z8 microcontroller programming

Program up to 450 parts per hour with the NTZ-818 at one-fifth of the cost of expensive, universal gang programmers. Now, you can dramatically increase in-house programming compared to Zilog Z8 family single-chip programmers. Conforms to Zilog's recommended programming algorithms.

Unique, user-friendly features save time.

- Burns 300 to 450 parts per hour, up to eight chips at once
- Supports all Zilog 18-pin microcontroller devices
- Flash upgradable firmware
- Universal input internal power supply
- Digital display
- Operates over an RS232 serial port with host computer
- User-friendly keyboard for stand-alone operation
- "One-touch" start switch to initiate and repeat blank/program/verify cycles
- Beeper to annunciate errors and relay task progress
- All allowable bit programming is supported where applicable.



Windows is a registered trademark of Microsoft Corporation.

For engineering or medium production use with more economy, the NTZ-418.

Program up to 100 parts per hour with the 4-chip NTZ-418 using your PC. The NTZ-418 is similar to the NTZ-818 in programming all Zilog 18-pin devices, and operates over an RS232 serial port with a host computer. It utilizes a standard 18 VAC, 500 mA external wall mount power supply.

Easy-to-Use Software

Both units include Windows® 95 and Windows 3.1 Graphical User Interface. Each supports simple ASCII download commands for operation with non-Windows operating systems via .bat file or DOS terminal program.

NovaTech Industries, Inc.

NovaTech Industries, Inc. 810 Tech Drive Telford, PA 18969
Tel: (215) 799-0123 (800) 459-9136 Fax: (215) 799-0125
e-mail: novatech@djs.com Web: <http://www.novatech-industries.com>

THE DC VOLT

by Ron Tipton

How many times each day do you pick up a probe to measure a DC voltage? You probably don't keep count and neither do I, but DC voltage is one of the most common measurements we make.

The meter reads, say 4.65 volts, and we usually accept it without question. But just what is a volt and how is it maintained? That's the subject of this article and it's a fascinating look at the search for increasingly more accurate methods of building a "standard volt." This progression is summarized in the Comparison Table. There is a lot of math connected with this subject and I'm going to mostly leave it out as it's not necessary to your practical understanding.

In 1881, it was agreed internationally at a Paris (France) meeting to define electrical units in terms of the basic mechanical units of length, mass, and time. The intention was to provide a consistent base for measurements in all branches of science and engineering but, unfortunately, it has proven to be a most difficult task — more on this as we go along.

In the United States, this effort is the responsibility of the National Institute of Science and Technology (NIST) and they do an outstanding job. (Prior to August 1988, NIST was the National Bureau of Standards (NBS) so many reports, monographs, and books bear the NBS name and publication number.)

THE CURRENT BALANCE

The current balance, shown in Figure 1, is a basic apparatus for defining the ampere. The current is adjusted so the position of the movable coil is balanced between the attraction of the fixed coil and the pull of gravity. The mutual inductance between the coils, the coil dimensions, the movable coil's mass, and the

acceleration of gravity relate the current to length, mass, and time. The current is also made to flow through a standard resistor, and so, by Ohm's law, we have a "standard volt." (We will ignore how we got the standard resistor, but it too is defined by the basic mechanical units.)

Although simple in concept, the mechanical and electrical properties of the coils are very difficult to measure to the required precision. Winding strain and impurities in the wire introduce still more uncertainty. So, as the "maintained" volt has improved (see

Table), NIST scientists have been hard pressed to keep up with the mass, length, and time verification. But let's not get ahead of our story.

A current balance can define the standard volt, but it's not a very convenient way to calibrate voltmeters. Some sort of battery with a fixed electromotive force (EMF) and excellent long term stability would be a lot easier to use.

STANDARD CELLS

Between 1879 and 1906, the volt

was maintained in the US by a group of seven Clark cells, a battery using a zinc sulfate electrolyte. During these 27 years, the cell was improved by several workers, but it had limitations — such as electrode gassing — that couldn't be overcome. Although not perfect by any means, Weston cells didn't have the gassing problem and also had an EMF temperature coefficient that was 30 times better than the Clark cell. So by 1908, the Clark cells had been phased out in favor of the more stable Weston cells. In 1965, the National Reference Group of Standard Cells consisted of 44 saturated Weston cells in a temperature controlled oil bath. The temperature was maintained at 28° C within 0.01° C.

A cell is removed from the reference group if its EMF drifts by more than 10 microvolts from its previously steady value. When a cell is removed, the average (or mean) EMF for the group is recalculated starting from the date the removed cell was added to the group. Obviously, this calls for very good recordkeeping. But since the cell group is kept fairly large, the average EMF change caused by a cell removal is usually less than one microvolt.



By 1974, cell groups were kept in enclosures with a temperature instability of less than 20 microdegrees over several days. As often happens, the cell's temperature coefficient became less important as temperature control technology improved. Ambient temperature changes now have a negligible effect on the cell EMF.

The sketch in Figure 2 shows a Weston standard cell, the only kind currently in use. "Saturated" refers to the cadmium sulfate solution; no additional cadmium sulfate will dissolve. Unsaturated cells are also used as secondary standards — more on this later.

NIST goes to incredible lengths to insure the purity of each cell "ingredient" and the result is excellent stability with a long useful life. But saturated cells are finicky. They don't like to be moved and if they are, they need a "rest period" at the new location for the EMF to settle down.

Also, they are not current sources. A discharge current of even one microampere for a few seconds changes the EMF for several minutes after the load is disconnected. A current as large as a milliampere can completely destroy the cell's usefulness.

So how can we use

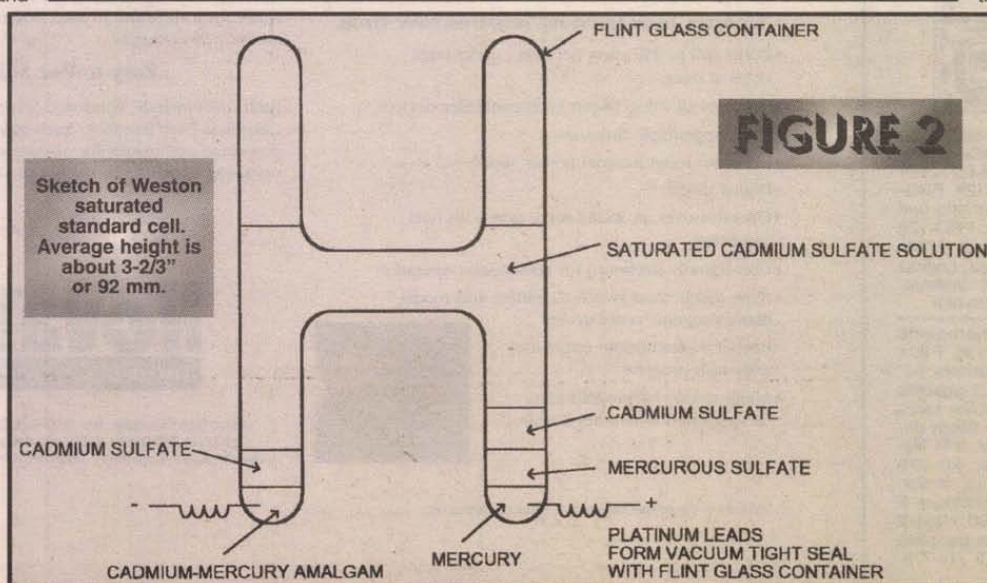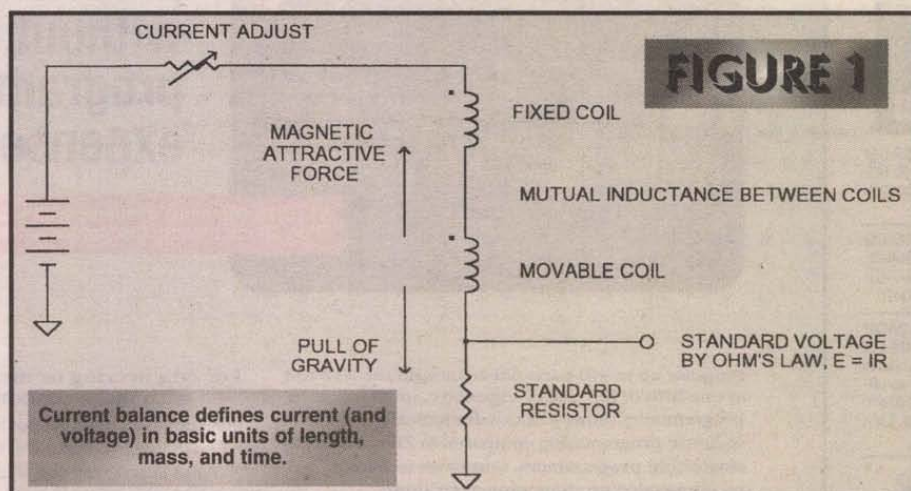

them to make practical voltage measurements?

THE POTENTIOMETER

The answer is an instrument which draws only a very brief, minute current from the cell: a laboratory potentiometer. I have diagrammed a simplified potentiometer in Figure 3 to show you how they work. The working battery is typically a two- to four-volt storage battery. The voltage isn't critical as its only job is to supply a stable working current. R3, a compensation adjustment, is first set to the EMF printed on the standard cell's label. With S1 in the "std. cell" position (as drawn in Figure 3), switch S2 is tapped and R1 is adjusted for no deflection on the galvanometer. In most potentiometers, this sets full scale to 1.6 volts (voltage drop between points one and three) because the voltage drop from point one to point two exactly balances the standard cell's EMF.


To measure an unknown voltage, S1 is placed in the "down" position

and switch S3 is tapped as the main dial (R2) is adjusted. R2 is a range switch in series with a long slidewire mechanically arranged in a spiral. Because of this length, any voltage between zero and 1.6 volts can be measured with a resolution of 10 microvolts. Higher voltages are handled with an accurate voltage divider called a "volt box."

Manufactured by companies such as Leeds and Northrup (L&N), Julie Research Laboratories, and Weston Instruments, and traditionally housed in a well crafted wooden box with a highly polished bakelite control panel, a potentiometer is a precision instrument and must be treated accordingly. In this day of many-digit digital voltmeters (DVMs), manual-balance potentiometers can appear on used-equipment dealer's shelves at bargain prices. A photo (Figure 4) of the author's L&N model 7552 is typical of the breed.

TRANSFER STANDARDS

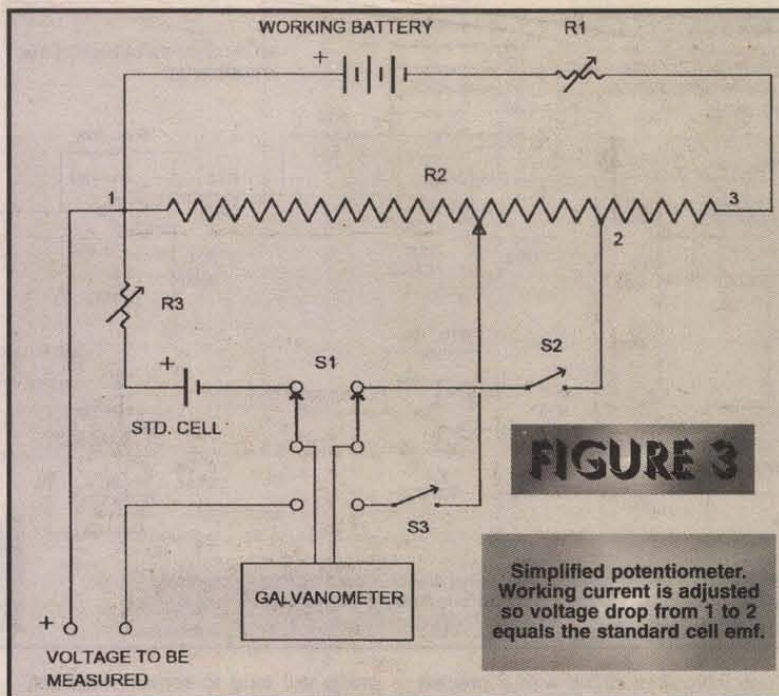Saturated reference cell groups in their constant temperature enclosures are difficult and expensive to move between laboratories for intercomparison. It was done for many years simply because there was no alternative. But starting about




Leeds and Northrup Model 7552 is a typical potentiometer. Input and output binding posts are on rear panel (not visible). Large "drum" with crank handle is the spiral slidewire.

1970, solid-state voltage references were introduced for this use, that is, as transfer standards. They are much more rugged than cells and are easier and less expensive to ship.

The solid-state units use several zener diode voltage reference modules in a constant temperature enclosure. Batteries supply power to the reference modules and temperature control during transportation.

The zener diode modules often supply 10 volts (which is preferred for calibrating digital voltmeters), as well as 1.018 volts which is compatible with existing potentiometers.

As an added advantage,

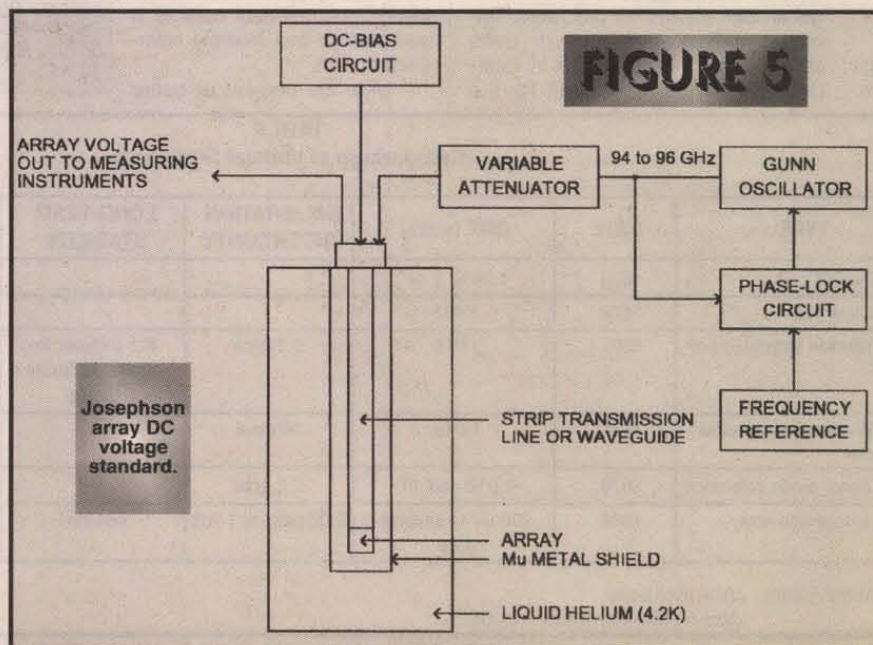

some zener units can supply some output current with no loss of accuracy or need for a recovery period.

Unsaturated Weston cells are not quite as accurate, stable, or long-lived as saturated cells. But they are less expensive and can be economically shipped by common carrier. They find use as secondary standards at schools and calibration laboratories.

Standard cells have been in use for over a hundred years, but the search goes on for an even more accurate standard. In 1987, work began at NIST to maintain the US (legal) volt with a Josephson array.

THE JOSEPHSON ARRAY

In the 1960s, British physicist Brian Josephson predicted that a radio-frequency (RF) signal directed through a "sandwich" consisting of a superconductor, an insulator, and a superconductor, would produce a specific, repeatable voltage. This sandwich is now known as a Josephson junction. This is a quantum device with a junction voltage given by:

$$V_n = \frac{n h f}{2e}$$

f is the frequency of the RF excitation signal, e is the charge of an electron, and h is Planck's constant. Both e and h are fundamental constants, but this isn't sufficient to tie this volt definition to length, mass, and time.

Primarily because of the physical size of practical Josephson junctions, the RF frequency is 94 to 96 GHz. Substituting into the above equation (for n = 1) gives a junction voltage of about 200 microvolts. The integer "n" varies with the DC bias current and RF excitation power. Still, many junctions in series, that is a Josephson array, are needed for a practical standard. NIST has built various size arrays to over 2,000 junctions with larger ones planned.

Individual junctions are quite small and are getting smaller as research continues on superconducting materials. NIST researchers hope to eventually produce a chip with one million junctions in one square centimeter.

There are several reasons for wanting smaller arrays. The cooling system can be smaller, there will be a lower temperature gradient across the array, and equally important, a small size makes it easier to equalize the microwave power into each junction. Equal power into each junction is needed to keep n (in the above equation) the same for the whole array.

A Josephson array standard is diagrammed in Figure 5 and you can see that it's not an instrument you could easily build at home!

In April 1996, NIST announced a transportable 10-volt Josephson calibration system. Its weight and size are considerably smaller than previous models, yet it holds enough liquid helium to operate for six to eight weeks. The final version of this system is designed to be cooled with a refrigeration unit.

Although it is constructed as a physical instrument, the Josephson effect is fundamentally different from a standard cell or a zener reference. Some Josephson arrays can "go bad" for, as yet, unexplainable reasons, but new arrays can be built. For these reasons, the long term EMF stability is "perfect" (at our current level of understanding the process). Why then are we concerned with verifying this volt definition in terms of the basic mechanical units?

The problem lies in our imperfect knowledge of e and h , the electron charge, and Planck's constant. The volt defined by the Josephson effect has excellent long-term stability, but is this volt the right "size?" An independent measurement will either confirm the size of the volt or let us adjust e or h to bring the measurements into agreement.

A very sophisticated superconducting current balance has been built to determine the "absolute ampere." Also, work is continuing on a liquid electrometer for a direct absolute volt determination. In this apparatus, the vertical displacement caused by electrostatic attraction between a fixed plate and the surface of a mercury pool is measured by a laser interferometer.

But the difficulties in making these verification measurements are illustrated by several experiments with the above instruments, in which the residual uncertainties are about the same size as the Josephson volt uncertainty. That is, the results are inconclusive.

And so this interesting and challenging work goes on!

A VOLTAGE REFERENCE YOU CAN BUILD

If you want your own secondary voltage reference, here's a suggestion for one that's pretty good and easy to build.

Several companies are now producing zener diode references with a laser-trimmed buffer amplifier in an easy-to-

use integrated circuit with a precise output voltage. I have evaluated many of these devices, and the best ones I've found are manufactured by Thaler Corporation (see Resources). Their VRE305A has a five-volt output with an initial error of not more than 500 microvolts ($\pm 0.01\%$) and a maximum temperature coefficient of 0.6 ppm per degree C — in an eight-pin DIP.

The circuit in Figure 6 will give you outputs of 1.018 and 10 volts. The specified 10,000 ohm resistors can be matched to 0.01% (1 ohm) with a 4-1/2 digit (or better) digital multimeter. (The actual resistance isn't important, just the match.) The chopper-stabilized opamps will each contribute no more than five microvolts uncertainty to the output voltage.

If you build several of these circuits and put them in a temperature-controlled box, you'll get improved long-term stability. You will also be able to intercompare their EMFs to get an idea about their drift rates. The output drift of the different units should be uncorrelated (that is, independent) so the mean EMF for the

group will tend to remain constant. Adding a sealed lead-acid battery pack and a charging power supply would give you power line independence and portability. It just depends on what you need or want.

Here are a few construction suggestions.

Use a PC board and then support the board by its wire leads to minimize strain-produced stray EMFs. If this is a mechanical problem, design the enclosure so the board slides into sidewall slots or use some support that puts no tension or compression on the board.

Carefully solder the ICs to the board; don't use sockets. Don't leave out the +15 volt regulator (78L15). This preregulation virtually eliminates supply voltage variation in the VRE305 output and helps insure uncorrelated outputs if you plan to use multiple reference boards.

Use one percent or better

better off without the trim. This is a basic "building-block" circuit and I've had very good results with it. **NV**

RESOURCES

A good source of information on standard cells is NBS Monograph 84, *Standard Cells: Their Construction, Maintenance, and Characteristics*. A photocopy can be ordered from **National Technical Information Service**, 5285 Port Royal Road, Springfield, VA 22161 as publication number COM7210513/LL.

Many NIST papers on DC voltage standards and calibration have been published in the *IEEE Transactions on Instrumentation and Measurements*. You should be able to find a complete set of back issues at any large library, especially college and university libraries.

To keep up with what is going on at NIST, in general, you can get a free E-Mail subscription to the biweekly *NIST Update* newsletter by sending a "subscribe" message to baum@micf.nist.gov

The VRE305A voltage reference is available from the **Thaler Corporation**, 2015 N. Forbes Blvd., Tucson, AZ 85745. (520) 882-4000.

The TelCom TC7652 chopper-stabilized opamp can be found at **Digi-Key Corporation**, 701 Brooks Ave. South, Thief River Falls, MN 56701, (800) 344-4539, as their part number 10111.

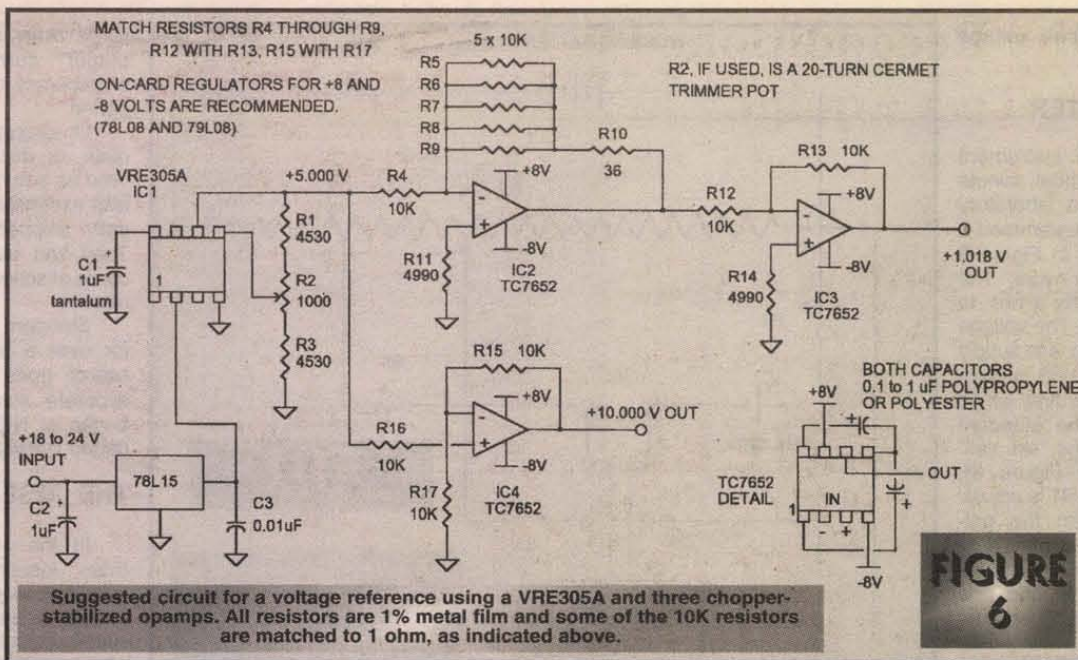


TABLE
Comparison of Voltage Standards

TYPE	DATE	EMF (volts)	CALIBRATION UNCERTAINTY	LONG-TERM STABILITY	COMMENTS
Daniell cell	1836	1.04 to 1.14			Poor long-term stability
Clark cell	1872	1.433			Better stability than Daniell cell
Weston saturated cell	1892	1.018	0.1 ppm	0.1 uV/year for National Reference Group	Former US legal volt
Weston unsaturated cell	1892	1.019	50 ppm		Secondary working reference
Zener diode reference	1970	1.018 and 10	0.2 ppm		More rugged than standard cells
Josephson array	1987	200 uV to several volts	0.02 ppm at 1 volt	see text	New US legal volt

Abbreviations: uV = microvolts
ppm = parts per million = 0.0001%

Top Quality Reconditioned Electronic Test Equipment

Hewlett-Packard • Tektronix • Fluke • Wiltron

BOUGHT & SOLD Test Equipment Wanted

Looking for Test Equipment Manuals?

Contact: Manuals Plus (801)882-7188 • Fax (801)882-7195

Corporate Offices
P.O. Box 1762
San Mateo, CA 94401

Seattle, WA 206-251-6653
285 S.W. 41st St.
Renton, WA 98055

415-579-1711 • Fax 415-579-5777
http://www.bellelect.com



**BELL
Electronics**

Write in 42 on Reader Service Card.

COMPUTER SOFTWARE

SHAREWARE PROGRAMS for IBM and compatible PCs. Write for free catalog-on-a-disk of the latest and best shareware programs. Please state diskette size. MicroData Computer Services, 6510 Parkland Ave., Brook Park, OH 44142. ASP member.

SEMICONDUCTOR CROSS-REFERENCE library on disk for IBM PC. Over 245,000 devices (transistors, diodes, ICs, SCRs, etc.). Specification, lead, and case configuration drawings for most. \$49 plus \$6 S&H. Checks, money orders, major credit cards accepted. Custom Software Creators, PO Box 1092, St. Bethlehem, TN 37155. 615-647-6120.

THE RELIABLE bulletin board service, software for all needs. Call 718 area code USA: 987-1932, 987-2913, 987-1617, 987-1660.

SHAREWARE CATALOG. Over 3,000 programs, free game on every catalog disk. Great prices, bonuses, free disks. Data Mate, Box 2811, Ronkonkoma, NY 11779.

FREE DISK CATALOG and discount coupon! Inexpensive, quality, IBM shareware and CD-ROMs. <ASP> vendor: **MOM 'N' POP'S SOFTWARE**, PO Box 15003-N, Springhill, FL 34609-0111. 352-688-9108.

THE MOST EXTRAORDINARY hacking catalog in the world! www.spectre-press.com

XRF SPECTRACE. Model 4020 wanted software/schematic. PO Box 999, Dewey, AZ 86327. 520-632-8774, E-Mail Tomollie@bsl.net.com

ENGINEERING SHAREWARE. Printed circuit design, logic simulation, pspsice, Autocad shareware. Over 700 engineering programs. Free catalog. CD-ROM available. Sector Systems Company, 416 Ocean Avenue, Marblehead, MA 01945. 617-639-2625.

FREE HACKING/phreaking/trubbleware diskette catalogue. Incredible subject matter. No commercial programming and NO SHAREWARE here! Peregrine Dynamics, 720 Portage Trail, Cuyahoga Falls, OH 44221.

18,000 + TECHNICAL REPAIRS for TVs, VCRs, PROJECTION TVs, CAMCORDERS, AUDIO on disk. Installs on your hard drive. Easy look-up by model/chassis number. **FREE DEMO. HIGHER INTELLIGENCE SOFTWARE**, 60 FARMINGTON LANE, MELVILLE, NY 11747. 1-800-215-5081/516-643-7740.

LINUX! LINUX! LINUX! If you aren't purchasing your Linux products from us, you are paying too much! We offer the major distributions (Yggdrasil, Slackware, Red Hat, etc) at **great prices!** We also carry a full range of books. Contact us at www.cheapbytes.com and use our secured web server. E-Mail: sales@cheapbytes.com Fax: 209-367-8518. Cheap Bytes, PO Box 2714, Lodi, CA 95241.

DO-IT-YOURSELF VR

Create Your Own Virtual Worlds
and Share Them with 10 Million People!

Six Publication Set!

Desktop VR contains a complete primer on using VR on your PC, plus: • Where to get low cost HMDs (head mounted displays) & other equip • The famous Mattel Powerglove hack (converting a \$69 Powerglove for use with VR) • Powerglove sources • Listings of virtual world building software • Comprehensive listings of HMD compatibility with popular games & software • Plus much more! • 36 pp.

VRML Primer explains VRML (Internet's "VR Modeling Language"), plus: • Building virtual worlds on the Internet • Virtual world authoring software & where to get it • Great VR worlds to visit on the Internet • Putting your virtual world on the Internet • More! • 32 pp.

Special Report: Virtual Reality an Exploding Technology Exclusive report on the explosion of VR in medical, amusement, consumer & other arenas • News blurbs on market entry by heavyweights & Fortune 500's • The VR marketplace • 28 pp.

VR InfoMania Time saving valuable resources including Listings of Internet websites devoted to VR • Listings of VR books • Listings of VR magazine articles & research papers • Listings of Internet FTP download sites & VR-related newsgroups • Article listings from back issues of VR magazines • Where to go to experience real VR • Reviews of popular VR books • Glossary of VR terms • Great VR applications • The future of virtual sex • Plus Much More! • 88 pp.

FREE DOUBLE BONUS!

FREE! VR Resource Directory is your guide to over 600 companies involved with VR products, software, R&D & consulting, plus professional trade organizations, clubs, more! 80 pp. Yours absolutely **FREE!**

FREE! VR Cartoons featuring dozens of funny cartoons about VR! Yours absolutely **FREE!** Limited printing, don't miss out! Order today!

● Learn How to Build Your Own Virtual Reality "Virtual Worlds" Quickly and Easily!

● Explore your Virtual Worlds on Your PC or put them on the Internet for Others to Explore!

● Explore your Worlds with your PC monitor and keyboard, or with Greater Immersion using Low-cost Homebrew Virtual Reality Equipment!

Convert this \$69 Mattel Powerglove into a VR Glove! Save \$Thousands! We show you how, and where you can buy Powergloves!

VR Goggles with head tracking cost over \$4,000 only a few years ago. Now they're under \$500! And 3-D VR Shutter Glasses are under \$100! Now Immersive VR is affordable!

We tell you where to get Virtual World Authoring Software, including **FREE** shareware! Even low-cost authoring packages allow you to wrap photographic textures around objects and walls. Render your worlds cartoon-like or photorealistic!



Our Customers Are Raving! "A Smorgasborg of info on VR!" -Sid Mirzad

"I love it! At under \$5 per book, don't miss out on this Incredible Value!" -Pam Eifert

90-Day
100% Satisfaction
Money-Back Guarantee!



24 HOUR TOLL FREE ORDER LINE

1-800-951-7100

FAX ORDERS 619-485-8968

You Get All 6 Publications!

ONLY \$49! Plus \$3 S&H

OVER 115 OFF! **ONLY \$29!**

Includes All 6 Publications!

2-3 Day Delivery 17% FedEx Overnight Air 114%

California residents add sales tax

UNDER \$5 PER PUBLICATION!

Send Check or Money Order to: Virtual Reality Publishing
16486 Bernardo Center Drive, Suite 378, San Diego CA 92128

*Same day shipping on FedEx orders received before 4 pm EST. Personal check orders held 2 weeks for check to clear. No COD orders. International orders must be paid in US funds. Call for International S&H charges. We participate in the BBB Care Program through the Better Business Bureau of San Diego.

ORDER TODAY... HAVE IT TOMORROW!!

Write in 62 on Reader Service Card.

BATTERIES

REPLACEMENT
BATTERIES
ALL NEW • MADE IN U.S.A.

KENWOOD		
PB1	12v @ 1100 mAh	\$50.00
KNB-3	7.2v @ 1200 mAh	30.00
KNB-4	7.2v @ 2200 mAh	69.00
PB6	7.2v @ 760 mAh	35.00
PB7	7.2v @ 1500 mAh	49.00
PB8	12v @ 850 mAh	49.00
PB-13	7.2v @ 750 mAh	37.00
PB-14	12v @ 800 mAh	49.00
PB-18	7.2v @ 1500 mAh	47.00

ICOM		
7S	13.2v @ 1400 mAh	\$53.00
8S	9.6v @ 1400 mAh	51.00
BP7	13.2v @ 600 mAh	53.00
BP8	8.4v @ 1400 mAh	50.00

SA/SAT		
BP82, BP83A		
BP84	7.2v @ 1200 mAh 3"	\$39.00
BP85B	12v @ 600 mAh 3"	69.00

YAESU		
FNB-2	10.8v 600 mAh	\$19.00
FNB-4	12v 750 mAh	39.00
FNB-4A	12v 1000 mAh	55.00
FNB-17	7.2v 600 mAh	30.00
FNB-10S	7.2v 1200 mah	39.00
FNB-12S	12v 600 mAh	40.00
FNB-26	7.2v 600 mAh	35.00
FNB-26S	7.2v 1200 mAh	44.00
FNB-27S	12v 800 mAh	49.00

ALINCO		
EPB-10N	7.2v @ 700 mAh	\$36.00
EPB-12N	12v @ 700 mAh	47.00
DJ-F1T		
EPB-16N	7.2v @ 750 mAh	\$37.00
EPB-16N	12v @ 600 mAh	47.00
DJ-180, DJ580		
EPB-20N	7.2v @ 800 mAh	\$34.00
EPB-20NX	7.2v @ 1600 mAh	44.00
EPB-22N	12v @ 800 mAh	49.00

CAMCORDER		
Panasonic PB 80/88		
ORIG PAN.....		\$39.00
Sony NP77H	2400 mAh	39.00
Sony NP55	1200 mAh	29.00
Sony NP22	500 mAh	29.00
Canon 8mm	2000 mAh	36.00
Panasonic Palm	2400 mAh	39.00
JVC GR Type C	1500 mAh	36.00
Sharp BT 21/22	2000 mah	45.00
RCA/Hitachi 8mm	2400 mAh	39.00

ALL BRANDS AVAILABLE

SALE!
ALL 7.2 VOLT
@ 1500 mAh*
**BATTERY
PACKS
\$39.00**

*EXCEPT FNB-35(S)(S)

MasterChargers®

MasterCharger I DELTA V,
RAPID CHARGER

ALL VOLTAGE 4.8v - 13.2v 1/2-2 HOURS

MasterCharger IIa
TAPER CHARGER

ALL VOLTAGE 4.8v - 13.2v 0 HOURS

DUAL CHARGERS

- MasterCharger I+II
- MasterCharger IIa+IIa*
- MasterCharger IIa+IIa*

*AUTOMATICALLY CHARGES TWO BATTERIES AT THE SAME TIME

- All MasterChargers (Single and Dual) Feature:
- Interchangeable Cups
- Fully Automatic Operation
- Built in Overcharging Protection
- User Friendly
- More Than 50 Cups Available
- Optional DC Charger

NEW!

KENWOOD TH22AT/79A

PB32 6v @ 600 mAh

PB33 6v @ 1200 mAh

PB34 9.6v @ 600 mAh

YAESU FT-11/51A

FNB-31 4.8v @ 600 mAh

FNB-33(S) 4.8v @ 1500 mAh

FNB-35SS 7.2v @ 1500 mAh

FNB-38 9.6v @ 600 mAh

ICOM-W21AT/2GX

BP-157 7.2v @ 900 mAh

BP-157(S) 7.2v @ 1500 mAh

BP-132 12v @ 850 mAh

*available with and without microphone**

MOTOROLA

GP-300 7.5v @ 1200 mAh



BATTERY-TECH, INC. 800 SOUTH BROADWAY, HICKSVILLE, NY 11801
800-442-4275 • FAX 516-496-9523

SEND FOR FREE CATALOG • DEALER INQUIRIES WELCOME IN NEW YORK STATE CALL: 516-496-9520

Write in 170 on Reader Service Card.

Metric
Equipment Sales, Inc.

800-432-3424

Fax: 415-341-8874
E-mail: metricsale@aol.com

RENT • BUY • SELL
Yes, we will buy your surplus equipment!

Scopes, Meters, Analyzers, Power Supplies, Signal
Generators, Counters, Recorders and more

Hewlett-Packard, Tektronix, Fluke, Dranetz, TTC, Anritsu,
Wavetek, Keithley, and more

Test & Measurement Instruments

Over 7000 Models • 6-Month Warranty
Save 30-90% • 5-Day Free Trial

Write in 190 on Reader Service Card.

CABLE TV
Buy Direct from
the Wholesaler

SAVE
100's of \$\$\$

Dealers Welcome

**We carry all
makes and models
IN STOCK**

Call for quantity discounts

**We'll beat
any price on
the market**


30 days money back full
warranty/guarantee

Visual Concept
1-888-838-4444

BLACK BAG TRIVIA QUIZ on disk. Includes
unique shareware and restricted book catalog
\$1. Mentor Publications, Box 1549-N, Asbury
Park, NJ 07712.

MASS E-MAIL your web site (or product) to
millions! Powerful free software. E-Mail:
76333.3601@compuserve.com

The Pocket Programmer

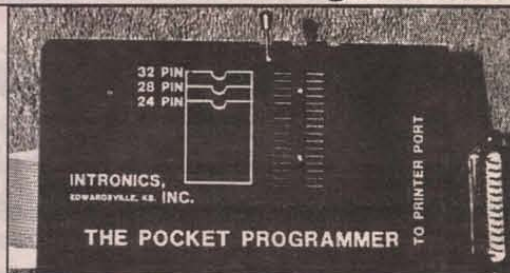

The portable programmer that uses the printer port of
your PC instead of an internal card. Easy to use
software that programs E(E)prom, Flash & Dallas
Ram. 27(C)/28(C)/28F/ 29F/29CXXXX & 25XX
series from 16K to 8 Megabit with a 32 pin socket.
Adapters available for Pic, MCU's 874X, 875X, 40-
Pin X 16 & Serial Eprom's, PLCC, 5-Gang and Eprom
Emulator to 32K X 8. **Only \$129.95**

Same Name, Address & Phone Number for 13 Years.....
Now isn't that Amazing ?

Intronics, Inc.

Box 13723 / 612 Newton St.

Edwardsville, KS 66113

Tel. (913) 422-2094

Fax (913) 441-1623

Add \$4.75 COD

Add \$4.00 Shipping

Visa / Master Charge

Write in 61 on Reader Service Card.



TEST EQUIPMENT SALES



HP 8012B.....\$595	FLUKE 752A.....\$2695	TEK 465.....\$475
KEI 224.....\$995	TEK 7104.....\$1895	FLUKE 5200A.....\$1895
DATRON 1065.....\$595	HP 8444A/059.....\$950	KEI 619.....\$995
HP 6205B.....\$225	HP 6940B.....\$195	HP 6237B.....\$495
TEK FG504.....\$525	HP 3312A.....\$795	TEK 11302A.....\$2495
DIO 2900.....\$1995	TEK DC5010.....\$895	TEK 2445.....\$1750
TEK DM5010.....\$550	TEK FG5010.....\$1095	AR 5014.....\$295
TEK SG503.....\$695	TEK 2215A.....\$650	WAV 801.....\$795
HP 8082A.....\$995	HP 8754A.....\$2495	TEK 2465.....\$2750

M/C & VISA

66 CHASE ROAD
LONDONDERRY, N.H. 03053
PHONE (603) 434-2544
FAX (603) 425-2945

WE BUY
SURPLUS

Write in 77 on Reader Service Card.

IBM SHAREWARE, free catalog, \$1 disk,
35¢ specials, huge selection, 100% virus
free. PMA, Box 2424, Scottsdale, AZ 85252.
602-496-6547. Specify disk size.

I WANT it and I want it now. I want all of your
SIMM memory. IBM, Mac, new, used, even
defective. I want it all. Highest \$ paid. Now
selling memory. We can beat any printed
price in Nuts & Volts. Call 1-800-4-MEMORY
now! Voice/FAX.

COMPUTER EQUIPMENT WANTED

WANTED: FOR historical museum, pre-1980
microcomputers, magazines, and sales litera-
ture. Floyd, VA 24091-0341 (540-231-
6478/540-763-2321).

EAGLE COMPUTERS Model II, IIe complete
or motherboard with EPROM for external
hard drive. 804-648-3041.

WANTED TO buy: Bodylog/Bodylink biofeed-
back add-on for Commodore C-64. Also other
biofeedback equipment. PC-based or not.
Call 718-390-7436, Bob.

WANTED: TERMINALS + PRINTERS: DEC,
Wyse, IBM, ADDS, Okidata, Data South,
Epson, C.I.TOH, etc. Call for quote on any
surplus computer equipment. Call Jeremy,
603-673-8077.

I WANT it and I want it now. I want all of your
SIMM memory. IBM, Mac, new, used, even
defective. I want it all. Highest \$ paid. Now
selling memory. We can beat any printed
price in Nuts & Volts. Call 1-800-4-MEMORY
now! Voice/FAX.

**WANTED: PRINTRONIX PRINTERS AND
PARTS.** Immediate cash paid for Printronix,
Genicom, and other computer printers and
related peripherals. Small or large invento-
ries, new/used/damaged. Fax us 860-349-
0333.

DEC EQUIPMENT WANTED!!! We are buy-
ing DEC systems, boards, terminals, drives
and peripherals. Also Scientific Micro
Systems (SMS), DSD, Datability, Dialog, other
DEC compatibles, and Computer Output
Microfilm (COM) units. Please call for a quote
or fax us your equipment list. We buy, sell,
and trade. **KEYWAYS, INC.**, 513-847-2300
OR fax 513-847-2350.

**ACP's 77th GIANT
COMPUTER
SWAP★MEET**

Orange
County's
Original!

Be a
Seller!
...for
space
call
Mary...

Sunday, 8am-2pm

Jan 26th

FREE Admission & Parking
Shop 100's of Sellers

in ACP's Giant Parking Lot

Advanced Computer Products, Inc.

**ACP
SUPER★STORE**
Since 1976

1310 E. Edinger
Santa Ana, CA
714-558-8813



RF POWER TRANSISTORS • TUBES • POWER MODULES

EIMAC • SVETLANA • AMPEREX

• MOTOROLA • MITSUBISHI

Best pricing on US & Russian

• TOSHIBA

Transmitting Tubes
Receiving Tubes

3-500Z 3CX400A7
3-500ZG 3CX400U7
4-400C 3CX800A7
572B 3CX1200A7
811A 3CX1200Z7
6146B 3CX1500A7
6146W 3CX3000A7
8072 4CX250B
8560AS 4CX400A
8873 3CX800A
8874 6LF6
8875 M2057

Etc!



Complete inventory for
servicing amateur
and commercial
communications
equipment.

MRF454 SAV6
MRF455 SAV7
2SC2290 SAV17
2SC2879 M5737

Etc!

Send for your
FREE
1996 Catalog

Same Day Shipping

Tel: (619) 744-0700

Fax: (619) 744-1943



Write in 137 on Reader Service Card.

NEED DRIVERS for MUSTEK page scanner model MFS-3000C. Will pay \$25 plus cost of shipping & fax. Please send 3.5" disk by Priority Mail to: Richard W. Horner, Box 1714-H104, Koror, Palau 96940 fax 011-680-488-1725.

WANTED: PRE1980 Microcomputers for museum collection. Microcomputer magazines and manuals also needed. 703-231-6478, 703-763-3311.

PRINTHEADS WANTED. We buy all quantities of dot matrix printheads for hundreds of printer model types. Working or dead units acceptable. Call Mike Anderson @ 1-800-969-0009.

RECOVER "SCRAP GOLD" from old computer junk. Free information packet. Call 24 hours: 603-645-4772.

TEST EQUIPMENT

HP 141T, 8555A, 8552B, \$2,000; HP 141T, 8554B, 8552B, \$1,800; HP 8553B, \$500; HP 8660A, \$250; HP 86290A, 2-18 GHz, sweep plug-in, \$1,800; HP P532A, wavemeter, \$150; Scientific Atlanta programmable microwave receiver, with digital phase gain meters, phase meters, \$2,500; Fluke 332B voltage calibrator, \$600; HP 3320B, \$400; HP 3330B, \$500; Rockland 5100 synthesizer, \$400; HP 334A, distortion ana., \$450; HP 332A, \$300; HP 331, \$250; Send for test equipment sales list. A-Comm Electronics, 7198 S. Quince Street, Englewood, CO 80112. 303-290-8012.

MICRODYNE 1100, 1200, 1400 series receivers all bands, FM and PM demods, SDU, IF filters, Aydin, Schlumberger, monitor systems bit syncs. 805-934-2058.

TEST EQUIPMENT Sale: Tektronix 7904, 7A24, 7A26, 7B85, 7B92A, \$900; HP 76XD dual directional couplers, \$150 ea.; HP 78XD directional detectors, \$150 ea.; HP H382A 0-50 dB attenuators, \$75 ea.; HP K422A Xtal detectors, \$150 ea.; Keithley 197 5.5 dig. DVM, \$200; HP 3455A, \$500; HP 3466A DVM with battery packs, \$300; Leeds and Northrup 8071 Mueller bridge, Keithley 169, \$100; HP 8683B sig. gen., \$2,500; Panasonic BT1300N video color monitor, \$250; Stoddard NM1727 EMI receiver, \$1,000; Stoddard NM3757, \$1,000; Clarostat 240C, \$100; Cornell Dubilier CDA decade cap., \$50; Fairchild TRF14 tunable rejection filter 14-110 MHz, \$250; E&G Electro Optics 460-A1 laser power meter with accessories, \$400; HP 200CD, \$125; HP 4260A RCL meter, \$250. A-Comm Electronics 303-290-8012.


SCOPES & PLUGS. Tektronix 7613 or R7613 as new 100MHz storage mainframe \$275; R7704 250MHz frame \$200; 7904 w/2 7A26, 7B53A & 7A13 \$750; SC-501 \$165; SC-504 80MHz scope as new \$375. 7A13 \$175; 7A16A \$50; 7A18 \$50; 7A16P \$100; 7A19 \$100; 7A24 \$150; 7A26 \$67; 7B50, \$65; 7B53A \$85; 7B80 \$100, 7B85 \$85; 7B87 \$200; 7B92A, \$150. 7CT1N curve tracer plug-in \$345; 7D01, DF1, DF2, call. 7D12 \$100, 7D15 \$250; 7D20 programmable digitizer \$390; 7M13 \$100; TEK 7612 \$150. DC-505A \$200; DC-509 counter timer \$375; PG-501 \$200; PG-502, 250MHz pulse generator \$300; PG-508 pulse generator \$400; PS-503A dual power supply \$150; SG-502 oscilloscope \$175; 7S12 sampler plug-in \$400; heads S-3 \$100; S-3A \$125, S-5 \$100, S-51 \$300, S-54 \$200 S-6 \$425, 7104A \$1,575. Psitech Plus 707-745-4804 request bi-monthly fax listings, Fax 707-747-5277.

LOWEST PRICES! Check out Metric's "Bargain Basement" at <http://www.metric-sales.com> Most items under \$125!



XC-2
DTMF To ASCII
Transceiver

<http://www.motron.com>

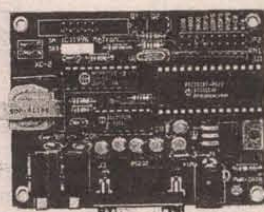

The New **Motron XC-2** is a versatile bi-directional DTMF to ASCII transceiver. DTMF digits are decoded from the audio line, converted to ASCII, and transmitted out through the serial port. ASCII data is received from the serial port, converted to DTMF digits and transmitted on the audio line. The **XC-2** uses the RS-232C serial communications protocol and includes a PTT output, which can be used to control a radio transmitter. The **XC-2** is user-configurable—select either 1200, 4800 or 9600 baud for the serial port and 5, 10, 15 or 20 cps DTMF transmission rate. Additional jumpers can be used to set DTMF "M" to generate an ASCII "CR", and to control an open-collector output with DTMF "*" (on) and "#" (off). Audio connection options allow combined audio signals, or separate audio input and output via standard 3.5mm jacks. A standard DE-9S is used for serial communications. The **XC-2** is a fully assembled and tested printed circuit board, requires +8 to +17 VDC @ 200ma, and is only 2-1/2" x 3-1/2". OEM and Quantity discounts are available.

XC-2 Bi-Directional DTMF to ASCII Transceiver PCB \$99.00 Plus Shipping

We accept American Express & Visa & MasterCard & Discover/Novus

Orders: (800) 338-9058

Info: (541) 687-2118

Fax: (541) 687-2492

ELECTRONIC TEST EQUIPMENT BOUGHT & SOLD

Alltech 360D11, Frequency Syn., 01-2GHz	\$1,000	HP 86290B, RF Plug-In, 2-18GHz w/Scales	\$1,400
Anritsu ME645A, Microwave Radio Test Set	\$1,000	HP 8640B, Signal Gen., 5-512MHz, Opt. 3	\$1,000
Arbitrator 1004A, Meter Calibrator, AC/DC Voltage/Current	\$1,200	HP 8654A, Signal Gen., 10-520MHz AM/FM	\$500
Argosystems AS210, Frequency Calibration System	\$3,500	HP 8656A, Signal Gen., 1-990MHz AM/FM, HP1B	\$2,000
Balco 911A, Frequency Response Analyzer (unused)	\$400	HP 8660A/100, Synth. Freq. Gen. Mainframe	\$650
Baseline 1827A, Scope Cal. with acc. heads	\$1,000	HP 8660C/100, Synth. Freq. Gen. Mainframe	\$1,200
Biontron 25A, Power Meter, w/Probe	\$800	HP 8660D/8663A/8663B, Freq. Syn., 2.6GHz, AM/FM, HP1B	\$3,000
Biontron 400, Power Meter, w/Detector, 100kHz-18GHz	\$800	HP 8660B/100, Synth. Freq. Gen. Mainframe	\$600
Biontron 425D, Microwave Meter, 2MHz-7GHz	\$300	HP 86601A, RF Plug-In, 110MHz	\$250
Biontron 518-AA, Q Standard	\$250	HP 86602B, RF Plug-In, 1300MHz	\$600
Biontron 82AD, Modulation Meter	\$850	HP 86603A, RF Plug-In, 1-2600MHz, Opt. 02	\$1,500
Biontron 92A, RF Millivoltmeter w/Probe	\$300	HP 86632B, Modulation Plug-In	\$400
Bruehl & Kjaer 1612, Bandpass Filter	\$250	HP 8683A, Signal Gen., 2.3-5.5GHz, Opt. 1, 2	\$1,500
Cushman CE248, Frequency Selective Voltmeter	\$800	HP 8750A, Storage Normalizer	\$250
Datron 1062, Digital Multimeter	\$650	HP 8821A, Medium Gain Bank Amp	\$150
DDC SR-400, Synco Resolver Simulator	\$400	HP 8901A, Modulation Analyzer	\$4,500
Dekoh COL300, Logic Analyzer w/Ext. Chassis & Pods	\$800	HP 8903A, Audio Analyzer	\$2,700
DR Thiedig MILLI-TO2, Chromometer	\$400	Keithley 201, Pile Amp. Source (unused)	\$300
1 Million-2 Teraohms	\$400	Keithley 614, Electrometer	\$700
Eaton 380K11, Synthesizer, 1-2000MHz	\$2,500	Keithley 616, Digital Electrometer	\$500
Opt. 01, 03, 183	\$2,500	Kapco ATE-100-1M, Power Supply, 0-100V, 0-1 amp (new)	\$200
EIP 371, Source Locking Microwave Counter, 18GHz	\$1,500	Leeds & North 1091, Capacitor Decade, .01uF-1uF	\$150
ESI 296, Auto LCR Meter	\$650	Marconi 2955, Radio Comm. Test Set, CXC0	\$4,500
Fluke 3330B, DC Voltage, Current Calibrator	\$400	Maury Micro LT105, Thermal Converter	\$100
Fluke 335A, DC Voltage Standard, 0-110VDC	\$600	Micro-Tel SG800, Sweep Signal Generator, 1-18GHz	\$1,000
Fluke 5200A, Programmable AC Voltage Standard HP1B	\$1,600	Narda 7000A/7027/7206, Microwave Multimeter, Opt. 01-18GHz	\$1,000
Fluke 540B, Thermal Transfer Standard	\$900	Narda 7927F, Attenuator, 2-12GHz, 0-20dB	\$100
Fluke 850A, Digital Multimeter 6.5 Digits, DC Only	\$250	North All 54010, Resolver Synchro Bridge	\$800
Fluke 8502A, Digital Multimeter, AC, DC, Ohms	\$300	Racal Dana 9052P, Signal AM, FM, 1-50MHz	\$1,000
Fluke 8505A, Digital Multimeter, AC, DC, Ohms	\$400	Phillips 3211, Scope, 15MHz 2Ch.	\$650
Fluke 8921A/03, True RMS Voltmeter	\$600	Phillips PM3267, Scope, 100MHz, Dual Trace	\$400
Fluke 9010A, Micro-System Troubleshooter Opt. 001	\$450	PMI 1018B, Peak Power Meter	\$350
Fluke A55, Thermal Converter	\$200	Polaroid 1105 E-L, Sig. Gen., 1020A Mod., 8-2.4GHz	\$300
General Microwave 478A, Peak Power Meter	\$1,000	Polaroid 1207, Signal Source 3.8-8.2GHz	\$200
General Radio 1422-CB, Standard Cap.	\$300	Polaroid 640, Spectrum Anyz., 18GHz, Dig. Storage	\$1,400
General Radio 1482Q, Standard Inductor, 2 Henry	\$100	Polaroid SPN8, Generator 20Hz 20KHz	\$450
General Radio 1538A, Stroboscopic, Strobe Scope	\$300	Racal Dana 1515, Delay Pulse Generator	\$500
General Radio 1538-PM, High Intensity Flash Capacitor	\$100	Racal Dana 1992, Universal Counter, High Stab. HP1B	\$800
General Radio 1650A, Impedance Bridge	\$300	Racal Dana 9052P, Signal AM, FM, 1-50MHz	\$1,000
Gilgistrans 6006-12, Synthesized Source	\$1,500	Racal Dana 9303, True RMS RF Level Meter	\$650
Gould 4500, Digital Storage Scope, 35MHz	\$450	Racal Dana 9515, Universal Counter, HP1B, Opt. 01	\$200
Guidline 9154C, Transvolt Standard Cell	\$400	Sencore TF30, Super Cricket Transistor Tester	\$200
Hameg HM 208, Digital Storage Scope, Unused	\$600	T.B.E. 208, C. L. Meter, 1F-10uF, 1H-10H	\$300
HP 105A, Quartz Frequency Divider	\$600	Tek 11302, Scope, 500MHz w/2 (11A71) Plug-ins	\$2,000
HP 1124A, 100MHz Active Dual Probe, Unused	\$100	Tek 1401/234, Spectrum Analyzer, 1-500MHz	\$800
HP 117A, VLF Comparator	\$250	Tek 178, Linear IC Test Fixture, For 577	\$300
HP 11971K, Waveguide Mixer, 18-26MHz, 8569B	\$800	Tek 2213A, Scope, 60MHz Dual Trace	\$450
HP 1415A, Time Domain Reflectometer Plug-In, 141T	\$300	Tek 2216, Scope, 60 MHz Dual Trace	\$450
HP 1454A, Digital Multimeter, 6.5 Digits	\$250	Tek 2245, Scope, 100MHz, 4 Ch. Cursors	\$1,400
HP 1707B, Scope, 75MHz Dual Trace	\$500	Tek 2430A, Scope, Digital Storage, 150MHz	\$3,500
HP 1725A, Scope, 275MHz, Dual Trace, DMM	\$450	Tek 284, Pulse Generator	\$650
HP 1741A, Scope, Storage, 100MHz	\$400	Tek 318, Logic Analyzer, with Pods	\$300
HP 1742A, Scope, 100MHz Dual Trace, DMM	\$400	Tek 336, Scope, 5MHz Digital Storage	\$500
HP 1744A, Scope, Storage, 100MHz Dual Trace	\$500	Tek 484, Scope/100MHz Dual Trace, Storage	\$500
HP 1815A/1816A, TRF/Sampler, DC-4GHz	\$400	Tek 465B, Scope, 100MHz, Dual Trace	\$500
HP 3300A, Function Gen. with 3302A Phase Lock	\$150	Tek 465M, Scope, 100MHz, Dual Trace, Delayed Sw.	\$400
HP 3320A, Frequency Synthesizer	\$350	Tek 466, Scope, 100MHz Dual Trace, Storage	\$600
HP 3320B, Frequency Synthesizer	\$250	Tek 466/DM44, Scope, 100MHz, Storage, DMM	\$650
HP 3325A, Synthesized Function Generator	\$1,800	Tek 475, Scope, 200MHz, Dual Trace	\$600
HP 334A, Distortion Analyzer (unused)	\$400	Tek 475A, Scope, 250MHz, Dual Trace	\$650
HP 3458A, Digital Multimeter, 6.5 Digits	\$250	Tek 475DM44, Scope, 200MHz, Dual Trace, DMM	\$650
HP 3575A, Phase Gen. w/Probe, Opt. 01, Dual Displays	\$600	Tek 520, XY Monitor	\$300
HP 3581C, Selective Level Meter	\$600	Tek 7104, Scope w/2 7A29, 7B10, 7B15	\$3,000
HP 394A, Attenuator, 1-2GHz, 200 Watts	\$125	Tek 7C71N, Curve Tracer Plug-In	\$600
HP 4270A, Automatic Capacitance Bridge	\$600	Tek 7D20, Programmable Digitizer PI	\$600
HP 432A/478A, Power Mtr., Cable, Mount, 10MHz-10GHz	\$300	Tek 7L13/7603, Spectrum Anyz., 1KHz-1.8GHz	\$2,000
HP 432B, Power Meter, Digital Display	\$250	Tek 7L18/7603, Spectrum Anyz., 1.5-18GHz	\$3,000
HP 435A, Power Meter, with Cable, Sensor	\$800	Tek 7S12/S6/S52/S53, TDR Sampler	\$3,000
HP 436A/022, Power Mtr., w/8481A HP1B	\$1,700	Tek AM501, Operational Amp Plug-In	\$150
HP 4800A, Vector Impedance Meter	\$600	Tek AM503, Current Probe Amp	\$400
HP 4815A, Vector Impedance Meter	\$1,000	Tek DAC5200, Digital Analysis System	\$900
HP 5004A, Signature Analyzer	\$1,000	Tek DC503, Universal Counter Timer TM500	\$150
HP 5282A, Universal Counter, 600MHz HP1B	\$950	Tek DC504, Counter Timer TM500	\$100
HP 5334A, 100MHz Universal Counter, HP1B	\$1,200	Tek DC505A, Frequency Counter, DC-225MHz	\$300
HP 5335A, Frequency Counter, 11 Digit, Opt. 010-040	\$1,000	Tek DC508A, Counter, 1.3GHz Opt. 01	\$500
HP 5340A, Frequency Counter, 18GHz	\$1,000	Tek DM502, Multimeter TM500 Modular System	\$100
HP 5340A, Frequency Counter, 18GHz, LED, HP1B	\$1,200	Tek FG502, Function Generator, 1-11MHz	\$300
HP 5341A, Counter, 10Hz-4.5GHz LEDs & HP1B	\$700	Tek MP001, XY Monitor Scope	\$200
HP 5342A, Frequency Counter, 10Hz-18GHz, Opt. 001	\$1,800	Tek PR520, Current Probe, Amp, Kit	\$250
HP 5342A, Frequency Counter, 10Hz-18GHz	\$300	Tek PR601, Current Probe, 6MHz (new)	\$250
Opt. 001, 002, 011	\$3,000	Tek PR604, FET Active Probe	\$100
HP 5345A, Universal Counter	\$450	Tek PR648, Differential Probe Kit	\$350
HP 54100A, Scope, 1GHz Digital, 100 GS/s	\$3,500	Tek PR649, FET Probe Kit, 500MHz, Unused	\$400
HP 54200A, Digital Storage Scope, Dual Trace, 200MG/s	\$1,000	Tek PR652, Data Acquisition Probe	\$50
HP 6177C, DC Current Source 0-50V, 0-500mA	\$300	Tek PR645, Pattern Generator Probe, New in Box	\$50
HP 6820A, Meter Calibrator	\$300	Tek PS503A, Dual Tracking Power Supply, TM500	\$200
HP 7015B, XY Recorder	\$200	Tek S3, Sampling Head	\$100
HP 7790, Directional Coupler, 1.7-12.4 GHz	\$200	Tek S5, Sampling Head	\$100
HP 8015A, Pulse Generator, 1Hz-50MHz, 30V	\$500	Tek SC51, Scope, 5MHz	\$250
HP 8018A, Serial Data Generator	\$300	Tek SC502, Scope, 15MHz, Dual Trace	\$250
HP 8165A, Programmable Signal Source, .0001-50MHz with sweep	\$1,800	Tek SC504, Scope, 80MHz, Dual Trace (unused)	\$250
HP 8550A/8552B, Sweep Gen., 2-18GHz HP1B	\$4,300	Tek SG502, Sig. Gen., 5Hz-50KHz TM500 Sys.	\$200
HP 8443A, Tracking Gen., 100K-110MHz LED Display	\$400	Tek SG503, Sig. Gen., 250KHz-250MHz	\$600
HP 8445B, Spectrum Anyz., Automatic Pre-Selector	\$400	Tek T202, Scope, LCD Handheld	\$500
HP 8484A, Power Sensor	\$400	Tek TG501, Time Mark Generator	\$400
HP 8552B, Spectrum Anyz., IF Section	\$400	Tek TM5006, Power Module Mainframe	\$400
HP 853A, Spectrum Anyz. Display Section	\$2,000	Tek TM503, Mainframe 3 Slot, TM500	\$100
HP 8553B, Spectrum Anyz., RF Plug-In, 1K-110MHz	\$200	Tek TR503, Tracking Gen., 1-1800MHz for 482, 4, 6	\$1,000
HP 8553B/8552B, Spect. Anyz. 141T System, 1K-110MHz	\$1,000	Wu-Da 5110, Semiconductor Tester, In/out Circuit	\$250
HP 8555A/8552B, Spect. Anyz., 141T System, .01-18GHz	\$1,600	Wavelek 1002, Sweep/Sig. Gen., 0-500MHz w/Markers	\$350
HP 8556A, Plug-In, Spectrum Analyzer, 20Hz-300KHz	\$300	Wavelek 1045/14139, Power Meter	\$800
HP 8557A/180TR, Spectrum Analyzer, .01-350MHz	\$1,000	Wavelek 144, HF Sweep Gen., 0.005Hz-10MHz	\$200
HP 8558B/180TR, Spectrum Analyzer, 1-150MHz	\$2,000	Wavelek 145, 20MHz Pulse/Function Generator	\$300
HP 8559A, Spectrum Analyzer, 10MHz-21GHz	\$3,000	Wavelek 154, Programmable Waveform Gen., .001Hz-10MHz	\$350
HP 8559A/853A, Spectrum Analyzer, Storage Mainframe	\$5,000	Wavelek 166, 50MHz Pulse/Function Gen.	\$500
HP 8569B, Spectrum Anyz. High Performance	\$6,000	Wavelek 2002A, Signal Gen., Sweeper, 1-2500MHz	\$1,000
HP 8620C, Sweeper Mainframe	\$400	Wavelek 452, Filter, Dual Hi/Low, 1Hz-10KHz	\$450
HP 8621B, RF Draw, with 86350A, 8-12.4GHz, 8620C	\$400	Wavelek 750, Phase Meter	\$300
HP 86222B, RF Plug-In, 0.1-2.4GHz, Opt. 02, 04	\$1,200	Wavelek 7530A, FFT Spectrum Analyzer 0-100KHz	\$1,000
HP 86214A, RF Plug-In, 3.2-5.5GHz	\$400	Wavelek 8501, Peak Power Meter, 30MHz-18.5GHz	\$2,000
HP 86250C, RF Plug-In, 8-12.4GHz	\$400	Wavelek 859, Programmable Waveform Gen.	\$1,000
HP 86260A, RF Plug-In, 12.4-18GHz	\$400	Wavelek 907, 7-11GHz Signal Generator	\$650
		Willson 560A, Network Analyzer, HP1B	\$1,500

PHelps INSTRUMENTS

2631 Hillside Ave., Norco, CA 91760 • 909-279-7347



Write in 25 on Reader Service Card.

Nuts & Volts Magazine/January 1997 25

by Karl Lunt

The Best in Robot Soccer

The goalie moved sharply to the left, staying between the ball and goal, while the right forward raced ahead, lining up a pass. A quick nudge sent the ball rolling across the field to the left forward, which redirected the ball into the now-open goal, well before the opposing goalie could react. This quick give-and-go play added yet another point, as the robots from the Newton Research Labs team powered their way to a 20-0 win in the finals of the first Micro-Robot World Cup Soccer Tournament.

The tournament — held November 9-12, 1996 — took place in Taejeon, Korea, and included 23 teams from all over the world. It was organized by Korea Advanced Institute of Science and Technology (KAIST), sponsored by the IEEE Robotics and Automation Society, and supported by LG Semicon Co., Ltd. Known by its acronym, MIROSOT, this event featured teams of three tiny robots in a single-elimination contest based on soccer.

The MIROSOT format plays very much like the regular game of soccer, but reduced in size and with added refinements designed to help its robot competitors. The pitch, or playing surface, is a smooth, dark-green wooden surface 90 cm wide and 130 cm long, covered with a grid of white lines 10 cm apart. The boundaries are marked with wooden vertical walls five cm high. The goals, set at opposite ends of the field's length, are 30 cm wide and 12 cm high, with a five cm wall behind each goal. An orange golf ball serves as a soccer ball.

Each team consists of two forwards and a goalie. Each robot must fit within a cube 7.5 cm (about three inches) on a side, excluding any antenna. If a robot uses a gripper or other appendage, it must still fit within the assigned size, even when fully extended. All robots must be fully self-powered, using self-contained motor systems. Only wireless communications between robot and host system are permitted.

All control signals must be generated solely by a host computer system. No human member of a robotics team may use joystick or keyboard input to control the motion of a robot. Should a team desire to use a vision system for scanning the playing area, the camera must be mounted directly over the pitch, no closer than two meters from the surface.

Additional rules cover topics such as fouls and penalties, goal-scoring, substitutions, time-outs, free kicks, and functions of the (human) referees. As of this writing (Thanksgiving, 1996), you could find all of the above information, and much more, from the MIROSOT web site at www.mirosot.org — Oddly enough, two weeks after the event was held, I was not able to find any scoring information or even the name of the winning team.

Designing the Robots

Speaking of the winning team, the four humans involved had never even heard of MIROSOT until six weeks before the event was scheduled. Randy Sargent, Anne Wright, Carl Witty, and Bill Bailey, all

AMATEUR ROBOTICS

members of the Seattle Robotics Society (SRS), were deep in the design of their winning AAAI entry (see my column, Oct. '96) when Randy got word of the looming soccer contest. When presented with the idea of entering this contest as well, the other three team members responded with a loud, "No way!" The AAAI design effort was already back-breaking; no one wanted to pile on yet another project.

But Randy wouldn't let the idea die, and mentally tinkered with what it would take to build so much capability into such a small package. Finally, he decided that he would spend one day, no more, trying to build a robot prototype to do the job. If, at the end of that day, he had a machine that was promising enough, he would once more ask the team about entering the MIROSOT event.

That evening, Randy had fashioned a small robot out of a cut-down 68hc11 Miniboard, some surplus gearhead motors, and two nine-volt batteries. The whole package fit within the required space, with 1/2" of headroom at the top, allocated

way FM stereo radio systems, designed to pipe audio from some source, such as your stereo TV, to one or more headsets for private listening.

Randy and Bill were intrigued about using the headset as the RF link on a robot. The transmitting side seemed simple enough; just add a resistor divider to the serial output from a PC's COM port and run the reduced signal into the audio input of the wireless headset transmitter. Whatever serial data you sent to the COM port would be transmitted as audio tones over the 900 MHz RF link and picked up on the headset's receiver.

Bill then designed a one-IC level detector and squaring circuit to convert the received signal into digital levels, for wiring directly into the Serial Communication Interface (SCI) of the Miniboard. Initial tests looked very good; the 9600 baud data stream appeared at the SCI port and was mostly accurate.

But not all of the characters came through cleanly. Tests showed that the headset's amplifier — which naturally treated the signal as audio — was

trying to keep the output centered at 0 volts. Bill's circuit would then drop out some of the bits, since the signal had settled outside the detector's threshold.


Rather than give up on the whole design, the two determined by experimentation that if a data byte contained three, four, or five one-bits, the byte came through intact. Apparently, these patterns kept the receiver's output signal in a suitable range for Bill's detector circuit. Armed with this data, they developed a table of the 182 different bit patterns that could be transferred successfully. They then built a conversion scheme that let them send the commands and data

they needed, using only the permitted characters.

Further tests showed that the RF link worked perfectly at 9600 baud. Randy bought a few more headsets, Bill worked up a mechanical mounting scheme for the liberated receiver boards, and the RF link was in place.

Next up, the team needed some type of pulse-width modulation (PWM) control for the DC gearhead motors they had selected. These were prime units, but they were never meant to run on 18 VDC. And since the event called for both speed and control, the motor controller really needed some type of feedback for sensing actual speed. But there was no physical room left for adding wheel encoders and sensors. The designers needed another way.

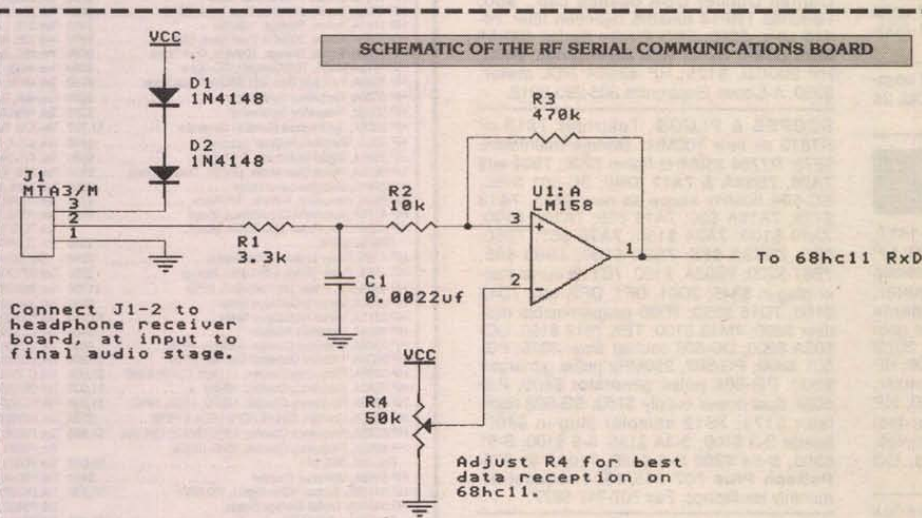Bill had been working for some time on just such a speed controller, based on an idea he had picked up from Lance Keizer, one of the SRS regulars. Bill's design uses a 68hc11 A/D port to monitor the voltage on a motor's power leads, sensing the back EMF as a measure of the motor's running load. The circuit is quite simple, consisting of a few passives, including some diodes to protect



for the not-yet-designed communications electronics. It was crude and didn't run straight, but it worked enough to convince the others that the design was indeed possible.

Following their triumph at the AAAI event, and after moving tons of computer and robot gear into a new house in Bellevue, the four teammates settled down to tackle the difficult design elements of the soccer robots. Tops on the list was some method of sending information between a host PC and the three small robots. Since the host PC would use the Newton Labs vision system to monitor the playing field, the team only needed a one-way link. But that link had to run at least 9600 baud, or it couldn't keep up with the vision system or the action.


The group quickly ran through existing possibilities, discarding each in turn. IR was out, as it was too susceptible to ambient light; the sodium vapor lights at AAAI proved that. The team couldn't find a small enough RF modem in time, and was running out of options when Randy stumbled onto the answer. He returned home one day with a couple of wireless stereo headphones from the local Radio Shack. These are basically short-range one-

the A/D port from out-of-bounds voltages. Coupled with the appropriate software, the little gearhead motors provided excellent performance. Bill's back-EMF motor sensor really deserves more attention than what little I'm providing here. Look for more info in an upcoming article.

Now Bill turned his attention to the mechanics needed to build the little robots. Three inches on a side doesn't leave a lot of room for hardware and, with Randy's help, Bill put together a robust platform with a minimalist design. Two small pieces of flat 1/8th-inch aluminum stock form the base. The motors, nestled side-by-side with the output shafts facing opposite directions, are held to the base with a thin, sheet steel clamp and metal screws. Four posts, made of threaded aluminum spacers, hold the stack of PCBs tight against the top of the insulated motor clamp.

The PCB stack consists of three boards. The cut-down Miniboard sits at the bottom, and holds the 68hc811e2 MCU, the motor power driver chips, and sundry LEDs for status. The middle board contains all of Bill's custom circuitry, including wiring for checking the remaining battery voltage. At the top sits the cannibalized RF board from the FM headset, held into place by short pieces of copper wire, acting as guys to nearby 4-40 hardware at the top of the spacer stacks.

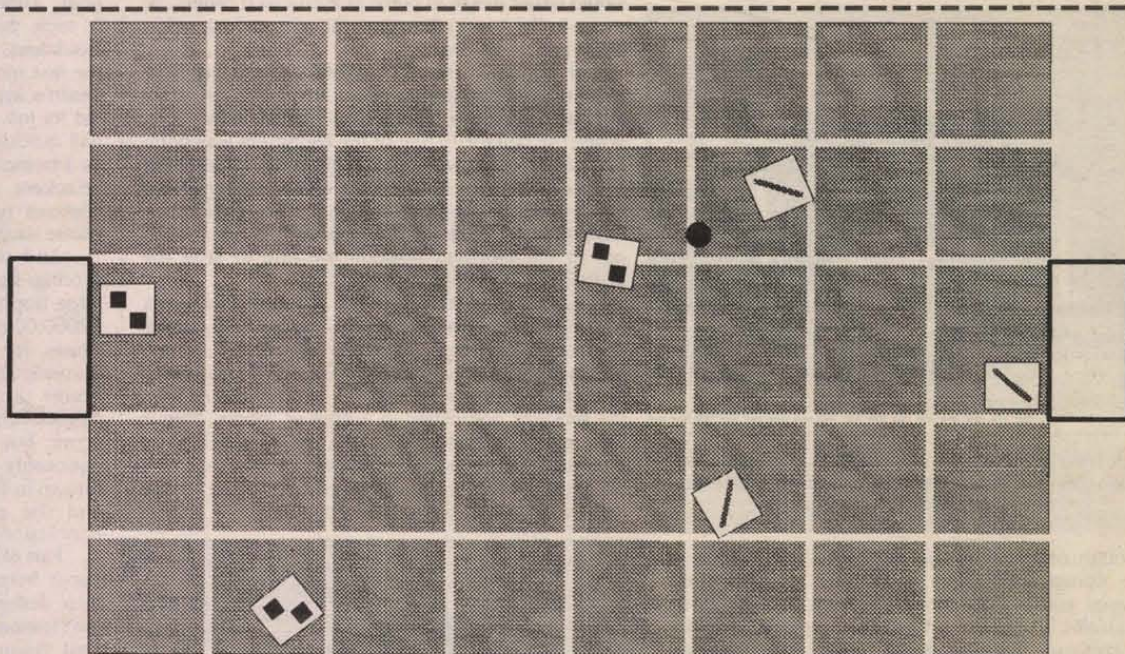Randy's original prototype had the drive wheels



OVERHEAD VIEW OF A TYPICAL MIROBOT ROBOT SOCCER LAYOUT

shaft after just a few starts. Various glues couldn't hold the steel shaft to the wheel, so more drastic measures were needed.

Bill machined a narrow slot down the center of a motor shaft, into which he wedged short wire. They fitted the wheel onto the shaft and tried again, but the motor's torque snapped the wire. A square metal wirewrap pin fared better; it bent, but did not break. Finally, Bill used a small piece of hacksaw blade, cut to the proper shape. Randy fitted a Lego wheel onto this shaft and key arrangement, potting the wheel in place with hot glue.

This mounting system has proved remarkably robust, and the team gets a charge out of seeing this item in the official bill of materials; "one hacksaw blade, heavily modified."

The robot power system proved another obstacle. The team had considered using small NiCd batteries for power, but abandoned that

more and more energy into the project. The programming team, headed by Carl Witty, needed to build three suites of software. The 68hc11 code didn't need to do much by most robot standards; just basic command parsing and motor control. But they only had 2K of code space to work with, and translating the incoming characters into the proper numbers and letters used up a lot of space. Finally, with only bytes to spare, the 68hc11 code was ready to lock down.

The host system, however, was a different story. It consisted of two machines, the 68332 board that ran the vision system and a Pentium PC running Linux, used to calculate robot motions and direct traffic on the playing surface. The 68332 ran a suite of code for translating the color video signal into a data stream for use by the Linux box. Most of the 68332 code carried over from previous projects, but fitting it all together into a cohesive unit still took valuable time.

The Linux code to run the whole soccer team required a massive amount of design effort and computational capacity. The vision system, providing updates at 60 frames per second, pushed the original Pentium system to the limits as it tried to keep up with a rolling ball, the coordinate system, and all the robots running around on the field. Shortly before leaving for Korea, the group decided that they simply needed more horsepower, so they picked up a P6-180 machine.

And I do mean "shortly." In fact, the box arrived the morning before the group got on the plane for Korea. The Linux installation obviously worked, given the contest's outcome, but that was cutting it way too close.

After all this effort under vicious deadline pressure, the group was beginning to worry that maybe they weren't going to be able to pull this one off. Whereas a few weeks prior they had naively determined to grab first prize, the size of the competition and the problems they had struggled to overcome made them rethink their objectives. They freely admit that by the time they boarded the plane, their goal was simply "not to embarrass ourselves."

The Big Event

After arriving in Taejeon, Korea, the group went




The winning soccer-bot designers — clockwise from lower left: Randy Sargent, Carl Witty (holding the trophy), Bill Bailey, and Anne Wright.

attached directly to the motors, resulting in off-center wheels. The unsymmetrical layout caused the robot to lurch sideways when it started up, aggravating the control and steering problems. While Bill worked on the mechanics, Randy looked into getting the wheels back on the frame's centerline where they belonged.

He ended up building a two-gear Lego drive system, using two Lego wheel-and-gear assemblies at the center axle. Fastening the Lego drive gear to the motor shaft proved difficult, however. Since the motor already had a substantial gear reduction built in, the resulting torque would pop the wheel off the

idea based on concerns over charger availability and charging time once the contest began. Instead, they opted to use a pair of nine-volt alkalines on each machine. Unfortunately, the power drain was so great that each robot could get only eight minutes of running time out of a pair of batteries. This didn't leave much spare time, since each game consisted of two five-minute halves and the team wouldn't be able to change batteries during either half. They solved the problem by sheer numbers, and boarded the flight to Korea with 100 alkaline batteries.

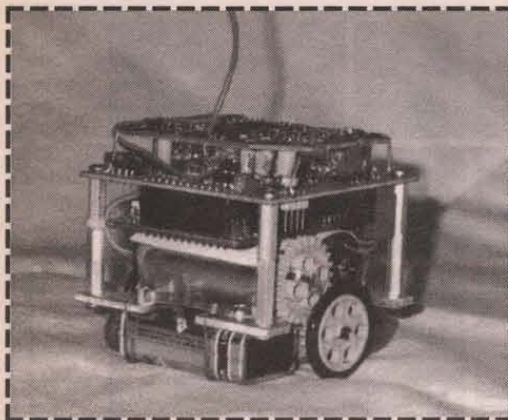As the deadline raced inward, the group poured



A frontal view of a soccer-bot, showing the two-gear Lego drive. Two nine-volt batteries, front and back, act as skids.

through registration and started to meet some of the competition. The MIROSOT contest drew several teams from Korea, as well as Singapore, Australia, France, Canada, Japan, Spain, Switzerland, Taiwan, Brazil, Italy, and Romania. Besides the Newton Labs team, the United States was represented by teams from The University of California (Riverside), The University of Southern California, and Carnegie Mellon University.

Repeated tests in the set-up area showed the strength of the group's design, and they were quickly marked as the team to beat. Since they officially represented Newton Research Labs, they became known throughout the venue as "Newton Team."

The initial draw for pairings had them set to compete on the second day, but officials wanted to change that to the first day, to provide a showcase round for various government officials. Several of the competitors involved protested, and rightly so, about the last-minute proposal. The Newton Team resolved the matter by offering to hold a demonstration match on the first day. This was accepted, and the venue prepared for the first look at this American entry.

It was (you've heard this before) not a contest. Newton Team took the demo event 12-3, and at least one of the goals scored against them was an own-goal, when the NT goalie booted the ball into its own goal. Still, the crowd applauded wildly at each score, and Newton Team got a chance to work out a couple of minor bugs before the real event began.

Looking back, one of the bugs was actually pretty funny. Both teams were set up for the kickoff and the referee blew her whistle to start the match. The NT goalie immediately raced the length of the pitch, elbowing its way through the crowd of robots, to take position at the opposite goal. Somewhere in the set-up, someone had not initialized a variable properly, and the goalie was determined to guard the other goal. At the first stoppage of play, the problem was corrected and the goalie took up a more orthodox style.


The demo match was as close as it ever got. Newton Team played a total of four matches in the single-elimination event, and in those four matches gave up just one goal, while scoring anywhere from 15 to 21 points per game.

The video tape of that event highlights a number of differences between the Newton Team robots and those of the other competitors. Tops on the list was the vision system frame rate. Every team used vision to guide their machines, but only the Newton Team was using a 60 Hz update rate; most settled for 10 to 15 Hz. This higher rate gave the NT machines a decided advantage in speed and reaction. Time after time, the opposing robots

would either freeze in place at a crucial moment, or move in the wrong direction, reacting to a situation of an instant before.

In contrast, the NT robots were never still. Jittering around like wind-up toys on Jolt, they appeared to hover in place waiting for some cue. When the ball rolled free or the alignment was right, one of the robots would suddenly shoot off after the ball, smacking it with the front end of its frame and sending the ball towards the goal. Often, this move happened too fast for the opposing goalie, which got to the blocking position too late to stop the score.

Many times, the two NT forwards set up a passing attack or a simple give-and-go, using either a direct pass from player to player or, in one instance, a bounce shot of the wall. These would often materialize seemingly out of nowhere. At first, the ball was enmeshed in a knot of robots, then it was rolling down the field with an NT machine in pursuit. When a defender moved to intercept, the NT robot passed across to its partner, which either scored or passed back to end the play.

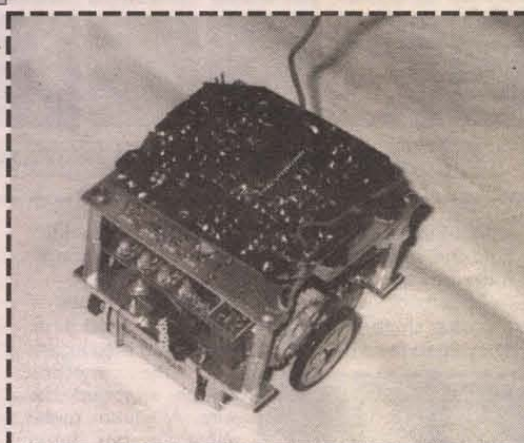

Looking down on a three-inch soccer robot. The top board came from a Radio Shack wireless headset, the second board holds Bill Bailey's custom electronics, and the third board is a cut-down Miniboard.

And these robots moved faster than I would have believed possible. After Newton Team's machines scored a goal, the opposing robots were set up to deliver a free kick from midfield. This meant that the ball would be placed in the center of the field, with an opposing robot immediately behind the ball and touching it. The NT machines, however, had to be set a minimum of six inches away. With monotonous regularity, an NT machine would streak to the ball and push it away from the opponent before that robot had even moved.

This doesn't mean the Newton Team design worked perfectly; only that the problems remaining were far less serious than those facing their competitors. For example, the power drain on the NT robots was so great that they slowed noticeably at the end of each half. In one case, the robots had actually dropped to about half speed, and it seemed doubtful that they would make it to the half before stopping altogether. They did, but it was a near thing.

In another contest, one of the robots developed a serious guidance problem that could not be fixed before halftime, so Bill Bailey, the head robot wrangler, simply turned off the power and left the robot sitting on the pitch. Even though it did figure in a later defensive play, the Newton Team played two on one for the final 45 seconds of that half; the opposing team, however, was unable to score.


This brings up the goalie. Carl's strategy for the goalie couldn't have been simpler. Just stay between the ball, wherever it goes, and the

goal. That's all the goalie had to do, and that's all it took to keep the opponents from scoring. Doubtless, other teams had the same design, but the fast motors and high frame rate of the Newton Team's system meant that the NT goalie actually did its job. Other goaltenders would not track the ball quickly enough, or would freeze momentarily as if trying to understand their instructions. The NT attackers were so fast and accurate that the slightest hesitation on the part of the defending goalie usually resulted in an NT score.

And the Newton Team robots did a lot of scoring. By the final round, played for first place, a large trophy, and the generous prize money of US \$2000.00 the audience was becoming pretty jaded. Hopes for the competitors were dashed almost immediately as NT grabbed a couple of quick scores on the way to a 20-0 rout. The audience, overwhelmingly Korean, still applauded every score, but by the second half the applause was noticeably restrained. A human team would have thrown in the towel early on, but these were robots, and the contest ground along to its foregone conclusion.

Part of the MIROSOT event included a published paper from each team, describing some aspect of their design they felt most important. Accordingly, the Newton Team presented a paper entitled, "Use of Fast Vision Tracking for Cooperating Robots in the MIROSOT." As I mentioned in my previous column on the AAAI event, the Newton Research Labs' vision system, dubbed Cognachrome, is available commercially. Stop by the Newton Labs web site at www.newtonlabs.com to leaf through the technical info.

When last I talked to the Newton Team, they were planning to kick back and relax, to wind down from the grueling (and self-inflicted, I might add) pace of the past several months. Anne and Randy have taken up the Magic game, Bill wants to get back to writing software, and Carl has wads of Linux systems scattered all through the new house on which to work his own magic. But it won't take much to get them cranked up again. Randy, in particular, is usually just one E-Mail away from charging down yet another avenue, and he always brings his friends along. So stay tuned; you haven't heard the last from these SRS members. **NV**

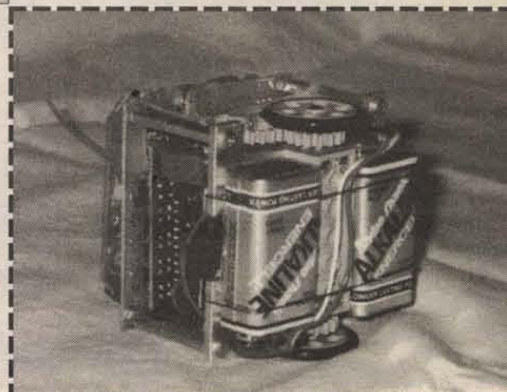

The underside of this little robot shows the two nine-volt batteries, with the Lego axle and drive train running between them. Thin wire clamps hold the batteries to the custom metal frame.

As always, you can reach me at:

Karl Lunt
2133 186th Pl., S.E.
Bothell, WA 98012

E-Mail: karl@mav.com
Web: <http://www.seanet.com/~karllunt>

Media-Tech

INTERNATIONAL

Your Source For All Your Cable TV Accessories!

And We Mean All!

DEALERS SPECIAL!

BUY A
MILLENNIUM CONVERTER, ETC...

\$89

Unassembled • Minimum order 50

FOR TECHNICAL SUPPORT CALL
(305) 234-9795

**SAME DAY
SHIPPING**

**90 DAY
LIMITED WARRANTY**

**9am - 5 pm
(Eastern) M-F**

FOR
ORDERS
ONLY
CALL...

1-800-673-6178

SORRY...NO FLORIDA SALES

C.O.D. - MONEY ORDER ONLY

90 DAY WARRANTY PARTS AND LABOR

10 DAY INSPECTION PERIOD

WE BUY AND SELL

HEWLETT PACKARD

200SR, 5 Hz to 600 KHz Oscillator.....	\$100
3400A, RMS Voltmeter, 10Hz-10MHz.....	\$175
415E, SWR Meter.....	\$150
432A, Power Meter.....	\$125
435A/848A, Power Meter.....	\$950
10 MHz - 18 GHz, -70 to -20 dBm	
5006A, Signature Analyzer.....	\$450
5302A, 50 MHz Counter.....	\$200
5303A, 500 MHz Counter.....	\$300
5303B, 525 MHz Counter.....	\$325
6012A, Autoranging Pwr. Sup.....	\$1100
0 - 60V, 0 - 50A, 1000 Watt	
6102A, Pwr. Sup., 0-40V at 0.5A.....	\$150
6114A, Precision Pwr. Sup., 20V at 2A, 20-40V at 1A.....	\$550
6200B (Har), Pwr. Sup., 40V at 0.75A, 20V at 1.5A.....	\$200
6202B (Har), Pwr. Sup., 0-40V at 0.75A.....	\$175
6384A (Har), Pwr. Sup., 4-5.5V at 8A.....	\$150
6824A, Pwr. Sup./Amplifier.....	\$375
+/- 50V, +/-1A, 20 dB gain, DC-10 KHz	
739AR, Voltmeter Calibrator.....	\$350
8082A, Pulse Gen., 250 MHz.....	\$1250
10833A, 3.3 Ft HPB Cable.....	\$25

MISCELLANEOUS

Ailtech 75, Precision Automatic Noise Figure Ind.....	\$750
Calif. Inst. Invertron 101TC, Pwr. Source.....	\$800
0-130VAC, 45Hz-5KHz, 350 Watt	
Calif. Inst. Invertron 351TC w/ 850T, Pwr. Source.....	\$1700
0-130VAC, 45Hz-5KHz, 350 Watt	
Calif. Inst. Invertron 351TC w/ 815T, Pwr. Source.....	\$1350
0-130VAC, 400Hz, 350 Watt	
Cober LMA-1-90, Amplifier, 30 dB, 1 - 2 GHz, 1 W.....	\$700
David Clark H3313, Headsets (new) w/ mouthcup.....	\$85
Drantz 606, Line Analyzer.....	\$625
EMI SCR500-10-1110, Pwr. Sup., 0-500V @ 10A.....	\$1200
Fluke 803, Differential Voltmeter.....	\$125
GenRad 219M, Decade Capacitor.....	\$75

GenRad 1432C, 3-Decade Resistor, 0-11,100 ohms.....	\$75
GenRad 1482-H, Standard Inductor, 10 mH.....	\$250
GenRad 1482-P, Standard Inductor, 1 Henry.....	\$250
Gigatronics 9002-8, Sweep/Sig. Gen.....	\$3500
2 - 8 GHz, opt 026 GPIB	
Heise 710A, Digital Pressure Gauge, 0 to 30 PSI.....	\$400
Heise 711B, Digital Pressure Gauge, 0 to 30 PSI.....	\$675
Hickok 539B, Tube Tester.....	\$275
Keithley 617, Programmable Electrometer.....	\$2700
Manufacturers Calibration, new 6011 Cable, Manual	
Krohn-Hite 3550, Passband Filter.....	\$350
Lambda LB-723-FMOV, Pwr. Sup., 0-36V at 135A.....	\$925
Lambda LH122FM, Pwr. Sup., 0-20V at 3.3A.....	\$200
Lambda LQ-521, Pwr. Sup., 0-20V at 3.3A.....	\$250
Tek T922R, 15 MHz O'Scope.....	\$250
Valhalla 4440, 4-1/2 Digit Voltmeter.....	\$100
Wavetek 130, 2 MHz Func. Gen.....	\$125
Wavetek 154, Prog. Waveform Gen., 100Hz-10MHz.....	\$350
Wavetek 2001, Sweep Gen., 1-1400 MHz.....	\$750
Wiltron 560, Network Analyzer, 0.1 to 18GHz.....	\$1500
560-97N50 SWR Autotester, (2)560-7N50 RF Detectors	

WANTED

Fluke 5100B Card Extenders, 420323 & 455758

Hewlett Packard Card Extenders

Tektronix 7000 Series Plug-In Extenders, 067-0589-00 & 067-0616-00

Tektronix TM500 Series Plug-In Extenders, 067-0645-02

• Test Equipment Catalogs, 1970's and 1980's

Used Test Equipment



TEST EQUIPMENT PLUS

(520) 575-6967, FAX (520) 575-6936
3331 W. Bright Terrace, Tucson, AZ 85741



Write in 59 on Reader Service Card.

TEST EQUIPMENT cont.

OSCILLOSCOPE MAINFRAME, TEK 5110, \$79 ppd; **TEK 7A26**, 200MHz, \$85 ppd; **KAY 1520A** sweep generator, 50KHz-1200MHz, \$145 ppd; **BALLANTINE 323** True RMS voltmeter, \$65 ppd; **TEK TM501** power module, \$35 ppd. Morgan Test Equipment Sales, PH/Fx 717-842-5590.

WANTED! TEST equipment. We pay top dollar for used scopes, generators, analyzers from HP, Tektronix, and others. Call Charles at Metric for immediate quotation. 1-800-432-3424.

PORTABLE SCOPES: Tek 222A (10MHz) handheld, battery-operated digital storage \$1,500. **Tek 465** (100MHz) \$425. **Tek 475A** (250MHz) \$650. **Tek 475A/DM44** (250MHz, multimeter) \$735. **Tek 466** (100MHz, storage) \$695. All with bright CRTs; excellent condition, warranty. Pepper Systems, 214-353-0257.

FEITEK HAS the test equipment you want at reasonable prices. We buy, sell, and trade HP, Tek, GR, etc. Call or fax Monday thru Friday, 9 to 5, 314-423-1770, or write us at Box 3423, St. Louis, MO 63143.

DEC EQUIPMENT WANTED!!! We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), DSD, Datability, Dialog, other DEC compatibles, and Computer Output Microfilm (COM) units. Please call for a quote or fax us your equipment list. We buy, sell, and trade. **KEYWAYS, INC.**, 513-847-2300 OR fax 513-847-2350.

WANTED: WESTERN electric test equipment. Tube-type only please. Freq. measuring sets, oscillators, amplifiers, parts, tubes, etc. 1-800-251-5454.

Quality
ELECTRONICS

Yes, we can help with all your cable needs

QUALITY PRICES

QUALITY SERVICE

QUALITY PRODUCTS

1-800-394-3043

9am-5pm M-S • Same Day Shipping

1 FULL YEAR GUARANTEE

CALL TODAY!

NO NV SALES

Learn MICROCONTROLLERS EMBEDDED SYSTEMS and PROGRAMMING...

with the AES learning system/
embedded control system.
Extensive manuals guide
you through your
development project.
All programming
and hardware details
explained. Complete
schematics. Learn to program the
LCD, keypad digital, analog, and serial
I/O. for your applications.



THREE MODELS AVAILABLE.
Choose from an Intel 8051,
Intel 8088, or Motorola 68HC11
based system.
All models come with:

• 32K Byte ROM, 32K Byte RAM • 2 by 16 Liquid
Crystal Display • 4 by 5 Keypad • Digital, Analog, and
Serial I/O • Interrupts, timers, chip-selects • 26 pin
expansion connector • Built-in Logic Probe • Power
Supply (can also be battery operated) • Powerful ROM
MONITOR to help you program • Connects to your
PC for programming or data logging (cable included) •
Assembly, BASIC, and C programming (varies with
model) • Program disks with Cross Assembler and
many, well documented, program examples • User's
Manuals: cover all details (over 500 pages) •
Completely assembled and ready to use • Source code
for all drivers and MONITOR • Optional Text Book

Everything you need. From \$279

Money Back Guarantee

Call for Free Info Pack, or see

WEB at <http://www.aesmicro.com>

714-550-8094, FAX 714-550-9941

Call 1-800 - 730-3232



AES 970 W. 17TH STREET, SANTA ANA, CA 92706, USA

TEKTRONIX EQUIPMENT: 184 time mark generator, \$150; 109 pulse generator, \$100; 106 squarewave generator, \$200; 130 LC meter, \$200; 475A, 250MHz scope, \$600; 620 XY display, \$250; dual 620 side by side rack mount, \$500; 634 video display, \$250; 7603 3 slot frame, \$250; 7904 500MHz 4 slot frame, \$500; 7834 400MHz storage frame, \$500; TM506, \$200, TM504, \$150; TM503, \$130; 7623A, 7A26, 7A26, 7B53A, \$650; 7A11, \$300; 7A26, \$200, 7A19, \$150; 7B80, \$200, 7B92A, \$250; C51 camera and back for 7000 series scopes, \$150; DM501A 4.5 dig DVM, \$200, FG503, \$300; R468 100MHz dual channel 10MHz dig storage, \$600; PG501, 50MHz pulse gen., \$200; PS501-2, \$150; PS503A, \$200, T922, 15MHz dual channel scope, \$200; TM515 5 slot frame, \$250; SG502, \$300. A-Comm Electronics 303-290-8012.

SPECIAL PURCHASE. Wavetek synthesized function generator \$475. 2 available. Psitech Plus 707-745-4804, Fax 707-747-5277.



HP 5328A COUNTER/TIMER 10Hz to 520MHz, large 9-digit LED, solid-state, high-stability OVEN timebase (<5x10-10), time, frequency, ratios. Frequency standard outputs of 1MHz and 10MHz. (Sale price this month only) \$525. [With DVM (for reading trigger levels) \$575] Gary N6ZD, 408-385-0301 VISA/MC.

HP 1710B 200MHz oscilloscope with probes \$495. **TEK PG502 250MHz pulse generator** \$190. **Lambda LPD 421A 0-20V, 0-1.7A** dual lab power supply \$190. All in excellent cond. For more great deals on used working test equipment visit our Web site at <http://www.odulo.com/corp/equipetek> or call 415-244-9438.

DIRECTIONAL COUPLER, KDI, 1MHz-1000MHz, 10dB, BNC, \$29 ppd; HP 332A distortion analyzer, \$85 ppd; PD 6050A, 0-60 VDC, \$79 ppd. Morgan Test Equipment Sales, Equipment Division. Ph/Fx 717-842-5590.

AFFORDABLE HP power sensor repair! Most 8481As repaired for \$230 or less. We also handle 478As and many others. Call or fax for more information. Willamette RF, Inc., 541-754-7226, FAX 541-753-4629.

TEK 7603A \$200. HP plotter 7475A HP-IB \$200. HP 5381A frequency counter \$25. Tek Z plug \$20. HP 1610A, 1610B logic state analyzer \$50. Tek 7704 oscilloscope, 7A18N, 7A26, 7B53A \$200. HP 432A power meter \$60. HP 350B attenuator set \$50. HP 34702A multimeter \$40. Fluke 1935AE counter timer \$100. Tek 7B71 \$50. Tek P6452, P6455 data acquisition \$25. General Radio 1432-K decade resistor \$40. Fluke 2204A scanner \$50. Data precision 1350 \$25. Sainclair multi-meter \$40. Simpson multimeter 461 \$40. Call 714-827-7345.

10TH ANNIVERSARY SALE! HP 3488A switch/control unit \$925. **HP 59306A** relay actuator (6-SPDT, HP-IB and lighted push-button) \$260. **HP 59307A** dual VHF switch (2-SP4T, HP-IB and lighted pushbutton) \$230. **HP 59401A** HP-IB bus analyzer \$350. **Stanford Research SR 510** lock-in amplifier \$1,750. **HP 4274A** LCR meter (5-1/2 digit, 100Hz-100kHz) \$3,800. **HP 3314A** .001Hz-20MHz function generator, lin/log sweep, etc. \$2,800. **HP 8015A** 50MHz pulse generator \$375. **HP 8016A** ECL/TTL word generator \$295. **HP 8161A/020** 100MHz programmable precision dual channel pulse generator \$3,300. **HP 8175A/002, 005** 50MHz digital/analog signal generator: TTL/CMOS pods, dual arbitrary waveform channels \$3,300. **HP 5334A** 100MHz auto rise/fall time, etc. counter \$850. **HP 5345A** 500MHz counter with HP-IB \$725. **HP 5370A** 100MHz time interval counter (oven time base) \$1,600. **Fluke 720A, 721A, 750A, 845AR** DC voltage calibration system components \$2,500. **Fluke 540B** transfer standard \$800. **HP 7580B** drafting plotter (sizes A-D) \$1,300. **HP 7586B** (sizes A-E) \$1,850. **HP 7595A** DraftMaster I (sizes A-E) \$2,000. **HP 7475A** \$220. **HP 7090A** measuring plotter \$2,100. Excellent condition! All with warranty. Pepper Systems, 214-353-0257.

AMAZING ELECTRONIC & SCIENTIFIC DEVICES

Lasers, Tesla, Ions, Anti-Gravity, Magnetics & More!
Plans • Ready-to-Use • Easy-to-Build Kits

Laser Ray Gun
Handheld, battery operated. Produces an intense burst of light capable of burning holes.
LAGUN2 Plans \$20.00
LAGUN2K Kit / Plans Price on Req

Visible Beam Gas Lasers
Millions degree temp equiv. Illuminates low level clouds.
• Light Shows
• Window Listener
• Optical Projects
• 12/115V
• Science Project
LASIKM 1mw, low cost Kit \$69.50
LGUK6 2-3mw Kit \$119.50
HNE70 5-7mw, ready to use \$299.50

Ion Ray Gun
Project Energy!
Star Wars technology demonstrates weapons potential. 10G7K Kit/Plans \$99.50

4000 Volts 10ma High Voltage
Module - Ready to use - for many projects from hoverboards to pyrotechnics.
MINMAX4 While they last! \$19.50

250KV Tesla Coil
10-14" of Explosive Bolts of Lightning!
• Transmuter Wireless Energy
• Ion Motors
• Anti-Gravity
• Strange and bizarre pyrotechnical effects
• Many other experiments shown in detail!
Award winning science project!
BTC3 Plans \$15.00
BTC3K Kit/Plans with coil \$299.50
BTC30 Assbld Ready to Use \$399.50
BTC4 Plans, 500KV unit \$20.00

Gravity Generator
Levitate an object!
Great science fair project!
GRA1 Plans \$15.00
GRA1K Power Supply Kit/Plans \$99.50
GRA10 Assbld Kit/Plans \$149.50
Includes text book on Anti-Gravity theory!

"Talking" Plasma Globe
Spectacular color. Pulsates to music, sounds! 8-9", with intensity and sound controls. PLASMA1 Ready to Use \$79.50

ATTENTION: Experimenters & Researchers!
Anti-Gravity, Rail & Coil Guns, Mass Warping, Levitation Research, Exploding Water, Propulsion Drivers, Lattice Snapping, EMP etc. Loss-less Energy Charger with triggered spark switch. • Adjustable 500 to 3KV out
• Charges up to 25KJ • Programmable Output
HEP1 Plans \$15.00
HEP1K Kit/Plans with 500J \$399.50
HEP10 Lab Assembled - to your spec's.
Write, call or fax for price & delivery
..... shown connected to potential rail gun system

Solid State Tesla Coil
• Generate fiery electrical plasma discharge
• Powers light and objects without contact
• Experiment with electrical and mechanical fields. TCL5 Plans \$8.00
TCL5K Kit/Plans 12VDC \$49.50

Pioneer a Futuristic Weapon!
Electric Gun - prototype designed in our lab - Join the research!
• Ballistic Velocities
• Handheld • Battery Operated
• Labelled as DANGEROUS Product
Experiment now before it is classified as a firearm! EGUN1 Plans \$20.00
(Must be 21 for purchase of hardware)

Electronic Hypnotizer
Control their minds! Programmable audible and visual stimuli induces hypnotic trances. HYP2K Kit with Book \$39.95
EH2 Hypnosis Book & Plans \$14.95

We can design and build high voltage systems - to your specs!
Call or fax us with your requirements!

TACTICAL ELECTRONICS

Cybernetic Ear!
Enhances normal hearing 3-4 times!
Adjustable volume control, fits easily into either ear. Many, many uses.
Ready to Use!
CYBEREAR \$19.95

3 Mi Telephone Xmitter
• Tune-able 80-130 Mhz • Undetectable
• Only transmits when phone is used
VWPM7K Kit/Plans \$39.50

Extended Play Telephone Taping System
• Tapes Phone Conversation • Extends Tape X4 • Check Local Laws before using!
TAP9X3 Ready to Use \$84.50

3 Mi Tracker Transmitter
• Tunable Output
• Uses FM Radio
• Excellent Signal Beacon
HOD1K Kit/Plans \$39.50

Window Bounce Laser Listener
Aim at window and listen to sounds from reflected light. CAUTION - Not for illegal use. LWB3 Plans \$10.00
LWB3K Kit/Plans (req's vid tripod) \$149.50

Telephone Line Grabber/Infinity Transmitter
Use lone phone anywhere in the world to:
• Monitor your premises - avoid break-ins
• Access ongoing calls - longwinded kids
• Control up to 8 appliances in your home!
• Re-direct costly toll calls from pay phones!
TELCON3 Plans (credit to purch) \$ 10.00
TELCON3K Kit/Plans \$99.50
TELCON30 Ready to Use \$149.50

3 Mi Voice Transmitter
• Ultra-Sensitive Mike
• Crystal Clear
• Tunes 80-130 Mhz.
FMV1K Kit/Plans \$39.50

"Drop-In" (Imi) Telephone Transmitter
Easily tunable over FM radio. Never needs battery! #DROPI Kit/Plans \$ 19.95

MIND CONTROL!
Places subjects under your control. Programmable audible & visual stimuli with biofeedback. Induces strange & bizarre hallucinations without drugs. Caution - not FDA approved.
MIND2 Plans \$15.00
MIND2K Kit and Plans \$49.50
MIND20 Assembled Unit \$69.50

Long Range "Ultra-Ear"
Parabolic Mic can hear a distant whisper! BUG Mother Nature!
20" dish uses satellite technology to capture distant sounds. PMS Plans \$ 8.00
PMSK Kit/Plans \$149.50
• Optional Wireless Retrofit transmits captured sounds to an FM radio.
WM5K Kit for Wireless Option \$29.50

FireBall Gun
Shoots flaming ball - two shot capacity. Great for special effects and remote fire starting. CAUTION REQUIRED!
FIREBALL Plans (dangerous product) \$10.00

See In Total DARKNESS!
• High Quality IR Night Vision Scope with IR illuminator.
SD10 Ready to Use \$199.50

FANTASTIC BRIGHTNESS!
High Quality Laser Pointer
LAPN64 15mw eqv, 2000' \$39.50
LAPN61 50mw eqv, 4000' \$84.50


1000' Potato Cannon
Not a Toy! Uses electronic or piezo ignition. CAUTION REQUIRED!
POT1 Plans (dangerous product) \$10.00

Phasor Sonic Blast Pistol
Rids areas of unwanted pests. Trains and conditions wild and domestic animals. Great for barns, attics, cellars, gardens.
PPPIK Kit/Plans \$39.50

Shocker Force Field/Vehicle Electrifier
Make hand and shock balls, shock wands and electrify objects. Great payoff for those wiseguys!
SHK1K Easy to Assemble Kit \$19.50

Electric Charge Gun
Life is Precious - PROTECT IT!
Stuns & immobilizes attackers 15 feet away! Check your state laws for legality. More knockdown power than most handguns. No permanent injury. ID coded. ECG1 Data
(Creditable to purch) \$10.00
ECG10 Charge Gun, Ready to Use, Includes FREE Stun Gun! \$249.50
STUN GUNS - sold separately:
STUN100 100,000 Volts \$34.50
STUN200 200,000 Volts \$49.50

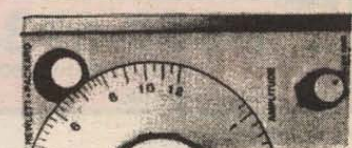VISIT US ON THE WEB!
<http://www.amazing1.com>



HP 204C OSCILLATOR 5Hz to 1.2MHz, .1% distortion, leveled (flat) 5V out. Sale: two for \$225, one \$125. Gary N6ZD, 408-385-0301 VISA/MC.

TEST EQUIPMENT SALE: The following equipment is offered at \$250 each PPD CONUS. All items include manual, accessories and have been lab tested. DATA Precision 3500 5-1/2 digit DVM, GR 1236 IF Amplifier, GR 1531AB Stroboscopes, ENI 300L Amplifier, FLUKE 1935A Frequency Counter, HP 432A Power Meter plus cable, HP 435A Power Meter plus cable, HP 428B Milli-ammeter w/probe, HP 400F AC Voltmeter, HP 400F AC Voltmeter, HP 182C Oscilloscope Mainframe, HP 652A Test Oscillator, HP608E signal Generator, HP 606A Signal Generator, HUNTRON TRACKER 1005B-S1, KROHN-HITE 4100 Pushbutton Oscillator, TEKTRONIX 7603 Mainframe, TEKTRONIX 575 Curve Tracer, WAVETEK 154 Function Generator. Call/Fax: E-Mail Brian at Kentronix 908-681-3229, 908-681-3312 Fax, brian@kentronix.com E-Mail, PO Box 2444, Farmingdale, NJ 07727.

FLUKE 5200A AC voltage standard \$1,400. Fluke 5215A power amplifier \$1,100; Fluke 332D DC voltage standard \$500; Fluke 3330B DC voltage, current standard \$200; HP 432A power meter \$150; HP 3478A 5-1/2 digit multimeter \$500; HP 5005A signature multimeter \$250; HP 1741A 100MHz storage oscilloscope \$400; Tektronix 7R903 500MHz oscilloscope \$300; HP 5335A universal/statistical counter \$900; HP 3400A RMS voltmeter \$110; Tenney BTRC temperature/humidity chamber \$5,500. Credit cards accepted. Call or fax to request list of other equipment. Phone: 908-722-6157, Fax: 908-722-6391.

FACTORY NEW Wavetek RF portable power meter, complete system, 1990 price \$2,860. Our price \$575. 4 units available. Psitech Plus 707-745-4804, Fax 707-747-5277.

SCOPEBOOSTER KITS close out. Nov. '96 issue, \$39.95, S&H \$4.50. Technology Systems, PO Box 1401, Torrington, CT 06790-1401.

INFORMATION UNLIMITED

Dept NV-7, Box 716, Amherst, NH 03031
Phone: 603-673-4730 FAX: 603-672-5406
MC, VISA, COD, Checks accepted Please add \$5.00 S & H

CATALOG!
FREE with Order or send \$1 P&H
24 Hour Phone
800-221-1705
Orders Only Please!

Move Up To The Ultimate In Robotic Kits.



OWI's "Next Generation" of affordable, rugged Robot Kits challenge the enthusiast to solder circuit boards and mechanically assemble.

Each OWIKIT also incorporates the basic principles of robotic experiments, sensing and locomotion, guaranteeing an exciting, hands-on adventure of knowledge and fun!

But remember! OWI is the recognized founder and leader in Educational Robot Kits.

ACCEPT NO IMITATIONS.

Visit our homepage
@ <http://www.owirobot.com>



Hyper Peppy	MY-969	Sound / Touch Sensor	46 Pg. Book	\$ 24.95
SELECTABLE GEAR BOX	OWI-GB25	6 Gear Ratios	(Ltd. Qty.)	\$ 10.00
ELECTRO-MAGNETIC TRAIN	OWI-653	Basic Electronics	(Ltd. Qty.)	\$ 10.00
S-CARGO	OWI-936K	Sound Sensor	47 Pg. Book	\$ 29.95
WAO II	OWI-961K	Programmable - Graphic	59 Pg. Book	\$ 69.95
SPIDER	OWI-962K	Infrared Sensor	49 Pg. Book	\$ 49.95
LINE TRACKER	OWI-963K	Infrared Sensor	48 Pg. Book	\$ 49.95
MANTA	OWI-966K	Sound / Touch Sensor	44 Pg. Book	\$ 29.95
MOON WALKER	OWI-989K	Solar Sensor	10 Pg. Book	\$ 34.95

1160 Mahalo Place, Suite B
Rancho Dominguez, CA 90220-5443
(310) 638-7970
Fax: (310) 638-8347



Order M - Fr. 8a.m. - 4p.m. PST

Write in 112 on Reader Service Card.

SALE: HEWLETT Packard 3400A True RMS voltmeter \$85, quantity discounts. **BOONTON RF** millivoltmeter 92A \$125; 92B \$225; 92C \$300; 93AD True RMS voltmeter \$375. Probes available. **GERTSCH** phase angle voltmeter \$65; Hewlett Packard 8614A, 5-2.4 GHz \$200; HP 8616A, 1.8-4.5 GHz \$175. **TTI** LED display SEND/REC test sets models 1120 \$250, 1122 \$200 mint. **Polaroid** signal generators model 1106EN w/1020T 1.8-4.4 GHz complete with acc and manual \$165. Model 107E-FT 3.7-8.4 GHz \$150. Mod. 107E-FWTJ \$275. **Hewlett Packard** 86242A, 5.5-9.0 GHz RF plug-in \$325; 86260A 12.4-18 GHz \$375, 5257A, 5-18 GHz transfer oscillator \$250; 6406A comb. generator \$275. **Interface Technology** RS-648 timing simulator & word generator complete with all manuals \$150. Without manuals \$100. **Quantech** transistor noise meter Model 310 \$85. **Psitech Plus** 707-745-4804 request bi-monthly fax listings, Fax 707-747-5277.

10TH ANNIVERSARY SALE! RF EQUIPMENT: HP 8761B coaxial switch (18GHz, SMA) \$90. HP 33300D (70dB), 33304D (11dB), 33305D (110dB) latching step attenuators (18GHz, 2W, SMA) \$190, 225, 265. HP 5342A/001 counter (18GHz, oven option) \$2,000. HP 11869A adapter for 8350B \$350. HP 436A, 8481A power meter, sensor \$1,650. HP 86290B, 8620C sweep oscillator (2-18 GHz) \$2,200. Excellent condition, with warranty. **Pepper Systems**, 214-353-0257.

LOGIC ANALYZERS Hewlett Packard 8407A & 8412A phase magnitude display w/11655A impedance probe \$750; network analyzer systems. HP 8410B/8412A/8413A/8414A \$950. **Tektronix 308** complete analyzer system \$450. Hewlett Packard 1600A \$200. Hewlett Packard channel pulse 1GHz single channel. **Psitech Plus** 707-745-4804, Fax 707-747-5277.

WANTED: MEASURING & Test equipment, microwave components, RF connectors, etc. **Top price paid!** Write or FAX you list to: **Steigerwald GmbH**, Ungerstrasse 180, D-80805 Munich, Germany. FAX 011-49-8441-804881.

USED TEST EQUIPMENT. HP, TEKTRONICS, FLUKE. WHOLESALE PRICES. CALL TO RECEIVE LIST BY FAX OR MAIL. TJ'S WHOLESALE SURPLUS. 904-897-6482.

EQUIPMENT MANUALS we have 1000's of service and operators manuals for all types of test and measurement equipment from 1950 to present. All test equipment manufacturers are represented. Call, write, or fax your want list. Please include mfg.'s manual P/N unit serial numbers if known. **Manuals Plus**, Box 549, TAD #601, Tooele, UT 84074. 801-882-7188, FAX 801-882-7195.

FOR SALE: HP 5326A 50MHz timer/counter/voltmeter \$285. **Hugh M. Adams**, 1011D Hondo Ave., Ft. Walton Beach, FL 32547. 904-864-2414.

HP 204B \$100; **HP 204C**, \$150; **HP 209A**, \$200; **HP 651A**, \$200; **HP 651B**, \$200; **HP 652A**, \$200; **HP 653A**, \$250; **HP 654A**, \$250. **Plotters:** HP 7475A six-pen RS 232, \$150; HP 7475A HP1B, \$250; HP 7470A, RS232, \$150; HP 7035B, XY \$200; HP 7044A, \$400; HP 7045A, \$400; HP 7046B, XY, \$600; HP 7550A graphics plotter, \$500; HP 7562A log converter, \$200; HP 7560A, \$150; HP 1725A, 275MHz scope and DVM, \$500; HP 1741A 100MHz storage scope, \$400; HP 302A wave ana., \$250. **A-Comm Electronics**, 303-290-8012.

SPECTRUM ANALYZERS: HP 8555A, 8552B, 141T (.01-18 GHz) \$1,600. **Tek 7L5/L3**, 20Hz-5MHz \$1,400; with tracking generator \$1,900. **HP 3580A** 5Hz-50KHz, 1Hz RBW, adaptive sweep, tracking generator \$790 (mech), \$1,250 (LED). Excellent condition, warranty. **Pepper Systems**, 214-353-0257.


WANT TO BUY HEWLETT-PACKARD and TEKTRONIX TEST EQUIPMENT. WILL PAY TOP DOLLAR. For used late model test instruments, call Dennis @ 408-749-9805, Fax 408-749-9806 <http://www.gpte.com>

HP 8640B signal generator .5 to 512MHz opt 323 still under calibration, \$395. 805-542-9574 leave mess.

Digital Storage Oscilloscopes

From \$189?

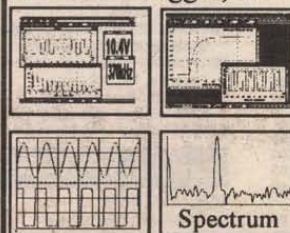ATC modules connect to your PC printer port and transform it into a full-function DSO, spectrum analyzer, logger, & DVM. Units DC to 25MHz



Captured Waveforms
Pico Tech
ADC-200 in
Windows

O-Scope II
in DOS




ATC proudly announces the addition of Pico Technology Ltd. products to our product line. Pico is based in Britain and offers a variety of data logging and virtual instrument modules.

O-Scope Ip (ST 50KHz).....\$189
O-Scope II (DT 500KHz).....\$349
ADC-100 (DT 12bit 50KHz).....\$449
ADC-200/20 (DT 10MHz).....\$699
ADC-200/50 (DT 25MHz).....\$925
Loggers 1-22 ch. (8-16 bit) from \$99
Shipping UPS \$7.50 grnd, \$11.50 (2 day)

800-980-9806
Allison Technology Corporation
8343 Carvel, Houston, TX 77036
Fax: 713-777-4746 Technical: 713-777-0401
BBS: 713-777-4753 email: atc@accesscomm.net
<http://www.atcweb.com>

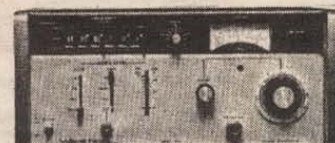LOGIC ANALYZERS: Fluke 9010 \$490 (includes docs and fancy case), pods \$90; Tek 1230 \$590, pods \$145; Global Specialties LTC-2 \$79. Synergetics Surplus, 3860 West First Street, Box 809, Thatcher, AZ 85552. 520-428-4073. synergetics@tina.ja.com VISA/MC.




WAVETEK 3001-691 RF synthesized generator, AM, FM, CW, & DC (for ± 500 KHz sweep), 1 to 512MHz, ± 13 to -13 DBM, six digits, .001% stability. \$745 (this month only). **Gary N6ZD**, 408-385-0301 VISA/MC.

SELL: TEKTRONIX PG508 generator, \$400; Tek P6046 differential probes \$250 ea.; HP 1335A XY display scopes \$250 ea.; Cohort Tropel 100 HeNe, laser, \$200; Fluke 5205A amplifier, \$1,000; chart recorders, HP 7155B, \$300; HP 7100BM, \$300; Brush Gould 222, \$400; HP 740A voltage std., \$200; Cushman CE-70 frequency selective level meter, \$300; HP 8405A vector voltmeter, \$500; Leitz Wetzlar microscope illuminator, \$200; Tektronix 2215 scope, \$450; GR1001A signal generator, \$200; GR1234 VSWR meter, \$150; HP 250B RX meter, \$300; HP 3586B selective level meter, \$800; Tektronix 335 portable scope, \$400. **A-Comm Electronics**, 303-290-8012 fax 303-290-8133. E-Mail: ACOMM@worldnet.att.net

TEKTRONIX: FG 504 40MHz function generator \$725. **A6302 & AM 503** current probe & amplifier \$850. **P6201 900MHz** active probe \$325. **AM 502, 7A22** high-sensitivity differential amplifiers \$375, \$350. **TR 503** tracking generator \$875. **7D20** digital storage plug-in \$700. **390AD** digitizer \$495. **5D10** waveform digitizer with readout \$295. **520A** NTSC vector scope \$1,150. Excellent condition, warranty. **Pepper Systems**, 214-353-0257.

ELECTRONIC COMPONENTS

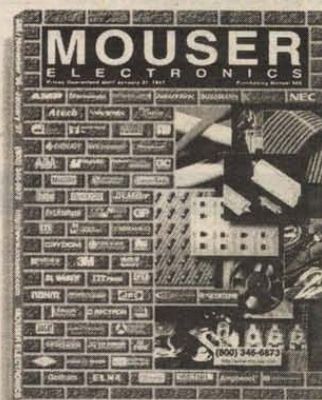

Call for your **FREE 332** page catalog **TODAY!**

- 68,138 Products
- 128 Manufacturers
- All Orders Ship Same Day
- No Minimum Order

800-992-9943
FAX: 817-483-0931

<http://www.mouser.com>
sales@mouser.com

MOUSER ELECTRONICS

658 North Main St., Mansfield, TX 76063

Write in 144 on Reader Service Card.



WE BUY AND SELL

Inquiries 303-438-9662 • Fax 303-438-9685

Orders only 800-538-1493

530 Compton St., Unit #C, Broomfield, Colorado 80020

OSCILLOSCOPES & ACCESSORIES

TO 100 MHz

TEK 2336YA 100 MHz Dual Trace Oscilloscope	\$1,000.00
TEK 7A18 75 MHz Dual Trace Amplifier	\$100.00
TEK 7A22 1 MHz High CMRR Differential Amplifier	\$300.00
TEK 7B53A 100 MHz Dual Time Base	\$175.00
TEK SC502 15 MHz Dual Trace Oscilloscope, TM500 series	\$375.00

ABOVE 100 MHz

TEK 475A 250 MHz Dual Trace Oscilloscope	\$1,000.00
TEK 7104 1 GHz Oscilloscope, with 7A29, 7A29-04, 7B10, 7B15	\$4,500.00
TEK 7844 400 MHz Dual Beam Oscilloscope frame	\$750.00
TEK 7844, 400 MHz Dual Beam Oscilloscope	\$1,250.00
with 7A24, 7A26, 7B80, 7B85	
TEK 7854 400 MHz Waveform Processing Oscilloscope frame	\$1,250.00
TEK 7904A 500 MHz System, with 7A24, 7A26, 7B92A	\$1,250.00
TEK 7904A, 500 MHz System, with 7A24, 7A26, 7B80, 7B85	\$1,250.00
TEK 7A13 105 MHz Differential Comparator	\$300.00
TEK 7A16A 225 MHz Single Trace Amplifier	\$125.00
TEK 7A19 600 MHz Single Trace Amplifier	\$175.00
TEK 7A19-opt.4 600 MHz Single Trace Amplifier, variable delay line	\$200.00
TEK 7A24 400 MHz Dual Trace Amplifier	\$350.00
TEK 7A26 200 MHz Dual Trace Amplifier	\$175.00
TEK 7A29 1 GHz Single Trace Amplifier	\$550.00
TEK 7A29-opt.04 1 GHz Single Trace Amplifier, variable delay line	\$650.00
TEK 7B15 1 GHz Delaying Time Base	\$450.00
TEK 7B80 400 MHz Delayed Time Base	\$175.00
TEK 7B85 400 MHz Delayed Time Base	\$200.00

STORAGE

TEK 7834 400 MHz Storage Oscilloscope	\$1,250.00
w/7A24, 7A26, 7B80, 7B85	
TEK SC503 10 MHz Dual Trace Storage Oscilloscope, TM500 series	\$700.00

SAMPLING

TEK R7903/7S11/7T11/S-4 12 GHz Sampling Oscilloscope System	\$1,750.00
TEK S-4 14 GHz Sampling Head	\$300.00

PROBES

TEK 1101 Accessory Power Supply, for FET probes	\$250.00
TEK P6046 100 MHz Differential Probe	\$750.00
TEK P6101A 34 MHz 1X Modular Probe, 2m length "NEW"	\$25.00
TEK P6108A 100 MHz 10X Modular Probe, 2m length "NEW"	\$50.00
TEK P6201 900 MHz 1X/10X/100X FET Probe	\$450.00
TEK P6202A 500 MHz 10X FET Probe	\$300.00
TEK P6203 10X 1 GHz Active Probe, for 11000 series	\$450.00
TEK P6701-opt.02 O/E Converter, 450-1050 nm/0.1 mW: DC-700 MHz, ST conn.	\$675.00

CALIBRATION

TEK CG5001-opt.01/TM5006 Programmable Oscilloscope Calibrator, with power module	\$7,000.00
TEK CG551AP/TM506A Oscilloscope Calibrator, with pulse head & power module	\$3,500.00

WAVEFORM GENERATORS

FUNCTION

HP 3310A 5 MHz Function Generator	\$325.00
HP 3310B 5 MHz Function Generator, monocyde & var.phase trigger	\$425.00
HP 3312A 13 MHz Function Generator, sweep, AM, FM	\$850.00
TEK DD501 Digital Delay & Burst Gen., for function & pulse gens	\$375.00
TEK FG501 1 MHz Function Generator, TM500 series	\$250.00
TEK FG502 11 MHz Function Generator, TM500 series	\$325.00
TEK FG503 3 MHz Function Generator, TM500 series	\$275.00
TEK FG504 40 MHz Function Generator, TM500 series	\$875.00
TEK RG501 Ramp Generator, TM500 series	\$225.00
WAVETEK 23 12 MHz Synthesized Function Generator	\$1,100.00

PULSE

HP 2148 10 MHz Pulse Generator, 50 V/50 Ohms, auto duty cycle	\$1,650.00
HP 2148-001 10 MHz Pulse Generator, 50 V/50 Ohms, counted burst opt	\$2,000.00
HP 8005B 20 MHz Dual Output Pulse Generator	\$450.00
HP 8007B 100 MHz Dual Output Pulse Generator, 3.5 nS fixed Tr	\$650.00
HP 8013B 50 MHz Dual Output Pulse Generator, 3.5 nS fixed Tr	\$600.00
HP 8015A 50 MHz Dual Output Pulse Generator	\$700.00
HP 8080A/81A/82A/83A 300 MHz Word Generator	\$600.00
HP 8080A/91A/92A/93A 1 GHz Single Channel Pulse Generator	\$950.00
HP 8080A/91A/93A 1 GHz Clock Generator	\$600.00
HP 8082A 250 MHz Dual Output Pulse Generator	\$1,400.00
PHILIPS PM5785B 125 MHz Dual Output Pulse Gen., burst mode, 1 nS Tr	\$875.00
TEK PG501 50 MHz Pulse Generator, TM500 series	\$250.00
TEK PG502 250 MHz Pulse Generator, Tr<1nS, TM500 series	\$700.00

PROGRAMMABLE

HP 3314A Multi-Waveform Generator, 0.001 Hz-19.99 MHz, HP1B	\$3,500.00
HP 3325A-002 Synth/Function Gen., 1 uHz-21 MHz, 40V out 1 uHz-1 MHz	\$2,400.00
HP 8160A 50 MHz Programmable Pulse Generator, HP1B	\$2,500.00
HP 8165A-002.003 Prog. Signal Source, 1 mHz-50 MHz, log sweep, rear out	\$2,000.00

TEK AWG5102 Arb. Waveform Gen., 20 MS/s, 12 bits, 50ppm synthesis <1MHz	\$1,400.00
TEK AWG5105 Arbitrary Waveform Generator, 50 MS/s, 12 bits	\$1,700.00
TEK AWG5105-opt.02 Arbitrary Waveform Generator, dual channel option	\$2,200.00
TEK FG5010 Programmable 20 MHz Function Generator, TM5000 series	\$1,200.00
TEK PFG505 Programmable 12 MHz Pulse/Function Generator	\$900.00
WAVETEK 288 20 MHz Synthesized Function Generator, GPIB	\$1,500.00

VOLTAGE & CURRENT

VOLTMETERS

HP 3456A 6-1/2 Digit Voltmeter	\$850.00
KEITHLEY 181 6-1/2 digit Nanovoltmeter, 10 nV sensitivity, GPIB	\$1,500.00
SOLARTRON 7081 8-1/2 digit Voltmeter	\$3,900.00
SOLARTRON 7150 5-1/2 digit Multimeter, GPIB	\$450.00

CALIBRATION

FLUKE 332BAF DC Voltage Calibrator, 0-1111 V, 0-50 mA, 7 decades	\$675.00
FLUKE 343A DC Voltage Calibrator, 0-1100 V, 7 decades, 20 ppm acc.	\$1,375.00
FLUKE 510A AC Reference Standard, 10 VRMS, 0-10 mA	\$450.00
FLUKE 515A Portable Calibrator, DC/AC/Ohms, line & battery power	\$1,500.00
FLUKE 5220A Transconductance Amplifier, DC-5 kHz, 0-20 A	\$3,750.00
FLUKE 720A Kelvin-Variety Voltage Divider, 7 decade	\$2,250.00
FLUKE 731B DC Reference Standard	\$400.00
FLUKE A55-series AC Thermal Converters	\$300.00

VOLTAGE SOURCES

HP 11049A AC Thermal Converter, 3 V, 20 Hz-100 MHz	\$175.00
VALHALLA 2703 AC Volt.Std., 0-120V/10 Hz-10 kHz; 120-1200V/10 Hz-1 kHz	\$2,500.00
HP 6114A Precision Dual Range Power Supply, 20 V 2 A / 40 V 1 A	\$875.00
HP 6115A Precision Dual Range Power Supply, 50V 0.8A / 100V 0.4A	\$875.00

CURRENT METERS & SOURCES

DRANETZ 656A (3)TR2019A Current Demand Analyzer, w/(3) current probes 300A max.	\$5,000.00
HP 6177C DC Current Source, to 50V, 500mA	\$600.00
HP 6181C DC Current Source, to 100 V, 250 mA	\$675.00
HP 6186C DC Current Source, to 300V, 100mA	\$750.00
KEITHLEY 414A Picoammeter, 0.1 nA-10 mA	\$325.00
KEITHLEY 486 Picoammeter	\$1,500.00
KEITHLEY 614 Electrometer	\$1,000.00
KEITHLEY 642 Electrometer	\$2,900.00
LEEDS & NORTHROP 4360 Precision Current Shunts, 15-500 Amp	\$650.00
TEK CT-5 opt.05 High Current Transformer for P6021/A6302, to 1000A	\$500.00
VALHALLA 2301 Programmable Single Phase Power Analyzer	\$1,250.00
VALHALLA 2575A AC/DC Active Current Shunt, 20 mA-100 A, DC-10 kHz	\$1,000.00

IMPEDANCE & COMPONENT TEST

L.C.R.

BOONTON 62AD 1 MHz Inductance Meter, 2-2000 uH	\$550.00
E.S.I. 296V 4-1/2 Digit LCR Bridge, 120 Hz & 1 kHz	\$700.00
HP 4261A 3-1/2 digit LCR Meter, 120 Hz/1 kHz	\$1,000.00
HP 4262A-101 4-1/2 digit LCR Meter, 120 Hz/1 kHz/10 kHz, HP1B	\$2,200.00

STANDARDS

E.S.I. RS-925 9-Decade Resistor, 0.01 ohm-1.2 Megohm	\$1,600.00
E.S.I. SR1010 Resistance Transfer Standards, 1 ohm-100 K/step	\$700.00
E.S.I. SR1050-10M Resistance Transfer Standard, 10 Megohms/step	\$3,000.00
FLUKE 5450A Programmable Resistance Standard, 2 & 4 wire	\$1,750.00
GR 1403-SERIES Standard Air Capacitors, 0.1% accuracy	\$150.00
GR 1406 Standard Air Capacitors, GR900 connector, 0.1% acc.	\$375.00
GR 1409-SERIES Standard Mica Capacitors, 0.05% accuracy	\$150.00
GR 1412-BC Decade Capacitor, 50 pF - 1.11115 uF	\$450.00
GR 1432-N-5-Decade Resistor, to 11,111 ohms, 0.1 ohm res.	\$175.00
GR 1432-U-4-Decade Resistor, 0-111.10 ohms, 0.01 ohm resolution	\$125.00
GR 1433-J-4-Decade Resistor, 0-1,110 ohms, 0.1 ohm resolution	\$350.00
GR 1433-L-4-Decade Resistor, 0-11,110 ohms, 1 ohm resolution	\$350.00
GR 1433-N-5-Decade Resistor, 0-11,111 ohms, 0.1 ohm resolution	\$400.00
GR 1433-Q-4-Decade Resistor, 0-1,111,000 ohm, 100 ohm resolution	\$350.00
GR 1433-U-4-Decade Resistor, 0-111.0 ohms, 0.01 ohm resolution	\$350.00
GR 1433-W-6-Decade Resistor, 0-11,111.0 ohms, 0.01 ohm resolution	\$450.00
GR 1433-X-6-Decade Resistor, to 111,111.0 ohms, 0.1 ohm res.	\$450.00
GR 1434-G-7-Decade Resistor, 0-1,111,111.0 ohms, 0.1 ohm res.	\$300.00
VALHALLA 2724A Programmable Resistance Standard, 0-11 Gigaohms, GPIB	\$1,675.00

HI & LO RESISTANCE

HP 4329A High Resistance Meter, 5E5-2E16 Ohms, 10-1000 V test	\$1,350.00
VALHALLA 4150-ATC 4-1/2 digit Ohmmeter, 20 milliohms-2 kilohms, 4-wire	\$1,000.00

CURVE TRACERS

TEK 576 Curve Tracer, with standard test fixture	\$2,350.00
TEK 577D1/177 Storage Curve Tracer, with standard test fixture	\$2,250.00
T.D.R.	
TEK 1502B-03.07 T.D.R., 0-2000 feet, chart recorder & battery options	\$4,750.00
TEK 1503-opt.04 Time Domain Reflectometer, 0-50,000 feet, chart recorder	\$1,600.00

POWER SUPPLIES

SINGLE OUTPUT

HP 6200B Dual Range Power Supply, 20 V 1.5 A / 40 V 0.75 A CV/CC	\$250.00
HP 6201B 20 V at 1.5A CV/CC Power Supply	\$200.00
HP 6206B Dual Range 0-60 V 0.5 A / 0-30 V 1 A CV/CL Supply	\$250.00
HP 6207B 160 V at 200 mA CV/CC Power Supply	\$300.00
HP 6209B 320 V at 100 mA CV/CC Power Supply	\$300.00
HP 6260B-027 10V at 100A CV/CC Power Supply	\$675.00
HP 6261B-027 20 V at 50 A CV/CC Power Supply	\$675.00
HP 6263B 20 V at 10 A CV/CC Power Supply	\$400.00
HP 6266B 40 V at 5 A CV/CC Power Supply	\$400.00
HP 6267B 40 V at 10 A CV/CC Power Supply	\$550.00
HP 6268B-027 40 V at 30 A CV/CC Power Supply	\$850.00
HP 6298A 100 V at 750 mA CV/CC Power Supply	\$250.00
HP 6384A 4.0-5.5 V at 8 A CV/CL Power Supply	\$175.00
HP/HARRISON 6443B 120 V at 2.5 A CV/CC Power Supply	\$400.00
LAMBDA LES-EE-03-OV 36 V at 14.5 A CV/CC Power Supply, LED metered	\$500.00
SOERENSON DCR 110-45T 110 V at 45 A CV/CC Power Supply	\$2,200.00
SOERENSON DCR 300-6B 300 V at 6 A CV/CC Power Supply, 120 VAC 30 A line	\$950.00
SOERENSON DCR 300-8A 300 V at 8 A CV/CC Power Supply, 208/230 VAC line	\$950.00
SOERENSON SRL 20-12 20 V at 12 A CV/CC Power Supply, low noise	\$550.00
SOERENSON SRL 60-8 60 V at 8 A CV/CC Power Supply, low noise	\$950.00

TEK PS501-1 Power Supply, 0-20 V, 2 mV res., 400 mA, TM500 series	\$175.00
---	----------

MULTIPLE OUTPUT

HP 6227B Dual 25 V at 2 A CV/CC Power Supply, tracking	\$550.00
HP 6253A Dual Output 20 V 3 A CV/CC Power Supply	\$500.00
HP 6255A Dual Output 40 V 1.5 A CV/CC Power Supply	\$500.00
TEK PS5010 Programmable Triple Power Supply, TM5000 series	\$800.00

MISCELLANEOUS

HP 59501A HP1B Isolated DAC/Power Supply Programmer	\$175.00
HP 6824A Bipolar Power Supply/Amplifier, to 50 V, 1 A	\$400.00
HP 6827A Bipolar Power Supply/Amplifier, to 100 V, 500 mA	\$800.00
KEPCO BOP 100-4M Bipolar Supply / Amplifier, 0-100 V, 0-4 A	\$1,000.00
TRANSISTOR DEVICES DAL-50-15-100 Programmable Load, 0-50 V, 0-15 A, 100 Watts max.	\$200.00

TIME & FREQUENCY

UNIVERSAL COUNTERS

HP 5315A-001 100 MHz/100 nS Universal Counter, TCXO reference	\$650.00
HP 5315A-001,003 100 MHz/100 nS Universal Counter, TCXO, 1 GHz C-channel	\$800.00
HP 5316A 100 MHz/100 nS Universal Counter, HP1B	\$750.00
HP 5316A-003,006 100 MHz/100 nS Counter, 1 GHz C-ch., offset/normalize	\$1,100.00
HP 5334A 100 MHz Universal Counter, HP1B	\$875.00
HP 5335A 200 MHz Universal / Statistical Counter	\$1,500.00
HP E1420A-010,030 VXI card 200 MHz/2 nS Univ. Counter, TCXO & 2.5 GHz C-ch	\$900.00
PHILIPS PM6654/056 12 Hz/2 nS Programmable High Res. Counter, OCXO, GPIB	\$850.00
RACAL-DANA 1992-04,55 100 MHz/1 nS Univ. Counter, 1.3 GHz C-channel, OCXO, GPIB	\$850.00
TEK DC5004 Programmable 100 MHz/100nS Counter/Timer, TM5000 series	\$350.00
TEK DC5009 Programmable 135 MHz Univ. Counter/Timer, TM5000 series	\$600.00
TEK DC5010 350 MHz/3.125 nS Univ. Counter, TM5000 series	\$1,000.00
TEK DC503A 125 MHz Universal Counter/Timer, TM5000 series	\$450.00

FREQUENCY COUNTERS

EIP 575 18 GHz Source Locking Counter, GPIB	\$3,250.00
FLUKE 7220A-opt.111 1.3 GHz Communications Counter, TCXO option	\$650.00
HP 5340A-001,011 18 GHz Frequency Counter	\$1,900.00
HP 5340A-005,011 23 GHz Frequency Counter, HP1B OCXO reference, HP1B	\$2,000.00
HP 5342A 18 GHz Frequency Counter	\$2,400.00
HP 5342A-003,011 18 GHz Freq. Counter, +22 dBm, -20 dBm dynamic range, HP1B	\$2,750.00



90 DAY WARRANTY PARTS AND LABOR • 10 DAY INSPECTION TEST EQUIPMENT WANTED CALL OR FAX LIST • OPEN ACCOUNTS



HP 5342A-01,04,05,11 24 GHz Frequency Counter, OCXO, DAC, and HP1B	\$3,900.00
HP 5345A/5355A/5356B 26.5 GHz CW/Pulse Frequency Counter	\$4,000.00
HP 5382A 225 MHz Frequency Counter	\$200.00
STANDARDS	
AUSTON 1250A Crystal Frequency Standard, 0.1/1.0/5.0 MHz	\$600.00
HP 105A Quartz Oscillator, 0.1/1.0/5.0 MHz	\$750.00
HP 5087A-031 Distribution Amp, 0.1/1.0/5.0 MHz x 4 channels each	\$1,250.00

AUDIO & BASEBAND

SPECTRUM ANALYZERS	
HP 8556A LF Section, 20 Hz-300 kHz	\$450.00
TEK 7L5-opt.025/L-31 Spectrum Analyzer, 20 Hz-5 MHz, 75/600/1M ohms	\$2,250.00
DISTORTION ANALYZERS	
HP 334A Distortion Analyzer, 5 Hz-600 kHz, -60 dB, auto nulling	\$550.00
HP 339A Distortion Analyzer, built-in low distortion osc.	\$2,400.00
TEK DA408A Programmable Distortion Analyzer, 0.0025% THD, w/frame	\$1,500.00
RMS VOLTMETERS	
FLUKE 8920A True RMS Voltmeter, 180 uV-700 V, 10 Hz-20 MHz	\$700.00
FLUKE 8921A True RMS Voltmeter, 180 uV-700 V, 2 Hz-2 MHz	\$700.00
OSCILLATORS	
FLUKE 6011A Synthesized Generator, 10 Hz-11 MHz, 10 Hz res.	\$1,200.00
HP 204D Oscillator, 5 Hz-1.2 MHz, 5 VRMS, 80 dB step attenuator	\$200.00
HP 209A Sine/Square Wave Generator, 4 Hz-2 MHz, 5 VRMS max.	\$225.00
HP 239A Low Distortion Oscillator, 10 Hz-100 kHz	\$450.00
HP 652A Test Oscillator, 10 Hz-10 MHz	\$300.00
ROCKLAND 5100 Synthesizer, 1 mHz-1.999999999 MHz	\$350.00
TEK SG502 Sine/Square Osc., 5 Hz-500 kHz, 70 dB step atten., TM500	\$350.00
TEK SG505-opt.01 Low Distortion Oscillator, 10 Hz-100 kHz, intermod. opt.	\$1,000.00
MISCELLANEOUS	
HP 3575A-01 Phase-Gain Meter, 1 Hz-13 MHz, dual display	\$900.00
HP 4437A Step Attenuator, 0-119.9 dB, DC-1 MHz, 600 ohms unbal.	\$200.00
KROHN-HITE 3103 High/Low Pass Filter, 10 Hz-3 MHz, 24 dB/octave	\$500.00
KROHN-HITE 3202 Dual High-Pass/Low-Pass Filter, 20 Hz-2 MHz, 24 dB/octave	\$600.00
KROHN-HITE 3342 Dual HP/LP Filter, 0.001 Hz-99.9 kHz, 48 dB/octave	\$1,100.00
KROHN-HITE 3750 LP/HP/BP/BR Filter, 0.02 Hz-20 kHz, 6/12/18/24 dB/octave	\$700.00
ROCKLAND 852 Dual Highpass/Lowpass Filter, 0.1 Hz-111 kHz	\$1,000.00
TEK AM502 Differential Amplifier, 0.1 Hz-1 MHz, TM500 series	\$575.00

RF & MICROWAVE

SPECTRUM ANALYZERS	
HP 11517A/18A/19A/20A Mixer, 12.4-40 GHz, w/adapters, for 8555A, 8565A, etc.	\$675.00
HP 11970A WR28 Harmonic Mixer, 26.5-40 GHz	\$1,100.00
HP 11970Q WR22 Harmonic Mixer, 33-50 GHz	\$1,400.00
HP 11970U WR19 Harmonic Mixer, 40-60 GHz	\$1,400.00
HP 11971A WR28 Harmonic Mixer, 26.5-40.0 GHz, for 8569B	\$1,100.00
HP 11971K WR42 Harmonic Mixer, 18.0-26.5 GHz, for 8569B	\$1,100.00
HP 8406A Comb Generator, 1/10/100 MHz increments, to 5 GHz	\$450.00
HP 8444A-059 Tracking Generator, 0.5-1500 MHz, for 8554, 8568, etc.	\$1,500.00
HP 8445B Preselector, 1.8-18.0 GHz, for HP 8555A	\$800.00
HP 8559A/853A Spectrum Analyzer, 10 MHz-21 GHz, 1 kHz res., w/display	\$5,500.00
HP 8565A-100 Spectrum Analyzer, 0.01-22 GHz, 100 Hz min. res. BW	\$5,500.00
TEK 7L13/7613 Spectrum Analyzer, 1 kHz-1.8 GHz, 30 Hz min. res., w/frame	\$2,250.00
TEK TR502 Tracking Generator, 0.1-1800 MHz, for 7L12/13/14	\$1,250.00
TEK TR503 Tracking Generator, 0.1-1800 MHz, for 4924/5/6	\$1,375.00
NETWORK ANALYZERS	
HP 11589A Bias Network, 0.1-3.0 GHz, N(f/f)	\$350.00
HP 11590A Bias Network, 1.0-12.4 GHz, N(f/f)	\$375.00
HP 11590A-01 Bias Network, 1.0-18.0 GHz, APC7	\$450.00
HP 11665B Modulator, 0.15-18.0 GHz, for use with 8755/6/7	\$375.00
HP 11666A Reflectometer Bridge, 0.04-18 GHz, for 8755/6/7	\$1,200.00
HP 8407A/8412A/8601A Network Analyzer, 100 kHz-110 MHz, with sweep generator	\$1,250.00
HP 85050D APC7 Calibration Kit, for 8510 series	\$1,100.00
HP 8505A-005/8503A Network An., 0.5-1300 MHz, w/S-Parameter & phase lock	\$5,000.00
HP 8755C(3)11664A/182T Scalar Network An. w/3 detectors, 10 MHz-18 GHz & frame	\$1,750.00
HP 8756A(3)11664A Scalar Network Analyzer, w/3 detectors, 0.01-18 GHz	\$3,750.00
NARDA 7000A/7202/7206 Microwave Multimeter System: scalar analysis 0.1-18 GHz	\$1,950.00
WAVETEK 1038D14A/H12/V13x2 Scalar Network An., w/3(1)5882 WR28 detectors, 26.5-40 GHz	\$2,200.00
WILTRON 640/G50/E(2)/7B50(2) Network An., w/1-1500 MHz source, (2) log amp, (2) det.	\$1,675.00

SIGNAL GENERATORS

FLUKE 6060AAN Synthesized Signal Gen., 10 kHz-520 MHz, 10 Hz res., GPIB	\$2,000.00
GIGATRONICS 600/10-18 Synthesized Source, 10-18 GHz, 1 MHz res., GPIB	\$2,600.00
GIGATRONICS 605/10-18 Synthesized Source, 10-18 GHz, 1 kHz res., GPIB	\$3,000.00
GIGATRONICS 875/50 Levelled Multiplier, x4, 50.0-75.0 GHz output, -3 dBm	\$3,500.00
GIGATRONICS 875/86 Levelled Multiplier, 26.5-40.0 & 50.0-75.0 GHz outputs	\$7,000.00
GIGATRONICS 910/12-18, opt.14, 16 Synthesized Source/Sweeper, 12-18 GHz, 1 Hz res., OCXO	\$3,500.00
HP 85100V Frequency Mult., 10-15 GHz in / 50-75 GHz out >0 dBm	\$4,250.00
HP 8616A Signal Generator, 1.8-4.5 GHz	\$450.00
HP 8640B-001,002,003 Signal Gen., 0.5-1024 MHz, AM, FM, var. audio osc.	\$2,500.00
HP 8654A Signal Generator, 10-520 MHz, calibrated AM & uncal. FM	\$550.00
HP 8656A Signal Generator, 0.1-990 MHz, 100 Hz res., AM, FM, HP1B	\$2,900.00
HP 8660C/86602B/86632A Synthesized Signal Gen., 1-1300 MHz, 1 Hz res., AM, FM	\$2,750.00
HP 8660D/86603A/86632B Synthesized Signal Generator, 1-2600 MHz	\$7,000.00
WAVETEK 907 Signal Generator, 7.0-11.0 GHz, 0 dBm levelled	\$1,000.00

SWEEP GENERATORS

HP 11869A Plug-In Adapter	\$450.00
HP 8350A/86290B-H08 Programmable Sweep System, 2.0-22.0 GHz, +4 dBm lvd	\$5,500.00
HP 8600A Digital Marker, for HP 8601A	\$400.00
HP 8601A Generator/Sweeper, 0.1-110 MHz, +20 dBm levelled	\$400.00
HP 8620C Sweep Oscillator Frame	\$550.00
HP 8620C-011 Sweep Oscillator Frame, HP1B programmable	\$675.00
HP 8622B-002 RF Plug-in, 10-2400 MHz, +10 dBm levelled, step atten.	\$1,750.00
HP 86230B RF Plug-in, 1.8-4.2 GHz, +10 dBm unlevelled	\$675.00
HP 86240A RF Plug-in, 2.0-8.4 GHz, +16 dBm levelled	\$1,000.00
HP 86240A-002 RF Plug-in, 2.0-8.4 GHz, +14 dBm lvd, 70 dB step atten.	\$1,200.00
HP 86241A-001 RF Plug-in, 3.2-6.5 GHz, +8 dBm levelled	\$500.00
HP 86242D-004,008 RF Plug-in, 5.9-9.0 GHz, +10 dBm levelled	\$500.00
HP 86245A RF Plug-in, 5.9-12.4 GHz, +16 dBm levelled	\$1,100.00
HP 86250D RF Plug-in, 8.0-12.4 GHz, +10 dBm levelled	\$675.00
HP 86260A RF Plug-in, 12.0-18.0 GHz, +10 dBm unlevelled	\$800.00
HP 86260A-H04 RF Plug-in, 10.0-15.0 GHz, +10 dBm unlevelled	\$800.00
HP 86290A RF Plug-in, 2.0-18.0 GHz, +7 dBm levelled	\$1,750.00
HP 86290C RF Plug-in, 2.0-18.6 GHz, +13 dBm levelled	\$2,500.00
WAVETEK 962 Sweep Generator, 1.0-4.0 GHz, markers, +12 dBm unlvld.	\$2,000.00

POWER METERS

ANRITSU MP-81B/ML-83A Power Meter, 75-110 GHz (WR10), -20 to +20 dBm	\$2,500.00
ANRITSU MP-82B/ML-83A Power Meter, 90-140 GHz (WR8), -20 to +20 dBm	\$3,250.00
BOONTON 42B/41-4E Analog Power Meter, with 1 MHz-18 GHz sensor	\$500.00
BOONTON 42B/42A-S3 Analog Power Meter, with 1 MHz-8.4 GHz N(f) sensor	\$375.00
GENERAL MICROWAVE 476/4240A Power Meter & Sensor, 0.01-18 GHz, -35 to +10 dBm	\$375.00
HP 432A/478A Power Meter, 10 MHz-10 GHz, -20 to +10 dBm f.s.	\$375.00
HP 432A/478B Power Meter, 10 MHz-18 GHz, -20 to +10 dBm f.s.	\$500.00
HP 432C Autoranging Digital Power Meter, 10 uW-10 mW f.s.	\$425.00
HP 435A/481A Power Meter, 10 MHz-18 GHz, -30 to +20 dBm	\$1,000.00
HP 435A/482A Power Meter, 100 kHz-4.2 GHz, -30 to +20 dBm	\$1,000.00
HP 435A/482B Power Meter, 0.1-4200 MHz, -15 to +34 dBm	\$1,150.00
HP K486A WR42 Thermistor Mount, 18.0-26.5 GHz, for 432 series	\$350.00
HP Q8486A Power Sensor, 33.0-50.0 GHz, WR22, for 435/6/7/8	\$1,500.00
HP R486A WR28 Thermistor Mount, 26.5-40.0 GHz, for 432 series	\$350.00

RF MILLIVOLTMETERS

RACAL 9303 TRMS Level Meter, 10 kHz-2 GHz, -77 to +23 dBm, GPIB	\$875.00
AMPLIFIERS, MISCELLANEOUS	
BOONTON 82AD FM/AM Modulation Meter, 10-1200 MHz	\$800.00
HP 8447A-001 Dual Amplifier, 0.1-400 MHz	\$450.00
HP 8901A-002,010 Modulation Analyzer, 150 kHz-1300 MHz, OCXO, int. cal.	\$5,500.00
M.P.D. LAB2-1020-2A Amplifier, 34 dB, 1.0-2.0 GHz, 2 Watts	\$800.00
M.P.D. LAB2-714-3A Amplifier, 34 dB, 0.7-1.4 GHz, 3 Watts	\$800.00
MARCONI TF2304 AM/FM Modulation Meter, 18-1000 MHz, FM dev. 1.5-150 Hz	\$500.00
MICROWAVE SEMI.CORP MC5112 Noise Source, 25.5 dB ENR, 1.0-12.4 GHz, N(m), +28 VDC	\$325.00

COAXIAL & WAVEGUIDE

AMERICAN NUCLEONICS AM-432 Cavity Backed Spiral Antenna, LHC, 2-18 GHz, TNC(f) "NEW"	\$95.00
CONTINENTAL MW.AT00L PLPT42 WR42 Low Power Termination, 18-26.5 GHz, 1 Watt	\$125.00
FXR/MICROLAB S3-02N Triple Stub Tuner, 200-1000 MHz, 100 Watts max., N(m/f)	\$90.00
GR 874-LTL Constant Impedance Trombone Line, 0-44 cm, DC-2 GHz	\$450.00
GR 900-Q GR900 14mm Interseries Adapters	\$125.00
HP 11691D Directional Coupler, 22 dB, 2-18 GHz	\$450.00
HP 11692D Dual Directional Coupler, 22 dB, 2-18 GHz	\$800.00
HP 776D Dual Directional Coupler, 20 dB, 940-1900 MHz	\$275.00
HP 777D Dual Directional Coupler, 20 dB, 1.9-4.1 GHz	\$275.00

HP 778D Dual Dir.Coupler, 20 dB, 100-2000 MHz, N(m/f/f/f)	\$550.00
HP 778D-011 Dual Dir.Coupler, 20 dB, 100-2000 MHz, APC7/N(f/f/f)	\$400.00
HP 8470B-012 Crystal Detector, 10 MHz-18 GHz, neg. pol., N(m)	\$250.00
HP K422A WR42 Flat Broadband Detector, 18.0-26.5 GHz	\$350.00
HP K532A WR42 Frequency Meter, 18.0-26.5 GHz	\$500.00
HP K752 A/C/D WR42 Directional Couplers, 3/10/20 dB, 18.0-26.5 GHz	\$450.00
HP K870A WR42 Slide Screw Tuner, 18.0-26.5 GHz	\$275.00
HP K914B WR42 Moving Load, 18.0-26.5 GHz	\$425.00
HP Q752D WR22 Directional Coupler, 20 dB, 33-50 GHz	\$650.00
HP R375A WR28 Variable Attenuator, 0-20 dB, 26.5-40 GHz	\$375.00
HP R422A WR28 Flat Broadband Detector, 26.5-40 GHz	\$400.00
HP R532A WR28 Frequency Meter, 26.5-40.0 GHz	\$500.00
HP R914B WR28 Moving Load, 26.5-40 GHz	\$300.00
HP X913A WR90 High Power Load, 500 Watts, 8.2-12.4 GHz	\$150.00
HUGHES 4511H-2000 WR28 Isolator, 25 dB, 26.5-40 GHz	\$450.00
HUGHES 4511H-1000 WR19 Isolator, 25 dB, 40-60 GHz	\$650.00
HUGHES 45514H-1001 WR15 Stepper Motor Driven 4-Port Switch, with driver	\$1,675.00
HUGHES 45521H-2000 WR28 Manual 4-Position Switch	\$750.00
HUGHES 45683H-1000 WR19 E-H Plane Tuner, 40-60 GHz	\$400.00
HUGHES 45713H-1000 WR19 Frequency Meter, 40-60 GHz	\$900.00
HUGHES 47316H-1111 WR10 Tuneable Detector, 75-110 GHz, positive polarity	\$750.00
HUGHES 47974H-1000 WR15 SPST PIN Switch, 250 MHz speed, 60-62 GHz response	\$375.00
MIA-COM 3-19-300/10 WR19 Directional Coupler, 10 dB, 40-60 GHz	\$450.00
NARDA 25171 Level Set Attenuator, 0-17 dB, 2-8 GHz, SMA(f)	\$100.00
NARDA 26298 20 dB Attenuator, 150 Watts, DC-1 GHz, N(f/f)	\$200.00
NARDA 3000-SERIES Directional Couplers	\$150.00
NARDA 3024 Bi-Directional Coupler, 20 dB, 4-8 GHz	\$300.00
NARDA 3090-SERIES Precision High Directivity Couplers	\$225.00
NARDA 369BNF High Power Termination, 175 Watts, 0.7-18 GHz, N(f)	\$325.00
NARDA 3753B Coaxial Phase Shifter, 0-60 deg./GHz, 3.5-12.4 GHz	\$1,250.00
NARDA 4000-SERIES SMA Miniature Directional Couplers	\$75.00
NARDA 4203-6 Directional Coupler, 6 dB, 2-18 GHz, SMA(f/f/f)	\$225.00
NARDA 4246B-20 Directional Coupler, 20 dB, 6-18 GHz, SMA(f)	\$100.00
NARDA 4317-2 Power Divider, 18.0-26.5 GHz, 3.5mm	\$175.00
NARDA 4799 Level Set Attenuator, 0-15 dB, 4-18 GHz, SMA(f)	\$135.00
NARDA 5070-SERIES Precision Reflectometer Couplers	\$300.00
NARDA 765-20 20 dB Attenuator, 50 Watts, DC-5 GHz, N(m/f)	\$135.00
NARDA 766-10 10 dB Attenuator, 20 Watts, DC-4 GHz, N(m/f)	\$100.00
NARDA 768-20 20 dB Attenuator, 20 Watts, DC-11 GHz, N(m/f)	\$125.00
NARDA 7922F Variable Attenuator, 0-20 dB, 2.0-12.4 GHz	\$375.00
PAMTECH KYG1014 WR42 Junction Circulator, 18.0-26.5 GHz	\$250.00
SOMATE SCIENTIFIC 21A3 WR42 Circulator, 20 dB, 20.6-24.8 GHz	\$125.00
SPACE LABS DQ-1 WR22 Flat Broadband Detector, 33-50 GHz	\$550.00
TELEONIC TTF-2250-5-SEE Tuneable Bandpass Filter, 1.5-3.0 GHz, 5% 3 dB BW, N(f)	\$350.00
TRG V510 WR15 Precision Rotary Vane Atten., 0-50 dB, 50-75 GHz	\$1,000.00
TRG V551 WR15 Frequency Meter, 50-75 GHz	\$600.00
TRG V559-10 WR15 Directional Coupler, 10 dB, 50-75 GHz	\$400.00
TRG V510 WR10 Precision Rotary Vane Atten., 0-50 dB, 75-110 GHz	\$1,000.00
TRG V559-10 WR10 Directional Coupler, 10 dB, 75-110 GHz	\$475.00
WAVELINE 822 WR42 Precision Rotary Vane Atten., 0-50 dB, 18-26.5 GHz	\$1,250.00
WAVELINE 898-DR WR42 Frequency Meter, 18.0-26.5 GHz	\$350.00
WEINSCHEL 49-6-34 dB Attenuator, 150 Watts, DC-8 GHz, N(f/m)	\$250.00
WILTRON 26N50 Precision Termination, N(m), DC-18 GHz	\$250.00
WILTRON 87A50 VSWR Bridge, 2-18 GHz, 35 dB dir., APC7 test port	\$600.00

LOGIC

FLUKE 9000A-series Microprocessor Pods: 6800; 6809; 8080; 8085; Z80	\$375.00
HP 5005A Signature Multimeter	\$350.00
HP 8170A-002 Logic Pattern Generator, 2 MB/s, address driver option	\$1,200.00
TEK 1240 Logic Analyzer, w/36(3) 50 MHz channels	\$1,500.00

COMMUNICATIONS

HP 4972A/18182A LAN Protocol Analyzer, with software	\$2,500.00
HP 59401A HP1B Bus Analyzer	\$700.00
TEK 1411R-opt.04 PAL Test Gen. w/SPG12, TSG11, TSP11, TSG13, TSG15, TSG16	\$2,750.00
TEK 147A NTSC Signal Generator, with noise test signal	\$800.00
TEK 520A NTSC Vectorscope	\$1,200.00
HP 3787B-001 Digital Data Test Set, T1/DDS/56Kb/Packet, DS1 jitter	\$2,750.00

MISCELLANEOUS

P.A.R. 5205-94,95,96,98 Lock-In Amp. 20 Hz-20 kHz, int. osc., lin/freq, GPIB	\$2,750.00
P.A.R. 5206 Two-Phase Lock-In Amplifier, 2 Hz-200 kHz	\$2,500.00
P.A.R. 5208-92,94,97,98 Two Phase Lock-In Amp., GPIB 5 Hz-20 kHz or 200 kHz	\$3,250.00
TEK TM5006 5000-series 6-slot Programmable Power Module	\$600.00
TEK TM503 500-series 3-slot Power Module	\$175.00
TEK TM504 500-series 4-slot Power Module	\$175.00
TEK TM506 500-series 6-slot Power Module	\$250.00
TEK TM515 500-series 5-slot Traveller Power Module	\$275.00

New Product

Our readers are always looking for new and interesting electronic items. Showcase your NEW PRODUCTS here to help stimulate your product's success. Submit all news releases, product information, and/or photos to:

NUTS & VOLTS MAGAZINE
NEW PRODUCT EDITOR,
430 PRINCELAND CT., CORONA, CA 91719

News

EQUIPMENT FILTER/SUPPRESSOR



Electronic Specialists announces upgraded wide-band interference filter/suppressors. Designed for OEM, laboratory, and experimental use, these filters now provide interference attenuation from 10 KHz to 250 MHz and 58,500 surge amp spike suppression. Response time of the suppressor is one pico-second. Bilateral design also prevents transmission of locally generated interference out to the power mains.

Units are available in commercial, industrial, and laboratory grades, reflecting differing filter levels to accommodate local interference severity. 3, 10, 15, 20, and 30 amp models are available. Terminal options include solder lug, push-on tabs, screw terminals, or wire leads. List prices start at \$45.00.

For more information, contact:

ELECTRONIC SPECIALISTS, INC.
171 S. MAIN ST., DEPT. NV
NATICK, MA 01760
1-800-225-4876
FAX: 508-653-0268

SERIAL DATA ACQUISITION & INSTRUMENT CONTROL

The Software Wedge™, from TAL Technologies, Inc., adds serial data acquisition and instrument control to Excel, Lotus, Access, VB, HMI's, statistical, and control software. It automatically collects data from PLCs, data loggers, sensors, quality, and process control instruments, flow meters, electronic balances, gauges, analyzers, bar code readers, telephone systems, modems... any serial device.

In addition to data acquisition,

the Software Wedge lets you completely control your instruments directly from the Software Wedge or from within any application program. It also has powerful DDE support in Windows allowing you to easily create sophisticated data collection and device control interfaces.

For more information, contact:

TAL TECHNOLOGIES, INC.
2027 WALLACE ST., DEPT. NV
PHILADELPHIA, PA 19130
215-763-7900 FAX: 215-763-9711
1-800-722-6004
<http://www.taltech.com>
E-MAIL: tal1@taltech.com

POLAROID MACRO CAMERA



The TMT-P619758 features the five-in-one close-up system with a unique light focusing feature that lets you document your work instantly in color. Ideal for medical imaging for teaching and communication visuals, in a manufacturing environment as a tool for quality control, and quality assurance.

For more information, contact:

TIME MOTION TOOLS
12778 BROOKPRINTER PL.
DEPT. NV
POWAY, CA 92064
1-800-779-8170
FAX: 1-800-779-8171
<http://www.timemotion.com>
E-MAIL: Time@Connectnet.com

CODE ROTATOR


The Code Rotator is the latest in security for the garage door. This new high-tech device protects from code grabbing and scanning. It is completely universal and will work on any garage door operator. It offers 70 billion randomly rotating

codes to give the highest level of security.

For more information, contact:

STREET SMART SECURITY
7147 UNIVERSITY AVE.
DEPT. NV
LA MESA, CA 91941
1-800-908-4737

RADIO MONITORING: THE HOW-TO GUIDE

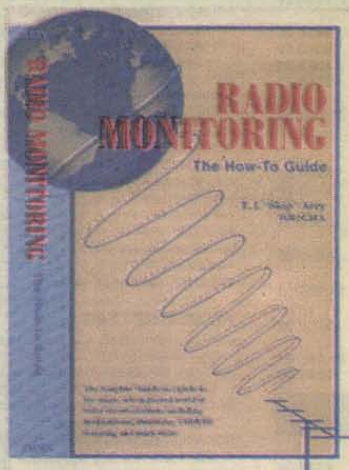

Radio Monitoring: The How-To Guide takes you to a fascinating world of action, adventure, intrigue, and awareness — and you never have to leave your armchair. This is the curious person's guide to discovery of the world in new and exciting ways. Here you'll learn how to capture radio signals from down the street, across town, around the world, and even from space, and become informed far beyond the content of TV and radio.

For more information, contact:

INDEX PUBLISHING GROUP, INC.
3368 GOVERNOR DR. STE. 273
DEPT. NV
SAN DIEGO, CA 92122
1-800-546-6707
619-455-6100 FAX: 610-552-9050
E-MAIL: ipgbooks@indexbooks.com
WEBSITE: www.electricti.com/~ipgbooks

GLOBAL PHONE

Repair technicians, field engineers, and traveling business


people no longer have to be in the office to link up with colleagues for video conference discussion. Instead, they can dial them up while on the road or in the field using portable, notebook computers equipped for video conferencing.

Using Global Phone 1.5 version software, a video camera and a slide-in PCMCIA video capture card, people can use laptops to show a construction site, a crime or accident scene, or close-ups of metal fatigue symptoms. VIC Hi-Tech Corporation sells the credit-card sized PCMCIA card and portable camera as add-on options for its Global Phone video conferencing software. The only additional equipment that users require are a portable battery pack, a modem-equipped laptop, and a cellular phone card, cellular phone, or pay phone connection.

For more information contact:

VIC HI-TECH CORP.
2221 ROSECRANS AVE. STE. 237
DEPT. NV
EL SEGUNDO, CA 90245
310-643-5193
<http://www.vic-corp.com>

THREE-AXIS STEPPER CONTROLLER KIT

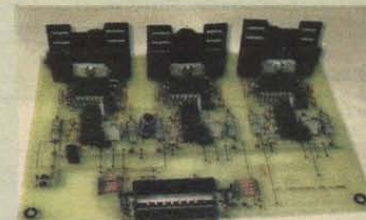

This three-axis controller kit together with included software will drive stepper motors in the full or half step modes at currents two amps per phase. The chopper frequency is 18.4 KHz and has jumper selectable phase or control chopping. An all winding off feature allows disabling the motor windings while the electronic position is maintained. Great for development, CNC, and robotic applications. The kit retails for \$145.00.

For further information, contact:

CAMTRONICS, INC.
18230 130TH PL. N.E., DEPT. NV
BOTHELL, WA 98011-3118
206-487-0013

KEYAT KEYBOARD PORT ADAPTER



L3 Systems announces the release of the Keyat keyboard port adapter. This new device allows

Continued on page 102

Events

CALENDAR

JANUARY 1997

JANUARY 3-4-5

IL - PEORIA - Computer Sale/Show. Peoria Civic Center. Blue Star Productions 612-788-1901

JANUARY 4

CA - OXNARD - Computer Show & Sale. Community Center. MarketPro 1-800-708-7555
CA - SACRAMENTO - Computer Show & Sale. Scottish Rite Center. MarketPro 1-800-708-7555
CA - SANTEE - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-In 619-561-0052
KY - LEXINGTON - Computer Show. Continental Inn. MarketPro 301-984-0880 xt15
MD - BALTIMORE - Computer Show. Martins West. MarketPro 301-984-0880 xt15
MI - LIVONIA - Super Computer Sales. Livonia Elks Lodge Hall, 31117 Plymouth Rd. 10am-3pm. Computers and You 313-283-1754
NH - PORTSMOUTH - Computer Show. Frank Jones Center. 10am-3:30pm. Northern Computer Shows 508-744-8440
PA - PHILADELPHIA - Computer Show. Adams Mark. MarketPro 301-984-0880 xt15
TX - MORRISTOWN - Hamfest. Lakeway ARC. Perry Hensley 423-828-4848

JANUARY 4-5

FL - CAPE CORAL - Hamfest. FL Myers ARC. Jackie Kampfert 941-542-6675
FL - TAMPA - Computer Show. FL State Fgnds. MarketPro 301-984-0880 xt15
PA - MONROEVILLE - Computer Show. Pittsburgh Expo Mart. MarketPro 301-984-0880 xt15
VA - CHANTILLY - Computer Show. Capital Expo Center. MarketPro 301-984-0880 xt15
VA - HAMPTON - Computer Show. Hampton Coliseum. MarketPro 301-984-0880 xt15

JANUARY 5

CA - LIVERMORE - Swapmeet. Las Positas College. Noel Anklam 510-447-3857
CA - SAN DIEGO - Computer Show & Sale. Scottish Rite Center. MarketPro 1-800-708-7555
CA - STOCKTON - Computer Show & Sale. Civic Auditorium. MarketPro 1-800-708-7555
GA - NORCROSS - Computer Show. Northeast Atlanta Hilton, 5993 Peachtree Industrial Blvd. Narissam Computer Shows 770-663-0983
IN - SOUTH BEND - Hamfest. Michiana Valley Hamfest Assn. Bob Denniston 219-291-0252
KY - FRANKFORT - Computer Show. Farnham Dudgeon Civic Center. MarketPro 301-984-0880 xt15
MD - TOWSON - Computer Show. Towson State University. MarketPro 301-984-0880 xt15
MI - GRAND RAPIDS - Super Computer Sales. Stadium Arena, 2500 Turner Ave. NW. 10am-4pm. Computers and You 313-283-1754
NJ - CHERRY HILL - Computer Show. Hilton at Cherry Hill. MarketPro 301-984-0880 xt15
PA - DICKSON CITY - Computer Show. Genetti Manor. MarketPro 301-984-0880 xt15
PA - MONROEVILLE - Computer Show. Pittsburgh Expo Mart. MarketPro 301-984-0880 xt15

JANUARY 10-11-12

WI - LA CROSSE - Computer Sale/Show. La Crosse Center. Blue Star Productions 612-788-1901

JANUARY 11

AZ - GLENDALE - Hamfest. Glendale Community College N. Lot. 6000 W. Olive. 6am-1pm. Mark

The Events Calendar is a free service limited to electronic events such as computer shows, hamfests, flea markets, etc. If your organization is sponsoring an event and would like a free listing, contact us at least 60 days prior to the event. Include your flyer, estimated attendance, name of the person to contact, and phone number.

Complimentary issues are available upon request for distribution to your attendees. A street address for UPS is required.

While we strive for accuracy in our calendar, we can not be responsible for errors or cancellations. The information contained in this column is for the use of the readers of *Nuts & Volts* and may not be republished in any form without the written permission of T & L Publications, Inc.

All listing information should be sent to:

Nuts & Volts Magazine

Events Calendar

430 Princland Court

Corona, CA 91719

Phone 909-371-8497

Fax 909-371-3052

E-mail events@nutsvolts.com

KC7BXS 602-931-1204

CA - FONTANA - Inland Empire ARC Amateur Radio & Electronics Swapmeet. A B Miller High School. Bill 909-822-4138 eves

CA - FRESNO - Computer Show & Sale. Fresno Fairgrounds. MarketPro 1-800-708-7555

CO - LOVELAND - Superfest. Larimer County Fgnds. 700 Railroad Ave. 9am-3pm. 970-352-5304

FL - FORT LAUDERDALE - Computer Show. The Westin Hotel, 400 Corporate Dr. Narissam Computer Shows 770-663-0983

MI - KALAMAZOO - Super Computer Sales. Kalamazoo County Fairground, 2900 Lake St. 10am-3pm. Computers and You 313-283-1754

NY - MARATHON - Hamfest. Skyline ARC. Barbara Mudge 607-849-6751

TX - SAN ANTONIO - Hamfest. San Antonio RC. Eric Smith 210-684-2513

VA - ANNANDALE - Computer Show. N. Virginia Community College. MarketPro 301-984-0880 xt15

JANUARY 11-12

FL - JACKSONVILLE - Computer Show Jacksonville Fairgrounds. MarketPro 301-984-0880 xt15

FL - SARASOTA - Hamfest. Sarasota ARA. Fred Auerbach 941-365-7679

GA - NORCROSS - Computer Show. North Atlantic Trade Center. MarketPro 301-984-0880 xt15

KY - LOUISVILLE - Computer Show. Commonwealth Convention Ctr. MarketPro 301-984-0880 xt15

OH - BEREA - Computer Show. Cuyahoga County Fairgrounds. MarketPro 301-984-0880 xt15

PA - ALLENTOWN - Computer Show. Allentown Fairgrounds. MarketPro 301-984-0880 xt15

JANUARY 12

AZ - PHOENIX - Computer Show & Sale. Shrine Auditorium. 10am-5pm. MarketPro 1-800-708-7555

CA - LANCASTER - Computer Show & Sale. Antelope Valley Fairgrounds. 10am-5pm. MarketPro 1-800-708-7555

CA - SANTA ROSA - Computer Show & Sale. Sonoma Co. Fairgrounds. 10am-5pm. MarketPro 1-800-708-7555

FL - WEST PALM BEACH - Computer Show. Palm Beach Airport Hilton, 150 Australian Ave. Narissam Computer Shows 770-663-0983

MD - NEW CARROLLTON - Computer Show. Ramada Conf. & Exhibition Ctr. MarketPro

301-984-0880 xt15

MI - SOUTHGATE - Super Computer Sales. Crystal Gardens, 16703 Fort St. 10am-4pm. Computers and You 313-283-1754

WI - WAUKESHA - Hamfest. West Allis RAC. Phil Gural 414-425-3649

JANUARY 18

CA - BAKERSFIELD - Computer Show & Sale. Kern Co. Fairgrounds. MarketPro 1-800-708-7555

CA - SANTEE - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-In. 619-561-0052

FL - CRYSTAL RIVER - Hamfest. Sky High ARC. Chad Johnson 352-746-1299

LA - HAMMOND - ARRL Hamfest. Southeast Louisiana ARC. Jack Stang 504-542-7605

MD - FREDERICK - Computer Show. Frederick Fairgrounds. MarketPro 301-984-0880 xt15

MI - DEARBORN - Super Computer Sales. Dearborn Civic Center, 15801 Michigan Ave. 10am-3pm. Computers and You 313-283-1754

MI - FLINT - Hamfest. Southwestern Academy. 8am-2pm. Keith Allen N8QNA 810-232-5170

MO - ST. JOSEPH - Hamfest. Ramada Inn. Missouri Valley ARC. I-29 & Frederick Ave. 9am-4pm. 816-424-6484

NH - NASHUA - Electronic Fleamart. 617-923-2665

NH - SALEM - Computer Show. Rockingham Park Race Track. 10am-3:30pm. Northern Computer Shows 508-744-8440

OH - MIDDLETOWN - Hamfest. SW Ohio Digital Symposium. Hank Greeb 513-385-8363

PA - LEBANON - Computer Show. Lebanon Valley Expo Center. MarketPro 301-984-0880 xt15

VA - RICHMOND - Computer Show. The Showplace. MarketPro 301-984-0880 xt15

JANUARY 18-19

CA - VALLEJO - Computer Show & Sale. Solano Co. Fairgrounds. MarketPro 1-800-708-7555

OH - DAYTON - Computer Fair. Dayton Convention Center. Trade Show Productions 513-263-3378

OH - DAYTON - Computer Show. Montgomery County Fairgrounds. MarketPro 301-984-0880 xt15


VA - NORFOLK - Computer Show. Norfolk Scope. MarketPro 301-984-0880 xt15

JANUARY 19

CA - SAN DIEGO - Computer Show & Sale. Scottish Rite Center. 10am-5pm. MarketPro 1-800-708-7555

Model PTS-10

\$55

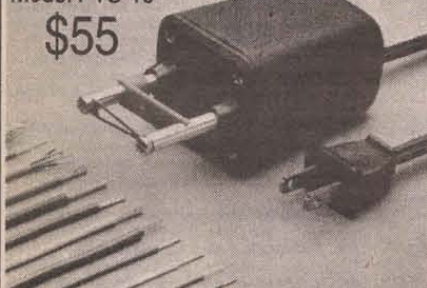

LIFETIME WIRE STRIPPER, a breakthrough in wire stripping technology. Extremely fast tool will strip PVC insulation #14 to #30 AWG from solid, stranded or shielded wires. High quality strip is achieved by patented stripping element (.008" thick) which thermally cuts the insulation all the way to the conductor without nicks. Five year test, with over 2 million stripped wires, using the same element, speaks for itself. The stripper has won a —

"FIVE STAR PRODUCT OF THE MONTH"

award in DESIGNFAX magazine. Strippers for TFE, KAPTON, KYNAR, SILICONE RUBBER, etc. and rechargeable, battery powered strippers also available.

PATCO Service, Inc., 2515 Glencoe Rd., Baltimore, MD 21234

(410) 444-4010 Fax (410) 254-9566

Write in 41 on Reader Service Card.



E.H. Yost & Co. - YOUR SOURCE FOR



BATTERIES!

★ AMATEUR / COMMERCIAL / AVIATION RADIO ★

★ LAPTOP COMPUTERS ★ VIDEO CAMCORDERS ★

★ CELLULAR & CORDLESS TELEPHONES ★

★ SEALED LEAD ACID ★ PHOTOGRAPHY ★

★ MEDICAL EQUIPMENT ★ TESTING EQUIPMENT ★

CALL OR WRITE TODAY FOR OUR FREE CATALOG!

Phone (608) 831-3443 / Fax (608) 831-1082

E.H. Yost & Company 2211-D Parview Rd., Middleton, WI 53562

❖ ATTENTION CABLE VIEWERS ❖

CABLE VIEWERS... get back to your **BASIC** Cable Needs



**BASIC
ELECTRICAL
SUPPLY &
WAREHOUSING
CORPORATION**

Call 1-800-577-8775

For information regarding all of your **BASIC** cable needs.

5 GOOD REASONS TO BUY OUR FAR SUPERIOR PRODUCT

- ❖ **PRICE**
- ❖ **EFFICIENT SALES AND SERVICE**
- ❖ **WE SPECIALIZE IN 5, 10 LOT PRICING**
- ❖ **ALL FUNCTIONS (COMPATIBLE WITH ALL MAJOR BRANDS)**
- ❖ **ANY SIZE ORDER FILLED WITH SAME DAY SHIPPING**

We handle **NEW** equipment **ONLY** - Don't trust last years **OBSOLETE** and **UNSOLD** stock!
COMPETITIVE PRICING — DEALERS WELCOME

It is not the intent of B.E.S.W. to defraud any pay television operator and we will not assist any company or individual in doing the same.
*Refer to sales personnel for specifications.

P.O. BOX 8180 • BARTLETT, IL 60103-8180 • 847-584-2099

Write in 142 on Reader Service Card.

Events CALENDAR

Tom Ellis 505-291-8122

PA - YORK - Computer Show. Holiday Inn Holldome & Conference Center. MarketPro 301-984-0880 xt15
TN - GALLATIN - Hamfest & Computer Show. Gallatin Civic Center off Hwy 31E. 8am-2pm. Bill Ferrell 615-230-7923

VA - HARRISONBURG - Computer Show. Rockingham Co. Fgnds. MarketPro 301-984-0880 xt15

JANUARY 25-26

CA - SACRAMENTO - Computer Show & Sale. Cal Expo. MarketPro 1-800-708-7555

CA - VENTURA - Computer Show & Sale. Ventura Fairgrounds. MarketPro 1-800-708-7555

FL - ORLANDO - Computer Show. Central FL Fairgrounds, Bldg. B. MarketPro 301-984-0880 xt15

MD - GAITHERSBURG - Computer Show. Montgomery Co. Fairgrounds. MarketPro 301-984-0880 xt15

OH - CINCINNATI - Computer Show. Cincinnati Gardens. MarketPro 301-984-0880 xt15

JANUARY 26

CA - SANTA ANA - Swapmeet. ACP Parking Lot. Mary Russo 714-558-8813

IL - VILLA PARK - Hamfest. WCRA. 630-545-9950

IN - FT. WAYNE - Computer Fair. Ramada Hotel, off I-69 exit 105A. 10am-3pm. AGI Services 317-299-8827

IN - SOUTH BEND - Computer Show. Century Center. MarketPro 301-984-0880 xt15

MD - ODENTON - Hamfest. Maryland Mobiles ARC. Jim Botluk 410-280-9815

MI - MADISON HEIGHTS - Super Computer Sales. UF & CW Hall, 876 Horace Brown Dr. 10am-4pm. Computers and You 313-283-1754

MI - MIDLAND - Computer Show. Holiday Inn. US-10 @ Eastman Rd. Exit. Five Star Productions. 810-230-0988

NH - NASHUA - Computer Show. Sheraton Tara Hotel. 10am-3:30pm. Northern Computer Shows 508-744-8440

OH - DOVER - Hamfest. Ohio National Guard Armory. 2800 N. Wooster Ave. Howard Blind 330-364-5258

PA - WILKES BARRE - Computer Show. Genetti's Best Western. MarketPro 301-984-0880 xt15

VA - RICHMOND - Computer Show. VA Sports Arena. MarketPro 301-984-0880 xt15

JANUARY 28

CA - SACRAMENTO - Computer Show & Sale. Cal Expo. MarketPro 1-800-708-7555

CA - VENTURA - Computer Show & Sale. Ventura Fairgrounds. MarketPro 1-800-708-7555

FL - ORLANDO - Computer Show. Central FL Fairgrounds, Bldg. B. MarketPro 301-984-0880 xt15

MD - GAITHERSBURG - Computer Show. Montgomery Co. Fairgrounds. MarketPro 301-984-0880 xt15

OH - CINCINNATI - Computer Show. Cincinnati Gardens. MarketPro 301-984-0880 xt15

MD - ODENTON - Swapfest. Odenton Vol. Fire Dept. Hall, 1425 Annapolis Rd. 8am-2pm. Bill Ziegler 410-987-2384

JANUARY 31-FEBRUARY 1-2

MI - ROCHESTER - Computer Sale/Show. Mayo Civic Center. Blue Star Productions 612-788-1901

FEBRUARY 1997

FEBRUARY 1

CA - FRESNO - Computer Show & Sale. Fresno Fairgrounds. MarketPro 1-800-708-7555

CA - SANTEE - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in 619-561-0052

MA - HYANNIS - Computer Show. Tara Cape Codder Hotel. 10am-3:30pm. Northern Computer Shows 508-744-8440

TX - AMARILLO - Hamfest. Potter Cty. ARES. Ben Pollard 806-381-8810

FEBRUARY 1-2

FL - MIAMI - Tropical Hamboree. Dade Radio Club. Youth Fair & Exposition Center. 10901 SW 24th St. Sat. 9am-5pm. Sun. 9am-4pm. 305-642-4139

MD - NEW CAROLLTON - Computer Show. Ramada Conference & Exhibition Center. MarketPro 301-984-0880 xt15

MD - PIKESVILLE - Computer Show. Pikesville Armory. MarketPro 301-984-0880 xt15

MO - ST. CHARLES - Computer Show. St. Charles Exposition Hall. St. Charles Ctr. I-70 & 5th St. Sat. 10am-4pm. Sun. 11am-3pm. Computer Central Shows 888-296-6066

MS - JACKSON - State Convention. Travis Cliett 601-939-9236

OH - COLUMBUS - Computer Show. Ohio Exposition Center. MarketPro 301-984-0880 xt15

PA - GREENSBURG - Computer Show. Greengate Expo Center. MarketPro 301-984-0880 xt15

VA - CHANTILLY - Computer Show. Capital Expo Center. MarketPro 301-984-0880 xt15

FEBRUARY 2

CA - LIVERMORE - Swapmeet. Las Positas College. Noel Ankiam 510-447-3857

CA - OXNARD - Computer Show & Sale. Community Center. 10am-5pm. MarketPro 1-800-708-7555

CA - STOCKTON - Computer Show & Sale. Civic Auditorium. 10am-5pm. MarketPro 1-800-708-7555

MA - BRAINTREE - Computer Show. Sheraton Tara Hotel. 10am-3:30pm. Northern Computer Shows 508-744-8440

FEBRUARY 7-8-9

WI - MADISON - Computer Sale/Show. Dane Co. Expo Center. Blue Star Productions 612-788-1901

FEBRUARY 8

CA - FONTANA - Inland Empire ARC Amateur Radio & Electronics Swapmeet. A B Miller High School. Bill 909-822-4138 eves

FL - ARCADIA - Hamfest. Doug Christ 941-494-5070

FL - FORT LAUDERDALE - Computer Show. The Westin Hotel, 400 Corporate Dr. Narissam Computer Shows 770-663-0983

FL - MILTON - Hamfest. Mark McAnally 904-626-7686

KS - LACYGNE - ARRL Hamfest. Mine Creek ARC. Bill VanKirk 913-795-2080

MN - BLAINE - Midwinter Madness. National Sports Center, Exit #32 off 35 W. N. of Minneapolis/St. Paul. 8am-3pm. RARC 612-537-1722

SC - CHARLESTON - Hamfest & Computer Show. Stall H.S. in N. Charleston. I-26 & Ashley Phosphate Rd. Northwoods Mall, Waccamaw. Jenny Myers 803-747-2324

FEBRUARY 8-9

FL - JACKSONVILLE - Computer Show. Jacksonville Fairgrounds. MarketPro 301-984-0880 xt15

MD - NEW CAROLLTON - Computer Show. Ramada Conference & Exhibition Center. MarketPro 301-984-0880 xt15

PA - KING OF PRUSSIA - Computer Show. Valley Forge Convention Ctr. MarketPro 301-984-0880 xt15

TN - NASHVILLE - Computer Show. Nashville Armory. MarketPro 301-984-0880 xt15

VA - CHANTILLY - Computer Show. Capital Expo Center. MarketPro 301-984-0880 xt15

WV - CHARLESTON - Computer Show. Convention Center. MarketPro 301-984-0880 xt15

FEBRUARY 9

CA - LANCASTER - Computer Show & Sale. Antelope Valley Fairgrounds. 10am-5pm. MarketPro 1-800-708-7555

CA - SANTA ROSA - Computer Show & Sale. Sonoma Co. Fairgrounds. 10am-5pm. MarketPro 1-800-708-7555

FL - WEST PALM BEACH - Computer Show. Palm Beach Airport Hilton, 150 Australian Ave. Narissam Computer Shows 770-663-0983

OH - MANSFIELD - Hamfest & Computer Show. Richland Co. Fgnds. 7am. Pat Ackerman N8YOB. 419-589-7133

PA - LATROBE - Hamfest. Chestnut Ridge ARC. 1811 Ligonier St. 8am-3pm. Bill Demosky 412-539-1552

FEBRUARY 14-15-16

FL - ORLANDO - HamCation & Computer Show. Central FL Fgnds., 4603 W. Colonial Dr. St. Rd. 50. Fri. 5pm-9pm, Sat. 9am-5pm, Sun. 9am-3pm. 407-823-7133

FEBRUARY 15

CA - BAKERSFIELD - Computer Show. Kern Co. Fairgrounds. MarketPro 1-800-708-7555

CA - VALLEJO - Computer Show & Sale. Solano Co. Fairgrounds. MarketPro 1-800-708-7555

CA - SANTEE - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in 619-561-0052

IN - INDIANAPOLIS - AGI Computer Fair. Indianapolis Events Center. 3655 E. Raymond St. 317-299-8827

MD - BALTIMORE - Computer Show. Martin's West. MarketPro 301-984-0880 xt15

MI - TRAVERSE CITY - Hamfest. Cherryland ARC. Joe Novik 616-947-8555

NH - SEABROOK - Computer Show. Greyhound Park. 10am-3:30pm. Northern Computer Shows 508-744-8440

NY - HORSEHEADS - Hamfest. State Armory, 128 Colonial Dr. Jack Slocum 607-739-4866

OR - RICKREAL - Salem Hamfair. Polk Co. Fairgrounds. 9am-3pm. James Pardey 503-651-3216

PA - OBERLIN - Winter Hamfest. Oberlin Fire Co. HRAC AnswerLine 717-232-6087

TX - SMITHVILLE - ARRL Hamfest. Bastrop Co. ARC. Charlie Claiborne 512-360-3670

VA - ANNANDALE - Computer Show. Northern VA Comm. College. MarketPro 301-984-0880 xt15

FEBRUARY 15-16

GA - NORCROSS - Computer Show. North Atlanta Trade Center. MarketPro 301-984-0880 xt15

PA - MONROEVILLE - Computer Show. Pittsburgh



- PRODUCT ENGINEERING
- FIRMWARE DEVELOPMENT

- MICRO CONTROLLER & EPROM HARDWARE & SOFTWARE DEVELOPMENT

**"QUALITY
IS OUR
CAPITAL
CONCERN."**

**Complete On Site
Electrical Engineering Lab**

- REVERSE ENGINEERING
- RF CIRCUIT DESIGN & MANUFACTURING

From Auto-Routing to CNC Routing to Electronic Assemblies. . .
Capital Electronics is Your Best Route For Printed Circuit Boards.

DESIGN/LAYOUT

- CAD LAYOUT SERVICES
- COMPATIBLE WITH ALMOST ALL CAD SYSTEMS
- FROM SCHEMATICS OR SAMPLE PCB'S
- PHOTOPLOTTING SERVICES
- 28,800 BAUDE MODEM

PRINTED CIRCUIT BOARDS

- SINGLE & DOUBLE SIDED
- MULTI-LAYER & FLEXIBLE PCB'S
- FROM QUICK TURN PROTOTYPES TO SCHEDULED PRODUCTION RUNS
- FINE LINES, SMT
- ELECTRICAL TESTING
- PRECIOUS METAL PLATING

ASSEMBLY SERVICES

- FAST TURN BOARD STUFFING
- WIRE HARNESSSES
- WAVE SOLDERING
- ACQUISITION OF PARTS
- FINAL TESTING
- TURNKEY SERVICES
- CUSTOM ENCLOSURES

**For Quick & Competitive Pricing or More Information,
Please Call Us Today!**

852 Foster Avenue • Bensenville, IL 60106

(630) 350-9510

Fax (630) 350-9760 • Modem (630) 350-9761

Internet Access:

For Automated Info Response:
INFO@capital-elec.com

E-Mail: Quote@capital-elec.com

Web Access: <http://www.capital-elec.com>

Write in 99 on Reader Service Card.

Events CALENDAR

Expo Mart. MarketPro 301-984-0880 xt15
VA - ROANOKE - Computer Show. Civic Center.
MarketPro 301-984-0880 xt15

FEBRUARY 16

CANADA - BC - WESTMINSTER - Hamfest.
Burnaby ARC. Harry Curtis 604-530-3962
CA - SAN DIEGO - Computer Show & Sale.
Scottish Rite Center. 10am-5pm. MarketPro
1-800-708-7555

IL - ROCK ISLAND - Hamfest. QCCA Expo Center,
2621 4th Ave. Davenport RAC. Kent Williams K9UQI
309-796-0718 4-9pm only

IN - NOBLESVILLE - Computer Fair. Hamilton Co.
Fairgrounds, off I-37 exit Pleasant Rd. near Walmart.
10am-3pm. AGL Services 317-299-8827

MA - TAUNTON - Computer Show. Taunton Holiday
Inn. 10am-3:30pm. Northern Computer Shows
508-744-8440

MD - BOWIE - Computer Show. Bowie State
University. MarketPro 301-984-0880 xt15
NC - ELKIN - Hamfest. Briarpatch ARC & Foothills
ARC. Jimmy Holbrook 910-957-3820

NY - FREEPORT - Hamfest. Long Island Mobile
ARC. Mark Nadel 516-796-2366

PA - LANCASTER - Computer Show. Holiday Inn
Lancaster Host. MarketPro 301-984-0880 xt15

FEBRUARY 17

CA - MODESTO - Computer Show & Sale. Centre
Plaza at Red Lion. MarketPro 1-800-708-7555
MA - BOXBOROUGH - Computer Show. Holiday
Inn. 10am-3:30pm. Northern Computer Shows 508-
744-8440

OH - NILES - Computer Show. Eastwood Expo
Center. MarketPro 301-984-0880 xt15

PA - ALLENTOWN - Computer Show. Allentown
Fairgrounds. MarketPro 301-984-0880 xt15

VA - RICHMOND - Computer Show. The Showplace.
MarketPro 301-984-0880 xt15

FEBRUARY 22

AR - RUSSELLVILLE - Hamfest. AR River Valley.
Dallas Scott 501-967-3317
FL - SPRING HILL - Hamfest. Hernando County
ARA. Lee Kent 352-799-1638

GA - DALTON - Hamfest. Dalton ARC. Harold Jones
706-673-2291

IN - LAPORTE - Hamfest. LaPorte Civic Center.
8am-2pm. John N9ROH, POB 30, LaPorte, IN 46352

ND - BISMARCK - CDARC Hamfest. Radisson Inn.
8am-4pm. Tim Rasset 701-663-6620

NH - MANCHESTER - Computer Show. Center of
NH Complex. 10am-3:30pm. Northern Computer
Shows 508-744-8440

NJ - TRENTON - Computer Show. Trenton State.
MarketPro 301-984-0880 xt15

TX - ORANGE - Hamfest. Orange ARC. Irene
Thomas 409-745-3061

VT - MILTON - Hamfest. Milton High School. Radio
Amateurs of Northern Vermont. Mitch Stern
802-879-6589

FEBRUARY 22-23

CA - SACRAMENTO - Computer Show & Sale. Cal
Expo. MarketPro 1-800-708-7555

CA - VENTURA - Computer Show & Sale. Ventura
Fairgrounds. MarketPro 1-800-708-7555

FL - TAMPA - Computer Show. FL State
Fairgrounds. MarketPro 301-984-0880 xt15

MD - GAITHERSBURG - Computer Show.
Montgomery County Fairgrounds. MarketPro
301-984-0880 xt15

OH - CINCINNATI - Conv. Great Lakes Division
Convention. Cincinnati Gardens Exhibition Center,
2250 Seymour Ave. 8:30am-5pm. Stan Cohen
513-531-1011

OH - DAYTON - Computer Show. Montgomery Co.
Fairgrounds. MarketPro 301-984-0880 xt15

TN - KNOXVILLE - Computer Show. Knoxville
Fairgrounds. MarketPro 301-984-0880 xt15

FEBRUARY 23

DE - NEWARK - Computer Show. University of DE.
MarketPro 301-984-0880

IL - GLEN ELLYN - Computer Show & Sale. College
of DuPage. Main Arena of Phys Ed Bldg. Corner of
Park Blvd. & College Rd. Computer Central Shows
847-940-7547

MA - WESTFORD - Hamfest. Greater Boston
Antique Radio Collectors. Lisa Friedrichs
508-371-0512

ME - PORTLAND - Computer Show. Verillo's Conv.
Center. 10am-3:30pm. Northern Computer Shows.
508-744-8440

MI - DEARBORN - Swap'n Shop. Dearborn Civic
Center. 8am-3pm. Neil Coffin 313-261-5486

OH - CUYAHOGA FALLS - Hamfest. Emidio's Party
Center. 48 Bath Rd. 8am-2pm. Bob Recny N8SQT
330-864-5810

PA - PITTSBURGH - ARRL Hamfest. South Hills
ARC. Eric Hegerle 412-341-02270

MARCH 1997

MARCH 1

AL - TUSCALOOSA - Black Warrior Swapfest. Kelly
Bruce 205-339-7882

CA - SANTEE - ARC of El Cajon Ham, Computer &
Electronic Swapmeet. Santee Drive-in. 619-561-0052

GA - ATHENS - Hamfest. NE Georgia Bubba Net.
James Daniel 706-742-2777

MD - NEW CARROLLTON - Computer Show.
Ramada Conference & Exhibition Center. MarketPro
301-984-0880 xt15

NJ - ABSECON - Springfest '97 Hamfest. Holy Spirit
High School. Shore Points ARC 609-653-1987

NJ - PARSIPPANY - Hamfest. PAL Building. Split
Rock/West Morris Radio Clubs. Bernie 201-584-5399

OK - ELK CITY - ARRL Hamfest. West Central OK
ARC. Earl Bottom 405-473-2572

TN - CLEVELAND - Hamfest. Ocoee ARS. Alan
Pinney 423-478-1141

MARCH 1-2

FL - FT. LAUDERDALE - Computer Show. War
Memorial Auditorium. MarketPro 301-984-0880 xt15

IN - FT. WAYNE - Computer Show. Allen County
Fairgrounds. MarketPro 301-984-0880 xt15

PA - HARRISBURG - Computer Show. Farm Show
Complex. MarketPro 301-984-0880 xt15

VA - NORFOLK - Computer Show. Norfolk Scope.
MarketPro 301-984-0880 xt15

MARCH 2

CA - LIVERMORE - Swapmeet. Las Positas College.
Noel Anklam 510-447-3857

MA - SWANSEA - Computer Show. Venus DeMilo.
9:30am-2:30pm. Northern Computer Shows
508-744-8440

MD - FREDERICK - Computer Show. Frederick
Fairgrounds. MarketPro 301-984-0880 xt15

PA - TREVOSE - Photographic Swap/Shop Show.
Radisson Hotel. 10am-3pm. OMM Productions
610-527-5903

MARCH 7-8

ME - LEWISTON - State Convention. Dave Blithen
207-353-6433

MARCH 7-8-9

LA - LAFAYETTE - ARRL Hamfest. Acadiana ARA.
L. Al Oubre 318-367-3901
NE - NORFOLK - State Convention. Rick Kropf 402-
371-7684

MARCH 8

CA - FONTANA - Inland Empire ARC Amateur &
Electronics Swapmeet. A B Miller High School. Bill
909-822-4138 eves.

FL - ENGLEWOOD - HamCom '97. Tringali
Community Center, SR 776 Englewood East. 8am-
3pm. George Shreve 941-697-3445

IN - INDIANAPOLIS - AGI Computer Fair.
Indianapolis Events Center. 3655 E. Raymond St.
317-299-8827

KY - HAZARD - ARRL Hamfest. Kentucky Mountains
ARC. 8am-2pm. John Farler 606-436-5354

NH - PORTSMOUTH - Computer Show. Frank
Jones Center. 10am-3:30pm. Northern Computer
Shows 508-744-8440

WA - PUYALLUP - Electronics Show & Fleamarket.
Pavilion Exhibition Hall, Western Washington
Fairgrounds. 206-631-3756

MARCH 8-9

FL - ORLANDO - Computer Show. Orlando Expo
Center. MarketPro 301-984-0880 xt15

NC - CHARLOTTE - Roanoke Division Convention.
Tim Slay 704-948-7373

PA - KING OF PRUSSIA - Computer Show. Valley
Forge Conv. Ctr. MarketPro 301-984-0880 xt15

VA - CHANTILLY - Computer Show. Capital Expo
Center. MarketPro 301-984-0880 xt15

VA - RICHMOND - Computer Show. The Showplace.
MarketPro 301-984-0880 xt15

MARCH 9

IN - INDIANAPOLIS - Hamfest. Morgan Co.
Repeater Assn Brian Elliott 317-342-7236

ME - AUGUSTA - Computer Show. Augusta
Armory. 10am-3:30pm. Northern Computer Shows
508-744-8440

NY - LINDENHURST - ARRL Hamfest. Great South
Bay ARC. Walter Wenzel 516-957-0218

OH - CONNEAUT - Ham/Computerfest. Human
Resource Center, 327 Mill St. Jack Martilla 216-593-
3353

Continued on page 112



NOVAPLEX

The One-Stop Source for Cable Parts, Tools & Accessories

Only Novaplex Brings You So Many Great Low-Cost Converters

Centurion



The New Centurion converter offers a number of powerful features:

- parental control
- switched AC outlet
- sleep timer
- remote control included
- auto/manual fine-tune
- favorite channel memory
- batteries included
- jumper cable included
- illustrated user manual
- LED display

Introductory Offer! For a limited time only, 10-lot price is only:

only \$65

Feature of the Month

MOTOROLA 68H705C8P MICRO BLOW OUT!

\$8.95

each
minimum order 100 lot

NOVAVISION

Watch one channel and record another any quantity **\$199**



MILLENNIUM

Configure the various option packages to suit your needs 10-lot: **\$62**



Panasonic TZPC 145 Converter SA 8511-300 Converter

Units sold with wireless remote control & batteries. Features include: parental control (Panasonic only), last channel recall, favorite channel memory, sleep timer, channel 2 or 3 available.

In quantities of 10 or more, **\$65**



Panasonic TZPC 145 **\$65**
channel 2 or 3; 10-lot prices

SA 8511 channel 3 8-lot: **\$65**

Also: Panasonic TZ-PC 175 Series Converter w/volume. Topcases for Panasonic, SA and Jerrold (all models) also available. Call for pricing and availability.



Quality SA-Compatible Remotes



SRC 8600A
Operates 8600 on-screen programming converters

\$6.25



SRC 475A (w/volume)
Operates 8540 & 8590 series volume-control converters

\$6.25



SRC 175A
Operates 8500-8590 series non-volume converters

\$5.75



SRC 075A
Operates all beige 8500 series converters

\$5.75

Also available: Tocom, Hamlin, Pioneer, and Panasonic compatibles; all prices quoted in this ad are:

10-lot prices



PIRC 82A
Operates Pioneer 8200 series converters

\$6.25



JRC 450A
Operates Jerrold DRZ 450 series converters

\$5.75



JRC 550A (w/volume)
Operates DP, DPBB, DPV, DQN 5&7, Starcom VI, & DL4 series converters

\$5.75



ZRC 3 (Zenith)
Operates all Zenith PM, PZ, ST series

\$6.00

Full Line of Jerrold-Compatibles

Dozens of other items in stock!

Jerrold- & SA-compatible topcases with lenses from **\$3.25**
Torx Bits & Drivers (all brands) from **3.95**
Capacitors (every voltage) at 1000-lot prices from **.06**

Call for quantity discounts!

Kester Solder 44 Coresize from **\$8.45/roll**
Jumper cables (1, 3 & 6 ft.) from **.60**
Jerrold- & SA-compatible bezels & lenses from **.95**

Call for your free catalog!

NO DESCRAMBLER SALES!



Call Toll-Free 8am-6pm PST 800-644-6682

Novaplex, Inc. 8818 Bradley Ave, Sun Valley CA 91352
FAX: 818/504-6522 COD, MasterCard, Visa, Credit Terms

Panasonic™, Jerrold™, Zenith™, Tocom™, Pioneer™ and Scientific Atlanta™ are trademarks of their respective corporations and are not affiliated with Novaplex, Inc.

SPECIAL PROJECTS

We design/build/modify/repair/consult on any device/system/process/project electronic/computer/mechanical/optical (eg: phone/auto/security/Radionic/lab/energy/HV/EM/RF/radar/ultrasonic/IR/UV/commo) for business and personal/invention needs. Describe & include nonrefundable \$30 pre-engineering fee. Time & cost estimates 7-10 days. Confidentiality guaranteed.

OFF-THE-SHELF HARDWARE

Van Eck Systems★Data Card Reader/Writers★RF/EM/μWave/Radar/Ultrasonic/IR/Light/Sound Detectors/Xmitters/Jammers/Blasters★Security/Surveillance★EM Weaponry/Countermeasures★Neurophone/Rife/Resonant Crystal Radionics★Bug & Tap Detectors/Blasters★Lineman's Handsets★Phone Color Boxes★Voice Disguisers★ESS Infinity Devices★DTMF Decoders★Child Finder★Panic Button★Slot Machine Masters★Subliminal Mixer/Amps (Ultrasonic/Infrasonic)★Alien Brainblasters★Electronic Dowzers★Shriek Modules★Ghost Detectors★Vortex Generator★Blackjack Devices★6th Sense Communicator★Much, much, much more! Buy our Catalog Today!!

CELLULAR & CORDLESS PHREAKING \$59

How cellphones operate and are modified. Vulnerabilities to hack attack and countermeasures. Comprehensive details on reprogramming NAMs, ESNs, etc (cloning), control data formats, computing encoded MINs, ESNs, SIDHs, operating systems, PROM programming, forcing ACK, test mode and resets, cable diagrams, scanning, tracking, scanner restorations, freq and channel allocations, roaming, ESN and SIDH tables, troubleshooting, parts/equipment sources, attendant stations, non-USA bands, health concerns, and the ECPA and critique. Step-by-step descriptions to keypad-reprogram 100+ popular cellphones. Plus complete section on phreaking cordless phones! Much more! 10 times more info than any competitor's manual!

Free Cellular Data Search: As a special service to C&CP buyers, we'll perform one FREE search of our massive cellphone database if requested within 30 days of your purchase. Search results not guaranteed. Request by mail (not fax); include a #10 SASE.

PAGER (BEEPER) MANUAL \$39

Describes in detail how Pagers work, different types and uses, frequencies, advantages over and uses with cellphones, and tips and tricks. How Pagers are hacked and countermeasures. Includes plans for your own **Personal Pocket Paging System** (xmitter and receiver).

HACKING FAX MACHINES \$39

Describes in detail how Faxes are hacked and countermeasures. Includes G3 Fax protocols, commo parameters, compression algorithms, Class 1 & Class 2 commands, Spy Fax Switcher, Fax Servers, FODs/FOCs, and Makeup/Terminating Codes. And insights into designing Fax interception devices and modifying existing Faxes into Stealth Faxes. **More!**

PBX HACKING \$29

PBXs (Private Branch eXchanges) are hacked to the tune of about \$8 Billion/yr! Exposes and details all issues relating to PBX hacking, including countermeasures. This is the **only** hacking manual ever featured in Forbes Magazine!

VOICE MAIL HACKING \$29

Exposes how Voice Mail Box systems are used and the specific ways they are hacked. Includes ASPEN, MESSAGE CENTER, BIX, GENESIS, CENTAGRAM, RSVF, EZ, AUDIX, SYDNEY, PHONE MAIL, CINDY, SPERRY LINK, etc. A must for all users, hackers and security personnel!

10% OFF
Orders Over
\$100!!

TOP SECRET

NOT
FOUND IN
BOOKSTORES!

CONSUMERTRONICS

P.O. Drawer 537 Alamogordo, NM 88311

ORDER TODAY! 505-439-1776

Fax: 505-434-0234 (ORDERS ONLY)

Customer Tech Support: 505-439-8551

Top Secret Homepage: users.aol.com/wizguru/hi-tech.html

Established in 1971. Featured on CBS "60 Minutes," Forbes, New York Times.

Add \$5 total S/H (US, Canada). Sold for educational purposes only.

Postal M.O. is fastest. VISA, MC OK. COD (\$49-\$999), add \$6.

AUTOMATIC TELLER MACHINES \$39

ATM crimes, abuses, vulnerabilities and defeats exposed! 100+ methods detailed, include: Physical, Reg. E, cipher, PIN compromise, card counterfeiting, magnetic stripe, false front, TEMPEST, Van Eck, tapping, spoofing, inside job, super-cool, vibration, pulse, high voltage - others. Case histories, law, countermeasures, detailed security checklist, labeled internal photos, figures. ATMs contain up to \$250,000 in cash! Add \$20 for Placak Report!

THE PLACAK REPORT \$39

Describes the reading (using a simple method) and decryption of the magnetic flux-reversals on popular credit, debit, security and other card magnetic stripes. How to easily determine the decrypted PIN, PAN, bank number, routing codes, dates, number of daily uses and uses remaining (ex: cards that are decremented after each use).

BEYOND PHONE COLOR BOXES

Dozens of PCB's described - many circuits. Plus Call Forwarding, Phreak History, Conferencing, Glossary, Diverters, Extenders, Loops, REMOBS, Bridging Heads & Cans, Optocom, 3rd Party and many other non-box methods - more! \$29.

HACKING ANSWERING MACHINES

All the known ways answering machines are hacked to listen to - even erase - messages, and to convert them into mini-VMBs. Plus countermeasures - protect yourself from hackers, thieves! \$29.

PHREAKING CALLER ID & ANI

Details on how they work and dozens of effective ways of defeating Caller ID, ANI, *69, *57, Call Blocking, *67 etc. Also describes Caller ID, Orange, Beige, Cheese & CF Boxes, ESS, S57, E-911, various Class services, CN/A, Non Pub DA, CAMA, DNR, 800-ECR, Diverters, LD Extenders, Centrex - much more! \$29.

BEYOND VAN ECK PHREAKING

Eavesdropping on TV and computer video signals using an ordinary TV described in detail. Includes security industry reports. Range up to 1 KM. Plans include both the Consumertronics and the original Top Secret Van Eck designs! \$29.

THE HACKER FILES

Compilation of 100s of the best eye-popping articles written by top hackers & phreakers. ASCII text. Covers every major topic in hackerdom! Comes on 3 HD PC Disks! \$49.

MIND CONTROL

Fear increases over EM and ultrasonic mind control technologies - especially implants! Many more lies published than facts. Secret agents are often used for reporting back to covert organizations. Learn shocking truth about this bizarre phenomena! \$39.

UNDER ATTACK!

Electromagnetic weapon attacks cause cancer, birth defects, and profound psychological and neurological disorders! This manual includes actual cases of EM attacks (we investigated!) Includes how to how to tell if you are under EM attack, and specific countermeasures. \$29.

BY AN ORDER OF THE MAGNITUDE

The most comprehensive, hard-hitting, hi-tech survival book ever written! Topics include electronic, computer, cryptography, chemistry, weaponry, commo, energy, concealment, revenge, alarm, disguise & ID change. Designs, tactics & strategies to survive an increasingly dangerous and brutal world. Field-expedient use of technology in various threat and conflict environments and scenarios. **More!** \$49.

THE ULTIMATE SUCCESS MANUAL

How to lie, cheat, steal, influence, and intimidate your way to success! Underpaid? Overworked? Harassed? Manipulated? Forget job performance. This manual exposes and outlines what it really takes to make it to the top in today's corporate BS world! \$19.

RADIONICS MANUAL

Exciting electronic and electromagnetic therapeutic, diagnostic devices (mostly experimental). History, descriptions, plans, availability! \$29.

STOPPING POWER METERS \$29

As reported on "60 MINUTES!" How devices can slow down (even stop) watt-hour meters - while loads draw full power! Device plugs into one outlet and normal loads into other outlets. Describes meter creep, overload droop, etc. Plans.

THE I.G. MANUAL: External magnetic ways (applied to meter) to slow down and stop power meters while drawing full loads. Plans \$25.

KW-HR METERS: How watt-hour meters work, calibration, error modes (many), ANSI Standards, etc. Demand and Polyphase Meters. Experimental results to slow and stop meters by others. \$25.

Special! All 3 (above), Only \$59!

COMPUTER PHREAKING \$39

Describes in detail how computers penetrate each other, and how VIRUSES, TROJAN HORSES, WORMS, etc are implemented. Dozens of computer crime and abuse methods and countermeasures. Includes disk filled with hacker text files and utilities, and the legendary FLUSHOT+ protection system (Ed. Choice, PC Magazine). Internet advice, password defeats, glossary - much more! Manual + PC Disk!

INTERNET CONS & SCAMS \$29

Net cons and related frauds rake in \$2+ Billion annually! Most are done with little fear of prosecution. This manual details most, and countermeasures.

INTERNET TRACKING & TRACING \$39

The Internet is infected with spammers, stalkers, scammers, infectors, and other wrongdoers who hide behind its anonymity. Learn how to trace them down in this comprehensive manual! **Invaluable!**

OTHER EXCITING TITLES!

CREDIT CARD SCAMS \$29

Describes every known means of credit card fraud and scams. Includes countermeasures. Protect yourself!

CONS & SCAMS \$34

The most comprehensive manual on cons & scams available! Details 100s, their many variations, and countermeasures.

STEALTH TECHNOLOGY \$29

Every known police radar error - stealth method and material used to minimize radar and laser reflections - tactic and strategy to fight speeding tickets - methods to detect and jam signals are fully described!

HEAL THYSELF! \$19

Detailed plans for 3 major electronic therapeutic health devices of the types approved by the FDA. **Real Alternative Medicine!**

HIGH VOLTAGE DEVICES \$29

Many HV device plans: Stun Gun, Taser, Prod, Cane, Flasher, Blaster, Zapper, Audio/RF/Radar Jammer, Jacob's Ladder, Plasma & Van de Graaff Gens., Fence Charger, Geiger Counter, Fish Stunner, Plant Stim., Kirlian, much more!

POLYGRAPH DEFEATS! \$29

How anyone can tell "the truth" to a "lie detector". Many methods to beat the test, and what to avoid. Eye-popping!

SHOCKING!

ALL-NEW TOP SECRET CATALOG. FEATURES 200+ HI-TECH PRODUCTS! WILL BLOW YOUR MIND! MAIL \$3, OR \$1 WITH ORDER! ORDER TODAY!!

THE NUTS & VOLTS SOLAR WORKSHOP

Welcome to The N&V Solar Workshop ...

Building A Small Solar Power Plant

One of the many letters that prompted me to write the *Nuts & Volts Solar Workshop* came from Eric of Palm Springs, who asked "Can you provide guidance on building a small solar station ... to provide solar power (photovoltaics) for an electrical sprinkler system?" Since then, I've received requests for solar-powered satellite dishes, Malibu lights, and other small applications.

Now that we have some theory and hands-on experience under our belts, I feel confident to push forward to bigger and better things. In this segment of the *Solar Workshop*, I'll show you exactly how to design and assemble a photovoltaic system that will run Eric's sprinklers or Craig Hueser's satellite dish. I'll be drawing from material presented in the last two *Solar Workshops* (Nov. and Dec. '96), so you might want to have those issues handy.

The Workshop

A 12-Watt Solar Installation

I hope you brought your work clothes, because we're going to spend a lot of time in the Workshop today, getting our hands dirty at times. If you don't completely understand some of the concepts set forth or have questions not answered here, take a moment to sit in on the Classroom, where there's a question and answer session in progress.

About the System

The first thing you do when designing a solar installation is to determine the system parameters. Always begin with the device to be powered and work backwards from there.

Let's take the sprinkler scenario, for example. We'll call this System A. The selenoids draws about 2 amps of current for two hours a day. The same is true of the satellite dish, which also draws 2 amps of current in short spurts, probably for a total of

an hour a day. We'll call the dish System B. Both devices are 12-volt operated, and need to have power available on demand, not just when the sun is willing to shine.

So for this design, we'll need a storage battery, which means we'll also need a charge controller, like the one described in the Dec. '96 *Solar Workshop*. Figure 1 shows a block diagram of our system. If you're ready, let's get started.

Amp-Hours vs. Watts

The following is going to be the hardest part of the design because it's not easy to understand the first time around. Typically, household appliances are rated in watts. For example, a 100-watt light bulb uses 100 watts of power. A toaster may consume 1,100 watts, and your TV is most likely a 250-watt consumer. The only thing these appliances have in common is their wattage rating, because heaven knows a TV set isn't the same thing as a toaster (well, mostly not, except for the crummy shows on it).

Photovoltaics work from two different camps. On one side, you have solar panels, which are rated in watts. Battery-operated devices, on the other hand, are rated in amp-hours, or Ah. What's an amp-hour? It's one amp of current flowing through a device (load, if you will) for one hour. One amp-hour doesn't equal one watt, though. Watts are the product of voltage times current ($W = E \times I$), whereas amp-hours are the product of current times time ($Ah = I \times t$).

If we turn on the sprinklers (system A) for two hours a day, and they draw 2 amps of current, then they consume 4 Ah of power. The satellite dish (system B) also draws 2 amps of current, but for only one hour a day, for a total of 2 Ah. To satisfy the needs of system A alone, we need 4 Ah; system B needs 2 Ah daily. Together they need 6 Ah. For the rest of this dis-

cussion, let's focus on system A, the sprinkler system, which is 4 Ah.

How much is that in watts, you ask? That's a good question because you can't buy an amp-hour solar panel. To get a wattage rating, we need to know the voltage of the system. In this case, it's 12 volts. If we multiply 12 volts by 2 amps, we get 24 watts; 12 volts at 1 amp is 12 watts. At this point, time isn't a factor, but it will be soon, so listen up.

Insolation

The next step is to introduce the element of time. We already know the time of the load, because it's expressed in amp-hours. What we need to determine is the amount of time the photovoltaics will be generating energy, which we'll then convert into amp-hours.

The amount of potentially useful radiation is called the insolation value. Solar insolation varies widely from one point on the planet to another, and involves many factors. Thankfully, the US Weather Bureau has rendered all these factors into simple insolation maps, like the one shown in Figure 2.

However, this map doesn't work for microclimates, such as a town nestled against a hillside. Fortunately, I've located a site on the Internet (<http://solstice.crest.org/renewables/solrad/data/index.html>) sponsored by CREST (Center for Renewable Energy and Sustainable

Technology) which has an interactive solar radiation and climate database for hundreds of cities in the US and its territories. You click on your city from a map (Figure 3), and up pops a detailed chart of your solar and weather conditions for the whole year.

However, if you look at the insolation map in Figure 2 carefully, you'll notice that the majority of cities in the continental US have an insolation value between 5 and 6. This means that over the course of a year, you can expect to receive five to six hours of productive solar power on average. These are the numbers we'll use for the next part of our design.

Crunching the Numbers

Let's say that we want to translate 4 Ah into wattage for San Francisco, which has an insolation rating of 5.5. First, we need to calculate the current using the formula

$$I = Ah / \text{insolation value}$$

or

$$I = 4 / 5.5$$


which is 0.73 amps. This tells us that a sustained current of 0.73 amps for 5.5 hours is the equivalent of 4 Ah.

Now that we have a current value, it's easy enough to calculate wattage. Let's assume, for the moment, the voltage is 12 volts. Plugging these values into our $W = EI$ formula gives us an answer of 8.76 watts. Now we're getting somewhere.

We now know that we need at least a nine-watt solar panel to keep our system afloat. Rather than have you wade through all the calculations, ripping out your hair or clawing at your face, I've done the homework for you in Table 1. Notice that the farther south you go, the higher the insolation value, and the smaller the solar panel wattage requirement.

Sizing the System

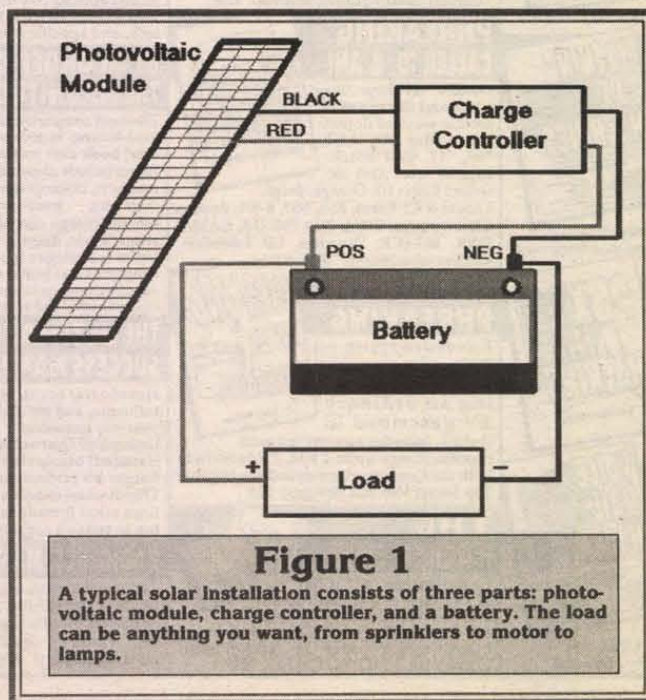The next step is to match the numbers in Table 1 to your load and solar conditions. This time, let's pick Los Angeles, which has an insolation value of 6.0,



THE NUTS & VOLTS SOLAR WORKSHOP

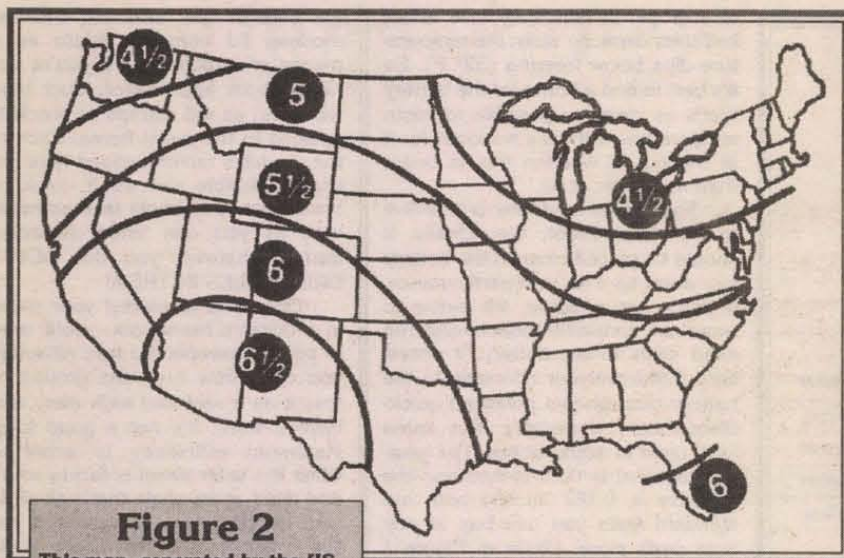


Figure 2

This map, generated by the US Weather Bureau, shows the number of hours of productive sunlight you can expect per day over the course of a year.

operating with a 4 Ah load. Our chart tells us the current is 0.66 amps and that the photovoltaic requirements are somewhere between 7.9 and 8.7 watts.

Why the two wattage ratings? Because not all solar panels are rated at the same voltage. Some vendors rate them at 12 volts (nominal) and others at 13.2 volts, the minimum voltage needed to charge a 12-volt battery. For now, let's go with the higher voltage, which specifies 8.7 watts.

Keep in mind that this is the power used on a daily basis, and not the power we need to generate. As I discussed last month in the Classroom (you did attend, didn't you?), you have to put more power back into a battery than you took out. Which means our battery will go dead in short order if we use an 8.7-watt solar panel.

Typically, you need to return at least 10 percent more power than you take out. The size of the solar panel has now jumped from 8.7 to 9.6 watts; let's call it 10 watts.

That done, we now need to match the photovoltaics to a battery. We know that the battery must be able to supply 4 Ah on a daily basis. However, fully depleting a battery on a regular basis (deep cycling) short-

ens its life. Moreover, what happens if the sun doesn't shine for a day, or two? Do you go without the sprinklers or forego watching TV? Hardly — you just buy a bigger battery.

But here's where you have to be careful, because oversizing the battery is as bad as undersizing it. Unless the battery is exercised, the plates will sulfate and suffocate the battery. Let's see what size is the best for this application.

If we select an 8 Ah battery, it will last two days without sunshine, and discharge to only 50 percent on average. That's cool, but not good enough. A 12 Ah battery would be better because it gives us three days of cushion and only discharges 33 percent daily. (When used in a system with a 3 Ah rating, this changes to four days storage and 25 percent daily discharge.)

This is the battery we'll select for

our Los Angeles solar site. If we follow this same scenario for Seattle, it would be wise to up the size of the battery to 20 Ah because of the more severe weather conditions. A 20 Ah battery will typically last up to five days and discharge to only 20 percent on average.

Shopping for Solar

With grocery list in hand, it's time to go shopping for the parts needed to put this system together. Let's tackle the solar panel first.

Depending on your geographical location, the solar panel will vary in size between 10 watts and 12

The first is the 10 Watt Lite "Clone" (part number 11-560) from Alternative Energy Engineering. This module was made in Korea as a power supply for a pump in a solar water heating system, but the dimensions were wrong. AEE bought a large quantity at a good price, and they're passing the savings on to you. The price is \$95.00. This stainless-steel-backed panel measures 10.6" x 17.6" and comes unframed.

Next is a 12-watt module from Jade Mountain (catalog number PV908). The solar panel was made by Chronar, which went out of business about 10 years ago. Jade Mountain acquired several thousand of these panels and is selling them for \$95.00. The module measures 12" by 36" and comes fitted in a metal frame.

Last, but not least, is the 11-watt solar panel from Solar Electric. Made by Unisolar, this flexible panel is unbreakable and is often used in RV and marine applications. It measures 12" by 24" and sells for \$99.00 unframed, or \$129.00 framed.

Finding a suitable battery isn't as easy as it first appears, especially if you're looking for a low-cost unit with good quality. My pick is the Model PS-12120 from Power-Sonic (Figure 4). It provides 12 Ah of power, and retails for under \$50.00 (call Power-Sonic for the dealer nearest you). It's a sealed, maintenance-free battery of spill-proof construction with valve-regulated recombination (see the Dec. '96 Classroom for details).

The battery can withstand between 200 and 1,000 charge/dis-

charge cycles, depending on the average depth of discharge, and recovers quickly from a very deep discharge. Under normal usage, the battery will last about five years. Power-Sonic also carries a full line of photovoltaic batteries ranging in

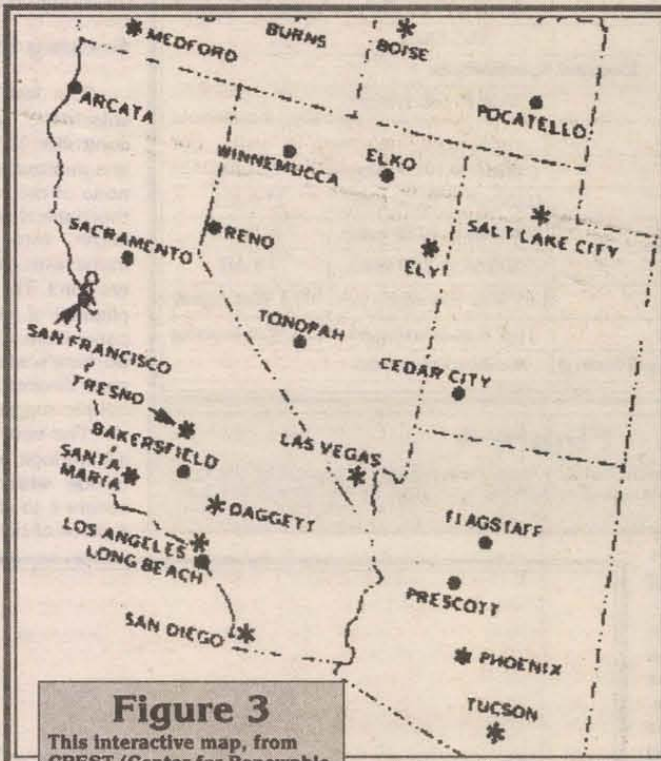


Figure 3

This interactive map, from CREST (Center for Renewable Energy and Sustainable Technology), lets you focus in on microclimates for precise weather and solar conditions.

watts. Well, I did some shopping around and came up with solar panels from three vendors that fill the bill (see "Where To Buy" for details). All sell for under \$100.00.

HOT! Photovoltaic Web Sites


CREST, the Center for Renewable Energy and Sustainable Technology (<http://solstice.crest.org/>) is specifically geared to providing info via the Internet, and includes a good database of US climate data, including detailed solar data on hundreds of cities (Figure 3).

The Solar and Renewable Energy Resources list (<http://www.ises.org/pages/solarinfo.html>), maintained by the International Solar Energy Society, is the most comprehensive solar Website I've ever seen. **This is a must — check it out.**

The National Renewable Energy Laboratory's Web site (<http://www.nrel.gov/research/pv/tapsun.html>) includes a comprehensive discussion of the economics of photovoltaics and descriptions of a range of applications.

The US Department of Energy's "Energy Efficiency & Renewable Energy Network" (<http://www.eren.doe.gov/>) is a good general source on efficiency and renewable energy, and includes a range of databases.

THE NUTS & VOLTS SOLAR WORKSHOP

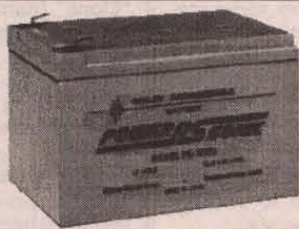

PS-12120 / 12V-12.0 Amp. Hr. Battery

Finished Specifications

Dimensions:

Length	5.94 inches	151 millimeters
Width	3.86 inches	98 millimeters
Height	3.70 inches	94 millimeters
Height over Terminals	3.94 inches	100 millimeters
Approximate Weight	9.0 pounds	4.1 kilograms

Terminals: Polarized

Quick Disconnect Tabs	(pos) 0.250"x0.032"	(neg) 0.187"x0.032"
-----------------------	---------------------	---------------------

Case:	ABS Plastic
-------	-------------

Electrical Specifications

Nominal Voltage:	12 Volts (6 cells in series)	
Nominal Capacity:		
20 hour rate	(600mA to 10.50 volts)	12.0 AH
10 hour rate	(1100mA to 10.50 volts)	11.0 AH
5 hour rate	(2000mA to 10.20 volts)	10.0 AH
1-hour rate	(7800mA to 9.00 volts)	7.8 AH
Energy Density (20 hour rate)	1.69 Watt-hours/cubic inch	103.6 Watt-hours/l
Specific Energy (20 hour rate)	16.4 Watt-hours/pound	35.1 Watt-hours/kg
Internal Resistance (Fully Charged Battery)	16 milliohms (approx.)	

Figure 4

The PS-12120 sealed lead-acid battery from Power-Sonic is typical of the type of battery needed for our design. For harsher climates, up the size of the battery to 20 Ah.

capacity from a few amp-hours up to hundreds of amp-hours.

Of course, Power-Sonic isn't the only maker of batteries. More are listed in the "Where To Buy" box. Moreover, batteries of this capacity can often be found on the surplus market for pennies on the dollar. While a car battery could be used in this application, it won't last more than a year because it's oversized and intolerant of the photovoltaic's erratic charging cycles. But if you want to see for yourself, who am I to stop you?

Assembly

Now comes the fun part — getting our hands dirty. Let's begin by positioning the battery in a warm, cozy place where it's not exposed to the elements. Lead-acid batteries lose a lot of their power when the tempera-

ture drops. In fact, they lose about half their capacity when the temperature dips below freezing (32° F). So it's best to find a home for the battery that's as close as possible to room temperature. If there's no room for it at the inn, a wooden box is better than no shelter at all.

The charge controller is sensitive to its environment, too. Ideally, it should be placed close to the battery in a warm spot for best performance. If that's not possible, it's better to move the controller indoors and run extra wires to the battery, if necessary. The controller connects to the battery through two polarized quick-disconnect connectors, the same kind used in automobiles. The positive terminal is 0.25 inches and the negative is 0.187 inches; both are standard sizes you can buy at any auto parts store. (Refer to Figure 1 for wiring details.)

Seeking the Solar Angle

The last step is mounting the solar panel and connecting it to the controller. This is going to take some imagination on your part because none of the modules have the same mechanical specifications. Some are larger, some smaller. One has a frame with mounting holes, the others don't. Things get even more complicated if you bought your solar panel from a different manufacturer. So here's where I leave you to your own devices. However, here are a couple suggestions.

The best place to start is to take a hard look at what you've got, then decide which is the best way to secure it to something solid, such as a piece of plywood or plastic pipe. In

the case of the unframed Unisolar module, I'd consider Velcro as a means of attachment. If you're not fussy about appearance, duct tape will work, as will clamps or brackets epoxied to the metal frame. Each of the modules recommended here are slightly flexible and won't crack or break, but you should take as much care as you can when mounting them. Whatever you do, **DON'T DRILL HOLES IN THEM!**

Once you've placed your panel in a suitable framework, you'll need to point it towards the sun. Although you can throw it on the ground or toss it on a roof and walk away and have it work, it's not a good idea. Maximum efficiency is achieved when the solar panel is facing south and tilted at an angle that's equal to your latitude plus 15 degrees. If you live in Los Angeles, the angle of the tilt will be 50 degrees (35 degrees + 15). San Francisco is 53 degrees, and Seattle is 62 degrees.


If you don't know your latitude, you can find it on almost any map. Another way to determine your solar angle is to pound a stake in the ground on a sunny day and wait for high noon (make sure the stake is straight up and down). Notice that the stake casts a shadow on the ground. At noon, drive a small tent peg into the ground at the tip of the shadow. Now run a piece of string from the peg to the top of the stake (Figure 5). This is the angle you want for your solar panel.

Of course, the length of the shadow is going to vary over the course of a year, so you may want to take the measurement around the vernal or autumnal equinox (March 21 or September 22) for best results. (The equinoxes are the days when the planet is evenly aligned toward the sun, with neither the north nor the south pole tilted toward Sol.)

After the solar panel is securely in place, run the wires to the charge controller. Be sure to observe polarity because you'll have to splice onto the short leads coming from the module.

If you're using the charge controller described in last month's Solar Workshop, set the value of Rs to 10 ohms. By the way, I made a mistake describing the calibration and operation of the controller last time. I stated that 12.6 volts was the trip point, when in fact it's 14.2 volts. Whatever made me think 12.6 volts could charge a battery to 13.2 volts is beyond me (12.6 is the nominal voltage of a 12-volt battery). Obviously, it was a typo that I perpetuated once I made it.

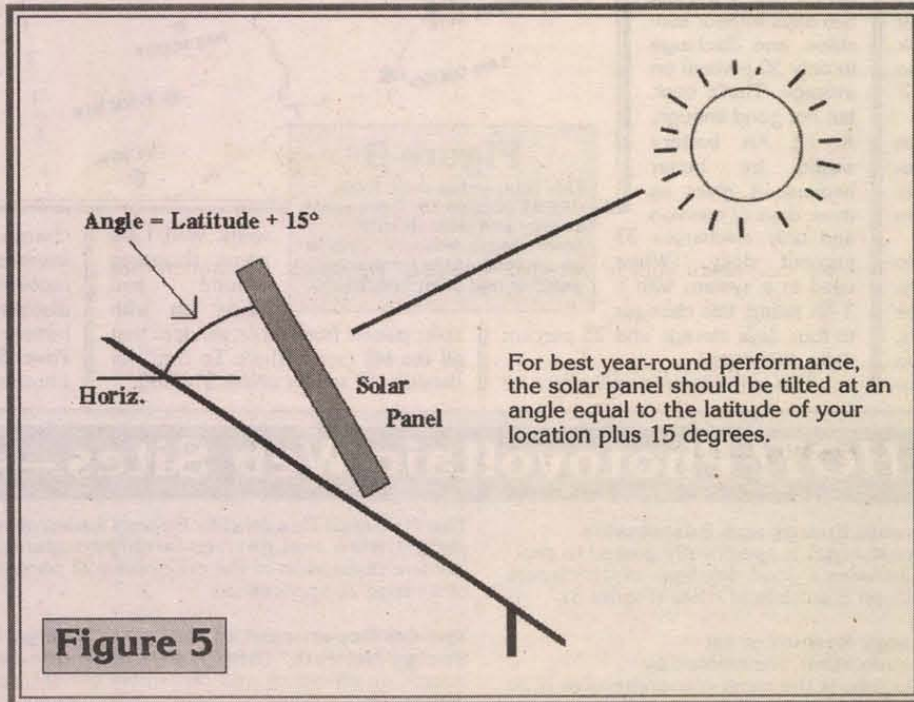With a voltmeter, monitor the voltage across the battery as it recharges. When the battery voltage reaches 14.2 volts (not



For best year-round performance, the solar panel should be tilted at an angle equal to the latitude of your location plus 15 degrees.

Figure 5

THE NUTS & VOLTS SOLAR WORKSHOP

Table 1. Solar Panel Wattage Requirements

4 Ah

Insolation Value Current (amps) Wattage @ 12.0V Wattage @ 13.2V

5.0	0.80	9.6	10.5
5.5	0.73	8.8	9.6
6.0	0.66	7.9	8.7

3 Ah

5.0	0.60	7.2	7.9
5.5	0.54	6.5	7.1
6.0	0.50	6.0	6.6

Table 2. Most Popular Module Comparisons (source: Jade Mountain)

Brand	Watts	Cost	Price/watt
Used Solarex PL110	60	\$220.00	\$3.67
Solec Specials	misc.	misc.	\$4.50
Solec 90s	90	\$445.00	\$4.95
Solec 100s	100	\$525.00	\$5.25
Solec 80s	80	\$432.00	\$5.40
Solec 55s	55	\$300.00	\$5.45
Siemens PC4	75	\$416.00	\$5.55
Kyocera	51	\$295.00	\$5.78
Solec 40s	40	\$240.00	\$6.00
Solarex MSX	60	\$382.00	\$6.37
Siemens M-55	53	\$345.00	\$6.51
Siemens M-75	48	\$319.00	\$6.65

12.6 volts as previously stated), advance VR1 until the relay just pulls in. If you decide to buy your controller instead of building it, it will come already calibrated. Charge controllers are available from the same people who sold you the photovoltaic panel.

Lastly, connect your load to the completed solar generator. Again, be sure to observe polarity if your device is polarity-sensitive (e.g., radio or TV). Now sit back and enjoy the fruits of your labor.

The Classroom

Frequently Asked Questions

I planned to give a lecture on photovoltaic theory today. You know, something about boring quantum physics and how it makes a solar cell produce electricity. But I've received so many requests from readers who are unclear on the practical aspects of solar power, that I decided the time would be better spent if I turned this Classroom session into a question and answer period. You ask the question, and I'll do my best to answer it. First question please.

1-What are photovoltaics?

Photovoltaics are solid-state

semiconductor devices that convert light directly into electricity. They're usually made of silicon, the same material used to fabricate transistors, LEDs, and microprocessors.

2-How does it work?

When sunlight hits the face of a solar cell, photons are absorbed in the semiconductor material, which pump up the energy level of the electrons in the silicon and sets them free. Metal contacts on both sides of the solar cell collect these free electrons and make them available to external devices, like motors and lamps.

As the electrons flow through these devices, they give up their energy, which causes the motor to spin or the lamp to light, and return to the solar cell where they're recycled. There are no moving parts and no materials are consumed or emitted.

3-Does solar electricity come from light, heat, or from some other force radiated by the sun?

It comes from light. While silicon solar cells respond to most wavelengths of visible light, they're most sensitive to light in the red part of the spectrum, including that which extends into the infrared region.

4-Where can I use photovoltaics?

Well, you can use the electricity

generated by photovoltaics to power any electrical device, including lamps for lighting, motors to pump water, radio transmitters, and much more. Presently, photovoltaics are finding widespread use in remote locations where conventional electricity isn't available, such as remote radio sites and vacation cabins.

5-Is there a limit to solar power?

The only limitation is the cost of the equipment and the amount of space you have for the installation. Because photovoltaics are modular, you can keep on adding as many solar panels as you wish to the array to increase the power output — well, at least until you run out of real estate.

6-What does solar power cost?

That depends on the application. Systems of 100 watts or more generally cost between \$10.00 and \$30.00 per watt at the time of installation. Smaller systems are typically more expensive — but not always.

For example, the 12-watt installation described in the Workshop costs just \$17.00 per watt. The photovoltaics themselves account for one-third to one-half the cost of any system (Table 2). The rest of the costs are incurred by the support equipment, batteries and controllers, and labor. While it's hard to compare photovoltaic costs to utility-provided electricity, the life cycle cost of solar generated energy generally ranges from \$0.30 to \$1.00/Kwh.

7-In reference to your Oct. '96 issue, can you tell me where I can buy 40-watt solar panels for about \$100.00?

You can't anymore. These were surplus ARCO Solar modules salvaged from the Lugo substation project in Hesperia, CA. These panels are now sold out. However, Carrizo Solar, the Lugo dismantler, has acquired a large number of utility grade photovoltaic modules (Solarex PL-110) from the Omniplex Museum in Oklahoma City. You can buy these 60-watt (actually, 70-watt) modules from Jade Mountain for \$220.00 each, which makes them just slightly more costly (\$3.67 per watt) than the ARCO Solar modules.

Unfortunately, they're four-volt panels, so you'll need four of them for 12-volt operation. But four modules nets you 240 watts or better, making them ideal for large power installations.

8-Do photovoltaics work on cloudy or rainy days?

Where To Buy

AAA Solar Service & Supply, Inc.
800-245-0311

<http://www.rt66.com/aaasolar>

Alternative Energy Engineering

P.O. Box 339-W
Redway, CA 95560
800-777-6609

<http://www.asis.com/ae/index.htm>

Carrizo Solar Corporation
800-776-6718

<http://www.rt66.com/carrizo/>

Jade Mountain Inc.

P.O. Box 4616
Boulder, CO 80304-4616
303-449-6601

800-442-1972 Orders only
<http://www.indra.com/jade/mtn/pv.html>

Power-Sonic Corporation

3106 Spring St.
P.O. Box 5242
Redwood City, CA 94063

415-364-5001
<http://www.power-sonic.com>

PV Resources International

1440 W. Meseto Ave.
Mesa, AZ 85202
602-897-6427

Siemens (Previously ARCO Solar)

P.O. Box 6032
Camarillo, CA 93011
805-482-6800

Sierra Solar Systems

109-N Argall Way
Nevada City, CA 95959
916-265-8441

800-517-6527 Orders only
E-Mail: solarjon@oro.net

Solar Electric Inc.

5555 Santa Fe St. #J
San Diego, CA 92109-1602
800-842-5678

<http://www.solarelectricinc.com>

Solarex Corporation

630 Solarex Ct.
Frederick, MD 21703
301-698-4200

<http://www.solarex.com/>

Specialty Concepts, Inc.

8954 Mason Ave.
Chatsworth, CA 91311
818-998-5238

<http://www.wp.com/SCINC>

Because photovoltaics respond best to low-frequency light in the red part of the spectrum, their output is only slightly affected by the weather. Typically, they can generate between 50 percent to 70 percent of their rated output under a bright overcast.

A dark, stormy day can reduce that number to 10 percent of full sun intensity, but they will still chug away as best they can. Only the cloak of night can stop them from generating electricity.

THE NUTS & VOLTS SOLAR WORKSHOP

9-What if it's snowing. Won't they freeze up?

Contrary to "practical" logic, where cars and buses grind to a halt on a snowy day, photovoltaics actually generate more power at lower temperatures. This is because photovoltaics are semiconductor devices (diodes, to be exact) which produce electricity from light, not heat. And, like most semiconductors, they operate more efficiently at cooler temperatures.

10-How about fog?

Unfortunately, fog is the fly in the ointment. Very little solar energy penetrates a heavy fog, such as you find in San Francisco and other port cities during certain times of the year. The solution is to oversize your system so that you can survive until the fog passes.

11-How about indoors?

Indoor light levels, even in a bright office, are dramatically lower than outdoor light levels, typically by a factor of several hundred or more. Photovoltaics designed for outdoor use will generally not produce any useful power under these conditions.

However, there is a class of photovoltaics designed specifically for indoor use, like the cells found on calculators, which work great indoors, but perform poorly in full sunlight.

12-I want to set up a small solar generator in my back yard, but the apartment building next door blocks the sun for most of the day. Does the collector have to face south?

Yes, south is where the power is (in the Southern Hemisphere, north is where the power is). However, you may be able to collect some rays by angling the solar panel to pick up bounced or scattered light (perhaps off a neighboring window) and gain some power there. What I'd do is ask permission to put the solar array on the roof of the offending building. Explain to the owner it's like a satellite dish, and that it does no harm. After all, you have nothing to lose and everything to gain. Good luck!

13-What maintenance is required of photovoltaics?

Virtually none, except for wiping

or hosing down the panels from time to time. But that's not even needed unless you live in an area where it never rains. If you have a battery in your system, you'll need to monitor it according to the manufacturer's instructions.

14-How long do photovoltaics last, and will my modules lose power over time?

That depends on the construction of the cell and the process used to make it. Single crystal cells (CZ) are the most stable and lose hardly any power over their 30-year lifespan.

Polycrystalline cells last almost as long, but they generally lose some of their oomph over the years (expect to see 80 percent of their original power after 20 years).

Thin film and amorphous cells have a predictable falloff in output in the first few months of operation, which slows down and stops after some time. The modules' output from then on is relatively stable.

Depending on the manufacturer, this drop-off can be anywhere from 20 percent to 50 percent. The life expectancy of a thin-film cell is in the range of 5 to 10 years.

15-Besides photovoltaic modules, what else do I need in my system?

Although a solar-powered system can be quite simple, you'll probably want no less than the minimal set-up described in this month's Workshop, which includes a battery and charge controller. In larger systems or systems that have to run AC appliances, an inverter is required. Beyond that, it's just a matter of the hardware, fuses, and wire needed to keep things together. Really, it's nothing fancy or complicated.

16-Can photovoltaics be used for space heating or heating pools?

At these prices, I wouldn't think so. If you're out in the sticks, it's cheaper to use propane for heating.

17-What do you know about photovoltaic electric cars? When will I be able to buy one?

Uh ... well, it sounds like this session is winding down. I'm sure more than a few of you still have things to do in the Workshop, so let's call it a day. See you next time. NV

LASER POINTERS & MODULES

INFINITER 300

2-1/4" L x 1/2" Ø - 650 nm
\$ 35



SUPER NBK/BBK POINTERS

5" L x 1/2" Ø - 650 nm \$ 36

ULTRA 635 nm \$ 59

SEND FOR FREE CATALOG - MANY LASER PRODUCTS AVAILABLE

INFINITER "6" POINTER

3" L x 3/4" Ø - 650 nm

\$ 30



670-650-635 nm

LASER MODULES

CALL FOR PRICING

BLACK & WHITE & COLOR VIDEO CAMERA BOARDS

- CME-255 "MINIATURE" BLACK & WHITE CAMERA \$ 75
- CME-100 SERIES BLACK & WHITE PINHOLE, STANDARD or "C" MOUNT LENS CAMERAS \$ 95
- CME-100(P) BLACK & WHITE PINHOLE or STANDARD LENS CAMERAS with MICROPHONE \$ 125
- CME-300 SERIES COLOR PINHOLE, STANDARD or "C" MOUNT LENS CAMERAS with MICROPHONE \$ 245



WE SUPPLY ALL TYPES OF CAMERA BOARDS - CALL US

2.4TRB WIRELESS VIDEO/AUDIO

TRANSMITTER RECEIVER SYSTEM \$ 160 (2 FOR \$ 150 EA.)



WIRELESS!

- TRANSMITS UP TO 500'.
- TRANSMIT VIDEO & AUDIO FROM VCR TO ANY OTHER ROOM IN HOUSE.
- USE WITH VIDEO CAMERA TO KEEP AN EYE ON "KIDS".
- HAS STANDARD VIDEO/AUDIO INPUTS & OUTPUTS.
- COMES COMPLETE WITH BUILT IN ANTENNAS, AC ADAPTERS & ALL NECESSARY CABLES.

WE CAN SUPPLY ALL YOUR WIRELESS VIDEO/AUDIO NEEDS ... GIVE US A CALL



2.4TR-CLOCK "NANNY CAM"

- KEEP AN EYE ON ANYTHING or ANYONE.
- 500' FOOT PLUS RANGE.
- VIDEO & SUPER SENSITIVE MICROPHONE.

\$ 895

COMPLETE SYSTEM

4LCD 4" ACTIVE MATRIX - BACKLIT

LCD COLOR MONITOR \$235



- 6-3/4" (W) x 6" (H) x 2-3/4" (D)
- STANDARD VIDEO INPUT
- 480(H) x 240(V) RESOLUTION

CREATIVE MICRO ELECTRONICS, INC. TO ORDER - CALL (800) 771-1295 (OUT OF NEVADA ONLY)

(702) 294-3159 (LOCAL) FAX: (702) 294-3158 (ALL AREAS) SEND FOR FREE CATALOG WE ACCEPT CREDIT CARDS




200W MINI TOWER POWER SUPPLY
Like new. Standard mounting and hookup.
92C023 \$9.95 each




STANDOFF ASSORTMENT
Popular sizes and styles used in electronics.
92J007 100 for \$4.95

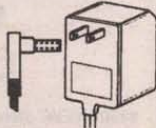9VDC, 200mA WALL WART
2.5mm x 5.0mm 90° coaxial power connector, center positive.
96E013 \$4.95



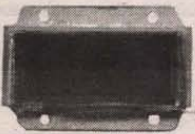HIGH SPEED SCOPE PROBE
Hewlett-Packard 10041A. 100 MHz, 9-14 pF. Includes tip accessories, adjustment tool and spec sheets.
95Z021 \$54.95 each



LIQUID CRYSTAL SHUTTER/VARIABLE DENSITY FILTER
0.5" x 1.625" active area. 0% to 23% transmission. Switching rate up to 4 KHz. Specs included.
92L012 Only \$9.95 each




TRUE NETWORKING - FAST!
DuoNet is the simplest way to get networked under Windows for Workgroups 3.11. No hassles with ethernet boards and dip switches. No need to open your computer. Just plug the DuoNet cable to the parallel ports of two computers, run the WFW3.11 network setup and within five minutes you're ready to share files, disks, CD-ROM drives and fax/modem cards, send mail and use a common scheduler. DuoNet is a full replacement for two ethernet boards, PCMCIA cards or pocket adapters. It is especially useful for notebook-to-desktop communication, since DuoNet uses any parallel port as a cost-effective built-in network adapter.
95C026 \$14.95 each



POWERFUL MAGNET
Assembly contains two neodymium magnets, approx. 0.75" x 1.75" x 0.25", which are cemented into a sturdy metal frame. Each magnet is about 300 Gauss and can pick up a ten-pound chunk of iron.
96N003 \$4.95 each



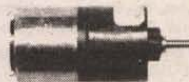HOLD-VAC® SURFACE MOUNT TOOL
This pen-style vacuum tool is delivered to you with four different size vacuum cups - ideal for handling and manipulating various surface mount components during assembly or repair operations.
HV-800 \$19.95 each



SMALL DC GEAR MOTOR
1.5" overall length, 0.625" diameter, with 0.25" long, 0.0625" dia. shaft. 144:1 gear ratio. Draws 85 RPM @ 5VDC, 25mA. Brand new!
96M004 \$6.95 each



H-P IB CABLES
IEEE-488 interface
96W009 - 2 meters \$14.95
96W008 - 1 meter 9.95



PC-COMPATIBLE MOUSE
400 DPI, 3 buttons. Drivers included.
MUS4B \$5.99 each



12VDC MINI FAN
60mm (2.375") square.
94F004 \$4.95 each



PENTIUM CPU COOLER
Miniature 12VDC 0.9W fan blows onto 2.25" square heatsink. With mounting hardware.
96C016 \$4.95 each


ALTHERNET™
AltherNet allows sharing of programs and hard disks on all PCs or notebooks that are interconnected, using the 25-pin D-SUB type cables that are included. Our parallel transfer protocol replaces serial transfer solutions and makes the data transfer faster and more reliable. AltherNet can even be used as an add-on in an ethernet networking environment.
95C025 \$19.95 each



ALIGNMENT TOOLS
Color TV-FM-AM-CB Alignment Set
Contains the following tools: .078 hex stopper type with flexible shank; .078 hex stopper type with rigid shank; 0.78 hex thru type; .101 hex stopper type with Magnavox-type screwdriver tip; .010 hex thru type; .101 metal double-tipped insulated oscillator screw adjusting tool; .025 x .156 tip non-metallic trimmer adjuster with non-metallic conical point probe; .080 square (RCA) type.
PA68-A \$4.95 each



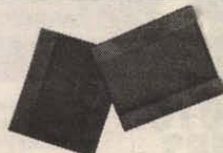SPDT POWER RELAY
24VDC, 470 Ohms, 10A, 240VAC/30VDC, 1/2HP, plug-in with 0.187 quick connectors.
96B012 \$2.50 each



GREMLIN GETTER
Tape over ribbon cable up to 50 cond. to eliminate unwanted radiation. 2.5" x 2.125" x 0.5".
96N002 \$4.95/set

UHF LINEAR AMPLIFIER
890 to 940 MHz. Gain: 17dB. Bias: 18V @ 100mA. Used in cellular communications equipment.
96W001 \$14.95 each



RUBBER FEET
Fastex brand stick-on bumpers, 0.75" dia. x 0.25" high, 42 per pad.
96Z006 \$1.50/pad

CARBON COMPOSITION RESISTORS

All Stock 5% Tolerance	
Value	Price
1/4W	\$.25
1/2W	.15
1/4W	.25
1W	.40
2W	.90

We Also Stock Power Resistors In The 3W to 200W Range.
Fax your Needs to (408) 943-9776.



TV AUDIO DEMODULATOR
Takes channel 3, 4 or 5 signal and demodulates the audio. Comes with info and schematics, and additional schematics to build add-on video demodulator board.
92A028 \$14.95 each

PHONE LINE MANAGER

Better than Caller ID! This device detects an incoming call. If you subscribe to caller ID, the unit will automatically receive and display the caller's telephone number. If not, the unit will ask the caller to enter their telephone or personal ID number. The device will then display and compare this telephone or personal ID number to a memory bank of numbers that you've installed. If the system finds a match your phone will ring. If the system does NOT find a match, the caller will be directed to leave a message. All messages are digitally recorded. No tape or answering machine necessary. New, in factory cartons, with documentation.
96U001 \$59.95 each



SUPER BRIGHT LIGHT BAR
Twenty very bright red LEDs mounted in a plastic reflector/lens housing. Measures 16.5" long by 1.2" wide. 12VDC @ 400mA operation. From auto brake light.
96L001 \$4.95 each



MINI UNENCODED KEYBOARD
Matrix-type. 43 keys. 5.625" x 2" metal frame.
96B007 \$1.49 each



HEAVY DUTY INSTRUMENT CASE

Unit splits apart for ease of access. Self-adhesive feet and screws included. ABS plastic used for flexibility and strength. Grey body complete with black front and rear panels. IC115B includes ventilation slots and speaker recess.
Order # Price Dimensions (HxWxD)
IC115A 6.20 2.5" x 8" x 6.4"
IC115B 8.20 3.1" x 10" x 7.4"



STEPPER MOTOR
400 step/rev. (0.9°/step). NEMA 17 size. 2.5 cm deep, ball bearing, 5mm dia. shaft front and rear. Front shaft has a sleeve pinned to it to make it 7mm dia. by 1.5cm long. Bipolar 70 Ohm coils. Menebea (Japan) P/N 16PY-Q203-01.
96M005 \$4.95 each

STEPPER MOTOR DRIVER IC
UCN5804. Drives a unipolar stepper in one of three operating modes: single phase, two phase or half step. Up to 1.25 Amps per phase. Step and direction input. Drive with a 555 oscillator, parallel port, etc. Build your own robot turntable for model trains, anything that requires precision positioning.
93I002 \$4.50 each
• Above, packaged with 5V stepper motor (92M010) and schematics.
93I003 \$9.95 each



ALLTRONICS

2300 Zanker Road - San Jose, CA 95131-1114
(408) 943-9773 - Fax (408) 943-9776

World Wide Web: <http://www.alltronics.com>
On-Line Ordering: (408) 943-0622 • 14400-N-8-1-24 Hrs

Store Hours: 9-6 M-F & 10-3 Sat. - Pacific
Visa, M/C, AmEx Accepted.
California Residents Add Sales Tax.
Shipping Additional on All Orders.
Prices Good 60 Days from Date of Publication



Send \$2.00 For Our Latest Catalog!
\$4.00 Foreign. Refundable on First Order.

010197

WANTED: SERVICE MONITORS. WE PAY TOP DOLLAR BY NEXT DAY FEDEX FOR USED IFR, MARCONI, MOTOROLA, AND HEWLETT PACKARD SERVICE MONITORS. ANY CONDITION, WORKING OR NOT. DON'T LOSE MONEY. CALL 1-800-476-2526 OR FAX 601-868-0133.

HP 4815A Z-METERS: Sandford Associates, the TOTAL service specialist with the HP 4815A RF vector impedance meter. Buy, sell, and restore, warranted to HP factory specs. Former HP factory tech/supv. with expertise, parts, tooling, and probe accessories. Tel/writer: 110 Highview Terr., Hackettstown, NJ 07840, 908-852-7989. E-Mail: 72540. 1345@compuserve.com

TEKTRONIX 7000 SERIES: 7CT1N curve tracer \$350. **7D20** digital storage \$700. **7L5/L3** spectrum analyzer, 20Hz-5MHz, 10Hz RBW \$1,400; with tracking generator \$1,900. **7S12, S-6, S-52** time domain reflectometer \$1,400. **7S14** 1GHz sampler \$600. Excellent condition! All with warranty. Pepper Systems, 214-353-0257.

SPECTRUM ANALYZER, HP 141T/8552B/8553B \$1,250. **8443A** tracking generator \$300. Warranty. Ridge Equipment, voice/fax 301-831-7671.

WANTED! TEST equipment. We pay top dollar for used scopes, generators, analyzers from HP, Tektronix, and others. Call Charles at Metric for immediate quotation. 1-800-432-3424.

ASHCROFT 1327D 10,000 psig portable gauge comparators includes pump, 4 test gauges, and all accessories, new \$1,000 ea., 4 available. Call 609-678-8691.

WANTED: TEST EQUIPMENT. We pay top dollar for late models of used spectrum and network analyzers, signal generators, sweepers, scopes, microwave components, waveguides, attenuators, couplers, splitters, etc. Call, fax, or send your list to: TOM at HTB ELECTRONIK, Alter Apeler Weg 5, 27619 Schiffdorf, Germany. Phone: 01149-4706-7044, Fax: 01149-4706-7049.

TEKTRONIX 475 100MHz scope, with cart, manuals, probes, viewing hood and cover. Like new condition. Recently calibrated. \$650 OBO. 815-961-1519.

WANTED: ALL MAKES OF TEST EQUIPMENT. WE WILL TAKE YOUR EQUIPMENT IN ON CONSIGNMENT OR PAY TOP DOLLAR FOR GOOD NEW OR USED LATE MODEL TEST EQUIPMENT. AMERITEK, BIRD, CUSHMAN, EIP, HP, IFR, MARCONI, MOTOROLA, NARDA, RYCOM, SMITH MYERS, TEKTRONIX, AND OTHERS. CALL 1-800-476-2526 FOR PRICING OR FAX INFO TO 601-868-0133.

SELL: HP 8640B, \$1,500; HP 3580A spectrum analyzer, \$900; HP 7155B chart recorder, \$250; HP 428B current meter and probe, \$300; HP 5328A counter, \$250; HP 5363B time interval probes, \$200; HP 537A wavemeter, \$200; HP 4800A vector Z meter, \$600; HP 461A amplifier, \$100; HP 465A amplifier, \$80; HP 4943A TMS, \$600; HP 4944A TMS, \$600; HP 432A power meter cable and HP 8478A, \$400; HP 59301A ASCII to parallel converter, \$100; HP 606A signal generator, \$300; HP 7562A log converter, \$150. A-Comm Electronics 303-290-8012, FAX 303-290-8133.

RAINBOW KITS

Many of our kits are available completely built!



WIRELESS FM MICROPHONE

Small but mighty this little jewel will out perform most units many times its price. It really stomps out a signal. The WM-2 kit is a buffered wireless

microphone that operates from 80MHz to 120MHz FM, the frequency of any broadcast FM radio. Includes a mini-electret mike. 6 to 12v DC. SIZE: 1.25" x 1"

WM-2

KIT \$14.95



MICRO-MINIATURE PHONE TRANSMITTER

We haven't seen a smaller phone transmitter than the MMPT2 kit. Powered by the phone, it requires no battery. Transmits both sides of a

phone conversation to an FM radio up to a 1/4 mile away. Tunable from 88 to 108MHz FM. Attach it to one phone or add it to the line to pick up all incoming calls. The MMPT2 is undetectable if properly installed. Unit has surface mounted parts, you install the leaded parts. Size .45" x .6"

MMPT2

KIT \$29.95



MICRO-MINIATURE WIRELESS MIKE

So small you could hide this one on some real bugs! It's the smallest we've ever seen. With it's super sensitive mike it transmits a whisper or a room of conversa-

tion to an FM radio, tunable from 88 to 108MHz FM. With a proper antenna it transmits about 1/2 mile. The kit is made with surface mounted parts, we have already mounted these parts. You install the leaded parts. Power requirement 6 to 12v DC. Size .35" x .9"

MMWM5

KIT \$34.95



STROBE LIGHT

Do you need an attention getter, warning light, or flashing light for model airplanes? Then this kit is for you. Use it as an emergency light for your auto,

radio tower, even use it on your bicycle. Has a variable flash rate. Power requirement 6 or 12v DC. Size 3.5" x 1.9"

ST-1

KIT \$11.95



FM STEREO TRANSMITTER

Own your own FM radio station. Any stereo signal you plug into the FMST-100 will be transmitted to any FM radio

tunable from 76 to 108MHz FM. Transmit a wireless link through an auditorium, from your car to your camper, listen to your CD's while mowing the lawn, Play music on one channel sing on the other. Clarity is excellent, approx. 40dB stereo separation. Length of antenna determines the distance of transmission. Complete with stereo input level controls & crystal for stereo separation. 9v battery operation. SIZE: 1.5" x 2.5" x 3"

FMST-100

Cabinet \$8.95 KIT \$29.95

TV NOTCH FILTERS FOR CHANNELS 2 thru 22 ONLY



Our TV filters eliminate unwanted TV channels or interference that alters both sound and video with a beep beep beep.

Works on cable channels (2 thru 22) only.

NOTE: All TV Filter Kits are sold for educational purposes only. You must obtain permission from your local cable company before using these filters on your cable system.

DF-222

KIT \$14.95



This Manual contains schematics, parts lists & P.C. board layouts for many of the Rainbow Kits. Use your own parts to construct our kits.

KIT BOOK \$14.95

\$9.95 with the purchase of any kit.



INDUCTANCE METER

This is the kit everyone has been asking for. Turn your digital volt ohm meter into an inductance meter. It will read inductors 3uH to 7mH. Power requirement 9v DC. SIZE: 1.75" x 2.5"

IA-1

KIT \$14.95

IA-1 CABINET \$8.95



DIGITAL THERMOMETER

The DT-3 kit will turn your digital volt ohm meter into an accurate digital thermometer with .1 degree resolution. Measure temperatures from -40° to 250°F. The remote sensor is .25" sq. and can be mounted many feet from the meter. Power requirement 9V DC. SIZE: 2" x 1.35"

DT-3

KIT \$8.95



CAPACITANCE METER

This kit will turn your digital volt meter into a capacitance meter. Turn that junk box of unmarked capacitors into a fortune of usable parts. Measure capacitors from <2.2pF to 2.2uF. Power requirement 9v DC. SIZE: 1.80" x 2"

CA-1

KIT \$12.95



ELECTRONIC RAINBOW

Please add sufficient postage First lb \$5.00 Canada \$7.00 Additional LB. Add \$1.00 US FUNDS ONLY We will accept telephone orders for Visa or Mastercard

Electronic Rainbow Ind., Inc.
6227 Coffman Rd. Indianapolis, IN 46268

CALL 317-291-7262 FAX 317-291-7269
INTERNET: www.rainbowkits.com

TEMPERATURE GENIE

Ever lost frozen food because your freezer stopped? The TC-2 kit would have saved you money. An alarm activates when the temperature reaches a critical point. Turn ceiling fans on automatically when it gets too hot. This kit gives you 100mA of output. SIZE: 2" x 1.4" Power requirement 6 to 15V DC.

If you want to switch more power see our Triac (TP-1) or Relay (RP-1) Power kit.

TC-2

KIT \$7.95



PHONE TRANSMITTER

Small but mighty, it fits anywhere. Phone line powered, never needs batteries. Transmits both sides of a phone conversation loud and clear, wireless, to any FM radio at

great distances. Variable tunes from 70MHz to 130MHz FM. You can also use it as a speaker phone. SIZE: 1.25" x .6"

TEL-B1

KIT \$12.95



SUPER SNOOPER BIG EAR

Listen through walls, hear conversations across the room. Add a parabolic reflector and hear blocks away. The BIG EAR can be hidden about

anywhere. Makes an ultra sensitive intercom. Can be used as a 1.5W AMP. We supply a mini-electret mike in the kit. Power requirement 6 to 12v DC. SIZE: 1.75" x 1"

AA-1

BUILT \$29.95

KIT \$10.95




RELAY POWER KIT

Increase the output of any kit from 100mA to 3 Amps If you need to switch more power, up to 300 Watts, with the Light Genie,

Temperature Genie, Timer or Vox kits, use the Relay Kit. We supply a two pole relay 1.5 Amps ea., tie both poles together and get 3 Amps. Size .75" x 2"

RP-1

KIT \$9.95

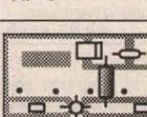

WIDE BAND PRE-AMP

Uses PCB and surface mount technology for better performance. Use for scanners, HT's, Frequency counters, Satellite Receivers. It amplifies low-level (weak) signals. If the signal is extremely low, two amplifiers can be used in a series.

- 1MHz to 2.5 GHz 2.8dB NF
- 1dB compression=OdBm
- Gain: 1MHz- 20dB to 2.5GHz-6dB
- Power requirement: 12v @ 6Ma

WBA-6

KIT \$19.95

\$250! NEW! stereo microscopes. Dual magnification 10 and 30X with dual lighting. Larger with 5 year warranties are \$325. Full line of new scopes available. Seabird Technical, 3580 Haven, Redwood City, CA 94063. 415-367-8320 Fax 415-365-5845. Visa/MC.

CALIBRATION EQUIPMENT. FLUKE DC reference standard \$200; CABLESCAN AHT-200C cable tester 200 pin \$95; Electronic Association 25163X standard capacitor 100 UF \$350; General Radio 1454AH 4 dial 100K precision divider \$50; Narda 8100B RF radiation monitor, complete test set \$200; Marconi TM6221 bal/unbal test transformer 10/20/600 \$50; radar range calibrator, military TS1787 \$325. Hewlett Packard late model 745A AC calibrator, opt. H18 \$350 with 746 amplifier \$500. Wika E4887 standard pressure gauge 200 psi \$75. Psitech Plus 707-745-4804 request bi-monthly fax listings, Fax 707-747-5277.

HIPOTS & OTHERS Slaughter 103.10.0 opt EJU AC HIPOT 0-10 KV @ 10mA \$450; 6265B 0-40V 0-3A \$250. DEL EBS 30-1-2, 0-30KVDC 0-2mA digital power supply w/complete documentation \$425. All as new. Psitech Plus 707-745-4804.

FED-LOG on CD-ROM. Have you wondered what all those numbers were on government sales catalogs? Now be able to identify all government stock numbers for price, mfg., part number, description. \$350 a set. Call TJ's Wholesale Surplus 904-897-6482.


POWER SUPPLIES, ETC.: HP 6237B triple output: 0-18V, 1A; 0-20V, .5A dual tracking \$425. HP 6253A 0-20V, 3A dual tracking \$300. HP 6255A 0-40V, 1.5A dual tracking \$350. HP 6443B 0-120V, 2.5A \$375. Tek PS 503A \$195. Xentek extreme isolation transformers for CLEAN POWER: 5KVA, 2.5KVA, etc., starting at \$195. Excellent condition, warranty. Pepper Systems, 214-353-0257.

SUCTION DESOLDERING stations: (pump built-in) Pace PPS100A rework \$250; Weller DS1000 perfect new head \$450, \$250 (read-out NG); Ungar 4000 mint \$250; Edsyn VP300 \$250 (= to Hakko); APE EX501 \$400 (= to Pace MBT 201A); Unger 2000 \$150 (ext. air); SMD removal: Mesei hot tweezer \$75; Raychem hot air pencil \$200, \$150 thermal wire stripper for \$25; soldering stations: Hexacon \$45; Weller WTCN \$35 to \$65; WTCN \$50; EC2000ESD \$100; EC2001ESD \$150. Jim Weller 310-515-2058.

WATT METERS: B&W 334-A includes 1KW dummy load \$79; Triplett 360-G \$24.50; Heath IG5206 video alignment gen. \$39; Shalco T-693 precision audio attenuator \$139; Vector WR-50C signal gen. \$79; Beckman Scopemate II \$159; Tek 1230 logic analyzer \$490. Synergetics Surplus, 3860 West First Street, Box 809, Thatcher, AZ 85552. 520-428-4073. synergetics@tinaja.com VISA/MC.

INSTRUMENT SALE: HP 5328A universal counter with 500MHz option only, \$375. **HP 8413A** phase gain indicator \$165. **HP 1122A** probe power supply \$75. **HP 5554A** preamplifier \$60. **HP 5381A** 80MHz counter \$65. **HP 8750A** storage normalizer \$275. **HP 4944A** transmission impairment test set \$350. **Fluke 8100B** digital meter \$80 shipping and COD extra. Misc. spare parts HP test equipment. Request list 415-842-3268 Fax: 510-389-4780.

FILMOHM 7147 step attenuators 1-110 dB, 0-250 MHz, 75 ohms, \$80; Honeywell 1858 Visorder with plug-ins, \$600; Grayson Stadler 1701 audiometer, \$300; GR1925 multimeter, \$400; HP140T, 8554B, 8553B spec. analyzer, \$1,500; HP 8016A, word generator, \$500; HP 8018A serial data gen., \$500; HP 8006A word gen., \$150; HP 8406A comb. gen., \$500; HP 2225A, printer GPIB, \$100; Phillips 6672A 1GHz counter \$450; EIP 371 source locking counter 18GHz, \$1,200; Pulse Instruments PI 5800A data generator, \$800. A-Comm Electronics 303-290-8012.

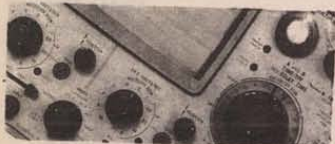

50MHz SCOPE BARGAIN Tektronix 453, solid-state. Dual trace. Sensitivity=5 millivolts. Excellent condition. manual copy. New probe. \$295 (this month only). Gary N6ZD, 408-385-0301 VISA/MC.

LABORATORY INSTRUMENT SYSTEM, LABVOLT. Contains DC amp/voltmeter, sine/squarewave generator, AC power supply, DC power supply, multifunction meter, \$185 ppd; TEK 75 ohm in-line termination, BNC, \$15 ppd; GENRAD 1396B tone burst generator, \$65 ppd. Morgan Test Equipment Sales, Equipment Division. Ph/Fx 717-842-5590.

WANTED: RADIO service monitors, IFR, Motorola, Marconi, HP signal generators, spectrum analyzers, and late model HP equipment. 716-763-9104 or 716-661-9964. Fax: 716-763-0371. <http://www.netsync.net/users/amtronix>

POOR MAN'S Spectrum Analyzer/Monitor Receiver Kit. 2 to 1,700 MHz. Basic kit only \$78. Now available with switched resolution filters, tracking generator and direct digital frequency readout. Works with ANY scope or IBM compatible computer. Send stamped envelope for details. Science Workshop, Box 310B, Bethpage, NY 11714.

TEST EQUIPMENT FOR SALE/WANTED: RF, microwave, video and fiber optic, cable TV, broadcast TV, satellite and related industries. Wavetek, Tektronix, Hewlett Packard and other manufacturers. Spectrum analyzers, signal level meters, sweep systems, TDRs, OTDRs, and much more. PTL Cable Service. Phone 407-747-3647, FAX 407-575-4635.

WANTED: USED electronics repair work benches/stations in nice condition will pick-up in MD area. 301-419-3189.

TEK 465M 100MHz oscilloscope \$295; Tek 454 150MHz oscilloscope \$195; Tek 464 100MHz storage oscilloscope \$275; Tek 475 200MHz oscilloscope, \$395. ISA, PO Box 6955, Laguna Niguel, CA 92607. 714-488-0288, Fax 714-488-0010.

FREQUENCY COUNTER HP 5245L DC-500MHz, excellent condition. Meets NIST calibration. \$400. 909-469-9100.

FLUKE CALIBRATOR Model 515A \$900; KROHN-HITE 3202R tunable filter \$250; General Radio 1390B random noise generator \$75; Tektronix 178 curve tracer adapter \$175. Hewlett Packard 4815A RF vector impedance meter \$200. Psitech Plus 707-745-4804, Fax 707-747-5277.

HUNTRON TRACKER model 2000 with model 410 switcher, manual and some IC cables. \$1,200 OBO. Dan at 206-743-4814.

TEKTRONIX 7104A 1GHz oscilloscope \$1,575. Psitech Plus 707-745-4804, Fax 707-747-5277.

Toner Cartridge Recharge



& Laser Printer Supplies

Three Ways to Earn Cash

You Do It

Dealer Program 1

You do the recycling work, and we'll supply all the materials, training, and technical support.

- Supplies cost from \$6 each
- Free Directions
- 1 Free Video Training Tape
- Starter Kit-approx. \$500 supplies for 36 recharges
- For complete information, see Fax document# 2040*

We Do It For You

Dealer Program 2

You ship us your customer's toner cartridges and OPC cartridges, and we'll recycle them at a reduced price for you.

- Attractive Marketing Flyers with your name available
- Fast Turnaround
- Generic Packaging
- See Fax document# 2092*

We Do It For Your Customer

Dealer Program 3

You recommend us and give literature with our name to your customer. We'll deal direct with your customer. You have your code on our prepaid shipping label.

- You earn commission
- You recommend us
- Prepaid UPS shipping labels
- For complete information, see Fax document# 2090*

*To obtain Fax documents, use our Fax-On-Demand system.

Call 516-467-0772 from any Fax machine equipped with a touch-tone phone, 24 hrs/day, 7 days/week. Dial document# 4633 for an index.

Chenesko Products Inc.

2221 5th Ave., Suite 4, Ronkonkoma, NY 11779

Phone: 516-467-3205 E-mail: chenesko@aol.com

Fax: 516-467-3223 Fax-On-Demand: 516-467-0772

800-221-3516

Write in 111 on Reader Service Card.

WHOLESALE CABLE BOXES


CONVERTERS · FILTERS



Call Us To Satisfy All Of Your Cable Equipment Needs!

WE CARRY ALL THE MAJOR BRAND NAMES!

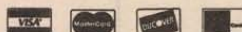30 DAY MONEY BACK GUARANTEE!
1 YEAR WARRANTY



Call Now and Take Advantage!!!

MODERN ELECTRONICS
1-800-906-6664

2125 S. 156TH CIRCLE • OMAHA, NE 68130

VISIT OUR WEB SITE

http://www.tiac.net/users/online/modern_electronics

Write in 198 on Reader Service Card.

WANTED: HP 5062C any condition, other atomic standards any make. For sale: Tracor 308A rubidium, Efratom M100 rubidium, FT 54050 cesium plus others. Please inquire! Corby Dawson 805-736-0288.

HP 3550B telephone test set, new in HP boxes w/manuals, \$145 ppd; 30dB attenuator, minicircuits, BNC, DC-1000MHz, \$13 ppd; ALAN 15dB BNC attenuator, DC-1000MHz \$12 ppd. Morgan Test Equipment Sales, Equipment Division. Ph/Fx 717-842-5590.

WANTED: BRUEL & Kjaer 4153 artificial ear, microphones, couplers, connectors, cables, etc. for acoustics. Fax info to James Welsh at 616-396-0092 or mail: 225 W. 30th St., Holland, MI 49423.

FOR SALE: Fluke 5100B calibrator with opts. 03 & 05, late model, 60-day guarantee, \$6,000. HP 8640B signal generator with opts. 001, 002, \$1,750. Many TEK plug-ins and oscilloscopes, \$200 and less. CALL 908-681-2032.

RF EQUIPMENT in top condition: **HP 8640B** signal gen. w/options 001, 002, 003; **8444A** tracking gen.; **141T** spectrum analyzer w/**8554B** RF & **8552B** IF sections (recently calibrated); current market over \$7 K. Sell all for \$5,500. Call 410-381-7970, ask for Marc 9-5 EST.

WANTED: LATE MODEL TEST EQUIPMENT (Tektronix, HP, Fluke). Also we buy test equipment manuals, catalogs. Pepper Systems, 214-353-0257; 214-902-9511 FAX.

FOR THE BEST PRICES ON PROFESSIONAL TOOLS, CALL ELECTRO-TOOL



platt - Case - Deluxe Polypropylene. Chemical Resistant. Tools by CooperTools and others. 800T Case, complete with tools... \$389.99
800T Case Only... \$114.80




platt - Case - Cordura Exterior. Two exterior pockets & one literature pocket. 660ZT Case, complete with tools... \$208.00
660ZT Case Only... \$57.40
Optional Sperry meter #DM6510 as shown... \$63.95



Weller WCC100 - Electronically controlled station, temperature adjustable from 350°F-850°F. Zero voltage circuit-safe for sensitive components, 40 Watt pencil... \$92.00

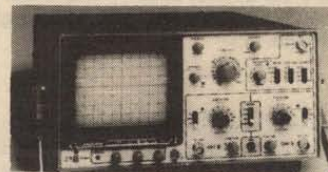OptiVISOR - Superior magnification, Optical Glass Prismatic lenses, (not plastic) Select any one of (6) magnifications... \$22.50



GoldStar - 20 MHz Dual Trace Oscilloscope OS-9020A-Large 6" rectangular, high sensitivity: 1mV/div, high accuracy: ±3%, stable, low-drift design, 8 divisions of displayed dynamic range and accurate, distortion-free waveform measurements... \$370.80

Electro Tool, Inc.

9103 Gillman, Livonia, MI 48150
Customer Service: (313) 422-1221
ORDERS ONLY: 1 (800) 772-3455

"Tools American Made."



Write in 33 on Reader Service Card.

HELP WANTED: Technician wizard wanted to perform repair and calibration of general purpose electronic test equipment. Move to the uncrowded mountains north of the wine country in northern California. Pay commensurate with ability. Call Roger at Naptech, 1-800-336-7723.

WANTED: COLLINS radio 40K-1 and Motorola Model 1011 frequency standards or any other early "precision" frequency standard ca 1920-1950. Bill Scolnik, 1-800-634-7036 or fax 201-405-1706.

DATA PRECISION 6000 FFT waveform analyzer, 610 plug-in, GPIB, RS-232, plotter options, manual, \$900. Fluke 45 dual display DMM, 5 digits, true RMS, RS-232 I/O, manual, \$400. 505-988-5233.

ELECTRONICS

Q & A

With TJ Byers

In this column, I answer questions about all aspects of electronics, including computer hardware and software. This column doesn't replace the Tech Forum that you've grown to love and support. Instead, it will supplement it, so feel free to participate as always with your questions and answers. You can reach me on America Online at TJBYSERS, on the Internet at TJBYSERS@aol.com or by snail mail at *Nuts & Volts Magazine*, 430 Princeland Ct., Corona, CA 91719.

Notebook Needs More Space

Q. I have a Toshiba T2200SX notebook with an itty-bitty 80 MB hard disk. Can I upgrade the hard disk to a bigger one? Ideally, I want to remove the internal one and replace it with the new one.

Hal N. Nguyen
via Internet


A. You have a couple problems here, in that this is a pretty old notebook and I'm not sure the upgrade is money well spent. Yes, you can replace the old hard disk with a new one — but I wouldn't tackle that task unless you've done it before. Cracking the shell on this system isn't easy (lots of hidden screws and wires), and once you get it open, you need to gingerly take out the old hard disk and insert the new. What I suggest is taking it to an expert, like Precision Digital Services (800-216-5525; <http://www.pdsusa.com/t2000.html>). For \$325.00 they'll upgrade you to 350 MB and for \$895.00 they'll install a 2.1 GB hard disk, postage included. If you think you can handle the mechanics, you can probably do the upgrade to 1.2 GB yourself for about \$350.00. However, you might want to consider putting this money towards a new Pentium notebook, instead.

Sequence Timer

Q. I'm looking for a circuit that would provide a cascaded string of 10 timers with different delay off and on times. Each stage would consist of two timers: one for delay and one for power on. I'd like each timer to be pot adjustable from two seconds to about five minutes. As a final request, I'd like to have a switch which would enable me to route the output of the final timer so that it could start the cycle all over again. If this is too complex a design, or beyond the scope of your 555 "Timer Wizards," I'd be glad to pay someone to provide me with this design.

Don Fleshen
Sterling, VA

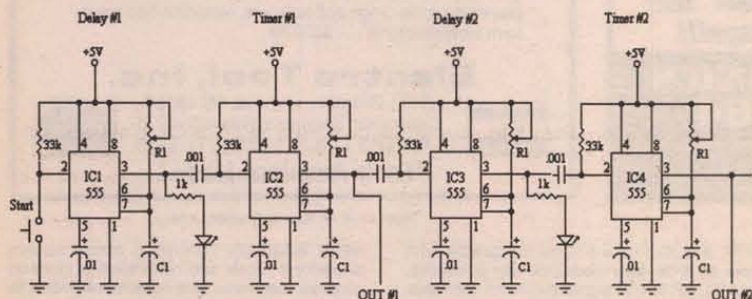A. Great, send me a check because here it is! Just kidding. How about a check to the subscription department and a kind letter to my editor. This design is based on the 555 timer, and is relatively simple to construct and use. I only included two stages, but it's easy enough to expand this to as many stages as you wish.




IC1 is the first delay timer. When it expires, it triggers IC2, which can now power whatever you want using logic output #1 to drive a transistor, relay, or other device. (Just for fun, I've connected output IC1 to an LED so that you can see where you are in the sequence, in case you get lost.) At the end of IC2's cycle, IC3 is triggered, which now pauses for whatever time you set the potentiometer for, after which IC4 kicks in ... well, you get the picture. If you want this to be recursive, simply provide a path from the last stage to S1. To reduce part count, use a 556 chip which contains two 555 circuits. If you need more precise timing, you'll have to go to a digital design, in which case you can get your checkbook ready.

Solar Satellite Dish

Q. I just bought an old C-band satellite dish hooked up to a Toki receiver that I'd like to convert to solar power. I've already taken the first step by buying a 2.25W panel from Electronic Gold Mine, but I'm not clear on how to hook it up to my 12-volt battery that provides the power to turn the dish. The dish has a Dayton DC model 4Z14S motor driving a worm gear to turn this dinosaur, and I would like to be able to switch directions inside the house, which I do now by just reversing the wires from a 12-volt, 2A power supply.

Craig Hueser
Clovis, CA

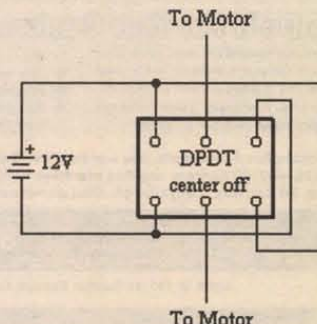

A. The first part of your question is answered in this month's Solar Workshop beginning on page 40. To reverse the motor remotely, I'd use a pair of DPDT relays installed at the antenna site and two momentary push-button switches inside the house. Unfortunately, the parts will cost about \$25.00, which is half of what you paid for your dish, so here's a simpler circuit using a \$3.00 Radio Shack switch (275-709 or 275-710).

DOS Invasion Stopped

Q. How do you prevent someone from shelling out to DOS while in another program (for example, pressing CTRL-F1 in WordPerfect)? This could mean the destruction of my machine if I can't stop it (security reasons).

Garrison Tuerack
Glendale, NY

A. You can't. However, I have two possible solutions that may curtail persons from messing with your PC via DOS. First, you can limit their access by using passwords that you find in Windows 95 (look under Start/Help/Index/Password). Encoding files or making them read-only is another method. Secondly, if this is such a threat to you, what I'd do is give this person his or her own computer terminal and link it to yours via LAN (local area network) or modem. That'll certainly stop him dead in his tracks.

Solar Panels For Sale

Q. In reference to your October Q & A response "Solar Powered Sprinklers," please tell me where I can buy 40-watt solar panels for about \$100.00.

C.H. Nelson
KA6ZWM

A. Check out this month's Solar Workshop on page 40.

Ohmmeters And Lies

Q. The power source for my "Olympus cold light supply" model ILK-5 has a bad power supply. The power supply looks very similar to that found in a PC as far as the layout goes, and I've even tried to use the repair tips put forth in your September 1996 article on repairing PC power supplies, but to no avail. I am not sure of the correct resistance values for the transformer windings, which I suspect is the culprit. Any suggestions will be helpful.

David Johnson
via Internet

A. Well, your ohmmeter won't tell you whether the transformer is good or not because the resistance is so low that it can't indicate a shorted winding. Given the fact that transformers seldom go bad, I'd look elsewhere first — mostly at the semiconductors. If memory serves me right, cold-light power supplies use a high-kick boot to ignite the tube. It could be that your tube isn't getting the kick it's looking for, which is why there's no light. Again, zero in on the semiconductors; if in doubt, replace them, it's cheap enough. BTW, are you sure the lamp itself is good?

DTMF Decoder

Q. I have a small airplane that has a engine heater pad attached to the oil pan which uses approximately 300 watts of power. I'd like to be able to remotely turn it on and off via my two-meter transceiver using a tone signal. I live only


a few miles away and my base station has a strong signal at the hangar where the airplane is. What I'd like too, if possible, is to be able to tell the status of the heater (either on or off) from my home.

**Tom Hale
Cotuit, MA**

A. Using a single tone to remotely trigger your heater isn't a good idea because your receiver is likely to run across that tone many times during the course of a day. A better solution is to use touch-tone telephone sounds, or DTMF. Basically, DTMF codes are two tones which, when combined, represent the numbers 0 through 9 plus a star and pound key, as shown in the table below.

Frequency	Designation	R1	Character	DTMF Code
697 Hz	A	13K	1	A + E
770 Hz	B	11.8K	2	A + F
852 Hz	C	10.7K	3	A + G
941 Hz	D	9.7K	4	B + E
1209 Hz	E	7.5K	5	B + F
1336 Hz	F	6.8K	6	B + G
1477 Hz	G	6.2K	7	C + E
			8	C + F
			9	C + G
			0	D + F
			*	D + E
			#	D + G

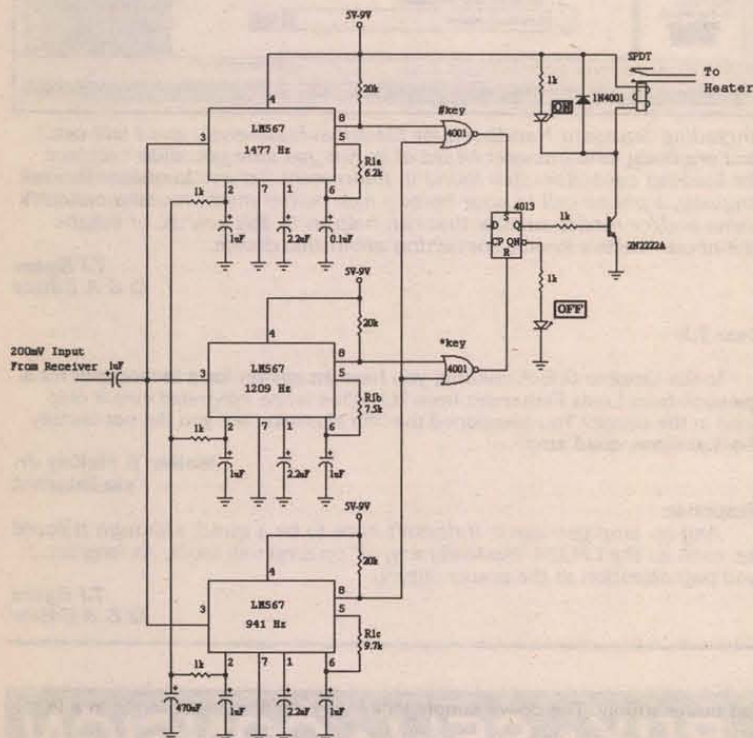What you do is send these codes from your house to the hangar by simply holding the transceiver's microphone to the earpiece of a telephone while you press the desired button. At the receiving end, you'll need a DTMF decoder, like the one shown below, connected to the audio output of your rig.




I've designed this circuit to respond to the pound and star keys of your phone pad. To turn the heater off, press star; to turn it on, press pound. If you'd rather use a different key combination, simply replace R1 with the values shown in the chart above. Because of variations in the 0.1 μ F timing capacitor, though, you may need to trim the resistance a bit to get your receiver to respond properly (I suggest a potentiometer in series with a slightly lower value resistor). I couldn't come up with a simple solution for checking the status of the heater (one that doesn't involve keying the receiver's mike or dialing a phone), so I added a couple LEDs to the circuit so that you can see the status of the heater when you walk into the hangar (sigh). By the way, this design will work in other applications to activate or deactivate appliances and other items. In fact, you can have up to 12 separate commands by simply adding more LM567 decoders of the right frequency and the proper logic gates. This circuit alone can have three responses by adding another NOR gate to detect the number "0," a fourth LM567 and three more NOR gates will net you six commands. Have fun flying!

Security Alarm Unarmed

Q. I would like to ask a question regarding a security circuit, specifically one that can turn on an alarm from a sensor input then turn off the alarm after a given time. The catch is that I want the alarm to turn off after about a minute, but I don't want it to trigger again for about four minutes – regardless of what the sensor does during this four-minute "cooling-off" period.

**Paul Hazelman
Cherry Valley, CA**

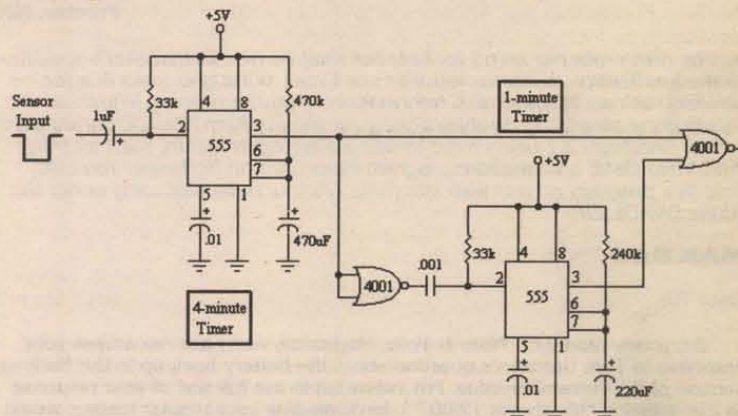A. One of these days, I really have to compile an article of the 555 designs I've put together over the years. Meanwhile, here's one that'll work for you.



It uses two 555 chips: one with a four-minute time-out and the other with a one-minute time-out. When the sensor triggers the four-minute timer, its output starts the one-minute time. The 4001 NOR gate now goes low and sets off your alarm. After one minute, the one-minute timer times out, and its output goes low, which causes the alarm driver to go high. This is how the circuit will stay until the four-minute timer times out, after which the alarm can again respond to sensor stimulus.

Electronic Barometer

Q. Can you tell me if an electronic barometer kit or assembled unit exists which uses a pressure sensor chip and RS-232 output? I want to plug this into my Sun Sparc5 and program it to give a reading every 30 minutes.

**Donald F. Parsons
via Internet**

A. Jeeze, I don't know where to begin to answer this question, because many, many vendors have products that fall into this category. If I read your question right, though, I think what you're looking for is a unit that detects and reports changes in weather conditions. If this is the case, I've located two promising candidates.

AgriWeather, Inc.
800-584-9331

<http://www.agriweather.com/NIMDIG.htm>

Druck, Ltd.
England

<http://www.druck.com/index.html>

Too Hot To Handle 486DX4

Q. I have an intermittent problem with a dedicated MPEG audio playback system I'm trying to put together. The project involves a couple dozen systems built around a popular Taiwanese 486DX4-100 motherboard mounted inside a conventional enclosure, and nearly all systems exhibit the same problem – which is two fold. First, during play, the computer will sometimes quit playing and refuse to boot. If I reseat any of the cards or even lift the PC a couple inches and drop it, the unit boots and will continue to run for hours, days, or weeks before the problem occurs again. Second, on occasion, the audio drops out for a few seconds and then returns. This, too, happens on the same infrequent basis. The systems consist of just a dedicated MPEG decoder, 2 MB of RAM, CD-ROM, and a serial port; there's no keyboard, disk drive, or video display. I don't get it.

**Boyd Collings
via Internet**

A. To begin with, the 486DX4 is a hot chip – literally. This sucker gets hot enough to fry an egg when it's going full blast, which I assume it must do from time to time as it wades through your MPEG files. Therefore, I think heat build-up is your problem. During times of stress, the chip will expand slightly, which could cause a misalignment of the pins in your ZIF socket. By turning the system off to tinker with the adapter cards or

to drop the system on the table gives the geometry time to realign itself through cooling or shock (the drop). If the chip doesn't already have its own cooling fan, get one. Next, make sure there's an unrestricted flow of air across the chip at all time; e.g., no cables or cards blocking an air path. Finally, you might want to consider adding an extra cooling fan to your cabinet. They're cheap and easily installed.

Viewing Application-Specific Files

Q. My son disappeared along with all his personal papers. I believe his records are still on computer disks. Is there any way to unlock the code to retrieve the information?

**Phil Clock
Proctor, MN**

A. The files probably aren't locked, but may be in a format that's specific to the application, such as WinWord or Excel. What you need is a file viewer that can decipher this information. If you're running Windows 95, this is done simply by double-clicking on the file from Start/Programs/Explorer. Windows 3.1 users need to use a viewing program, such as Drag And View Gold, a shareware program from Canyon Software. You can find this program on our Web site (<http://www.nutsvolts.com>) under the name DVAOL.ZIP.

MAILBAG

Dear TJ:

I'm a new reader of *Nuts & Volts Magazine*, and I just ran across your response to Tom Harrison's question about the battery back-up in the Mailbag section of the November issue. I'm interested in the full text of your response to the question "It's always 12:00." I don't imagine your regular readers would want to see reprints of old questions, so I'm wondering if you can E-Mail me the original response? If not, I'll understand.

**Eric Bonnie
via Internet**

Response:

At some point, (hopefully after the Holidays), we plan to have the *Electronics Q & A* column on our Web site (<http://www.nutsvolts.com>), but until then I suggest you buy a back issue for that month. Not only will you find the answer to your question, but a lot of other great features, too. The cost is \$5.00 each prepaid and includes postage for delivery inside the US. (P.S.: Please don't tell any one that I sent you that file via E-Mail.)

**TJ Byers
Q & A Editor**

Dear Mr. Byers:

I wrote you last month asking if you knew the formula for fluorescent capacitor ballast values. Your reply was they won't work as a ballast. The reason I asked was because I bought a twin-lamp F40 shop light in 1985 that went very noisy after just a few months and, upon pulling it apart, I discovered that it had a paper/foil capacitor of the cheapest quality money can buy instead of a ballast transformer. After measuring its value with my digital capacitance meter, I replaced it with an exact value and everything worked fine. Unfortunately, I sold my house with the lamp still attached and I can't remember the value of the capacitor. I would appreciate it if you could research your data base on this subject.

**Chris
Bieber, CA**

Response:

Well, I did another search of my data bases and engineering manuals


Reader's Tip

Do you know what ATAPI means, or how it applies to your computer? If computer jargon confuses you, check out PC Webopaedia Lite from Sandy Bay Software at the address below. Here you'll find computer-related definitions from the excellent Random House Personal Computer Dictionary in Windows help file format, for free! The help file contains clear, concise, and up-to-date definitions of nearly 2,000 computer terms with 70 illustrations and 30 tables. What's more, the PC Webopaedia Web site is linked to thousands of other Web pages containing related information and up-to-the-minute additions.

Sandy Bay Software

<http://www.sandybay.com/pc-web>

**J. Golomb
via America Online**

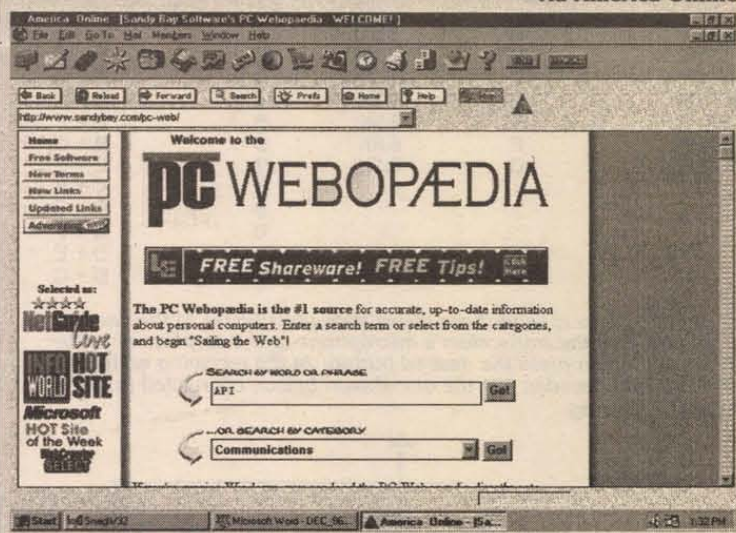

(including Standard Handbook for Electrical Engineers), and I still can't find anybody who has ever heard of it. Are you sure you didn't replace the lead-lag capacitor often found in fluorescent fixtures to reduce flicker? Anyway, a phone call to your home's new owner might reveal a vendor's name and/or model number that can help us in this search, or maybe one of our readers knows something about this device.

**TJ Byers
Q & A Editor**

Dear TJ:

In the October Q & A column, you have an answer for a tachometer for a question from Louis Fernandez from N.J. What is the integrated circuit chip used in the circuit? You mentioned the 555 alternate, but you did not identify the, I assume, quad amp.

**Walter T. McKay Jr.
via Internet**

Response:

Any op amp you want. It doesn't have to be a quad, although it could be, such as the LM324. Basically any ol' op amp will work, as long as you pay attention to the power supply.

**TJ Byers
Q & A Editor**

EZ-EP DEVICE PROGRAMMER - \$169.95



INEXPENSIVE - Best programmer under \$200.
PORTABLE - Attaches to PC parallel port.
FAST - Programs 27C010 in 23 seconds.

VERSATILE - Supports devices 2716 thru 27080 plus EE and Flash to 32 pins. Reads and writes binary, ASCII hex, Intel Hex, and Motorola S formats.

SERVICE - Information and software updates via BBS or voice. 30 day money back guarantee.

ADAPTERS for additional devices are available.

EP-51 (8751,C51)	\$39.95	EP-PIC (16C5x,61,71,84)	\$49.95
EP-51-PLCC	\$59.95	EP-750 (87C750,751,752)	\$59.95
EP-SOIC28/32	\$49.95	EP-SEE (24xx,93xx Serial EE)	\$34.95
EP-11 (68HC11)	\$59.95	EP-16 (16bit EPROMs)	\$49.95
EP-55 (8755)	\$39.95	EP-49 (8742,48,49)	\$49.95
EP-PLCC32	\$49.95	EP-PEEL (18v8,20g10,22v10)	\$59.95

M2L ELECTRONICS 310/837-7818
3526 Jasmine, Suite #4 Mon-Fri 9-5
Los Angeles, CA 90034 BBS/FAX: 310/841-6050

URL: <http://www.cs.ucla.edu/csd-grads-gs3/loving/www/m2l.html>
CA - add 8.25% tax. UPS Ground - \$5; 2 Day - \$10; Overnight - \$17 CDD \$4.75

BUY • SELL • CONSIGN

WANTED

- Electronic Test Equipment
- Electronics Inventory
- Scientific Equipment
- Mfg. Shop Equip.
- Data/Telco
- Memory

DEXIS

9749 Hamilton Road
Eden Prairie, MN 55344

We Sell
Nationwide!
Call our Fax-On-
Demand System, or our
Internet site for current availability.
Visit our 25,000 sq. ft. showroom warehouse
M-F 9 to 6; Sat 9 to 5

PHONE: (612) 944-7670
INTERNET: WWW.GO2DEXIS.COM
FAX: (612) 942-9712 • FAX-ON-DEMAND: 1-800-547-4636 X 300

TEST EQUIPMENT cont.

HP 400EL AC voltmeter \$95. Also misc. PD & HP power supplies. Ed Matsuda 619-479-0225 E-Mail: ematsuda@themall.net

BATTERY ANALYZER with PC interface. DOS or Windows software \$279. **LaMantia Products**, 1136 Aldersbrook Road, London, ON, N6G 2X8. 519-472-5566 Fax 519-472-1702.

MANUALS, HP, Tektronix, Fluke; over 1,500 in stock. Call or write with specific needs. Also used test equipment. Allen Fulmer, 2538 Sweetgum Way, West Clearwater, FL 34621. 813-796-3424.

WAVETEK 3001 generator, new cal. \$550. Cushman CE 15 spectrum analyzer, new CRT \$1,000. 414-769-3227.

TEST EQUIPMENT: TEK/SONY 305-DMM SCOPE W/DMM BATT PWR XLNT \$350, TEK 5441 \$450 DC509 \$250, DM 502 DMM \$50, TM 506 CHASSIS \$125, Fluke 335A volt std \$300, 8000A DVM w/o-ohms and Ni-Cad \$60. Four Designs Co. 360-887-1555. VISA, MC, AMEX, DISCOVER.

WANT: V1380 CRT for Tek 475 scope. Griffith, 476 Keenan Ave., Ft. Myers, FL 33919. 941-481-6499.

HP 8900B PEAK power calibrator, \$120. HP 86242D RF plug-in, \$150. Phone 218-724-4131, or fax 218-728-0260.

FOR SALE: HP 5245L freq. counter w/HP 5262A time interval unit \$350. Hugh M. Adams, 1011D Hondo Ave., Ft. Walton Beach, FL 32547. 904-864-2414.

SUCH A DEAL! On-line auction of popular test equipment. Check out Metric's "Auction" at <http://www.metricsales.com> There's nothing else like it!

WANTED! TEST equipment. We pay top dollar for used scopes, generators, analyzers from HP, Tektronix, and others. Call Charles at Metric for immediate quotation. 1-800-432-3424.

REMOTE CONTROL A/B SWITCH



\$29.95

A/B/C SWITCH \$39.95
Plus shipping - Money Back Guarantee
DEALER PRICING ON REQUEST

CONTROLLED BY ANY REMOTE!

Now you can switch between two TV signal sources without getting up or even reaching for a different remote control! Simply press any button on any remote control and hold it down for two seconds. QuikSwitch contains a patented sensor that causes it to switch sources each time it receives an uninterrupted infrared signal for two seconds. And you won't need a spare AC outlet, because QuikSwitch operates a full year on 2 "AA" alkalines, 3 years on lithiums!

HIGH ISOLATION

100% SOLID STATE

MADE IN U.S.A.



MILESTONE PRODUCTS
5698 WESTBOURNE AVE - COLUMBUS, OH 43213
1-800-831-0184



Licensed Under U.S. Patents 4,935,733 and 5,047,765 Other Patents Pending

FEITEK PROVIDES repair, calibration and certification on many makes of test equipment. We also have a large selection of used equipment. Send large SASE envelope for list. VISA and MasterCard accepted. Feitek Inc., 2752 Walton Road, St. Louis, MO 63114, 314-423-1770.

ATTN: TELECOM transmission engineers. For sale: HP AC voltmeter model 403B 1mw, 600 ohm. \$100 OBO. 714-494-0072.

SECURITY

THE MOST EXTRAORDINARY hacking catalog in the world! www.spectre-press.com

WANTED: CONTROL unit for Cohu ARC-14Hz or Pelco PT550M camera pan and tilt unit. Call Bill Scolnik, 1-800-634-7036 or fax 201-405-1706.

SPY EMPORIUM privacy security. Professional recorders, parabolic mic., wireless covert video, bugging/phone tap detectors, scramblers, locksmith tools, etc. FOR CATALOG, SEND \$5 to Security Trade, 6065 Hillcroft, Suite 413, Houston, TX 77081. 713-774-1000, FAX 713-774-6222.

PAGER OWNER! Use your pager as a security monitor to monitor your burglar alarm and telephone answering machine using Pageout automatic paging system \$99.99. Other systems available. Call 410-483-6211. <http://www.worldprofit.com/maateez.htm>

Software Clearance Outlet

Deadly Tide	\$34 ⁹⁵
3D Website Builder	\$69 ⁹⁵
Act 2.0	\$149 ⁹⁵
Select Phone 96	\$49 ⁹⁵
Civilization CD	\$10 ⁹⁵
Warcraft II	\$34 ⁹⁵
Floorplan Plus 3D / Windows	\$10 ⁹⁵
Monopoly Deluxe	\$19 ⁹⁵
Windows 3.0	\$19 ⁹⁵
Personal Law Firm	\$5 ⁹⁵
Cafe	\$99 ⁹⁵
Dos 5.0	\$14 ⁹⁵
QuickBooks Pro 4.0	\$159 ⁹⁵

Claris Works for Windows
\$19.95

MS Dos 6.22
Upgrade version of 6.0 with free setup to 6.22
\$29.95

Fax Works Pro 3.0 for Windows
with OCR **\$19.95**

11th Hour
Sequel to the 7th Guest
\$24.95

New Products in everyday call for availability and our FREE catalog or surf our Web Site @ WWW.SoftwareOutlet.com Email: SCOutlet@AOL.COM
MACINTOSH also Available!

3501 W. Moore Ave. #C Santa Ana, CA 92704
Fax (714) 434-4799

Open 10-8 Mon-Fri
Open 10-6 Sat-Sun
(714) 434-4799

Pacific Standard Time
1-800-230-SOFT (7638)
Quantities are limited. Compatibility not guaranteed. No returns on used or opened merchandise. Returns must have an Authorization Number! Defective products will be replaced with identical items. Add \$5 min. for shipping. Policies, Availability, and Prices subject to change without notice.
We also Buy New Software and Closeouts
Call (714) 434-4797 or Fax (714) 434-4799

Write in 207 on Reader Service Card.

MCM ELECTRONICS

Value And Selection From One Source...

Nuts and Volts Readers!

Save Up To 50% on select items. Take advantage of this tremendous offer. Call today, time is limited! To take advantage of this offer, you must supply this special price code: **CODE: NVM10**



SAVE 45%
TENMA
DMM w/Logic Function
3 1/2 digit LCD DMM measures voltage, resistance, capacitance, frequency and amperage.

Also tests transistors, diodes and includes logic function. Input Impedance 10Mohm. Requires 9V battery.

#72-4025
Reg. \$65.95.....Sale **\$35.95**



Aluminum Tool Case
Heavy-duty case is made of lightweight aluminum and designed to take rough field use. Attractive black finish holds up after years of use. Measures 19" x 14" x 6".

#21-3460
Reg. \$49.95.....Sale **\$32.95**



30 Piece Security Tool Set
This is a complete set of security bits for all of those difficult service applications made difficult because of tamper resistant screws. Items such as computer monitors, telephone equipment, cable equipment and many others. Includes security torx bits, security hex bits, spanner bits, tri wing bits and more.

#22-1475
Reg. \$39.95.....Sale **\$19.95**

SAVE 50%

SAVE 41%



TENMA
Digital Solder Station
Ideal for most soldering applications including static sensitive devices. Closed loop control and digital readout offer precise operation from 320-900°F. A variety of replacement tips are available.

#21-1590
Reg. \$119.00.....Sale **\$69.95**

Prices effective January 1 through February 15, 1997

FREE Catalog

For complete information on the items listed, or a free catalog, Call...

1-800-543-4330

Authorized
Panasonic
Quasar/Technics
Original Parts Distributor
Premier
RCA/GE
Distributor



MCM ELECTRONICS
650 CONGRESS PARK DR.
CENTERVILLE, OH 45459
A PREMIER FARNELL Company

Same Day Shipping! In stock orders received by 5:00p.m. (YOUR TIME), are shipped the same day from distribution centers near Reno, NV and Dayton, OH.

CODE: NVM10

Write in 149 on Reader Service Card.

Nuts & Volts Magazine/January 1997 **51**

Last month, we discussed many of the specifications used to describe oscilloscope performance. Analog bandwidth and probe considerations were explored in conjunction with determining how much scope is enough. This month, we continue with a discussion on digital storage scopes and information on a few specialty scopes.

How Much Scope is Enough?

Part 2

by Jeffrey Mazur

SELECTING A DIGITAL STORAGE SCOPE

Specifications

A DSO processes signals in two stages: acquisition and display. The acquisition stage samples and digitizes the signal for storage into memory. The display stage then creates a viewable image on the CRT based on these samples. Additional processing may also be done, e.g., to interpolate or peak detect amongst the data samples.

When analyzing the bandwidth specifications of DSOs, there are actually two distinct parameters to consider.

First, is the absolute bandwidth of the input circuits. Just as with an analog scope, this specification determines the highest frequency that can be measured with reasonably low distortion.

Secondly, the sample rate (how many times the signal is sampled per second) also sets an upper frequency limit to signals which can be accurately displayed by the DSO. This sometimes leads to confusion, especially when you consider that DSOs operate in one of two fundamental modes of waveform acquisition: real-time and equivalent-

time sampling.

Real-Time Sampling

To create a waveform accurately, DSOs must gather a sufficient number of samples. In theory, a digital scope needs at least two samples per period to faithfully reproduce a sinewave; otherwise the acquired waveform will be a distorted representation of the input signal. The Nyquist theory further states that sampling at less than this rate will create false signals, or aliases (see Figure 1). In practice, most DSOs need at least 2.5 samples per period and, ideally for more accurate display, signals should be over-

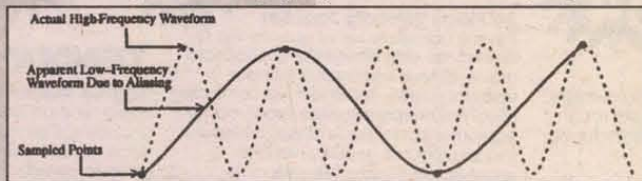


Figure 1. Aliasing caused by sampling at too low of a rate.

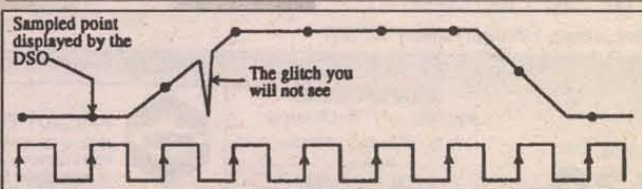


Figure 2. A momentary glitch between sample points can be missed on a DSO.

sampled at a rate of at least five times the highest input frequency (the five times rule again).

Thus, the sampling rate usually limits the highest frequency which a digital scope can acquire in real-time. Because of this limitation in real-time acquisition, most DSOs specify two bandwidths: analog and real-time. The analog bandwidth — defined by the circuits composing the input path of the scope — determines the highest frequency signal a DSO can accept without adding distortion. The second bandwidth, called the real-time bandwidth, defines the maximum frequency the DSO can acquire by sampling the entire input waveform in one pass — using a single trigger — and still gather enough samples to reconstruct the waveform accurately. The following equation describes the maximum real-time bandwidth:

$$\text{Real-Time Bandwidth} = \text{Sample rate} / 2.5$$

For some DSOs, the real-time bandwidth can theoretically exceed the analog bandwidth. But since the input path distorts any signal above its frequency limit, the real-time bandwidth can only be equal to or less than the analog bandwidth.

Both sample rate and bandwidth can affect a scope's ability to catch short transitions or "glitches" in an otherwise stable waveform. For example, Figure 2 shows how a glitch might be missed when it occurs between samples; unless it just happens to fall during a sample time, it will go completely unnoticed. Increasing the sample rate would be the only reasonable approach to avoid this.

Figure 3 shows some real-life examples of how an oscilloscope with inadequate bandwidth and sample rate can hide information. In this figure, a 50 MHz signal is viewed with three different bandwidth and sampling rates. Example 1 of Figure 3 clearly shows a glitch. It has a risetime of approximately 500 pS and was acquired with 1 GHz bandwidth at a 5 GS/s (Samples per second) sampling rate. In Example 2, the bandwidth is still 1 GHz, but the sampling rate has been reduced to 1 GS/s. Example 3 shows the waveform captured with 250 MHz bandwidth and a sampling rate of 1 GS/s. Note that in both Examples 2 and 3, the glitch is concealed from the user.

Equivalent-Time Sampling

When a DSO uses equivalent-time sampling, it can acquire any signal up to the analog bandwidth of the scope regardless of the sample rate. In this mode, the scope gathers

the necessary number of samples across several triggers. The input signal therefore must be repetitive to generate the multiple triggers needed for equivalent-time sampling. In equivalent-time, a slower, lower-cost digitizer provides the same accuracy on repetitive waveforms as a higher cost DSO would do with a faster sampler.

In order to achieve a more accurate waveform, most DSOs use a technique called random equivalent-time sampling. Although the samples are acquired sequentially after each trigger, each acquisition starts at a slightly different time with respect to the trigger. Figure 4 depicts how random equivalent-time sampling compares to real-time sampling.

Interpolation Modes

After gathering samples of the input signal, the display section then uses these points to create a waveform on the oscilloscope screen. In the Dot Mode, a scope will display the sample points directly, with no interpolation (i.e., without attempting to fill in missing points between them). This is sometimes useful — it presents the sampled data in its raw form — but most often, some form of interpolation will be used to create a more readable display. When a scope interpolates, it draws lines between the samples on the display, creating a continuous waveform instead of a string of individual dots.

Creating the missing points requires some compromise. As shown in Figure 5 (bottom), one approach would be to simply draw a line between each sample point. This is known as linear interpolation; waveforms reconstructed in this fashion have a jagged, angular look to them. This method works well with pulses and digital signals, but may produce distortions on sinewaves.

Sine interpolation, as shown in Figure 5 (top), connects the samples using a curve fit. Ideal for sinusoidal signals, this approach can produce apparent overshoot or undershoot when displaying pulses. Most DSOs offer a modified sine interpolation that reduces the inaccuracies when displaying pulses. This $\sin(x)/x$ method uses an adaptive prefilter to locate and compensate for fast signal transitions. Although this method requires more calculations than linear or sine interpolation, the result is a much smoother, yet more accurate display.

However, there is no substitute for having enough samples to recreate a waveform accurately. Figure 6 shows how linear and $\sin(x)/x$ interpolation affects the display of sine, triangular, and

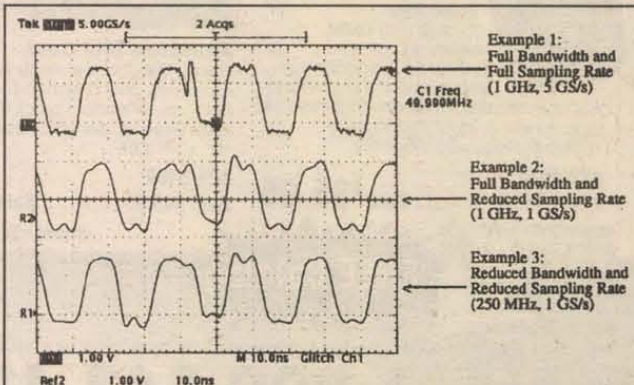


Figure 3. Three examples of how an oscilloscope with inadequate bandwidth and sample rate can hide information.

How Much Scope is Enough?

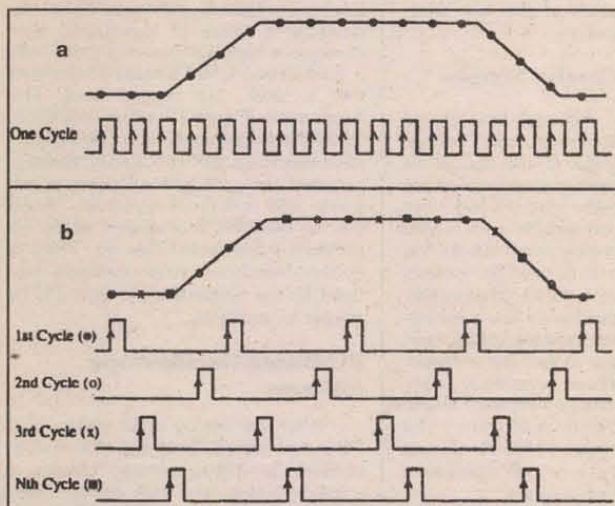


Figure 4. Real-time sampling, a) captures all samples in one pass; equivalent-time sampling, b) requires several cycles.

squarewaves which have been sampled at just the minimum rate (1.25 times the Nyquist rate, or 2.5 samples per cycle). Figure 7 shows the same results when sampled at twice that rate.

Two conclusions can be drawn from these waveforms. First, if there are not enough points to accurately recreate the waveform, the interpolation method will fill in all of the points between samples and probably give a distorted and inaccurate view of the true signal.

Secondly, even when the triangle and squarewaves are sampled at five times their fundamental frequency, they still do not look very much like triangle or squarewaves. This is because these sig-

nals contain higher order harmonics which are necessary to reconstruct the waveform accurately.

Although these harmonics theoretically go on forever, their amplitude rapidly decreases. It is usually sufficient to include up to the fifth harmonic for a reasonable display of a squarewave. Therefore, a good rule of thumb is to use a sample rate which is at least — you guessed it — five times higher than the equivalent frequency sinewave. If we use our previous rule of sampling at five times the input frequency, this means that the sample rate must be at least 25 times the fundamental frequency of the squarewave.

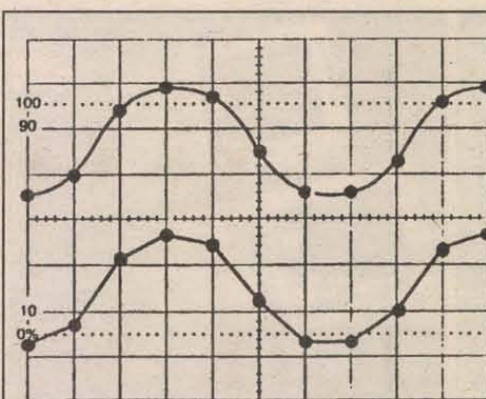


Figure 5. Effects of a) sine and, b) linear interpolation on a sinewave.

Other Acquisition Modes

Many scopes offer other acquisition modes which allow more accurate representations of the sampled signal. For example, by adding a peak detector, the scope can retain the minimum and maximum levels of the input signal for a given sample period. This greatly enhances the scope's ability to catch glitches.

An averaging mode is useful for displaying noisy signals. The scope will display a waveform that is the result of several acquisitions averaged over time. Of course, the signal must be repeating and stable for this mode to be effective. Beware, however. Although this method can reduce noise in the vertical channel, it can add "noise" in the horizontal channel in the form of jitter. This is caused by the fact that the sample clock runs asynchronously to the trigger event and, therefore, the waveform horizontal posi-

tion has an ambiguity of plus or minus 1/2 clock period.

Memory Depth

One of the greatest features of a DSO is the ability to show the waveform before the trigger point. Since the scope is continuously sampling the signal waiting for a trigger event, it has a history of the signal already in memory when that event occurs. Thus, it can immediately display the waveform leading up to the trigger instead of recording in and displaying those

samples taken after the trigger.

Most DSOs allow the trigger point to be displayed either toward the start, in the center, or toward the end of the captured display. Larger memory will allow more of the waveform to be captured giving you a longer look at the signal. Alternatively, you could use the larger memory to sample at a faster rate, giving a more detailed (i.e., higher resolution) picture of the waveform.

When comparing memory depth, however, always check whether the listed amount is per channel or combined total. For example, a scope claiming a 32K record length may assume that only one channel is operating. For a dual channel display, the memory would only store 16K samples per channel.

SPECIALIZED SCOPES

We have seen that analog scopes are sometimes best for catching elusive glitches and metastability which often do not appear on a DSO. On the other hand, signals which do not occur at a reasonable rate will also not leave much of a trace on an analog scope. For catching these types of signals, you need a specialized scope such as the Tektronix 2467B BrightEye™, or the TDS 700A TruCapture™ DSO.

The Microchannel Plate

The Tektronix 2467B scope uses a special Microchannel plate (MCP) CRT to enhance the display of high-speed, low-repetition rate signals. Basically, the MCP amplifies the intensity of the electron beam to yield a brighter display on the face of the CRT. The results are quite impressive as shown by the comparison to a conventional scope in Figure 8.

InstaVu

The Tektronix TDS 700 series (Figure 9) are DSOs that solve this problem with a different approach. Figure 10 shows why a conventional DSO will miss many low-repetition rate signals.

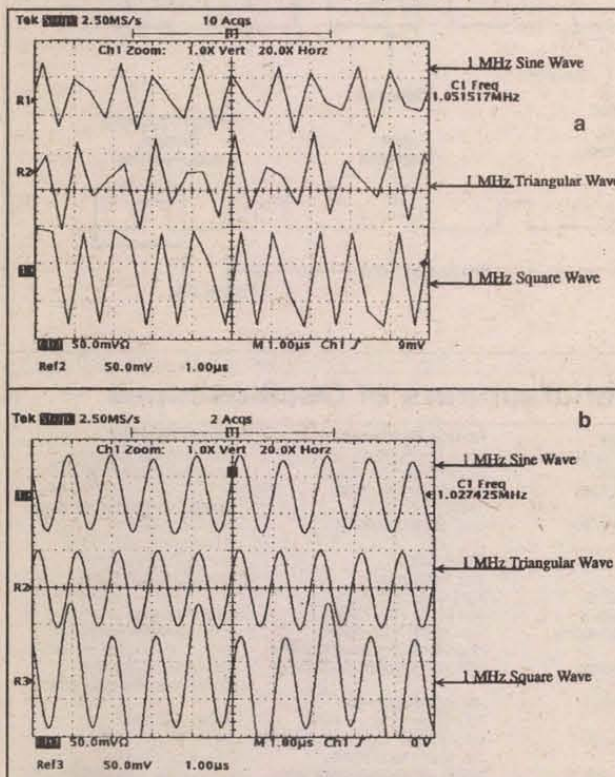


Figure 6. In a) a 1 MHz signal is captured at 1.25 times the Nyquist rate (2.5 MS/s) using linear interpolation; in b), the same signals using sin(x)/x interpolation.

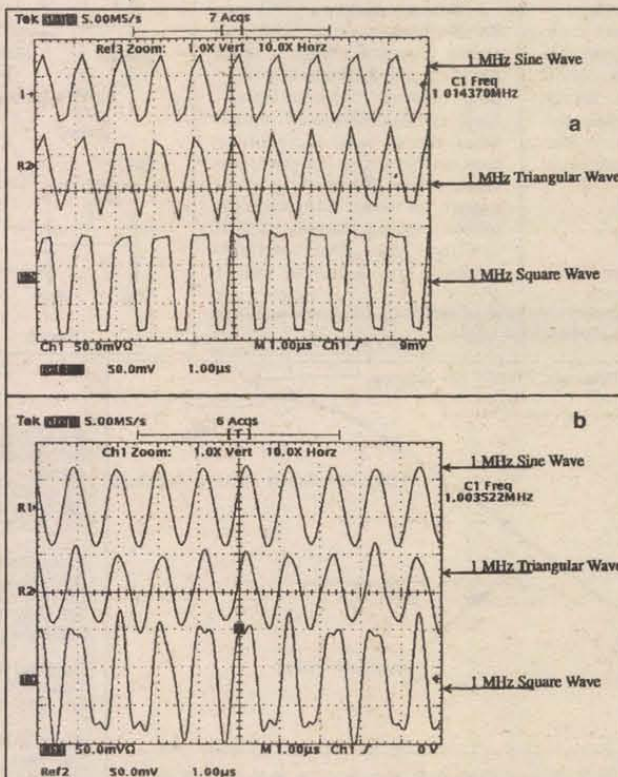


Figure 7. In a) a 1 MHz signal is captured at 2.5 times the Nyquist rate (5 MS/s) using linear interpolation; in b), the same signals using sin(x)/x interpolation.

How Much Scope is Enough?

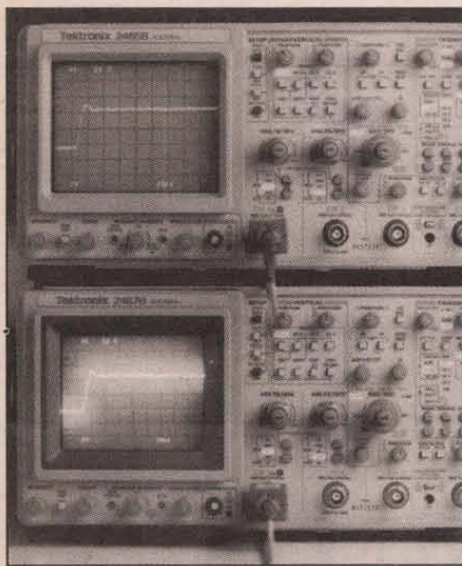


Figure 8. In this comparison of a conventional 2465 analog scope to the 2467B with MCP, the infrequent, erroneous pulse is totally invisible to the 2465. The 2467B, however, intensifies this weak trace to make it visible. Note the INTENSITY settings of the two scopes (in the lower left corner) — all the way up on the 2465, but only half-way on the 2467B.

Because the DSO spends much of its time processing the acquired samples, it is not available to begin sampling again for a relatively long period of time. If the event of interest occurs during these processing times, it will be missed by the DSO.

The TDS 700 addresses this problem with a new mode called InstaVu™. By creating a tighter integration between the acquisition and display sections — and multiplexing four independent channels — up to 400,000 waveforms per second can be captured. This almost equals the capture rate for an analog scope (see Figure 11). Unfortunately, this much power does have its price — literally; the InstaVu family of scopes start at \$10,000.00.

TruTrace

A new feature found on the Classic

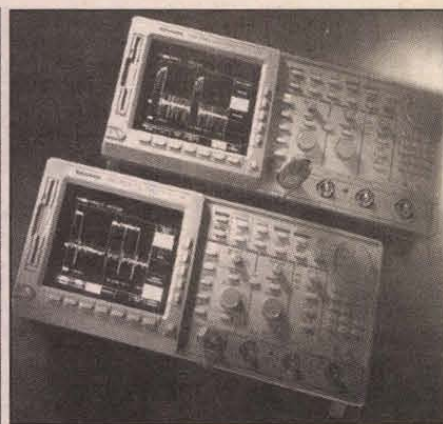


Figure 9. Tektronix TDS 700 series of DSOs with InstaVu.

6000 DSO from Gould Instrument Systems, is the ability to emulate the Z-axis, or intensity modulation, inherent in analog scopes. Called TruTrace, this feature helps distinguish infrequently occurring events from normal waveforms and also can reveal details in long waveform records that a DSO's min/max or peak detection mode throws away. For example, consider a false pulse that occurs only one percent of the time. On an analog scope, this pulse would show up as a faint trace against the brighter waveform of the normal signal. This intensity difference provides information about the signal which is often lost on a DSO.

When a standard DSO uses its min/max mode to display all values recorded within a given sample point, it creates a band of dots between these extremes. Each dot is illuminated equally which throws away any information on how often a particular value occurs. By creating a histogram of when the signal is within certain discrete ranges, TruTrace can then intensity-modulate the display to restore

much of this lost information.

Combo Scopes

Although InstaVu and TruTrace can restore some of the feel of an analog scope, there are those who still feel more comfortable with a true analog scope but once in a while need the features of a DSO. Fortunately, there are a few combination analog/digital storage scopes still available. These essentially combine two separate instruments into one. The Fluke PM3394 (Figure 12) is a good example of such a scope.

On the digital side, the PM3394 offers 200 MS/s — which allows up to 25 GS/s in equivalent-time sampling — and 8K (standard) or 32K (optional) of acquisition memory. The touch of a button however transforms the PM3394 into a full-featured 200 MHz analog scope.

Handheld Oscilloscopes

When performing field service, especially in hostile environments, a DSO would usually be considered a

luxury. Fortunately, however, Fluke has designed a series of instruments that combine a high-performance DSO with a full-featured DMM (Digital Multimeter) into a sleek, but rugged case. The Scopemeter (Figure 13) offers dual-trace, 100 MHz performance at 5 GS/s (equivalent-time) and 30K of memory. Battery-powered and packaged in a shock-proof, water, and dust-proof enclosure, allows you to take the Scopemeter where no ordinary scope would dare go. There is even an interface to send waveforms captured by the Scopemeter to your PC or printer for archiving.

PC-Based Oscilloscope Systems

After the analog input stages of a DSO (i.e., sample/hold and D-to-A conversion), lie digital memory circuits, a microprocessor, and the display hardware. Realizing that these latter functions are all found in every common personal computer, several manufacturers have designed PC-based DSO systems. These consist of some software and a plug-in card, or similar device, which contains all of the analog circuitry. By using the PC's memory, CPU, and monitor display, it is possible to build a decent DSO for very little cost.

For example, the O-Scope I from Allison Technology Corp. turns your PC into a DSO for as little as \$129.00 (in kit form). The O-Scope Ie (Figure 14) adds

Analog Scope


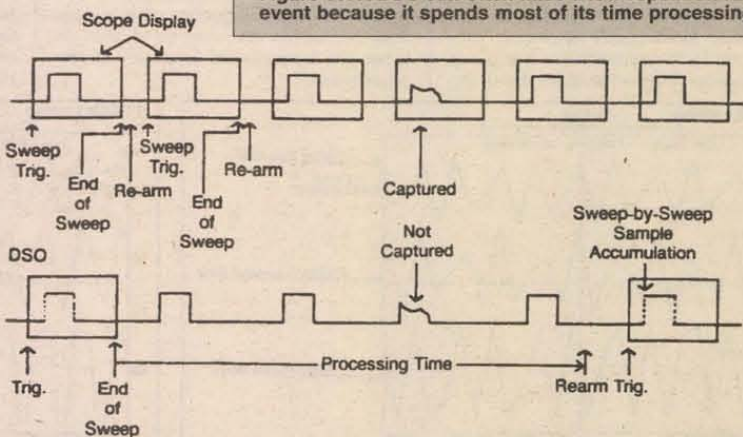


Figure 11. Comparison of the capture rate of the TDS 700A vs. analog and conventional DSOs.

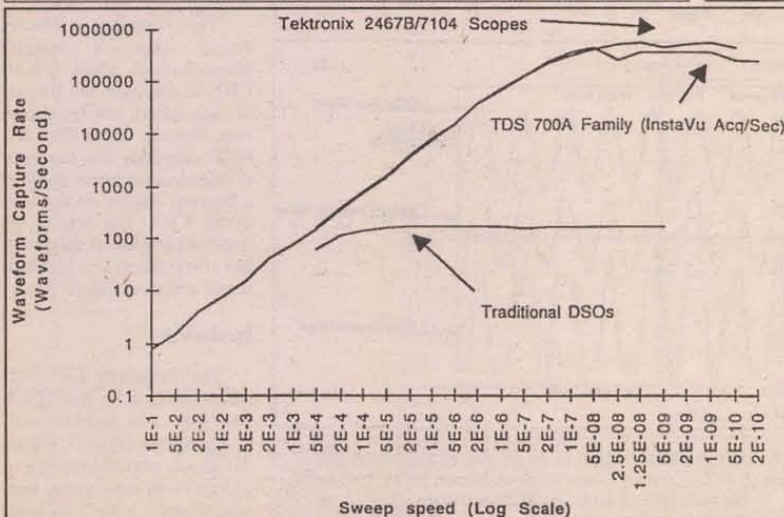

Manufacturers of Oscilloscopes

B & K Precision
6470 W. Cortland St.
Chicago, IL 60635
Tel: (312) 889-1448;
(800) 462-9832
Fax: (312) 794-9740

Fluke Corp.
P.O. Box 9090
Everett, WA 98206
Tel: (800) 443-5853
<http://www.fluke.com/>

Goldstar Precision
Cerritos, CA
Tel: (310) 921-6227

Gould Instrument Systems, Inc.
Cleveland, OH
Tel: (216) 328-7400
<http://www.gould.co.uk/>

Hameg Instruments
1939 Plaza Real
Oceanside, CA 92056
Tel: (619) 630-4080;
(800) 247-1241
Fax: (619) 630-6507

HC Protek
154 Veterans Dr.
Northvale, NJ 07647
Tel: (201) 767-7242
Fax: (201) 767-7343
<http://www.techexpo.com/>
<http://www.hcprotek.com/>

Hewlett-Packard
P.O. Box 4026
Englewood, CO 80155-4026
Tel: (800) 452-4844
<http://www.tmo.hp.com/tmo/>

Hitachi
Torrance, CA
Tel: (310) 328-6116

Iwatsu America
430 Commerce Blvd.
Carlstadt, NJ 07072

Leader Instruments Corp.
380 Oser Ave.
Hauppauge, NY 11788
Tel: (800) 645-5104
Fax: (516) 231-5295

LeCroy Corp.
700 Chestnut Ridge Rd.
Chestnut Ridge, NY 10977
Tel: (800) 553-2769
<http://www.lecroy.com/>

Tektronix, Inc.
26600 S.W. Parkway
P.O. Box 1000
Wilsonville, OR 97070-1000
Tel: (503) 682-3411;
(800) 835-9433
<http://www.tektronix.com/>
Measurement/

How Much Scope is Enough?

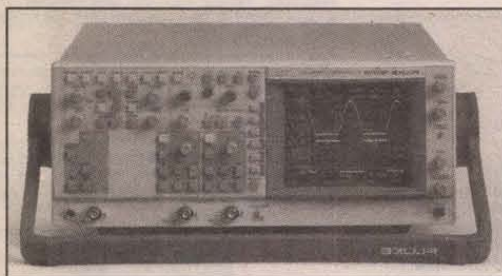


Figure 12. Push a button on the Fluke PM3394 combination DSO and it becomes a true analog scope.

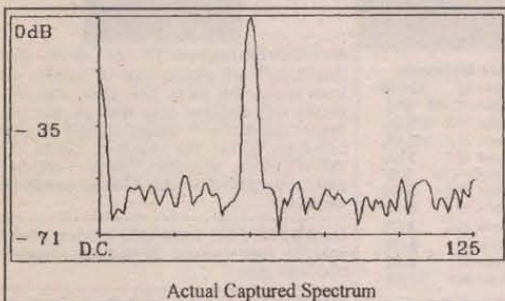


Figure 15. Spectrum display from the O-Scope.

external trigger capability, and the top-of-the-line O-Scope II offers dual input with X-Y capability for only \$349.00. By using the computational power of the PC, all of these models can also generate a spectrum display of the sampled signal (see Figure 15).

So what's the catch? At these prices it almost sounds too good to be true. And it is. When you look closer at the specs on these units you find that the bandwidth is only 22 KHz (250 KHz for the O-Scope II). This all but relegates these devices for analyzing audio or other low-frequency signals. It also makes them ideal for long-time data logging where the time between samples may be measured in seconds or even minutes.

Of course, there are more expensive

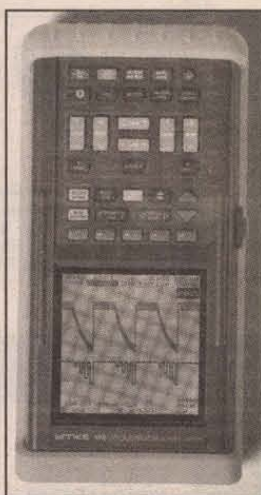


Figure 13. Fluke 99B Scopemeter handheld DSO.

PC-based solutions, some of which have bandwidths up to 400 MHz. As the cost approaches that of a dedicated DSO, however, you then need to consider

whether any advanced features are worth giving up portability and/or tying up your PC.

CONCLUSION

Choosing the right scope is not difficult if you know what to look for. Read the specifications carefully, especially when comparing one brand of scope to another.

Start with your application and the types of signals you are likely to encounter. Figure 16 shows some common scope applications and the typical frequencies involved. Use this only as a general guideline — the actual signals may be much higher. Whenever you need to see the fine details of a signal,

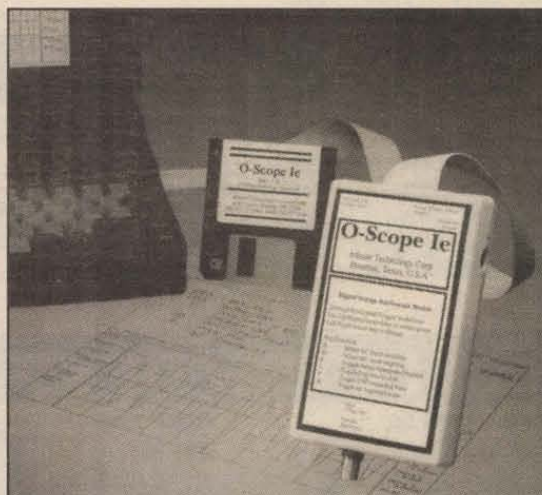


Figure 14. The O-Scope turns your PC into a low-end DSO.

such as high-frequency noise or signal spikes, be sure to allow adequate bandwidth. Analyzing noise spikes on even a lowly 60 Hz power line may require a 100 MHz scope!

In general, engineering and design applications will require a higher quality scope. For circuit design and performance evaluation, high speed, fast rise-time, and accurate amplitude measurements are necessary. Consider using an oscilloscope with at least 200-300 MHz bandwidth for these jobs.

Typical service or repair applications are less demanding. The absolute accuracy of a waveform may not be as criti-

cal; just knowing that the signal is present and that it has the approximate waveshape as expected may be enough. Relative observations, such as comparing a device under test against a known working unit, do not require the extreme accuracy of a high-end scope. A general-purpose scope with 100 MHz bandwidth should prove adequate.

Of course, when working on very high-frequency RF circuits (VHF up to microwave), you will need the highest bandwidth available. Many scopes are designed for just this purpose. These scopes are capable of analyzing signals well into the 10-50 GHz range. **NV**

PC-BASED DSOs

Allison Technology Corp.
8343 Carvel
Houston, TX 77036
Tel: (800) 980-9806
Fax: (713) 777-4746
<http://www.atcweb.com>

ADInstruments, Inc.
(Mac-based DSO)
Milford, MA 01757
Tel: (800) 234 1757
Fax: (508) 634 8869
<http://www.maclab-usa.com/>

Emulation Technology, Inc.
Santa Clara, CA
Tel: (408) 982-0660
Fax: (408) 982-0664
<http://www.emulation.com/>

Link Instruments, Inc.
369 Passaic Ave., Suite 100
Fairfield, NJ 07004
Tel: (201) 808-8990
Fax: (201) 808-8786
<http://www.LinkInstruments.com/>

NCI
6438 University Dr.
Huntsville, AL 35806
Tel: (205) 837-6667
Fax: (205) 837-5221
<http://www.ro.com/customers/nci>

USED AND/OR REFURBISHED UNITS (BUY OR SELL)

Test Equipment Central
<http://www.tecentral.com/>

The Test Equipment Depot
P.O. Box 708
99 Washington St.
Medford, MA 02155-0006
Tel: (800) 517-8431
<http://www.fotronic.com/usedoscspcl.htm>

OSCILLOSCOPE PROBES & ACCESSORIES

Tucker Electronics
http://www.tucker.com/ComPages/com_mi10.html

		Typical Highest Frequency	Bandwidth Required	Need Storage?
AC Line		50-60 Hz	1 KHz	No
Computer		50-150 MHz	100-500 MHz	Yes
Auto		0-5 MHz	25 MHz	No
TV		5 MHz	25 MHz	Desirable
Stereo		20 KHz	1 MHz	No
Satellite (Microwave Applications)		1-10 GHz	1-10 GHz	No
VCR		5 MHz	25 MHz	Desirable
Phone		5 KHz	1 MHz	Desirable

Figure 16. Sources of common waveforms and the oscilloscope requirements to view them.

The author wishes to thank Tektronix, Inc. (especially Heather Wyse) for their help in preparing this article. Many of the photos and drawings used are Copyright Tektronix, Inc. "All rights reserved" and were reproduced with permission.

WIRELESS COVERT CAMERAS W/BUILT-IN 300' TRANSMITTERS. SMOKE DETECTOR \$285, IN-WALL SPEAKER \$260-B/W, \$395-COLOR, ALL WITH AUDIO + 3.6mm PINHOLE LENS. QUAD CCTV SYSTEM \$895 WITH 4: CAMS, 6mm LENS, MOUNTS, PS, + 1 REALTIME QUAD DISPLAY W/T + DATE GEN. LENS BLOWOUT 1/3" 2.8mm, 3.8mm, 4mm \$39. HUNDREDS OF CCTV ITEMS AT 50% OFF DEALER PRICES. CALL 617-933-0827.

PROFESSIONAL ALARM control panels and all equipment. For a free catalog: voice or fax: 908-840-1390.

Subscribe to Nuts & Volts Today!
Call 1-800-783-4624
and Use Your Visa or MasterCard.

MILITARY COMPONENTS wanted. Capacitors, resistors, diodes, transistors, semiconductors, ICs. Electronic Material Industries, 818-842-5953, FAX: 818-845-3613.

SATELLITE EQUIPMENT

THE MOST EXTRAORDINARY hacking catalog in the world! www.spectre-press.com

RACK-MOUNTED VC2s. Pulled from service in working condition. \$150 each while supply lasts. Credit cards okay. Fax: 501-223-9406. Internet: pager@aristotle.net **Surplus City**, Box 23016, Little Rock, AR 72221.

DBS SOLUTION: The DBS solution will allow you to fully test the audio and the video safely and economically. Individual units and dealer packages available. Call 1-800-923-0722 for info.



FREE CATALOG of Big Dish systems, upgrades, and accessories. Warranties & satisfaction guaranteed. **Skyvision**, 1016 Frontier Dr., Fergus Falls, MN 56537. www.skyvision.com Call 1-800-334-6455.

WANTED: LARGE SATELLITE ANTENNAS: 7-20 meter, commercial grade only. Also transmitters for uplink, HPAs, exciters, etc. Prefer Scientific Atlanta, Andrews, Vertex, RSI, etc. Will remove. PTL Cable Service, Inc. Phone 407-747-3647, FAX 407-575-4635.

USED SATELLITE EQUIPMENT. You name it, we have it. LNAs, downconverters, drives, receivers. Working condition guaranteed. Call 317-385-2305.

MILITARY TRANSISTORS & DIODES & INTEGRATED CIRCUITS WANTED. ELECTRONIC MATERIAL INDUSTRIES 818-842-3539, FAX 818-845-3613.



SAT-COVER for your 18", 24", or 30" dish. Sat-Cover™ will protect your 18" satellite dish from snow, ice, sleet, hail, dust, and other debris OR disguise your dish in restricted areas. Sat-Cover™ allows signals through. Look for us on the Internet. **DEALERS WANTED!** Ph. 812-689-3715 or 1-800-642-2907, Fax 812-689-7227 E-Mail: kweaver@venus.net

GUARANTEED LOWEST prices on 18" satellite dish system. \$199 after rebate 1-800-937-2431.

THE DISH NETWORK. U seen it in USA Today @ \$499. Buy it now and save \$50. The minidish \$449 with 1 year programming. UPS to your door. Satellite TV, 120 W. Centennial, Muncie, IN 47303. 317-288-0074 11-5 E. 15 yrs. same location.

SATELLITE EQUIPMENT available: Receivers \$35 and up; 20-25 LNB \$35; C-KU feed horns \$65. Call 804-599-4408.

COMPLETE LIQUIDATION! 20 Hughes satellite 2-way network systems (V-SAT) complete with antennas and hardware. 50 Hughes (V-SAT) digital interface units. 70 Proelin 1.8 meter antennas. 2 2.4 meter antennas. 1 4.5 meter antenna. 19 B-MAC (9700) decoders. 25 sets of non-penetrating antenna roof mounts. 5,000 Plus splitters (2-way, 4-way, 8-way) and taps. 30 Plus rolls 500' and 1,000' plenum cable RG6-RG11. I WOULD LIKE TO SELL IN ONE LOT TO HIGHEST OFFER. WILL FAX LIST. PH/FAX 505-296-3650.

LPTV TRANSMITTERS. Broadcast TV to little communities, from satellite dishes. Write: Electronica Sonora/Eduardo Robles, 252 Grand Ave., Nogales, AZ 85621-2637. Call: tel/fax: (62) 150199- (MEX).

TELECODE™

DSS BIBLE. Book covers: L-card & battery cards, Sony receiver schematics, battery card programmer schematic & software, annotated source, chip programmer software/plans, resources, unbiased "hack" reviews, DS5000 Sip-Stik technical information, card sellers addresses, rip-offs, Web sites. Over 200 files and much more. \$49.95 postpaid. 520-726-2833. **TELECODE**, Box 6426-NV, Yuma, AZ 85366-6426. <http://www.hackerscatalog.com>

SYNC-A-LINK UNIVERSAL VIDEO SYNC GENERATOR restores all horizontal & vertical sync lines, DC level, compensates for inverted video, color phase, from standard or distorted analogue video-type formats. Comes complete with operations manual & 90-day warranty. \$160. 918-479-6451 or write to Sync-A-link Communications, PO Box 4, Locust Grove, OK 74352.

VIDEOCYPER II descrembing manual, schematics, video, and audio. Explains DES, EPROM, CloneMaster, pay-per-view (HBO, Cinemax, Showtime, Adult, etc.) \$16.95, \$2 postage. Schematics for Videocypher Plus, \$20. Schematics for Videocypher 032, \$15. Collection of software to copy and alter EPROM codes, \$25. VCII Plus EPROM, binary, and source code, \$30. Cabletronics, Box 30502N, Bethesda, MD 20824.

ALFA ELECTRONICS

HIGH QUALITY TEST EQUIPMENT
BEST PRICE

DMM 89 \$179.00
Most Advanced DMM
-80.7 to 81.4 dBm with 40-1200Ω
20 reference impedances
True RMS
Frequency counter: 100 Hz - 10MHz
Capacitance: 5nF-50mF
Measure AC volt to 20kHz
5000 counts, 0.1% basic accuracy
Auto/manual range, fast bar graph
Min/Max/Ave/DIV/Relative/Zoom
Auto power off
Input warning
Splash proof
Volt, amp, ohm, logic, diode, continuity
Ruggedized case
Rubber holster included

DMM A91 \$49.95
NOW \$39.00
Plus Free Case
Solar Cell Powered
Large Display
Diode, Continuity
Volt, Amp, Ohm
Data Hold
Auto power off
7 functions, 19 ranges
3.5 Digit, 0.8% accuracy
Auto/manual ranging
Energy saver
Student & hobbyist's favor

DMM 20 \$74.95
Inductance: 2mH-20H
Capacitance: 2nF-200μF
Resistance: 200-200MΩ
Frequency: 24Hz-20MHz
3.5 Digit, 0.5% accuracy
DC/AC Current and Volts
Transistor hFE, diode test
Continuity, Duty %
Peak hold/Max
Ruggedized case
Rubber holster \$6.00
Full line of DMMs, economy, compact, ruggedized, solar cell, automotive, heavy duty, industrial, electrical starts from \$19.95

Fluke Multimeter
Fluke 12 \$84.95
Holster C-10 \$10
Fluke 70 II \$75.95
Fluke 73 II \$97.50
Fluke 75 II \$129
Holster C70 \$16
Fluke 77 II \$155
Fluke 79 II \$175
Fluke 29 II \$175
Fluke 76 \$175
Fluke 87 \$287
Fluke 867 \$1199
Scope Meter
Fluke 97 \$1785
Fluke 105 \$2799

LCR Meter 131D \$229.95
Most Advanced LCR
Dual display: L/Q or C/D
Inductance: 10mH-10,000H
Capacitance: 10nF-10mF
Resistance: 10Ω-10MΩ
Auto/manual range
Dissipation factor & Q factor
Serial & parallel mode
Relative mode for comparison
and to remove parasitics
Statistics, tolerance,
Best for design, incoming
testing & production
SMD and chip component
test probe \$25.00

LCR Meter 814 \$189.95
Best Resolution LCR
Inductance: 200μH-200H
Capacitance: 200pF-20,000μF
Resistance: 20-20MΩ
Resolution of 0.1μF, 0.1pF, and
1mΩ are useful for high frequency
and SMD
Dissipation factor indicates leakage
in capacitor and Q factor in inductor
Zero adjustment to reduce parasitics
Best for high frequency RF
SMD and chip component test probe
\$25.00
Deluxe case \$5.00

Frequency Counter FC-1200 \$129.95
Frequency: 10Hz-1.25GHz
Display: 8 digit LCD
Period: 0.1μs-0.1s
Records Max/Min/Average
Data hold, relative mode
Telescoping antenna \$8.00
Deluxe case \$5.00
Also Available:
AC/DC clamp meter, Light meter,
Thermometer, pH meter, High voltage
Probe, Digital Caliper, Anemometer,
Electronic scale, Force Gauge, Tachometer,
Stroboscope, Humidity & EMF adapter,
Sound level meter, Frequency counter,
SWR/field strength/power meter, Dip meter

20 MHz Oscilloscope with Delay Sweep PS-205 \$429.95
Dual Trace, Component test, 6" CRT, X-Y Operation, TV Sync, Z-Modulation, CH2 Output, Graticule Illum, 2 probes each has x1, x10 switch. Best price with delay sweep.
PS-200 20 MHz DUAL TRACE \$339.95
PS-400 40 MHz DUAL TRACE \$494.95
PS-405 40 MHz DELAY SWEEP \$569.95
PS-605 60 MHz DELAY SWEEP \$789.95
PS-1000 100 MHz DUAL TRACE \$999.95
Scope Probe: 60MHz x1, x10 \$15, 100MHz x1, x10 \$22, 250MHz x1, x10 \$29, 250MHz x100 \$39

Digital Storage Scope
DS-303 30MHz, 20M Samples/sec \$849.95
DS-303P with RS-232 interface \$1,049.95
Switchable between digital and analog modes
2 K word per channel storage
8 bit vertical resolution (25 Levels/div)
Expanded Timebase 10ms/div - 0.5 s/div
Refresh, Roll, Save all, Save CH2, Pre-Trig
Plotter control

DC Power Supply PS-303 \$159.00
0-30 VDC, 0-3A output
Constant voltage & constant current mode
0.02% + 2mV line regulation
0.02% + 3mV load regulation
1 mVrms noise and ripple
Short circuit and overload protected
PS-5200 with digital voltmeter \$179.00
Also available: 30V/5A, 60V/3A, 60V/5A, 16V/10A, 30V/10A

DC Power Supply Triple Output PS-8202 \$499.95
Two 0-30 VDC, 0-3A outputs
One fixed 5VDC, 3A output
Capable of independent or tracking operation
Constant voltage and constant current mode
Four digital meters for volt and current display
Excellent regulation and low ripple
Short circuit and overload protected
Also available: 30V/5A triple output \$549.95
Dual tracking 30V/3A, 30V/5A, 60V/3A, 60V/5A

RF Signal Generator SG-4160B \$124.95
100 kHz-150MHz sine wave in 6 ranges
RF Output 100mVrms to 35 MHz
Internal 1kΩ, External 50Ω-20kΩ
AM modulation
Audio output 1 kHz, 1 Vrms
Output Impedance: 50 Ohm
Size: 5.9" x 9.8" x 8.1" D
Accessory: RF cable, AC power cord, manual
RF Signal Generator/Counter SG-4162 AD \$229.95
Generates RF signal same as SG-4160B
6 digit frequency counter 1Hz - 150 MHz for internal and external source
Sensitivity <50mV

Audio Generator AG-2601A \$124.95
10Hz - 1MHz in 5 ranges
Output: 0-8Vrms sine wave
0-10Vpp square wave
Synchronization: ±3% of oscillation frequency per Vrms
Output distortion: 0.05% 500Hz - 50kHz
0.5% 50Hz - 500kHz
Output impedance: 600 ohm
Audio Generator/Counter AG-2603AD \$229.95
Generates audio signal same as AG-2601A
6 digit frequency counter 10Hz - 150MHz for internal and external sources
Sensitivity <50mV

Function Generator FG-2100A \$169.95
0.2 Hz - 2 MHz in 7 ranges
Sine, square, triangle, pulse and ramp
Output: 5mV-20Vp-p
1% distortion, DC offset ±10V
VCF: 0-10V control frequency to 1000:1
Function Generator/Counter FG-2102AD \$229.95
Generates signal same as FG-2100A
Frequency counter 4 digits
Feature TTL and CMOS output
Sweep Function Generator/Counter \$329.95
0.5Hz to 5 MHz in 7 ranges
Sweep: Linear 10:1 Log 10:1 20ms to 2s
AM Modulation
Gated Burst, Voltage Control Generator
Generator Control Voltage & 8 digit counter 1Hz-10MHz for internal & external sources

ALFA ELECTRONICS

P.O. BOX 8089, Princeton, NJ 08543-8089

(800) 526-2532/(609) 897-1135

FAX: (609) 897-0206

Visa, Master Card, American Express, COD, Purchase Order Welcome

1 YEAR PARTS AND LABOR WARRANTY

CALL / WRITE / FAX FOR FREE CATALOG

Write in 204 on Reader Service Card.

OBTAINING SOUND for your VCII and VCII Plus is easy! No codes needed. Also DSS TEST CARD information. **FREE DETAILS.** 1-800-211-5635.



NOTHING ELSE COMPARES™. Digital 18" satellite systems, mobile satellite systems, home entertainment, accessories and more. www.skyvision.com Call 1-800-500-9264.

MILITARY SURPLUS ELECTRONICS

RECOVER "SCRAP GOLD" from old computer junk. Free information packet. Call 24 hours: 603-645-4772.

DEFENSE SUPPLY Technical Data CD-ROM. NSNs, Cage codes, item name, pricing, supplier, and characteristics information. \$100. Also, Defense Medical Catalog CD-ROM. \$100. 334-889-4637.

AUDIO/VIDEO/LASER

MICRO TV CAMERAS. Pin hole or standard lens with sound. Same as the ones costing \$129 and up. Why pay more? Blow out sale at \$65 each. Hurry, limited quantities with factory warranty. 310-305-1030.

FIBER OPTIC TRANSMITTER/RECEIVER. BACK IN STOCK! Transmit composite video images from any video source (cameras, VCRs, etc.) over fiber optic cable. SMA connectors. Package includes transmitter, receiver and two AC adapters. Brand new in the box. Only \$49 while supplies last. Credit cards okay. Fax/message: 501-223-9406. Internet: pager@aristotle.net Surplus City, Box 23016, Little Rock, AR 72221.



CROWN-TECHRON 5000W (@1Ω) 208V/3-phase (only) mono amplifiers. Industrial version compares directly to \$10,000 Macro-Tech 10K. Clean used/checked condition. 90-day warranty. This Crown model only. \$1,195, FOB Columbus, OH. 614-279-2383 24-hour faxback information.

FACTORY VIDEOS: VHS. Beta 8mm movies need splice or fix \$75/100 pcs. Jim 310-515-2058.

LASER SHOW Systems: rack mount digital controller with keypad and LCD. Scanner head with X/Y galvos, shutter, grating, choice of laser. Many preprogrammed patterns and beam effects + create your own. Complete systems starting at \$695. **RED LINE LASER PRODUCTS** 314-831-3014.

LASER SURPLUS New and used equipment for the hobbyist or professional. HeNe, Argon, YAG, Ruby, CO₂, and visible laser diodes. Also stocking optics, galvos, computer and test equipment. **Free Catalog.** Laser Surplus Inc., 759 Laurel Road Dept. 5C, Clinton, TN 37716-5454. lasersur@ix.net.com

LASER RANGEFINDER measures distances up to 1000 meters: 1 yard/meter accuracy. Built into binoculars, 9V battery operated w/LCD display: \$300. Laser Sensor Technology, 3873 Easy circle, Marietta, GA 30066-2031. 770-928-2867 fax & phone. E-Mail: JClark3873@aol.com

PRO AUDIO, video & projection equipment for sale!! Microphones, mixers, switchers, cameras, monitors, TBCs, tubes, slide & film projectors & lenses. Great buys for the smart shopper. Call Tom for a detailed list. Tel 609-222-0636 Fax 609-222-0638.

LASERS: TUBES, power supplies, diodes, project kits. From \$10. **FREE CATALOG.** Toland Electronic Products, PO Box 1353, Glendale, AZ 85311.

OUT OF BUSINESS SALE: TV/VCR repair shop. Everything must go. Priced at more than 50% off cost. Parts, equipment, SAMs, and brand-specific manuals. Super deals, guaranteed. Pro Tech, POB 4076, Butte, MT 59702. Phone 406-723-8922, Fax 406-723-4411.

START YOUR OWN TECHNICAL VENTURE! Don Lancaster's newly updated **INCREDIBLE SECRET MONEY MACHINE II** tells how. We now have autographed copies of the Guru's underground classic for \$18.50. Synergetics Press, Box 809-K, Thatcher, AZ 85552. 520-428-4073. VISA/MC.

NVG, INC. offers a complete line of OEM laser modules, including all NM bands, low & high MW, as well as the world's smallest 6.4 module. Most are stock items, eliminating long lead times and providing fast delivery. Also available are laser diodes and module components. 912-379-9000 x2.

THE MOST EXTRAORDINARY hacking catalog in the world! www.spectre-press.com

BROADCAST VIDEO equipment wanted: all types, new or old. Please call, Jon with info. 317-539-2859.

Sell Nuts & Volts
in your store and earn \$\$\$!
Contact us for details. 909-371-8497
E-Mail distributors@nutsvolts.com

CABLE TV

1997 SPECIALS: New multimode kits (22) and educational boards for most models as low as \$9. Forty pin microprocessors as low as \$13. ZL1, T3055, T7055, D5 as low as \$3. Minimum order \$50. COD only. All kits sold for educational and test purposes only. All merchandise has 30-day repair or replacement guarantee. Call toll free at 888-579-8479 or leave a message at 818-578-8449.

NEW! VIDEO cassette storage cases now available \$1.25 each, plus shipping and COD. 100 piece minimum order black grain finish with interior hubs, call Ken Erny Electronics 24 hour order and information hot line 516-389-3536.

ALL ELECTRONICS

C O R P O R A T I O N

QUALITY PARTS

FAST SHIPPING

DISCOUNT PRICING

CALL, WRITE, FAX or E-MAIL For A Free 64 Page CATALOG. Outside the U.S.A. send \$2.00 postage.



PC MOUNT POWER RELAY 24 Vdc

Potter & Brumfield # T90N5D12-24 24 Vdc, 675 ohm coil. SPDT contacts rated 20 amps (N.O.), 10 amps (N.C.) @ 240 Vac. 1.15" X 0.09" X 0.65". PC terminals. UL and CSA listed.

CAT# RLY-55 \$2.00 each

10 for \$18.50 • 100 for \$150.00


SPECIAL PRICE! TWIST ON F-56 CONNECTOR

We recently made a large purchase of this twist-on co-ax connector for RG-6 cable. Special pricing while the supply lasts.

100 for \$15.00
500 for \$50.00
1000 for \$70.00

CAT# FTO-56R

S-VHS VIDEO CORD

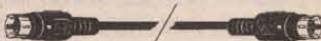

4' cable with miniature 4 pin mini DIN plugs on both ends.

CAT# CB-363

\$3.00 each 10 for \$25.00 100 for \$150.00

"HI-8" VIDEO CASSETTE (USED)

SONY HI-8

Top quality, metal particle 120 minute video cassettes. Used for a short time, then bulk-erased. Each cassette has its own plastic storage box. Satisfaction Guaranteed.



\$3.00 each

CAT# VCU-8

10 for \$28.00 • 100 for \$250.00

THE INSULTINATOR A Programmable Electronic Insult Machine with Thousands of Sayings

"You're A Completely Slobbering Greasy Dweeb!"
"You're a totally ugly gross boring nerd!"
"You're A Totally Freaky Wacky Bonehead!"



Hand-held voice synthesizer plays a variety of insults which can be altered by selecting various programming buttons. Even though no profanity is used, a major nationwide retailer rejected these as being too insulting for their customers. Wild green and black case with belt or pocket clip. Includes 3 AA batteries. Attractive display package.

CAT# INS-5 \$4.95 each

case of 24 - \$4.50 each

POWERFUL NEODYMIUM, RARE EARTH MAGNETS

Aprox. 1.86" X 1.02" X 0.08" thick.

CAT# MAG-26

\$1.50 each 25 for \$31.25 100 for \$100.00

RECHARGEABLE SEALED LEAD ACID BATTERIES

6 Volts 7 A/h
Yuasa # NP7-6
5.95" X 1.3" X 3.7".
0.1875" qc connectors



\$15.00 each CAT# GC-67

SECURITY ALERT SIGNALLING SYSTEM

Designed for the traveler to hang on the inside of a hotel door, the Datawave KL-1 Security Alert emits loud beeps and flashing lights when someone knocks or if someone tampers with the door. Ideal for hearing impaired, the four high-brightness LEDs are easy to see from far away. Can be switched for audible alarm with lights or lights only. Requires 3 AA batteries (not included).



CAT # KL-1 \$9.50 each

SMALL STEPPER MOTOR

Unipolar, two phase, 6 lead stepper motor. 53 ohm coil. Operates well on 12 Vdc. 15 degree per step. Motor body is 1" diameter X 0.5" 0.08" (2mm) diameter shaft is 0.365" long. The shaft is covered with a threaded plastic sheath (0.25" dia X 0.75" long) which acts as a worm gear. This mechanism, if not required, is easily removable. Rectangular mounting bracket, 1.73" X 1.10".



\$1.50 each

CAT# SMT-21 10 for \$12.50

EDGEVIEW PANEL METER FS=1 MICROAMP

Mura Beautifully constructed edgeview meter movement. 2.75" X 0.8" face. Scale is labeled "BEATS/MINUTE" and is calibrated from 50-150. It can be easily removed or reversed to create a blank scale. The black bezel is 3.53" X 1.33" and can be adjusted or removed. 0.1" thick clear plexiglass case. Maximum case size behind mounting plate: 2.75" X 1.18" X 2.18". Solder lug terminals.



CAT # MET-47 \$5.50 each

ORDER TOLL FREE

1-800-826-5432

MAIL ORDERS TO:
ALL ELECTRONICS CORP.
P.O. BOX 567
VAN NUYS, CA 91408-0567

FAX (818) 781-2653 • INFO (818) 904-0524
INTERNET <http://www.allcorp.com/>
E-MAIL allcorp@allcorp.com

NO MINIMUM ORDER • All Orders Can Be Charged to Visa, Mastercard, American Express or Discover • Checks and Money Orders Accepted by Mail • Orders Delivered in the State of California must include California State Sales Tax • NO C.O.D. • Shipping and Handling \$5.00 for the 48 Continental United States • ALL OTHERS including Alaska, Hawaii, P.R. and Canada Must Pay Full Shipping • Quantities Limited • Prices Subject to change without notice.

MANUFACTURERS - We Purchase EXCESS INVENTORIES... Call, Write, E-MAIL or Fax YOUR LIST.

DESCRAMBLING, NEW secret manual. Build your own descramblers for cable and subscription TV. Instructions, schematics for SSAVI, gated sync., sinewave (HBO, Cinemax, Showtime, UHF, adult) \$12.95, \$2 postage. Cabletronics, Box 30502N, Bethesda, MD 20824.

EVERYTHING YOU NEED FOR CABLE! 1-800-663-8530. FORMERLY 1-800-MODULE-0.

CABLE UNSCRAMBLED. Everything you want to know about cable, but are afraid to ask. \$10. VISA/MC/AMEX. Free catalog. ELECTROMAN, Box 24474, New Orleans, LA 70184. 504-482-3017.

"DESCRAMBLER SCHEMATICS REVEALED." A powerful guide to descrambling schemes. \$10. VISA/MC/AMEX. Free catalog. ELECTROMAN, Box 24474, New Orleans, LA 70184. 504-482-3017.

UNBELIEVABLE PRICES. We carry a full line of cable tools and equipment for all your cable needs. Also a wide variety of electronic parts & accessories, tools, diagrams, converters, step-by-step instructions, and full technical support. 9am-7:30pm EST 1-800-562-8442.

THE MOST EXTRAORDINARY hacking catalog in the world! www.spectre-press.com

SUPER TRAP. 1,000 times more powerful than a FM trap! Exclusive multi-pole design. \$29.95 + \$3 S&H. VISA/MC/AMEX. Free catalog. ELECTROMAN, Box 24474, New Orleans, LA 70184. 504-482-3017.

"BASEBAND VIDEO EXPLAINED." Discover what a baseband signal is and how it's constructed. Learn the advantages of doing things the baseband way. \$10. VISA/MC/AMEX. Free catalog. ELECTROMAN, Box 24474, New Orleans, LA 70184. 504-482-3017.


EVERYTHING YOU NEED FOR CABLE! 1-800-663-8530. FORMERLY 1-800-MODULE-0.

UNMODIFIED CABLE box pulls Zenith ST 1000, 1086. Regal CR-83 plain converter. Oak RKDM-400 \$20. Other brands available. Call 405-631-1856.



NOTCH FILTERS 110, 108.5, 106.5, 97.5 75dB deep notch. \$19.95 ea., 1-5 qty. \$14.95 ea., 6-10 qty. \$10.95 ea., 11+ qty. \$8.95 ea., 21 or more qty. Call 24 hr. order and information hot line 516-389-3536.

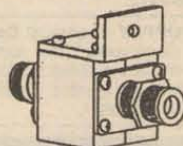SIGMA 3D/2000 converter kit. Gets all channels. \$175. Fax name, address, city, state, zip, phone to 808-955-3959. Fully guaranteed.



EXPLOSIVE CABLE TV GRAB! BRINKER ZAPPER/SNOOPER STOPPER combo module all in one! Buy wholesale factory-direct, no middleman. Let others get fined + zapped instead. Protect your cable box now! 100% COMPATIBLE. We supply over 80 advertisers weekly! Your order shipped fast, within hours! Why pay \$39 when you can buy direct! LIFETIME GUARANTEE! We accept VISA/MC/COD/MO/CHECKS. ONLY \$10 (3/\$22). Descrambler plans \$5. SUPER-ZAPPER MODULES ONLY \$16! Call/fax us anytime 904-234-8302 ext. 5, BRINKER ENGINEERING LABS

BLUE BE GONE. Stops "blue" screen (video mute) VCR function. \$49.95 + \$5 S&H. VISA/MC/AMEX. Free catalog. ELECTROMAN, Box 24474, New Orleans, LA 70184. 504-482-3017.

HAMLIN, PIONEER, ZENITH, AS and other manufacturer converters, various models including 6600, 6000 and 5000, 90s, 80s 29s, 28s 25s, and 100s, 5130, 5135, 4135 and 9310s, ST-1000 288 and 165 MP, 1086 and 1600, plus other models. LARGE QUANTITIES, CALL FOR PRICING. 1-800-380-9530.

SELLING UNMODIFIED cable equipment, boxes, and converter. For all software needs call 909-941-4858.

DEALERS! WELCOME. All makes & models available. Call Marco for best deal. 718-358-6237.

CABLE PRODUCTS & MORE! BEST PRICES! 1-800-663-8530. FORMERLY 1-800-MODULE-0.

FOR SALE: Jerrold 2214, 2014 genuine unmodified. SA 8600, 8580 genuine unmodified. Zenith 1086, 1600 series original unmodified, Pioneer 5430 \$35 genuine unmodified. Tocom VIP 5503A genuine unmodified, 10-lot only. 1-800-500-9825.

PICS, GALS READ if you've lost your masters. Programming service available. Call for info. Network Sales, 616-683-0500.

WANTED: TEKNIKA 6510 cable converter boxes 415-221-5940.

TELECODE™

CABLE HACKERS SPECIAL: Volume 1 & 2 books plus CABLE HACKERS VIDEO and Volume 3, MASTER FILES. Save \$\$\$\$. \$149.95 PPD USA. 520-726-2833. TELECODE, Box 6426-NV, Yuma, AZ 85366-6426. http://www.hackerscatalog.com

TORX SECURITY tool set. Required for cable converters, games, VCRs, etc. Complete 7 piece set. Only \$19.95 shipping included. To: TDS, PO Box 1652, Homosassa Sp., FL 34447.

Synthesized FM Stereo Transmitter



Microprocessor controlled for easy freq programming using DIP switches, no drift, your signal is rock solid all the time - just like the commercial stations. Audio quality is excellent, connect to the line output of any CD player, tape deck or mixer and you're on-the-air. Foreign buyers will appreciate the high power output capability of the FM-25; many Caribbean folks use a single FM-25 to cover the whole island! New, improved, clean and hum-free runs on either 12 VDC or 120 VAC. Kit comes complete with case set, whip antenna, 120 VAC power adapter - easy one evening assembly.

FM-25, Synthesized FM Stereo Transmitter Kit \$129.95

Tunable FM Stereo Transmitter



A lower cost alternative to our high performance transmitters. Offers great value, tunable over the 88-108 MHz FM broadcast band, plenty of power and our manual goes into great detail outlining aspects of antennas, transmitting range and the FCC rules and regulations. Connects to any cassette deck, CD player or mixer and you're on-the-air, you'll be amazed at the exceptional audio quality! Runs on internal 9V battery or external power from 5 to 15 VDC, or optional 120 VAC adapter. Add our matching case and whip antenna set for a nice finished look.

FM-10A, Tunable FM Stereo Transmitter Kit \$34.95

CFM, Matching Case and Antenna Set \$14.95

RF Power Booster Amplifier



Add some serious muscle to your signal, boost power up to 1 watt over a frequency range of 100 kHz to over 1000 MHz! Use as a lab amp for signal generators, plus many foreign users employ the LPA-1 to boost the power of their FM Stereo transmitters, providing radio service through an entire town. Power required: 12 to 15 volts DC at 250mA, gain of 38dB at 10 MHz, 10 dB at 1000 MHz. For a neat, professionally finished look, add the optional matching case set.

LPA-1, Power Booster Amplifier Kit \$39.95

CLPA, Matching Case Set for LPA-1 Kit \$14.95

LPA-1WT, Fully Wired LPA-1 with Case \$99.95

Micro FM Wireless Mike



World's smallest FM transmitter. Size of a sugar cube! Uses SMT (Surface Mount Technology) devices and mini electret condenser microphone, even the battery is included. We give you two complete sets of SMT parts to allow for any errors or mishaps-build it carefully and you've got extra SMT parts to build another! Audio quality and pick-up is unbelievable, transmission range up to 300 feet, tunable to anywhere in standard FM band 88 to 108 MHz. 7/8" w x 3/8" h x 3/4" h.

FM-S Micro FM Wireless Mike Kit \$19.95

Crystal Controlled Wireless Mike



Super stable, drift free, not affected by temperature, metal or your body! Frequency is set by a crystal in the 2 meter Ham band of 146.535 MHz, easily picked up on any scanner radio or 2 meter rig. Changing the crystal to put frequency anywhere in the 140 to 160 MHz range-crystals cost only five or six dollars. Sensitive electret condenser mike picks up whispers anywhere in a room and transmit up to 1/4 mile. Powered by 3 volt Lithium or pair of watch batteries which are included. Uses the latest in SMT surface mount parts and we even include a few extras in case you sneeze and lose a part!


FM-6, Crystal Controlled FM Wireless Mike Kit \$39.95

FM-SWT Fully Wired FM-6 \$69.95

Call for our Free Catalog!

RAMSEY

Super Pro FM Stereo Radio Transmitter

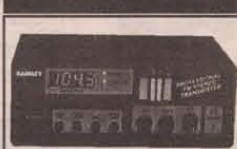

A truly professional frequency synthesized FM Stereo transmitter station in one easy to use, handsome cabinet. Most radio stations require a whole equipment rack to hold all the features

we've packed into the FM-100. Set frequency easily with the Up/Down freq buttons and the big LED digital display. Plus there's input low pass filtering that gives great sound no matter what the source (no more squeals or swishing sounds from cheap CD player inputs!) Peak limiters for maximum punch! In your audio - without over modulation. LED bargraph meters for easy setting of audio levels and a built-in mixer with mike and line level inputs. Churches, drive-ins, schools and colleges find the FM-100 to be the answer to their transmitting needs, you will too. No one offers all these features at this price! Kit includes sharp looking metal cabinet, whip antenna and 120 volt AC adapter. Also runs on 12 volts DC.

We also offer a high power export version of the FM-100 that's fully assembled with one watt of RF power, for miles of program coverage. The export version can only be shipped outside the USA, or within the US it accompanied by a signed statement that the unit will be exported.

FM-100, Professional FM Stereo Transmitter Kit \$299.95

FM-100WT, Fully Wired High Power FM-100 \$429.95

Speech Descrambler Scrambler



Decode all that gibberish! This is the popular descrambler / scrambler that you've read about in all the Scanner and Electronic magazines. The technology used is known as speech inversion which is compatible with most cordless phones and many police department systems, hook it up to scanner speaker terminals and you're in business. Easily configured for any use: mike, line level and speaker output/inputs are provided. Also communicate in total privacy over telephone or radio, full duplex operation - scramble and unscramble at the same time. Easy to build, all complex circuitry contained in new custom ASIC chip for clear, clean audio. Runs on 9 to 15VDC, RCA phono type jacks. Our matching case set adds a super nice professional look to your kit.

SS-70A, Speech Descrambler/Scrambler Kit \$39.95

CSS, Custom Matching Case and Knob Set \$14.95

SS-70AWT, Fully Wired SS-70A with Case \$79.95

AC12-5, 12 Volt DC Wall Plug Adapter \$9.95

Tone-Grabber Touch Tone Decoder / Reader



Tones are used, your TG-1 will decode and store any number it hears. A simple hook-up to any radio speaker or phone line is all that is required, and since the TG-1 uses a central office quality decoder and microprocessor, it will decode digits at virtually any speed! A 256 digit non-volatile memory stores numbers for 100 years - even with the power turned off, and an 8 digit LED display allows you to scroll through anywhere in memory. To make it easy to pick out numbers and codes, a dash is inserted between any group or set of numbers that were decoded more than 2 seconds apart. The TG-1 runs from any 7 to 15 volt DC power source and is both voltage regulated and crystal controlled for the ultimate in stability. For stand-alone use add our matching case set for a clean, professionally finished project. We have a TG-1 connected up here at the Ramsey factory on the FM radio. It's fun to see the phone numbers that are dialed on the morning radio show! Although the TG-1 requires less than an evening to assemble (and is fun to build, too!), we offer the TG-1 fully wired and tested in matching case for a special price.

TG-1, Tone Grabber Kit \$99.95

CTG, Matching Case Set for TG-1 Kit \$14.95

TG-1WT, Fully Wired Tone Grabber with Case \$149.95

AC12-5, 12 Volt DC Wall Plug Adapter \$9.95

Mini-Peeper Micro Video Camera



Super small, high quality fully assembled B & W CCD TV camera the size of an ice cube! Provides excellent pictures in low light (2 lux), or use our IR-1 Infra-Red light source to invisibly illuminate an entire room on a pitch black night! Imagine the possibilities... build it into a smoke detector, wall clock, lamp, book, radio. Exact same camera that's in big buck detective catalogues and stores. Kit includes: fully assembled CCD camera module, connectors, interface PC board kit with proper voltage regulation and filtering, hook-up details, even a mini microphone for sensitive sound! Two models available: Wide Angle Lens 3.6mm/12, adjustable focus lens, 92 degree view; Pinhole Lens 5.5mm/4.5, 60 degree view. The Pinhole Lens is physically much flatter and provides even greater depth of focus. The camera itself is 1.2" square. The Wide Angle Lens is about 1" long. Pinhole Lens about 1/2", interface PC board is 1" x 2" and uses RCA jacks for easy hook-up to VCRs, TVs or cable runs. Power required is 9 to 14 VDC @ 150 mA. Resolution: 380 x 350 lines. Instruction manual contains ideas on mounting and disguising the Mini-Peeper along with info on adding one of our TV Transmitter kits (such as the MTV-7 unit below) for wireless transmission!

MP-1, Wide Angle Lens CCD TV Camera Outfit \$169.95

MP-1PH, Pin-Hole Lens CCD TV Camera Outfit \$189.95

MicroStation Synthesized UHF TV Transmitter



Now you can be in the same league as James Bond. This transmitter is so small that it can fit into a pack of cigarettes - even including a CCD TV camera and battery! Model airplane enthusiasts put the MTV-7A into airplanes for a dynamite view from the cockpit, and the MTV-7A is the transmitter of choice for balloon launches. Transmitter features synthesized, crystal controlled operation for drift-free transmission of both audio and video on your choice of frequencies: Standard UHF TV Channel 52 (which should only be used outside of the USA to avoid violating FCC rules), and 439.25 MHz or 911.25 MHz which are in the amateur ham bands. The 439.25 MHz unit has the nifty advantage of being able to be received on a regular "cable-ready" TV set tuned to Cable channel 68, or use our ATV-74 converter and receive it on regular TV channel 3. The 911.25 MHz unit is suited for applications where reception on a regular TV is not desired, an ATV-79 must be used for operation. The MTV-7A's output power is almost 100 mW, so transmitting range is pretty much "line-of-sight" which can mean many miles! The MTV-7A accepts standard black and white or color video and has its own, on-board, sensitive electret microphone. The MTV-7A is available in kit form or fully wired and tested. Since the latest in SMT (Surface Mount Technology) is used to provide for the smallest possible size, the kit version is recommended for experienced builders only. Runs on 12 VDC @ 150 mA and includes a regulated power source for a CCD camera.

MTV-7A, UHF TV Channel 52 Transmitter Kit \$159.95

MTV-7AWT, Fully Wired Channel 52 Transmitter \$249.95

MTV-7A4, 439.25 MHz TV Transmitter Kit \$159.95

MTV-7A4WT, Fully Wired 439.25 MHz Transmitter \$249.95

MTV-7A9, 911.25 MHz TV Transmitter Kit \$179.95

MTV-7A9WT, Fully Wired 911.25 MHz Transmitter \$269.95

ATV-74, 439.25 MHz Converter Kit \$159.95

ATV-74WT, Fully Wired 439.25 MHz Converter \$249.95

ATV-79, 911.25 MHz Converter Kit \$179.95

ATV-79WT, Fully Wired 911.25 MHz Converter \$269.95

RAMSEY ELECTRONICS, INC.

793 Canning Parkway
Victor, NY 14564

Order Toll-free: 1-800-446-2295

Sorry, no tech info or order status at this number

Technical Info, Order Status
Call Factory direct: (716) 924-4560



ORDERING INFO: Satisfaction Guaranteed. Examine for 10 days, if not pleased, return in original form for refund. Add \$4.95 for shipping, handling and insurance. Orders under \$20, add \$3.00. NY residents add 7% sales tax. Sorry, no CODs. Foreign orders, add 20% for surface mail or use credit card and specify shipping method.

CABLE PRODUCTS & MORE! BEST PRICES! 1-800-663-8530. FORMERLY 1-800-MODULE-0.

UNBELIEVABLE PRICES. We carry a full line of cable tools and equipment for all your cable needs. Also a wide variety of electronic parts & accessories, tools, diagrams, converters, step-by-step instructions, and full technical support. 9am-7:30pm EST 1-800-562-8442.

\$ WANTED \$: Cash for genuine, unmodified PV5, PV7, R2/V5, and DBB converters. 512-854-8989 evenings.

WANTED TO buy: Current models Pioneer 5000 and 6000 series, genuine unmodified Tocom 5503 VIP 5507, SA 8550, 8570, 8580, etc. Genuine unmodified Jerrold DBBB 7312, PR20C, 7322P, DPV 7, etc. Call or fax. 718-262-0900, FAX 718-657-4015.

SSAVI: SAVVY Scrambling Today. Learn the secrets of this popular scrambling scheme. \$10. VISA/MC/AMEX. Free catalog. **ELECTROMAN**, Box 24474, New Orleans, LA 70184. 504-482-3017.

EQUIPMENT FOR ALL of your cable TV needs. All popular makes and models. Newest up-to-date items. Best prices. 717-462-4657.

CABLE PARTS! Computer parts. Call for great prices or visit us soon on the Web: [HTTP://WWW.CB-Electronics.com](http://WWW.CB-Electronics.com) or call 1-800-436-8630.

WANTED: DEALER & DEALERS! AUTO-MATE MULTIMODE 2200s. RFT-2 MULTIMATE 2200 SELLS! CONCEPT ENGINEERING 602-309-0367.

ELECTROMAN, YOUR source for video products, amplifiers, inverters, & processors. Free catalog. **ELECTROMAN**, Box 24474, New Orleans, LA 70184. 504-482-3017.

WE HAVE what you want. #1 cable distributors. Dealers welcome. For your best price, call 1-800-640-9948.

UNBELIEVABLE PRICES. We carry a full line of cable tools and equipment for all your cable needs. Also a wide variety of electronic parts & accessories, tools, diagrams, converters, step-by-step instructions, and full technical support. 9am-7:30pm EST 1-800-562-8442.

CABLE PRODUCTS & MORE! BEST PRICES! 1-800-663-8530. FORMERLY 1-800-MODULE-0.

AAA CABLE PRODUCTS. CALL US FOR ALL YOUR NEEDS! AUTOMATIC MULTIMODE SELLS. CONCEPT ENGINEERING 602-309-0367.

TELEPHONE/FAX

CELL PHONE cloning for the guy who has (two of) everything. Must have current service contract. Motorola, Tandy. For more info, call Keith, 512-259-4770.



CELLULAR PROGRAMMERS PACKAGE OFFER! Volumes 1 & 2 Cellular Hackers Bibles, Cellular Programmers Bible, Bagphone Video Bible, and Cloning Cellular Telephones Videos. Software for Motorola bag, flip, & brick, NEC, Panasonic, Nokia, & ESN loader chip. Also includes: OKI-900 package of software and documents! Complete package \$199. Postpaid USA. 520-726-2833. **TELECODE**, PO Box 6426-NV, Yuma, AZ 85366-6426. <http://www.hacker-scatalog.com>

BLUE BOOK PHONE REPAIR. Fix 500+ models; American Oak to Western Electric; answer machines, cordless, wired phones. \$25. KEN'S, 2825 Lake, Kalamazoo, MI 49001. 616-345-4609.

PHONE SYSTEMS WANTED!!! We buy AT&T MERLIN, SYSTEM 25/75/85 and other AT&T phone systems. Please call for a quote or fax us your equipment list. **KEYWAYS, INC.**, 513-847-2300 or FAX 513-847-2350.

THE MOST EXTRAORDINARY hacking catalog in the world! www.spectre-press.com

OCTEL VOICE mail system model Aspen Branch XP, 16 ports, 10 hrs. storage. Like new, with books, hook-up cables, and programming terminal. \$2,500. Call Rick 203-723-4459.

PANASONIC, SOUTHWESTERN Bell, BBS Telecom, telephones, jacks, and systems. Free catalog: voice or fax: 908-840-1390.

PARTY-LINE Caller-ID Phoneline Simulator Kit. Demonstrate telephone devices without phoneline! Six direct dial extensions, Caller-ID, distinctive ringing. Authentic dial tone, busy signals, 20Hz ringing. Deluxe kit \$199.95. Includes PCB, all electronic parts, microcontroller, documentation. Custom enclosure \$32.95. Fully assembled \$425. Shipping \$8. Major credit cards, money order. Digital Products Company, 134 Windstar Cir., Folsom, CA 95630. 916-985-7219, Fax 916-985-8460, E-Mail: DigProd@aol.com

CELLULAR EXTENSIONS \$60 plus shipping. Motorola loader phones \$200. Loader kits \$100. Quality used phones programmed on your number \$150 plus shipping. Call or E-Mail Stuart for details. 601-831-8708 after 5:30pm CST. E-Mail: ccomco@aol.com

NORTHERN TELECOM #2960 telephone network interfaces (RID/MTU). Easily converted into extension phone lockout. \$1.50 each, \$9.90 for ten, \$59 per hundred. Full docs available. **SYNERGETICS SURPLUS**, Box 809, Thatcher, AZ 85552. 520-428-4073. VISA/MC.


CELLULAR ESN READER: "ESP" extension service pro handheld model displays ESN, MIN, etc. w/many more advanced features. CALL FOR INFO. PROGRAMMERS: MOT, NEC, GE, AVX, SONY, MITS. CALL FOR INFO. **CELLTRONICS** 818-709-1143 OPEN 9-5 PST.

ESN READER connects between AR3000 or PRO-2006 scanner and personal computer, reads and logs to disk. Scanner and computer not included. \$995 US postal money order to Keith Perry, PO Box 816, Leander, Texas (78641). SASE for info. 512-259-4770.

OKI 900 chips. Original blank Toshiba TC54512AF chips for the OKI 900 cellular phones, \$50 each. Call Bob at 703-758-4643 and leave a message.

BEEPER, TWO-WAY radio repairs, modifications, duplications, all models, test equipment. Call TJ 718-341-1849, Fax 718-978-4616.

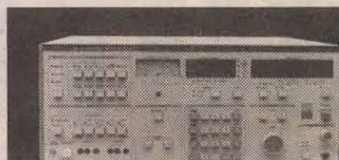OKI 900 MODIFIED program up to 5 number \$400. Also Cetek cable program. Use your OKI 900 as a cellular scanner. \$200. Purchaser agrees not to use the above mentioned equipment for illegal use. Call 708-614-7439.



Anritsu ML 422B

Selective Level Meter covers the 50 Hz to 30 MHz range, providing highly accurate measurements of signal levels, can function as a wideband level meter, psophometer or voice band analyzer. Opt 31.

New boxed \$1000.00

Hewlett-Packard 214B

Pulse Generator, high power 100 V, 2 A output into 50Ω, 10 MHz repetition rate, constant duty cycle.

New \$1995.00

Hewlett-Packard 427A

Voltmeter, measures dc voltages from 100 mV to 1 kV full scale, ac voltages from 10 mV to 300 V full scale at frequencies up to 1 MHz, 10Ω to 10 MΩ center scale in 7 decade ranges, New. Opt 001.

\$150.00

Ballantine 3046A


AC Voltmeter, primarily a dB meter, voltage ranges 1 mV to 300 V full scale, has a linear dB scale referenced to 1 mW into 600Ω, scale extends from 10 to +2 dB, voltage scales from .25 to 1.0 and .8 to 3.2. New, has rechargeable battery option.

\$150.00

★ JANUARY SPECIAL ★

"You won't believe this!"

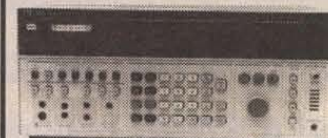Hewlett-Packard 3586B Selective Level Meter



Makes carrier measurements to 32.5 MHz, voice channel measurements from 50 Hz to 100 kHz, can use the 3336B Level Generator as an automatic tracking generator. With manual & 2 BNC adapters.

New Cost \$12,700.00

Our Price \$700.00

Ruggedized carrying case \$50.00

Quality Reconditioned Test Equipment

Hewlett-Packard 3582A


Spectrum Analyzer, .02 Hz to 25.5 kHz, band selectable analysis for .02 Hz resolution, sensitivity -120 dBv, 2 channel input, digital trace storage.

\$2500.00

Hewlett-Packard 141T Spectrum Analyzer System

141T with 8552B and 8553B. The mainframe provides variable persistence and storage. Covers 1 kHz to 110 MHz, 10 Hz resolution bw, high sensitivity -140 dBm.

Jan. Special \$1500.00

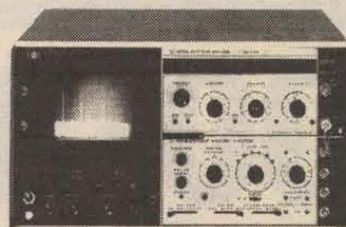

Hewlett-Packard 141T Spectrum Analyzer System

141T with 8552B/ 8555A. Covers from 10 MHz to 18 GHz, amplitude capabilities from +10 to -125 dBm.

Jan. Special \$2250.00

Midwest Microwave 1092

Step Attenuator, Dc to 18 GHz, 1 dB steps, .max input power 1.5 Watt, attenuation accuracy, connector type (N) f. New boxed.

Special Purchase \$239.00

JFW 75PD-001 Power Divider

2 Way Power Divider, Dc to 1000 frequency range, power division asymmetry (Dc to 500 MHz ±2 dB, 500 to 1000 MHz ±4 dB), 75 Ω impedance, input power 1 W average @ 25 C, 1000 W peak (1 microsecond).



\$12.50 or 2 for \$20.00

Please call for our Free 1996 Catalog

14455 NORTH 79TH STREET, UNIT #C • SCOTTSDALE, ARIZONA 85260
(602) 483-6202 • Fax (602) 483-6403

Write in 145 on Reader Service Card.

Wavetek 3520

Signal Generator, 1 to 2080 MHz, -137 to +10 dBm, frequency resolution is 100 Hz to 1040 MHz and 200 Hz to 2080 MHz, GPIB programmability.

\$3250.00

Tektronix 2213

60 MHz Oscilloscope, 2 mV sensitivity, 5 ns/div sweep speed, advanced trigger system, w/ probes.

\$650.00

Tektronix 2215

60 MHz Oscilloscope, dual channel, 2mV sensitivity, 5 ns/div sweep speed, advanced trigger system, with probes.

\$750.00

Fuke 6011A

Synthesized Signal Generator, 0.1 Hz (7 digit) resolution to 110 kHz; 10 Hz resolution to 11 MHz, storage up to 9 different frequencies, residual noise -50 dBc, harmonics -35 to -50 dBc, level flatness = 0.05 dB.

\$1000.00

ESI SR1030

Resistance Transfer Standards, set of 6: 1k, 10k, 100k, 1Ω, 10Ω, and 100 Ω. Like new condition.

\$4750.00

Hewlett-Packard 54100D

Digitizing Oscilloscope, 1 GHz bw, 350 ps rise time, 10 ps resolution, 40 ms/sec maximum digitizing rate, pre-trigger viewing, includes 3-HP 54002A 50Ω bnc input pods.

\$3500.00

Hewlett-Packard 54110D

Digitizing Oscilloscope, 1 GHz bw, digital storage, auto pulse parameter, pre-trigger viewing, with 4-54003A, 1 megohm, 10:1 probe pods.

\$4000.00



TONY TALLI'S ORIGINAL TELEVIEW DISTRIBUTORS

WHERE OUR VALUED CUSTOMERS' BUSINESS
IS HONESTLY APPRECIATED

**SERVING YOUR CABLE
NEEDS SINCE 1984**

1-800-847-3773

Vega One **ORDERS ALSO ACCEPTED**

Not
affiliated
with NCCA.

1-800-525-0428 P.M. SALES

Orders called in by 1:00 pm shipped same day. \$15 shipping.
NO NEVADA SALES • Hours: M-F 9-4 PST

FREE

**1 YEAR
SUBSCRIPTION TO
NUTS & VOLTS
WITH \$500.00
MIN. ORDER**

FREE Golf Hat with \$150 purchase.

FREE T-Shirt with \$500 purchase.

Call for this month's Nuts & Volts Specials

**YES!
WE HAVE
COUPONS!**

GIVE TELEVIEW TONY A CALL TODAY!

1-702-253-1852 • FAX 1-702-253-1854 • P.O. BOX 71465 • LAS VEGAS, NV 89170-1465

Tony Talli's Original Teleview is not affiliated with Teleview, Inc.,
NV Corp., or Teleview Distributors, Inc. of Illinois.





*For all your cable needs
Call us first!*

**SIX-MONTH GUARANTEE
(30-DAY MONEY BACK)**

**Phone 630-616-8050
or
Fax 630-616-8094**

For orders only: 1-800-742-2567

HOURS: MON.-FRI. 8-6 CST • SAT. 10-2 CST

Greenleaf Electronics • P.O. Box 538 • Bensenville, IL 60106

COMPUTER PARTS - SCSI DRIVE ACCESSORIES - SURPLUS ELECTRONICS

QTY DISCOUNTS AVAILABLE* - GOVERNMENT/EDUCATIONAL PURCHASE ORDERS ACCEPTED - APPLE II / MAC & IBM

MPEG & TV Tuner!
Miro 20TD
2MB VLB SVGA

Xing MPEG Player & Compton's Multimedia Encyclopedia CD's Included.
64Bit Windows Accelerated graphics. No jumpers to mess with, just install the software and go! Miro 20TD Live!
\$119.00

Visit Our Web Page
For specials and more info. on these items.
<http://www.allelec.com>

6 HH Bay SCSI Tower Case

- 200W P/S
 - 6 HH Bays
 - 6 ID Selectors
 - No-tip stands.
- All bays Open Face for CD ROM, SyQuest, Optical, Etc.
250 Pin Centronics Connectors & 6 IDC 50 Pin connectors. 6 SCSI ID Selectors.
- \$99.00**



Power Supplies

Power Supplies are Refurb unless Noted otherwise.
Mini Tower 145 Watts.\$12.00
Mini/Mid Tower 200W\$19.00
XT Power Supply. 135W\$10.00
XT Power Supply 150W\$15.00
IBM XT 65Watt\$5.00
Side Switch or remote wired
AT Power Supply. 200W\$19.00

FLOPPY & CD DRIVES

New 360K 5.25" HH Drive...\$10.00
Used 1.2 Meg 5.25" HH\$15.00
Used 720K 3.5" Drive.....\$10.00
New 1.44M 3.5" Drive\$25.00
CD ROM Drives
4x IDE Int. CD ROM Drive \$59.00
2x SCSI Int. CD ROM Drive \$39.00
1x SCSI Int CD ROM Drive \$24.00

External Drive Enclosures • SCSI • CD ROM • Floppy • Computer Cases

External Cases for:
All SCSI Cases have 250 Pin Centronics connectors and 30 Watt P/S. Open Face has RCA's for CD Audio
1 FH or 2 HH Floppy Drives w/ P/S\$19.00
1 HH 5.25" SCSI (Open Face).....\$35.00
1 HH 5.25" or 3.5" SCSI (Closed Face).....\$29.00
1 3.5" SCSI HD (Lunch Box Portable)\$19.00
2 CD's or SyQuest Side by Side\$45.00
1 IDE CD ROM w/cables\$49.00

EXTERNAL DRIVE CASES

\$19 to \$65.00



Monitors

Open frame composite 9". B&W Monitor assembly. Build your own monitor.\$19.00
9" B&W Security Monitor. "Box" type with 75 Ohm input\$59.00
9" Composite "Box" type cabinet. Green screen. Good for security monitor. Input for 75 Ohm (standard) or High impedance\$35.00
Color Composite Monitor. Not suitable for 80 column text but can be used for computer games, Nintendo, as a video monitor. Some have sound input also. Specify.\$69.00
Used/Refurbished Mono. DB9\$29.00

digital

ColorWriter 120ic
Inkjet Printer
(Refurb)
\$119.00



Monthly Specials

Cases • CD ROM Drives • Accessories

HP Colorado T1000 (Travan) Tape Backup Drive
400/800 Meg & Qic 40/80 R&W Compatible.....\$49.00
Seagate/Conner Travan CTT3200 Tape Drive...\$119.00
NSC WorkGroup 6 Port 10 Base T Hub.....\$69.00
"J" mouse keyboard.....\$24.00
PC Pals DOS/Windows Trackball.....\$14.95
230 Watt PS/2 Power Supply, NEW\$29.00
SIMM Converter 430 Pin to 172 Pin.....\$14.95
SIMM Quadripler 430 Pin in one 30 pin socket\$19.00
Apple Standard Mac Microphone\$9.00
Apple PlainTalk Microphone.....\$9.00
104Key Windows Keyboard\$14.95
IBM Compatible Mouse(PC 3-key, MS 2-key).....\$5.95



FREE!
With Min. \$50 Order
Mention this offer when you order!
Mono Wireless Headset!
Great for late night gaming, kids, etc.

NTSC Output • 1/3 inch CCD • FCC Class B
Fixed Focus 330 x 491 Resolution • 75 Ohm 6VDC Operation .27A • Approx 4" high. Great for C-U SeeMe / Internet use!
FULL MOTION COLOR



\$149

Alltech Electronics Co

2618 Temple Heights. Oceanside, CA 92056
\$25.00 Min. Purchase for Mail Orders

Phone Orders
619/724-2404
<http://www.allelec.com>
Fax: 619/724-8808
School & Government POs Accepted!
Phone Order Hours 9AM - 5:30PM Mon- Fri

3 Southern California Locations!
World Wide Web <http://www.allelec.com>
1300 E. Edinger. Santa Ana - 714/543-5011
2018 W. Lomita BLVD. Lomita - 310/539-2260
1401 El Camino Real. Oceanside - 619/721-0093
We buy surplus & unwanted computer inventory as well as scrap electronics related inventory.

386 System
Refurbished
1.2 or 1.44 Floppy
1024 K Ram
CGA Monitor
Keyboard
\$149.00

Motorola Cellular

Extra Life FlipPhone Btry.....\$9.95
Brick Phone Cig. Adapter. Inside is outlined for upper cncor. \$9.95
Flip Phone Cig. Adapter
Replaces the battery, does not plug into the bottom jack.\$9.95
Flip-Less Fone leather case\$9.95
Flip phone battey, leather case & cig. lighter adapter\$19.00

Accessories

Modem Madness!

Internal 2400 (PC).....\$9.95
Internal 2400 w/NMP1-5\$12.95
Internal 9600 v.32/v.42bis...\$19.95
Ext. 1200 Blue Motorola UDS...\$12.95
Ext. 2400 96/48 Fax (PC)\$15.00
Ext. 14.4K & Fax.....\$69.00

Fax & Data Modems

Ensoniq Soundscape



The Ensoniq Soundscape is a 16 Bit Soundcard with 32 Voice Capability. This card is music to your ears.
\$59

Colorado T1000 Tape B/U



Attaches to your floppy controller with provided cable. Travan 400MB / 800MB Compressed. QIC 40/80 Compatible.....\$49.00
TR-1 (T1000) 4/800MB Tape\$24.95

EPROMS

MICROCONTROLLERS

2716 or 273275¢
2764/27128/27256\$1.50
27512, 271000, 8748.....\$2.00
8749\$6.00
8751\$9.00

CHIPS & ROMS

Intel 486 SX-25\$14.95
Intel 486 DX2-50\$25.00
AMD 486X/2-66.....\$14.00
80287-8\$19.00
80387DX-33\$19.00
82450\$2.00 8250\$1.00

RAM
Shortlead 41256 -10.60¢ -08.75¢
41024-10 (1 Meg x 1) or 44256 -12\$1.50 -10.\$2.00 -80/-70\$2.50
256x8-15 SIMM.....\$3.00 /-12.\$3.00
256x9 SIMM-80.....\$3.00
1 Meg x 9-10 SIMM\$6.00
1 Meg x 9-80 SIMM\$7.00
1 Meg x 9-70 SIMM\$9.00

Batteries
1/2 AA size, 3.6V lithium.....\$6.95
AT type "plug in" 3.6V or 6V\$6.95

PC Cards & Accessories

9 Pin Serial Mouse.....\$9.00
Microsoft InPort Bus Mouse Card\$9.00
30 to 72 Pin SIMM Converter (430 to 172)\$14.95
Sony 256K Pipeline Cache, 80pin standard\$14.95
IBM Aptiva 8 Way Joystick\$9.95
CGA/EGA Video Card\$19.00
EGA Video Card.....\$14.95
AT MFM HD Only Controller.....\$9.95
AT 2 Meg Mem. Exp Card w/2 Meg\$19.00
RAM Sack III AT/386 up to 8 Meg card (OK).....\$19.95
5 Pin kybd to PS/2 adapter (Specify direction)\$2.95
8 Bit VGA Card\$17.00
AT Floppy, Serial & Par Controller\$9.95
Super I/O IDE, Floppy, 2 Serial, 1 Parallel\$14.95
AT MFM HD & Floppy Ctrl\$14.95
AT IDE HD Controller\$4.95
Mono/Parallel Port.....\$9.95
Full Length CGA w/RCA out.....\$14.95
32 Bit Mem Exp. (9 Meg/OK) SiliconValley\$20.00
101 XT/AT Keyboard\$29.00
101 AT Keyboard (NEW)\$14.95
Slot Expanders (3/4 or 5 Slot, for slim type PC cases) Installs in single slot and rises vertically\$9.95
XT Motherboard\$14.95
AT Motherboard w/1024K\$29.95

CA Residents please add 7.25% Sales tax. * Minimum shipping & handling charges \$6.50. * Warranty: Used/Refurbished products have a 90 day warranty. * ALL Returns must have an RMA #, call before shipping back to us. * No Returns without an invoice. Shipping & Handling charges are non-refundable. * 20% Restocking charge, applies to products purchased in error & incompatibility problems. School & University Purchase Orders accepted, others on AOC only. * Prices and availability subject to change at anytime without any notification whatsoever.

RS-232 DIGITAL INPUT/OUTPUT

BY TERRY J. WEEDER

The potential to write/create computer programs to incorporate into your own custom applications is an asset which every computer owner has, though most seem to overlook it or just plain take this for granted. Sure, all the bells and whistles, and fancy graphics accompanying the herd of software packages which come with your computer keep you entertained at first, however, you still have not truly discovered the capability of this desktop tool until you've jumped in and started building your own programs.

If you've never tried it before and don't know where to start, check out that easy-to-learn programming language called QBASIC which can be found in your DOS directory. Of course, in order to fully appreciate the power at hand, being able to link these programs with external switches and relays is a must, and can now be accomplished using your serial port and an I/O module costing as little as \$32.00.

The RS-232 digital input/output module as described in this text connects directly to the serial port of a PC and enables your home-brewed computer program to interact with its outside environment. Twelve I/O pins are available and can be individually configured for input or output. The module is addressable using a DIP switch setting on the board, and is specifically designed to share the same RS-232 port with other units. Up to 16 units may be stacked in parallel on the same com port allowing a total of 192 I/O points.

Using an I/O pin for an input allows your program to sense button presses, change of state of switches, alarm trips, etc. Setting a pin for an output will let your program turn on/off electrical devices with the aid of a relay, triac, or switching transistor. In addition, there are a few special commands which use 8 of the 12 I/O pins as a group. A 4x4 matrix keypad can be decoded allowing

access panel activating an electro-mechanical lock, or a control panel for your computer-based alarm system. You can also read or write an eight-bit word directly to these eight I/O pins.

The set of commands which can be issued from

FIGURE 1 25-PIN



9-PIN



Pin diagram for both a 9 and 25 pin RS-232 connector. Wire the "RD," "TD," "DTR," and "SG" pads on the I/O board to the corresponding pins of your connector. Include the jumpers as shown.

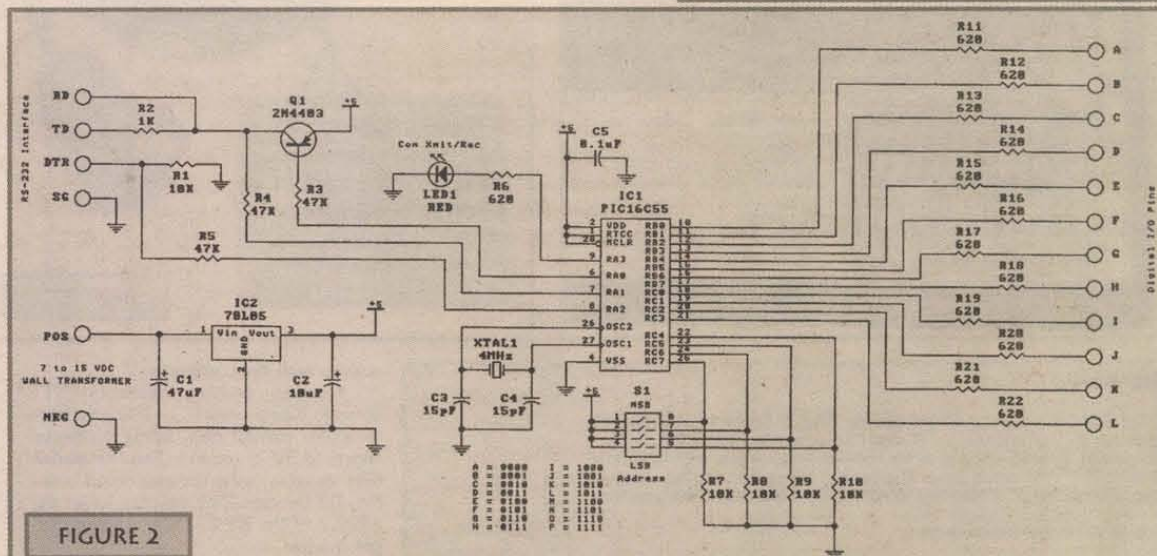


FIGURE 2

Schematic diagram of the I/O module. The microcontroller (IC1) is manipulated by the PC via the serial port — acting on specified I/O pins, and reporting any action sensed by an I/O pin.

16 buttons to be monitored using only eight I/O pins. These keypads come in handy to use, for instance, on a security

your program via the com port to configure and control the I/O module is shown in Listing 1. These include:

HIGH/LOW — Sets a specified I/O pin to a desired state.

TOGGLE — Changes a specified I/O pin to the opposite state.

BUTTON — Configures a specified I/O pin to sense a button press using automatic debounce and repeat if the button is held down.

SWITCH — Configures a specified I/O pin to sense a switch transition using automatic debounce.

MATRIX — Configures the first eight I/O pins to be used to decode a 4x4 matrix keypad using automatic debounce and repeat.

READ — Reads the state of a specified I/O pin, or reads the first eight I/O pins as an eight-bit port.

WRITE — Writes data to the first eight I/O pins as an eight-bit port. Data can be in the format of hex, binary, or an ASCII character.

Circuit Theory

Refer to the schematic diagram shown in Figure 2. The heart of the circuit is IC1 (part no. PIC16C55-XT/P), an EPROM-based eight-bit CMOS microcontroller manufactured by Microchip. This microcontroller has two eight-bit I/O ports, one four-bit I/O port, and an internal EPROM memory which holds the program used for encoding/decoding the data sent to and from the computer, reading and writing to the I/O pins, and reading the DIP switch setting (S1) which sets the board address. Crystal (XTAL1) sets the clock frequency. A detailed description of IC1's firmware is explained later.

The voltage levels used for serial communications on an RS-232 port are +3V to +25V for a logic 0, and -3V to -25V for a logic 1. Most RS-232 devices use +12V and -12V, respectively. Bit 0 of port-A is used to send data to the serial port. A logic 1 is generated by placing bit 0 at a high level which turns off Q1, thus allowing the -12V from the TD (Transmit Data) pin to be applied to the RD (Receive Data) pin through R2.

Bit 0 is sent low to produce a logic 0 which turns on Q1, pulling the RD pin to +5V. Because the TD pin of an RS-

LISTING 1

COMMAND SET TITLE	COMMAND	DESCRIPTION
HIGH	H pin	Make pin an output and set it high (pin = A-L).
LOW	L pin	Make pin an output and set it low (pin = A-L).
TOGGLE	T pin	Make pin an output and toggle state (pin = A-L).
BUTTON	B pin	Make pin an input and respond to button press. Returns "pinL" when pressed (pin = A-L).
SWITCH	S pin	Make pin an input and respond to switch transition. Returns "pinL" or "pinH" when toggled (pin = A-L).
MATRIX	M	Make pins A-D an output, pins E-H an input, and decodes 4x4 matrix keypad presses. Returns "Mrow,col" (row = A-D, col = E-H).
READ	R pin	If pin = A-L, make pin an input and read state. Returns "pinH" or "pinL." If pin = P, make pins A-H an input and read pins as eight-bit port.
WRITE	Wfd	Make pins A-H an output and writes data(d) to pins as eight-bit port; format(f) can be "h" for hex, "b" for binary, or "s" for ASCII character.

Note, all commands must be preceded by the WTDIO header character D, and address character A-P. All responses from the WTDIO will also contain this preface.

Have your QBASIC program send these commands out the comport to control the I/O module.



 



PHOTO 1

 


64 January 1997/Nuts & Volts Magazine

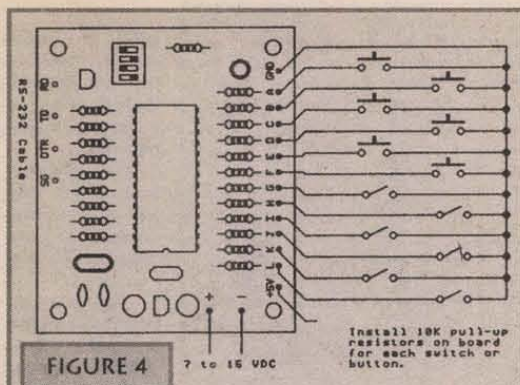

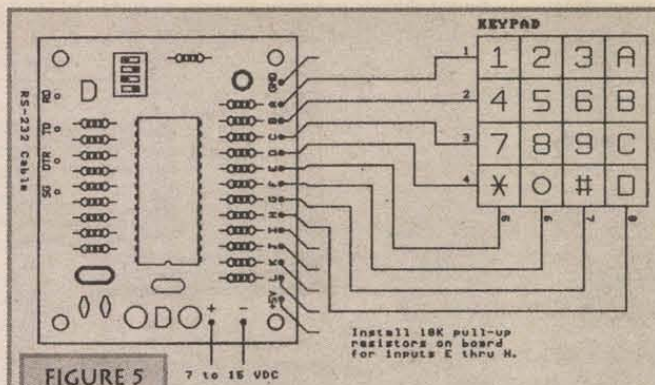
Notice the ease at which the I/O module can be wired up to switches, buttons, or alarm contacts.



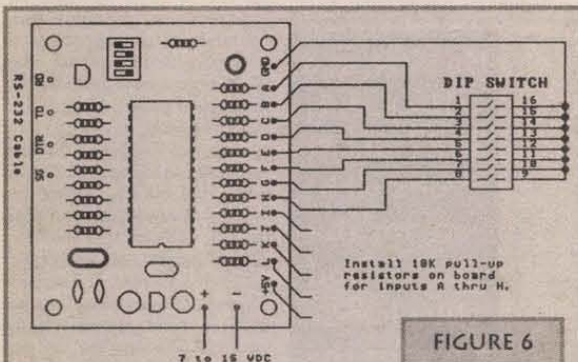
Decode a 4x4 matrix keypad using this set-up.



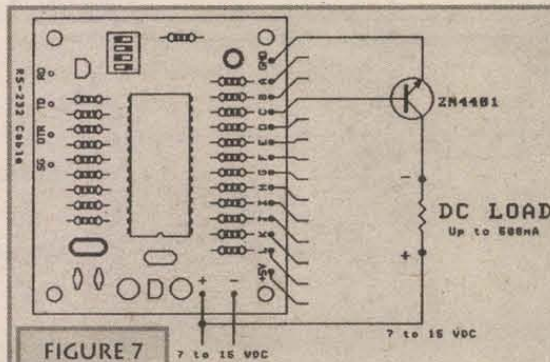A DIP switch can be used with the READ command to set/change a variable or configuration within your program from a remote location.



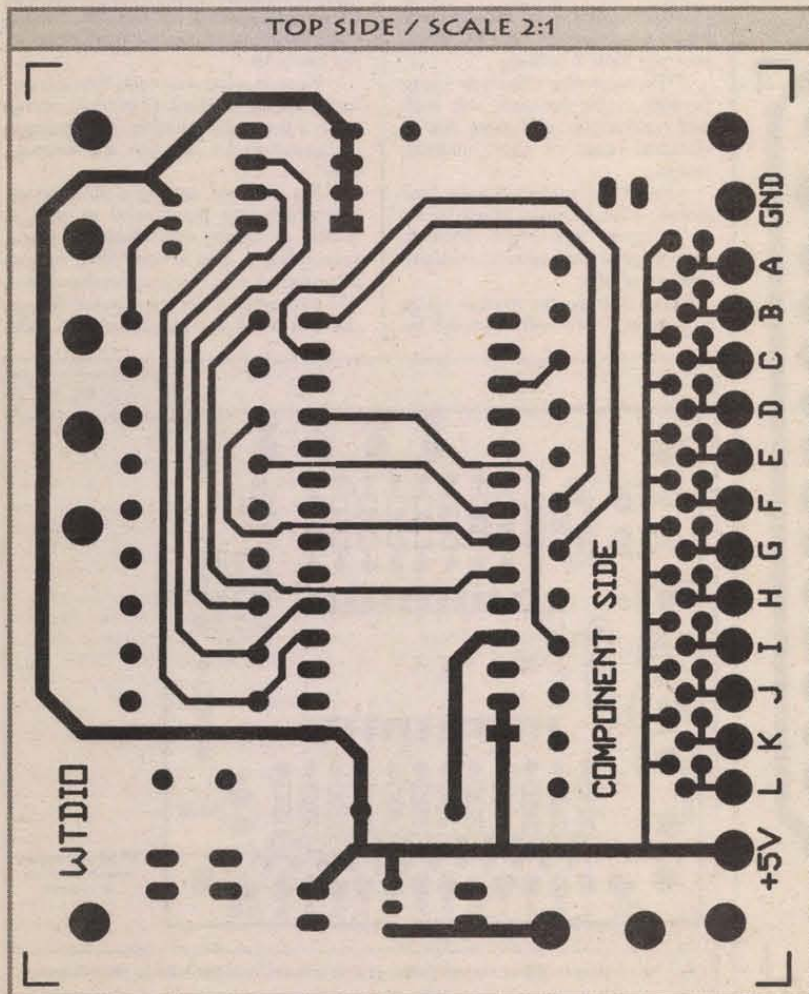Turn on/off a DC load up to 500mA using this circuit.



solder, if necessary. Carefully plug IC1 into its socket using the orientation as shown in the parts placement diagram.

Operation

The RS-232 digital input/output kit can share the same serial port as other kits of its kind simply by wiring each kit in parallel to the same RS-232 connector. You must, however, remove R1 and R2 on any subsequent kit, i.e., of all the kits paralleled on the same port, only one kit should have R1 and R2 installed).

Doing this will allow you to piggyback up to 16 I/O modules and use them on the same port which currently supports the home automation controller and/or telephone/computer interface kits as described in the July/August '96 issues of *Nuts & Volts*.

Solder a solid-conductor wire onto each I/O pad (A through L) and run the opposite ends to a solderless breadboard, as shown in Photo 1. Use the set-up shown in Figure 3 along with the simple QBASIC program shown in Listing 2 to test out your circuit.

Plug the wall transformer into an electrical outlet and plug the RS-232 connector into your PC. Note: Always apply power to your kit before plugging into an active RS-232 port or the oscillator may fail to start.

Start the program, then hit "C" on your keyboard. A prompt will appear asking you to type in a command. Type "HA" — using caps — then hit enter. LED1 will flash as

the unit receives the data from the serial port, then the I/O pin labeled "A" will change to an output and be set high, which will turn on its LED on the breadboard.

Hit "C" again and type in "LA." This will set I/O pin "A" back to low, thus turning off the LED. Try this command using each I/O pin label and watch as the corresponding LEDs turn on and off.

If LED1 on the I/O board does not flash when sending data out the com port, there is either a wiring error in your serial cable or your program is not accessing the correct port. Closely examine your cable including the jumpers on the RS-232 connector, and verify that the serial port you are plugging into is the same one you are opening in your QBASIC program.

With correct hook-up to the serial port, and the QBASIC program not running, the DTR, TD, and RD pads on the board will all be a negative voltage. After starting the program, the DTR pad will change to a positive voltage.

The WRITE command can be used to send an eight-bit word to pins A through H, and can be of three different formats selected by the character which precedes the data. For example, decimal value 74 can be sent as a hex character pair using the syntax "Wh4A," as a binary string using "Wb01001010," or as an ASCII character using "W\$J."

Creating Your Own Program

The RS-232 digital input/output module communicates at 1200 baud, no parity, eight data bits and one stop bit. Your program should contain the line OPEN "COM1:1200,N,8,1" FOR RANDOM AS #1, or similar. Also, the ON COM GOSUB statement should be used as shown in the sample program to handle branching to a subroutine when data is received from the module.

All data sent by the I/O module to the serial port is preceded by the header character (D) and the board address character (A-P), then ending with a carriage return. All commands sent by the PC to the I/O module must also be preceded by these header and address characters.

Two important notes here: because of the structure of the RS-232 interface used by the I/O module, all characters that are sent to the module are also echoed back to the PC. Therefore, your program must use the COM(1) OFF statement prior to using the PRINT #1, and then a LINE INPUT #1 statement to dump all echoed characters in the buffer before issuing a COM(1) ON statement.

Also, always use the COM(1) OFF statement at the beginning of your subroutine branched to by the ON COM GOSUB statement, then a COM(1) ON statement at the end, after all characters have been received. Failure to turn off event trapping as mentioned above will cause communications errors between the PC and the I/O module.

Figure 4 demonstrates the ease at which this module can be wired to buttons and switches. Pull-up resistors should be installed on the I/O board for each; these can be mounted vertically in the extra holes provided near the I/O pads.

Normally-closed alarm zones can be

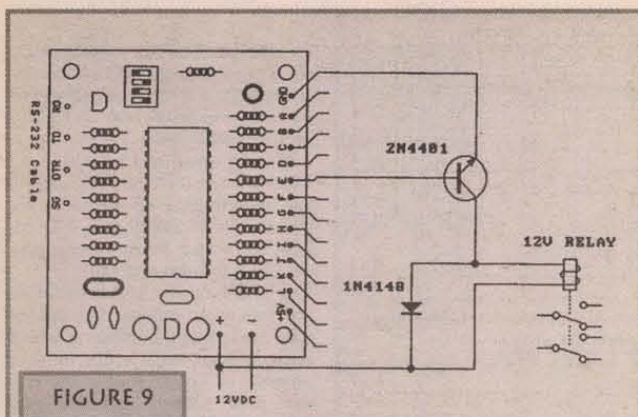


FIGURE 9

For larger currents, a relay can be used as shown. Supply voltage should be that which is required by the relay (up to 25 VDC).

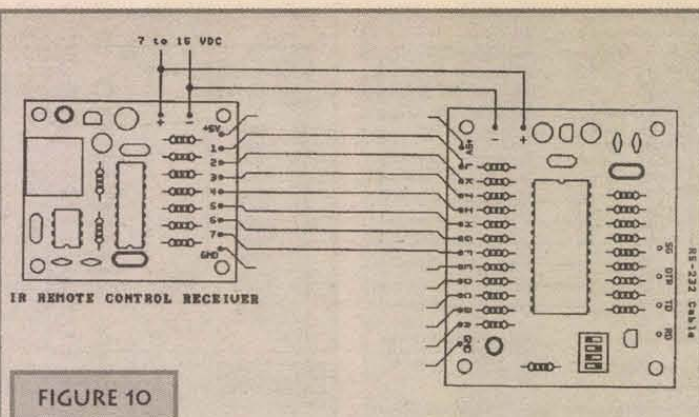


FIGURE 10

A standard TV remote transmitter can send commands to your PC using the IR remote control receiver kit as shown here (see source mentioned in parts list).

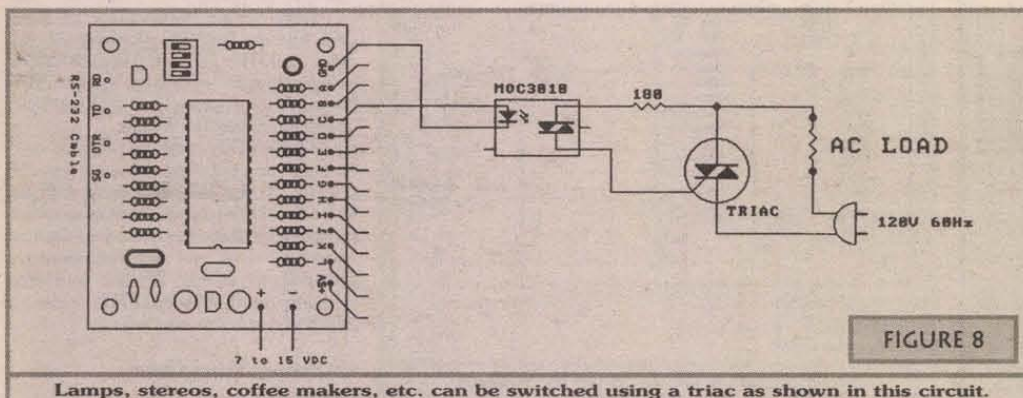


FIGURE 8

Lamps, stereos, coffee makers, etc. can be switched using a triac as shown in this circuit.

Be sure and check out the Nuts & Volts web site for the source and object code files for the PIC!


figuration or variable within a program which issues the READ command periodically. Again, use pull-up resistors on the input pins.

Figures 7 through 9 give examples of using an I/O pin with the HIGH, LOW, or TOGGLE commands to turn on/off electrical devices. These circuits can be copied on each I/O pin. A standard TV remote transmitter can be used to send commands to your PC using the set-up shown in Figure 10.

Configure these I/O pins for switches and have your program respond to the transitions. Detailed information about the IR remote control receiver kit can be obtained from the source mentioned in the parts list.

Keep in mind that each time a command is sent to the I/O module acting upon a particular I/O pin, any previous configuration for that pin will be canceled.

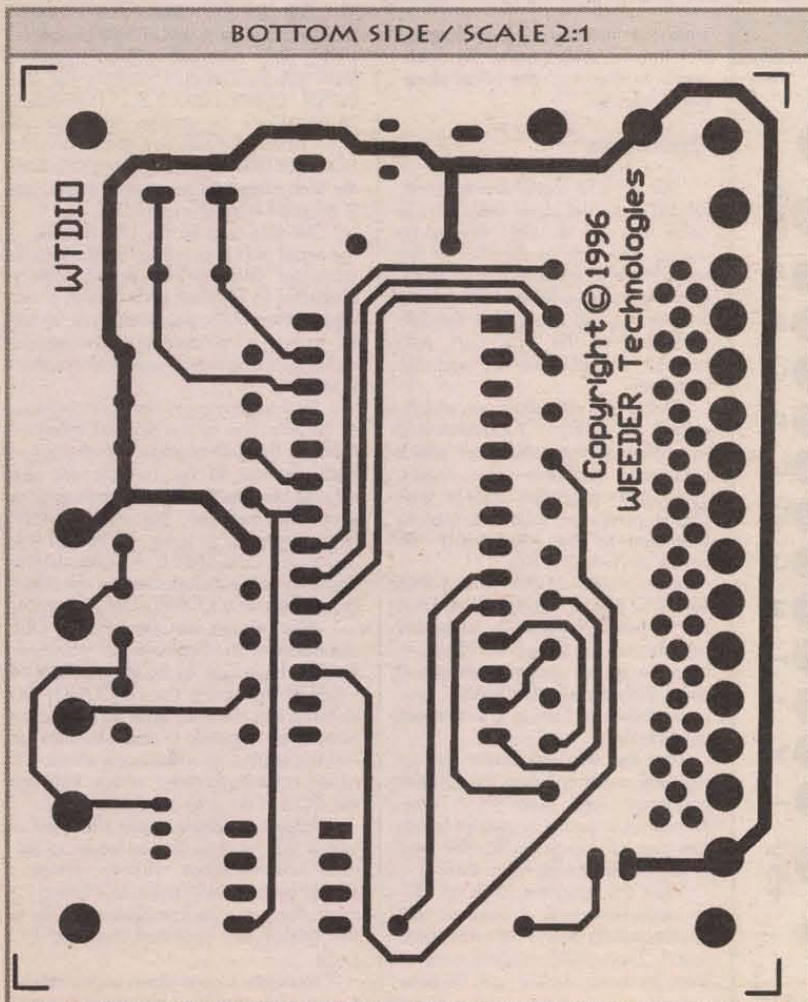For instance, setting a pin high or low which was being used to read a switch or button will disable it from responding to that action. Also, issuing a command which acts upon any of the I/O pins used for decoding a matrix keypad will disable the matrix function. NV




wired to each of the 12 inputs. Configuring these for switches will return a response to your PC whenever any loop is broken.

The automatic debounce incorporated in the firmware will work well, preventing false trips due to electrical noise or short intermit- tences.

To further protect against false alarms, your program could be set up to ignore trips which return to their original state within a minimal amount of time.

Figure 5 shows the module set-up to decode a 4x4 matrix keypad. Be

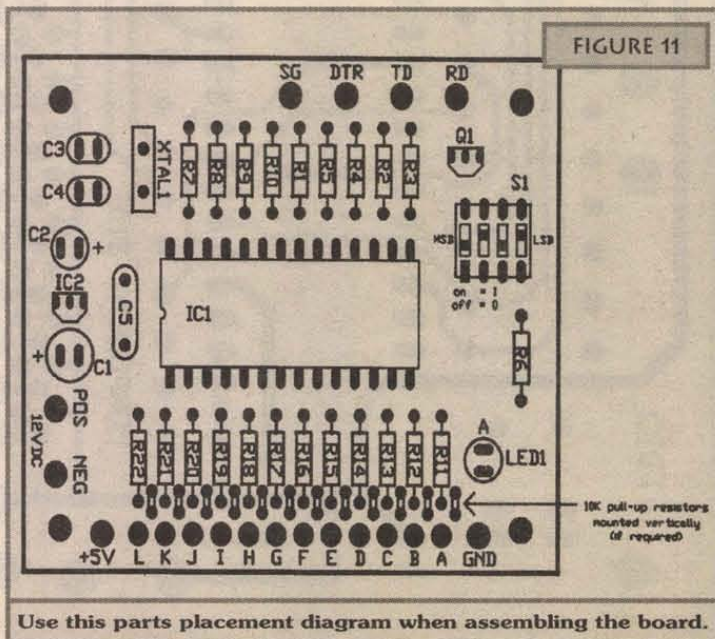

Use this parts placement diagram when assembling the board.

Nuts & Volts Magazine/January 1997 67



\$89-\$399 SALE, EXTENSION CELLULAR PHONES. MOTOROLA, REFURBISHED WITH ACCESSORIES, IDEAL FOR BACK-UP EMERGENCY USE. PHONE IS ACTIVATED TO ACT AS EXTENSION PHONE OF YOUR PRESENT CONTRACTED TELEPHONE NUMBER (NAN AND YOUR PERSONAL ESN NUMBER). REFURBISHED PHONES PRICE INCLUDES ACTIVATION TO EXTENSION, NEW ACCESSORIES: EXTENDED LIFE BATTERY, LEATHER CARRY CASE, AC BATTERY CHARGER AND BONUS DC CAR CHARGER! MODEL 8000 BRICK PHONE \$89, ULTRA CLASSIC SLIM \$129, ULTRA CLASSIC II, WITH MEMO/3 PRIORITY HOT KEYS \$149, MOTOROLA FLIP \$179, LITE FLIP \$269, ELITE FLIP WITH ANSWERING MACHINE \$399. BAG PHONE ATTACHE LOW PROFILE SERIES III, 3 WATT CAR PHONE, PLUGS INTO CAR CIGARETTE LIGHTER JACK, INCLUDES INTEGRAL BATTERY & AC CHARGER NOW \$139. 90-DAY DEFECTIVE EXCHANGE WARRANTY. TO ORDER: ACTIVATED-EXTENSION CELLULAR PHONE, REQUIRES MAILED OR FAXED COPY OF YOUR CELLULAR CARRIER'S ACTIVATION SERVICE CONTRACT. CATALOG/INFORMATION TELEPHONE OR FAX 702-642-3558 OR <http://www.lessbustlers.com> S&H CHARGES FEDEX AIR COD \$19.95 PER ORDER, USA POSTAL MONEY ORDER OR CASHIERS CHECK ONLY. SORRY NO NEVADA SALES. TELEPHONE/FAX ORDERS ONLY. (OUR 4TH YEAR OF SALES NUTS & VOLTS MAGAZINE, 99.5% SATISFIED CUSTOMERS) LESS BUSTER'S ELECTRONICS, 2039 CIVIC CENTER DRIVE #176 N. LAS VEGAS, NV 89030.



UJ'S GENIE MARK I KEYPAD ESN PROGRAMMER. NOW AVAILABLE for Motorola cellular phones (flip/pocket) with 8 pin data port jack, firmwares to 96C1 (includes EE-2-3). The Genie is completely portable, fits in shirt pocket (3"x2"x1"), utilizes CPs keypad & battery for programming. Genie includes modified Motorola 8 pin interface cable (no dangling wires or IC clips), dual voltage automatic NiCad car-battery charger and UJ's 80 page cellular technicians programming manual, price \$1,495. **GENIE MARK II** programs all 15 pin D/P Startups 10 pin D/P Elites & 8 pin D/P flip/pocket phones including EE-2-3 versions to 96C1. \$1,995. MK-1 upgrade to MK-2 \$395, both available late APRIL '97. Other upgrades to follow. The Genie is manufactured in the USA and includes quick, full free technical back-up (all products) check with our 99.5% satisfied customers. **WINTER SALE: UJ'S OLD FAITHFUL, INEXPENSIVE EMULATOR SYSTEM, PROGRAMS ALL MOTOROLA PHONES TO FIRMWARE 9525. REGULAR PRICE \$399 NOW \$299, INTERFACE CABLE SETS \$129 now \$99. UJ'S 80 PAGE CELLULAR PROGRAMMERS MANUAL: \$19.95 FREE WITH \$99 OR MORE ORDER. NEW: WHOLESALE/RETAIL SALES CELLULAR PHONE ACCESSORIES. FREE CATALOG & DETAILS ALL PRODUCTS CALL 702-642-0325 or <http://www.lessbustlers.com> LESS BUSTER'S ELECTRONICS (OUR 4TH YEAR SALES N&V MAGAZINE, 99.5% SATISFIED CUSTOMERS!), 2039 CIVIC CENTER DRIVE #176, N. LAS VEGAS, NV 89030.**

MODIFIED OKI 900. BEST DEALS AROUND. UNMODIFIED OKI 900 US \$275. MODIFIED OKI 900 US \$375. Up to 5 NAM/ESN. WE ACCEPT COD. CALL 905-790-8111 FOR FURTHER INFORMATION.

WANTED: AUDIOVOX cellular interface STI-85 (or spectrum equivalent 2-08AVMT1-00), new or used. Jeffrey Race, Fax 617-623-1882 or jrace@ibm.net

FIVE ESN/NAM modification installed in your OKI 900 for \$250. Chip only \$150. Phone with chip \$600. Call Keith at 512-259-4770.

COMPONENTS

FIBERGLASS: COMPLETE line. Round tube, square tube, solid rod, quad spreaders, masts, crossbooms. Visit <http://www.aaw.com/mgs> for list. Max-Gain Systems, Inc., 221 Greencrest, Marietta, GA 30068-3825.

LOW, LOW prices for high quality overstocked parts. Call 817-561-2999. IME, PO Box 170415, Arlington, TX 76003.

ELECTRONIC PARTS catalog two stamps. Dan's Small Parts, Box 3634, Missoula, MT 59806. Ph/Fax 406-258-2782. Online catalog <http://www.fix.net/dans.html>

I WANT it and I want it now. I want all of your SIMM memory. IBM, Mac, new, used, even defective. I want it all. Highest \$ paid. Now selling memory. We can beat any printed price in Nuts & Volts. Call 1-800-4-MEMORY now! Voice/FAX.

CRTs CHEAP. Buy direct from the manufacturer. Save money. Mfg. all CRT types since 1950. 3 year warranty. Reg-Res 19" tubes \$75; 25" \$100; hi-res 13" tubes from \$80. We specialize in hi-resolution video/computer CRTs. T.M.C. 215-226-0749/215-223-0388.

VACUUM VARIABLES and vacuum relays. Jennings RF4B ceramic latching SPST, coils 26VDC, contacts 30A, 8KV, \$9.50! SASE for list. E-Mail: mgs@avana.net Bond, 221 Greencrest, Marietta, GA 30068-3825.

ICs CHEAP: DIP pkg 74AS00, 02, also 04, F00, 04, 08, HC157, HCT04, LS03, 157, MC14163BCP, 79L05ACP-T092. All 12¢ ea. Sold full tubes only, \$25 min. Visa, M/C. Fax us your semi-reqs. Great prices. Abbott Electronics. Ph. 617-935-2040, Fax 617-933-7127.

RESISTORS 20 FOR \$1. Catalog \$1. Foreign add \$1. ZIPFAST, Box 12238, Lexington, KY 40581-2238.

WE BUY gold plated parts, transistors, hybrids, ICs, diodes, circuit boards, patch panels, military pins, tantalum capacitors, relays, old test equipment and all types of electronic material. **GOLD'N WEST SURPLUS** in Corona. Ph: 909-340-1501, FAX: 909-340-1504. ASK FOR MARK.

24 Hr. Shipping

To Order Call 1-800-292-7711 Fax: (847) 541-9904

Quality Kits for Hobbyist and Students

Micro-Master® MM-8000K

Starting from scratch, you can build a complete computer system. Elenco's Micro-Master® Trainer teaches you to write the initial instructions in permanent memory in a 2816 EPROM. Teaches you all about input and output ports and computer timers. Build your own keyboard and learn how to scan keyboard and display. No previous computer knowledge required. Simple, easy-to-understand instruction teaches you to write in machine language. Upon completion of this course, you will be proficient in computer technology. Complete with 126 page lesson manual, instructions and experiments.

\$99



TK-1000

All the tools you'll need to build these kits. 25 tools contained in a heavy-duty carrying case.


\$39.95



Stereo Cassette Player Kit Model TR-18K

- Transparent Case
- Belt Clip
- High Resolution
- Includes Headphones

\$15.95

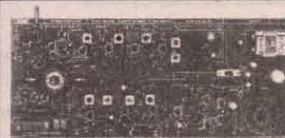

AM/FM-108K

\$29.95

AM/FM Radio Kit and Training Course 14 Transistors and 5 Diodes

Training course of 52 pages is divided into 9 lessons: Audio Amplifier, AM Detector, AM IF, AM Amplifier, AM Mixer & Oscillator, FM Detector, 1st FM IF, FM RF Stages. "Superheterodyne" receiver of standard AM (amplitude modulation) and FM (frequency modulated) broadcast frequencies. (PC board 11 5/8" x 5 1/4")

AM Radio Kit and Training Course 7 Transistors and 1 Diode \$19.95

XK-550 Digital / Analog Trainer

Elenco's advanced designed Digital / Analog Trainer is specially designed for school projects. It is built on a single PC board for maximum reliability. It includes 5 built-in power supplies, a function generator with continuously sine, triangular and square wave forms. 1500 tie point breadboard area.

XK-550
Assembled and
Tested
\$169.95

XK-550K - Kit
\$139.95



Tools and meter shown optional

M-2665K

Deluxe Full Function Digital Multimeter Kit



Extra large 1 1/4" x 2 1/2" LCD display area, 3 1/2 digit display, 34 ranges (cap., trans. test, diode test).

\$54.95

M-1005K

Digital Multimeter Kit



Low cost, 3 1/2 digit LCD, 18 ranges, transistor test, diode test, overload protection and pocket size.

\$19.95

FG-500K

100KHz Function Generator Kit




Provides sine, square or saw tooth waveforms continuously variable 1Hz to 100KHz. Amplitude adjustable to 2.5V peak to peak. Complete with all parts, PC board, schematic, deluxe case with handle and extensive assembly manual.

\$34.95

FO-30K

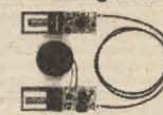Fiber Optics Technology with training course



Learn the basics of fiber optics data communications while you build this exciting kit. Comes complete with all necessary components. \$19.95

Robotic Arm Y-01

The Movit Robotic Arm is an educational kit that teaches the fundamentals of a basic robotic arm as well as your own motor skills.



\$59.95

Sound Activated Switch

Clap and the light comes on, clap again and off it goes.



\$8.95

Christmas Tree Kit Model K-14

The Christmas Tree Kit comes with a uniquely shaped Christmas Tree PC board. Eight (8) green and red LEDs produce a dazzling effect.

\$11.95

Motion Detector Kit

SS-50K

Compact and portable. Adds safety to your home & office.



\$18.95

Telephone Line Analyzer Kit

Model TT-400K



A telephone line analyzer that provides fast indication of telephone line polarity, ring and line voltage levels.

\$19.95

Telephone Kit Model PT-223K

Build this high-tech see-thru plastic telephone. Learn theory on how telephones work and then proudly show off your work with the transparent phone case. Complete with all parts and manual. Neon lamps flash when the phone rings.



\$15.95

Telephone Hold Button

Put all incoming and outgoing calls on hold at the press of a button.



K-18
\$6.50

Strobe Light

Produces a bright flash via xenon flash tube. The flashing rate is adjustable.



K-12A
\$8.95

0-15V Power Supply

A low-cost way to supply voltage to electronic games, etc.



\$14.95

K-11

Telephone Bug

Size of a dime yet transmits both sides of a phone conversation to any FM radio. No battery needed.



K-35
\$8.95

FM Mic

Transmit your voice on any FM radio. Range up to 100ft. Case incl.



K-30
\$9.95

WE WILL NOT BE UNDERSOLD

UPS SHIPPING: 48 STATES 5%
IL Residents add 8% Sales Tax

C&S SALES, INC.

150 W. CARPENTER AVENUE
WHEELING, IL 60090
FAX: (847) 520-9904 (847) 541-0710
http://www.elenco.com/cs_sales



2 year warranty on all parts and free technical support.

Prices subject to change without notice



2.4 GHZ VIDEO/AUDIO TRANSMITTER/RECEIVER

4 Channels, 300 Foot Range,
Cables and AC Adapter Included

\$160

2.4 GHz Video/Audio
Transmitter/Receiver w/Remote & IR Control Option **\$225**

DBS 14" Antenna and Downconverter **\$195**

Color CCD Camera **\$195**

ALJON TECHNOLOGIES, INC.

3892 Del Amo Blvd. #703, Torrance, CA 90503

Tel **(310) 793-1788**

Major Credit Cards Accepted

Write in 39 on Reader Service Card.

Miniature Transmitters and Receivers

Small, Attractive, High End Quality, 2 Channel Transmitter
\$9,049 Settable Codes, 150'-300' Range, 1-1/4"x2"x7/16", Assembled

	Qty	1	5	10
RF300T 150' Transmitter		24.95	19.95	15.95
RF300XT 300' Range Transmitter		29.95	24.95	19.95

Small, High End Quality, Receiver for the RF300 Transmitters
1-1/4"x3-3/4"x9/16", 8-24 vdc CMOS Input / Outputs, PCB

RF300R Receiver, assembled	24.95	20.95	16.95
RF300RK Receiver, Parts Kit	19.95	15.95	12.95

Small, Economical, Transmitter and Receiver Set
Set Code, 60' Range, 1-7/8"x2-3/8"x7/16" (T), 2"x2-3/4"x9/16" (R)
RF60 Transmitter and Receiver 24.95 19.95 14.95

Add \$4 shipping for first item + \$1 for each additional item. Ca. residents add 8.25% tax
Visa, Mastercard, Money Orders, Personal Checks and Cash C.O.D.s

Visitec Inc. (510) 651-1425 Fax (510) 651-8454
P.O. Box 14156 Fremont, CA. 94539

Write in 28 on Reader Service Card.

ABC ELECTRONICS 315 7TH AVE N. MPLS. MN. 55401 (612)332-2378 FAX (612)332-8481 30 DAY WARRANTY WE BUY TEST EQUIPMENT AND COMPONENTS.

TEK 7A13 DIFFERENTIAL COMPARATOR	\$150.00	TEK 7B15 1 GHZ DELAYING TIME BASE	\$250.00
TEK 7A16P PROG.200MHZ VERT. AMPLIFIER	\$75.00	TEK 7B50A 150 MHZ TIME BASE	\$75.00
TEK 7A17 150 MHZ SINGLE TRACE AMPLIFIER	\$50.00	TEK 7B52 DUAL TIME BASE	\$75.00
TEK 7A18 75 MHZ DUAL TRACE AMPLIFIER	\$50.00	TEK 7B53 100 MHZ DUAL TIME BASE	\$75.00
TEK 7A19 600 MHZ SINGLE TRACE AMPLIFIER	\$150.00	TEK 7B70 200 MHZ TIME BASE	\$75.00
TEK 7A22 DIFFERENTIAL AMPLIFIER	\$200.00	TEK 7B71 DELAYING TIME BASE	\$75.00
TEK 7A24 400 MHZ DUAL TRACE AMPLIFIER	\$200.00	TEK 7B80 400 MHZ DELAYED TIME BASE	\$100.00
TEK 7A26 200 MHZ DUAL TRACE AMPLIFIER	\$75.00	TEK 7B85 400 MHZ DELAYING TIME BASE	\$125.00
TEK 7D11 DIGITAL DELAY UNIT	\$50.00	TEK 7B90P PROGRAMMABLE TIME BASE	\$200.00
TEK 7D12 A/D CONVERTER MAINFRAME	\$50.00	TEK 7B92A 500 MHZ DELAYING TIME BASE	\$125.00
TEK 7D13 DIGITAL MULTIMETER	\$50.00	TEK AM502 DIFFERENTIAL AMPLIFIER	\$75.00
TEK 7M11 DUAL 50 OHM DELAY LINE	\$100.00	TEK MX5010 MULTIFUNC. INTERFACE EXTEN.	\$200.00
TEK 7M13	\$50.00	TEK 7834 400 MHZ STORAGE MAIN FRAME	\$400.00
TEK 7S11 SAMPLING PLUG IN	\$200.00	TEK 7844 400 MHZ MAIN FRAME	\$400.00
TEK 7S12 GENERAL PURPOSE SAMPLER	\$350.00	TEK 7854 400 MHZ DIGITAL STORAGE FRAME	\$500.00
TEK 7S14 1 GHZ SAMPLING PLUG IN	\$350.00	TEK 7904 500 MHZ MAIN FRAME	\$250.00
TEK 453 50MHZ OSCILLOSCOPE	\$200.00	TEK 7104 1GHZ FRAME WITH-	\$2750.00
TEK 485 350 MHZ PORTABLE SCOPE	\$600.00	(7A29,7A29,7B10,7B15)	
KEITHLEY 480 PICOAMMETER	\$300.00	GENRAD 1637 RLC BRIDGE	\$750.00
TEK 608 MONITOR	\$650.00	TEK 577 D1/177 CURVE TRACER	\$1500.00
TEK DAS9100 WITH PROBES	\$750.00	TEK 7D20 PROGRAMMABLE DIGITIZER	\$500.00
KIKUSUI 5020 20 MHZ OSCILLOSCOPE	\$180.00	TEK 465 100 MHZ OSCILLOSCOPE	\$400.00
PHILLIPS PM3212 25 MHZ OSCILLOSCOPE	\$200.00	TEK 465B 100 MHZ OSCILLOSCOPE	\$450.00
TEK 422 15 MHZ OSCILLOSCOPE	\$150.00	TEK 2335 100 MHZ OSCILLOSCOPE	\$1200.00
TEK 455 50 MHZ OSCILLOSCOPE	\$250.00	TEK 834 DATA COMMUNICATION TESTER	\$130.00
HP 6428B 0-20V/0-45A POWERSUPPLY	\$400.00	HP 5359A TIME SYNTHESIZER	\$1000.00
BRADLEY 132 SCOPE CALIBRATOR	\$700.00	HP 6033A 0-20V/0-30A POWERSUPPLY	\$1200.00

Write in 27 on Reader Service Card.

TONER AND PARTS OEM and compatibles, for copy machines and laser printers. Call NAMETECHS: 312-395-1142, Fax 312-395-1042.

SILVER N-female panel UG-58U plastipak Amphenol \$1, PLCC sockets #821573-1 50¢, 20-pin ribbon latch #499572-4 50¢, F-male 15¢. All new, large quantities. Don Russell, PO Box 451, Dallas, NC 28034. 704-922-8870.

MILITARY TRANSISTORS & DIODES & INTEGRATED CIRCUITS WANTED. ELECTRONIC MATERIAL INDUSTRIES 818-842-3539, FAX 818-845-3613.

RECOVER "SCRAP GOLD" from old computer junk. Free information packet. Call 24 hours: 603-645-4772.



WANTED: EXCESS ELECTRONIC INVENTORIES, ICs, MEMORY, EPROMs, PALS, LEDs, CIRCUIT BOARDS, DIODES, AND TRANSISTORS. CALL ACTIVE MICRO, 310-494-4851 OR FAX 310-494-4913.

CD DUPE-IT!

INSTANTLY COPY CD-ROMS NO COMPUTER NEEDED!

COMPLETE STAND ALONE DUPLICATION SYSTEM



MAKE IDENTICAL COPIES OF:
CD-ROM (MODE 1)
CD-XA (MODE 2)
CD-DA (DIGITAL AUDIO)
MACINTOSH HFS
ISO 9660
MIXED MODE
OR MASTER YOUR OWN CD-ROMS!

INCLUDES FREE CD DESIGN SOFTWARE A \$400 VALUE!
for Windows'95/NT, OS/2, and Macintosh

Not for export to China.

INTENDED FOR BACKUP & IN-HOUSE DUPLICATION PURPOSES ONLY

Instantly duplicate CD-ROM disks for software distribution. Make spare backup copies of your favorite software titles on permanent rugged, media. Produce disks quickly and economically. No CD mastering or digital multimedia experience is required. The **CD DUPE-IT!** does it all.

Insert your original disk and press "START". The on board multimedia micro-processor quickly copies any disk to the internal A/V hard drive. Insert blank disks and make as many copies as you like. You'll produce identical, bit-for-bit duplicates. The new **CSC CD DUPE-IT!** system is totally self contained - no connection to a PC or Mac is required to copy disks. Just plug in the power cord and press "START".

Use the **FREE** included CD mastering software and **CD DUPE-IT!** will work "double duty" as your personal CD mastering system. Just attach a SCSI cable to your PC or Mac, and you're ready to design and create your own original CDs.

Similar systems used in commercial CD duplication houses cost over \$10,000. Now you can easily copy disks for a fraction of the price with **CD DUPE-IT!**

ONLY \$1495



CORPORATE SYSTEMS CENTER

1294 Hammerwood Avenue
Sunnyvale, CA 94089

Tel. (408) 743-8739

DEALERS AND RESELLERS-CALL FOR QUANTITY DISCOUNT PRICE STRUCTURE
We gladly accept Discover, Visa/Mastercard, COD or prepaid orders. No surcharge for credit cards.

SCSI PERIPHERAL EXPERTS • HARD DRIVES • CD-ROMS • TAPE DRIVES • M/O DRIVES

Write in 49 on Reader Service Card.

Nuts & Volts Magazine/January 1997 69

S&N CELLULAR

The Electronics SuperStore



We offer a complete line of
Cellular Programming Equipment

"7 WAY COPY KAT" includes Motorola EE3/9611, 96-G.E.
Ericsson, Panasonic, Mitsubishi-Diamond Tel 5000 & 25X,
Sony (H333), Audiovox 800, and N.E.C. P7

\$3000 buys 2 Kats with 2 sets of Cables

Sale Price

1997 Special Packages For You Guy's On The Go.

1-Moto EE3/9611 ESN clip
1-951C Moto copy cat w/4 cables
1-GE Ericsson (95w40) ESN clip
1-NEC 100 series ESN clip
Package A - \$1500

1-Moto EE3/9611 ESN clip
1-GE/Ericsson (95w40) ESN clip
1-NEC 100 series ESN clip
Package B - \$1000

1-Moto EE3/9611 ESN clip
Package C - \$800

Please visit our website at:
<http://www.ftlauderdale-online.com/SN/default.html>

NEC ESN Clip - Programs Model #'s 110, 120, 180,
181**\$500**

NEC ESN Clip - Programs Model #'s P700, P701,
P760, P761**\$500**

GE, Ericsson ESN clip - Programs Model #'s G.E.
CT700, CT550, CT750, CT800

Ericsson Model #'s AH210 AH220, AH235, AH237,
AH238, AH300, AH310, AH320**\$400**

NEW C-TEK Cable - Turn OKI 900 or AT&T
3730 into a cellular monitor**\$250**

GE Ericsson - Programmable phone, modified
& complete**\$600**

OKI 900 - Programmable phone, modified
& complete**\$500**
Chip installation only**\$300**
Chip only**\$175**

*** Call for Best Prices on Readers - EE3 Elite & Startac ***

Please call your courteous service representatives for complete details at:

(954) 974-6161

S&N Cellular • 934 University Drive • Coral Springs, Florida 33071

AGREEMENT FOR PURCHASING OF CELLULAR PROGRAMMING SOFTWARE AND EQUIPMENT: Purchaser agrees not to use said software and equipment for any illegal purposes. This includes line fraud, computer fraud, cellular service fraud, and any other fraudulent acts according to all federal and local laws, including rules of the FCC title #18, section 1029, and all Florida statutes. All software and equipment is sold only to qualified buyers. All software is sold for educational purposes ONLY!!!

MICRO SIZE CCD VIDEO CAMERAS



New Catalog
Available for
All Models.

Prices valid during
this months Ad Only!

Video Camera
\$99.95



Pinhole Version
Available

MB-750U

MB-705UX
C-Mount Camera
with Lens Included;
8 or 12mm Lens
your choice!

Board Camera Options

- Models to 600 Line Res.
- 9V Battery Operation.
- Monitor in Darkness with IR Option.
- Can be plugged into any VCR or Monitor.
- Low Power Consumption.
- Standard NTSC Output.
- Options: Switchers/Optics/Wireless/Fiber Optics & More.

Micro Lipstick Cameras for Teleconferencing.



PANASONIC & SONY Imaging Distributor

Polaris Industries
1-800-752-3571

Visit Polaris Ind. Web Site at:
<http://www.polarisusa.com>

470 Armour Drive NE • Atlanta GA 30324 • Tech Info: 404-872-0722 • FAX 404-872-1038

Prices, availability and specifications are subject to change without notice. Shipping and Handling are not included with price.

FILTERS • CONVERTERS • FILTERS • CONVERTERS • FILTERS • CONVERTERS

FILTERS • CONVERTERS • FILTERS • CONVERTERS

FILTERS • CONVERTERS • FILTERS • CONVERTERS

Converters, All Pro-Filters
All Cable Equipment, Good Prices
Shipped Same Day COD
Just Call: 1-800-A-WIRE 4U
(1-800-294-7348) or 1-888-219-3111
Plazac Sales, Inc.
Sorry, no New Jersey sales.

FILTERS • CONVERTERS • FILTERS • CONVERTERS • FILTERS • CONVERTERS

Write in 151 on Reader Service Card.

ELECTRONIC COMPONENTS bought. All
xsistors, diodes, resist, caps, ICs. Labb
Assoc., Ph. 215-364-5414, Fax 215-364-
5415.

**DON LANCASTER'S ACTIVE FILTER
COOKBOOK** is back in print. Autographed
copies of the seventeenth(!) classic printing
\$28.50. **SYNERGETICS PRESS**, Box 809-N,
Thatcher, AZ 85552. 520-428-4073. Visa/MC.

RACAL RA-6790GM general coverage
receiver, looks and works great, \$995 with 3
filters. Manual, \$55. Also have many checked
boards and filters. E-Mail: mgs@avana.net
Bond, 221 Greencrest, Marietta, GA 30068-
3825.

RF TRANSISTORS, tubes, electrolytics.
MRF477, 2SC2879, 2SC1969, MC145106P,
2SC2075, MRF454, SRF numbers, tubes,
4CX250B, 6KG6A, 12D6Q, 6146W, 3-500
graphite, trimmers, all types. Westgate 1-800-
213-4563.

TEST DEVICES, manuals and software. Call
Jack at 313-384-3949. No Michigan sales.



MINIATURE TOGGLES 1/4" PANEL HOLE:
SPDT on-on 35¢. SPDT on-off-on 35¢. SPDT
(mom)-off-on 35¢. DPDT on-on 40¢. DPDT
on-off-on 40¢. DPDT (mom)-off-on 40¢.
MICRO-MINIATURE 3/16" HOLE: SPDT on-
on 30¢. DPDT on-on 40¢. Brand new switch-
es. Rated 6A/125V. Hardware included. \$20
minimum order. Add \$5 freight. Gateway
Products Corporation, PO Box 936397,
Margate, FL 33093. 954-974-6864, Fax: 954-
974-6818. VISA/MC. Free catalog.

WIRELESS MONITORING SYSTEMS



V-Pack 101

#VP-30
6.5" Screen
Monitor/Receiver

#VP-20
Pod Stands
10" Tall
w/o Antenna

#VP-50
Camera is 4" Tall
w/o Antenna

V-Pack 202
Shown with
Optional Transmitter
for second channel

#VP-40
5 x 5.5" Receiver

#VP-50

Wireless Specs

- 900 MHz for Best Picture quality.
- Monitor in Darkness with IR LEDs.
- Monitor has dual Channel mode.
- Battery or AC Operation.
- Plug & Play Installation.
- Mobile Security.
- Condenser Mic.
- VCR Compatible.

Stamp Applications:

Putting
the Spotlight on
BASIC Stamp Projects,
Hints, and Tips

by Scott Edwards

Motors fascinate Stamp users. They seem to be looking for a mythical universal motor-controller that interfaces to Stamps, controls any motor from 0.1 to 100 amps at 1 to 50 volts, is 100% efficient, and costs less than \$5.00. We keep those on a shelf in the back, between the perpetual-motion machines and the replacement teleprinter pattern buffers. This month, we'll look at several types of practical motor-control circuits suitable for use with the Stamps.

Electronic Control for DC Motors Using Discrete Bridge Circuits

Gallery of motor-control circuits and motor-control basics

DC Motor ABCs

Before we look at our gallery of circuits, let's agree on a couple of terms:

- In this article, motor means a permanent-magnet, direct-current (DC) motor of the sort used in toys, models, cordless tools, and robots. These motors are particularly versatile because both their speed and direction can be readily controlled; speed by the voltage or duty cycle of their power supply, and direction by its polarity. DC motors also work as generators. Since generators slow down when they are heavily loaded, DC motors

can be electronically braked.

- Control means at least on/off and direction control. Variable speed and braking are also desirable.

Most people already know a bit about DC motors from science-fair demonstrations like Figure 1. When the motor is disconnected from the battery, it is off; when it is connected with the red wire to the + terminal and black to -, it turns forward; and when the wires are reversed, the motor turns backwards.

You can also demonstrate the motor/generator braking effect. Disconnect the battery and spin the motor shaft with your fingers, noticing how freely it spins. Now connect (short) the motor power wires together and try it again. The motor is harder to spin. The short-circuit load on its generator output makes it harder to turn.

Manual Motor Controllers

Figure 2 shows how our understanding of DC motor control translates into five manual motor-control circuits using switches.

Figure 2a is the most closely related to the science-fair demo. A single-pole, single-throw (SPST) switch turns power to the motor on or off, while a double-pole, double-throw (DPDT) switch controls the polarity of the motor connections.

Don't be scared off by this talk about poles and throws. The component we call a switch can actually contain several switches, all activated by the same handle. These joined switches are indicated on a schematic by a dotted line joining their symbols. Each joined switch is referred to as a pole. So a switch component containing two switches is a double-pole unit.

Throws refer to the number of circuits a switch can make. An ordinary on/off switch makes or breaks just one connection, so it's a single-throw switch. The direction switches at the top of Figure 2 select one of two connections, so they are



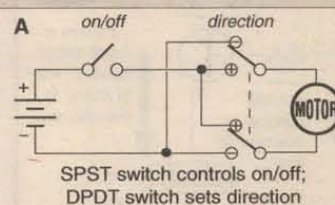



Figure 2
Motor controllers using manual switches.

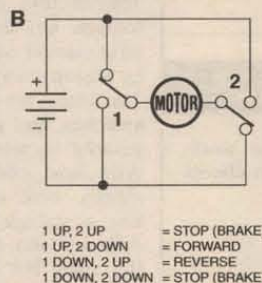

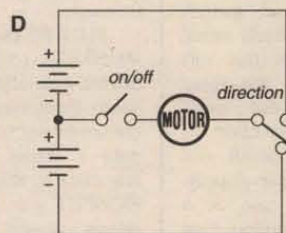
A pair of SPDT switches controls on/off and direction; brakes to a stop



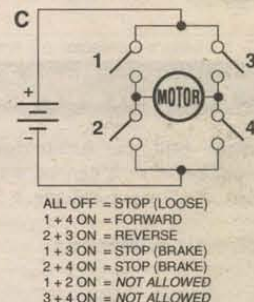SPST switches controls on/off; SPDT sets direction



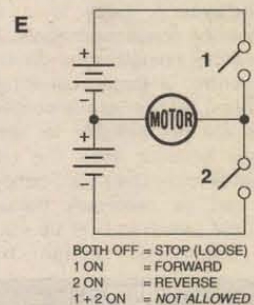Four SPST switches (H bridge) control on/off, direction & braking



Two SPST switches (half bridge) control on/off & direction

Figure 1. DC motor basics.




double-throw switches.

Figure 2b uses a pair of SPDT switches to control direction and on/off. If the two switches are set so that they both connect to the same power-supply rail, the circuit brakes the motor using the motor/generator principle. Figure 2c is very similar, but uses four SPST switches. These switches must be turned on and off in specific combinations to run and stop the motor. Note that a couple of switch settings are not allowed, because they would short out the power supply.

You might consider Figures 2d and e to be cheater's solutions to the motor-controller problem. They use a second battery to reverse the motor, thereby simplifying the arrangement of switches. However, extra batteries mean extra weight and expense. And the batteries may wear out at different rates, since, in most applications, motors spend more time going in one direction or

Stamp Applications:

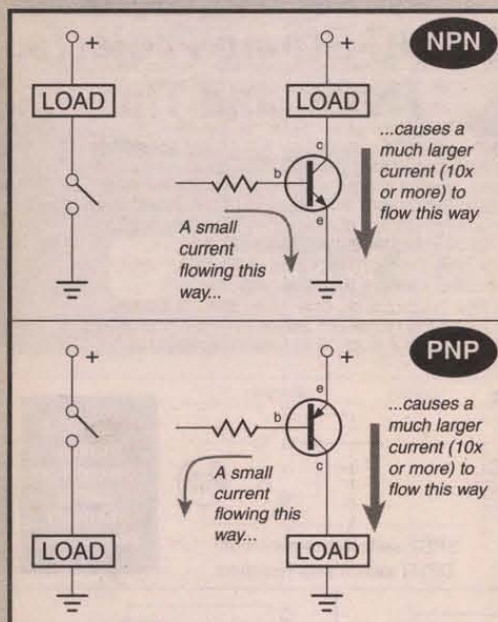

NOTE: b = base; c = collector; e = emitter

Figure 3
Transistors make good switches.

Applications No. 6 (available from the *Nuts & Volts* Web site) for more info.

Relays have two useful properties for small motor controllers: (1) Their contacts have very low on-resistance, meaning that very little power is wasted. (2) They are available in just about any combination of poles and throws you can imagine. As we'll see, solid-state multipole/multithrow switches are usually built up from many SPST units.

On the downside again, relays are slow, make noise, and wear out. They are almost useless in schemes that switch power on and off rapidly to control motor speed (duty-cycle control).

Transistors. By allowing a small base current to control a larger collector current, transistors make good switches; see Figure 3. They're fast, quiet, and can last forever. On the other hand, the base current can be somewhat high by Stamp standards (20 to 25 mA). Transistors are usable only as SPST switches, and you have to consider polarity in selecting the transistor type and connecting the load. Finally, even a fully-on transistor has a voltage drop between the collector and emitter. It's typically 0.5 volts, but can be one volt or more in Darlington configurations (discussed later). This wastes power and generates heat, which can damage or destroy the transistor.

MOSFETs. At first glance, MOSFETs (metal-oxide semiconductor field-effect transistors) would seem to eliminate all the problems of relays and conventional transistors. Their control input — the gate — draws almost no current. It switches in response to the presence of a voltage. A turned-on MOSFET can offer an on-resistance that many relays would envy. And reasonably priced MOSFETs are available in current ratings that look like a misprint — 50 amps or more out of a thumbnail-sized package.

Really, the only trouble with MOSFETs is that they are at their best with supply voltages above 10 volts, and with control voltages higher than the supply. And if they are to be switched on and off rapidly, you can forget about that "almost no gate current" stuff because the gate acts like a pretty high capacitance. MOSFETs don't hold up well in tinkers' workshops where anti-static pre-

Sources

For more information on the BASIC Stamp, contact:

Parallax, Inc.

3805 Atherton Road, #102, Rocklin, CA 95765

phone (916) 624-8333

Internet <http://www.parallaxinc.com>

Mondo-Tronics offers goodies for robotics, including the motor controller and motor-gearbox mentioned in the article (controller is part no. 3-301).

Mondo-Tronics Inc

524 San Anselmo Ave. 107-11, San Anselmo, CA 94960

phone 415-455-9330; <http://www.robotstore.com>

Wirz Electronics

sells H-bridge driver ICs. See them at

<http://cec.wustl.edu/~blw2/index.html>

Jameco supplies many of the electronic components listed in the circuits.

Jameco Electronic Components

1355 Shoreway Road, Belmont, CA 94002-4100

phone 415-592-8097 or 800-831-4242

fax 415-592-2503 or 800-237-6948.

Zetex transistors are available from

Digi-Key

701 Brooks Avenue South, P.O. Box 677

Thief River Falls, MN 56701-0677

phone 1-800-344-4539, fax 218-681-3380

Internet <http://www.digikey.com>

For a catalog of Stamp-related products, contact

Scott Edwards Electronics

P.O. Box 160, Sierra Vista, AZ 85636-0160

phone 520-459-4802; fax 520-459-0623

Internet at <ftp:nutsvolts.com> in /pub/nutsvolts/scott

E-Mail: 72037.2612@compuserve.com


the other. Still, the half-bridge design is worth knowing, because it can be very useful in cheap, efficient, dual-motor designs.

Electronic Switches

The manual motor controllers described above can all be converted to electronic (Stamp) control using one or more of the following types of electronic switches:


Relays. A relay is a mechanical switch operated by an electromagnet. The relatively small current that energizes the electromagnet (the coil) can control a larger current through the relay switch(es), known as the contacts. However, most relays are not suitable for direct connection to Stamps because even the relatively small coil current is more than the Stamp's pins can supply. This can be overcome through the use of a transistor switch to beef up current handling. See the Transistors section below or Stamp

Figure 4
Controller combines IC driver with DPDT relays.

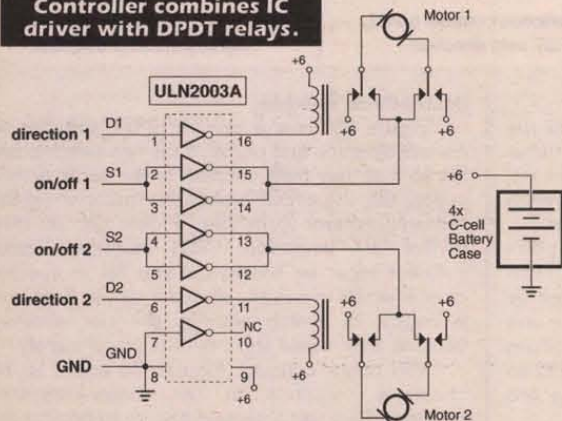

PARTS:
Relays—DPDT, 1A (or more) contacts, 5Vdc coil (JC: 99346)
ULN2003—7-channel Darlington transistor array (JC: 34278)
Motors—DC permanent magnet motors, ≤ 500 mA at 4Vdc
[See Sources for Jameco (JC) contact info]

Figure 5
Mondo-Tronics H-bridge.

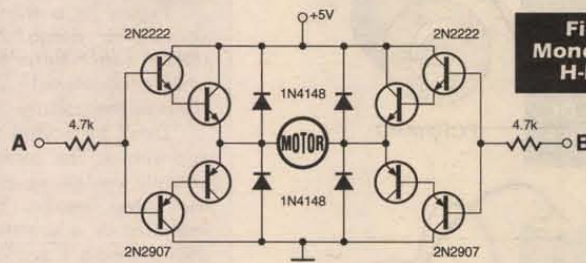

A	B
0	0
0	1
1	0
1	1

PARTS:
2N2222—NPN switching transistor (JC: 28628)
2N2907—PNP switching transistor (JC: 28644)
1N4148—Silicon switching diode (JC: 36038)
Motors—DC permanent magnet motors, ≤ 300 mA at 6Vdc
[Available as complete kit from Mondo-Tronics, see Sources]

Stamp Applications:

ICs that are popular with robotics enthusiasts are the L293D and LMD18200. Wirz Electronics sells these parts and provides design information via the Internet; see Sources. Basic specs are:

L293D: motor supply voltages up to 36V, current to 1A (2A peak). Voltage drop across each leg of H-bridge, 1 to 2V.

LMD18200: motor supply voltages of 12 to 55V, current to 3A. On-resistance of each leg of H-bridge 0.33 Ω typical, 0.6 Ω max.

The robotics-supply store Mondo-Tronics offers motor-control kits that are inexpensive, educational, and easy to build. The program listing is an example of motor speed- and direction-control using their Mini Dual H-bridge Motor Driver kit, shown in the accompanying photos. Mondo also carries suitable DC motor assemblies (like the Tamiya motor/gearbox in the picture) and robotic components.

A nice feature of Mondo's controller kits is that all have the same connector layout and interface requirements. If you build a small robot (or motorized widget) and later want to build a larger one, just swap motor controllers.

Packaged motor controllers — called electronic speed controls (ESCs) — are available from hobby shops for use in remote-control cars, boats, etc. Some ESCs are brutes capable of switching 10s or 100s of amperes. Best of all, they accept just a servo-control pulse train input to operate. That's a 1- to 2-ms pulse repeated 60 times a second. As the Stamp and Counterfeit application notes show, it's relatively easy to generate these pulses from PBASIC. If you need to control more than one motor, or your PBASIC program is too tied up to meet the 60-pulse-per-second requirement, you can use my company's Mini SSC (serial servo controller) to generate eight continuous pulse streams. See Sources for catalog information.

Example Circuits. Figures 4, 5, and 6 are representative motor-control designs derived from the ideas presented in Figure 2a, c, and e. These are tested, proven circuits suitable for use with small DC motors. Even if your application requires a much larger motor, it makes sense to get your feet wet with smaller motors so that you can begin to understand some of the issues involved. And a small geared motor assembly, like the Tamiya unit shown in the photo, has enough oomph to propel

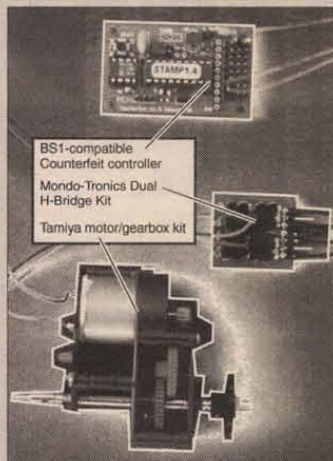


Photo of motor, controllers.

robots up to a couple of pounds at reasonable speeds. This particular motor was used to test the control circuits presented here, and draws approximately 250 mA at 3.0 VDC. Note that current is dependent on voltage, so the figures in the descriptions below are based on actual measurements.

Figure 4, Dual Relay Controller. This design uses DPDT relays to control motor direction, and an IC-packaged transistor array to turn the relays and motors on and off. Experienced eyes will spot an apparent error — this design gangs two of the ULN2003 Darlington transistor outputs together for motor on/off control. This is normally a bad idea, because slight differences in transistor characteristics will cause one of the transistors to bear all of the load. However, because these transistors are on the same silicon die, their characteristics and temperature are close enough to identical to make this trick safe.

Because the transistors inside the ULN2003 are Darlington transistors, they require only a small (<1mA) control current to turn on. The downside is that they have a higher-than-normal voltage drop of about 1.5V. If the circuit is driving our sample motors, that means that the motors get 4.5V x 0.40A = 1.8 watts (W) of power, while 1.5V x 0.40A = 0.6W is wasted. (This assumes no loss through the relay contacts.) So 75% of the total 2.4W gets to the motor. To be fair, we need to also factor in the relay coil current, 4.5V x 0.1A = 0.45W to the waste (non-motor) side of the balance sheet. Now our total is 2.85W, of which the motor gets 63%.

Figure 5, Darlington H-bridge. This is the circuit used in the Mondo Mini H-bridge kits. It also uses Darlington pairs of transistors to keep control current to approximately 1mA. As with other Darlington arrangements, the penalty is increased voltage drop — I measured it at about 1.2V per conducting leg of the bridge for a total of 2.4V (since two legs of the H have to be conducting for the motor to move).

With the sample motors, the motors get 3.6V x 0.30A = 1.08W of power, while 2.4 x 0.30A =

Listing. BS1 Program to Demonstrate Mondo-Tronics H-bridge
 Program: MONDOMOT.BAS (Demonstrate Mondo-Tronics H-bridge)
 This program demonstrates the Mondo motor controller to control the direction and speed of a DC motor. Connect input A of the controller to Stamp pin 0; B to pin 1; and GND to GND. Run the program. The motor will slowly accelerate to top speed, then stop and repeat the acceleration in reverse. This program uses a carry-the-1 method of generating duty cycle control of motor speed. When you add a number to an "accumulator" (a memory location of fixed size), the accumulator will overflow if the result is bigger than it can hold. The larger the number added, the more likely an overflow or "carry" is. This program adds the desired motor duty cycle to an accumulator, and turns the motor on only when there's a carry. Higher duty cycles make the motor run faster. This method works well with the Stamp because it is more or less independent of speed.

SYMBOL motAcc = b11
 SYMBOL motDir = bit0
 SYMBOL spd = b10
 SYMBOL cycles = b9
 SYMBOL A_ = pin0
 SYMBOL B_ = pin1

' Motor-speed "accumulator."
 ' Motor direction: 0=fwd; 1=reverse.
 ' Motor speed, 0 (off) to 15 (full on).
 ' Number of loops at a given speed.
 ' Controller A input.
 ' Controller B input.

dirs = %11
 again:
 for cycles = 0 to 255
 speed.
 gosub motor
 next
 spd = spd + 1
 if spd <= 15 then again
 spd = 0
 motDir = motDir ^ 1
 goto again
 motor:
 motAcc = motAcc & %1111
 motAcc = motAcc + spd
 if motAcc >= 16 then motOn ' If carry, then turn on motor.
 A_ = B_
 return

' Set pins 0 and 1 to output.
 ' Turn 255 cycles at each
 ' Output to motor.
 ' Increase speed.
 ' If speed is > 15, then..
 ' ..turn motor off..
 ' ..and reverse direction.
 ' Loop forever.
 ' Limit motAcc to 4 bits.
 ' Add speed.
 ' Otherwise, motor off.

' If you look at the table accompanying the H-bridge, you'll see that the motor is on only when inputs A and B are opposite. Programming shorthand for this is to set A to the motor direction, and make B = NOT A. PBASIC1 does not have a NOT function per se (see LET in the manual), so we make do by XORing A with 1, which has the same effect: B = A ^ 1.
 motOn:
 A_ = motDir: B_ = A_ ^ 1
 return

0.72W is wasted. So 60% of the total 1.79W gets to the motor.

Figure 6, Half bridge. This circuit offers the pleasant combination of high efficiency and low parts count, at the expense of splitting the battery supply into separate sections


The circuit takes advantage of the Stamps' relatively high-current outputs to eliminate the need for an input transistor or Darlington. Where the previous circuits needed just 1 mA of control current, this one requires almost 10 mA. It's a worthwhile trade for the reduced parts count.

Performance of a half bridge varies depending on which transistor is turned on; the PNP transistor dropped 0.5V and the NPN just 0.3V. Taking the worst case, the motor received 2.5V and drew 0.27A for 0.675W of power. The transistor wasted 0.27A x 0.5V = 0.135W. So 83% of the power goes to the motor.

I substituted high-performance switching transistors in the circuit (Zetex ZTX689B for NPN and ZTX788B for PNP; see Sources). I also changed the upper 4.7K resistor to 1K to prevent the high-gain transistors PNP from switching partly on due to the difference between the motor supply (6V) and the logic-level input (5V).

The improved transistors reduced the worst-case voltage drop to 0.2V. This improved performance as follows: motor, 0.81W; waste, 0.058W; efficiency, 93%.

So splitting the battery supply may be

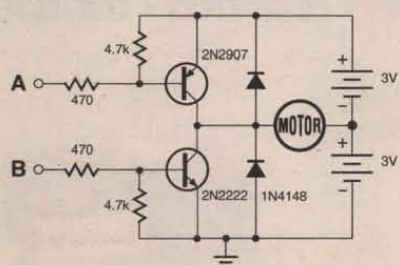

A	B	
0	0	forward
0	1	PROHIBITED
1	0	stop
1	1	reverse

PARTS:
 2N2222—NPN switching transistor (JC: 28628)
 2N2907—PNP switching transistor (JC: 28644)
 1N4148—Silicon switching diode (JC: 36038)
 Motor—DC PM motor, < 300 mA at 3Vdc
 [See Sources for Jameco (JC) contact info]

Figure 6
 Half bridge is cheap, efficient.

Stamp Applications:

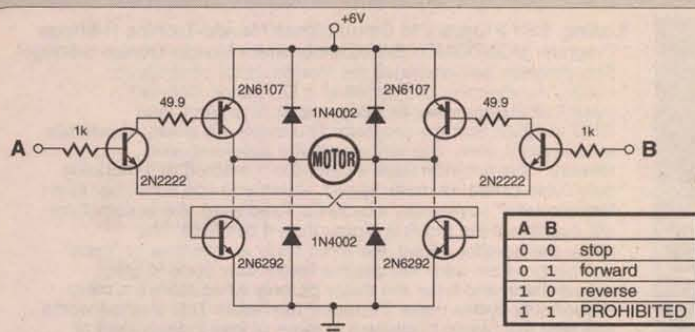


Figure 7. Ingenious H-bridge design by Rick Moll.

worthwhile when you have to get the most out of a set of batteries. If you tear apart motorized toys, you may find a circuit like this.

but I was struck by its cleverness. It was designed by Rick Moll, editor of the late lamented *Robotics Practitioner* magazine.

The half bridge can make sense for small robots with dual drive motors for propulsion and steering. Wire the motors so that they use opposite battery supplies when the robot is rolling forward, and you'll even out the wear on the batteries.

Figure 7. Ingenious H-bridge. I did not design and have not had a chance to build this last circuit,

The circuit is an H-bridge with a twist — each input transistor transfers current out of the base of a PNP and into the base of the opposite NPN. The current switches on both transistors to make the motor run. Control current is approximately 3.6 mA; not as low as the Darlington's, but better than the half bridge. And there's no voltage-drop penalty; figure a 0.5V drop across each leg of the circuit, for a total 1V drop. Almost the best of both worlds. This H-bridge cannot brake the motor, since that requires turning both NPNs or both PNPs on simultaneously.

Wrap-up

I'm out of space, but I've just scratched the surface of this fascinating subject. I'll revisit motor control in a future column. The continuation of last month's BASIC for Beginners will appear next month. **NV**

"The Most Advanced Motorola Cell-Phone Programmer"

The MAGIC-BOX™ is a small and powerful Universal Cell-Phone Programmer. It only requires the phone and a lead (supplied) to program the phone using the phone's own keypad. With the MAGIC-BOX™ attached the ESN is simply entered on the phone's keypad and then after a few seconds the phone is programmed! It is supplied to do the Motorola models as standard, but can be upgraded (before and after purchase) to become a complete Multi-Programming tool for almost all phones in use today. "This is the only Cell-Phone Programmer you will ever need!"



The unit Programs & Repairs (0000FFFF faults) all MOTOROLA models up to the later 9630 versions, including EE1, 2, 3 and STARTAC.

The MAGIC-BOX™ is supplied with 550(Flip), Elite and StarTac leads.

only \$1299

Call Us Now on....
01144-188-333-0060

Also... "Special Offer" 7 Way Copy-Cat with all cables for only \$999.

M.F.M. COMMUNICATIONS. 57 Addison Road, Caterham. CR3-5LU. UK.

"For Information Purposes Only"

Write in 132 on Reader Service Card.

CONVERTERS • CONVERTERS • CONVERTERS



JERROLD DRX-3-105
61 Channel, Fine Tuning
Factory Refurbished
Single: \$45.00
5+: \$39.00
10+: \$35.00

BRAND NEW!
Factory Fresh

PANASONIC 550MHz

Single \$69.00
5+ \$65
10+ \$62
20+ \$59

Call Re: Models 145 & 175

JERROLD STARCOM
DQN-7 — CALL \$\$

Remote, Batteries & Coax Cable Always Included
WE DO NOT SELL DECODERS, TEST DEVICES, CHIPS, ETC!

CONVERTERS • CONVERTERS • CONVERTERS

34 East Main St.
Smithtown, NY 11787
1-800-322-9690

CONVERTERS, LTD.

ALL PRODUCTS
1 yr. Warranty



UNIVERSAL REMOTES!
REPLACEMENT REMOTES!
\$5.00 & up



REGAL CR-83
83 Channel - Parental Lock-Out
More! Factory Refurbished
Single: \$55.00
5+: \$49.00
10+: \$45.00

CALL NOW!
1-800-322-9690



Catalog 8 arrives in April!

400 Pages Of Hard-To-Find Electronic Parts.
This is the one you have waited for. Three years in the making. Order now to reserve your copy and receive a \$5 rebate on first order.

Antennas, Blowers, Audio parts, Capacitors: (Disc, silver mica, feedthru, doorknob, electrolytic, air & vacuum variable, transmitting), Insulators, Collins Parts, Tools, Circuit Breakers, Toroids, Fuses, Connectors: (RF, electrical, computer), CRTs, Crystals, Dust Covers, Cords, Enclosures, Transformers, Rack Cabinets, Variacs, Wire and cable of any type, Equipment: (Test++ big selection of TEK & HP repair parts), Scope Cameras, Ham, Computer), Fiber Optics, Filters, Finger stock, Hardware, Tubes, Sleeveing, Inductors - coils & chokes, Knobs, Lamps, Lasers, Manuals, Microwave parts, Motors, Pots, Resistors, SIPS/DIPS, Power Supplies, Relays: (Vacuum, contactors, solid state, time delay), Rubber clamps & feet, Selenium rectifiers, Gages & Thermometers, Semiconductors, Shaft hardware, Switches, Telephones/parts, oddities like 1950 Tube Type Bendix Computer, etc.

\$5 (U.S. 48 states)

\$10 (All Others)

Mail Orders to: 1502 Jones Street, Omaha, NE 68102

402-346-4750 • Fax: 402-346-2939 • e-mail: grinnell@probe.net


Surplus Sales of Nebraska

Write in 188 on Reader Service Card.

COMPONENTS cont.


ELECTRONIC PARTS for sale: For list, send SASE to A&A Engineering, 2521 W. La Palma, Unit K, Anaheim, CA 92801. You can also call 714-952-2114 or Fax 714-952-3280.

MICROCONTROLLERS

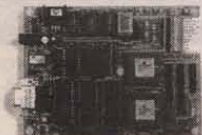


MICROCHIP PIC Downloader. Emulate and test PIC 16C6x, 16C7x, and 16C8x programs in real time using our PicEm-14™ downloader board. Simply plug PicEm into your circuit and download your code from any serial port. Prices start at \$295. Call MSD at 408-296-4000. <http://www.msd.com/picem>

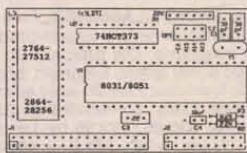HIGH SPEED MICROCONTROLLER DC80C320 (8051 compatible), 64K-128K RAM, 64K-128K ROM, RS232, RS485, I2C EEPROM, RTC, parallel I/O (8255), AT keyboard input, 2-8 bit ISA slots, expansion header, LCD interface. Minimum system \$89, full system \$149. Free monitor/debugger. CG Microsystems, PO BOX 1074, Redlands, CA 92373. Voice/Fax 909-793-3917. <http://home.earthlink.net/~cgmicro/>



8051 MICROCONTROLLER. Only 1.8 x 3.0". Use EEPROM or EPROM for data storage. Quality bare PCB, software, schematics, \$19.95. Kit \$29.95. Logical Design Tools, Inc. 512-888-4535. <http://www2.interconnect.net/ldt/hom.htm>

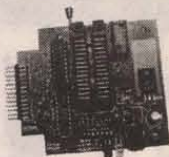STAND-ALONE programmer Micromot Labs -68HCXX programmers. Program your 68XX chips in seconds. No computer needed. Call Micromot Labs. Other goodies available. 305-651-5183.



EEPROM PROGRAMMER 2864-28256. Easy parallel port operation. Escape EPROM erase/burn cycle. Assembled, complete. \$49.95. In 3 x 5" case \$69.95. LDT 512-888-4535. <http://www2.interconnect.net/ldt/hom.htm>

Serial Display Modules

We offer top-quality LCDs that accept data through a serial interface at up to 9600 baud. Easy to use with computers and controllers (e.g., BASIC Stamps, PCs)—if you can send serial (RS-232), you can have a display working in minutes!

Contact us or download sample user manuals, catalogs, schematics and other docs from our FTP archive.

OEMs: serial-to-LCD chips and boards available at great quantity discounts

\$45
non-backlit
\$55
LED backlit



\$89
LED backlit




\$139
non-backlit
\$159
LED backlit




Counterfeit Kits

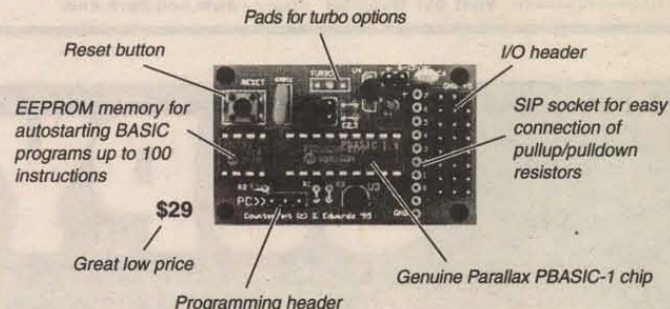Designed by the author of the *Stamp Applications* column, the Counterfeit is no fake! It's the **genuinely** easy, **truly** inexpensive kit equivalent to the BASIC Stamp I microcontroller. Get started with microcontrollers today with a \$69 Counterfeit Development System, or add a Counterfeit to your Stamp collection for \$29.



Mini Serial Servo Controller

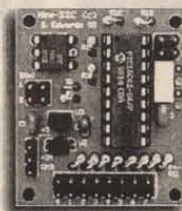

\$29 kit
\$44 assembled

Control hobby servos with a Stamp or PC computer. Build robots, automated camera positioners, test equipment, etc. The Mini SSC generates precise, stable servo-control signals based on simple, serial instructions. Want to know more? Get our catalog or download info from our Internet archive.

Scott Edwards Electronics

We accept Visa, Mastercard, Discover, and American Express. Personal/company checks OK for mail orders. CODs incur a handling fee.

Scott Edwards Electronics • PO Box 160 • Sierra Vista • AZ • 85636-0160
ph: 520-459-4802 • fax: 520-459-0623 • e-mail: 72037.2612@compuserve.com
Internet: <http://ftp.nutsvolts.com/pub/nutsvolts/scott>

BASIC Stamp is a registered trademark of Parallax Inc.

Write in 119 on Reader Service Card.

Write in 117 on Reader Service Card.

Nuts & Volts Magazine/January 1997 75



TNR

TECHNICAL, INC.

Your Largest Stocking Distributor
For **SANYO** Batteries

Call for Competitive Pricing

FREE CATALOG

Receiver & Transmitter Packs • Laptops, Camcorder, Cellular
Sealed Lead Acid, Lithium, & More

Immediate Delivery • Custom Assemblies • Technical Support • Full Production Facilities
301 Central Park Drive • Sanford, FL 32771
(New Location, Same Owner!)

Fax 407-321-3208

800-346-0601

email - tnrbattery@aol.com

Web - <http://www.batterystore.com>



MAJOR COMPONENT AUCTION!

On behalf of



Packard Bell™

A Packard Bell NEC Company



International
Component Exchange

Computer Cases & Partial Assemblies (NMB's)

A rare opportunity to purchase and assemble computer desktop and mini-tower hard cases. Each system consists of a computer chassis, power supply, floppy drive, 486 or Pentium® board (populated w/o CPU) riser cards and more! Thousands of CPU's, memory and assemblies available. Build your own 486 or Pentium® system with the components available in this auction.

Thousands of

- CPU's
- Floppy disk drives
- Tape backup units (up to 400MB)
- Hard disk drives
- Disk and tape drives
- 16 bit sound cards
- 101 keyboards
- 2 button mice
- Stereo speakers
- TV/FM Cards
- Modems (up to 28.8)
- CD ROMS, 2X and 4X

LATE JANUARY 1997

Sacramento, California

A Buyer's Premium Will Apply At This Sale • Bond #B2488496

Call for a FREE Color Brochure **(800) 665-1043**

KOLL DOVE 1241 East Hillsdale Blvd. • Foster City, CA • (415) 571-7400
GLOBAL DISPOSITION SERVICES Visit Our Website! <http://www.koll-dove.com>

CELLULAR DATA INTERPRETER ESN/NAM READER

A few 'CDI' Features:

- *ONE PIECE DESIGN 7" X 6" X 2" (Requires use of PC) *BUILT IN RECEIVER
- *DISPLAYS COMPLETE ESN, MIN, SCM, DTMF/NUMBER DIALED
- *ESN DISPLAYED IN HEX AND DECIMAL *AUTO SCAN
- *SILENT MODE **DTMF DECODING *DISK LOG ON/OFF/PARTIAL
- *INDICATOR CHIME SOUNDS AFTER SUCCESSFUL READING
- * LOGGING TO DISK/ OR HARD DRIVE

ONLY \$2995.00 + SHIPPING

TECHNICAL ADVISORY GROUP

6780 ABRAMS ROAD SUITE 103-282

DALLAS, TEXAS 75231

214.246.3609 MSG 214.890.7735 FAX

PAYMENT MUST BE COLLECTED FUNDS, WESTERN UNION/MONEY GRAM/US POSTAL M.O. It is the responsibility of the Buyer (not the distributor) to ascertain and obey all applicable local, state, and federal laws with regard to possession and/or use of the following hardware and software. CASHIER'S CHECK OR CERTIFIED FUNDS MUST CLEAR PRIOR TO SHIPPING. SORRY NO CDS AT THIS TIME.

Pursuant to U.S. Federal laws illegal operation or misuse of this hardware and software are subject to both criminal as well as civil penalties (U.S. Title 18 Sec. 1029).



ANTIQUE ELECTRONICS

ANTIQUE RADIO CLASSIFIED. Free sample copy! Antique radio's largest-circulation monthly magazine. Old radios, TVs, ham equip., 40s & 50s radios, telegraph, books, & more. Ads & articles. Free 20-word ad monthly. Subscribe today. Six-month trial: \$18.95. Yearly rates: \$36.95 (\$53.95 by 1st class). Foreign: Write. ARC, PO Box 802-G18, Carlisle, MA 01741. Phone: 508-371-0512; Fax: 508-371-7129; Web: www.antiqueradio.com

RECOVER "SCRAP GOLD" from old computer junk. Free information packet. Call 24 hours: 603-645-4772.

WESTERN ELECTRIC WANTED: 1927-1960S. Amplifiers, speakers, tubes, etc. Free offer. 1-800-251-5454.

MILITARY TRANSISTORS & DIODES & INTEGRATED CIRCUITS WANTED. ELECTRONIC MATERIAL INDUSTRIES 818-842-3539, FAX 818-845-3613.

RADIO AND TV tubes from 1927 to 1977. \$1 for list to: Preller TV, 208 South 2nd St., Augusta, AR 72006. Ph. 501-347-2281.

WANTED: FOR historical museum, pre-1980 microcomputers, magazines, and sales literature. Floyd, VA 24091-0341 (540-231-6478/540-763-2321).

AVIATION ELECTRONICS

MILITARY TRANSISTORS & DIODES & INTEGRATED CIRCUITS WANTED. ELECTRONIC MATERIAL INDUSTRIES 818-842-3539, FAX 818-845-3613.

COPY CATS

CELLULAR PROGRAMMING EQUIPMENT

WE OFFER YOU THE LOWEST PRICES IN THE USA!!


6-WAYS..7-WAYS..STARTACS..ELITE AND ELITE EE-3 WE HAVE WHAT YOU WANT!!

CALL US AFTER YOU'VE CALLED THE REST...

We ship same day with next day delivery anywhere in the world. Payment must be collected funds, Western Union or U.S. Postal Money Orders only.

All equipment is sold solely for educational or experimental purposes.

CALL 817 633-5991 24 HOURS

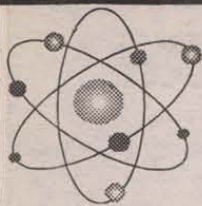

BRIGAR ELECTRONICS

7-9 ALICE ST.-BINGHAMTON, NY 13904

SERVING: ■INDUSTRY ■SCHOOLS ■HOBBYISTS ■EXPERIMENTORS ■CONSUMERS

OPEN: MONDAY THRU FRIDAY 7:30AM TO 4:30 PM, SATURDAY 7:30AM TO NOON

PHONE: (607) 723-3111
FAX: (607) 723-5202
E-MAIL: BRIGAR2@aol.com



CREDIT CARD DISCOUNT


\$ 0.00 - \$ 99.99	NET
\$100.00 - \$249.99	LESS 10%
\$250.00 - \$499.99	LESS 15%
\$500.00 - \$999.99	LESS 20%
\$1000.00 AND UP	LESS 25%

SEND FOR FREE CATALOGUE


SEMICONDUCTORS



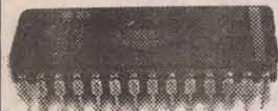SGS-THOMSON - CMOS EPROM
PART # M27C1001-20FI
32 PIN DIP 1 MB (128K x 8)
200 NS ACCESS Vcc=5v ±5%
LIST PRICE ... \$7.95 BRAND NEW
BRIGAR SALE PRICE..... \$4.25



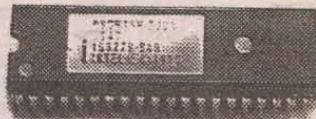8000 SERIES MICROPROCESSOR
INTEL # P8051AH
8 BIT CMOS CPU, 256 BYTES RAM
12 MHz - 40 PIN
(Tie pin 31 low to bypass
the internal ROM)
PRICE... \$2.50 EA.
100 PCS & UP \$1.75 EA.



PART #	MFG	PIN	DESCRIPTION	PRICE
SN74LS02N	Motorola	14	Quad 2-input nor gate	.22
SN74LS10N	Motorola	14	Triple 3 input NAND gate	.20
SN74LS193N	Motorola	16	Binary up/down counter	.40
SN74LS279AN	Texas inst.	16	Quad set-reset latches	.25



MOTOROLA



OPTREX #DMF50140NF-SEW INTELLIGENT GRAPHIC LCD MODULE
"SUPERTWIST" Modules utilize surface mount technology. Displays Blue pixels on White background. Modules have E-L Backlighting - Graphic Figure Character Display. Unit comes complete with built in drivers & 8 bit tti interface.

•CONTROL LSI T6963C TOSHIBA
•VIEW ANGLE: 6:00 •DOT SIZE: .44(W) x .57(H) mm
•DIT PIXELS 143(W) x 153(H) mm •VIEW AREA 74.8(W) x 98.4(H) mm
•DC VOLTAGE: 5VDC •GRAPHIC, FIGURE & CHARACTER DISPLAY
•HIGH CONTRAST & WIDE VIEW ANGLE •FILM TYPE BACKGROUND
COMES COMPLETE WITH PIN OUT, SCHEMATIC, AND PROGRAM DISK.
SCHEMATIC SHOWS LCD INTERFACE TO 68HC11 MICROCONTROLLER
THE PROGRAM IS ALSO FOR 68HC11 - Using this information, one should be able to interface the LCD to any microcontroller or a microprocessor.
LIST PRICE... \$119.95 **BRIGAR SPECIAL \$59.95**




Display comes complete with 3.5" diskette. Files contain 68HC11 program, list of commands, schematic and initialization steps.



ULTRASONIC LIGHT SWITCH MFG: LITRONIC
Replaces existing wall switch - Great for home alarm systems or controlling lights & small appliances, ON-OFF Switch-LED TRIP Indicator COLOR: WHITE
SIZE: 5"W x 5"H x 1-3/8"D

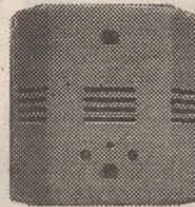●VOLTAGE 120 OR 277VAC 50/60HZ
●MIN LOAD 80 WATT 120V
●MAX LOAD 1000W 120V
Sensor Low Power Ultrasonic 25KHZ
●ADJUSTMENT: Sensitivity & Time out (0 TO 25 MINUTES)
●Documentation & schematic included. ENERGY SAVINGS
30 TO 60% ORIGINAL PRICE \$100.00
SPECIAL SALE PRICE
..... \$12.95 EA.
5 FOR \$60.00



MOTION SENSING
AUTOMATIC SWITCH




CK05 SERIES - MOLDED RADIAL MULTILAYER CERAMIC CAPACITORS MIL-C-11015 for general purpose bypass and coupling applications in telecommunication & instrumentation equip.
PART # CKR05BX103KR

CAP.	Tolerance	VOLT	PRICE
10,000	+/-10%	100	\$20.00 per Hundred

Seagate MODEL # ST3243A 3.5 214 MB HARD DRIVE

	R/W	Sectors	F' Matted
<u>Cyl.</u>	<u>HEADS</u>	<u>Per Track</u>	<u>Mbytes</u>
1024	12	34	214

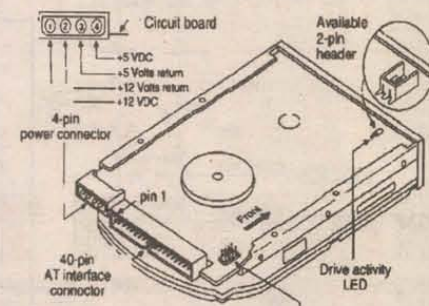The ST3243A was designed for IBM or IBM compatibles AT(286,386,and 486) systems. AT interface IDE Hard Drive. Complete with installation guide book. **BRAND NEW.... \$115.95**




OPTICAL ENCODER

DYNAMICS RESEARCH 160 SERIES Compact Incremental Optical Rotary Encoder. #162-021-250-11uf
■2 channel square wave with compliments
■Size: 1.625" dia. x 1.61"L
■Shaft: .250" dia. x .620"L
■250 count/rev. ■Input Volt: 5Vdc
RFE Mint Cond. PRICE... \$25.00



NMB SMART FAN MODEL #4715ML

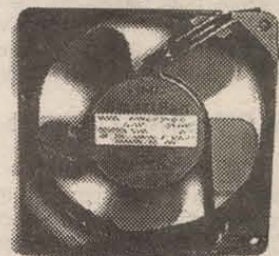■12 VDC ■0.5AMP ■120CFM
■BRUSHLESS ■5 BLADE
■8" WIRE LEADS
■BALL BEARING
■ALUM HOUSED.
SIZE: 4 11/16" SQ. X 1-1/2"D
Fan complete with thermostat control sensor. **BRAND NEW SALE PRICE...\$10.95 EA.**




Computer Grade Capacitor

NIPPON CHEM-CON
27000 UF - 40 VDC
Part # 602D2464
Size: 4-1/4"H x 2" dia.
PRICE \$3.00



UNINTERRUPTIBLE POWER SUPPLY (UPS) MODEL# ON2000A-SO

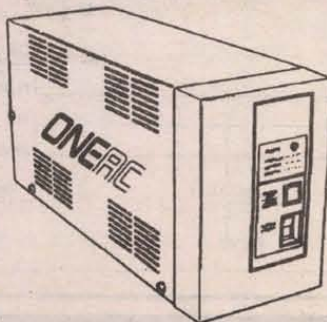FEATURES:
Open communications interface
UPS/RM Rs232 control language
ONBoost
Overload indication
Load power & battery voltage meters
Low battery indication
Replace battery indication
On-site, on-line replaceable battery
Fulltime, on line isolating transformer
Automatic self test - UL & CSA Approved.



Max capacity (Volt-amps,watts) 1850 va,1300
Input 120vac 60hz Output 120vac 60hz
Reserve time 8 min.
Transfer time: 2.0/2.25 milliseconds
Surge volt withstand 6kV/200 & 500 amp
Output sockets: 8
Size: 12"H x 8.3"W x 20.3"D
Weight: 128 lbs New cost \$3,895.00
BRIGAR SALE \$1,200.00



LOOK AT BRIGARS
LOW, LOW PRICES!

Back in November, I wrote about the advantages a DC servo motor control has over the basic stepper motor. I also described some of the considerations that ought to go into crafting a reliable servo motor controller. This time around, we'll get down to the brass tacks of building an industrial strength servo motor control system on a hobbyist budget.

Actually, I'll be describing two separate controllers: a simple single-axis controller with an RS232 interface, and an RS485-based motor control module which can be daisy-chained to easily create multi-axis systems. These controllers can either execute position or speed control for small DC motors with TTL-compatible incremental encoders. They are both based on the *PIC-SERVO* motor control chipset which provides virtually all the servo control and communications functionality.

The PIC-SERVO Chipset

The *PIC-SERVO* chipset consists of two pre-programmed micro-controllers (one PIC16C73 and one PIC16C54) which together perform four critical motor control functions:

1. The *PIC-ENC* chip (a PIC16C54) performs the time-intensive task of counting optical encoder transitions to form a 16-bit motor position. This 16-bit position count is read by the *PIC-SERVO* (a PIC16C73) and augmented with two more bytes to form a 32-bit position count. The *PIC-ENC* can count transitions at up to 500 KHz. This means that a motor with a 100-line encoder (a total of 400 encoder transitions/revolution) can rotate at up to 75,000 RPM.
2. The *PIC-SERVO*, at rates up to 2 KHz, reads the current motor position, compares it to the desired position, and then applies a PID (proportional-integral-derivative) control filter to produce the proper control signal for the power amplifier. This con-

trol signal is a 20 KHz PWM amplitude output, plus a direction output bit.

3. To create smooth motions from one goal point (or velocity) to the next, the *PIC-SERVO* also performs trajectory profiling calculations which will smoothly accelerate the motor up to the operating velocity, slew at a constant speed, and then decelerate smoothly to a stop at the desired goal position. (In velocity mode, the trajectory profiling simply accelerates smoothly from the current velocity to the new goal velocity.)

4. The *PIC-SERVO* has an asynchronous serial interface and command protocol which allows it to communicate over a standard serial port. The communications protocol supports multiple devices so that several motors

can be controlled directly from a single serial port.

The *PIC-SERVO* also performs a handful of other useful little functions (detecting error conditions, reading limit switches, homing, etc.), but the functions listed above really define the core of the servo controller. Complete documentation for the *PIC-SERVO* chipset can be found on the Web at:

<http://users.aol.com/dcservo/picservo.html>

The Single-Axis Controller

Figure 1 is a schematic for a very basic *PIC-SERVO*-based motor controller. As you can see, all that is needed besides the *PIC-SERVO* chipset is an RS232 transceiver chip like the MAX232 — and a PWM — power amplifier. Your host computer's COM port will send motion commands directly to the *PIC-SERVO* through the MAX232, and the *PIC-SERVO* produces a PWM and direction output for the LMD18200 power amplifier.

Garden variety TTL optical encoder signals can be connected directly to the CH-A and CH-B inputs


of the *PIC-ENC*. If your encoder has an index pulse output, it can be connected to the index input on the *PIC-SERVO*. Otherwise, the index input can be used as a general-purpose input. The *PIC-SERVO* reads the encoder position from the *PIC-ENC* over an eight-bit bus with an addition of a byte select line (ENC_SEL) and a reset line (ENC_RES).

The LMD18200 is an H-bridge power amplifier which can drive up to three amps continuously, and six amps peak, and can operate with a supply from 12V to 55V. It has an automatic thermal shutdown, with a thermal shutdown warning output which is activated if thermal shutdown is imminent. (This output is ignored in this design, but could easily be connected to one of the limit switch inputs.) The device is also overcurrent and undervoltage protected.

The design is pretty straightforward, but there are a few things to note:

1. Some optical encoders (like the HP HEDS5510 series) do better with a 2K pull-up resistor to +5V on the encoder signal lines. To

Figure 1

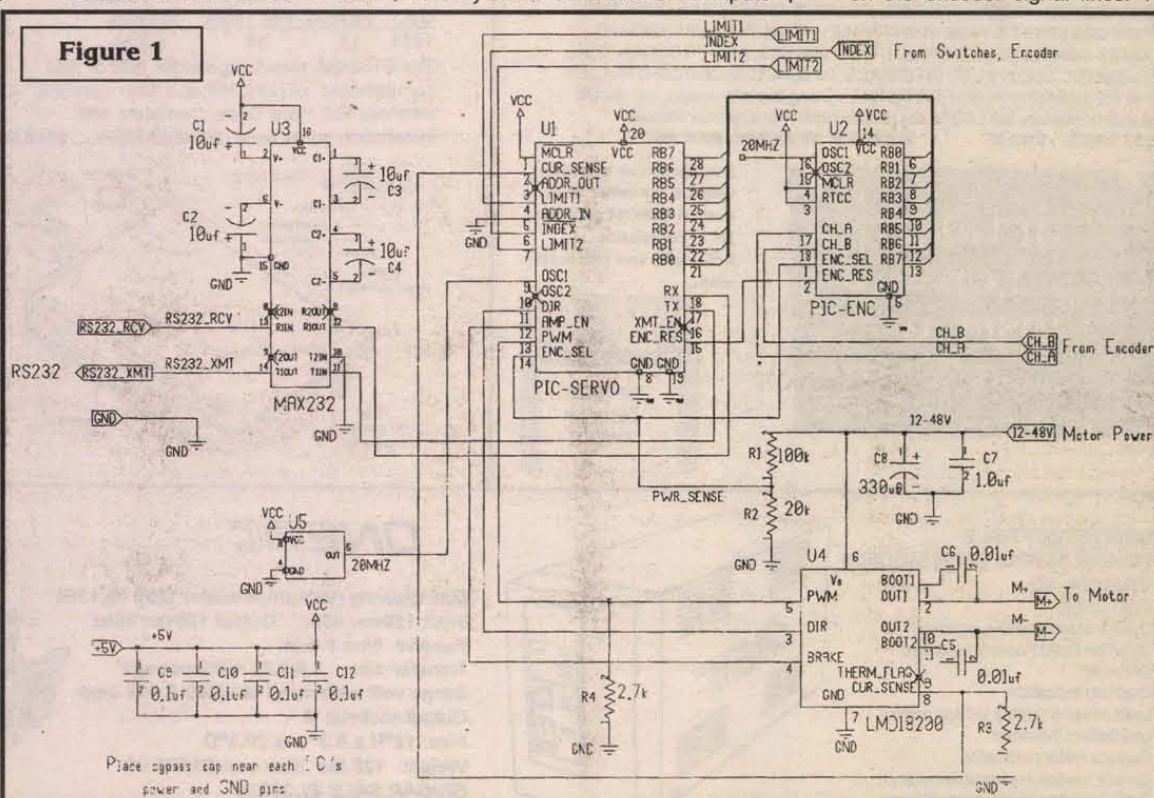

- further improve the noise immunity, you may want to run the encoder signals through a Schmitt-Trigger buffer.
- The LMD18200 amplifier has the brake input, which disables the amplifier when high, connected directly to the amplifier enable output of the *PIC-SERVO*, which is normally used to disable the amplifier when low. This doesn't really matter because the actual use of this bit is controlled in your software. The only thing to note is that on power-up, the brake will be low (amp enabled), but the PWM signal will also be low (so that no drive current will be applied). This will create a self-braking effect in the motor, rather allowing the motor to freewheel. You'll see in the next circuit that an inverter is used, which allows the motor to free-wheel on power-up.
 - The current sense output of the LMD18200 is connected to ground through a 2.7K resistor. This will cause the pin to produce a voltage of about one volt per amp of motor current. This pin is then connected to the *PIC-SERVO*'s analog input for current monitoring. The slightly cheaper version of this amplifier — the LMD18201 — is pin compatible, but does not have the current sense output (its pin 8 should be connected directly to ground).

- The MAX232 chip actually has two receivers and two drivers. The spare receiver can be connected to your RS232 port's DTR or RTS to give you an extra output bit, and the spare driver can be connected to DCD, DSR, or CTS to give you a spare input.
- The ENC_SEL pin on the *PIC-SERVO* is a dual-purpose pin which gets used for both hi/lo byte selection and for detecting the presence of the motor power supply voltage. As shown in the schematic, it is connected to the motor supply voltage through a high-impedance voltage divider. If the *PIC-SERVO* ever detects a loss of motor power, it will automatically disable the servo. If you want to override this protection, simply tie the ENC_SEL pin to +5V through a 5K resistor.
- If you are running your motor control signals more than a foot or so, you should be very careful with your cabling. At a minimum, the M(+) and M(-) leads should be twisted together and CH-A and CH-B of the encoder should each be twisted with ground or +5V. It would be even better to separately shield the motor wires and the encoder wires.

The Expandable Control Module

Figure 2 is a schematic of the daisy-

chainable motor control module. This circuit is the actual circuit used on the *PIC-SERVO* Experimenter's board (see the *PIC-SERVO* web site for more information). The motor control, encoder interface, and power amplifier all work the same as in the single axis design, but some of the finer points of the RS485 interface and the daisy-chaining need a little discussion.

A Bit About RS485

For the most part, RS485 serial communications is conceptually identical to RS232 communications. The two main differences are that 1) the signals are differential rather than single ended, and 2) RS485 driver outputs may be disabled with an output enable signal, allowing multiple transmitters to be connected to the same differential pair of wires.

The differential signals, in addition to being generated easily from a 5V source, provide much better noise immunity than RS232 signals. If RS485 cabling is done properly (shielded twisted pairs, etc.), the signals can be driven up to 4,000 ft. at rates up to one megabit per second. (For compatibility's sake, we'll just be running at up to 115.2 Kilobits/sec.)

The output enable input available on most RS485 driver chips is what allows networks of devices (up to 32) to hang off of a single RS485 port. In

general, there are two different types of RS485 networks: two-wire half-duplex networks, and four-wire full-duplex networks.

With the half-duplex network, all nodes both send and receive over the same pair of wires. As you would imagine, this type of network requires a sophisticated enough communications protocol to prevent two different nodes from speaking at the same time. In a real-time control network, communication errors over a half-duplex network can create real problems.

The four wire, full-duplex network typically has a master node which transmits to all of the slave nodes over one dedicated pair of wires, and then all of the slaves transmit back to the master over a shared pair of wires.

In this scheme, slaves do not communicate directly with one another. The advantage is that the communications protocol can be much simpler, and the host can always send commands to the slave modules, even if one is confused and speaking out of turn. This is the protocol used by the *PIC-SERVO*, and as we will see later on, is very robust and nearly fool-proof.

The master node on a full-duplex RS485 network does not ever need to disable its transmit signal because its transmit lines are not shared. Therefore, the master node can use a standard RS232 port with a simple RS232 - RS485 signal adapter. These adapters are commonly available from places like Jameco, or you can easily build your own using the MAX232 from the first circuit, and the LTC491 from the second circuit, hooked back-to-back.


Daisy-Chaining

With any sort of network with multiple devices, each device must have a unique address for making sure that information goes to the right place. Typically, you would have a set of dip switches or jumpers for setting unique addresses. Not only is this a pain, but it also uses up several I/O pins. The *PIC-SERVO* takes advantage of the RS485 network topology — nodes hanging off of a single straight cable — to allow the master to dynamically set the address of each of the controllers on power-up.

The scheme works like this ... The *PIC-SERVO* has two pins used for addressing: ADDR_IN and ADDR_OUT. On power-up, all *PIC-SERVO*s have a default address set to 0, the ADDR_OUT is set high, and all communications are disabled until the ADDR_IN pin goes low.

Once the ADDR_IN pin goes low, communications are enabled, and the *PIC-SERVO* will respond to any command sent its default address of 0.

One of the commands in the *PIC-*

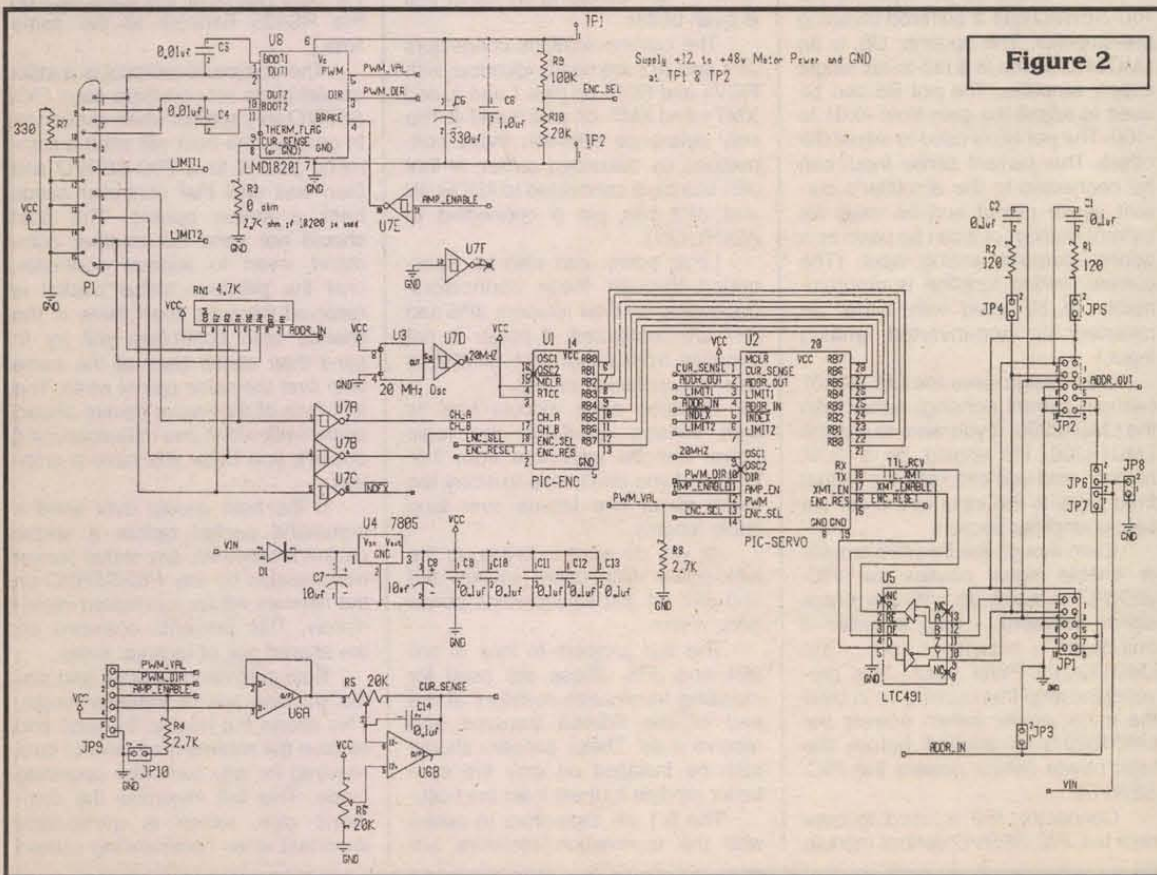

SERVO command set is used to change the address to a different value from the default. When this command is issued, the chip will then lower its ADDR_OUT signal.

Figure 3 shows how ADDR_IN and ADDR_OUT are used to initialize several daisy-chained PIC-SERVO controllers with unique addresses. On power-up, only the last PIC-SERVO in the chain — with its ADDR_IN line tied low — will be enabled for communications. The first command issued by the host will be to change the address of device 0 from 0 to 1. The end PIC-SERVO will become device 1 and then enable the communications of the adjacent PIC-SERVO by lowering its ADDR_OUT. This adjacent PIC-SERVO will then wake up with device address of 0. The next command from the host will be to change the address of a device 0 from 0 to 2. This process proceeds until all of the PIC-SERVOs in the chain have been assigned unique addresses.

Furthermore, because each PIC-SERVO will always send back a status packet after it receives a command, the number of controllers can be determined dynamically by continuing to issue change-address commands until no status packet is received in return.

To support this dynamic daisy-chaining address scheme, jumper JP3 in Figure 2 should only be installed on the last PIC-SERVO control module in the chain. You will also notice that the two communications connectors, JP1 and JP2, are nearly identical, except for that one has pin 5 connected to ADDR_IN and one has pin 5 connected to ADDR_OUT.

Additional Resources

Complete information about the PIC-SERVO, including data sheets, application notes, ordering information, and test software for DOS and Windows (with C and Visual Basic source code) can be found at the PIC-SERVO web site:

<http://users.aol.com/dcservo/picservo.html>

This site also has details for making your own RS232-RS485 converter. In fact, for the really ambitious and entrepreneurial-spirited motor control hacker, this site even has complete copies of the Gerber files used for fabricating the PIC-SERVO Experimenter's board and the Z232-485 converter board. Knock yourself out.

All the parts for these two controller circuits, except for the PIC-SERVO chipset, can be ordered from Digi-Key. The PIC-SERVO chipset can be ordered from HdB Electronics (Phone: 1-800-287-9432, Fax: 1-415-368-1347). Bare circuit boards for the circuit in Figure 2 (the PIC-SERVO Experimenter's board) can also be ordered from HdB Electronics. (Pre-assembled versions of this board are also available.)

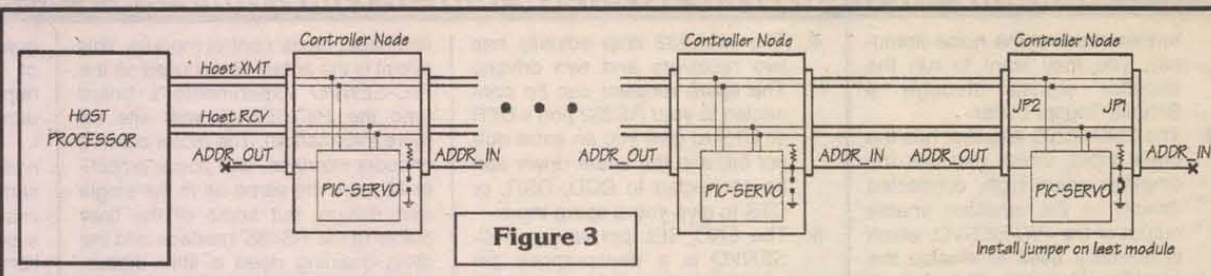


Figure 3

When interconnecting modules, the end module should have JP1 left open, with JP2 connected to JP1 of the previous module. The module closest to the master, or host, will have JP2 connected to the host's RS485 compatible serial port.

Other Points of Interest

Referring back to Figure 2, you will notice that all of the encoder signals are run through Schmitt-Trigger inverters and have pull-up resistors. Note that as long as the both CH-A and CH-B of the encoder are inverted, position counting will happen exactly as if neither of the signals were inverted.

Inverters were used rather than non-inverting buffers because I opted to invert the amplifier enable signal before feeding it into the LMD18201's brake input; the spare inverters were handy so I used them. (I also used one of the inverters to buffer the clock signal, although this probably wasn't necessary.)

The current sense input of the PIC-SERVO has a buffered inverting pre-amplifier. The op-amp, U6, is an LMC6492 which is a rail-to-rail single supply amplifier. The pot R5 can be used to adjust the gain from -0.01 to -100. The pot R6 is used to adjust the offset. This current sense input can be connected to the amplifier's current sense output and be used for current limiting, or it can be used as a general-purpose analog input. (The current limiting function is programmable to be used with either an inverted or non-inverted analog input.)

This design uses the LMD18201 (without current sensing) rather than the LMD18200. If you want to use the LMD18200, R3 should be a 2.7K resistor, and you can feed the output from pin 8 to the input of the current sense amplifier section.

Even though the inverted amplifier enable signal causes the PIC-SERVO to wake up with the brake signal activated, I also included a pull-down resistor on the LMD18201's PWM input. This prevents the amp from turning on in case the motor power (which powers the LMD18201) is applied before the logic power (which powers the PIC-SERVO).

Connector JP9 is used to connect the PIC-SERVO control module

to an external amplifier for applications where the three amp continuous output of the LMD18201 is not beefy enough. The amplifier enable output appearing on this connector has an optional pull-down resistor (via jumper JP10) for external amplifiers which are enabled if the amp enable signal is left floating. This connector also has an input pin for the op amp section.

The motor connector, P1, has pins for the motor power, encoder inputs, limit switch inputs, and a pin pulled up to 5V with a 330-ohm resistor for driving the LED portion of an optical limit switch. If the motor is located more than a foot or so from the controller, care should be taken in the cabling to isolate the motor power wires from the encoder wires.

It is quite easy to pick up unwanted feedback loops if the encoder signals pick up too much noise from the motor power wires. At a minimum, the motor power wires should be twisted together and the encoder CH-A and CH-B wires each twisted with either GND or +5V. Shielding on top of that is even better.

The communications connectors JP1 and JP2 are nearly identical, with RCV+ and RCV- on pins 1 and 2, and XMT+ and XMT- on pins 3 and 4. The only difference between these connectors, as described earlier, is that JP1 has pin 5 connected to ADDR_IN and JP2 has pin 5 connected to ADDR_OUT.

Logic power can also be transmitted through these connectors, depending on how jumpers JP6 and JP7 are configured. If power is not supplied from either JP1 or JP2, it can be supplied from JP8.

Because each module has its own voltage regulator, the logic power can be anywhere from 7.5-24V, and you don't have to worry too much about line losses over long cable lengths.

If you do want to break up the logic power distribution, jumpers JP6 and JP7 let you select which power goes where.

The last jumpers to look at are JP4 and JP5. These are used for installing termination resistors at the end of the RS485 transmit and receive lines. These jumpers should both be installed on *only* the controller module furthest from the host.

The 0.1 uF capacitors in series with the termination resistors are

used to save power when no data is being transmitted. When the PIC-SERVO disables its transmit driver, however, a lingering charge on C1 may cause havoc with RS485 receivers with insufficient biasing, particularly at higher communications rates. If this is the case, C1 can simply be shorted out.

Communications Software

The full command set of the PIC-SERVO is a bit too involved to discuss here, but I can give you the basics of the communications protocol. Note that you will use the same protocol described here whether you are talking to a single-axis system, or if you are talking to a whole network of controllers.

The PIC-SERVO wakes up with a default baud rate of 19,200 bps. After initialization, the baud rate can be boosted as high as 115,200 bps. (The PIC-SERVO has a special group command format, described in the datasheet, which lets you change the baud rate of all the controllers on the RS485 network at the same time.)

The command protocol is a strict master/slave set-up where each PIC-SERVO only speaks when spoken to. In general, the host will send a command packet to a PIC-SERVO and then wait until that controller sends back a status packet. The host should not send out another command, even to another controller, until the previous status packet is received because then there is the chance both controllers will try to send their status back at the same time over the same pair of wires. The first byte of the status packet should come back within one millisecond; if it doesn't, you know you have a problem.

If the host should ever send a command packet before a status packet is received, any status packet transmission by any PIC-SERVO on the network will be terminated immediately. This prevents collisions on the shared pair of receiver wires.

Both command packets and status packets are of variable length. This allows the host to transmit and receive the minimum amount of data required for any particular operating mode. This will maximize the command rate, which is particularly important when commanding splined

motions.

All command packets consist of the following bytes:

Header byte (0xAA)
Address byte
Command byte
Data bytes (0-15 depending on the command)
Checksum byte

The header byte is always sent at the beginning of a command packet to help synchronize communications between the host and the *PIC-SERVO*. When the *PIC-SERVO* is expecting to receive a new packet, it will throw out all incoming bytes until it sees a header byte. It will then interpret the data following the header byte as a command packet.

Each *PIC-SERVO* can have an address of 0-255 which is set as described earlier. Each controller will only respond to command packets where the address byte matches its own address. All other command packets will be received, but ignored.

The command byte is broken up into an upper and lower nibble. The lower nibble is the command number between 0 and 15. The upper nibble contains the number of additional command bytes required by that particular command number.

For example: The command to set the PID servo gains requires 13 additional data bytes, the command to change the baud rate requires only one additional byte, and the command to reset the position counter requires no additional data bytes.

The *PIC-SERVO* will always try to read the specified number of data bytes, independent of however many are actually required by the given command. The reason for this is that we may wish to communicate with devices other than the *PIC-SERVO* on the same RS485 network.

For example: A data acquisition system designed to work on the same network may know nothing about *PIC-SERVO* commands, but it still must read in the proper number of bytes in order to maintain synchronization. Likewise, the *PIC-SERVO* will know nothing about the commands for other devices, but is still required to read in a complete packet's worth of bytes.

The last byte in a data packet is an eight-bit checksum of all of the previous bytes in the packet *except* the header byte. If this checksum

The *PIC-SERVO* chipset was designed by J. R. Kerr Prototype Development to support industrial development projects in robotics and machine design. The *PIC-SERVO* chipset, as well as a low-cost experimenter's board, are now available as products. Please visit <http://users.aol.com/dcservo/picservo.htm> for complete documentation, application notes, sample schematics, and ordering information. You can E-Mail any questions about the *PIC-SERVO* to DCSERVO@aol.com

Parts List for Single-Axis Controller

U1, U2	<i>PIC-SERVO</i> chipset
U3	MAX232 transceiver
U4	LMD18200 PWM amplifier
U5	20 MHz TTL/CMOS oscillator
C1-C4	10 uF electrolytic capacitor
C5, C6	0.01 uF monolithic capacitor
C7	1.0 uF monolithic capacitor
C8	330 uF electrolytic capacitor
C9-C12	0.1 uF monolithic capacitor
R1-R4	1/8W resistor (assorted values)

Parts List for Multi-Axis Control Module

U1, U2	<i>PIC-SERVO</i> chipset
U3	20 MHz TTL/CMOS oscillator
U4	7805 +5V voltage regulator
U5	LTC491 RS485 transceiver
U6	LMC6492 rail-rail op-amp
U7	74HCT14 Schmitt-Trigger inverter
U8	LMD18201 PWM amplifier
C1, C2	0.1 uF monolithic capacitor
C3, C4	0.01 uF monolithic capacitor
C5	330 uF electrolytic capacitor
C6	1.0 monolithic capacitor
C7, C8	10 uF electrolytic capacitor
C9-C14	0.1 monolithic capacitor
R1, R2	120 ohm, 1/4W resistor
R3, R4, R8	2.7K, 1/8W resistor
R7	330 ohm, 1/8W resistor
R5, R6	20K pot
R9	100K resistor
R10	20K resistor
RN1	4.7K, 8 pin resistor network

does not match the checksum computed by the *PIC-SERVO*, the command will not be executed, but a communications error bit will be set in the returned status packet. Note again that only the *PIC-SERVO* with the matching address will send back a status packet in the event of a checksum error.

The status packet returned by the *PIC-SERVO* consists of the following bytes:

Status byte
Status data bytes (0-14)
Checksum byte

The status byte contains basic information about *PIC-SERVO*, including a communication error flag, a move done flag, assorted error flags, and limit switch input values. The additional status data bytes may include a variety of additional data including the current motor position, the current Motor velocity, the A/D value, etc. Exactly which data is included in these additional status bytes is programmable by the host.

For example: A tracking application may require the current position to be returned with every command, but velocity, A/D value, and home position may not be required. Once the required status data bytes are specified (using a define-status command), they will be returned after every subsequent command, even if that command had a checksum error. The details of commands for the

PIC-SERVO can be found in the *PIC-SERVO* datasheet, along with the particulars for initializing devices, sending commands synchronously to groups of controllers, status data options, etc. In general though, there are commands for initializing the address and baud rate, reading and defining status packet data, loading motion parameters and starting motions, loading PID servo parameters, stopping the motor in various modes, resetting the position counter and status bits, and homing and I/O commands.

Other Network Devices

As mentioned earlier, the communications protocol was designed so that devices other than the *PIC-SERVO* can be operated on the same network. In fact, I have built data acquisition boards, multi-function I/O boards, and even a simple sound board, which all operate quite nicely on the same cable as the *PIC-SERVO* controllers. Unlike other RS485-based networks (like the CAN bus), the *PIC-SERVO*'s full-duplex network protocol is much simpler and can be easily implemented for any eight-bit microcontroller, even with only a software UART.

The only commands which must be supported by all controllers are the set-address command, the set-baud command, the hard-reset command, and the command to read the controller device type. NV

Write your PIC programs in BASIC!

PicBasic Compiler

\$99⁹⁵



BASIC makes it easy for you to program the fast and powerful Microchip PIC microcontrollers.

- Expanded BASIC Stamp I compatible instruction set
- True compiler provides faster execution & longer programs than BASIC interpreters
- New!** Peek & Poke to access PortA, A/D converter; any PIC I/O port or register in BASIC
- In-line assembler & call support
- Supports PIC16C6x, 7x & 8x
- Use with most PIC programmers

*Formerly PBASIC Compiler.
BASIC Stamp is a trademark of Parallax, Inc.

Also: PICProto Boards - \$8.95-\$17.95
EPIC Pocket PIC Programmer - \$59.95

microEngineering Labs

Box 7532 Colorado Springs CO 80933
(719) 520-5323 FAX 520-1867
www.melabs.com

Write in 123 on Reader Service Card.



The RF Connection
213 North Frederick Ave.
Suite 111N
Gaithersburg, MD USA
20877

Complete Selection of MIL-Spec Coax, RF Connectors and Relays

UG-21B/U N Male for RG-213/214 \$5.00
UG-21D/U N Male for RG-213/214 \$3.25

N Connectors for 9913/Flexi4XL/9096

UG-21B/9913.....\$5.75 Pins Only.....\$1.50
UG-21D/9913.....\$4.00 Extra Gasket......50

Amphenol 83-1SP-1050 PL-259 \$0.90
UG-176/U Reducer RG-59/8X..... .25 or 5/\$1.00
UG-175/U Reducer RG-58/58A..... .25 or 5/\$1.00
J&I Silver Teflon PL-259 MIL-Spec.....
.....\$1.25 or 10/\$10.00

MIL-Spec Coax Available (Teflon, PVC 11A)
Certified CQ Flexi 4XL811A (Flexible 9913)

New Product: International's 9096-2A Low Loss RG-8 Size, Stranded Center Conductor Same Specs As 9913..... .70/ft or \$59.00/100ft

Also New: RG-8X Clear w/UV Jacket 98% Cu Intro Price \$14.00/100ft

Call for Specials of the Month

Full Line of Audio Connectors for Icom, Kenwood, and Yaesu

8 Pin Mike Female.....\$2.00
8 Pin Mike Male Panel.....\$2.50
13 Pin DIN for Kenwood.....\$2.75
8 Pin DIN for Icom.....\$1.00
8 Pin DIN for Kenwood.....\$1.50

Prices Do Not Include Shipping

Orders 800/783-2666
Info 301/840-5477
FAX 301/869-3680

Write in 152 on Reader Service Card.

AIRCRAFT TESTING equipment, oscilloscopes, counters, signal generators, and many others. Repair and NIST traceable calibrations available. We also manufacture test sets and other equipment for the aviation industry. Guaranteed professional work. Call: 305-267-8418 or 305-269-8681.

BUY, SELL, trade avionics equipment, IFR, Collins, TIC, Mil, HP, Linaire, King, Shop equipment, Kingsley, Eubanks wire stamp machines. Need Litton INU, type LTN-72. 941-575-0138, fax 24 hrs. 941-575-2361.

Subscribe to Nuts & Volts!
Call 1-800-783-4624

PUBLICATIONS

WORLD'S MOST UNUSUAL Communications Books! Large selection covering Scanners, "confidential" frequency (HF/VHF) registries, wireless history, bugging, wiretapping, electronic surveillance, monitoring, etc. Big free catalog! CRB Research, Box 56-NV, Commack, NY 11725.

THE CASE AGAINST PATENTS. Don Lancaster's tested and proven alternatives that work in the real world. \$28.50, Synergetics Press, 3860 West First Street, Box 809, Thatcher, AZ 85552. 520-428-4073. synergetics@tinaja.com VISA/MC.

"FORBIDDEN SECRETS Of The Legion of Doom Hackers." Big 224-page handbook. Condensed programs & techniques from the infamous LOD's shut down BBS. Hacking, phreaking, & more! Limited edition. \$20.95 plus \$5 S/H (\$6 Canada). NYS add \$2.14 tax. VISA/MC OK. CRB Research, Box 56-NV, Commack, NY 11725. Phone orders: 1-800-656-0056.

ENGINEER'S SECRETS of radio, 200 pages, tube amps, schematics/projects \$15. Low power radio book for schools/experimenters \$10. J. R. Cunningham, PO Box 8, Stonewall, OK 74871.

THE MOST EXTRAORDINARY hacking catalog in the world! www.spectre-press.com

START YOUR OWN TECHNICAL VENTURE! Don Lancaster's newly updated **INCREDIBLE SECRET MONEY MACHINE II** tells how. We now have autographed copies of the Guru's underground classic for \$18.50. Synergetics Press, Box 809-K, Thatcher, AZ 85552. 520-428-4073. VISA/MC.

HOME AUTOMATOR: "The Newsletter of Home Automation Ideas." Each issue contains technical articles, schematics, feature homes, how-tos, and product reviews. Subscription \$19.95/year. <http://www.auto-mator.com> Home Automator Newsletter, 2258 Sandy Lane, Mebane, NC 27302. 910-578-9519 (voice), 910-578-0012 (fax).

HACKERS AND EXPERIMENTERS BOOKS. Cable Hackers Bible Volumes 1 & 2 \$44.45 each, Scanner Hackers Bible Volume 1 & 2, \$34.45 each, Satellite Hackers Bible \$54.45, 8.6 megabytes hacker software \$29.95, Black Box Bible \$34.45, Phone Phreakers Bible \$34.45, Phone Box Bible \$43.45, Superhackers Bible Volumes 1 & 2, \$34.45 each. Add \$2 per order for insurance. Many more plus videos! Ask for **new 40-page 1996 catalog**. Only \$1 in USA, \$3 elsewhere. TELECODE 520-782-2833. <http://www.hack-erscatalog.com>

MILITARY COMPONENTS wanted. Capacitors, resistors, diodes, transistors, semiconductors, ICs. Electronic Material Industries, 818-842-5953, FAX: 818-845-3613.

PLANS/KITS/SCHEMATICS

MILITARY COMPONENTS wanted. Capacitors, resistors, diodes, transistors, semiconductors, ICs. Electronic Material Industries, 818-842-5953, FAX: 818-845-3613.

THE MOST EXTRAORDINARY hacking catalog in the world! www.spectre-press.com

RECOVER "SCRAP GOLD" from old computer junk. Free information packet. Call 24 hours: 603-645-4772.

RING-IT! Phoneline Simulator Kit. Authentic dial tone, busy signals, 20Hz ringing. Easily tests or demonstrates phones, voice mail, modems, fax, etc. Deluxe kit \$149. Includes PCB, all electronic parts, microcontroller, documentation. Custom enclosure \$34.95. Shipping \$6.50. Major credit cards, money order. Digital Products Company, 134 Windstar Cir., Folsom, CA 95630. 916-985-7219, Fax 916-985-8460, E-Mail: DigProd@aol.com

TEST DEVICES, manuals and software. Call Jack at 313-384-3949. No Michigan sales.

HOBBY CATALOG: Broadcast, ham, CB transmitters, amplifiers, antennas. TV add-ons, descramblers, bugging devices, science projects, start your own radio station books and more. PAN-COM International, Box 130-V, Paradise, CA 95967.

HEATH COMPANY is selling photocopies of most Heathkit manuals. Only authorized source for copyright manuals. Phone: 616-925-5899, 8-4 ET.

SCHEMATICS AND DOCUMENTATION for remote control miniature encoded RF and IR transmitter and receiver boards. \$5 Inventive Solutions, PO Box 8, Stratford, NY 13470. E-Mail: invent@klink.net

200+ ELECTRONIC PLANS & KITS. Build for pleasure or resale. Make 100% profits reselling printed plans. LSASE for list & dealer info. MATCO-A3, POB 509, ROSEVILLE, MI 48066-0509.

ATTENTION HACKERS AND PHREAKERS. For a catalog of plans, kits and assembled electronic "TOOLS" including the RED BOX, RADAR JAMMER, SURVEILLANCE, COUNTERSURVEILLANCE, CABLE DESCAMBLERS and many other HARD-TO-FIND equipment at **LOW PRICES**. Send \$1 to M. Smith-01, PO Box 371, Cedar Grove, NJ 07009

QUALITY KITS. Electronic project kits for assembly. Please call for free catalog 1-888-GO-4-KITS, or check out www.qkits.com

12-24 VDC Hi-Torque Gear Head Motor \$34.50

This worm drive permanent magnet motor was originally designed to drive wheel chairs - so it is pretty powerful! We have two types, single and double shaft. The single shaft motor runs 760 rpm @ 12vdc. The double shaft runs 160 rpm @ 12vdc. Both motors have 1/2 inch shafts, and measure approximately 9.5" x 4.5" at the widest points, with a motor diameter of about 3". These are great for all kinds of projects, from wheelchair carts to sled pullers! Mailorder customers include \$6.50 for shipping/handling.

VIRTUAL REALITY COLOR VIDEO HEADSET WITH AUDIO AND MOTION SENSOR \$65.00

Watch late night TV without disturbing anyone! This video viewing system can be connected to your vcr and you can watch (and hear) your program on the headset! Of course, it is not like the picture on that 12 foot big screen at the local sports pub, but you can watch in your jammies and see who the guests are on your favorite late night talk show!

Play your favorite video games arcade style! Designed for use with many Super NES and Sega Genesis games, the headset has both audio and motion sensing capabilities. Generally speaking, this is ideal for racing, flight, and tank simulators with a first person or rear view perspective, and games with an eye level perspective.

System features volume control, sensitivity control, brightness control, tint control, as well as a reset button and mode switches to select your application.

Composite video headset system includes headset, tracking tube (for motion sensing), AC adapter, Super NES cable assembly and Sega Genesis cable assembly. A pinout is also included for TV/VCR wiring.

30 pc. TAMPER-PROOF SECURITY BIT SET \$16.95

Drive bits with hollowed tips designed for those security screws often found in computers and other modern equipment. This set includes 9 different sizes of Torx bits (T1-T9), 4 sizes of square drive bits (S0 thru S3), 7 different sizes of hex bits (from 5/64 to 1/4), as well as flat and Phillips bits, a socket holder, a 1/4" adapter, and a magnetic tipped handle to accommodate all the bits in the set. Handle also has a storage compartment for pocket use, and the complete set comes in a sturdy plastic storage case. Ideal for the bench or toolbox.

THE FINE PRINT: PRICES SUBJECT TO CHANGE WITHOUT NOTICE. GATEWAY IS NOT RESPONSIBLE FOR PRINTING ERRORS. *MASTERCARD, VISA AND DISCOVER ACCEPTED. *YES, I'LL TAKE YOUR CREDIT. *SORRY, NO C.O.D.s. *\$10 MERCHANDISE MINIMUM ON MAIL ORDERS. *SUPPLY OF SOME ITEMS IS LIMITED. *PRICES DO NOT INCLUDE SHIPPING. *UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL FEES ARE NOTED). *\$4.95 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. *RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. *ILL LISTEN TO PERSON WHEN IT COMES OUT ON COMPACT DISC!

3-TIER SPLIT TOP TOOL CASE \$61.00

Aluminum tool case measures 14-1/8" x 8-1/2" x 9-1/4". Split top for easy access, this great case features three levels of sectioned compartment space for parts, tools, etc. Compartments are easily adjustable for various size items. Compartments are stacked tackle-box style for maximum space usage. Silver-tone case features sturdy handle and rugged safety latches with key lock.

ATTACHE TOOL CASE WITH TOOL PALLET \$41.00



A professional looking aluminum briefcase style tool case with removable recessed pallets for your tools. This silver colored case features combination locks, a sturdy handle, and compartment separators in the bottom of the case for additional storage. The perfect pick-up-and-go tool case. Dimensions: 18" x 13" x 6".

ATTACHE TOOL CASE WITH TOOL PALLET & CUSTOM FOAM INSERT \$51.00

A professional looking aluminum briefcase style tool case with removable recessed pallet for your tools. This silver colored case features key locks, a sturdy handle, and foam section separators in the bottom of the case for additional custom storage. Ideal for specialized tool transport or just as a great all-purpose tool attache. Dimensions: 18" x 13" x 6".

127 THERMOCOUPLES Peltier Junctions



The peltier junction is a solid-state thermoelectric device. Current applied to the device will produce heat on one side of the device and a cold surface on the other side.

Water placed on the surface will freeze or boil depending on polarity of applied voltage. Ideal for applications from 3-12 VDC - grab a battery and let your imagination run wild!

DOCUMENTATION INCLUDED!!!

Small Peltier Junction \$20.00 (approximately 1.17"x1.17"x.12")

Large Peltier Junction \$29.50 (approximately 1.56"x1.56"x.15")

HAM RADIO TO CAR SPEAKER ADAPTER \$11.50

Now you can listen to your ham radio or scanner (mobile or handheld) through the speakers of your car stereo system as well as control tone and volume. Imagine the quality of stereo sound as you listen to the latest 2m rag-chew or tune into a hot police pursuit! This adapter fits in the cassette player of your car audio system, and connects via a 3.5mm plug to your radio speaker jack. Makes your handheld or mobile sound like a base station. Also can be used to play your portable cd player through your car audio system.

VISIT US ON THE INTERNET:
www.gatewayelec.com

AA NICKEL METAL HYDRIDE BATTERIES

1200 mAH Nickel Metal Hydride rechargeable batteries are AA size with standard button end. Ideal for many projects, and cellular phone and handheld radio battery packs, etc.

set of 4 batteries \$13.50 MONITOR AMERICA! \$29.95

The bible for scanner users, this new 3rd edition national communications guide is bigger and better than ever. Wherever you are in the U.S., you can enjoy your scanner and keep up with your favorite scanning activities. Frequencies, maps, codes and descriptions of State Police/Highway Patrol, Federal Government, U.S. Military, Colleges & Universities, Marine Radio, Cellular and Cordless phones, Civil Defense, Fish, Game & Wildlife, and more. Special sections on race car teams and tracks, Disneyland and Disneyworld, Amusement parks, Museums and concert halls, news media...the list goes on and on!

TV TRANSMITTER KIT \$27.95

Tired of lugging the VCR to another room to see a movie while Aunt Martha watches reruns of the Julia Child special on PBS? Sick of stringing wires through the house so Junior can watch the latest Power Ranger movie in the comfort of his room? Never fear, we've got the solution! This kit allows you to send any audio and video source, like a VCR or TV camera, to any TV set for up to 300 feet. With this little kit, you're the producer and the programming director of your own TV station. Tunable to any TV channel 2-6, runs on 12 VDC, and accepts standard audio and video signals. Optional matching case set, \$14.95.

BE A FLY ON THE WALL!!!

Well, actually, those little wings would look pretty stupid on you, but you can build a miniature "bug". Surface mount technology is the latest techno-buzz word, and a challenging new frontier for kit builders. The manufacturer understood that the first try might be a bit rough, so they included enough components to assemble two units. (so it is o.k. to lose or damage a SMT component). With the entire FM broadcast band (from 88 - 108 MHz) for your receiver, and a transmit range of 300 feet, even James Bond would like this kit! This unit is powered by a 1.5 volt watch battery (included) and features an electret type high gain microphone for superior audio quality and extended pick up range - hear a whisper at 10 feet. A lot of fun in less than a square inch!! Micro Size FM Wireless Transmitter Kit \$19.95



gateway ELECTRONICS, INC.

8123 PAGE BLVD. * ST. LOUIS, MO 63130
(314)427-6116
9222 CHESAPEAKE DR. * SAN DIEGO, CA 92123
(619)279-6802
2525 FEDERAL BLVD. * DENVER, CO 80211
(303)458-5444
MAIL ORDERS CALL TOLL-FREE
1-800-669-5810
FAX ORDERS (314)427-3147


RADIO DATA MODULES



Transmitters

- Only 30 x 10 x 5mm
- ERP 0.25mW into 50Ω
- 3V, 5V(F) or 6-12V(A) versions
- Up to 20k bps data transfer
- 418 or 433.9MHz FM
- Simple to integrate - simply add antenna, data, power
- Range up to 200m
- Analog or digital data i/p
- SAW controlled - stability

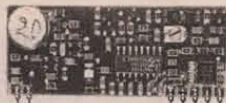TXM-4XX-A..... \$24.50
TXM-4XX-F..... \$25.80



Receivers

- Only 21 x 47 x 5mm
- 13mA; 130uA on power save (100:1)
- Carrier detect o/p
- Simple to integrate
- Up to 20k bps
- 418 or 433.9MHz FM Superhet
- SAW controlled - stability
- Analog or digital o/p
- Wide supply range 4.5-9V (A/F ver.)
- Fast enable time <3ms

SILRX-4XX-A..... \$39.38
SILRX-4XX-F..... \$41.92



Transceiver

- Only 23 x 33 x 11mm
- Up to 40,000bps of balanced code
- 19200 baud with ASCII
- Up to 170m range.
- 5v operation
- 0.25mW into 1/4 wave antenna
- 418 or 433MHz FM
- Fast 1ms enable for power saving
- Direct interface to 5V CMOS logic
- Auto TX/RX changeover

BIM-4XX-F..... \$87.36

Transceiver with RS 232 Interface & Controller



- 4,800 to 38,400 bps half duplex
- 3-wire RS232 interface
- Microcontroller with user EEPROM
- RS232 interface protected to ±15kV
- Auto TX/RX changeover
- 418 and 433MHz versions
- Windows operation under file mode
- Range 120-200m
- 0.25mW, 1mW & 10mW versions
- Reset switch and status LED's
- 9V dc via 9 pin connector <20mA

BIM-4XX-RS232 \$139.30



Call 416-242-3120



ABACOM
TECHNOLOGIES

67 Hamptonbrook Dr., Etobicoke, ON, M9P 1A2

Fax: 416-242-2697
Faxback: 416-242-3082



Volume discounts • Free Catalog available.

CNC-STEPPER MOTOR controllers. 3 axis chopper driver kits \$145. Assembled \$195. 3 axis L/R controller kit \$95. Single stepper motor controller kit \$20. See <http://www.seanet.com/~dmauch> for additional information on low cost CNC, or call 206-487-0013. Camtronics, Inc., 18230 130th Pl. NE, Bothell, WA 98011-3118.

WHOLEY NAUSEA Batman! Sick to tears of nothing but O.J. lunacy on the glass imbecile generator? Why not curl up with a cup of hot cocoa and some of our calming schematics. 2700+ reverse engineered prints clumped into 22 catalogs. Send us 4 STAMPS for list of catalogs and guaranteed O.J. less propaganda. **BOMARC SERVICES**, Box 1113, Casper, WY 82602. 307-234-3488.

REVERSE ENGINEERS BIBLE. Theory and operation behind reverse engineering: computers, cell phones, scramblers, GALS/PALS, encryption, dongles, patents, and more. Software included for file editing, comparison, logic determination, cracking, disassembling, and more. \$46.45 postpaid 520-726-2833. **TELECODE**, PO Box 6425-NV, Yuma, AZ 85366-6426.



CIRCUIT BOARDS Single sided. Small runs. No minimum. No set-up fees. No drilling fees. No hidden costs. No per hole charges. Complete price list available. We even pay shipping on pre-paid orders. Circuit Design, PO Box 5415, Central Point, OR 97502, 541-664-7904. Phone or Fax.

CopyCat

Motorola EE3
\$1295

- Pocket Size
- Operates on 9-volt Battery
- Easy to read LCD Display



Now Available:

***EE3**

*7-Way Boxes

*Load Code Removal

*Repair & Update Old Units

"CopyCat, Black Box, Stand-alone Programmer"
You have all heard of this amazing device, now you can own one for yourself. Complete with cables, and easy instructions. No kit to put together. Completely Assembled & Pre-tested.

Electronic Service & Supplies
219-744-4788

BYDN38B@Prodigy.com
<http://www.cris.com/~macguyvr>

Write in 85 on Reader Service Card.

ATTENTION DEALERS

BUY DIRECT FROM THE WHOLESALE

GET THE BEST PRICES AND SERVICE

ALL UNITS ARE IN STOCK FOR IMMEDIATE SHIPMENT

CABLE CONVERTERS AND ACCESSORIES

CALL FOR PRICING ON ITEMS NOT LISTED

NEW CONVERTERS

	QTY 5	QTY 10	QTY 20	QTY 50+
CENTURY CT-3000	\$68	\$64	\$60	CALL
COMMERCIAL-11	\$75	\$70	\$65	CALL
PANASONIC-1003	\$59	\$55	\$50	CALL
ZENTEK	\$45	\$40	\$37	CALL

NOVAVISIONS

NV-5600	\$205	\$195	\$185	CALL
NV-5700	\$195	\$185	\$175	CALL
NV-5800	\$195	\$185	\$175	CALL
NV-5750	\$305	\$295	\$285	CALL

REFURBISHED CONVERTERS
REGAL • PANASONIC CALL FOR THIS MONTH'S SPECIALS

1-800-800-0766

KIMTRONIX

30 day money back guarantee. All shipping and handling at customers expense. Anyone implying theft of cable service will be denied sale. NO FLORIDA SALES. WE WILL MEET OR BEAT ALL COMPETITOR'S PRICES IN THIS MAGAZINE

Write in 113 on Reader Service Card.

Learn by Example!

The PRIMER 8085 Based Microprocessor Training and Control System shows you how to program by example. Program examples take you from writing simple programs to controlling motors. This trainer can be used stand alone via the keypad and display or connected to a PC with the optional upgrade (\$49.95). The Upgrade includes: an RS232 serial port, a serial cable, 32K of battery backed RAM and Assembler/Terminal software.

EXPERIMENTS USING THE PRIMER INCLUDE:

- Measuring Temperature
- Using a Photocell to Detect Light Levels
- Making a Waveform Generator
- Constructing a Capacitance Meter
- Motor Speed Control Using Back EMF
- Interfacing and Controlling Stepper Motors
- Scanning Keypads and Writing to LCD/LED Displays
- Using the Primer as an EPROM Programmer

The PRIMER is only \$119.95 in kit form. The PRIMER Assembled & Tested is \$169.95. Please add \$5.00 for shipping within the U.S. Picture shown with upgrade option and optional heavy-duty keypad (\$29.95) installed.

ENAC, inc.
P.O. BOX 2042, CARBONDALE, IL 62902
618-529-4525 Fax 457-0110 BBS 529-5708

1985 - 1996
OVER
10
YEARS
OF SERVICE

Write in 133 on Reader Service Card.

January 1997 **83**

TECH FORUM

This is a READER TO READER Column. All questions AND answers will be provided by *Nuts & Volts* readers and are intended to promote the exchange of ideas and provide assistance for solving problems of a technical nature. All questions submitted are subject to editing and will be published on a space available basis if deemed suitable to the publisher. All answers are submitted by readers and **NO GUARANTEES WHATSOEVER** are made by the publisher. The implementation of any answer printed in this column may require varying degrees of technical experience and should only be attempted by qualified individuals. Always use common sense and good judgement!

QUESTIONS

Can someone give me information on building directional AM broadcast band antennas, or a simple antenna preselector/booster? I've seen a device called a Select-A-Tenna advertised and would like to homebrew something along these lines.

1971 Gary De Pietro, Deltona, FL
gary.depietro@dlbbs.com
gary.depietro@juno.com

I have a Uniden satellite receiver. Is it possible to capture weather signals from any satellite and send it to the TV? I would need a loop Yagi to get 1691 MHz and downcount to 137.5 MHz. Will this receiver do the job?

1972 Richard Trowbridge, Tucson, AZ

I have a nice little laptop sharp PC 5500 (Model #5541). It's old, but dear. I wonder if it can be upgraded either CPU, memory, or anything. I have tried to obtain a manual from Sharp, but they sent the wrong one. Does anyone have a similar model? It works off 10 nicads (at 1.2 volts), but the supply feeds it 17 volts. Why the higher voltage?

1973 Jim Wiggins, Atlanta, GA

What's the simplest, reliable method of sensing a load to make a gasoline 120-volt generator throttle up, then to come back to idle when the load is removed. There is 12 volts present when the power plant is in idle mode. What circuitry would this require?

1974 John W. Jones II, El Dorado Springs, MO

I would like information on how to use the WWV time signal that is broadcast on 25 MC to set a digital clock each time it receives the signal.

1975 W. Schopp, Livermore, CA

When tuning in stations, my AM/FM radio integrated receiver started fading, then returning to normal. There is also lots of static. The antenna checked out okay. What is the problem?

1976 S. Palaski, Crestline, CA

I recently bought a used Identity

Systems Technology, Inc. hand scanner, part #GS8-Rev. #114 ID SCAN GS8.01. I need the card and software to make this thing work. I can't find IST on the Net. Any ideas on how to interface it? Any information would be helpful.

1977 Jim Poelstra, Stockton, CA
E-Mail: jimpolstrami@juno.com

In the Sept. '96 issue you ran an article on the repair of PC power supplies. In the PC power supply, there is also a POWER OK signal which is sent to the motherboard, or received from the motherboard(?). I assume it originates in the power supply.

Just what is the characteristics of that signal, and how does one simulate it if they want to use a power supply which either doesn't have that POWER OK capability, or the POWER OK circuit is faulty.

1978 Joseph A. Dickerson, Baltimore, MD

ANSWERS

ANSWER TO #12964 - DEC. 1996

Every gel-cell I've encountered uses good old fashion lead/acid technology, with a modern gelled electrolyte. A 12V gel-cell has the same charging characteristics as a common automobile battery. The internal resistance of the battery will limit the charging current of the cell.

As long as Mr. Delany's alternator is functioning correctly, no additional regulation should be required for charging the gel-cells. The simplest connection would be directly to the car batteries terminals. A 12V gel-cell has a voltage of 13.8V when fully charged, the same as a car battery.

I've float charged my gel-cells on the output of my 13.8V/35A power supply constantly, and when I want to take them mobile, I float charge them from my car's cigarette lighter. I've done this for over two years without any damage to my gel-cells.

Darryl Gibson, via Internet

ANSWER TO #12967 - DEC. 1996

You can't run this motor on the specifications you mentioned because the windings in the motor are wound for a different impedance.

The purpose of the 400 cycles is to reduce the amount or size of the windings necessary. The faster rate of cycle lowers the resistance for a

given, while maintaining the same amount of power output.

Applying a slower frequency such as 60 Hz will overheat the windings while producing less power, and the motor may not run at all.

Rewinding the motor is impractical because purchasing a replacement motor is far cheaper.

Making a solid-state 400 Hz inverter is only practical if this application warrants it, and the only inexpensive alternative is a WW2 surplus inverter which is commonly referred to as a Dynamo or Dynamotor.

This inexpensive unit can be purchased through surplus companies such as Fair Radio Sales in Lima, OH, and are usually less than \$30.00.

These units usually consist of 12 or 24 VDC motor attached to an alternator which spins at an exact rate, and the alternator, in turn, produces 400 cycles at the desired AC voltage. Each unit has a maximum amperage and voltage rating while maintaining 400 Hz. Choose a unit that has more amps and volts than necessary. You can lower the input voltage to the Dynamo slightly for a voltage adjustment as long as you don't go overboard and smoke the windings.

Unfortunately, a variable output voltage to control the RPM on your motor is impractical due to the three phase requirements of your motor. You can purchase a three-phase chopper circuit similar to a light dimmer and install it on the Dynamo output, but because these units consist of two perfectly matched single units, they are usually very expensive. A three-phase chopper will lower the voltage while maintaining the 400 cycles.

I use a miniature Dynamo to operate my gyroscopes and power this unit from my wall socket using a 120 volts light dimmer, diode bridge, and capacitor to achieve the 24 DC volt input to the Dynamo. Varying the unit's input by $\pm 20\%$ hasn't caused any adverse effects to either the Dynamo or the gyro which spins at over 50,000 RPM.

Chris Bieber, CA

ANSWER TO #12963 - DEC. 1996

First, in direct answer to your question, there is no book that I am aware of that will give you hook-up techniques for your situation. Most people have manuals that come with each piece of gear when purchased that show them the proper usage

ANSWER INFO

- Include the question number that appears directly below the question you are responding to.
- Payment of \$25.00 will be paid within four weeks of publication if your answer is printed.
- Only one answer per question will be printed.
- If you do not want your name, address, or phone number available to the reader please so indicate or it will be assumed that you have no objection.
- In the event that more than one person submits the same solution, the choice will be made at the discretion of the publisher.
- Due to space limitations, we can not reprint the original questions with the answer. The question number and the issue it appeared in are printed above the answer.

QUESTION INFO TO BE CONSIDERED FOR PUBLICATION

All questions should relate to one or more of the following:

- 1) Circuit Design
- 2) Electronic Theory
- 3) Problem Solving
- 4) Other Similar Topics

INFORMATION/RESTRICTIONS

- No questions will be accepted that offer equipment for sale or equipment wanted to buy.
- Selected questions will be printed one time on a space available basis.
- Questions may be subject to editing.

HELPFUL HINTS

- Be brief but include all pertinent information. If no one knows what you're asking, you won't get any response (and we probably won't print it either).
- Write legibly (or type). If we can't read it, we'll throw it away.
- Include your Name, Address and Phone Number. Only your name will be published with the question, but we may need to contact you.

and installation requirements to enjoy their devices.


To assist you with your situation, the following explanation is given. It seems like you wanted to record tape and play tape on your VCR at the same time. This is not possible. Then it was not stated in what fashion you wanted to operate. That is, did you want to watch a broadcast television station and record a satellite program or record a broadcast television program and watch a satellite program?

You did not describe the connec-

TECH FORUM

ANSWER TO #12962 - DEC. 1996

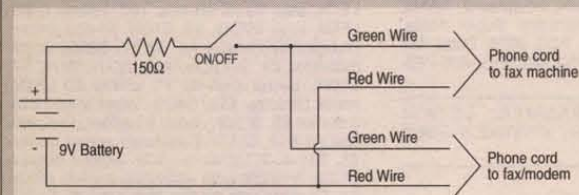Your hunch that a little money could be saved by building your own fax machine to PC fax/modem interface is correct. The following circuit will do the job at a very minimal cost:



The ON/OFF switch is not required if the interface is disconnected when you're finished scanning. The black and yellow phone cord wires are not used.

I have successfully used this interface with a Brother InstaFax

300, Sharp FO-510, and Tandy 1500 fax machine to scan graphics and text into my PC. The software I use is Windows Procomm Plus Ver. 2.0. The scanning procedure is very simple. Set the fax resolution and prepare to transmit the document as you normally would, select "Receive Fax Now" from the fax pull-down menu, and lift the

handset and push the start button on the fax machine. With some fax machines you may need to key in a phone number before they will transmit.

John McMichael
Laramie, WY

tion capabilities of your equipment, so I will make some assumptions. It would be best if you had two separate input connections to choose from on your television. Let's assume you don't. The easiest way to approach this is split the output of both your broadcast feed and your satellite feed. Hook one of each to two A/B type switches. One switch will feed the VCR and the other will feed the TV. The problem then arises on how to view the recorded material. You would need a third A/B switch for the input to the TV to select from either the VCR feed or the "antenna" feed. With this combination of switches you can do all you wish. The only drawback is all the additional wiring and switch signal losses.

A simpler method would be using a newer television that has two or more antenna/source connections that can be viewed independently. This would eliminate at least one of the three switches above. Even simpler would be to own a second VCR and the multiple input television. Then wiring would remain simple and you could record anything to your hearts content.

Mark Hanz
Houston, TX
mhanz@wt.net

ANSWER TO #12965 - DEC. 1996

You can find lightning arrestors by calling most amateur radio dealers. One would be Amateur Electronic Supply, 1-800-558-0411. They stock lightning arrestors and are affordable.

Mark Hanz
Houston, TX
mhanz@wt.net

ANSWERS TO #12966 - DEC. 1996

I'm assuming the spindle and not the reel is missing and so aside from getting new or used parts from somewhere, with the help of a good mechanic or tinkerer, you can replace the take-up spool with a motor out of an old VCR and adapt it as a take-up spindle either directly or via a belt drive.

The problem with the take-up

spindle is that it has to feed at a higher rate than the tape speed because the reel speed varies according to the amount of tape on it. Consequently, you need a very weak motor which attempts to spin too fast while not adding any significant pull to the tape because any excess pull will speed up the feed rate of the tape, and thus change the recording or playback speed. In essence, it slips like a clutch and continually tries to accept more tape than is available, while not pulling at the tape too hard.

VCR motors are perfect for this job because they do the same function in the VCR and draw very little power.

Chris
Beiber, CA

Many radio stations use reel-to-reel tape recorders for program production. You might try contacting the engineer at your local station to see where he obtains parts. He might even have some parts that he could sell or give to you. He may also know a good source for reel-to-reel tapes. If not, Radio Shack stocks 5" take-up reels (cat. no. 44-278), 7" reels (44-279), and 5" tapes (44-1883), plus 7" tapes (44-1884).

Packet modems for the Commodore 64 are available through the special order catalog at Radio Shack (11264678) as a kit. The case is part #11264686. Other sources have this modem also.

Steven Vail
Martinsville, IN

ANSWER TO #12968 - DEC. 1996

Nuts & Volts may have the solution to your remote control application. In the Dec. '96 issue, check out the Street Smart Security ads on pages 34 and 102. On page 80, Inventive Solutions is selling schematics and documentation for remote control RF and IR transmitter and receiver boards for \$5.00.


John McMichael
Laramie, WY



Global Connections


P.O. Box 8547, St. Joseph, MO, 64508
1-800-626-0834, FAX (816) 364-2619

New Owners and Management

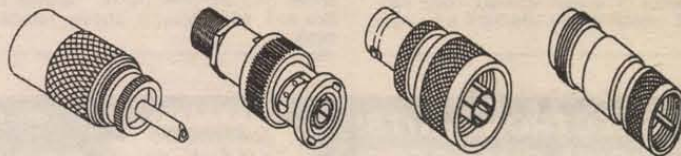

Consistently low prices on your connection needs.

Call, FAX or Write for a catalog

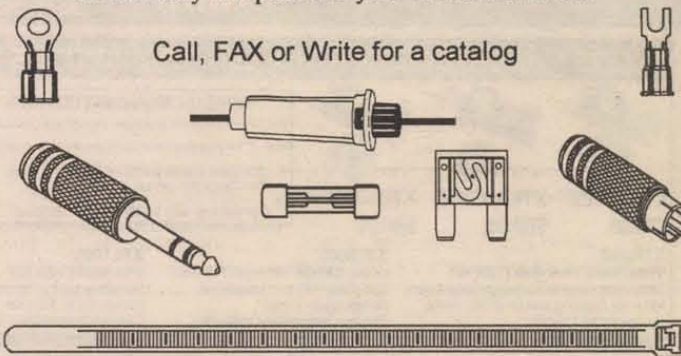

Celebrating our 14th Year Of Service !!

RECTANGLE LED - (.124" x .212")				
		• Forward Volt. -		
		1.7-2.2V		
		• Forward Current -		
		50ma		
		• Diffused		
STOCK#	COLOR	1-24	25-99	100+
SB1089	Bright Green	.24	.23	.21
SB1090	Yellow	.15	.14	.13
SB1091	Bright Yellow	.24	.23	.21

INFRA-RED COLLIMATOR PEN				
		A low power collimator pen containing a MOVPE green gain GaAlAs laser diode. Pen delivers 2.5mW @ 820nm. Operating voltage of 2.2-2.5V @ 90-150mA is designed for lower power applications. Measures 11 mm x 27 mm.		
STOCK#	1-4	10-24	25+	
SB1052	49.99	47.49	42.74	

COMPUTER CARE KIT				
		A complete computer care kit containing:		
		• Cleaning diskette		
		• Head-cleaning fluid		
		• Cleaning swabs		
		• Anti-static cleaner		
		• Anti-static screen wipes		
STOCK#	1-4	10-24	25+	
SB1099	3.99	3.79	3.41	
SB1100	3.99	3.79	3.41	

LOW PROFILE IC SOCKETS				
		• Tin Plated Contacts		
		• .125" Lead Length		
		• .156" Body Height		
STOCK#	PINS	1-24	25-99	100+
S08	8	.08	.07	.06
S014	14	.08	.07	.06
S016	16	.09	.08	.07
S020	20	.09	.08	.07
S024	24	.12	.11	.10
S028	28	.12	.11	.10
S032	32	.14	.13	.12
S040	40	.14	.13	.12

SINGLE TURN POTENTIOMETERS				
		• 1/2 Watt		
		• 10% Tolerance		
		• 3/8" Square		
		• 10-5 Grid		
		• Top Adjustment		
STOCK#	VALUE	1-24	25-99	100+
P0150	50 Ω	.69	.66	.59
P01100	100 Ω	.69	.66	.59
P01500	500 Ω	.69	.66	.59
P011K	1K Ω	.69	.66	.59
P012K	2K Ω	.69	.66	.59
P015K	5K Ω	.69	.66	.59
P0110K	10K Ω	.69	.66	.59
P0120K	20K Ω	.69	.66	.59
P0150K	50K Ω	.69	.66	.59
P01100K	100K Ω	.69	.66	.59
P01200K	200K Ω	.69	.66	.59
P01500K	500K Ω	.69	.66	.59
P011M	1 Meg Ω	.69	.66	.59

Switching Power Supply				
		• 115/230 V input		
		• 41 watt		
		• 5v @ 3.75 A		
		• 12v @ 1.5 A		
		• -12v @ 0.4 A		
		• 7" L x 5.25" W x 2.5" H		
STOCK#	1-4	10-24	25+	
PS1003	17.99	17.09	15.38	

What Do We Have ?				
• I.C.'s	• Capacitors	• Connectors	• Trimpots	• Kits
• Oscillators	• Crystals	• Diodes	• Vises	• LED's
• Tools	• Laser Diodes	• Vises	• Transistors	• And more!
• Resistors				

GADGETEER'S GOLDINE				
		This exciting collection of electronic projects features experiments ranging from magnetic levitation and lasers to high-tech surveillance and digital communications.		
		• By Gordon McComb		
STOCK#	1-4	10-24	25+	
TB3360	19.99	18.99	17.09	

- Order Line — (800) 824-3432 • International — (412) 495-1230 • Fax Orders — (412) 495-7882
- Technical Support — (412) 495-1231 • No Minimum Order — (Orders under \$15 subject to \$5 charge)
- UPS 3 day, Blue, Red, & Fed. Ex. Shipping Available (Call for charges) • PA Res. Add 7 % Sales Tax.
- Open Mon-Fri 9:00 AM - 5:00 PM (EST) • Corporate Accounts / Quantity Discounts Available
- We accept M/C, VISA with no surcharge • Call For FREE Catalog (\$2.00 Outside U.S.)
- We Carry A Complete Line Of Electronic Components • Email - Unielec@aol.com

FREE SHIPPING!!

on pre-paid orders

Write in 78 on Reader Service Card.

Unicorn Electronics
1142 State Route 18
Aliquippa, PA 15001

Nuts & Volts Magazine/January 1997 **85**

MANUALS/SCHEMATICS WANTED

WANTED: COLLINS Radio Company literature. Jim Stitzinger, 805-259-2011, FAX 805-259-3830.

WANTED: MANUAL for Dana 5005/5006 digital multimeter. Phone/fax 505-988-5233.

WANTED: DIAGRAMS for radio frequency heating equipment. Induction, dielectric, plastic, microwave. YOUNGSON'S, INC., 6701 Melrose Ave., Louisville, KY 40216. 502-448-6228.

WANTED: REPCO repeater manuals/schematics dimension repeater model 830-250-05. 464MHz. 501-935-9429 after 5pm CST.

WANT: OPERATING and programming manuals for TI-59 printing calculator and PC-400 printer and blank and programmed cards. Manual for Heath 10-4550 scope with electrical diagram. Weitemann, 3737 Oakwood, Hubertus, WI 53033. 414-628-4321 evenings.

MILITARY COMPONENTS wanted. Capacitors, resistors, diodes, transistors, semiconductors, ICs. Electronic Material Industries, 818-842-5953, FAX: 818-845-3613.

WANTED: DELCO RADIO. Disabling sequence/factory back-up code for disabling theftlock on my Delco radio/CD model no. 16163141. Also schematics for repair of above radio and other Delcos. '58 Mike, PO Box 921, Midlothian, IL 60445. 708-389-2493.

WANTED: TEST EQUIPMENT SERVICE MANUALS! And catalogs, for HP, Tektronix, Fluke, etc. Pepper Systems, 214-353-0257; 214-902-9511 FAX.

MISC. ELECTRONICS FOR SALE

OUT OF BUSINESS SALE: TV/VCR repair shop. Everything must go. Priced at more than 50% off cost. Parts, equipment, SAMS, and brand-specific manuals. Super deals, guaranteed. Pro Tech, POB 4076, Butte, MT 59702. Phone 406-723-8922, Fax 406-723-4411.

E(E)PROM PROGRAMMER: EETools RomMax, 1 gang, 32 pin, \$75 OBO. 815-961-1519.

FIBER OPTIC TRANSMITTER/RECEIVER. BACK IN STOCK! Transmit composite video images from any video source (cameras, VCRs, etc.) over fiber optic cable. SMA connectors. Package includes transmitter, receiver and two AC adapters. Brand new in the box. Only \$49 while supplies last. Credit cards okay. Fax/message: 501-223-9406. Internet: pager@aristotle.net **Surplus City**, Box 23016, Little Rock, AR 72221.

CLOSEOUT ITEMS from BNF: blinking LEDs, stop lite kit blinking, red, yellow, green LEDs, reqs 6VDC, \$3, \$10/4. Ni-cad battery charger/rejuvenator kit, \$7.77, \$20/3. Alarm indicator kit, 2 LEDs, steady, blinking \$2, \$10/6. Letter sign kit 1", letters 40 LEDs, some blinking, \$15, \$40/3. Wind speed indicator kit \$5, \$13/3. Jacob's Ladder, 25K voltage kit \$19, \$55/3. Fan/motor speed control \$3, \$10/4, 2-1/2"ID 1-1/2"D. Solder pot \$3, \$13/3. Voice/sound activated switch mod. \$1. Components by the foot asst'd, \$1/10'. 500 pps., 2 speed sw. motor/lamp control \$1/2, 12/\$5. Mallory Sonalot SC628 \$3.50, \$16/5. Security keylock switch, w/2 keys \$3/2. Cable boxes Oak L30 or Oak G26 \$3, \$10/4, mix or match. All working units. 14550 UART \$1.5. Send SASE for flyer. BNF, Rte. 1S, Peabody, MA 01960. WWW.BNFCOM V508-536-2000, F508-536-7400. Estab. 1964.

ELECTRONIC KITS! VOICE CHANGERS! AND MORE!

PRICES SUBJECT TO CHANGE WITHOUT NOTICE



TOLL FREE ORDER LINE: 1-800-336-7389
FAX LINE: 1-602-731-4748
TECH SUPPORT NUMBER: 1-602-894-0992

XANDI ELECTRONICS, INC.

MANUFACTURER OF HIGH QUALITY KITS

143.775 MHz CRYSTAL CONTROLLED TRANSMITTER KITS



XTR300EZ \$79.95
XTL3000EZ \$99.95
XTL1000EZ \$69.95

XTR300
TRACKING TRANSMITTER KIT
Transmits continuous beep-beep-beep
Ideal for locating lost or stolen items
Range up to 1/2 mile

XTL3000
LONG RANGE TRANSMITTER KIT
Sensitive built in microphone
Range up to 1 mile
Custom frequencies available

XTL1000
TRANSMITTER KIT
Sensitive built in microphone
Range up to 1/2 mile
Custom frequencies available

CRYSTAL TRANSMITTER KITS

- Ultra-miniature surface mount construction.
- E-Z kit approach makes assembly a snap.
- Miniature battery and holder mounted directly to the circuit board.
- Transmit to any scanner type receiver

BUG DETECTOR

XBD500
\$149.95

- Professional quality.
- Not a kit, ready to use.
- Covers 1 to 2,000MHz.
- Uses new Microwave Integrated Circuit amplifier.
- Adjustable sensitivity.
- Audio jack for privacy ear phone.

Any intercepted signal causes an audio tone that increases from a low pitched growl to a high pitched squeal as the signal strength increases.



SOLAR-POWERED FAN HAT. Baseball type hat with solar powered fan. Great for sports fans, golfers, etc. Available in red or blue. \$19 plus \$2.00 shipping. CA residents add 7.75% sales tax. Visa/MC/Disc/Amex OK. H.T. Orr Computer Supplies, 249 Juanita Way, Placentia, CA 92670. 714-528-9822, 1-800-377-2023, FAX 714-993-6216.

SOLAR KING'S many millions of dollars of solar panels in stock. Solar panels: credit card solar panel, 6V, 30mA. Flexible plastic panel add more panels for other voltages & amps. \$4.95 ea., \$45/10, \$210/50, \$400/100. 2" sq. tempered glass solar panel 12 volts 20 watts in a frame with wire leads. Plug-in-play \$195 ea., \$1,650/10, \$8,000/50, \$15,000/100, 12"x12" 15V, 3W, .25A \$19.95, \$170/10, \$800/50, \$1,550/100, 12"x6" 15V @ .125A, 1.5W, \$15.95, \$140/10, \$1,200/100, \$9,000/1000, 6"x6" 7.2V @ .065A, .75W, \$6.95, \$59/10, \$500/100, \$3,990/1000. Wholesale/retail/mail order. Material running low. New solar material coming in all the time. Many other solar items available. Cat'l SASE. BNF, Rte. 1S, Peabody, MA 01960. WWW.BNFCOM V508-536-2000, F508-536-7400. Estab. 1964.

MAGIC WAND: You have to see it to believe it! Display your message in the AIR. This microcontrolled wand, when waved at night or under dim lighting conditions, will DISPLAY A MESSAGE IN THE AIR! USER programmable with built-in graphics. Can be seen up to 100 meters with the proper lighting. Auto message sequence, Mod B2-610. 6 message, 10 char., \$39.95. Manual Mod SIG 2, 2 msg., 8 char., \$24.95. Mod MB 2, 2 msg., 8 char., \$24.95. Ship & Hand \$4.25 ins. incl. B* Inc., PO Box 681546, Orlando, FL 32868-1546. FX 407-290-8555.



SOLAR BATTERY CHARGER. Comes with aluminum frame and cig. lighter attachment. Send \$19.95 to: Quad Energy, PO Box 690073, Houston, TX 77269. PH 281-259-0393 Fax 281-259-7593. http://members.aol.com/quadenergy

PCB Design software. Free unrestricted trial. Schematic, Autorouter, SMDs, Gerber, etc. Why pay more? http://www.bestproto.com/ftp site

88-108 MHz FM RECEIVER

XMR2000
\$29.95

- Worlds smallest FM radio.
- As small as a hearing aid.
- Weighs less than 1/4 oz.
- Digital touch tuning.
- Ideal for use with our 88-108MHz FM transmitters



88-108 MHz FM TRANSMITTER KITS



XST 500EZ \$49.95
XWB 1000EZ \$46.95
XFM 100C \$21.95



XSP 250EZ \$34.95
XTR 100C \$29.95
XTT 100C \$19.95

XST 500 Voice transmitter. Range up to 1 mile. Supersensitive mic. Uses 9 volt battery. Uses surface mount components.

XWB 1000 Voice transmitter. Range up to 1/2 mile. Includes mic and battery on circuit board. Uses surface mount components.

XFM 100 Voice transmitter. Range up to 1 mile. 9 v battery and leaded components.

XSP 250 Super-miniature telephone transmitter. Range 1/4 mile. Powered by phone line. Uses surface mount component.

XTR 100 Tracking transmitter. Range up to 1 mile. Uses 9 volt battery. Transmits a BEEP - BEEP - BEEP tone

XTT 100 Telephone transmitter. Range up to 1 mile. Uses 9 volt battery.

PHONE VOICE CHANGER

16 levels of digital voice changing. Sound tougher, older or younger, female or male. Powered by 4 AA batteries. (Batteries not included).

Works with regular or multi-line phones. Connects between handset and phone. Note will not work with cordless or handset type telephones.



T-2001
Assembled
\$69.95



ULTRALIFE
XLB-9 \$8.95
9V LITHIUM BATTERY

Worlds most powerful 9V battery! Twice the life of alkaline batteries.

XLB-3 \$3.95
3V CAMERA BATTERY

Small 3V Lithium battery. For use with XTL3000, XTL1000, XTR300, and XWB1000.

PROJECT BOX
\$14.95

Ideal project box to give your kits that professional look. Available custom drilled for the following kits: XFS108, XPS1000, XLC900, and XVA250.

XANDI ADVANCED HOBBY KITS

 XPS 1000C \$55.95 TELEPHONE SNOOP KIT • Dial home from anywhere and hear inside your home. • Touch Tone coded for secure operation. • Stop burglars and intruders. • Reliable 24 hour protection.	 XLC 900C \$49.95 SCANNER CONVERTER KIT (800-950MHz) • Uninterrupted coverage of the 800 to 950 MHz band. • Works with any 400-550MHz scanner. • Gain: 6 dB typical. • Noise figure: 3 dB typical.	 XVA 250C \$49.95 VOICE-STRESS ANALYZER KIT • See at a glance if your lying to! • Subject need not be present. Works with voices from recordings, TV or radio. • Has built-in microphone. • Easy to use LED display output.	 XFS 108C \$39.95 88-108 MHz FM STEREO TRANSMITTER KIT • Separate level control for both left and right channels. • Output level circuit with test points for quick and easy tuning. • Transmit from any stereo audio source to most any FM stereo receiver.
---	---	--	--

Serving the public since 1981
XANDI ELECTRONICS, INC.
1270 E Broadway Rd. # 113
Tempe AZ 85282

WE ACCEPT CHECK, VISA, MC, MO, COD
SHIPPING & HANDLING EXTRA

Master Card
VISA
REFUNDABLE ON FIRST ORDER

SEND \$2.00 FOR COMPLETE CATALOG

SEND MAIL ORDERS TO:
XANDI ELECTRONICS
BOX 25647
TEMPE, AZ 85285-5647

The dealers listed below carry the latest issue of Nuts & Volts, for your convenience.

ALABAMA

Little Professor Book Center
2717 S. 18th St.
Birmingham 35209
RT Systems Amateur Radio Supply
8207 Stephanie Drive
Huntsville 35802

ARIZONA

Batteries, Batteries
3415 W. Glendale Ave. #4
Phoenix 85051

1829 E. Southern Ave.
Tempe 85282

6245 E. Bell Road
Scottsdale 85254

Tower Records

3 E. 9th St.
Tempe 85281

CALIFORNIA

Abletronics

9155 Archibald Ave. Unit E
Cucamonga 91730

Advanced Computer Products, Inc.

1310 "B" E. Edinger Ave.
Santa Ana 92705

All Electronics

905 S. Vermont Ave.
Los Angeles 90006

14928 Oxnard St.
Van Nuys 91411

Allen's To Go

13461 Hwy. 88
Lockeford 95237

Alltronics

2300-D Zanker Road
San Jose 95131

Black Feather Electronics

3004 E. 7th St.
Long Beach 90814

Centerfold International

716 N. Fairfax Ave.
Los Angeles 90048

Computing Technology

251 Balsam St.
Ridgecrest 93555

Darrell Electronics

4910 Santa Anita Ave.
El Monte 91731

DAV TV

212A Miller Ave.
South San Francisco 94080

Del Amo Books & News

3758 Sepulveda Blvd.
Torrance 90505

Digitcity.Net

4549 Quail Lakes Dr.
Stockton 95207

Ford Electronics

8431 Commonwealth Ave.
Buena Park 90621

Gentek Electronics

11652 Monarch St.
Garden Grove 92841

Harding Way News

113 W. Harding Way
Stockton 95204

Hi-Fi Doctor

1814 E. Ball Road
Anaheim 92805

HSC Electronic Supply

4837 Amber Lane
Sacramento 95841

3500 Ryder St.
Santa Clara 95051

6819 Redwood Drive
Cotati 94931

JK Electronics

6395 Westminster Ave.
Westminster 92683

Laurel Park News

4346 Laurel Canyon Blvd.
Studio City 91604

Olive Drab Enterprise

12819 Loma Rica Dr. #153
Grass Valley 95945

Op Amp Technical Books

1033 N. Sycamore Ave.
Los Angeles 90038

Pace Electronics

369 Hampshire Road
Thousand Oaks 91361

Panorama Electronics

8737 Van Nuys Blvd.
Panorama City 91402

Quantum Enterprises

1566 Simpson Way
Escondido 92029

Sav-On Electronics

13225 Harbor Blvd.
Garden Grove 92643

Survival Books & Equipment

11106 Magnolia Blvd.
North Hollywood 91601

The Radio Place

5675-A Power Inn Road
Sacramento 95824

Tower Books

1280 E. Willow Pass Road
Concord 94520

630 San Antonio Road
Mountain View 94040

1600 Broadway
Sacramento 95818

2538 Watt Ave.
Sacramento 95812

2727 El Camino Real
San Mateo 94403

Tower Magazines
2605 Del Monte St.
West Sacramento 95691

Tower Records/Video
220 N. Beach Blvd.
Anaheim 92801

212 F St.
Davis 95616

5703 Christie Ave.
Emeryville 94608

5611 Blackstone
Fresno 93710

2052 Redwood Hwy
Greenbrae 94904

6310 E. Pacific Coast Hwy.
Long Beach 90803

2280 Market St.
San Francisco 94114

3205 20th Ave.
San Francisco 94132

2525 Jones St.
San Francisco 94133

871 Blossom Hill Road
San Jose 95123

14570 Ventura Blvd.
Sherman Oaks 91403

Valencia Newsstand
23164 W. Valencia Blvd.
Valencia 91355

Video Electronics
3829 University Ave.
San Diego 92105

CANADA
Corn-West Radio Systems Ltd.
48 E. 69th Ave.
Vancouver, BC V5X 4K6

Lection Enterprise
120-11 Ave. N
Creston, BC V0B 1G0

Muir Communications Ltd.
3214 Douglas St.
Victoria, BC V8Z 3K6

COLOMBIA
Roboti-K
Carrera 38 No. 10-60.
Local 258, Bogota

COLORADO
Fistell's Micro Electronics
7023 E. Colfax Ave.
Denver 80220

International Tesla Society
2220 E. Bijou St.
Colorado Springs 80909

TH Electronics
216 Commerce Dr., Unit 2
Fort Collins 80524

Tower Records/Video
2500 E. 1st Ave.
Denver 80206

Western Test Systems
530 Compton #C
Broomfield 80020

CONNECTICUT
Archway News
64 Bank St.
New Milford 06776

Derric Electronics
1660 Whitney Ave.
Hamden 06517

DISTRICT OF COLUMBIA
Tower Records
2000 Pennsylvania Ave.
Washington 20006

FLORIDA

Clarks Out of Town News
303 S. Andrews Ave.
Fort Lauderdale 33301

Mike's Electronic Distributing Co.

1001 NW 52nd St.
Fort Lauderdale 33309

Skycraft Parts & Surplus, Inc.

2245 W. Fairbanks
Winter Park 32789

Sunny At Sunset

2260 Sunset Strip
Sunrise 33322

GEORGIA

Tower Records
3400 Around Lenox Drive
Atlanta 30326

HAWAII

Tower Records
4211 Waiialae Ave.
Honolulu 96816

611 Keaumoku
Honolulu 96814

IDAH0

Hi-Tech Surplus
605 E. 44th St.
Boise 83714

The Current Source
5159 Glenwood
Boise 83714

ILLINOIS

City Newsstand
4018 N. Cicero
Chicago 60641

Pick's Electronics
Lewis Park Mall
Carbondale 62901

Tower Records/Video/Books
383 W. Army Trail Road
Bloomington 60108

2301 N. Clark St. #200
Chicago 60614

1209 E. Golf Road
Schaumburg 60173

INDIANA

Harbortown Sales
108 Park 32 West Dr., #D
Noblesville 46060

KANSAS

Lloyd's Radio & Electronic, Inc.
220 W. Harry St.
Wichita 67213

LOUISIANA
Gameforce Central HQ
13623 Hooper Rd. #CA
Baton Rouge 70818

Lakeside News
3323 Severn Ave.
Metairie 70002

Tower Records
408 N. Peter St.
New Orleans 70130

MARYLAND
Keep In Touch Communications
700 Mace Ave., Store B
Baltimore 21221

Silicon Valley Electronics
2014-A Industrial Drive
Annapolis 21401

Tower Records/Video
2566 Solomons Island Road
Annapolis 21401

1601 Rockville Pike #210
Rockville 20852

MASSACHUSETTS
Tower Records #172
360 Newbury St.
Boston 02115

MICHIGAN
Family Electronics
111 E. Superior St.
Alma 48801

Little Professors Book Center
22174 Michigan Ave.
Dearborn 48124

MW Electronics
229 E. Michigan Ave.
Paw Paw 49079

Purchase Radio Supply, Inc.
327 E. Hoover Ave.
Ann Arbor 48104

Tower Records
1214 S. University Ave.
Ann Arbor 48104

MINNESOTA

Radio City, Inc.
2633 County Road 1
Mounds View 55112

MISSOURI

Accurate Instruments
11201 E. 24 Highway
Independence 64054

Electronics Exchange
8644 St. Charles Rock Road
St. Louis 63114

Stewart & Associates
204 Sonderen St.
O'Fallon 63366

NEVADA
Amateur Electronic Supply
1072 N. Rancho Drive
Las Vegas 89106

Less Buster's Electronics
2930 N. Las Vegas Blvd. VSTG-22
North Las Vegas 89030

Radio World
1656 Nevada Hwy
Boulder City 89005

Tower Records/Video
4580 W. Sahara Ave.
Las Vegas 89102

6450 South Virginia
Reno 89511

NEW JERSEY
JR Tech Systems
1309 Highway 71
Belmar 07719

Tower Records
809 Route 17 South
Paramus 07652

NEW YORK
All Phase Video Security, Inc.
70 Cain Drive
Brentwood 11717

Ham Central
3 Neptune Road
Poughkeepsie 12601

Hirsch Sales Corporation
219 California Drive
Williamsville 14221

Tower Records/Video
105 Old Country Road
Carle Place 11514

350-370 Route 110
Huntington 11746

1961 Broadway
New York 10023

383 Lafayette St.
New York 10003

OHIO
Compustuff
2751 Medina Road
Medina 44258

Dayton Software
3903 Wilmington Pike
Kettering 45429

Digital One
7603 Mentor Ave.
Mentor 44060

Footsteps
4925 Jackman Rd. Store #58
Toledo 43613

Hosfelt Electronics, Inc.
2700 Sunset Blvd.
Steubenville 43952

Keyways, Inc.
611 S. Main St.
Miamisburg 45342

Leo's Book Shop
330 N. Superior St.
Toledo 43604

Magazines & More
26880 Brookpark Rd. Ext.
North Olmsted 44070

Powermaxx, Inc.
1587 U.S. Route 68 North
Xenia 45385

OREGON
News & Smokes
2295 W. Main St.
Medford 97501

News & Smokes #8
259-C Barnett Road
Medford 97501

Norvac Electronics
7940 SW Nimbus Ave. Bldg. 8
Beaverton 97005

960 Conger
Eugene 97402

1545 N. Commercial NE
Salem 97303

Powell's Technical Bookstore

33 NW Park
Portland 97209

Tower Books

1307 NE 102nd Ave.
Portland 97220

PENNSYLVANIA

Lehman Scientific
2997-F Cape Horn Road
Red Lion 17356

Penn Electronics
2310 A Walnut St.
Harrisburg 17103

Surplus Al
RR 1 Box 337
Hunlock Creek 18621

Tower Books
425 South St.
Philadelphia 19147

Tower Records
340 W. Dekalb Pike
King of Prussia 19406

SOUTH CAROLINA
555 Electronics
5646 Farrow Road
Columbia 29203

TENNESSEE
Tower Books
204 West End Ave.
Nashville 37203

TEXAS
Electronic Parts Outlet
3753-B Fondren Rd.
Houston 77063

Tanner Electronics
1301 W. Bellline #105
Carrollton 75006

The Communication Source
2713 Galleria Drive
Arlington 76011

Tower Records
2403 Guadalupe
Austin 78705

UTAH
Omega Electronics
1500 North 150 West
Provo 84604

VIRGINIA
Electronic Equipment Bank
323 Mill Street NE
Vienna 22180

Riley's Distributing
1045 Edom Road
Harrisonburg 22801

Satellite Headquarters
7920 Timberlake Road
Lynchburg 24502

Tower Records/Video/Books
4110 W. Ox Road #12124
Fairfax 22033

1601 Willow Lawn Drive
Richmond 23230

8389 E. Leesburg Pike
Vienna 22182

VA Ham Radio Supply, Inc.
2208 Childress Rd.
Christiansburg 24073

WASHINGTON
A-B-C Communications, Inc.
17541 15th Avenue NE
Seattle 98155

Amateur Radio Supply Co.
5963 Corson Ave. S. #140
Seattle 98108

Superfronix
18650 68th Avenue South
Kent 98032

Tower Books
10635 NE 8th St.
Bellevue 98004

20 Mercer St.
Seattle 98109

2501 S. 38th St.
Tacoma 98409

WISCONSIN
Amateur Electronic Supply, Inc.
5710 W. Good Hope Road
Milwaukee 53223


Little Professor Book Center
307 N. Bridge St.
Chippewa Falls 54729

News & Hobby Center
4758 Packard Ave.
Cudahy 53110



Aircraft type Nickel Cadmium Batteries. Vented construction for fast charging. Used surplus from commercial and military aviation, communications. Each cell is 1.25 Volts. Tested and guaranteed.

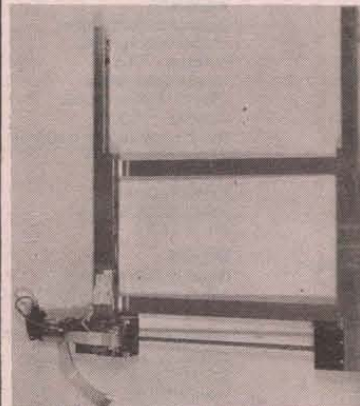40 Amp-Hr.....\$8.00 2 Lbs
23 Amp Hr.....\$5.00 1 Lb
10 Amp-Hr.....\$4.00 Postpaid
5 Amp-Hr.....\$2.50 Postpaid




Linear Motion Mechanism. This consists of a pair of timing belts that move a cross slide. It is driven by a Maxon DC gearhead motor with a Hewlett Packard encoder. 7/8" Diam. Various gear ratios.....\$39.00 PP



Sealed Nickel Cadmium Rechargeable Battery Packs. These are new, but slightly outdated. Tested and guaranteed full capacity.

Military Starlight pack, 4.8 Volts
2.8 Amp-Hr (Shown).....\$5.00 PP
DEC pack 10AA cells....\$4.00 PP
Quantum pack 4 cells.\$2.50 PP

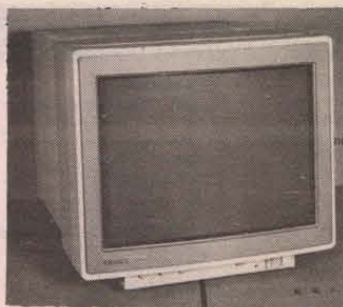**IMPOSSIBLE?
SONY
TRINITRON
MONITOR
17"
\$175.00
RESOLUTION
TO 1280 X 1024**



**REFRESH
TO 75 HZ
(NOT
MULTISYNC)
USED-LIKE NEW
.25 DOT PITCH**

This is our most popular item. Originally used on Hewlett Packard workstations, it carries HP number 98789A. Brought back from their Singapore design center, they saw little use. We have sold over 500 of them. Available in several different configurations. **For Macintosh, with cables, fine tuned for Mac...\$225.00.** Because this is not a Multisync monitor, we recommend that for **IBM compatibles** the monitor be used with the **Photon Torpedo graphics card.** We sell the combination for **\$375.00** including the appropriate cable. Experimenters can use the basic \$175.00 Monitor on the IBM at one resolution only, by ordering a cable and sync adapter for **\$50.00.** Shipping weight is 52 Lbs.

I also have Trinitron 20" monitors at \$500.00. Similiar specs.



Maxon DC Motor with gearhead and Hewlett Packard encoder. 7/8" Diam. Various gear ratios.....\$39.00 PP



Light table uses grid type fluorescent tube. Requires Neon sign transformer to operate. **Closeout ...\$30 PP**
Neon sign transformer 15KV.....\$30.00 15 Lbs



Size 12" x 18"



Dear Readers,

Ordering from V&M Surplus is easy. No minimum order, no hidden charges, most items postpaid. Your satisfaction guaranteed, or your money back. I am an avid collector, right now I am looking for the following items: Norden Bombsight, M209 Converter (cryptomachine), K9 Ball Turret Sight. Cash or trade. *Franklin D. Finch*

**Vision and Motion Surplus
222 Pleasant Street
Marlboro, MA 01752**

1-800-471-0747, 1-508-485-3561

Fascinating Corner Cube Prism Assemblies

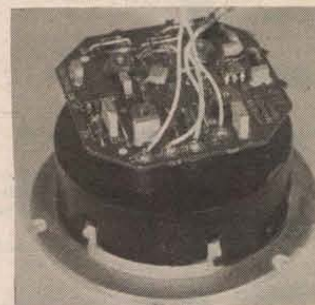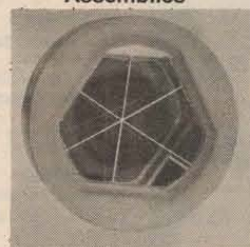

One of the most fascinating optical components. The corner cube (retroreflector) directs light precisely back to its source. Used by surveyors for distance measurements, planted on the moon by the Apollo astronauts, these beautiful gem-like prisms are usually priced in the \$200-\$300 price category. Two types are available:

1. 60mm diameter 5 sec accuracy, surveyor type, mounted with bolt hole in back. 20mm offset. **\$49.00 Postpaid.**
2. Military assembly with corner truncated and electronic unit with IR filter mounted. If anyone knows what these were used for, please let me know. **\$49.00 Postpaid**



DC Current Transformer
Measure currents of up to 200 Amperes with no drop.

Nemec LTA 50P. Measures to 50A at 0.25% accuracy. Wire goes through toroid....**\$10.00 Postpaid.**



Sony XC37 Scientific grade Monochrome camera. 2/3 inch equivalent. With quality Computar 25mm lens. No weak or missing pixels. 12VDC. Free extension tube set. **Price reduced \$229.00 Postpaid**

Calcomp 1044 "E" size plotter. Excellent condition with manual. Sheet or roll paper.....**\$600.00**

Don Lancaster's

RESOURCE BIN

number sixty

Finding answers on the web.

Our usual reminder here that the *Resource Bin* is now a two-way column. You can get tech help, consultant referrals, and off-the-wall networking on nearly any electronic, *tinaja* questing, personal publishing, money machine, or computer topic by calling me at 520-428-4073 weekdays 8-5 Mountain Standard Time.

I'm now in the process of setting up my new *Guru's Lair* web site you will find at (where else?) www.tinaja.com

This is the place you go for instant tech answers. Among the many files in our library, you will find complete reprint sets for all of the *Resource Bin* and other columns.

You will get the best results if you have both *Netscape Gold* and *Acrobat Reader 3.0*. You download these from www.netscape.com or www.adobe.com

Getting Web Answers

This month, I was going to tell you about a few of my favorite web sites. But I've had so many calls and letters asking how to do web research, that I thought we'd first look into how you use the web to find useful info.

Nailing the goodies.

For instance, I just got a call from someone beginning a major university study on exactly how cellular phones interfere with hearing aides. Entering the key words of *cellular phone hearing aide interference* into *Alta Vista* quickly led to the definitive Swedish study on this subject.

Somebody else wanted to know all about formaldehyde litigation. This time *Deja News* gave us hundreds of useful results. A few of which end up hilarious. If you didn't happen to be the one in the barrel.

Or, in this case, the jar.

First off, note that the really superb stuff may not yet be net available. For somebody somehow has to pay for all top quality research.

Your "best" info traditionally comes from premium data bases. Each field has its name brand biggie or two. The doctors use *Medline*.

Lawyers use *Lexus* or *Nexus*. Engineers often will start off by using *INSPEC*. Then may step over to *MathSci* or *Compendex*.

Librarians prefer *Bowker*, *Oxbridge*, or *Gale*. Accessing *Ulrich's Periodicals Dictionary*, *Books in Print*, that *Science Citations Index*, or else the *Encyclopedia of Associations*.

These premium data bases typically had to get accessed through fee-based online services, such as *Dialog* That do charge as much as \$2.00 per minute. But often end up by far your fastest and cheapest way to get crucial information in a big hurry.

A fine pair of offline traditional info sources are *UMI* and *The Information Store*. These are your places to go for hard copy reprints of nearly anything. But you'll have to know the exact title, author, journal, and page.

Thanks to Adobe's new *Acrobat 3.0*, instant reprints that are faster,

NEXT TIME: Don tells us all about his favorite world wide web sites.

better, and cheaper are quickly being offered online by the thousands from many hundreds of sites. Freebie *Acrobat 3.0* readers at www.adobe.com

More webmasters are discovering that they can get zillions of hits by up-front paying for and then distributing premium research. Material that is not available elsewhere on the net. As an example, free *Medline* access can now be found on a dozen web sites.

Even if they seem weaker, new and free services sometimes may cut into the traditional territory of all the one-time big players. For instance, *Books in Print* is not yet on the net. At least I have yet to find it. But *Amazon Books* has a free book search service which sometimes is "almost as good."

Let's look at a few key tools

needed to get web answers ...

A Master Resource

There are several hundred sites that specialize in providing search engines and related web access tools. One of the best *meta* sites that I've found is *lookup.com* who have gathered up 74 of the best search engines all together in one place, at one time.

Ifen the right one don't git ya, the left one will.

I have got a link for this site on my *Guru's Lair* at www.tinaja.com — Links to other mentioned sites also show up here. Additional answer getting tools will often be found on the *Guru's Lair* *webmastering* library shelf.

The Yahoo Dice

The highest profile search engine is *Yahoo*, but I don't care for them. First, because it is way too painful to enter your own site into their registry. And second, because I'll usually get faster and better results elsewhere.

But one handy feature of *Yahoo* is their *dice icon* which will warp you somewhere in cyberspace, totally at random. I like to hit their dice at least 30 times a day. First, to get a full and accurate picture of what the net is all about. Second, to pin down sites I wouldn't have otherwise found.

The dice also gets you started on the *avalanche effect*. For most, any site will provide a *hot links* button, one which leads you into dozens or hundreds of new sites of potential use to you, and those sites direct you to yet thousands more. By linking the links, you should be able to waltz around cyberspace with a vengeance. Theoretically, any site is less than a dozen mouse clicks away from a random selection.

Incidentally, these *Yahoo dice* also tell you a lot about the "severity" of all the porn on the net. I have found that something around one dice hit in 175, yields content someone might find offensive. Around one hit in 1374 is a real porno site. And fewer than one hit in 19,763 is a primo porno site.

At least that's the number of times so far that I have hit the dice without being able to find one. Let me know if you have any better luck.

A faster accessing mirror for these *Yahoo dice* is on www.tinaja.com

Whenever it comes to serious web searching, instead of picking *Yahoo*, I very much prefer ...

Alta Vista

You'll find a dozen or more

new from
DON LANCASTER

ACTIVE FILTER COOKBOOK

The sixteenth (!) printing of Don's bible on analog op-amp lowpass, bandpass, and highpass active filters. De-mystified instant designs. \$28.50

CMOS AND TTL COOKBOOKS

Millions of copies in print worldwide. THE two books for digital integrated circuit fundamentals. About as hands-on as you can get. \$28.50 each.

INCREDIBLE SECRET MONEY MACHINE II

Updated 2nd edition of Don's classic on setting up your own technical or craft venture. \$18.50

LANCASTER CLASSICS LIBRARY

Don's best early stuff at a bargain price. Includes the CMOS Cookbook, The TTL Cookbook, Active Filter Cookbook, PostScript video, Case Against Patents, Incredible Secret Money Machine II, and Hardware Hacker II reprints. \$119.50

LOTS OF OTHER GOODIES

Ask the Guru I or II or III	\$24.50
Hardware Hacker II, III or IV	\$24.50
Micro Cookbook I	\$19.50
PostScript Beginner Stuff	\$29.50
PostScript Show and Tell	\$29.50
Intro to PostScript Video	\$29.50
PostScript Reference II	\$34.50
PostScript Tutorial/Cookbook	\$22.50
PostScript by Example	\$32.50
Understanding PS Programming	\$29.50
PostScript: A Visual Approach	\$22.50
PostScript Program Design	\$24.50
Thinking in PostScript	\$22.50
LaserWriter Reference	\$19.50
Type 1 Font Format	\$16.50
Acrobat Reference	\$24.50
Whole works (all PostScript)	\$380.00
Synergetics Surplus Catalog	FREE
Technical Insider Secrets	FREE

POSTSCRIPT SECRETS

A Book/Disk combination crammed full of free fonts, insider resources, utilities, publications, workarounds, fontgrabbing, more. For most any PostScript printer. Mac or PC format. \$29.50

BOOK-ON-DEMAND PUB KIT

Ongoing details on Book-on-demand publishing, a new method of producing books only when and as ordered. Reprints, sources, samples. \$39.50

THE CASE AGAINST PATENTS

For most individuals, patents are virtually certain to result in a net loss of sanity, energy, time, and money. This reprint set shows you Don's tested and proven real-world alternatives. 28.50

BLATANT OPPORTUNIST I

The reprints from all Don's Midnight Engineering columns. Includes a broad range of real world, proven coverage on small scale technical startup ventures. Stuff you can use right now. \$24.50

RESOURCE BIN I

A complete collection of all Don's Nuts & Volts columns to date, including a new index and his master names and numbers list. \$24.50

FREE SAMPLES

Check Don's *Guru's Lair* at <http://www.tinaja.com> for interactive catalogs and online samples of Don's unique products. Searchable reprints and reference resources, too. Tech help, hot links to cool sites, consultants. email: don@tinaja.com

FREE US VOICE HELPLINE VISA/MC

SYNERGETICS
Box 809-NV
Thatcher, AZ 85552
(520) 428-4073

Write in 44 on Reader Service Card.

RESOURCE BIN

SOME TRADITIONAL RESEARCH TOOLS

Adobe Systems P.O. Box 7900 Mountain View CA 94039 (800) 833-6687	Compendex 1 Castle Point Terrace Hoboken NJ 07030 (201) 216-8500	Information Store 500 Sansom St #400 San Francisco CA 94111 (415) 433-5500	Medline 8600 Rockville Pike Bethesda MD 20894 (800) 638-8480	Soc Am Scientists 1549 El Prado San Diego CA 92101 (800) 873-8767
Amazon Books Box 80387 Seattle WA 98108 (800) 201-7575	Dialog Info Svcs 3460 Hillview Ave Palo Alto CA 94304 (415) 858-2700	Inspec/IEEE 445 Hoes Ln Piscataway NJ 08855 (201) 981-0060	Nomadness Report P.O. Box 2185 El Segundo CA 90245 (310) 322-1655	Synergetics Box 809 Thatcher AZ 85552 (520) 428-4073
Books in Print 121 Chantlon Rd New Providence NJ 07974 (908) 464-6800	Encycl of Assns 835 Penobscot Bldg Detroit MI 48226 (313) 961-2242	Lexus/Nexus 9443 Springboro Pike Dayton OH 45401 (513) 865-6800	Oxbridge 150 5th Ave #202 New York NY 10011 (212) 741-0231	Ulrich's Dictionary 121 Chantlon Rd New Providence NJ 07974 (908) 771-7714
RR Bowker 121 Chantlon Rd New Providence NJ 07974 (908) 464-6800	Gale Research 835 Penobscot Bldg Detroit MI 48226 (313) 961-2242	MathSci Box 6248 Providence RI 02940 (401) 455-4000	Science Citation Index 3501 Market St Philadelphia PA 19104 (215) 386-0100	UMI 300 N Zeeb Rd Ann Arbor MI 48106 (800) 521-3044

major Internet general search engines. With names like *Yahoo*, *Alta Vista*, *Matilda*, *Webcrawler*, *Magellan*, *Disinformation*, *Lycos*, *Excite*, or *Inktomi*.

Many of these go to the trouble of having an entire warehouse full of linked PCs that maintain a *complete* model of some 100 million web pages. These models create a back index of which words appear where.

When combined with *relevance* stats of how often your word appears how close to your other selected words, a quite fast and ultra powerful search ability usually results.

To use any search engine, you enter one or more keywords. These days, a keyword can be any word or number that appears in the document, not just a selection from a restricted list. The engine chomps on through everything it knows about the net and finds those pages with the highest number of hits on the most keywords.

You do have to carefully choose the keywords. Select too loose, and you'll find thousands of false hits. Too tight, and you will get nothing. Sometimes you have to find one useful hit to spot those real words that the authors will use for your target subject.

I guess I like *Alta Vista* the best. At least it is usually my starting point on typical searches. Deeply buried in my *www.tinaja.com* web site is a story on the *Mount Graham Aerial Tramway*, an utterly amazing engineering feat from the 1920s. I'll use this tram query string to find out how good an Internet search engine really is.

Alta Vista nails it in five seconds flat as numero uno on their hit list.

Whois and WhoWhere

How do you find out if a company has a web site? Or if an author has an E-Mail address? Several specialized net services ease these tasks.

Two examples are located at *Whois* and *WhoWhere*.

Whois is a service from the Internet registration service you should find at *www.internic.org*. —

You can use *Whois* to find out whether a domain name is in use or to find the name and address of an existing domain name or to pin down the location of a company.

WhoWhere at *www.whowhere.com* is more people oriented. You enter their name in any order and back comes a list of exact matches, near misses, and at least one or more "pretty nigh, but not plumb" wild guesses.

Needless to say, if you are active on the net and want to be reached, it is essential that you go out of your way to make sure you get listed.

You'll also find an *Internet Address Finder* at *www.iaf.net* — Plus the *Domain Name Search* at *alfredo.wustl.edu/htbindomain_search?* — But, at least on all my tests, these two sites could not find a pig in a dishpan.

News Groups

A *newsgroup* is simply a collection of people who publically E-Mail each other via the Usenet. Newsgroups are places where you can post questions and get answers.

Typically, a newsgroup will have a single, tightly targeted interest. Such as the owners of 1987 tan Volkswagen 4WD non-Westly Synchro Vanagons having double diff locks but no Saint Bernards. You will find many tens of thousands of newsgroups.

Most newsgroups are *moderated*. A moderator is a person in charge who filters all the raw input into coherent text. Some moderators edit heavily; anything goes with others.

A moderator will often maintain a *FAQ*, or *Frequently Asked Questions* file or library. This allows somebody new to the group to pick up the basics and not have to ask a lot of very tedious and repetitive questions.

As you might guess, the quality of newsgroups varies all over the lot. A few promptly offer current and expert opinion. Sadly, others are plagued by totally irrational and juvenile flaming egomaniac newbies

who flat out do not have the faintest clue. And, in the process of proving so, drive those real experts away.

Always remember that *NET stands for Not Entirely True*. Do not ever use newsgroup info as your sole source! Anybody posting to a newsgroup has an axe to grind. And a hidden agenda that almost always is not in your best interests. There is no peer review, nor any competence filtering.

Always be sure to independently check all newsgroup content! Newsgroups are intended to give you *possible* or even *probable* answers.

But *never* act on them without an independent check. Especially if the content is medical, financial, or legal in nature. Always verify.

Most newsgroups are free and open to anybody. Others require passwords and might involve charges. Typically, you E-Mail a usegroup using the word *subscribe* in the message. Or *subscribe digest* to get the summary transcript, rather than zillions of shorter ones. To get off a group, you'll typically put the word *unsubscribe* in your E-Mail. The main site header message often gives you specific details.

Let's look at three examples. Shawn Carlson's *Society of Amateur Scientists* has both a web site at *www.sas.org* and a newsgroup. To subscribe, E-Mail the word *subscribe* to *postmaster@sas.org*. — To unsubscribe, E-Mail the single word *unsubscribe*. This is one example of an *automated list robot*. To ask a question or provide an answer, you E-Mail your contribution to *talk@sas.org*.

Steve Roberts is big on nomadics. His web site is *www.microship.com* — You subscribe to his newsletter by sending E-Mail to *wordy@qualcomm.com* — This is one instance of an unautomated, or a *personally handled request*.

Links to both of these sites can be found on *www.tinaja.com*

And to access the Vanagan Synchro stuff, you'll E-Mail a *subscribe vanagon firstname lastname* message directly to

LISTSERV@lenti.med.umn.edu

Deja News and Friends

Exactly how do you find out which newsgroups are for you? Two useful resources are *Deja News* and *PAML*. The latter is an acronym that is short for *Public Accessible Mailing Lists*.

Which is a directory of some 12,000 newsgroups. Arranged alphabetically and by subject.

Once selected, specific details show up on who hosts the newsletters and how to subscribe. There's only a few hundred subjects, instead of a good in-depth search engine. For instance, you can quickly find *automotive*, but not search on *Synchro*.

Instead, your general power search tool is *Deja News*. You simply enter a search string, and *Deja News* returns *every* newsgroup message where all of your words appear. Either as a quick search on current contents or for an in-depth scan of older content.

Let's look at another example. I got this call the other day from a person who was looking for a schematic on an older PowerMate power supply. A call to PowerMate revealed that they flushed all their old docs.

Uh, this one is a rather specialized request. PowerMate products weren't all that popular. You could probably trace out the supply in a few minutes or fix it with a scope.

If you get on *Deja News* and look for *PowerMate*, you should get several hundred *false hits* on NEC computers, on strange vacuum cleaners, and even on Coleman generators. Oops.

All of my usual ploys of tightening the search or patiently mining their dregs for a gem or two did not seem to work this time.

So, you can use the *indirect method* instead. Get on *Deja News* and search for *Power Supply Schematic Wanted*.

Not surprisingly, nobody seems to have already asked about PowerMate products. You will get around 15 current hits and maybe a hundred or so on the backlist.

Of these, your most promising candidate sites are *sci.electronics.basics*, *sci.electronics.repair*, *sci.electronics.misc*, *sci.electronics.design*, and possibly over at *misc.industry.electronics*.

Your next step is to check out these groups for activity and relevance. You then post your question to the best of them. Chances are you should score an answer in a day or two. Provided, of course, that you post a concise and answerable question.

You do have to be careful what you enter as keywords. Too tight

and you get no hits. Enter too loose and you'll get overwhelmed. You are also sure to find a lot of false hits. I was recently searching on *vacuum forming* and kept getting all sorts of returns on *fruitcake*. Which, I guess, is something that I've always suspected.

Putting my own name through Deja News also led to bunches of false hits. Apparently because the word "don't" is treated the same as "don."

Deja News also has a handy feature which can tell you exactly where else any particular individual happens to be posting messages. This can be real useful to evaluate the credibility of your new source and to lead you on to other interesting sites.

The Deja News web site is up at xp9.dejanewsdnquery.xpPAML is found at www.NeoSoft.cominternet-pamlindex-index.html

This Month's Contests

Let's have us a pair of contests this month. Tell me about a web searching or web access or web answer finding resource that I don't yet know about.

Or else finish this sentence for me: "You are spending too much time on the net if ..." For instance: "You are spending too much time on the net if the Yahoo dice keep repeating."

There will be a largish pile of my new *Incredible Secret Money Machine II* books going to the dozen or so better entries, plus an all-expense-paid (FOB Thatcher, AZ) *tinaja* quest for two that will go to the very best of all.

Send all your written entries to me here at Synergetics, rather than to Nuts & Volts editorial. NV

Microcomputer pioneer and guru Don Lancaster is the author of 33 books and countless tech articles. Don maintains his no-charge US tech helpline found at (520) 428-4073, besides offering all of his own books, reprints, and consulting services. Don also has two free catalogs full of his resource secrets waiting for you. Your best calling times are 8-5 on week-days, Mountain Standard Time.

Don is in the process of setting up his Guru's Lair at <http://www.tinaja.com>

Full reprints and preprints of all Don's columns and ongoing tech support appear here. You can reach Don at Synergetics, Box 809, Thatcher, AZ 85552. Or send any messages to his US Internet address of don@tinaja.com

MISC. ELECTRONICS FOR SALE cont.

ELECTRONIC PARTS SALE: Carbide PC drills \$0.30 ea. Mallory #FP433.3, 450V, Quad Lytics \$3.75 ea. Mot. #MTP50N05E, 50A MOS-FETs (1-9) \$1.55 ea., (10+) \$1.25 ea. Mot. #MJ15024 & MJ15025 transistors (1-9) \$1.75 ea., (10+) \$1.25 ea. Gold plated dual 5 way binding posts (1-4) \$2.25 ea., (5+) \$1.85 ea. 25A/400V bridge rectifiers (1-4) \$1.75 ea., (5+) \$1.25 ea. Many other elec. parts. Call/send for free flyer. Hoffman Industries, 853 Dundee Ave., Elgin, IL 60120. Ph: 847-622-8201, Fax: 847-622-8202 (Visa, MC, Discover, Amex).

TUBES: RADIO and television 70 year collection, from 4 pins to compactors, new and used. Will test all first. Name your wants and what you want to pay. 718-531-5676.



JAN 12AT7WC, Phillips ECG, brand new government excess. 100 pcs./carton; \$195/carton. Flame Enterprises, 20945 Osborne Street, Canoga Park, CA 91304. Ph: 1-800-854-2255; Fax: 818-700-9168; E-Mail: info@flamecorp.com We accept Visa, M/C, Amex.

ELECTRONIC ASSEMBLY MACHINERY. We buy and sell assembly machinery including solder machines and board cleaners, insertion machines and lead formers. Petlock Inc., Rialto, CA. 909-877-8900, FAX 909-877-8902.



GENERAL SCANNING G120 scanners for sale \$350 ea. Very little use. New 35mW red HeNe \$1,800 w/supply. Laser Max card and software \$900. Beam Fan effect \$595. Data Systems, Box 80586, Austin, TX 78758. www.datas.com/laser

NEW: PHANTOM, POLICE LASER/RADAR JAMMER & DETECTOR: No more tickets or manufacturer pays them! Guaranteed lowest prices. Free brochures. 30-day money back guarantee, 3-yr. warranty. Visa/MC/COD. Kortesis Marketing, order 303-548-3995, FAX or messages 303-699-6660.



ANAHEIM WIRE PRODUCTS. DISTRIBUTOR OF ELECTRICAL WIRE AND CABLE since 1973. Items available from our stock: Hook up wire, Automotive primary wire, GXL, SXL, Plenum cable, Teflon wire, Multi-conductor cable, Irradiated PVC, SO-CORD, Mil-Spec wire, Building wire, Welding cable, Battery cable, Telephone wire, Shrink tubing, Cable ties, Connectors. If interested, please call 1-800-626-7540, FAX: 714-771-5043. Visa/MC.

FROM OUR stock, general test, microwave, instrument test, aviation, rate tables, boxcars, plotters, GCs, spectrophotometers, optic rail and misc., bolometer, magnetometer, SEM, and many other types of unusual equipment. New '97 list mailed. AMSL, Vermont. Ph. 802-254-9459, FAX 802-257-4862.

PCB DRILLS: 50 assorted tungsten-carbide bits in plastic cabinet, only \$5. Jack 503-581-6654, fax: 503-581-4382.

NEW, USED, and "as is" Radio Shack items. Software, printers, computers, books, parts for R/C cars, etc. Free list. B and B Enterprises, 208 S. Pulaski St., Baltimore, MD 21223. 410-566-5388.

Rave Review
Pop Comm
April '96

Professional 10 HOUR RECORDER

"BUILT LIKE A BATTLESHIP"

- Heavy duty commercial recorder - NOT improvised from consumer models
- 12, 14, and 16 hour models also available
- BUILT-IN voice activation (add \$30)
- Applications information included
- Dimensions: 11.5 x 7.0 x 2.75"

SPECIAL Nuts & Volts Price..

\$159

Includes UPS to 48 States

COD's OK. Calif. residents add tax. Sorry, no credit cards. Free catalog USA only, other countries \$5.

Viking International 150 Executive Park Blvd. #4600 San Francisco, CA 94134
Factory Direct Phone: (415) 468-2066 Fax: (415) 468-2067 "Since 1971"

Write in 118 on Reader Service Card.

CIRCUIT BOARD drill, Excellon uni-drill drill model 1230, two drilling heads/10X comparator unit is in very good condition \$500. 12" telescope, wood, 10" reflector 8" long, studio camera tripod, 4 different eye pieces \$650. High Noon Trading co. 513-429-5403.

TEST DEVICES, manuals and software. Call Jack at 313-384-3949. No Michigan sales.

NICAD BATTERIES: Maglite sticks 6VDC 2.5AH \$1.50 each 50 pcs./\$450. JIM 310-515-2058.

RECORDING PAPER 15W x 500L, 8 ch., 96 ea., \$25 ea., or OBO for all. BSE, POB 09649, Bexley, OH 43209-0649. 614-239-5763, Fax 614-231-2224.

WIRE STRIPPERS, thermal, handheld, used. \$10 + \$3 shipping. Strategic Technology, Box 145-V, Newville, AL 36353.

RADAR GUNS: MPH Industries, model K-55. Displays your speed & target speed. Comes w/case & instructions. Only \$300. 1-800-539-2859.

C and H SALES COMPANY

2176 E. Colorado Blvd., Pasadena, CA 91107

WE BUY AND SELL!

ORDER VIA TOLL FREE NUMBER BELOW OR FAX US AT (818) 796-4875

☒ Master Charge ☒ Visa ☒ American Express ☒ Discover

±15 VDC BECKMAN POWER SUPPLY



BECKMAN, #MPS-60. Input 120 VAC 60 Hz @ 1 amp. Dual adjustable outputs 0 to ±15 VDC @ 0-2 amps. Resolution 10 mV and 100 mA. Accuracy ±20 mV and 100mA. Has digital display for voltage and current. Dim.: 12" wide x 4-1/4" high x 13-1/4" deep. Weight 16 lbs. New, with manual.

Stock #PS9410 \$195.00

RETRO-REFLECTIVE PRISM /IR FILTER

Very high quality retro-reflecting prism. This prism returns an incoming light beam back to the source. Beam divergence is 10° or less. A light ray is returned to its source irrespective of reception angle up to approx. 30°. In addition, this prism has the apex of the reflecting surfaces flattened and polished. An infrared filter is bonded to this flat surface. With this modification the prism can be used as a retro-reflecting objective lens. These units are ideal for use as IR receiving or transceiving elements. Two could be used with co-axially mounted emitter/receiver pairs to form an infrared transceiver, etc. Also can be used for any retro-reflection, range finding applications or experiments. Front surface has anti-reflection coating. New, in perfect condition. Dimensions: 2.610" max. O.D. Filter is 18mm dia. x 2mm thick. Overall depth of prism and filter is 1.412". NOTE: We have production quantities of these units available.

Stock #OL9600 \$69.50

Without truncated apex or attached infrared filter.

Stock #OL9601 \$79.50

3600 RPM DC MOTOR WITH ENCODER



ELECTRO-CRAFT #M1140 or equiv. 30 volts nom. input voltage. Permanent magnet, reversible servo motor.

Has Hewlett Packard optical encoder. Ball bearings. No load speed at 30 VDC input is 4600 rpm. No load current 0.75 amp at 60 oz-in load rpm is 3600, current is approx. 6.6 amps. Torque constant is 9.1 oz-in per amp. Rotor inertia 0.0007 oz-in-sec. Terminal resistance 0.89 ohm. Optical encoder has 1024 counts per revolution, two channel quadrature output. Outputs are TTL compatible. Dual shafts: front shaft is 3/8" dia x 3/4" long. Rear shaft is 1/4" dia x 7/16" long. Dimensions: 4" dia x 5-1/2" long (excluding shafts.)

Stock #DCME9601 \$45.00

HEWLETT PACKARD TEST EQUIPMENT

#4328A. Milliohmeter. (No Probes)	\$275.00
#141T. Spectrum Analyzer Mainframe.	\$500.00
#8552A. Spectrum Analyzer IF Plug-in, Linear or 10 dB Div. Log	\$400.00
#8555A. Spectrum Analyzer RF Plug-in	\$500.00
#432B. Power Meter.	\$150.00
#204C. Oscillator	\$125.00
#333A. Distortion Analyzer	\$695.00
#3330B. Automatic Synthesizer	\$650.00
#8614B. Signal Generator. 0.8-2.4 GC	\$695.00
#216A. Pulse Generator	\$295.00
#8445B. Automatic Prescaler	\$495.00
#8057. Noise Generator	\$295.00

See our catalog for more models in stock.

CALL OR WRITE FOR OUR FREE 120 PAGE CATALOG FILLED WITH GOODIES—ELECTRONIC, OPTICAL, MECHANICAL, AND MUCH MORE! ALSO, PLEASE VISIT OUR RETAIL STORE WHEN YOU'RE IN PASADENA.

TOLL FREE: 1-800-325-9465

Write in 121 on Reader Service Card.

Nuts & Volts Magazine/January 1997 91

AAA TRADING/AUDIOPAGING, INC. CELLULAR CLOSEOUTS WHOLESALE TO THE PUBLIC

MOTOROLA 550 FLIP	\$149.95	LIMITED QUANTITY
MOTOROLA LITE	\$199.95	LIMITED QUANTITY
MOTOROLA FLIPSS	\$119.95	LIMITED QUANTITY
MOTOROLA 8000s	\$69.95	LIMITED QUANTITY
ALPHASTAR 950	\$179.95	LIMITED QUANTITY
NOKIA 100+101	\$110.00	LIMITED QUANTITY
BLAUPUNKT TC142	\$79.95	LIMITED QUANTITY
AUDIOVOX 450	\$119.95	LIMITED QUANTITY
AUDIOVOX 525	\$149.95	LIMITED QUANTITY
AUDIOVOX 400	\$99.95	LIMITED QUANTITY
NEC P120/110	\$119.95	LIMITED QUANTITY
DIAMONDTEL20X	\$139.95	LIMITED QUANTITY
UNIDEN CP 6000	\$69.95	LIMITED QUANTITY
NOKIA P 30	\$49.95	LIMITED QUANTITY
TANDY (NOKIA) CT350	\$69.95	LIMITED QUANTITY
GTI CP900	\$49.95	LIMITED QUANTITY
PANASONIC EB3510	\$69.95	LIMITED QUANTITY
NOVATEL 825 HANDHELD	\$79.95	LIMITED QUANTITY
AT&T 3610 (NECP120)	\$119.95	LIMITED QUANTITY
AT&T 3850 (NOKIA 232)	\$199.95	LIMITED QUANTITY

MANY MORE HANDHELDS IN STOCK CALL FOR PRICING

MOTOROLA TOTE BAG	\$95.00	WE BUY & SELL PAGERS
NOKIA BAG	\$59.00	
CHEAP BIG OLD BAGS	\$29.95	

TO ORDER CALL **215-483-4085** OR FAX **215-483-7732**
6186-88 RIDGE AVENUE, PHILADELPHIA, PA 19128

U.T.S. WHOLESALE

"The Real Wholesalers"

NOBODY BEATS OUR PRICES

NOVAVISION

**\$175
NEW**

**PANASONIC
WITH VOLUME**

**\$99
NEW**



We stock a full line of cable equipment and accessories.

PLEASE CALL 10:00 AM TO 6:00 PM E.S.T. M-F

1-800-633-4540



For ALL Your Cable Needs



SORRY, NO FL SALES.

Turn Your Multimedia PC into a Powerful Real-Time Spectrum Analyzer

Features


- 20 kHz real-time bandwidth
- Fast 32 bit executable
- Dual channel analysis
- Up to 65,536 pt FFT
- Octave analysis (1/1 - 1/24)
- THD, IMD, SNR measurements
- Signal Generation
- Digital Filtering
- Triggering, Decimation
- Transfer Functions, Coherence
- Dynamic Data Exchange (DDE)
- Time Series, Spectrum Phase, Spectrogram and 3-D Surface plots
- Real-Time Recording and Post-Processing modes

Applications

- Distortion Analysis
- Frequency Response Testing
- Vibration Measurements
- Acoustic Research

System Requirements

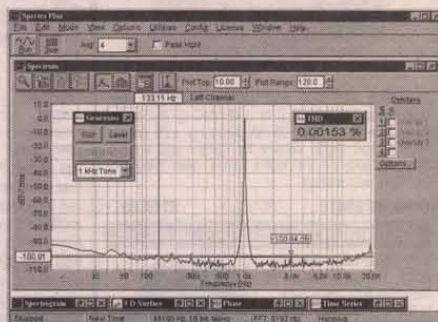- 486 CPU or greater
- 8 MB RAM minimum
- Win. 95, NT, or Win. 3.1 + Win.32s
- Mouse and Math coprocessor



Real-Time FFT Analyzer (single channel)\$299

Options:

Dual Channel Operation\$99

Recording, Post-Processing Modes\$99

Signal Generator.....\$99

Professional Quality Sound Cards AvailableCall

DOWNLOAD FREE 30 DAY TRIAL!

www.telebyte.com/pioneer

PHS

Pioneer Hill Software
24460 Mason Rd. N.W.
Poulsbo, WA 98370

Spectra Plus 4.0
Affordable Signal Processing Software

Sales: (360) 697-3472

Fax: (360) 697-7717

e-mail: pioneer@telebyte.com

FOR SALE: 200K VanGraf generator, cost \$120. Digital capacitance meter, cost \$70. Box of capacitors. Elco tube signal generator. Tenmar Laboratory oscilloscope, cost \$200. Make offer. Peter 305-223-7202 or write: 9953 NW 9th St. Circle #1, Miami, FL 33172.



PRC-25 AND -77 MAGNESIUM BATTERIES. LATE '90s MFD. 5/\$30 ORDNANCE UNLIMITED. 20945 OSBORNE STREET, CANOGA PARK, CA 91304. PH: 818-700-2905; FAX: 818-700-9168. VISA, MC, AMEX OK! ASK FOR DEAN.

HIGH QUALITY TOOLS AND STAINLESS STEEL HARDWARE. European and American screwdrivers, nutdrivers, pliers, hex keys, balldrivers, and much more! Wiha, Bondhus, and Knipex! Stainless cap screws, machine screws, nuts, washers, U-bolts, and eyes. Free catalog. Robert Mink Import-Export, Box 6437V, Fair Haven, NJ 07704. Telephone or fax 908-758-8388.

MODEL NBP2.4, precision, 2.4GHz, low phase error, narrow band pass filters, \$148 each, quantity available 2525. FAX PO or requests for information to AMR-LORAN at 609-764-1643.

MISC. ELECTRONICS: Sony LDP2000-3 laser discs 10/hrs, BARCO video switchers, Videoshow HQs, Fluke 27/FM, 8000A, HP 3435A DVMs, Kodak overhead mono/LCD/panel, HP 8640B-003 signal generator, new 3M-UCA60s \$10 ea., plus calculators, computer and satellite TV misc. prices/offers/info. Voice 719-630-1492.

MILITARY TRANSISTORS & DIODES & INTEGRATED CIRCUITS WANTED. ELECTRONIC MATERIAL INDUSTRIES 818-842-3539, FAX 818-845-3613.

ELECTRONIC PARTS: audio/DC power jacks and plugs, transformers, adapters and chargers, cords, sets & cables assemblies, connectors, jacks, & plugs, lamps & bulbs. Send for our items list: Alex Mastin (Reseller), PO Box 8802, Canton, OH 44711-8802.

MISC. ELECTRONICS WANTED

WANTED: LATE MODEL TEST EQUIPMENT (Tektronix, HP, Fluke). Also we buy test equipment manuals, catalogs. Pepper Systems, 214-353-0257; 214-902-9511 FAX.

RECOVER "SCRAP GOLD" from old computer junk. Free information packet. Call 24 hours: 603-645-4772.

WESTERN ELECTRIC audio equipment wanted. 1927-1960's. Amplifiers, "receivers," speakers, x-overs, tubes, etc. 1-800-251-5454.

MILITARY TRANSISTORS & DIODES & INTEGRATED CIRCUITS WANTED. ELECTRONIC MATERIAL INDUSTRIES 818-842-3539, FAX 818-845-3613.

WANTED: AVIONICS test equipment. IFR 1200Y3, 401L, 750B, 600A, Also Collins, King, Microline, Proline, Silver, Gold Crown Ground Power Units, Fox Carts. Avionics Plus, 28000 Airport Rd., Box A17, Hangar 97, Punta Gorda, FL 33982. 941-575-0138 P, 941-575-2361 F.

WANTED: JENNINGS type J-1004 or J-1005 high voltage voltmeter. Equipment in all types of condition accepted. Youngson's, Inc., 6701 Melrose Ave., Louisville, KY 40216, 502-448-6228.

CHADWICK HELMUTH equipment wanted! Spectrum analyzers and peripherals. Please contact Andrew Smith today with model numbers, condition and best price. AMSL, 67 Main St., Suite 16, Brattleboro, VT, USA 05301. Ph. 802-254-9459, FAX 802-257-4862.

FREE!!

COPY

7-WAY

7-WAY

CAT*

IMPORTANT LATE NOTICE!

WE NOW HAVE

STAR

TAC

AND

EE3

ELITE

Does... 1. All MOTOROLA's (including 951C & Elite)! 2. NEC's P1, P2, P4, P6, P7! 3. AUDIOVOX (includes new 800)! 4. GE-ERICSSON (includes new version)! 5. MITSUBISHI/DIAMONDTel! 6. SONY (H333) AND 7. PANASONIC! FULLY ASSEMBLED 5-YR WARRANTY.

***DETAILS...**

SIMPLY BUY ONE 7-WAY COPY CAT AT OUR REDUCED PRICE OF \$2995 WHICH INCLUDES ALL CABLES AND WE'LL SEND YOU A SECOND 7-WAY COPY CAT.. FREE!!**

**EXCLUDES CABLES

ORDER TODAY

FREE!! 7-WAY

COPY CAT!!

ABOUT US

Midnight Communications (a division of Cellular Technology Group) was one of the first importers/distributors of the "stand alone" programmer (i.e. "black box", "copy cat", "kopy cat", etc..) WE ARE PARTICIPANTS IN THE BBB's CARE PROGRAM AND DO NOT OPERATE OUT OF A LETTER SUITE OR USE A P.O. BOX. You are invited to call or visit us at 2170 Roswell Road, Marietta (Atlanta) GA. 30062. Purchaser of any product agrees to comply with all local, state and federal laws, including all FCC rules and regulations. All products are sold for EDUCATIONAL PURPOSES ONLY. VISIT US ON THE WEB <http://www.celltec.com> **NO GEORGIA SALES..**

CALL US TODAY AT 770.973.8474 or e-mail ctg@mindspring.com

CALL TOLL-FREE

(800) 292-7711

Se Habla Español

C&S SALES

EXCELLENCE IN SERVICE

**CALL FOR A
FREE 60 PAGE
CATALOG!
(800) 445-3201**

**AFFORDABLE, HIGH QUALITY ELENCO OSCILLOSCOPES
2 YEAR WARRANTY**




STANDARD SERIES

S-1325 25MHz \$325
S-1340 40MHz \$419

Features:

- TV Sync
- 1mV Sensitivity
- X-Y Operation
- High Luminance 6" CRT
- Complete Schematic
- Plus much, much more!!

2 FREE probes with each scope!!

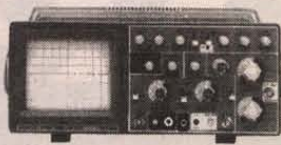

DELUXE SERIES

S-1330 25MHz \$459
S-1345 40MHz \$549
S-1360 60MHz \$749

Features:

- Delayed Sweep
- Automatic Beam Finder
- Z Axis Modulation
- Dual Time Base
- Illuminated Internal Gradicule
- Built-in Component Test
- Plus all of the features of the "affordable" series!!

MX-9300

Four Functions in One Instrument

Features:

- One instrument with four test and measuring systems:
 - 1.3GHz Frequency Counter
 - 2MHz Sweep Function Generator
 - Digital Multimeter
 - Digital Triple Power Supply
- 0-30V @ 3A, 15V @ 1A, 5V @ 2A



\$479.95

B&K 4040 w/ Frequency

- 2Hz to 20MHz
- AM and FM Modulation
- Linear and Log Sweep
- Counter Range 5Hz to 30MHz
- 5 Digit Display

\$425



GF-8026 w/ Frequency

- .02Hz to 2MHz
- Linear and Log Sweep
- Counter Range 1Hz to 10MHz
- 4 Digit Display

\$225




Model XP-581

4 Fully Regulated Power Supplies in One Unit

4 DC voltages: 3 fixed - +5V @ 3A, +12V @ 1A, -12V @ 1A • Variable - 2.5 - 20V @ 2A

Ideal for laboratories,
service shops and hob-
byists.

\$85

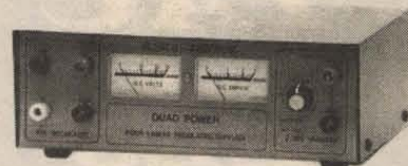

Fluke Multimeters

70 Series

Model 701L.....\$69.95
Model 731L.....\$97.50
Model 751L.....\$135.00
Model 771L.....\$154.95
Model 791L.....\$175.00

80 Series

Model 83.....\$235.00
Model 85.....\$269.00
Model 87.....\$289.00



M-1700

Digital Multimeter

11 functions including freq to 20MHz, cap to 20µF. Meets UL-1244 safety specs.

\$39.95

**Model M-6100
Programmable DMM**

Includes FREE Computer Interface
and FREE Software



- Analog Bar Graph
- Large 3 3/4" LCD Display
- Menu Driven
- Triple Display
- RS-232 Interface
- True RMS
- 9 Basic Functions including cap. & freq.
- Auto Power Off
- Easy-to-use

\$125

B&K Model 1688

High Current (25 DC amp) Power Supply

- Variable 3-14VDC
- 25 amps @ 135V
- Thermal Protection

\$249.95



**1.3GHz Universal Counter
Model F-1300**

- Period
- Frequency & 8 other functions

\$225



XK-550 Digital / Analog Trainer

Elenco's advanced designed Digital / Analog Trainer is specially designed for school projects. It is built on a single PC board for maximum reliability. It includes 5 built-in power supplies, a function generator with continuously sine, triangular, and square wave forms. 1560 tie point area.



XK-550

Assembled and Tested

\$169.95

XK-550K - Kit

\$139.95

Tools and meter
shown optional

Kit Corner over 100 kits available

Model AR-2N6K

2 meter / 6 meter
Amateur Radio Kit

\$34.95



Model AM/FM-108

AM/FM Transistor
Radio Kit

\$29.95



Model M-1005K

Low cost, 3 1/2 digit LCD, 18 ranges,
transistor test, diode test, overload
protection and pocket size.

\$19.95



Model TR-18K

Stereo Cassette Player Kit

- Transparent case
- High resolution

\$15.95



WE WILL NOT BE UNDERSOLD

UPS SHIPPING: 48 STATES 5%
OTHERS CALL FOR DETAILS
IL Residents Add 8% Sales Tax

C&S SALES

150 W. CARPENTER AVENUE
WHEELING, IL 60090
FAX: (847) 541-9904 (847) 541-0710

**15 DAY MONEY BACK
GUARANTEE**

FULL FACTORY WARRANTY

PRICES SUBJECT TO CHANGE WITHOUT NOTICE
http://www.elenco.com/cs_sales/



Quick Tracey Semiconductor Sleuth

by Fred Blechman

In the "lineup" were Danny Diode, Zachary Zener, Sammy Selenium, "Silly" Con Rectifier, Tommy Transistor, Usiah Unijunction, and Phineas Photoconductor. The problem: which one was the "bad guy?" Clearly a case for that surreptitious semiconductor sleuth, Quick Tracey ...

Using your oscilloscope and "Quick Tracey," it's a simple, quick job to wade through various types of "bargain" semiconductors and sort out the bad ones by interpreting a trace on your scope screen. Quick Tracey's regular "report" can include checking transistors for polarity (PNP or NPN), approximate gain, and linearity. Also, all tests are "dynamic" rather than "static," and will thus uncover some defects that static tests won't show.

When testing diodes, shorts or opens show up like the proverbial sore thumb; so does reverse polarity. On low-voltage zeners, not only will you be able to tell if they are good or bad, but you'll also be able to estimate their breakdown voltage. Even the less common semiconductors, such as unijunction transistors, tunnel diodes, and silicon-controlled-rectifiers, are cases easily handled by Quick Tracey. Costing under \$20.00 to build from all new parts (and less if you have some common parts in your junk box), Quick Tracey even has its own built-in calibration circuit.

Modus Operandi

Figure 1 is the schematic of the complete Quick Tracey. Since this actually contains three circuits (calibrate, diode test, and transistor test) we have shown each circuit separately in Figures 2, 3, and 4 to simplify the explanation of circuit operation. Although Quick Tracey can be used without any understanding of the circuit theory, you'll find other uses for the unit if you are familiar with its "modus operandi" (that's Latin for "how da' t'ing woiks").

Figure 2 shows the power and calibration circuit. When pushbutton switch S1 is depressed, equal voltages appear across R1 and R2 (since they have the same resistance value), thus giving equal deflection voltages across the scope vertical and horizontal inputs. (The scope sweep selector must be set to "horizontal input" or "external sweep.") By proper adjustments of the scope vertical and horizontal gain controls, you will get a sloping 45 degree line on the screen. This, in effect, sets the scope controls for equal gain on the vertical and horizontal inputs.

IMPORTANT NOTE: The 45-degree slant shown in the Figure 2 illustration, leaning to the right, may lean to the LEFT on your scope. If this is so, then ALL your scope traces will be the opposite (mirror-image) of the illustrations in this article. This has to do with your scope's horizontal deflection (left-to-right or right-to-left), which varies with different manufacturers.

Figure 3 shows the diode test circuit. Think of the diode under test as a switch; when it's conducting (forward-biased), it's like a closed switch, and when it's reverse-biased, it's like an open switch.

Now when we apply 6.3 volts AC, we are alternately opening and closing this "switch" (the positive half-cycle forward biases the diode, the negative half-cycle reverse biases the diode).

When the diode is conducting, it's the same as if we had shorted the horizontal scope terminal to the ground terminal, and the full voltage appears across R1. The scope shows only a vertical line under this condition. However, on the other hand, when the diode is not conducting, there is NO current flowing through R1, therefore NO vertical deflection, but FULL horizontal deflection. (The scope, remember, draws only infinitesimal current at 60 cycles, 6.3 volts.)

When the recurrent half-cycles are combined in the scope trace, the pattern is half vertical and half horizontal for a perfect diode. The poorer the diode, the less perfect the pattern. Representative traces for typical cases are shown in Figure 3.

When testing a low-voltage zener diode, the horizontal leg will "break down" at some distance out from the junction if the zener is rated at less than 10 volts. Higher voltage zeners can only be checked on Quick Tracey for diode action, but not zener effect.

Poor diode back resistance shows up on the trace as a down-ward slanting of the horizontal leg; with poor forward conduction, the vertical leg slants to the right. Selenium rectifiers, for example,

usually show a relatively high forward resistance, high-voltage drop (short vertical leg) and poor recovery characteristics (rounded junction of horizontal and vertical trace).

All testing done with the Quick Tracey is done at a very low power level;

a low-voltage, low-current diode, and the lower curved leg shows breakdown (though controlled, therefore not damaging) at the test voltage. Later on, we'll show you how to use the diode test circuit for other tests.

Figure 4 shows the PNP transistor

Figure 1. Schematic diagram of Quick Tracey.



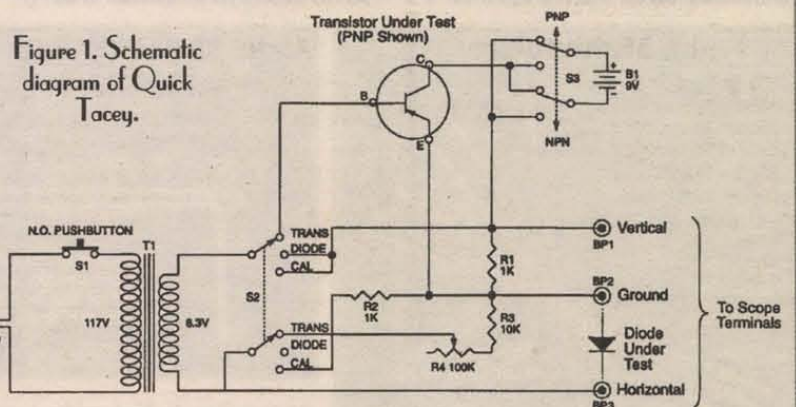


Figure 2. Calibration circuit of Quick Tracey.

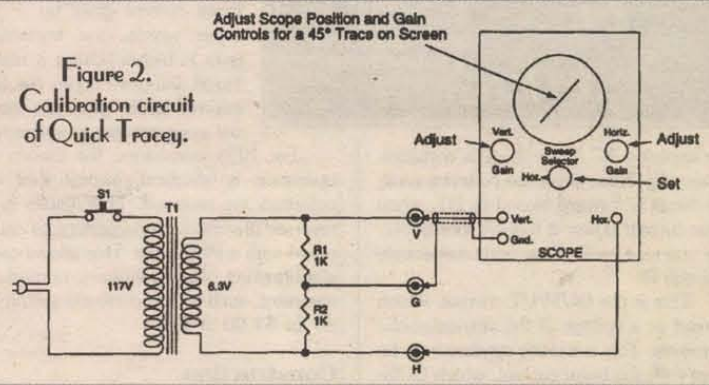

there is no danger in harming the unit under test. Even the touchy 1N23 microwave crystal diodes are undisturbed by Quick Tracey's investigation, although they do yield a peculiar trace (see Figure 3 microwave diode pattern). The 1N23 is

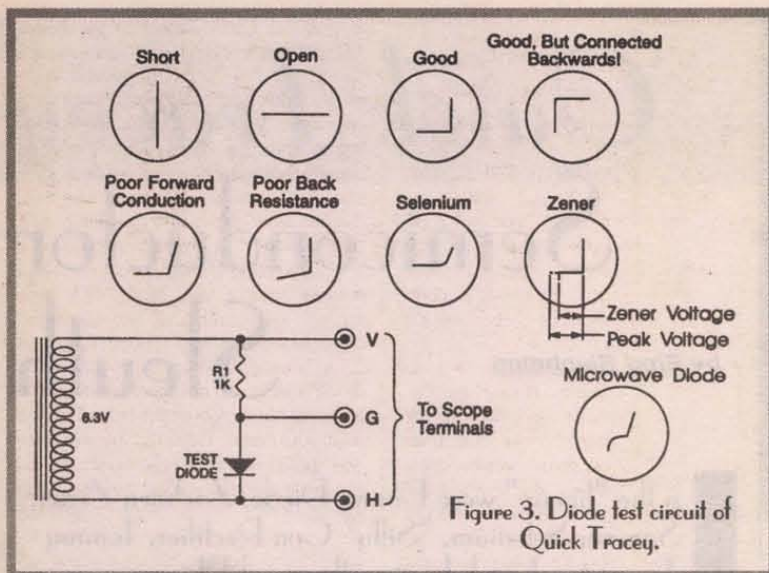test circuit. With a PNP transistor under test, the emitter has positive battery voltage applied through R1, and the collector is at negative battery potential. However, unless there is current flow in the base-emitter circuit, only a very small leakage



current flows in the collector-emitter circuit; that's what transistors are all about.


Notice that the base is directly connected to one side of the 6.3 volt AC supply, and the emitter is connected to the other side through R3 and R4. Therefore, whenever the alternate half-cycles make the emitter positive with respect to the base, emitter-base current flows through R3 and R4 (R3 is used for current-limiting when R4 is set at zero).

This current flow is measured as a voltage across R3 and R4 at the horizontal scope terminals, and is a measure of the transistor INPUT current. Since we

control. When the slope is 45 degrees, it means that the "input" and "output" VOLTAGES are equal. However, the voltages are dependent on the current flow through resistors R1, R3, and R4.

Remember Ohm's Law? If R4 is set at zero to get a 45 degree slope, then there is 10 times the current flowing through 1K output resistor R1 than flowing through 10K input resistor R3 to make their voltage drops equal. Plainly and simply, the output current is 10 times the input current, so the transistor has a "beta" (current gain) of 10.

As the value of R4 is increased to set

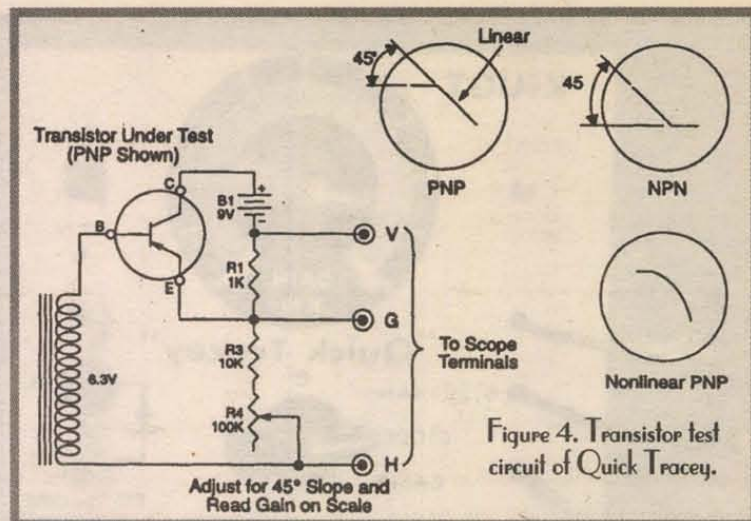

in your junk box.

First of all, decide on the cabinet you will use. If you use an aluminum cabinet (the Radio Shack #270-239 should do nicely if you use a small transformer for T1), be certain that your 117 VAC input voltage is isolated from the cabinet.

Certainly, placing the gain control, polarity switch, binding posts, and function switch on the front panel are logical. The power switch (S1) could be a toggle or slide switch instead of the pushbutton specified in the parts list; we preferred a pushbutton to insure that the unit was OFF except when actually viewing a trace.


Various transistor sockets could be

necessary.

Dry transfer labels or decals complete the job. NOTE: You may have a problem finding the nice dial plate shown in the photo (30 years ago they were readily available), but you can instead easily mark the front panel with decal numbers or make a paper dial plate.

Sleuthing With Quick Tracey

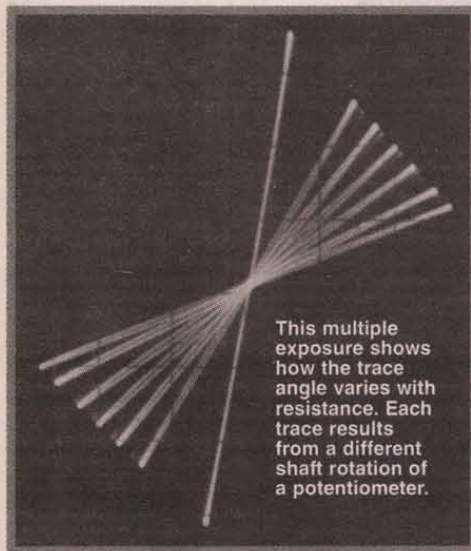
CALIBRATION: Regardless of whether you're "investigating" diodes, transistors or whatever, you must first calibrate the unit. Plug the line cord into a 117V, 60 cycle source and connect the scope as shown in Figure 2. Be sure to



are applying AC, this voltage is constantly varying. Now, since the collector-emitter circuit is forward biased by B1, when base current flows, it follows that collector current will flow simultaneously through R1.

This is the OUTPUT current, which is read as a voltage at the vertical scope terminals. This is exactly synchronous (in step) with the input current, which CONTROLS the output current.

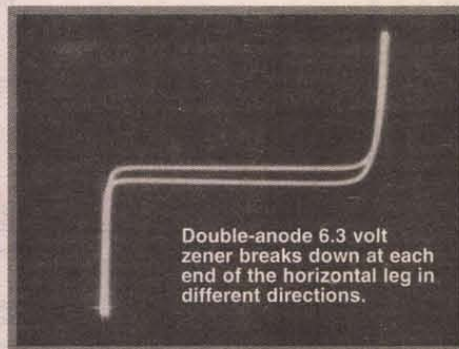What does all this mean? Well, remember we calibrated the scope for equal vertical and horizontal deflection back in Figure 2, and now we use this fact to set our transistor-test scope trace slope to 45 degrees, using the R4 gain




the trace slope to 45 degrees, the ratio of output current to input current goes up — in other words, the transistor gain is higher. Using a numbered dial plate under the R4 control knob, you can read the approximate gain directly.

For NPN transistors, the theory of operation is identical, except that all polarities are reversed. This results in a reversed (inverted) scope pattern as compared with a PNP trace. This allows easy identification of an unknown, unmarked transistor, such as are currently selling at 20 for \$1.00 or less.

Construction

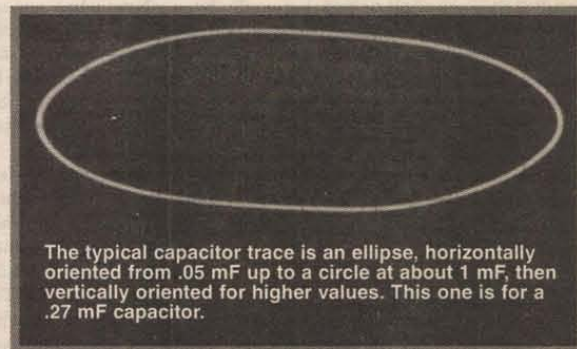The photos show our original unit — which, by the way, was built over 30 years ago and still functions perfectly! None of the wiring is critical, so you can decide which features you want to incorporate. You may have many of the parts



wired in parallel instead of the three alligator clip leads. A screw-type terminal strip could replace the five-way binding posts. Any 6.3-volt transformer will do; we used the least expensive one we could find. If you can't find a 6.3-volt transformer, use half of a 12-volt center-tapped transformer, such as a Radio Shack #273-1365.

Function switch S2 is any two-pole three-position type — rotary or slide; you can use three positions of Radio Shack's #275-1386 two-pole six-position rotary switch. The battery, a standard transistor radio nine-volt type, is held to the case with a home-made bracket made from a thin 1.5" by 2" piece of scrap aluminum.

The battery connector was salvaged from a dead battery of the same type. A terminal strip was used to anchor the alligator clip leads, and another terminal strip to anchor the power cord and transformer input leads. With the push-to-test power switch, a pilot light is not

set the scope sweep selector to the horizontal input. Put S2 in the "Calibrate" position and depress power switch S1.

A slanted line will appear on the scope screen; adjust the vertical and horizontal gain and position controls until this line is in the center of the screen, at a 45 degree angle, and filling about two-thirds of the screen diameter. You are now calibrated for equal vertical and horizontal voltages at the Quick Tracey output terminals. As mentioned earlier, the line may slant in the opposite direction, in which case, all other test traces will be flipped horizontally.

DIODES: To test a diode or rectifier, connect it between terminals G (ground) and H (horizontal), with the cathode connected to H, as shown in Figure 3. Put S2 in the "Diode" position. The trace tells the story when S1 is depressed. Compare your pattern with the typical traces shown in Figure 3.

Connecting the diode backwards will give you an inverted trace, which

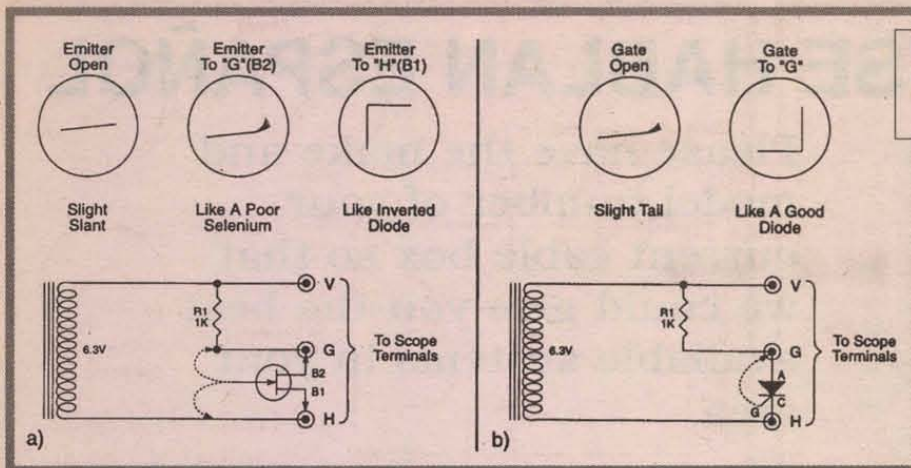


Figure 5: a) Unijunction transistor test; b) silicon-controlled rectifier test.

tom of the PNP slope) is "leakage," which is probably not going to bother you unless you have a critical application. This tail is common, but no tail is preferable.

Incidentally, on all Quick Tracey testing, don't be upset if the traces show dual lines on some oscilloscopes. This is due to a non-linear

allows you to determine the cathode of unmarked diodes. Zener breakdown voltage can be estimated as a proportion of 10 volts by measuring the distance of the breakdown point from the junction, as compared to a regular diode (Figure 3 zener pattern).

Shorted or open diodes are instantly spotted by the straight vertical or horizontal line. Selenium rectifiers usually have a rounded junction and a slanted, shorter vertical leg. Tunnel diodes (where as the voltage increases, the resistance increases, then decreases, then increases again) show a distinctive double-

test, so flick S3 to the PNP position. Still nothing? Throw the transistor away — it's no good.

On a good transistor, you will get a trace like the patterns shown in Figure 4. Using the gain control on Quick Tracey, set the slope to about 45 degrees, and read off the approximate gain on the R4 scale. Even with the gain control set to minimum, you still have a gain of 10, because of the series current-limiting resistor R3.

Of course, all this assumes that the transistor is properly connected. Transistor basing is pretty well standard-

ear condition in the scope common at the Quick Tracey working frequency of 60 cycles, and is not the fault of the part you are testing.

Defective transistors will either exhibit no trace at all, or one which is obviously not right. Finding defective transistors in "bargain" packs is a cinch with Quick Tracey. You can sort them out by approximate gain, linearity, and type (PNP or NPN), and use colored dots of paint for coding. Quick Tracey will uncover the high percentage of undesirables in many bargain packs.

Odd Jobs For Quick Tracey

Using the principles outlined in the circuit descriptions, the astute reader will realize that Quick Tracey can be used for many other tasks, some of which follow:

(1) **Relative Resistance Measurement:** Set for diode test. Connect unknown resistor as for diode, except there is no polarity consideration. A horizontal trace means a high resistance; as resistance decreases, the trace slants more and more vertical. Vertical, as you recall, means a short circuit. A resistance of 100K shows an almost horizontal trace, tilting upward to about 20 degrees at 10K, 70 degrees at 1K, and essentially vertical at 100 ohms or less. This is a good way to test potentiometers for open spots or noise (noise will make the trace fuzzy as you rotate the shaft).

(2) **Capacitance Testing:** You can not only tell if the capacitor is good (at low voltage), but you can estimate the value of capacitance for all units from .05 microfarads to several hundred microfarads, including those difficult-to-test low-voltage transistor electrolytics! Even more surprising, you don't have to worry about polarity when testing an electrolytic.

ic. Just use Quick Tracey as for diodes. The pattern will be a horizontal long and thin ellipse for .05 mF, growing to a circle at about 1 mF, and becoming a vertical ellipse beyond that value, slowly closing to a vertical line at several hundred microfarads (which is essentially a short circuit to 60 cycles). You can make a calibration chart from known values, plotting value against ellipse proportions.


(3) **Testing Photoconductors:** These devices have a very high "dark resistance," and a relatively low resistance when exposed to light. Connect the leads of a photoconductor as described for diode testing, except there is no polarity to worry about. Cover the face of the cell with your hand. When S1 is depressed, you should get an almost horizontal line (depending on the normal dark resistance of the type of cell you are using). When you remove your hand and expose the cell to light, the line will tilt towards vertical if the cell is good. The more light, the more vertical. A graph of the trace angle plotted against light intensity could be used as a rough light measurement device. Some types of cells show relatively little change; others will go from straight horizontal to straight vertical!

(4) **N-Type Unijunction Transistor Testing:** As shown in Figure 5A, connect Base 2 to the G terminal of Quick Tracey, Base 1 to the H terminal. Leave the emitter unconnected. Set S2 to "Diode" and depress S1. You should get a slightly slanted horizontal line, since the unijunction has a high resistance with an open emitter. Now touch the emitter to G and then to H and you should get the traces shown in Figure 5A.

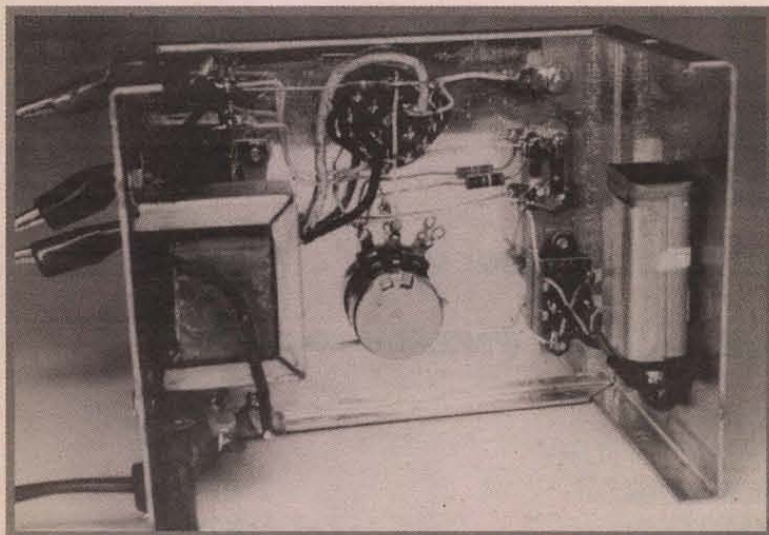(5) **Silicon-Controlled Rectifier (SCR)** Testing: Connect the anode and cathode as shown in Figure 5B. Leave the gate unconnected. Set Quick Tracey for diode test. When S1 is depressed, you'll get a horizontal line, perhaps with a curved tail. When the gate is connected to G (use a clip lead), you'll get a trace that looks like a normal diode. The vertical leg shows that the SCR is properly conducting during the half-cycle when the anode and gate are positive with respect to the cathode.

Our original Quick Tracey prototype has been in use for over 30 years, and has easily paid for itself in savings on bargain transistors, diodes, and SCRs. Super-sleuth Quick Tracey will uncover defects that other testers miss, and show some things that only the most expensive testers check.

Quick Tracey's fee is low for the service performed. Quick Tracey's motto: "Stamp out bad semiconductors!" **NV**



Although there is not much inside Quick Tracey, the reflections from the mirror finish make it look like there is. The nine-volt battery is held to the side of the box with a simple homemade aluminum bracket.

curve trace.

TRANSISTORS: Connect the collector, base, and emitter transistor leads to the C, B, and E of Quick Tracey. Put the polarity switch S3 in the more common NPN position, unless you know for sure that you are testing a PNP transistor. Put function switch S2 in the "Transistor" position. When S1 is depressed, you should get a sloping pattern with a flat bottom section. Adjusting Quick Tracey's gain control, R4, should change the slope. Don't touch the scope controls which you previously calibrated for equal gain! If you get no significant pattern, or the gain control has no effect, you may have a PNP transistor under

ized these days, and there are many sources of basing diagrams. If you're not sure, try various combinations; Quick Tracey is very forgiving of "goofs" and we have yet to hurt a transistor or diode by hooking it up wrong on Quick Tracey. You will get some mighty weird patterns with some mis-connections, and that should tip you off.

Minor variations in the trace can be significant. For instance, if the sloped line is perfectly straight, the transistor has linear response (at least in the low current range). A curved, sloping line is characteristic of RF transistors, which need not be linear in most applications. A short "tail" at the top of the NPN slope (or bot-

- TI** - Small 6.3-volt filament transformer (see text)
S1 - Normally open SPST pushbutton switch (see text)
S2 - two-pole three-position miniature rotary switch (see text)
S3 - DPDT slide switch
BPI, BP2, BP3 - five-way binding posts (Radio Shack 274-62)
B1 - 9V battery, Burgess 2U6 or equivalent
R1, R2 - 1K 1/4-watt carbon resistor
R3 - 10K 1/4-watt carbon resistor
R4 - 100K linear-taper potentiometer
Cabinet - See text
Dialplate - Mallory #380, Ohmite #5000 (see text)

Miscellaneous: AC line cord, pointer knob, three alligator clips, dry transfer lettering, wire, solder, screws, nuts, aluminum scrap for battery mounting bracket, and terminal strips.

PARTS LIST

SE HABLAN ESPAÑOL

Please have the make and model number of your current cable box so that we could give you the best available systems in your area.

- **PERSONALIZED ASSISTANCE** •
- **COMPETITIVE PRICING** •

CATV 1 PC. SYSTEMS

NOVA 5600	\$235.00
NOVA 5700	\$225.00
NOVA 5800	\$225.00
NOVA 5750	\$320.00
Also new Maestro	\$300.00

All stock is new and also comes with step-by-step hook-up sheet.

FILTERS

CHANNELS #2 THRU #23	\$20.00
----------------------	---------

CONVERTERS: (PARENTAL LOCKOUT)

PANASONIC:	\$89.00
NOVA CENTURY:	\$79.00
VIEWSTAR:	\$79.00
REMOTES:	\$20.00
REMOTE A/B SWITCH:	\$35.00
PATCH CORDS:	\$1.25
FILTERS:	\$20.00
TV 86:	\$75.00

30 DAY MONEY BACK GUARANTEE

1 YEAR WARRANTY

Prices subject to change without notice!

P.O. BOX 1494

ADDISON, IL 60101

INFO 1-630-889-0281

FAX 1-630-889-0283

HOURS: Mon. thru Fri. 9-6, Sat. 10-2

**K
D
E**

ELECTRONICS CORP.

All orders leave same day or shipping is on us.

Call for your complete cable accessory needs.

TOLL FREE ORDER LINE
1-800-361-4586

• **NO ILLINOIS SALES:**

TECHNICAL HELP: 1-630-889-0281



by
Harry Helms

L

ast year in this column, we discussed using custom controls in developing Windows software. Custom control technology has advanced so rapidly that a good chunk of that

earlier column is now obsolete information. Forget about the .VBX and .OCX controls

Software Wizardry

Controls are an example of object-oriented programming. Controls are not subroutines; instead, the programming code and data of each control is "encapsulated" and entirely separate from other controls (that is, objects) and the

rest of the program. Because of this, controls can be reused from one application to another without modification. You don't program controls; instead, you set their "properties."

Properties include such things as the name by which the control is referred to in a program, the text of any caption displayed by the caption, and the foreground and background colors of the control and any displayed text. Each control will have its own individual set of properties, and their settings can be changed during execution of the program in which they are used. For example, you could change the text of a control's caption property as a result of program execution.

Some familiar Windows controls include buttons, message boxes, horizontal and vertical scroll bars, radio buttons, check boxes, and even windows

mentioned in the previous column — Microsoft has now decreed that the future of custom controls now revolves around something they call ActiveX controls.

ActiveX isn't nearly as new as its name, however. ActiveX control technology is really an improvement of existing .OCX controls. Like .OCX controls, ActiveX components are "packages" of code that accomplish specific functions and communicate with Windows programs and other ActiveX components. However, there are some major differences between ActiveX components and .OCX controls.

For one, ActiveX controls can be used in Web pages, stand-alone applications written in Visual Basic or C++, and in Visual Basic for Applications (VBA) macros written for Windows applications like Excel or Adobe's Photoshop.

Another major difference is that ActiveX controls can be developed using the comparatively simple Visual Basic language, unlike the heavy-duty C++ programming required for .OCX development.

Finally, ActiveX controls can also work with the Macintosh version of Internet Explorer (version 2.1), as well as the Mac version of Netscape Navigator with the ActiveX controls plug-in.

Microsoft is backing ActiveX to the hilt as the basis for Windows programming, macro development for Windows applications, and to add functionality to Web pages. ActiveX is Microsoft's main counter-strike against Java for Web development. All this means is that it doesn't matter if you love or hate ActiveX technology; you'll need to know something about it.

ActiveX technology is developing rapidly and is in a major state of flux. For the very latest developments, you must visit Microsoft's Web home page at <http://www.microsoft.com> — Several ActiveX controls can be downloaded free from this site along with documentation for ActiveX technologies.

The Idea Behind Controls

In the previous column on controls, I compared Windows to a solderless breadboard. A solderless breadboard has a pattern of conducting strips underneath that allows easy interconnection of integrated circuits and other electronics parts along with common connection points for the supply voltage and ground. In the same way, the Windows operating system provides pathways for different programs to communicate with each other, standard memory locations, etc. The "integrated circuits" of Windows are controls. In fact, Windows itself is nothing more than a large collection of controls.

All About ActiveX Components

themselves. Not all controls are visible to users. One very useful control that has been available since the introduction of Visual Basic is the timer. Its properties allow it to trigger another event, such as displaying a message box, after a pre-set amount of time. However, this control is not displayed in the user application (although it is visible to programmers).

Controls respond to events, such as a mouse click, the cursor entering and/or leaving a certain area, calculation of a certain numeric or logical value, occurrence of an error, etc. Events are communicated to/from controls via messages passed between controls and the user interface (i.e., Windows). The exact event(s) a certain control will respond to can usually be set like other properties, although some controls are written to respond only to one event.

Controls must be used within "containers." A container is Windows itself, an applications program, a programming environment (like Visual Basic, Visual C++, or Delphi), or a Web browser.

The first controls available for use with Windows applications were .VBX (Visual Basic extension) controls, which were 16-bit controls. Visual Basic came supplied with a set of controls, and soon a cottage industry grew up to supply additional .VBX controls. .VBX controls could also be used in Microsoft's Visual C++ and Borland's Delphi, and they could be created using C++ and the Microsoft Foundation Classes (MFC) library of routines for C++ programmers.

.VBX controls were replaced by .OLE (object linking and embedding) controls, which were soon renamed .OCX controls. These were similar to .VBX controls, but were 32-bit controls designed to take advantage of Microsoft's OLE standard to allow communication between Windows applications. .OCX was also part of a concerted effort by Microsoft to force

Windows users to migrate to a 32-bit environment as quickly as possible.

While Microsoft was focusing on desktop PCs and their hard drives, Netscape and Sun were focusing on the Internet and emerging Web technologies. When Netscape released their Navigator browser and Sun released the Java programming language for Web applications, Microsoft was caught flat-footed. They were desperate to come up with some sort of meaningful response.

The response turned out to be ActiveX.

Inside an ActiveX Control

All Windows controls, including ActiveX, are based on Microsoft's component object model (COM). The COM standard describes how any object used as a control is able to communicate with other controls. Such communications are called messages, and involve the properties and status of a control (such as its background color or whether it is enabled or not), and data and instructions for other controls. Messages are passed between controls through interfaces. Control interfaces are a set of software protocols that allow controls to make requests of each other and transfer data. COM also specifies that controls are not stand-alone programs, but instead must be used within a container.

While the COM standard was originally developed for Windows, it is not restricted to Windows. COM now includes cross-platform support with full binary capability, as demonstrated by the recent introduction of ActiveX controls for Mac browsers.

The next element of an ActiveX control is OLE. OLE is best known for its linking and embedding between Windows applications. OLE means you can embed an Excel spreadsheet in a Word document, and if changes are made in the Excel spreadsheet, the embedded copy in the Word document is automatically changed. OLE also enhances data transfer between objects and controls, as well as data storage by both.

When Microsoft decided to get serious about the Web, they had no trouble getting a competing browser ready, since a browser is a relatively simple development task (compared to an operating system, for example). Responding to Java was a little more difficult, since developing a new programming language would not be a simple task. Moreover, Microsoft wanted a high level of integration between its desktop software and Web software. The obvious solution was to enable .OCX controls to use Web browsers as a container. However, the .OCX specification needed to be modified for use over the Web. The result was ActiveX.

One big problem with many .OCX controls was that they were simply too big for efficient transfer over the Web at 28.8 or slower rates. ActiveX solves this problem by significantly reducing the mandatory "overhead" called for in the .OCX specification, such as the object linking and embedding software protocols. Since ActiveX controls will not have parts of a word processing document embedded in them, or be linked to a spreadsheet, such protocols are unnecessary. (Such OLE protocols can be added to ActiveX if desired, however.)

In programming environments like Visual Basic, Visual C++, or Visual Basic for Applications, ActiveX controls can be added to their "toolboxes," much like the standard button, slider, text box, etc. controls supplied with those programming environments. ActiveX controls are used like the standard controls by clicking on the desired control in the toolbox and locating the icon for the control on a form. (See the sidebar about Visual Basic for Applications.)

Microsoft's Internet Explorer browser comes supplied with several ActiveX controls specifically developed for use with Web pages. A list of these is given in Table 1. If a Web page using those controls is browsed, those controls are automatically loaded from the PC's hard drive. If the control is not one of those supplied with Internet Explorer, the control is automatically downloaded and installed on the user's hard drive (we'll discuss this in more detail later). While the latest version of Netscape's Navigator browser does not support ActiveX, a "plug-in" for Navigator that

Software Wizardry

supports ActiveX is available. This can be included on the Web page and downloaded by users. For more information about this plug-in, visit <http://www.nccompasslabs.com>

Adding ActiveX controls to Web pages you're developing is a different matter, however. You'll have to go into the HTML file for the Web page to add them.

Adding ActiveX Controls to HTML Files

ActiveX controls are used as part of a scripting language for a HTML browser, such as the VBScript used with Internet Explorer 3.0. ActiveX controls are "declared" by placing a description of the control and its properties between a pair of OBJECT tags. The declaration includes a name for the control, and the control is referred to by that name in VBScript.

Let's suppose that you want to use a timer control in a HTML file. Here's the code you would use:

```
<OBJECT
  classid="clsid:59CCB4A0-727D-11CF-AC36-
  00AA00A47DD2"
  id="tmrEventTrigger"
>
<param name="Interval" value="500">
<param name="Enabled" value="True">
</OBJECT>
```

The "classid" line is a unique identifier for the specific ActiveX control that is being made available for use (in this case, the timer). When your browser encounters the classid line, it checks your PC to see if a copy of that control is located somewhere on your hard drive. If not, the Internet Explorer browser will display a message box notifying the user that the control is not available and must be downloaded. The user has the option of canceling the download or proceeding.

The "id" is the name by which the control will be referred to in VBScript; you can use any name you want as long as it follows Visual Basic naming conventions. (Notice we use the "tmr" prefix to identify the name as

belonging to a timer control.) For controls that are visible to the user (unlike the timer), an "align" can follow "id" to specify where on the Web page the control should be placed. The "param name" lines identify and initially set the properties of a particular control. For a timer, the properties are "enabled" (whether the control is functional or not) and "interval" (the time interval in milliseconds before the timer event will be triggered). Different ActiveX controls will have different properties to be set.

Using ActiveX controls in HTML documents is simplified through the use of the ActiveX Control Pad, which contains a full set of the controls included with Internet Explorer 3.0. A beta version of this is currently available from Microsoft's Web site. To be honest, using ActiveX controls in HTML documents is currently a big pain in the nether regions, and Control Pad is far from a satisfactory solution. However, future Web authoring tools from Microsoft and other vendors are expected to have extensive support (like point-and-click from a toolbar) for ActiveX controls.

Creating ActiveX Controls

"Creation" of an ActiveX control does not always involve writing a lot of original code. Some ActiveX authoring tools, like the forthcoming new version of Visual Basic, will allow you to enhance existing ActiveX controls by adding new properties and events to them. (See the accompanying sidebar about new developments in Visual Basic.) These same tools also let you create new ActiveX controls by assembling existing controls into new controls. However, you cannot distribute (whether for free or for profit) any controls you create using existing controls without obtaining the permission of the original control developer(s).

Totally new ActiveX controls can be created using any 32-bit Windows programming environment that can produce a stand-alone executable (.EXE) file. This includes C, C++, Visual J++ (Microsoft's visual Java programming tool), and the forthcoming new versions of Visual Basic and Delphi. If you use C++, developing an ActiveX control is greatly simplified by using version 4.1 or later of Visual C++ and the Microsoft foundation classes (MFC) library. Microsoft has recently introduced a new tool called the ActiveX template library (ATL), which includes several C++ templates that do a lot of the tedious work of OLE programming for you.

Developing ActiveX controls is not something for the casual programmer, however. You'll need a good understanding of the Windows applications program interface (API) and the registry, which is the Windows95/NT system-level database that will largely replace .INI files in all current and future versions of Windows. The Windows95 registry is REGEDIT and the Windows NT version is REGEDT32. You should also be familiar with basic registry system calls. This emphasis upon the registry is because all ActiveX controls are "inventoried" there using their "classid" identifiers. When a Web page using an ActiveX control is accessed by a PC using Internet Explorer 3.0, Windows looks at the registry to see if the control is already on the PC's hard drive.

You will also need to have a good understanding of how OLE functions and OLE calls to develop

ActiveX components. In particular, knowledge of the various COM interfaces and calls will be necessary so your ActiveX controls can successfully communicate with other controls, applications, and Windows itself. None of this — the registry, OLE, COM interfaces — is especially difficult, but it is unfamiliar to many Windows developers. To help developers, Microsoft has an ActiveX software development kit (SDK) that contains a library of COM interfaces and calls, utilities, sample controls, and a documentation library. Information on obtaining the SDK can be obtained from the Microsoft Web site.

Earlier in this month's column, we mentioned that ActiveX controls can be used with Macintosh Web browsers. ActiveX controls for Web pages can also be developed on the Macintosh. The only Macintosh programming environment suitable for ActiveX control development is Metrowerks Code Warrior used in conjunction with Microsoft's ActiveX SDK for the Macintosh.

There is promise that ActiveX control development will soon get much easier for Windows developers. For several weeks prior to writing this column, I have been using a beta version of the control creation edition (CCE) of Microsoft's Visual Basic. The CCE will be incorporated in the upcoming version 5.0 of Visual Basic, and it greatly simplifies the development of ActiveX controls. The CCE handles most of the OLE and COM calls/interfaces for developers, allowing programmers to focus on developing the control itself rather than spending time and effort on the control's communications with other controls and Windows. The big disadvantage of the CCE is that it uses Visual Basic to develop ActiveX controls, which limits the power and versatility of the controls. However, the trade-off for simpler, faster development is worth it in many situations. Expect to see a version of the CCE to start appearing in the future versions of other programming tools like Visual C++, Delphi, etc.

Security Issues

Two concerns whenever any software — like ActiveX controls — is transferred over the Web involve getting payment from developers who use the control and protecting against viruses and other corruption. On the first point, ActiveX has a lot going for it; on the second, it significantly lags Java-based code.

ActiveX allows controls to be distributed with either a developer or a runtime license. A developer license lets users use the control when developing other software or Web pages. In contrast, a runtime license lets users access the control as part of an application or Web page, but prevents the control from being copied into another application or development tool. Licensing agreements can be implemented on-line, if desired. For example, if a user accesses a Web page using runtime licensed controls, the controls could not be downloaded to the user's PC and displayed until the user completed an on-line licensing agreement. Many ActiveX developers, like Microsoft, distribute controls that require no runtime licensing, but which do implement developer licensing. However, there is no requirement to implement any licensing arrangements.

When it comes to preventing a virus or other problem from entering a user's PC via a downloaded ActiveX control, however, ActiveX is currently a less secure technology than Java. Tests conducted by several industry publications have clearly shown that a virus can be introduced into a PC far more easily by downloading an ActiveX control than by downloading a Java applet. Not surprisingly, Microsoft disputes the severity of the problem and promises that any security concerns will be addressed in future updates to ActiveX technology. However, this security "hole" will be a real limiting factor in the use of downloaded ActiveX controls on the Web until it is successfully resolved. Perhaps the best short-term strategy is to restrict use of ActiveX controls on Web pages to those controls already part of Internet Explorer 3.0.

Table 1
ActiveX Controls Supplied with Internet Explorer 3.0

Web Browser: Displays HTML pages and ActiveX controls
HTML Layout: Displays two-dimensional HTML areas
Gradient: Shades a specified area of a HTML page or transitions between colors
Hotspot: Adds transparent hotspot to a HTML document
Image: Displays .WMF, .JPG, .GIF, or .BMP format image files
Label: Creates text labels
TextBox: Creates multiple line text-entry and text-display boxes
ComboBox: Creates a drop-down option list and select box
ListBox: Creates a scrollable list of options
CheckBox: Lets users select options by checkable boxes
OptionButton: Lets users select between multiple options
ToggleButton: Creates a button with a toggle (on/off) selection
CommandButton: Creates a pushbutton control
ScrollBar: Creates horizontal and vertical scroll bars
TabStrip: Creates multiple pages that can be selected via tabs
SpinButton: Creates a button that can be pushed up or down
Menu: Creates a pull-down menu or menu button
Popup: Displays specified HTML documents in a pop-up window
ActiveMovie: Displays streaming and non-streaming media, including sound, video, and video synchronized with sound
Chart: Creates various types of charts in different styles
Marquee: Scrolls an HTML file in a horizontal or vertical direction at a specified rate
StockTicker: Continuously displays changing data that can be downloaded from a specified URL
Timer: Causes certain actions to be performed or scripts executed at specified time intervals
Preloader: Downloads a specified URL and puts it into the cache

Software Wizardry

The Future of ActiveX

In previous columns, I've stressed how programming is moving toward an object-based model in a visual environment. Programming in the future will largely involve the skillful assembly and manipulation of objects to create applications instead of the writing of thousands of lines of code. ActiveX is a major step toward realizing that future.

There are three big advantages of ActiveX controls over Java applets. Perhaps the most important is that ActiveX controls can be used in Web pages, in stand-alone applications, and in Visual Basic for Applications macros while Java applets are generally restricted to Web pages. For developers, this means a far larger market for ActiveX controls than for Java applets, and I

expect more ActiveX controls to be created than Java applets.

A second advantage is that ActiveX controls can be created using a variety of programming languages that many people already know, like C++ and Visual Basic. Java applets must be written in Java, which is a relatively difficult language most developers will have to learn. (If they already know Java, Visual J++ can be used to create ActiveX controls.)

The final big advantage is that a substantial number of ActiveX controls are already available — over 1,000 as of September, 1996 — with more introduced each month.

Because of these factors, I believe a good working knowledge of

ActiveX will soon be an absolute necessity for Windows programmers and Web page developers. I also feel that people who can create ActiveX controls are going to be in very big demand over the next few years. The ActiveX wave will be enormous, and those who are prepared to surf it will be in for the ride of their lives! NV

Big Changes in Visual Basic

Late in 1996, Microsoft made two moves to increase Visual Basic's popularity. One — the control creation edition (CCE) — is discussed in this month's column. The other move was more subtle, but may have even greater long-term impact.

Figure 1 shows the opening screen that greets you when you open Visual Basic CCE. Notice that you have a choice of three options for a new project: a standard .EXE file, a control group (CTLGROUP), and an ActiveX control. The standard .EXE file is similar to programs created with previous versions of Visual Basic, and these files are intended for distribution on floppies or CD-ROMs. A CTLGROUP file is a collection of ActiveX controls that make up a new ActiveX control. The ActiveX option is the one you select when you want to create a new ActiveX control from scratch.

When creating a new ActiveX control, Visual Basic CCE discards all elements of Visual Basic not required for a functioning control. This includes items like the Jet database engine, report writing functions, file

management functions, etc. Through such "streamlining," Visual Basic CCE produces compact, executable files well-suited for distribution over the Web or included as part of larger applications.

Figure 2 shows the design interface of Visual Basic CCE, and this interface will be used in all future versions of Visual Basic. The interface shown in Figure 2 is set for ActiveX control design, and displays three windows: a properties window, a form layout window, and a project window. The properties window lets you view a list of control properties in alphabetical or categorical order. The form layout window lets you arrange the visual appearance of the control. The project window shows all the files that go into making the control. In Figure 2, only one file (Axbutton.vbp) is in use.

Figure 3 shows the code window for the Axbutton control. If you've used Visual Basic before, this code will look very familiar: it is Visual Basic! There are a few new additions to facilitate Web use (such as for handling URLs), but it is essentially the same Visual Basic that's been around for years.

Microsoft also recently announced that it has licensed Visual Basic for Applications (VBA) to other software companies. This is part of Microsoft's strategy to make VBA the standard macro scripting language for applications programs. Among the first adopters of VBA include Great Plains Software, Adobe, Micrografx, Visio, Autodesk, Intergraph, Texas Instruments, Rockwell, Seagate Software, Symantec, and Siemens. Many of these companies — Texas Instruments, Rockwell, Siemens, etc. — produce

Windows software for manufacturing and industrial applications where the required macros can be quite complex. But VBA will also be the macro language for future editions of such popular applications as Adobe's Photoshop. Of course, VBA will remain the macro language for all of Microsoft's applications.

C and C++ will still be required tools for many advanced programming tasks (such as writing device drivers), but Visual Basic will let

A Marriage Between the BeBox and the Macintosh???

My column a few months ago about Be, Inc., and their BeBox provoked a lot of interest. Now, it seems as though *Nuts & Volts* readers weren't the only ones excited over the BeBox.

It's no secret that Apple's efforts at developing a new version of its Macintosh operating system have not been very successful. System 8 — code-named "Copland" — had been promised since 1993, but Apple announced in mid-1996 that it was abandoning the effort. In the meantime, Windows 95, and especially Windows NT, closed the gap on the Mac's System 7. In several key areas — such as multitasking, protected memory, and file systems — Windows NT is clearly superior to System 7 and even the promises of System 8.




In my column about the BeBox, I noted the many links between Be and Apple. Be was founded by former Apple executive Jean-Louis Gassée, the BeBox uses PowerPC microprocessors, and it is possible to develop software for the BeBox on the Macintosh. One big difference, however, is the Be operating system. The "BeOS" is a couple of quantum levels above anything available on a desktop sort of a workstation. It's the sort of operating system that could give Apple a decisive advantage over a Windows PC.

Gil Amelio, Apple's new CEO, must've thought so too. At the time this was written, Apple and Be admitted they are in negotiations over licensing the BeOS to Apple!

In the fall of 1996, Be released a version of the BeOS for Power Mac platforms. Power Computing, the Mac clone manufacturer, started bundling it with their Power Mac clones. Tests by Macintosh magazines showed the Power Computing clones ran faster and had fewer problems (crashes, "hang ups," etc.) when running BeOS instead of System 7 and its enhancements.

Whether Apple will license BeOS, and whether Apple will make changes to it, was still not finally decided at the time this was being written. However, the raw performance of the BeOS, coupled with its state-of-the-art multitasking and multimedia features, would make it a natural for the Macintosh. With no viable options of its own, the decision to license BeOS would seem like a no-brainer. I hope Apple has done so by the time you read this!

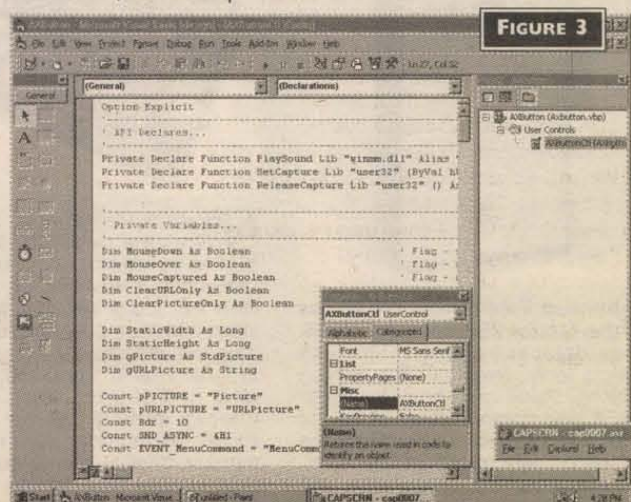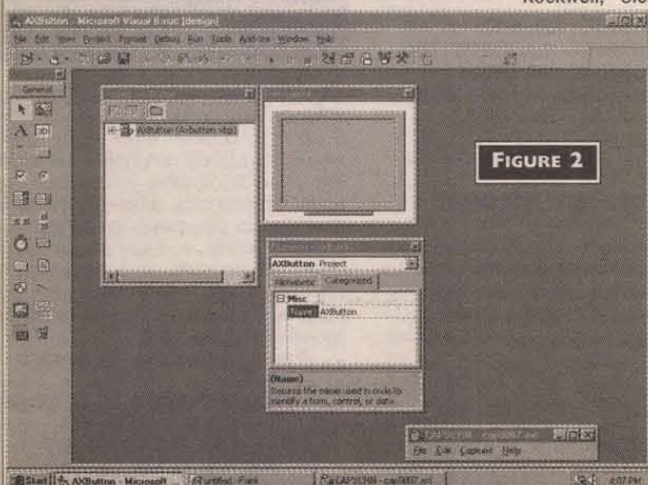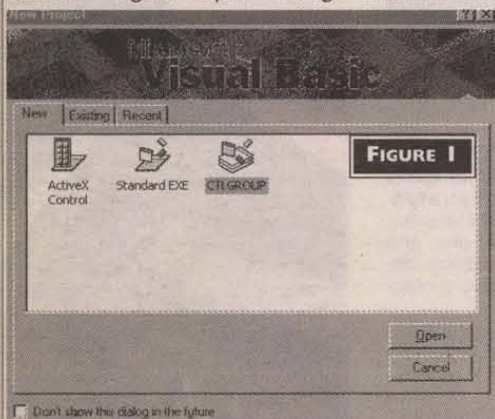you create stand-alone applications, ActiveX controls, and develop macros for a growing number of applications software. Add its ease of use and short learning curve to such versatility, and you get the feeling that Visual Basic will soon be the programming language to know for most technical professionals.



New Products

you to connect to a PC's keyboard port using either RS-232 or RS-485 interfaces, and still be able to use the existing keyboard. The Keyat is designed to aid software testing, allowing a test controller to simulate keyboard use without having to add any special software or communication hardware to the target computer system you are testing. The Keyat is addressable, and the RS-485 interface allows you to have one host computer control the testing of up to 58 target systems simultaneously.

You can send the Keyat ASCII, scan codes or keyboard codes. The Keyat can also monitor keyboard sessions for developing regression test data, or for detecting key combinations which are causing software problems. The compact unit (3.5"x2.2"x1.5") comes complete with manual and keyboard adapter cable.

For more information, contact:

L3 SYSTEMS
P.O. BOX 2954, DEPT. NV
REDMOND, WA 98053

COUNTERSURVEILLANCE DETECTION SYSTEM



Sheffield Electronics introduces the Model 262 countersurveillance detection system. This unit detects room, telephone/fax, pulsed tracking, video, and body transmitters. It also demodulates FM RF for voice verification. Other features include carrier-current and subcarrier demodulation, telephone line input, a high gain contact microphone amplifier, sensitivity control,

and a recording output jack.

For more information, contact:

SHEFFIELD ELECTRONICS
P.O. BOX 377940, DEPT. NV
CHICAGO, IL 60637-7940
312-324-2196

18-PIN MICROCONTROLLER




Microchip Technology, Inc. introduces the PIC16C715, an eight-bit one-time-programmable microcontroller for mixed-signal applications that are space constrained, highly complex, and feature intensive. The PIC16C715 brings affordable and accurate eight-bit analog-to-digital converter capabilities with 2048 words (2K x 14) of on-chip EPROM program memory and 128 bytes of RAM for data memory to applications requiring the execution of complex algorithms and control code.

For more information, contact:

**MICROCHIP TECHNOLOGY
INCORPORATED**
2355 W. CHANDLER BLVD.
DEPT. NV
CHANDLER, AZ 85224-6199
602-786-7200 FAX: 602-899-9210

40 MHZ DIRECT DIGITAL SYNTHESIZER

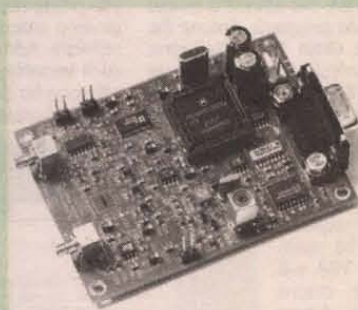

Novatech Instruments, Inc. introduces the model DDS6m direct digital synthesizer module. The DDS6m is a 40 MHz signal source on a 2.5" x 3.5" circuit board. It provides both sine and clock output signals simultaneously and is RS232 programmable from 100 Hz to 40 MHz in 0.025 Hz steps. The frequency setting can be saved in EEPROM memory so it returns to the saved value after a power interruption. The DDS6m has excellent spectral purity with a typical phase noise value being <125 dBc @ 1

KHz offset. The timebase is jumper selectable between an internal 5 ppm crystal oscillator or an external clock input. The phase of the output signal is programmable in 11.25 degree increments.

The DDS6m is available from stock at \$295.00 list.

For more information, contact:

NOVATECH INSTRUMENTS, INC.
1530 EASTLAKE AVE. EAST,
STE. 303, DEPT. NV
SEATTLE, WA 98102
206-322-1562 FAX: 206-328-6904
E-MAIL: novatech@eskimocom

PVC HEAT SHRINKABLE TUBING



Insul-Grip HS-105 heat shrinkable tubing is highly conformable and comes in sizes up to 4" OD that can be custom color matched to blend with surrounding substrates. Unaffected by chlorinated cleaners, most chemicals, gasoline, oils, and salt water, this UV stable tubing creates a smooth and attractive protective covering.

Insul-Grip HS-105 PVC heat shrinkable tubing is priced according to size, quantity, and color requirements.

For more information, contact:

INSULTAB, INC.
50 EVERBERG RD., DEPT. NV
WOBURN, MA 01801
1-800-468-4822, 617-935-0800
FAX: 617-935-0879

ELECTRONIC IMAGERS

Electrim Corporation announces the addition of two cameras to their solid-state electronic imagers. The new color model, the EDC-1000E permits the user to digitize an RGB color image at up to 652x494 pixels (with 24-bit color depth). The monochrome model, the EDC-1000N, provides 256 gray scales at 652x494 pixel resolution. Like their earlier versions of electronic imagers, the EDC-1000E and EDC-1000N are compact, digitally

controlled/digital output, television-like cameras.

The EDC-1000E and EDC-1000N use low noise (15 electrons per pixel) frame transfer CCD image sensors operating in non-interlaced (progressive scan) mode. Other features include: low dark current, anti-blooming, high photo response uniformity, 7.4µ square pixels, geometric fidelity, no dead space between pixels, computer controlled exposure time, computer control of gain and dark level, computer controlled sub-array scanning, asynchronous scanning (external triggering of frame reset and scan), and data collection rates of up to two megabytes per second.

Price of the EDC-1000E is \$900.00 and price of the EDC-1000N is \$800.00. All Electrim cameras include camera head, ISA interface card, cable, and software.

For more information, contact:

ELECTRIM CORPORATION
356 WALL ST., DEPT. NV
PRINCETON, NJ 08540
609-683-5546 FAX: 609-683-5882
1-800-683-5546
www: http://electrim.com

METAL STAMPINGS



A. J. Knott intricate metal stampings are produced in sizes from 0.005" to 0.060" thick with tolerances to ±.0005" on holes, depending upon thickness, and ±.003" on form dimensions. Manufactured in production volumes, parts can be supplied loose, reel-to-reel, on tape-and-reel, on strip, in tubes, and in thermoformed trays to accommodate a wide variety of automated assembly equipment.

For more information, contact:

A. J. KNOTT TOOL & MFG. CORP.
179 FORTUNE BLVD.
P.O. BOX 368, DEPT. NV
MILFORD, MA 01757
508-473-1234 FAX: 508-473-0824

Javanco

The Electronics "Five & Dime!"

40,000 FT² OF REAL BARGAINS

- | | | | |
|------------------------|--------------------------|----------------|--------------------|
| • computer parts | • diodes | • tie-wraps | • wire & cables |
| • misc software | • LEDs | • batteries | • obsolete parts |
| • TV/VCR service parts | • telephone parts & acc. | • fuses | • equipment racks |
| • ICs | • resistors | • crystals | • knobs & hardware |
| • sockets | • capacitors | • oscillators | • circuit boards |
| • tubes | • switches & relays | • fans, meters | • subassemblies |
| • transistors | • connectors | • speakers | • neat "junkie" |



We have one of the largest selections of common and "hard to find" integrated circuits available. Check out our huge inventory of new and used computer equipment. We offer quick turn-around order processing. Call us first for the best selection and lowest price!

Call or write
for a catalog

Orders only: 1-800-JAVANCO (528-2626)
(615) 244-4444
BBS: (615) 244-4445 Fax: (615) 244-4446
http://www.javanco.com



501 12th Avenue South - Nashville, TN 37203
Hours: 8:30a-5:30p CST M-F 9a-1p CST Sat

Write in 97 on Reader Service Card.

MISC. ELECTRONICS WANTED cont.

TESTERS WANTED: Immediate offers made for Ultrasonic, Magnetic Particle, Eddy Current, X-Ray and Borescopes, 24hrs. Leave detailed message with make/model. 1-800-530-3371.

WANTED: OLD, new, used, Western Electric, RCA, Telefunken, GE, Jan, McIntosh, Marantz, Dyna, Fisher, JBL, EV, Tannoy, Jensen, EMT, Thorens, Fairchild, Altec, Westrex: **TUBES,** speakers, amps, etc. Maury Corb, 713-728-4343, FAX 713-723-1301.

WANTED: ELECTRICAL materials, Allen-Bradley, Agastat, Appleton, Crouse-Hinds, T&B, Square D, Pyle National, Russel & Stoll, circuit breakers, fuses, connectors. Call Beiner Sales, 805-376-9044, FAX 805-376-8207.

WANTED: HIGHEST prices paid for Western Electric tubes and equipment, also wanted 2A3, 10, 45, 50, KT-66, KT-88, 5691, 5692, 6550(st), and Altec 604B/C speakers. Don Singerhouse, PO Box 768, Maywood, NJ 07607. Phone/Fax: 201-843-8682.

EXCESS INVENTORY WANTED: Transistors, semiconductors, capacitors, PC boards, & diodes. We buy it all! Contact: **SEMITECH, INC.,** 334 Cooper Road, Bldg. A., Berlin, NJ 08009. Phone 609-768-0030, FAX 609-768-5690.

WANTED: ALLEN Bradley/stackpole carbon composition resistors, 1/2W, 1W, & 2 watt. Any quantity. Contact Charlie 818-444-7079, FAX 818-444-6863.

MICROWAVE MIKE, the RF Plumber, needs waveguide, fixed and transportable microwave radios, and related hardware. Fax your available inventory to 609-875-7577 or Call 609-875-1189.

WANTED: ELECTRON tubes, ICs, semiconductors. Astral, PO Box 707NV, Linden, NJ 07036. Call 1-800-666-8467.

WANTED: GOOD TEKTRONIX 434. CALL DAVID, 415-567-8504.

I WANT it and I want it now. I want all of your SIMM memory. IBM, Mac, new, used, even defective. I want it all. Highest \$ paid. Now selling memory. We can beat any printed price in Nuts & Volts. Call 1-800-4-MEMORY now! Voice/FAX.



WANTED: EXCESS ELECTRONIC INVENTORIES, ICs, MEMORY, EPROMs, PALs, LEDs, CIRCUIT BOARDS, DIODES, AND TRANSISTORS. CALL ACTIVE MICRO, 310-494-4851 OR FAX 310-494-4913.

WANTED: BALANCING machines & vibration analyzing equipment manufactured by the following: Spectral Dynamics, Hofmann, Bentley Nevada, Schenck, IRD Mechanalysis, Gishott. Contact Mike Park at E.T. Balancing, 12823 Athens Way, Los Angeles, CA 90061. 310-538-9738, FAX: 310-538-8273.

WHOLESALE CABLE

COMPLETE LINE OF CABLE PRODUCTS

- ☒ Quality merchandise by brand name manufacturers
- ☒ Satisfaction guaranteed ☒ Free gift on first order
- ☒ Technical support
- ☒ 2 year warranty on new converters
- ☒ COD shipping & overnight shipping by request
- ☒ Experience where it counts ☒ Volume pricing

PLAIN CONVERTERS: ZENITH, OAK, PANASONIC, PIONEER, EAGLE, HAMLIN, STARGATE, PLUS MORE.

REMOTE CONTROLS: ALL MAJOR BRANDS, INCLUDING 2-4 FUNCTION UNIVERSAL REMOTES

WHOLESALE CABLE M-F 11am-6pm EST
(718) 262-0900 • FAX (718) 657-4015 • (718) 297-9221

No NY sales. Federal and local laws provide criminal and civil penalties for unauthorized use. Check with your cable providers for permission to use equipment. Must be paying for all services you receive. Order by model number only. Some equipment refurbished as new.



Tell us the
best price you
were offered,
where you got
it from, and
let us try to
beat it.

The Filter Company

Positive Notch Filters

Large STOCK on all Available Channels

2 thru 24, 95 thru 99

0, 1, 57, 58, 59, 60, 61, A1, A2, A3, A4, A5

ORDER BY SINGLE CHANNELS

We Specialize in Large Quantities on every Channel

PRICES AS LOW AS \$6.00EA

NOBODY BEATS OUR PRICES

Monday - Friday (8am to 5pm) Central Time

QUALITY METAL CYLINDER TYPE NON-TUNABLE

ABSOLUTELY NO DRIFTING PROBLEMS

Standard Positive Filters

1pc-\$16.00 5pcs-\$14.00 10pcs-\$12.00

25pcs-\$10.00 50pcs-\$8.00

Positive "G" Series Filters

1pc-\$30.00 5pcs-\$28.00 10pcs-\$25.00

Tom G. - FL Excellent Service, fast and quick. The only bad thing about this company is they don't sell Cable Boxes. We hope someday they will....

David P. - CA We called around for help on filters and nobody had any answers except one, call the "THE FILTER COMPANY" we did and had an answer in a matter of minutes....

John B. - IL Our company buys in the 100 quantities and needs a large selection of different channels. "The Filter Company" was the only one who was able to supply....

PHONE & FAX ORDERS:

1-800-235-8080

VISA, MASTERCARD
DISCOVER, UPS COD
CHECKS BY PHONE

Anyone implying theft of Cable
Service will be denied assistance
We do not sell Data Blockers,
Bullets or FM Traps !!!!



Give our 800 line a howl for the best
service in the Country.....!!!!

A "TFC" Company

PRINT T-SHIRTS FOR FUN OR PROFIT!

With your computer!



FAST, EASY with Heat Transfer Printer Ribbons!

1. Put Ribbon into your printer.
2. Print message or design onto regular paper but print it in a mirror image. (Print Shop and other programs have this capability.)
3. Place paper face down on T-shirt and iron the back of paper to transfer the image.

Available in red, green, blue, or black at \$10.95 each for the following printers (specify make and colors wanted):
Panasonic 1080/1180/1090/1190/1123/1124; IBM
Proprinter, Epson MX/FX/RX 80/85/86/LX800/
LQ500/LQ510/LQ570/L1000; Star NX/NL NP10;
Sokosha SP800/1000; Tandy DMP130; Apple
ImageWriter, Citizen 120D/180D/GS140; Okidata
182/192/320.

\$11.95 each for Epson MX/FX-100/286, LQ1000/
1050, LQ2500/2550/EX800/1000/LQ860, AP3250/
LQ100 Star NX1020/2400/2410/2415/2420,
Panasonic KX-P 2180/2123/2124/1624/1524,
Toshiba P321/351/1340. \$5.95 each for Okidata 82/
92/83/93, Gemini 10X/15X.

Available in BLACK only at \$10.95 each for Star
NX1000, NEC P2200, Commodore MPS-801.

Available in 4-Color Heat Transfer for ImageWriter II,
\$12.95; Star NX1000 \$14.95; Star NX1020 \$23.95;
Star NX2420 \$23.95; Star NX2450 \$23.95; Citizen
GSX-140 \$23.95; Epson LQ2500/2550/EX800/1000
\$16.95; Fujitsu DX2100/2200/2300/DL 3300/3400/
3600 \$27.95; Panasonic KX-P 2180/2123/2124
\$23.95.

HEAT TRANSFER MARKING PENS

Add colors to the computerized design or use alone.
Set/5 Colors (red, orange, yellow, green, blue) wide pens
\$15.00, narrow pens \$14.00.

HARD-TO-GET PRINTER RIBBONS

Gorilla Banana, Commodore 1525 \$8.00; Adam
Coleco \$12.00; TI-850/855 \$6.00; Centronics 700
Zip Pack \$5.00; C. Itoh Prowriter Jr., Riteman
C+/F+ \$6.00; Riteman Infomunner \$8.00;
Commodore MPS-801 \$5.00; MPS 803 \$5.00;
Decwriter LA30/36 \$4.00; Apple Scribe \$4.00;
Mannisman Tally Spirit 80, Commodore 1526
\$5.00; Epson JX-80 4-Color \$14.00. Printronix
P-1013 \$11.00.

Over 200 different ribbons in stock. All ribbons new, not re-
linked. Fully guaranteed. Order directly or send SASE for
complete list.

Add \$2.00 per order shipping. California residents add 7.75% sales
tax. On ribbon orders over \$30.00 deduct 10% discount.


H.T. ORR Computer Supplies
249 Juanita Way, Placentia, CA 92670

714-528-9822
800-377-2023
FAX **714-993-6216**

<http://www.extremepay.com/accamp/orr.htm>

Write in 211 on Reader Service Card.

STEPPER MOTOR CONTROLLER

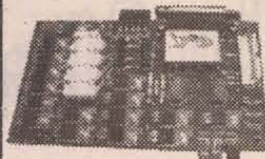

ADDRESSABLE STEPPER MOTOR
CONTROLLER: JWP1X-1A

\$199.95

NON-ADDRESSABLE STEPPER
CONTROLLER KIT: RENIX-1A

\$29.95

Controls up to 4 unipolar stepper motors per
controller with 8 digital inputs with a throughput
of 500k bytes / sec. Up to 256 Controllers can
be stacked on a single parallel port.

Can be used for the following tasks:

- CNC Conversion
- Telescope Guidance
- Robotics
- Manufacturing
- Positioning Platforms
- Animatronics

PARAMAX INC.
1 (800) 473-8080

Write in 31 on Reader Service Card.

DIGITAL I/O CONTROLLER



ADDRESSABLE DIGITAL I/O
CONTROLLER: JWP1X-3

\$179.95

NON-ADDRESSABLE DIGITAL
I/O KIT: RENIX-3

\$29.95

8 Bit Digital I/O controller, 8 buffered digital
outputs and 8 buffered digital inputs that function
at 500k bytes / second. Up to 256 Controllers
can be stacked per parallel port.

Can be used for the following tasks:

- Robotics
- Automated Manufacturing
- Animatronics
- Controlling Solenoids
- Servos
- Digital Prototyping

<http://www.digitalage.com/VM/Paramax>

Paramax products also available through:
FORD Electronics: (714) 521-8080

PARTS - PARTS - PARTS

65.8 mHz Saw Filters	100 pcs. - \$2.40@	300 pcs. - \$2.00@	600 pcs. - \$1.75@
18 Pin IC Sockets	500 pcs. - \$.09@	1,000 pcs. - \$.07@	5,000 pcs. - \$.05@
18VAC, 300mA, Wall Transformers (Perfect for Stealth Units)	50 pcs. - \$3.00@	100 pcs. - \$2.50@	250 pcs. - \$2.00@
4 Mhz Resonators, 3 pins	100 pcs. - \$.50@	500 pcs. - \$.45@	1,000 pcs. - \$.41@
8 Mhz Crystals, 2 pins	100 pcs. - \$.50@	500 pcs. - \$.45@	1,000 pcs. - \$.41@
24 Mhz Crystals, 2 pins	100 pcs. - \$.60@	500 pcs. - \$.55@	1,000 pcs. - \$.49@
Micro-Chip Pic-16C54RC	100 pcs. - \$2.10@	250 pcs. - \$1.95@	500 pcs. - \$1.85@
Micro-Chip Pic-16C56RC	100 pcs. - \$2.30@	250 pcs. - \$2.25@	500 pcs. - \$2.15@

Call for Larger Quantity Quotes



E-Mail: sales@capital-elec.com

Web: <http://www.capital-elec.com>

Phone: (630) 350-9510

Fax: (630) 350-9760

BBS: (630) 350-9761

852 Foster Avenue
Bensenville, Illinois 60106

WE ACCEPT



Write in 26 on Reader Service Card.

HELP! I'M looking for a pager-monitored
household alarm capable of dialing 6 different
zone-correspondent numbers to my pager.
910-313-0029, leave a message. Dan.

WANTED: OLD transistor (bipolar) data
books 1965-1975, Motorola, GE, Texas Inst.
(single copier). Call Ray 508-683-1830
Methuen, MA.

WANTED: TUBE HiFi, Tube theater/commer-
cial amps, speakers etc. Corner
speakers/coaxials/triaxials. Old guitars & guitar
amps. Altec, McIntosh, Marantz, Western
Electric, Scott, Fisher, Dynaco, Electrovoice,
Jensen, Gibson, Fender, Vox etc. Sonny
Goldson, 1413 Magnolia Ln., Midwest City,
OK 73110. 405-737-3312. FAX 405-737-
3355.

WANTED: TUBES, radios, transmitters,
receivers, gyros, bearings, connectors,
relays, lamps, synchros. Hyness Company,
709B Delair Road, Cranbury, NJ 08512-4212.
Phone: 609-395-1116, FAX 609-395-1117.

1/2-INCH BETAMAX VCR player or
player/recorder in totally working condition.
Can pick-up in Washington DC/Baltimore
area. 301-464-8513. State price, including
shipping.

NEED SPECS on UTC CG-302 xfmr, want
info on class "A" triode "Heising" modulator.
Write to: Fred Fabishak, 8230 W. Grand
Ave., River Grove, IL 60171. Thanks for all
14 letters on "56" handbook.

Z-METER WANTED. Looking for a Sencore
LC75 Z-meter, working or not. Just so it's
intact. Call 601-335-7805 about noon CST.

DEC EQUIPMENT WANTED!!! We are buy-
ing DEC systems, boards, terminals, drives
and peripherals. Also Scientific Micro
Systems (SMS), DSD, Datability, Dialog, other
DEC compatibles, and Computer Output
Microfilm (COM) units. Please call for a quote
or fax us your equipment list. We buy, sell,
and trade. **KEYWAYS, INC.**, 513-847-2300
OR fax 513-847-2350.

BBS & ONLINE SERVICES

SIMPLE INTERNET PUBLISHING! No com-
puter needed. Send \$19.95 for kit to:
NetPlace, PO Box 700309, San Jose, CA
95170. Price includes your original designed
page on the Internet for a year! 1-888-NET-
PLACE (toll-free).

SHARE REPAIR. E-Mail tech support for TV-
VCR technicians. For information, E-Mail:
rhett@dump.com

EDUCATION

LEARN PC ASSEMBLY LANGUAGE. Disk
\$5, book \$15, assembler \$5. ZIPFAST, Box
12238, Lexington, KY 40581-2238.

ESP, BIOELECTRICITY, microwave hearing
introduction comprehensive booklet \$1.
Research Associates, PO Box 3583, Boynton
Beach, FL 33424-3583.



Zenith ST1000's
\$25.00

Also available:

SA-8550 SA-8580 SA-8590

DPV-5 DPV-7 DPBB-7

Pioneers, Basics & more!

Check out our new web site @
<http://www.kableworks.com>

All ZTACS available including 1600's - All converters are unmodified



Write in 199 on Reader Service Card.

WHY IS THE COMPETITION SHAKING?

BECAUSE **1 • 800 • 4 • MEMORY** IS HERE
"WE CAN BEAT ANY PRICE IN NUTS & VOLTS"

WE SELL/BUY ALL MEMORY SIMMS • DIMMS • NOTEBOOKS • MODULES

- LIFETIME WARRANTY
 - FREE TECH SUPPORT
 - NO CREDIT CARD SURCHARGE
 - NO RESTOCKING FEE
 - MOST ORDERS PROCESSED SAME DAY
 - TRADE YOUR OLD MEMORY FOR CASH OR NEW MEMORY
 - WE EVEN BUY BROKEN MEMORY
- CALL AROUND THEN CALL US
WHAT MORE COULD YOU WANT!!**

1-800-4-MEMORY 908-238-2300
FAX: 908-238-4404
Trade-ins accepted too!

Write in 83 on Reader Service Card.

DON LANCASTER'S ACTIVE FILTER COOKBOOK is back in print. Autographed copies of the seventeenth(!) classic printing \$28.50. **SYNERGETICS PRESS**, Box 809-N, Thatcher, AZ 85552. 520-428-4073. VISA/MC.

START YOUR OWN TECHNICAL VENTURE! Don Lancaster's newly updated **INCREDIBLE SECRET MONEY MACHINE II** tells how. We now have autographed copies of the Guru's underground classic for \$18.50. **Synergetics Press**, Box 809-K, Thatcher, AZ 85552. 520-428-4073. VISA/MC.

KNOWLEDGE CARDS. Facts and formulae from math, English, science, and electronics. Fun and educational. For elementary school thru college. Box 12238, Lexington, KY 40581-2238.

BUSINESS OPPORTUNITIES

THE CASE AGAINST PATENTS. Thoroughly tested and proven alternatives that work in the real world, \$28.50. **SYNERGETICS PRESS**, Box 809-N, Thatcher, AZ 85552. 520-428-4073. VISA/MC.

RECOVER "SCRAP GOLD" from old computer junk. Free information packet. Call 24 hours: 603-645-4772.

RECOVER PURE GOLD from old electronic junk and broken scrap jewelry. Free information! Just dial 403-425-6049 from your fax machine to my fax-on-demand and retrieve document #27.

memory monitors cpus hard drives motherboards cases
multimedia scanners mouses video cards desktop systems

CHOOSE FROM 30,000 ITEMS AT UNBEATABLE PRICES!

Order via the InterNet at: <http://www.apcn.com>



Order Toll Free: (800)878-1701

Inside Florida: (305)883-9133

Credit Cards,
Gov. & Corp.
PO's Accepted

- CUSTOM BUILT DESKTOP COMPUTERS
- MONTHLY SPECIALS ON OUR WEB SITE

Acer AMD Artec APC Adaptec AMI AT&T ATI Boca Brother
BusLogic Canon CNet 3Com Citizen CreativeLabs Diamond
Dlink DPT Epson HP IBM Intel Iomega Keytronics Kingston
Kodak Labtec Soyo MAG Micropolis Motorola NEC Okidata
Panasonic Phillips Pinnacle Pioneer Microsoft Cyrix Quantum
Samsung Seagate Sony Toshiba Western Digital US Robotics

APC net - 4471 NW 36 ST. Suite 110 - Miami Springs, Florida 33166 - Fax: (305)883-9152

Write in 159 on Reader Service Card.

HOME AUTOMATION DEALERS WANTED. Free information. Call 1-800-838-4051 or fax name, address, and telephone to 402-729-3863.

DID YOU know Chaffin Electronics offers: Programming service, circuit board manufacturing, thousands of obsolete and hard to find ICs, same day shipping, computerized parts search? Call for more information. Phone: 614-574-4456 or 6906, FAX: 614-574-2124.

START YOUR OWN TECHNICAL VENTURE! Don Lancaster's newly updated **INCREDIBLE SECRET MONEY MACHINE II** tells how. We now have autographed copies of the Guru's underground classic for \$18.50. **Synergetics Press**, Box 809-K, Thatcher, AZ 85552. 520-428-4073. VISA/MC.

GOLD! EXTRACTION, recovery and refining gold from scrap electronics. Book contains chemical formula and process \$35. Strategic Technology, Box 145-V, Newville, AL 36353.

MILITARY COMPONENTS wanted. Capacitors, resistors, diodes, transistors, semiconductors, ICs. Electronic Material Industries, 818-842-5953, FAX: 818-845-3613.

HOLDER OF US Patent #4,797,671 (Motor Vehicle Locator System) wishes to license or sell technology. System is of relatively simple design and is NOT GPS-based. Call 518-356-1879 for details.

Check out the Nuts & Volts Web Site!
<http://www.nutsvolts.com>

THIEFBUG


Protect your Electronic Equipment from Theft

Hi-Tech Protection for Computers (PCs, Notebooks, Laptops) TVs, VCRs, Fax Machines, Lab Equipment, etc.

United States Patent No. 4,328,482 British Patent No. 2,008,299 Canadian Patent No. 1,128,162

Thiefbug, Model TX-BUG1

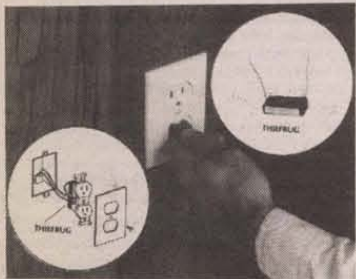Protection against the theft of Electronic Equipment that is plugged into an electrical power outlet. One Thiefbug is required for each item protected.



The Thiefbug is concealed in the electrical outlet box, where it cannot be seen or detected. Installation is easy, all you need is a screwdriver. Instructions are included.

The Thiefbug is automatically Armed when an item is plugged into the socket, then, it cannot be disconnected (unplugged or cord cut) without tripping the Thiefbug. If it is disconnected, the Thiefbug sends a signal, that identifies its location, over the electrical power wiring where it can be monitored at remote locations by a variety of Receivers, both plug in and concealed. The location code is selected by a DIP switch.\$59.00

Plug-in Receiver Modules

When the Thiefbug or other Transmitter is tripped, the Alarm signal is available at every outlet in every house in the neighborhood (8 to 10 houses), and every outlet in an Apartment or Condo complex regardless of size. You can plug-in as many Receiver Modules, and in as many places as you like. Each Module has a DIP switch for Code selection.

Buzzer Module, Model RX-BZM

Loud "Beeping" (90db) Output when Alarm Signal is received. Example: Plug-in at Neighbors house or apartment (Buddy system).



....\$49.00

Contact Closure Module, Model RX-CCO

Relay Output (Form C, NO-C-NC), that switch when Alarm Signal is received. Example: Use to tie into an Alarm Panel or Phone Dialer.



....\$49.00

Remote Alarm Module, Model RX-RAM

120 VAC, 600 watt Socket that switches ON when Alarm signal is received. Example: Use to sound a Siren, Horn, or Strobe.




....\$49.00

- For use in Homes, Apartments, Offices, Hotels/Motels, Industrial Facilities, Hospitals, Schools, Institutions, Retail Store Displays, etc., one building or several, without the expense of new wiring, and the added flexibility of plug-in Modules. For a starter you need at least one Thiefbug and one or more Receivers.
- Add Additional Modules to the System and: Protect Electronic Equipment against Theft; Monitor doors and windows for intrusion; Signal Fire, Panic, or Medical Emergencies, all integrated into one system that can Monitor and Annunciate up to 1000 locations. Product Catalog and Applications Guide free with your order, or send \$5.00. If you have questions, just call or fax. Dealers Inquiries Invited.

CEPCO, 9540 Owensmouth Ave.
P. O. Box 5377, Chatsworth, CA 91313
Phone (818) 998-8569 Fax (818) 998-8560

Money Back Guarantee

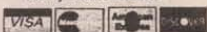

Add \$5.00 Shipping and Handling

MO-TECH DISTRIBUTORS YOUR MIDWEST PANASONIC CONVERTER WHOLESALE

PANASONIC

10 PC 20 PC 50 PC

TZPC1453G2 \$63- \$61- \$59-

"Top of the line converter" featuring sleep timer, parental lock, standard/HRC switchable, last channel recall, favorite channel memory, and 83 channel capable.

TZPC1003 \$49- \$44- \$42-

One of our best selling converters featuring sleep timer, parental lock, last channel recall, favorite channel memory, and 80 channel capability.

TZPC175DG2 \$89- \$85- \$82-


Our "Top of the line" converter with volume control. Featuring sleep timer standard/HRC switchable, parental lock, last channel recall, favorite channel memory, and 83 channel capable.

PHONE (810) 566-7262
FAX (810) 566-7253

RESOURCES UN-LTD.

SONY, PICTURE/TEL 450Line, 8X, NTSC & Y/C OUT COLOR VIDEO CONFERENCE CAMERA,

Serial Control of all functions: Pan, Tilt, Zoom, Auto Iris Auto Focus. Like having your own R2D2! They were intended for high end use in fortune 500 board rooms. The video performance is absolutely stunning. Superior to almost anything we have seen. The camera and lens is an integral assembly. Excellent Condition. Rugged black ABS enclosure with mini-DIN and RJ-11 I/O. Size: 8" x 6" x 5" H. Sorry, we have no data on using the serial port. The units sell fast on power up and the video is active. 1993 price over \$4K. We will provide a swell gift to the first person to tell us what the serial commands are? Do you think you can? **PRICE..\$299ea.**

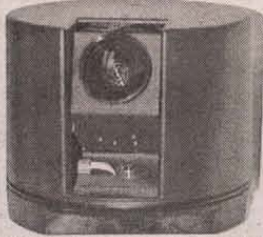

MOTORIZED SLIDE with MICRON (.000040") RESOLUTION, LINEAR OPTICAL ENC. 10" travel, dual THK slides, flex coupled, Pittman 30VDC gearmotor. This is one of the nicest units we have ever seen. Usa two for a superior X-Y table. Overall dimensions: 12" x 22" x 2.5" Heavy 15lb. cast and machined aluminum base/table. Dual optical limit sensors. Encoder: DRC model LB4A-0270-EN, 50LP/mm basic res. Internal 5X multiplication! Diff. TTL outputs, 5VDC pwr., 10.6" trav. Assembly Cost ~\$1800, the encoder alone is \$470!
OUR PRICE..\$229ea, 2for \$399



SECRET SIGNAL SYSTEM!

MINI IR Flasher

can identify friend or foe when observed with CCD camera or night vision. NEW, keychain fob sized unit, 1.5" diam x 0.5" T made by polaroid for triggering camera remotely. The 810nm, IR LED is powered by an internal COB circuit and button cell. (supplied) **4/55 or 20/\$20**



SEE in TOTAL DARKNESS!

IR FLOOD has 168 LED's!!

Powerful, not power hungry. Projects up to 20 meters. 24V wall adap., incl. Size: 4.5" Wx6.6" Hx1.5" d. Commercially made and BRAND NEW! IR FLOOD....\$159ea.



**ATTENTION ADVERTISERS
DID ATECH SYSTEMS GET YOU?
GET EVEN....call 800-810-4070**

VIDEO TRANSMITTER, WORLDS SMALLEST!

Crystal controlled, 100mW, Transmits up to 2000 ft. line of sight. Super small module shown next to my watch size: 1.15" x 0.8" x 0.4" Operates with super clarity for color or B&W on Chan. 59 (cable). We provide all accessories. UHF Bow-Tie antenna for TV with F-adaptor, balun and 3ft. cable.



TVX100 with accy's. \$199. ea
TVX100 w/pinhole cam. \$299. complete.

TIME for a COVERT CAMERA ?

Nine Models Available. All New.

(Disguised cameras per model H. specs.)


- A. CLOCK CAMERA, Functional wall clock. 9" diam. Black or White available.
- B. THERMOSTAT CAMERA, Non functional thermostat with pinhole camera. Beige color.
- C. MOTION DETECTOR CAMERA, Non functional motion detector with camera. Beige color.
- D. SMOKE DETECTOR CAMERA, Non functional detector w/pinhole camera. A, B, C or D\$169ea.
- E. PIR FLOODLIGHT, functional dual flood with passive IR light control and internal camera. Mounts to Std box. Dark grey color.
- F. EXIT SIGN CAMERA, Functional, lighted, two sided with pinhole camera. E or F\$189ea.

G. IR CAMERA, See in Total Darkness or
H. PINHOLE CAMERA, See through a 1/8" hole!
High performance micro cameras. The B. model has 92° FOV. The C. model has a 72° FOV. Both provide 410 Lines res., 0.1Lux sens. AGC and Electronic shutter. Power: 12VDC @ 100mA operation, 225mA for the IR model, 6 IR LED's illuminated. Invisible 780nm. Infrared LED's allow observation in total darkness up to 20 feet. Perfect for garage, front door, or dark hallway. Both are 1.75" square and utilize SONY CCD and video chipset. First quality throughout.

G or H\$119ea.
Enclosure for G or H,\$14.95

J. MINI SUPER SENSITIVE, C-mount. GM-410, B&W, Size: 38mm SQ. x 40mm D. 1/3", 410 Lines, Sens. 0.05 LUX, AGC & Electronic shutter. Pwr. 12V @ 110mA. Optional lenses exploit the superior performance. IR SENSITIVE, RCA video conn., DC pwr. jack. Performance not hype! Will out-perform ANY camera in this magazine guaranteed!

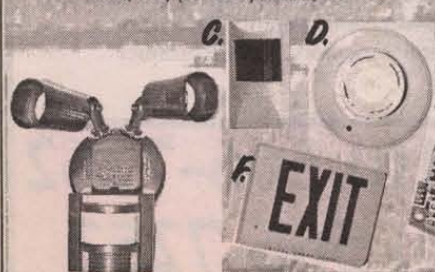J. less lens lens.....\$179
16mm, f1.6, (15° FOV).....\$210
8mm, f1.3, (30° FOV).....\$229
4mm, f1.4, (56° FOV).....\$229



FANTASTIC LASER LIGHT SHOW SYSTEM,

Operates with Internal or External Laser! The versatile Beamscan system requires no external PC. The processor is built-in. The beam scan is controlled using an integral twenty key touchpad and backlit 2X16 LCD display. The user can create simple or complex patterns with a few keystrokes. Beam effect sequences are played back for a user programmable position and duration. Events may be triggered by external audio. Over 80 patterns and 15 beam effects are pre programmed. Three line level inputs, 4 oscillators, envelope generator, user name for custom input sequences, 8K NV-EEPROM. Virtually plug and play operation. One year warranty.

Model GM-XYPN without internal laser \$649
Model GM-XYPY, with 5mW HeNe Laser \$849
Model GM-SHXYP 2nd Scanner \$229

MILITARY INFRARED RANGE FINDER SYSTEM! NOW HALF PRICE!

Cubitape model DM-60 IR based optical distance measuring system offers precise measurement up to 2000M or 6000FT. with resolution of .001m and repeatability of .01M. (less than 1/2") Reading displayed on 8 digit LED display. Accessories include, New 12VDC gel cell pack with charger, DC pwr cable, triple retroreflector target (required for use). Transit cases for laser and reflector. Operating instruction card. Complete technical manual with schematics. You test them and save. These cost Uncle Sam a bundle.
OUR PRICE Untested.....2 for \$349.00



**holidays
have you
a little
OFF the WALL?**

We have tested them all and offer only the best laser pointers. Selected for style, power & reliability. All use 650nm or 635nm lasers. 5X to 10X BRIGHTER than 670nm, with better beam quality! Pointers that perform as well as they look.

- A. The brightest laser pointer available. 635nm pen style with satin nickel finish. Long range (800 yard) capability. Operates from 2 AAA batteries supplied. Gift boxed.
- B. A truly classic and functional laser and pen. This "MONT BLANC" style body has the substantial feel and distinctive look of a powerful, (400 yard range) 650nm laser inside! Aluminum and brass with a black lacquered finish and gold accents. Operated via a faux diamond on the side of the cap! Operates from SR44 batteries provided. Gift boxed. You will love it.
- C. An exclusive compact design with 400 yard range. Very unobtrusive and comfortable in the hand. Size only 2 1/2" Long. 3 SR44's provided.
- D. Lab style with X-Y adj. set screws, on/pa switch, CR123A included. A....\$89ea. B....\$59ea. C....\$45ea. D-50 650nm \$69ea. D-35 635nm \$109ea

CO2, 120Watt CW, SEALED GLASS LASER HEADS

Integral Hard Sealed Mirrors, Factory Refurbished. High quality water cooled heads. Were originally designed for medical application. All models are similar in construction. Size of the model 103: 60" L x 3.2" diam. Model 160: 44" L x 3.2" diam. Model 135: 35" L x 3.2" diam. Power requirement, model 103, 40KV trigger with 25KV @ 10 to 30ma operating current. Model 160 and 135, 30KV trigger with 15-20KV @ 7 to 20mA operating current. These are not toys. They must conform to Class IV CDRH regulations when assembled into a functioning system. Perfect for engraving, cutting and drilling most materials. Only three available. We don't expect any more when these are gone. **120Watts \$1475ea., 60Watts \$1095ea., 35Watts \$895ea.**


NEW! PASSIVE INFRARED MOTION SENSORS Commercial quality at distributor prices. The latest dual element pyroelectric technology from the leading manufacturer. Two models to choose from. Both with pulse counting, anti false circuit, temperature compensation, high RF noise immunity, adjustable pulse count, internal tamper switch, LED "walk test" and adjustable angle of view. Operates from 9-16VDC @ 15mA. Alarm and tamper contacts N.C. The model 7000 provides 90° FOV detects up to 90ft. Can be wall or corner mounted. "Zodiak" model provides 108° FOV detects up to 50ft. Includes an integral universal swivel mount. Both are cream color.

TYPE 7000, 24.95ea. 3 for \$59

TYPE ZODIAK, 19.95ea. 3 for \$49

TEK 7104, 1GHz, MICRO CHANNEL PLATE CRT

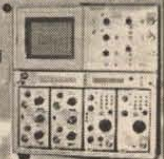Has the highest bandwidth and highest writing speed, unsurpassed single shot capability, trace brightness 1000x brighter than conventional CRT. 350ps risetime! 200 ps per division fastest calibrated sweep rate. Includes two 7A29 1GHz vertical amplifiers, one 7B10 and one 7B15 horizontal amplifiers. Complete operating manual, warranty, 1991 price over \$45K **OUR PRICE...\$2995**



**THE QUALITY YOU DESERVE
PRICES YOU CAN AFFORD**

VISA, MC, AMEX, DISCOVER, COD.
ORDERS: 800-810-4070, TECH. LINE: 603-668-2499
FAX: 644-7825, E-Mail: unlfda4u@tiac.net
8030 So. Willow St., Bldg. 2, Manchester, NH 03109



Don't Lose Your Head over these PLANTRONICS BOOM MIC HEADSETS
Single ear with over the head metal band for comfort. New, boxed with RJ11 style plug attached to 6ft. cable with clothing clip. Grey. **14.95 or 2/\$25**



Doing the Numbers — Or Distributing Saltwater Taffy?

"He uses statistics as a drunken man uses a lamp post — for support rather than illumination."

— Andrew Lang

One of the things I enjoy doing every year is judging science fairs. I volunteer for one high school, two middle school (which we called "Junior High School" when I was a kid), and one area-wide (multi-school) fair. Over the 10 years that I have done this chore, there has been a noticeable decline in the ability of students — not all, but all too many — in analyzing and presenting data. And that touches one of my pet peeves.

When I see a person (whether a kid or not), who uses a voltmeter to find a potential of $V = 4.56$ volts, and a current of $I = 126$ mA (0.126 A), the calculated resistance $R = V/I$ is not 36.19047619 ohms! I don't care what your calculator or improperly written BASIC computer program says, the correct answer is "36" or — if you have particularly good meters — maybe "36.2"... but certainly not 36.19047619. Good analysis of data is critical.

Analyzing Test & Measurement Data

Data that is not analyzed is a bit like bread that hasn't risen: all the ingredients are there, but somehow it isn't quite the same loaf. One of Reid's Rules is that no data should be collected without analysis. Unfortunately, the analysis step is all too often overlooked.

One reason for bypassing the analysis function is that people frequently don't know how to analyze numerical data. That problem is easily rectified by knowledge. But there is another problem that is less easy to deal with. Many people are, by their nature, action oriented, while many others are more reflective. A story borrowed from the medical world (where it highlights the difference between surgeons and internists):

A Surgeon and an Internist were out hunting quail. A bird flew up from cover, and the Surgeon shouts: "Quick! Shoot it ... it's a quail!" The Internist retorts: "No, first rule out dove and pheasant!"

Why Analysis?

Numbers have meaning, and when properly collected data contains information that you need to do your job, they have a critical meaning. That information isn't always on the surface, and may not jump out at you until the data are analyzed, patterns noted, and exceptions explained. Analysis is the art of breaking something apart, looking at the constituent pieces, and then reassembling them into a whole that is better understood.

Analyze ALL of the Data

Data analysis need not be complex, but it must be complete. On January 28, 1986, that came into violent focus as the space shuttle Challenger exploded a little more than a

minute into its lift-off flight, killing all seven people aboard. Subsequent investigation revealed the cause of the accident was failure of the "O" ring seals on one of the two solid fuel booster rockets.

It is now known that the seals have a high probability of failure at cold temperatures; the temperature prior to launch was only 36° F. The question that had to be asked was whether or not the facts were known — or should have been known — prior to the accident. According to the findings of the Commission empaneled to investigate the accident:

"The managers compared as a function of temperature of the flights for which thermal distress of O-rings had been observed [author's note — see Figure 1] — not the frequency of occurrence based on all flights [Figure 2]. In such a comparison, there is nothing irregular in the distribution of O-ring "distress" over the spectrum of joint temperatures at launch between 53° F and 75° F. When the entire history of flight experience is considered, including 'normal' flights with no erosion or blow-by, the comparison is substantially different [Figure 2].

"This comparison of flight history indicates that only three incidents of O-ring thermal distress occurred out of 20 flights with O-ring temperatures at 66° F or above, whereas all four flights with O-ring temperatures at 63° F or below experienced thermal distress.

"Consideration of the entire launch temperature history indicates that the probability of O-ring distress is increased to almost a certainty if the temperature is less than 65° F."

Disaster could have been prevented by correct data analysis.

Without proper data analysis, and possibly succumbing to program and political pressures, the managers responsible for flight readiness

certification used a probability of failure of 1-in-100,000. There was no provable basis for this figure. It was probably only a hunch or guess based on the experience of the managers (unless it was made up). That incident shows the folly of using experience rather than data as a guide.

The engineers, by the way, using real data accumulated on both the shuttle launches and more than 1,500 US Army launches of a similar design calculated a 1-in-55 to 1-in-70 probability of mishap ... a much riskier assessment. The 1-in-100,000 number was used, without analysis or basis in reality, and the result was tragedy. Where did that 100,000 figure come from? Whether it was simply made up, or guessed at, it was none the less little more than a PFA (plucked from air) estimate.

An incident in the investigation showed the folly of dismissing the concerns of the technical people. An engineer who reported the dismal prospects of 1-in-55 was sarcastically told to "... put on your management hat ...", implying that he should accept the 1-in-100,000 and go with the launch decision. One of the Commissioners investigating the accident remarked something to the effect: "Asking an engineer to 'put on his management hat' is usually tantamount to an invitation to commit malpractice."

The lesson to take away from the Challenger accident is that numbers have meaning. Properly collected and analyzed data would have revealed the weakness, and made it possible to make a correct flight decision. But, by examining only part of the data, and using PFA probabilities, seven lives were lost and the US space program was set back many, many months.

Open Channel

by Joseph J. Carr
K4IPV

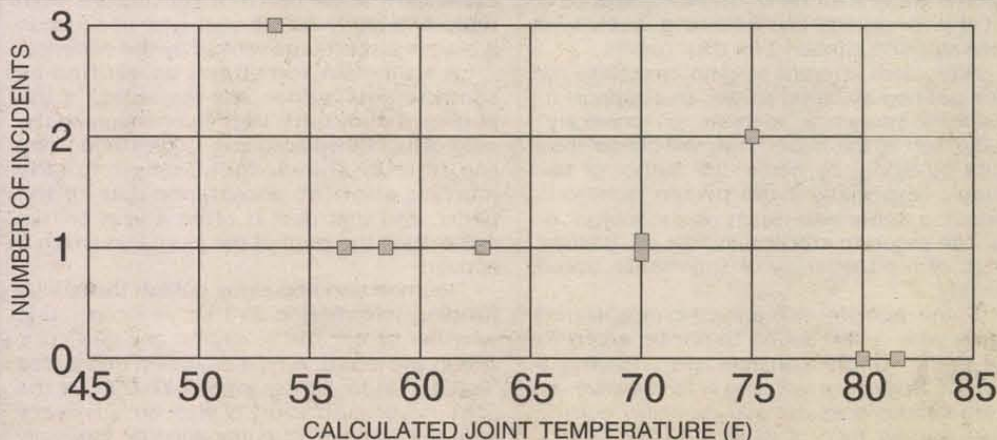


Figure 1
Data that was analyzed.

■ INDIVIDUAL FLIGHTS

Open Channel

Is Saltwater Taffy Being Distributed?

Advocates for causes want you to accept their point of view. Otherwise, you cannot be persuaded to their way of thinking. The tendency — and temptation — is for strong advocates to overinterpret favorable data, and either underinterpret or suppress unfavorable data. How do you separate trash from treasure? How do you detect whether the offered food is nutritious, or merely saltwater taffy? Several tactics help shed light on the truth.

First, ask who is supplying the information. There are advocacy groups that put out information to support or refute a position on controversial issues. When dealing with the northwest timber issue, for example, one finds opinions on both sides. Both sets of opinions are based on facts and supported by extensive studies, but they reach contradictory conclusions.

Both the lumber industry and the environmentalists have truth and beauty on their side, according to their own estimation. The sad fact is that both are equally suspect. Leaving out the possibility of fraud and deceit, most people are biased in one way or another. And those biases tend to color the interpretation of facts, affect which facts are put into play, and decide which studies are declared valid and which are not. And when you crank in the possibility of outright deceit — rooted in an "ends justify the means" ethic — the situation becomes even murkier.

Newspapers and magazines often misinterpret studies. While some of them are guilty of blatant advocacy, they are also afflicted by three pressures that force distortion: deadlines, the need to "scoop" the competition, and the fact that startling results "sell" better than the truth. Add to that the fact that journalists are rarely competent to interpret scholarly work, and the result is bad information being presented to the public. No one should accept popular media articles on any subject without independent verification.

Verification doesn't mean seeing the same material in two or more different media sources. Journalists often pick-up stories from other publications. Seeing the same material in three publications could mean that one reporter wrote it for his or her newspaper (and got it wrong), and the following week, two more reporters cribbed it for their papers.

Advocates attempt to gain credibility for their position by citing studies that support it. And if the study is a "scientific" or "university" study, then all the better. They will bolster their point by citing, by name, the author of the study ... especially if the person quoted is famous, a well-known expert on the subject, or has the requisite credentials. "Dr. M. Weldon Smith of the University of Smyrnville stated recently ..."

Some people cite a well-credentialed expert who is later found to not be expert in the matter under consideration. Having a doctoral degree, or winning a Nobel Prize, or being famous does not add credibility outside one's narrow field of expertise. Tom Clancy may be a real good military yarn spinner, but that does not qualify him as a military affairs expert.

When a study is cited by an advocate, it is

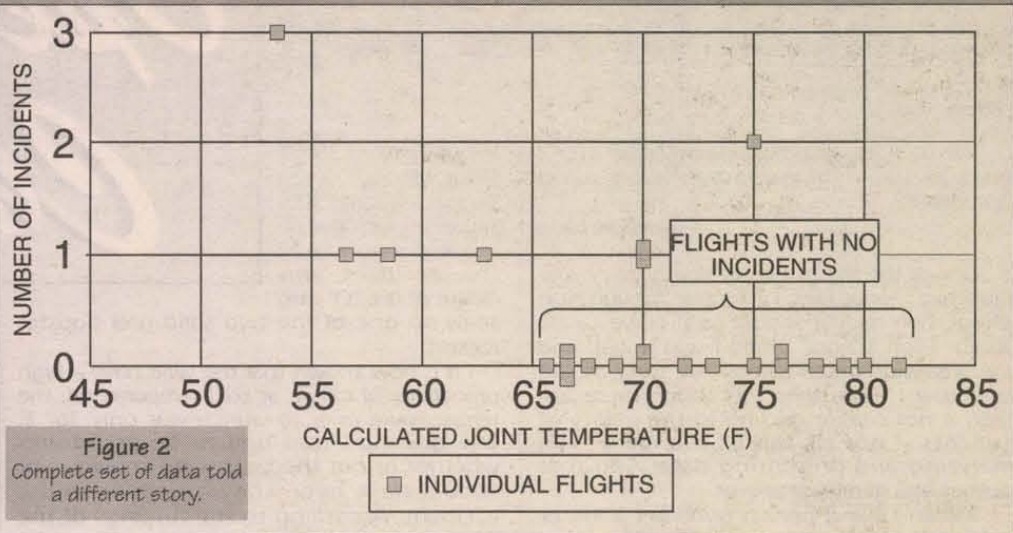


Figure 2
Complete set of data told a different story.

a good idea to look further. I often follow-up on footnotes in order to judge the quality of research. In one case, an advocate's paper had plenty of footnotes, so on the surface looked pretty good. Footnotes are a paper's bona fides, they tell readers that the author did her homework. In that case, I found that a critically important footnote didn't even exist! The journal cited was real, but when the actual copy of the cited issue was located in a library, the article claimed in the footnote did not exist. Checking the annual index for that year, and the two years either side of it, revealed no articles or letters by the author cited in the paper. Mistake? Possibly. Deceit? I'd bet on it!

Critical footnotes need to be examined carefully to see:

- a) Does the cited source actually exist?
- b) Is the source accurately quoted?
- c) Is the source fairly used?

The last criterion — fairly used — is especially important. Very often, one finds that cited sources are either taken out of context, or the conclusions of the study are twisted beyond recognition. If the author of the study would be surprised at the conclusions drawn, then it's a good bet that the study is not fairly used. While it is possible that an advocate could fairly draw different conclusions from those of a study author, that type of situation is always suspect until verified by the evidence.

A study can sometimes be verified by contacting its author. Ask the author if the published study is the latest information on the subject (published academic studies tend to lag the state of knowledge). Some scholarly journals print the acceptance date of the paper, and that date is often a year or two earlier than the issue of the journal in which it appears.

Journals also frequently publish the study's funding information so that you can judge whether or not there may be any particular bias in the results. A typical citation might read "Funded under NIH grant XXX-YZ-1230." If the funding organization is also an advocacy group or commercial entity, then be especially skeptical of the reported results (regardless of how well the group fits your own biases).

When you call the author of the study, ask about the methodology used. A lot of studies,

especially those in the social sciences, are terribly sensitive to the methodology. Responsible researchers recognize that fact, and take it into account when reading the study, but journalists often don't. By understanding the methodology, it is often possible to detect any biases, flaws, or limitations to the study.

Also, find out whether the journal in which a published study appears is peer reviewed or merely editor reviewed. A peer review publication sends every manuscript out to one or more disinterested reviewers. They ask hard questions, provide critique, and serve as general quality control. They point out weaknesses, and suggest areas for improvement.

Another factor often left out of popular expositions of scholarly research is critical qualifying factors. Studies are often tightly controlled as to the conditions being examined, and may not be valid in situations that depart from the controlled situation. It is often the case that studies will look at very narrow populations, and the results are not applicable to the population at large.

It may also be true that the interpretation of a study is different because critical information is left out of the report. A report says that the US population grew by 22 million people in the decade of the 1980s. On the surface, that figure looks horrific: 22 million new mouths to feed, with the required new jobs to support them! But a critical bit of information was missing: that growth rate for the decade was 9.8 percent, and was the second lowest on record.

Even the multi-hundred billion dollar US budget deficits of recent years doesn't look too awful when viewed as a percentage of gross national product (GNP). At least one paper in *Harvard Business Review* argued that the deficit is not so horrible as people believe, and may actually stimulate the economy if the debt is incurred for the right things.

Another thing that distorts the interpretation of otherwise valid studies out is the improper combining of the results of two or more studies. This mistake is the "apples and oranges fallacy." Advocates cite two or more studies on the same subject to bolster their position in a manner that suggests the studies are somehow mutually reinforcing or

Open Channel

complementary. A conclusion drawn as a synthesis from the results of two or more non-related studies is always suspect, and may be quite meaningless.

Studies almost always have some constraints, a basic methodology, and some (hopefully not hidden) basic assumptions. If the two studies cited do not share those factors in common, then drawing any conclusion that depends on combining them is invalid. The synthesized result is meaningless unless there is some means for compensating for the fundamental differences in the studies. Unless one is counting the category "fruit," one cannot fairly compare apples and oranges. It is very difficult for a layperson to make valid comparisons in such cases, so be wary when it is done without a good reason.

Scientific Studies

Scientific studies seem to be particularly subject to abuse when presented to a lay audience. Few people outside science understand that the results of studies are always considered tentative. They also understand that very few issues can be definitively proven by a single study. The public is often confused when two or more studies seem to contradict each other. "Is vitamin-C good for the common cold or not?" "Does eating bran lower cholesterol or not?"

Science makes progress by iteratively examining issues, and then holding up new data to public (and often very brutal) examination. As a result, each new study should build on earlier work, and refine its focus to overcome objections to the earlier studies. After this is done a number of times, some good approximation of the truth should emerge. But if one takes a "snapshot" of the research by looking at only one study at a single point in time, then an erroneous picture is seen. Scientists understand this problem, and account for it in their thinking, but laypersons rarely know how to look at studies. All that disagreement between studies may indicate is that scientists haven't refined their knowledge of a subject well enough to ask nature the right question ... yet.

Some General Advice

We can list several questions that should be asked of any claimant of truth:

- How do you know that such-and-such is true?
- Is the published data preliminary or final?
- Do other experts in the field concur?
— Is their concurrence general or highly specific?
- What is the information based on?
- Have the assertions been validated in a formal study or experiment?
- Was the study designed according to generally accepted standards?
- Who funded the work?
- What stake does the researcher have in the outcome (reputation, \$\$\$, promotion potential)?
- Who disagrees with the conclusions and why?
- How sure are you of the conclusion?
- Are the conclusions backed up by statistical evidence?
- Have the studies been replicated by others?

What were the results?

- Were the results reasonably consistent from one study to the next?
- Are other explanations possible?
- Who else in the field has seen the work?
— Was it peer reviewed?
- What methodology was employed?
- What are the study's weak points?
- What criticism has been received? From who?
- Do you agree with the advocate's conclusions drawn from your study? Was your work fairly used?

When evaluating a researcher, look for agendas (hidden and otherwise), the backgrounds and qualifications of the researchers, their normal job function, their self-proclaimed mission (if any), and the source of funding to detect possible biases in the study. Ask a real pertinent question: "Why is this person interested, and how does it affect the results?" The word "interested" to mean "has a stake in" rather than "curious about."

It is also relevant to know what peer recognition the researcher enjoys (or is afflicted by). It may also be pertinent to note who referred you to that researcher. Was it someone you respect? Was it a self-nominated advocate? Do they have a general reputation for reliability and integrity?

So Why Bother?

So why should you care that saltwater taffy is being distributed by those trying to persuade you? Because it pulls out your dental fillings, rips off your crowns, rots your teeth, raises your blood sugar level, is hard to chew, is generally unhealthy, yet doesn't provide any form of intellectual or spiritual nourishment in return for all its evils. It's icky stuff, so shun it. Better yet, stick the taffy maker to the wall with his own stuff.

Integration Revisited

The column on methods of integration must have really struck a resonant chord. I received 14 E-Mails, all of the positive. A surprising number of them came from E-Mail addresses ending in ".edu" indicating an educational institution. Several told me they were going to incorporate some of the material into various classes (electronics technology, introduction to laboratory Science, and math were mentioned.) Several of them suggested other methods. Those might form the basis for a future column, but probably not for a year or so (we don't like to repeat the same topic too often in deference to readers who don't care for that topic, and only tolerate it knowing their favorite topic is coming up soon). Thanks for the comments and suggestions.


Sensor-to-Computer Analog-to-Serial Interface Module

Another area where readers have responded positively is sensors and the associated interfacing circuits (I am writing a book on the topic, but I'm not sure the publisher approved my title: with all due apologies to Jane Austin, it was *Sensors & Sensorability*). As part of the research for the book, I started using Parallax BASIC Stamp and Micromint Pic-Stic modules. Micromint has a new product out that sensor users will find interesting.

The Answer MAN module comes in two varieties: one priced at \$49.00 and the other (Answer MAN Senior) at \$149.00. It is a 28-pin DIP module that incorporates eight-bit programmable digital inputs and outputs, analog inputs and outputs, power supply regulation, communications line drivers (RS-232A, RS-422, and RS-485). The Answer MAN will read frequency, count events, provide a pulse width modulation (PWM) output, among other abilities. It sounds a bit like a souped-up version of their PicStic products.

For information, contact: Chris White, Micromint, Inc., 4 Park Street, Vernon, CT 06066; (voice) **860-871-6170**, (FAX) **860-872-2204**. The data sheet is available on their web site at <http://www.micromint.com/> — Try it ... it may solve a lot of serial input problems. **NV**

Figure 3
Micromint Answer MAN.

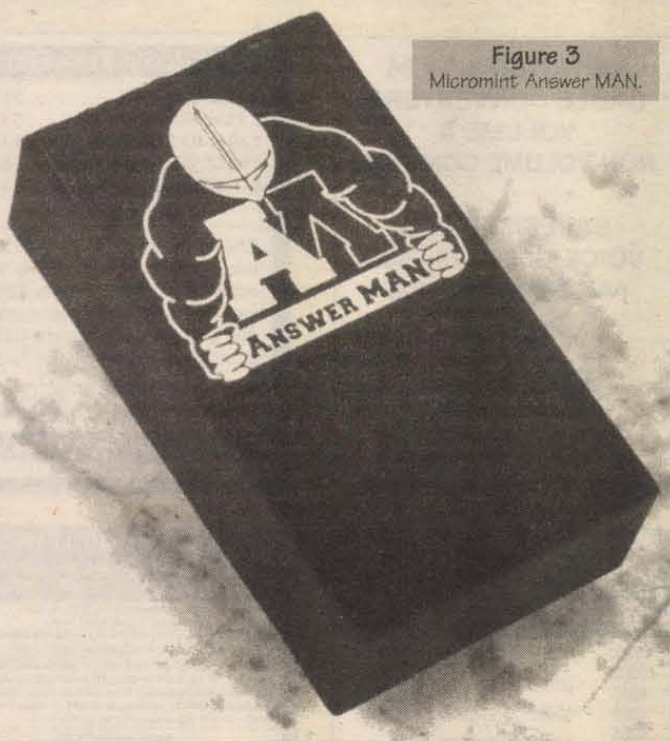

Connections ...

I can be reached in either of two ways:
1) by snail mail at P.O. Box 1099, Falls Church, VA 22041, or **2)** via Internet E-Mail at carrjj@aol.com — I appreciate your comments, suggestions, and criticisms.

BROWNDOG PROTOTYPES

Prototyping Adapters

BrownDog offers adapters to convert a variety of components to 0.1" center pitch wire-wrap prototyping boards including:

- RF connectors including BNC and SMA
- Terminal blocks
- Mini-DIN receptacles
- Power receptacles
- Memory SIMM sockets
- ... and more

Call, write, fax, or e-mail for free data sheets or visit our web page <http://www.browndog.com>.

Phone (toll free): (888) 484-3545
Fax: (918) 747-4849
email: bdsales@browndog.com

BrownDog Prototypes

1611 S. Utica, #276

Tulsa, OK 74104

Visa and MasterCard Accepted

SURPLUS SALE

200,000 WALL TRANSFORMERS



3.6 VDC	900 MA	2.25
12 VDC	100 MA	1.10
12 VDC	500 MA	1.75
12 VDC	800 MA	2.10
14 VAC	500 MA	1.75
16 VAC	1.25 A	2.95

Min 1000/type -- Call for other types

SURPLUS TRADERS

PO Box 276

Alburt, Vt. 05440

Tel: 514-739-9328

Fax: 514-345-8303

FREE CATALOG!

PROGRAMMERS OVER 50 MODELS

ADVANTECH EETOOLS NEEDHAM DATA I/O ICE TECHNOLOGY HILO SYSTEM GENERAL CHROMA MODULAR CIRCUIT TECHNOLOGY XELTEK



CALL ADVANTECH LABTOOL 599 EETOOLS SIMMAX
629 ICE TECH MICROV 795 CHROMA SIMM/SIP
650 EETOOLS ALLMAX + 359 MOD-MCT-EMUP/R
409 EETOOLS MEGAMAX 279 MOD-MCT-EMUP/R
509 EETOOLS MEGAMAX4 49 EPROM 1G TO 512K
369 XELTEK SUPERPRO II 69 EPROM 1G TO 1MEG
409 XELTEK SUPERPRO II P 99 EPROM 4G TO 1MEG
249 XELTEK SUPERPRO L 199 EPROM 16G TO 1 MEG
165 XELTEK ROMMASTER II 89 EPROM 1G TO 8MEG
479 MOD-MCT-EMUPA 129 EPROM 4G TO 8MEG
739 STAG ORBIT-32 250 EPROM 8G TO 8MEG



LABTOOL48 MICROMASTER SUPERPRO ALLMAX PLUS ROMMASTER2

General Device Instruments

Sales 408-241-7376 Fax 241-6375 BBS 983-1234

Web www.generaldevice.com E-Mail idevice@best.com

Mobil

Printer

12 VDC

Datel Model

APP-M20

5" X 2.75" X 9"

Here it is! Brand new factory boxed,

20 column mobile printer. Rugged

construction conforms to Mil STD 202E

and 810C for shock, humidity and vibra-

tion. Extra tall character printing, paper

advance and illuminated printout for

easy night viewing. Quiet, non distract-

ing thermal printing. RS 232 serial

input. Low 360 mA standby/1.2 A

printing power consumption.

BCD Electro

214.343.2170

\$29.99

3.50 S&H per order



Serial Problems???

Use your PC compatible desktop or laptop computer to debug serial communications problems with **Serial**, our test tool for serial communications.

Serial works with the standard data rates and asynchronous serial formats commonly found in modern office and industrial environments. Suitable for development, service work, and end-user problem diagnosis.

- Easy to Use
- Menu and Windows
- Highly Configurable
- Contextual Help
- Autobaud Detect
- Time Stamping
- Custom font editor for EGA/VGA Screens
- Saves Configurations
- Extensive Manual
- Block transmit ability
- CRC/LRC generation

Serial, with manual \$99.95

Cable for full duplex monitoring \$49.95

For Orders and Inquiries Call: 1-800-980-9806

Allison Technology Corporation

8343 Carvel, Houston, TX 77036

FAX and BBS 1-713-777-4746

SEND FOR FREE CATALOG

CURTIS KEYS KIT MARCONI
VIBROPLEX® KEYS J-POLE ANTENNAS
CODE PRACTICE OSCILLATOR KIT. SEEN IN
ARRL'S NOW YOU'RE TALKING!...\$22.95 PP

NEW! HI-POWER MARCONI ANTENNAS

\$0 M. APPROX. 64" OVERALL \$71.20 PP

160 M. APPROX. 130" OVERALL \$86.20 PP

JADE BOOK: HARD TO FIND ENGINEERING

DATA. HUMOR. FOLKLORE..... \$ 6.00 PP

SMART BATTERY CONTROLLERS:

AC OR SOLAR 110/220 FROM 1 AMP TO 6

SPECIAL! BUY A 6 AMP VAC OR A 6 AMP

SOLAR BATTERY CONTROLLER KIT GET THE

LO-VOLT DISCONNECT FREE. SAVE \$18.00!

1-800 JADE PRO (523-3776)

www.hampstead.k12.nh.us/diade/index.html

VISA, MASTERCARD, AMEX, NOVUS. CHECK OR MO

JADE PRODUCTS INC. E. HAMPSHIRE NH 03826-0368

PCB's in Minutes From LaserPrint!*

8 1/2" x 11" Sheets * Or Photocopier Use household iron to apply.



PnP BLUE or PnP WET

For High Precision Professional PCB Layouts

Easy Hobby Quality PCB's

1. LaserPrint

2. Iron-On

3. Sock-Off w/ Water

4. Etch

Adds an Extra Layer of Resist for Super Fine Lines on Std Clad Bds

205H/\$30/405H/\$50/1005H/\$100 Blue/Lit (No Mix)

Sample Pack 5 Shirts Blue + 5 Shirts Lit: \$20

VISA/MC/PO/CK/MO \$4 S&H -- 2nd Day Mail

Techniks Inc. P.O. Box 463 Ringoes NJ 08551

(908)788-8249

100% Money Back Guarantee-Dealer Inquiries Invited

Convert RS-232 to RS-485 or TTL/CMOS for Only \$49.00

Communicate up to 4,000 feet, at up to 1 MEGA-BPS, full or half duplex, up to 32 units on one serial link, with 31 jumper options for flexible configuration, LED indicators.

COMMUNICATIONS CONVERTER

• FULL SCHEMATIC AND DOCUMENTATION

• FULL FAMILY OF MODULAR DESIGNS

• RS-485/RS-422 REMOTE I/O MODULE KITS

• NETWORK SOFTWARE AND SOURCE CODE

• AUTOMATIC OR RTS UNITS AVAILABLE

• RJ-11/12 CONNECTORS OR TERMINAL STRIP

• TURN YOUR PC INTO A DISTRIBUTED DATA ACQUISITION AND CONTROL SYSTEM

R.E. SMITH

(513) 874-4796

4311 TYLERSVILLE RD. ■ HAMILTON, OHIO 45011

FAX (513) 874-1236



VIEWSTAR & TV 86 CABLE CONVERTERS VOLUME & NON-VOLUME CONTROL

SALES/SERVICE
VOICE 1-800-473-0506
FAX 1-800-488-0525

FOSS
WAREHOUSE
DISTRIBUTORS
285 Schenck St.
N. Tonawanda, NY 14120

TELEPHONE TEST DEVICES

2 Line Simulator	\$185.00
7 Line Simulator	\$399.00
Caller ID Simulator	\$395.00
20 HZ Ringing Module	\$49.95
9-1-1 Training System	\$370.00

*** And Much More ***

Check out our Web Site for detailed info about our unique line of test equipment. The CID-max Caller ID Simulator is a stand alone test unit that generates 10 different Caller ID messages per the Bellcore Specs!

Call John Today!

<http://www.infinet.com/~jtech>

1-800-631-0349

While They Last!



Peltier Junction (Thermoelectric Cooler) with heatsink and leads

\$15 EACH
OR TWO FOR \$25

Shreve Systems

318-424-9777

Ask for Jake

TOUCH-SENSITIVE TRACKPAD SUBASSEMBLY



Originally designed for Apple PowerBook 500 series

ONLY \$10 EACH

Returns subject to a 15% restocking fee. Prices are subject to change without notice.

WE ACCEPT VISA, MASTERCARD, AMEX, DISCOVER

<http://www.shreve-systems.com>

SPECIAL

ALL MAJOR BRANDS - ALL GUARANTEED

PROCESSOR	EPROM	STATIC RAM
80C31	8741	27C040
8202	8742	27C020
8219	8748H	27C010
8253	8749H	27C512
8255	8751	27C256
8254	87C51	27C128
82288	8752	27C64
FLASH EPROM	8755	27C32
28F010	8755	27C32
28F020	8755	27C32

AND MUCH MORE...

WE BUY YOUR EXCESS MEMORY AND CIRCUIT BOARDS

SINACO ELECTRONIC - 818-705-1880 - FAX 818-705-1881

ADAPT-11 • 68HC11 Module for Solderless Breadboards & Embedded Applications

• low-cost, versatile, compact (2.8" x 1.7") module
• reset circuit, pushbutton, & mode select switch
• RS-232 interface, 5V regulator & external power connector
• I/O lines brought out to breadboard-compatible header
Starter Package (AD11-SP) has ADAPT-11 module, 68HC11E3 microcontroller (2K EPROM on-chip), PC serial cable for downloading code, Motorola Programming Reference Guide, User Manual, freely distributable 68HC11 software, & ADAPT-11 demo program. US \$74.95 + \$5 S&H (discount available for qty 5 or more)

NEW MODULES

• ADAPT-11C75: Module for use with 68HC11 & 68C75 (adds 8K EEPROM + dual I/O ports), same size/outline as ADAPT-11...from US \$48, depending on configuration.
• ADAPT-11C75DX: Same as above, but includes 32K SRAM on a slightly larger board (2.8" x 2.1"). Use with a 68HC11E3 to get 12K EPROM, 8K EEPROM, and 32K SRAM, all on one compact board!...from US \$87.
• Choice of 6 header styles for the ultimate in flexibility!

Use any PLCC with your solderless breadboard! Socket adapters for most PLCC sizes, from \$7.50
Solderless breadboard adapters also available for DB9 & DB25 connectors, and IDC (ribbon cable) connectors.

TECHNOLOGICAL ARTS

voice fax: (416) 963-8996 www.ia.org/techart
309 Aragona Blvd., Suite 102-418, VA Beach, VA 23462
1644 Bayview Ave., Suite 1704, Toronto, ON M4G 3C2

NEW BOARDMAKER SCHEMATIC AND PCB CAD

For IBM PC and compatibles

BOARDMAKER

Entry Level - Only \$95

Easy to use

Dot matrix, laser, plotter

Gerber & NC drill output

Advanced - \$395

Accepts netlists

Design rule checking

Board Capture - \$395

Full feature schematic capture

Board Router - \$200

Gridless autorouter


Free Demo

7840 ANGEL RIDGE ROAD


ATHENS, OHIO 45701

(614) 592-1810

Visa & MasterCard Accepted

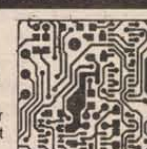

DEVICE PROGRAMMERS & MEMORY TESTER

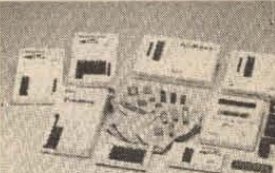

SIMMax (MEMORY TESTER)

AllMax+ (Parallel Port Universal Programmer) \$665

MegaMax4G (Parallel Port 4-Gang Programmer) \$745

MegaMax \$445 RomMax \$159 RomMax4G \$219

Free-updates, Made in USA, 1 Yr. warranty

EPROM Emulators, Erasers, PLCC, SOIC, TSOP adapters available

Electronic Engineering Tools

544 Weddell Drive Ste. 6

Sunnyvale, CA 94089

(408) 734-8104

FAX (408) 734-8185

BBS (408) 734-8945

Mini-Mods

..... Miniature Engineering Modules

- Pocket Watch** \$19.95
Real time clock w/ alarm & leap year compensation
- RamPack** \$19.95
8Kb serially addressable SRAM
- Motor Mind** \$24.95
Serially controlled H-Bridge driver
- Mini-Watt** \$24.95
5V/200mA battery power supply w/ charger. Add \$10 for power cube and NiCads

All products perfect for use with micro-controllers, micro-processors, single board computers. S&H extra.

S3 SOLUTIONS CUBED
3029 F Esplanade
Chico, CA 95973
(916) 891-8045
www.solutions-cubed.com

CCTV SPECIALS

Panasonic WV-BP312
1/3" B/W CCD Camera



0.06 lux @ F1.2
570 line resolution
12vdc • C/7 CS mount
ALC or Electronic Shutter

\$259

Panasonic AG-RT600
40 hour Real Time VCR



5/24/40hr
Time/Date Generator
Auto Repeat Recording
Alarm Search • Alarm Input
Auto Restart • Tape End Alert

\$749

Panasonic Industrial
AG-720 • Miniature VHS VCR



12vdc • Under 5 pounds
Small! 9.75 x 3.5 x 8.2 in.
2500 Hour Audio & Video
S-VHS Model Available

\$895

Computer
CEC-E38 • 1/3" B/W Camera



380 lines • 9 VDC
45 or 70 degree lens
BNC Video • power strip
indoor wall/ceiling mount

\$169





TOGGLE SWITCH SUPERMARKET WHOLESALE PRICES

FERTIK'S
5400 ELLA ST., PHILA., PA 19120
FREE LIST PH/FAX
215-455-2121


EPS EPROMS AS LOW AS 50¢

27C256	27C040	27C1024	87C51
27C512	27C400	28F010	8751
2732A	27C4096	28F020	8755
27C32	574000	28F040	68705
27C128	574200	8749H	2564
27C64	27C402	8748H	2516
2716	27C020	8741	
2708	27C210	8742	
27C512-90	27C010	8744	

PROCESSOR
8255
8254
80C31
8219
8202
8253
8284

Many more parts in stock. Call us for all those hard-to-find ICs and this month's special. Also memory for all PCs & laser printers.

TEL: (818) 774-9444 • FAX: (818) 774-0822
WE BUY EXCESS INVENTORY



FREE SAMPLE COPY!

ANTIQUE RADIO CLASSIFIED

*Antique Radio's Leading
Monthly Magazine*

Articles - Classifieds - Ads for Parts & Services. Also: Ham Equip. - Books - Telegraph - 40's, 50's & 60's Radios - Early TV - Auction Reports & more...

1-Year: \$36.95 (\$53.95 by 1st Class)
6-Month Trial - \$18.95. Foreign - Write.

A.R.C., P.O. Box 802-G17
Carlsile, MA 01741

Call: 508-371-0512 — Fax: 508-371-7129
Web: www.antiqueradio.com

EQUIPMENT FOR SALE

ELECTRONIC TEST

Tektronix	EXT 330
Hewlett-Packard	EXT 331
Other Manufacturers	EXT 332
MEASURE & INSPECT	EXT 333
VIDEO PRODUCTS	EXT 370
SCIENTIFIC & LAB	EXT 335
LASERS	EXT 340
POWER SUPPLIES	EXT 334
COBWEB CORNER	EXT 380
MFG	
COMPLETE INDEX	EXT 300

To obtain information via FAX: A) Have your fax number ready. B) Dial 1-800-547-4636. C) Request above Extension Numbers.

DEXIS CORPORATION
(612) 944-7670 FAX (612) 942-9712
9749 HAMILTON ROAD
EDEN PRARIE, MN 55344

CUT MANUFACTURING COSTS!

Mexico City plant specializes in manufacturing and design of prototypes and medium size production runs. Reverse engineering, manufacture of spare parts for obsolete electronic equipment. PCBs, cabinets, chassis, brackets, and other metal parts. Custom silk screen printing. Send us your hand-drawn diagrams or blue prints, we will deliver a finished product tested and operational. You procure the parts or we do. Very low prices! We handle all import, export and ship to your door as any domestic company.

USA Office: V&V Mach. & Equipment, Inc.
Ph: (713) 397-8101, Fax: (713) 397-6220.
Mexico Plant: Marketing Tech.
Ph: 011 (525) 361-3351, Fax: 011 (525) 361-5996.

HIGH PERFORMANCE ULTRA-MINIATURE PINHOLE LENS CAMERA WITH AUDIO

The PH200A is the smallest pinhole camera in the industry.

- High Sensitivity - needs only .2 lux • High resolution - more than 400 lines • Ultra miniature - measures only 30mm x 30 mm x 14 mm • Camera comes complete with connectors and power supply • Includes 5.5mm wide angle pinhole lens • Can be easily mounted behind a 1/8" hole for any custom or cover applications. **ONLY...\$125.00**

Surveillance Catalog \$5.00

SPY OUTLET
2468 Niagara Falls Blvd
Tonawanda NY 14150
(716) 695-8660 Fax (716) 695-7380

Universal Programming -WITHOUT MODULES!

PLUS built in ROM/RAM emulators

EPMaster LV 40 pins: 8/16 bit E(P)ROMs, Serial, Flash. REAL 1.8V/3.3V/5V logic. With 128K by 8 emulator \$495, 128K x 16 \$565	\$349
Speedmaster 1000+: Memories, 8751, PALs, GALs, No extras to buy or lose!	\$495
Speedmaster LV: E(P)ROM, Serial, PROMs, BROMs, NVRAMs, Flash, PALs, GALs, MACH, MAX, EPLDs, 8748/51, etc. REAL 1.8V/3.3V/5V logic	\$595
Micromaster 1000+: EPROMs, EEPROMs, Serial PROMs, BROMs, NVRAMs, Flash, PALs, GALs, EPLDs, MACH, MAX, MAPL, PSD, PIC, 286, 576, 68HC705, 68HC711, 87C00x, 89C00x, COP etc. NO MODULES OR ADAPTERS FOR DIL	\$695
Micromaster LV: Ultimate universal programmer with REAL 1.8V/3.3V/5V logic.	\$795
Speedmaster GLV32 8 gang EPROM/Flash. Supports 3.3V and 5V devices. ALSO AVAILABLE: COP Gang Programmer (40 pins)	\$995

Made by ICE Technology Inc 1 800 624 8949 (919 693 0678)
FAX: 919 693 0681 24 hour FAXBACK: 919 693 1509
web: http://www.icetech.com
P O Box 1438, Henderson NC27536

CONTROL • MEASURE • INPUT

MODEL 40-\$99

- RS-232 interface
- 28 lines digital I/O
- Eight analog inputs
- PWM output
- Three stepper ports

MODEL 100-\$279

- 12-bit 100KHz A/D • Four analog outputs
- Three timer counters • 24 digital I/O

PRAIRIE DIGITAL, INC.
646 SEVENTEENTH ST., INDUSTRIAL PARK
PRAIRIE DU SAC, WI 53578
TEL: (808) 643-8599 • FAX: (808) 643-8754

LOWEST PRICES UNDER THE SUN!

SOLAR ELECTRIC INC.

5555 Santa Fe St. #J
San Diego, CA 92109-1602
(619) 583-8760
(619) 287-8774 fax
TOLL FREE 1-800-842-5678
e-mail: solar@cts.com
http://www.solarelectrinc.com

FREE DETAILED PRICE LIST

SIEMENS STARPOWER UNI-SOLAR

Robot Explorer™

The Robot Explorer™ newsletter is your guide to the world of intelligent mobile robots. Receive 8 issues packed with robot explorations: from Antarctica, to the depths of volcanoes, to desktop mechanical creatures.

Build the newest robot kits, review the latest books, and receive expert guidance from master robot crafters.

Whether you're a professional robot designer, researcher, educator, hobbyist, or simply love to read about robots, Robot Explorer contains the articles you need to keep up to date with the quickly evolving world of intelligent machines. Eight issues for \$14.95.

Call Now!
MC/Visa 1 (800)GO-ROBOT 1(800)487-6268
POB 458, Peterborough NH 03458 603.924.6079
\$14.95 North America \$29.95 World-Wide

Stamp Applications: now on the Web!

Putting the Spotlight on BASIC Stamp Projects, Hints, and Tips

That's right. You can now access all of Scott's great columns online at the Nuts & Volts Web site. Each column is available as a separate .PDF file and requires an Adobe Acrobat reader to view. A direct link to Adobe is also provided so you can download the reader if you need it.

These columns are provided to all absolutely free — for now. Soon, some of them will be moved to a special subscribers only section, and will remain free and available to current subscribers only.

The files are in 8 1/2 x 11 format, so they will print out and fit nicely into your reference binder.

http://www.nutsvolts.com

ATTENTION DEALERS

**BUY DIRECT FROM
THE WHOLESALER**

**GET THE BEST PRICES AND SERVICE
ALL UNITS ARE IN STOCK FOR IMMEDIATE SHIPMENT**

NOVAVISIONS

	QTY 10	QTY 20	QTY 50
NV-5600 (PIO)	\$199	\$185	\$170
NV-5700	\$199	\$185	\$170
NV-5800	\$199	\$185	\$170
NV-5750 (JBB)	\$275	\$260	\$245

NEW CONVERTERS

	QTY 10	QTY 20	QTY 50
CENTURY CT-3000 ..	\$65	\$60	\$55
PANASONIC 145	\$79	\$74	\$69

**ALL TYPES OF CABLE
EQUIPMENT AVAILABLE.
CALL FOR DETAILS.**

CALL FOR THIS MONTH'S SPECIALS

**1-800-808-3356
DIRECT CABLE SUPPLY**

ROBOTICS

STEPPER IC: New EDE1200 is ideal for 5/6 wire stepper motors. Download our datasheet or call E-Lab Digital Engineering, Inc. 712-944-5344. Visa/MC. <http://www.netins.net/showcase/elab>



ROBOTIC ARM KIT, five axis with gripper. Control with any serial port. Very accurate and repeatable. \$195 includes all hardware, structural components, software, illustrated assembly manual, 6 Hitec servos and MiniSSC servo controller. Add S&H \$7.50 USA and Canada, \$25 International Airmail. IL residents add 6.25%. Credit cards welcome. TSS, 104 Partridge Road, Pekin, IL 61554-1403, 309-382-1816. www.lynxmotion.com NEW mobile version \$250.

STEPPER/SERVO motors and drives, rotary/linear optical encoders, and industrial control microcomputers for sale at surplus prices. Great for robotics projects. Call or E-Mail for list. Mark Shaw, Motionex, Inc. Phone: 1-800-476-4450/704-523-2222. E-Mail: marks@motionex.com

REPAIRS/SERVICES

PRINTED CIRCUIT boards from your artwork. For quotes, call or fax requirements. ILIADIS 904-641-9942.

18,000 Plus TECHNICAL REPAIRS for TVs, VCRs, projection TVs, CAMCORDERS, CD players, & audio organized in an EASY to use computer program. **The TECHNICAL TIP REPAIR program. PROFESSIONAL BOARD LEVEL & COMPONENT LEVEL REPAIRS.** Add your own tips. **PRINT** tips. Ask about our **TIP EXCHANGE** policy with **FREE updates.** Works on IBM compatible computers with a hard drive (also on some Apple Macintosh). **Only \$150 & FREE SHIPPING.** Works in DOS, WINDOWS 3.1 & WINDOWS 95. **FREE DEMO. HIGHER INTELLIGENCE SOFTWARE, 60 FARMINGTON LANE, MELVILLE, NY 11747. CALL 1-800-215-5081/516-643-7740.**

PICS, GALS READ if you've lost your masters. Programming service available. Call for info. Network Sales, 616-683-0500.

CABLE CONVERTER REPAIR: Specializing in all Zenith models. Very reasonable price. Give me a call. 619-630-1909, ask for Paul.

ENGINEERING CONSULTING. Product development from conceptual to manufacturing stages. Digital, analog, and RF expertise. Microcontroller designs for HC05XX, HC11XX, PIC 16C5X. Software design for IBM PC. ASIC design using XILINX. In-house schematic capture and PWB. Steve Hicks, DiaSystems Electronics, 7508 E. Granada Rd., Scottsdale, AZ 85257. 602-970-3162. steveh@terrestrial.com

WELD ALUMINUM WITH PROPANE! Now you can weld alum. and other metals with propane fuel, with our special alloy rods. Easier than solder. No flux. As strong as hell-arc. Repair or fabricate antennas and more. E-Z instructions. Money back guarantee. One pound kit (22 rods) \$29 including 2nd day postage. Weeks Dist., 36 Carolina St., Taylors, SC 29687. 1-800-547-WELD (9353), Fax 864-244-6349. MC, Visa.

PINBALL MACHINES! Books, Magazines, Manuals, Diagrams, Supplies, Parts. \$2 catalog. Marco Specialties, 5290-N Platt Springs Rd., Lexington, SC 29073-9252. 803-957-5500. FAX 803-957-6974. E-Mail: tilt@ix.net.com <http://magenta.com/marco>

HARDWARE & SOFTWARE ENGINEERING. Zagros Robotics, PO Box 460342, St. Louis, MO 63146-7342. 314-768-1328, zagros@mo.net

Events CALENDAR

Continued from page 37

WI - WAUKESHA - Swapfest & Computer Expo. County Expo Center, N1 W24848 Northview Rd. 8am-2pm. SEWFARS 414-650-0724

MARCH 15

CA - SANTEE - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-In. 619-561-0052
GA - MARIETTA - ARRL Hamfest. Kennelwoodchess ARC. Margaret Durham 770-977-4405

NH - SALEM - Computer Show. Rockingham Park Race Track. 10am-3:30pm. Northern Computer Shows 508-744-8440

TN - KNOXVILLE - Hamfest. Kerbel Shrine Temple. 8am-4pm. Paul Baird 423-986-9562

VA - HARRISONBURG - Computer Show. Rockingham Co. Fgnds. MarketPro 301-984-0880 xt15

MARCH 15-16

FL - TAMPA - Computer Show. Florida State Fairgrounds. MarketPro 301-984-0880 xt15

GA - NORCROSS - Computer Show. North Atlanta Trade Center. MarketPro 301-984-0880 xt15

OK - TULSA - State Convention. Merlin Griffin 918-272-3081

PA - MONROEVILLE - Computer Show. Pittsburgh Expo Mart. MarketPro 301-984-0880 xt15

TX - MIDLAND - ARRL Hamfest. Midland ARC. Beverley Harwood 915-686-1841

MARCH 18

IL - STERLING - Hamfest. Sterling High School Field House. 1606 4th Ave. 815-336-2434

MA - WORCESTER - Computer Show. Crowne Plaza Hotel. 10am-3:30pm. Northern Computer Shows 508-744-8440

OH - MACUMEE - Hamfest/Computer Fair. Lucas Co. Recreation Center, 2901 Key St. 8am-3pm. TMRA. Paul Hanslik 419-243-3836

PA - YORK - ARRL Hamfest. Keystone VHF. John H. Shaffer 717-764-8193

WV - CHARLESTON - Hamfest & Computer Show. Jimmie Hewlett 304-768-1142

MARCH 21-22-23

WI - MILWAUKEE - Computer Show. Milwaukee State Fair. Blue Star Productions 612-788-1901

MARCH 22

FL - AVON PARK - Hamfest & Computer Show. National Guard Armory, 2500 US Hwy 27 South. 8am-2pm. Clyde Scruggs 941-453-7181

FL - STUART - Hamfest. Martin Co. Fairgrounds. Martin County ARA. Romund Madson 561-337-1841

MA - ROCKLAND - Computer Show. Sons of Italy. 10am-3:30pm. Northern Computer Shows 508-744-8440

MO - KANSAS CITY - ARRL Hamfest. Ararat Shrine RC. Steve Dowdy 816-941-0620

NJ - WEST ORANGE - Hamfest. West Orange H.S. 600 Pleasant Valley Way. 9am-2pm. Jim Howe 201-402-6066

MARCH 22-23

FL - JACKSONVILLE - Computer Show. Jacksonville Fairgrounds. MarketPro 301-984-0880 xt15

IN - INDIANAPOLIS - Computer Show. Indiana State Fairgrounds. MarketPro 301-984-0880 xt15

IN - NASHVILLE - Computer Show. Nashville Armory. MarketPro 301-984-0880 xt15

MARCH 23

IL - GLEN ELLYN - Computer Show & Sale. Harper College. 9:30am-3pm. Computer Central Shows 847-940-7547

IL - GRAYSLAKE - LAMARSFEST '97. Lake County, IL Fairgrounds. 8am-2pm. Frank Avellone 847-234-4124

NC - KINSTON - ARRL Hamfest. Dwon East Hamfest Assn. Dough Burt 919-524-5724

NH - NASHUA - Computer Show. Sheraton Tara Hotel. 10am-3:30pm. Northern Computer Shows 508-744-8440

NJ - TRENTON - ARRL Hamfest. Delaware Valley Radio Assn. Darryl Foyuth 609-882-2240

NY - YONKERS - ARRL Hamfest. Westchester Emergency Communications Assn. Thomas Raffaelli 914-741-6606

OH - MADISON - ARRL Hamfest. Lake County ARA. Roxanne 216-256-0320

PA - WILKES BARRE - Computer Show. Genetti's Best Western. MarketPro 301-984-0880 xt15

VA - ROANOKE - Computer Show. Civic Center. MarketPro 301-984-0880 xt15

MARCH 28-29

GA - COLUMBUS - ARRL Hamfest. Columbus ARC. Randy Hancock 706-596-8820

MARCH 29

IN - MICHIGAN CITY - Hamfest & Computer Fleamarket. Michigan City High School, 8466 W. Pals Rd. 8am-2pm. Ron Stahovick 219-325-9089

MD - GAITHERSBURG - Computer Show. Montgomery Co. Fgnds. MarketPro 301-984-0880 xt15

OH - COLUMBUS - Computer Show. Veterans Memorial. MarketPro 301-984-0880 xt15

by Gordon West

FAMILY RADIO SERVICE ON THE AIR

The Federal Communications Commission (FCC) has gone full circle on its personal radio service called Citizens Band (CB). Class A Citizens Band on UHF frequencies 462 MHz/467 MHz attracted only a few licensees almost 50 years ago. The equipment was bulky, and I can remember the frequency tuning process of a Vocaline Class A CB as slightly squeezing, or slightly separating two parallel plates to put yourself on channel.

Class A Citizens Band ultimately turned into the UHF general mobile radio service (GMRS), a well-disciplined radio service continuing to fare well today under the guidance of Personal Radio Steering Group, Inc., P.O. Box 2851, Ann Arbor, MI 48106; 313-MOBILE3. If any one non-profit group deserves due credit in keeping a radio service created by the FCC orderly and useful, credit goes to the Personal Radio Steering Group for their untiring efforts in watching over GMRS.

A GMRS radio requires the operator to be licensed by the Federal Communications Commission for which the FCC would normally issue one channel pair spaced 5 MHz, with a second channel or channel pair assigned at the request of the applicant. The channel pair 462.675 MHz/467.675 MHz could also be used for the purpose of soliciting or rendering assistance to a traveler, or for communicating in an emergency pertaining to the immediate safety of life or the immediate protection of property.

Most recently, the FCC also granted small base stations and portable operations in the simplex mode on the following 462 MHz interstitial frequencies:

462.5625
462.5875
462.6125
462.6375
462.6625
462.6875
462.7125

If you possessed a valid GMRS license, you could operate voice on these interstitial frequencies with no more than five watts of effective radiated power.

Keep these five-watt interstitial frequencies in mind when we soon talk about the new Family Radio Service operating on these same frequencies, but with only one-half watt of power. Guess who has the

advantage!

In the mid-1950s, the FCC also established Class D Citizens Band under Part 95 as an additional short-range radio service operating on 27 MHz. Just like Class A CB, a license was required, and an operator would receive a grant to operate on any one of the 27 MHz 23 channels. As 27 MHz Citizens Band began to grow popular in the 60s and 70s among truckers and radio enthusiasts, the channels were expanded from 23 to 40, and millions of 27 MHz CB radio operators began to go out of control.

Ultimately, the FCC could not keep up with licensing nor control on the band, and simply threw in the towel saying the rules still hold, but you no longer need a license for Class D 27 MHz CB. And that's the way it is today — an unlicensed radio service, totally out of control with a "no license, no rules" philosophy by many of the operators.

REACT still tries to do their best on Channel 9, the designated emergency channel, but since no one needs a license, how can anyone really control the rule violators?


Interesting to note, the FCC has recently unlicensed the domestic use of VHF marine radios, as well as VHF aeronautical radios. Mariners and pilots are hoping that undisciplined chaos doesn't break loose on these important bands, too. Time will tell.

But there was still a void in a radio service that would allow short-range, handheld-to-handheld communications among family and friends, backpackers and skiers, business

and pleasure.

The GMRS UHF Citizens Band Radio Service was not a likely candidate for short-range casual or business communications because FCC licensing was still a requirement, the equipment relatively expensive, and the same licensing requirements even to get access at those seven relatively new interstitial frequencies.

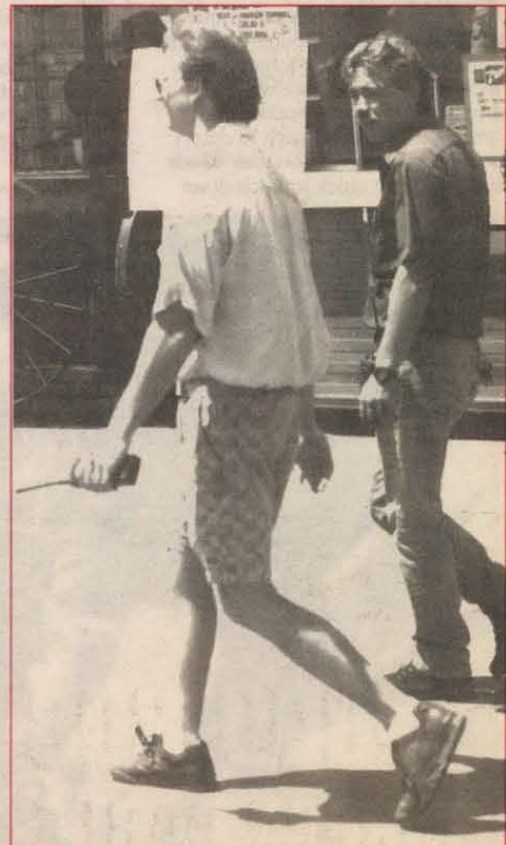Business band radio on both VHF and UHF required FCC licensing, and the channels were jammed pack and not authorized for personal communications. There was even a period when business band itinerant channels were used for unit-to-unit communications, but these channels



The small FRS radios operate just like bigger, commercial handheld radios.

GMRS CHANNELS ...


GMRS FREQUENCY ALLOCATIONS FCC Rules Part 95, Subpart A

Base Station, Mobile Relay
Station, Fixed Station, or
Mobile Station

Channel 1 - 462.550
Channel 2 - 462.575
Channel 3 - 462.600
Channel 4 - 462.625
Channel 5 - 462.650
Channel 6 - 462.675
Channel 7 - 462.700
Channel 8 - 462.725

Mobile Station, Control Station,
or Fixed Station Operated in the
Duplex Mode

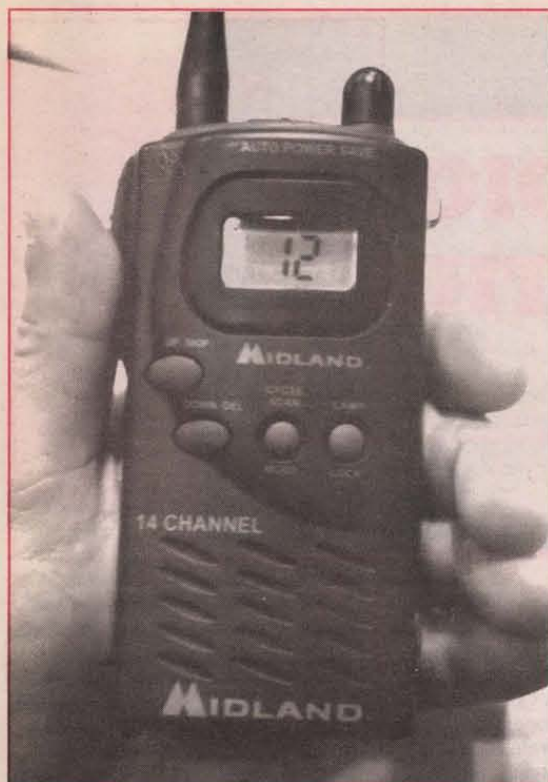Channel 1 - 467.550
Channel 2 - 467.575
Channel 3 - 467.600
Channel 4 - 467.625
Channel 5 - 467.650
Channel 6 - 467.675
Channel 7 - 467.700
Channel 8 - 467.725




All channel, half-watt, UHF family radio service portable transceiver.

were soon filled with high-powered stations and now the itinerant channels on both VHF, as well as UHF are considered just about useless by the thousands of licensed and unlicensed operators.

Ham radio for pleasure required the ham test, even though the Morse Code requirement for a ham radio Technician class license was dropped. Long-term licensed ham operators were also quick to detect unlicensed operators on their bands, and they were quick to track down

pensive because of the number of sets coming in from Japan was also not a wise choice for the casual hunters or skiers wanting to stay in touch. The FCC views the marine and aviation services as safety of life, and they take swift action to track down unlicensed operators. But now that the marine VHF and aeronautical service have gone FCC unlicensed, time will tell whether or not illegal operators are quickly apprehended.

About a year ago, amateur radio

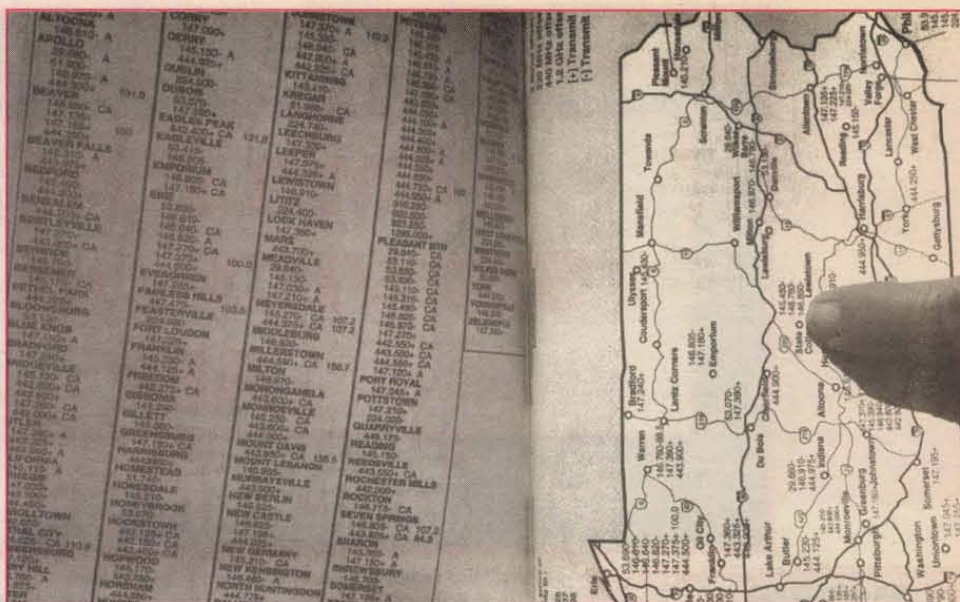

A cloned ham radio gets new hams on the air fast (through local repeaters!)

unlicensed operators and get them off of their valuable VHF and UHF frequency assignments.

Using marine VHF radios that were relatively inex-

operator Robert Miller AA5FL, proposed a new short-range UHF radio system called Family Radio Service, utilizing interstitial (split frequencies) within the GMRS band.

Channel 1 - 462.5625 MHz
Channel 2 - 462.6875 MHz
Channel 3 - 462.6125 MHz
Channel 4 - 462.6375 MHz
Channel 5 - 462.6625 MHz
Channel 6 - 462.6875 MHz
Channel 7 - 462.7125 MHz

Channel 8 - 467.5625 MHz
Channel 9 - 467.5875 MHz
Channel 10 - 467.6125 MHz
Channel 11 - 467.6375 MHz
Channel 12 - 467.6625 MHz
Channel 13 - 467.6875 MHz
Channel 14 - 467.7125 MHz

Miller's proposal for the new 14 channels situated in between the long-standing GMRS channels took about one year from concept to FCC rulemaking. His vice-president position with Radio Shack most likely had a big impact on the FCC, realizing that a low-cost, short-range, no-license radio service would be a boon to both the public, as well as the economy with the expected millions of little radios to be sold. But for the licensed GMRS operators throughout the country, low-power "anything goes" radio sets in between regular GMRS mobile and repeater output frequencies could spell big-time problems.

The Personal Radio Steering Group (313-MOBILE3) did an exemplary job of investigating all positions in this issue, and presenting a professional un-emotional, alternate opinion on how half-watt, unlicensed, handheld FRS radio sets could cause interference to their long-standing, professionally licensed and managed, general mobile radio service.

Although the Commission ultimately adopted the Bob Miller Radio Shack Family Radio Service proposal, the Personal Radio Steering Group newsletter *PERSONAL RADIO*

EXCHANGE indicates two parties have filed Petitions for Reconsideration of the rules that the FCC recently adopted for the Family Radio Service. But it may be too late — the newsletter indicates Family Radio Service models "are already on the market, and we expect to see many (sold) before the end of the Christmas 1996 shopping season."


Now that the Family Radio Service is on the air with brand new equipment, some surprises are taking place out in "radio land." Some of these "surprises" were anticipated, yet others may show the creativity of radio enthusiasts wanting to "do their thing" on the new 14 UHF interstitial frequencies.

The first revelation came when new FRS operators discovered the first seven channels already occupied with licensed GMRS operators running LEGALLY 10 times more power on Channels 1 through 7. FCC Rule 95.29(f) allows five watt ERP licensed GMRS operators to use voice on the following interstitial channels:

Channel 1 - 462.5625 MHz
Channel 2 - 462.5875 MHz
Channel 3 - 462.6125 MHz
Channel 4 - 462.6375 MHz
Channel 5 - 462.6625 MHz
Channel 6 - 462.6875 MHz
Channel 7 - 462.7125 MHz

Licensed GMRS users on the first seven Family Radio Service frequencies not only could run 10 times more power, but also operate small base stations or mobile stations that sounded a lot louder than the small half-watt Family Radio Service portable stations. This "loudness" is due to the fact that FRS equipment operates at 3 KHz deviation, and GMRS equipment might operate up to 5 KHz deviation. The more deviation, the louder the signal appears out of the little FRS handheld sets.

Both FRS, as well as GMRS

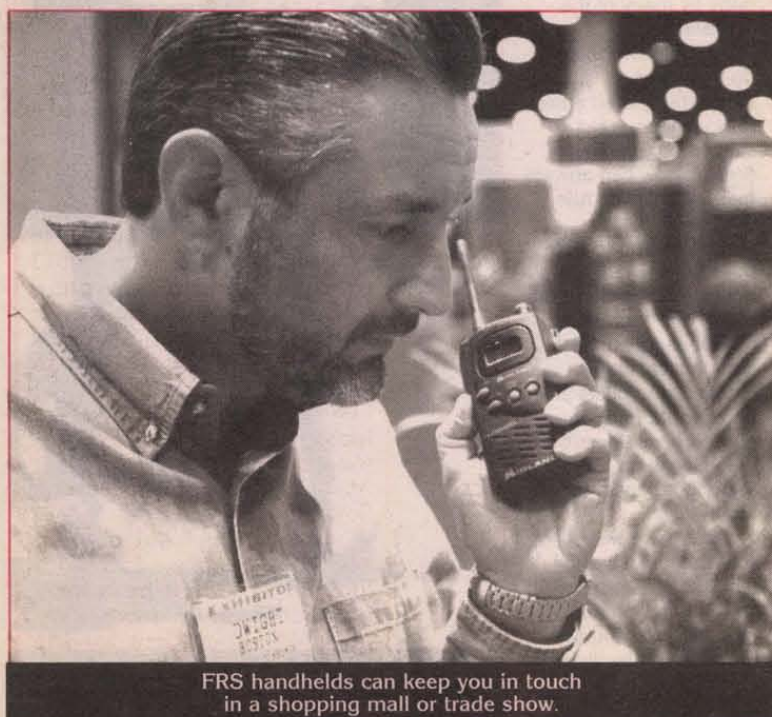

FRS handhelds can keep you in touch in a shopping mall or trade show.



In a matter of seconds, ham radios may be cloned for instant repeater access and public safety receive.

operators, on these interstitial frequencies would sometimes be clobbered with co-channel interference on regular GMRS channels because the 50-watt output GMRS systems would repeat out right next to the first seven interstitial frequencies.

Immediately Family Radio Service operators saw the benefit of choosing FRS Channels 8 through 14 to get away from GMRS interstitial operators, as well as the nearby

outputs of GMRS repeaters. And good news for FRS operators — the 467 MHz FRS channels were absolutely clear and quiet. If you have FRS equipment now, Channels 8 through 14 are your best choice for good range.

So far, FRS units on Channels 8 through 14 have not caused interference or desensitization to licensed GMRS repeater systems which listen in on 467 MHz, and transmit out on 462 MHz. This was a concern of GMRS operators. I suggest you do not operate your small FRS radio near repeater sites that may have GMRS systems. So how far do these small half-watt FRS units actually transmit on simplex?

About one mile in residential neighborhoods, a few hundred yards inside shopping malls, and up to five miles down at the beach or on lakes and rivers. And for the Family Radio Operators interested in being the first to talk half-watt handheld to half-watt handheld over 100 miles, you are too late — I have already done it with a pair of little handhelds between a mountain top in Santa Monica, CA, and a little FRS handheld aboard a boat near the Mexican border. On this line-of-sight basis, our 100-mile contact was absolutely noise-free, and we probably could have extended it an additional 50 miles or so if the boat operator had more gas. But FRS equipment is really intended for short range — parents to kids in a shopping

mall — two skiers out on the slopes — one residential block captain to another three blocks away. And with one-half watt output on UHF, the little FRS equipment goes hundreds of times further than 49 MHz CB play toys, and usually a lot further than Class D Citizens Band when the channels are crowded with skywave interference. On FRS, skip is nonexistent.

Innovative Family Radio Service operators were quick to discover they could turn their little handheld with voice-activated transmit into a quasi-repeater station, repeating signals from other handhelds, or for that matter, any other radio service.

Although FRS equipment may not have the antenna system enhanced or added to, placing a VOX-operated FRS unit high atop an office building could act as a type of repeater. There is even talk of the relatively obscure amateur radio digital talker simplex repeaters being interfaced with a VOX-operated FRS transceiver.

These digital store-and-forward ham radio simplex "repeaters" listen to about 30 seconds of conversation, and then voice out this same digitally memorized conversation on the same frequency — much like a long delay echo device, but one that could allow a VOX-operated FRS set being placed in operation not necessarily envisioned by how typical FRS sets would be used.

Everyone is hoping the new 14 channels of FRS will blossom with useful communications in an orderly manner. Although Part 95 rules don't spell out exactly what may or may not be transmitted over FRS, it is everyone's hope that intentional interference, sound effects, obscene and indecent language won't take place on FRS.

After all, the intent of FRS is as a family radio service where mom and dad can chat, and still keep track of the kids out on the lake, or in that big shopping mall. This is the way Bob Miller has envisioned it, and everyone hopes this new Family Radio Service will maintain some semblance of sanity and civility for its intended short-range service.

I encourage everyone who operates on GMRS, or who plans to operate on Family Radio Service, to sign up for the Personal Radio Steering Group newsletter to stay up-to-date on this exciting existing and new UHF radio service. (Subscriptions are available for \$30.00 a year, first class mail, PRSG, P.O. Box 2851, Ann Arbor, MI 48106.)

Equipment from Motorola, Radio Shack, Cobra, Alinco, and Midland is just hitting the marketplace, with prices from \$50.00 on up to a couple hundred bucks. Keep in mind your best channels are 8 through 14, and let's see some good radio operators on this newly created set of frequencies, paired closely and shared with the presently licensed GMRS. **NV**

NEWS ANNOUNCE- MENT

CLONING AROUND AT ALL HAM RADIO OUTLET STORES

Beginner ham radio operators can now buy ICOM America single-band and dual-band VHF/UHF transceivers pre-programmed with their local area "Top 40" VHF and UHF active frequencies.

"Local open repeaters, simplex, and local public safety channels will give the beginning operator a head start in taking advantage of their new ICOM equipment which has been cloned by their local ham radio outlet dealer," explains Jim Newcomb N7MBA, of ICOM America. "This Top 40 list will also add exposure to all of the local amateur radio clubs who sponsor a repeater and may hold evening nets," adds Newcomb.

Will a pre-programmed radio lead to a beginner not learning how to program in additional frequencies? "In a trial program between HRO, ICOM America, and Gordon West Radio School students, we found a much higher enthusiasm for newcomers learning how to clone and change memorized frequencies with this equipment, and beginners began programming and reprogramming at a much higher rate than other students who started off with a radio and an uncharged battery with only 144 MHz and 446 MHz coming up in the VFO mode," explains Newcomb. "We think ham radio outlet stores are offering the new operator a major benefit in being able to tune in and take advantage of all of the local radio systems in their area, pre-memorized in their new VFO/UHF radio set," finalizes Newcomb.

To receive a list of "Top 40" frequencies for your local area served by a local ham radio outlet store, simply stop in and ask for the list which is absolutely free.



New Alinco family radio service UHF radio with flip-up antenna for extra range.

HOW TO PLACE A CLASSIFIED AD

TYPE or PRINT your **ELECTRONICALLY RELATED** ad copy **CLEARLY** (not all caps) on a separate piece of paper. Spell out words when submitting handwritten copy. Calculate the number of words and multiply it by the appropriate rate (see RATE PER WORD section). Include any charges for bold and/or CAPPED words, any artwork costs that would be applicable, and/or costs for boxing your ad (explained below). Choose the appropriate classification for your ad(s) to appear in (see below). If no classification is indicated, it will be placed in Misc. Electronics or wherever we deem most suitable. **Enclose your name, address, phone number, and Nuts & Volts account number from your mailing label** (if available) for identification purposes. Include full payment — **CLASSIFIEDS RUN ON A PRE-PAID BASIS ONLY** — and mail your completed order to:

NUTS & VOLTS MAGAZINE, 430 Princeland Ct., Corona, CA 91719.

RATE PER WORD

The ad rate for **current PAID subscribers** is **60¢** per word. All others pay **\$1.20** per word. There is a **\$9.00 minimum** charge per ad per insertion.

WORDS IN BOLD AND/OR ALL CAPS

Words to be set in **bold** or **CAPS** are each **10¢** extra PER WORD. **BOLD CAPS** are **20¢** extra per word. The first two words of each ad are bold capped at no charge. Indicate bold words by underlining. Words normally written in caps (e.g., IBM) and accepted abbreviations such as VAC or MHz are NOT charged as all cap words. Use a two-letter abbreviation for states.

PHOTOS, DRAWINGS, AND BOXES

A photo or drawing may be run at the top of your classified ad for an additional **\$10.00** (1" depth max.) for camera-ready art. No wording is allowed in this area. Add a one-time charge of **\$5.00** to enlarge, reduce, or duplicate line art,

or **\$8.00** for halftone of photographs. To **BOX** your ad, include an additional **\$50.00** for copy-only ads, or **\$75.00** for ads with art or photos.

FAXING IN AD COPY

You may fax in ad copy or changes before the closing date (5:00pm on the 10th) at 909-371-3052 using MasterCard or Visa. Include credit card expiration date, the name that appears on the card, a daytime phone number, and your Nuts & Volts account number. Ads without credit card information will not be listed as received until payment is received in full. **WE DO NOT CALL OR FAX BACK VERIFICATION OR QUOTES OF FAXED-IN ADS.** For verification of faxed-in ads, please call 909-371-8497.

DEADLINE

Prepaid ads received by 5:00pm on the closing date (10th of the month) will appear in the following month's issue. Ads postmarked through the 10th, but received after the closing date, will be placed in the next available issue. No cancellations or changes after the 10th. Cancellations and changes must be submitted in writing.

IMPORTANT INFORMATION

All classified ads are running copy only. No special positioning, centering, dot leaders, extra space, etc. is allowed. All advertising in Nuts & Volts is limited to **electronically related items ONLY**. All ads are subject to approval by the publisher. We reserve the right to reject or edit any ad submitted. We do not take ad copy or changes over the phone. We do not bill for classified ads. Repeat ads or ads run in multiple classifications within the same issue are allowed. Paid subscribers may run ads at the 60¢ rate only through their subscription expiration date. **NO REFUNDS.** Credit only. No credit for typesetting errors will be issued unless you clearly print or type your ad copy.

Choose a category for your ad from the classifications listed below.

10. Ham Gear For Sale	80. Test Equipment	120. Components	155. Manuals/Schematics Wanted
20. Ham Gear Wanted	85. Security	125. Microcontrollers	160. Misc. Electronics For Sale
30. CB/Scanners	90. Satellite Equipment	130. Antique Electronics	170. Misc. Electronics Wanted
40. Music & Accessories	95. Military Surplus Electronics	135. Aviation Electronics	175. BBS & Online Services
50. Computer Hardware	100. Audio/Video/Lasers	140. Publications	180. Education
60. Computer Software	110. Cable TV	145. Robotics	190. Business Opportunities
70. Computer Equipment Wanted	115. Telephone/Fax	150. Plans/Kits/Schematics	200. Repairs/Service

ADVERTISER'S INDEX

AAA Trading/Audiopaging, Inc.92	Danbar Sales Company59	M.F.M. Communications74	Skycraft Parts & Surplus, Inc.5
Abacom Technologies83	Detection Dynamics111	MHZ Electronics, Inc.7	Software Clearance Outlet51
ABC Electronics69	Dexis50, 111	microEngineering Labs81	Solar Electric Inc.111
ACP Super Store24	Digicom Communications, Inc.16	Micromint, Inc.2	Solutions Cubed111
Advanced Educational Systems29	Direct Cable Supply112	Midwest Electronics16	Spy Outlet111
Alfa Electronics58	Earth Computer Technologies18	Milestone Products51	Square 1 Electronics6
Alfon Technologies, Inc.69	E.H. Yost & Co.35	Modem Communications18	Street Smart Security8
All Electronics Corporation57	Electro Tool, Inc.47	Modern Electronics47	Surplus Sales of Nebraska75
All Phase Video-Security, Inc.18	Electronic Engineering Tools110	Mo-Tech Dist.5, 105	Surplus Traders110
Allison Technology Corporation.31, 110	Electronic Rainbow Ind., Inc.46	Motron Electronics25	Synergetics89
Alltech Electronics Co.62	Electronic Service & Supplies83	Mouser Electronics31	Technical Advisory Group76
Alltronics45	EMAC, Inc.83	Mr. NiCd35	Techniks, Inc.110
American Innovations, Inc.5	EPS111	MWK Industries17	Technological Arts110
Andromeda Research9	Fertik's Electronics111	Netcom17	Television Distributors60
Antique Radio Classified111	Foss Warehouse Distributors110	Novaplex, Inc.38	Test Equipment Plus29
APC net105	Gateway Electronics, Inc.82	NovaTech Industries, Inc.19	Test Equipment Sales24
Ar ² Communications Products15	General Device Instruments9, 110	Ohio Automation, Inc.110	Test Lab Co.15
Axin Financial Services, Inc.5	Global Connections85	Optoelectronics119	The Filter Company103
Base2 Computer Corp.7	Greenleaf Electronics61	One Stop Supplier11	The Greater Baltimore Harbor and Computerfest15
Basic Electrical Supply & Warehousing Corp.36	Halted Specialties Co.3	OWI31	The M.O.O. Corp.10
Battery-Tech, Inc.23	H.T. Orr Computer Supplies104	Parallax, Inc.Back Cover	The RF Connection81
Baylin Publications15	ICE Technology, Inc.111	ParaMax, Inc.104	Timeless Products10
BCD Electro110	Index Publishing Group, Inc.11	PATCO Service, Inc.35	TNR Technical, Inc.75
Bell Electronics23	Information Unlimited30	Phelps Instruments25	Tropical Harbor9
Bismar Computer, Inc.10	Intronics, Inc.24	Pioneer Hill Software92	Unicom Electronics85
Brigar Electronics77	I.S.E., Inc.6	Plazac Sales, Inc.70	USI Corp.16
BrownDog Prototypes110	J & M Microtek, Inc.6	Polaris Industries70	U.T.S. Wholesalers92
C & S Sales, Inc.68, 94	Jade Products, Inc.110	Prairie Digital, Inc.111	V&V Mach. & Equipment, Inc.111
C and H Sales Company91	Javanco103	Prime Electronic Components, Inc.67	VersaTech Electronics11
CA Grapevine9	Jectech110	Quality Electronics29	Viking International91
Capital Electronics, Inc.37, 104	Kable Works, Inc.104	R & S Surplus8	Virtual Reality Publishing23
Cellular Technology Group93	KDE Electronics Corp.98	Ramsey Electronics, Inc.58	Vision and Motion Surplus88
CEPCO105	Kimtronix83	Reboot Electronics, Inc.7	Visitect, Inc.69
Chenesko Products, Inc.47	Koll-Dove76	Resources Un-Ltd.106	Visual Concept24
Consumertronics39	La Paz Electronics Int'l.18	R.E. Smith110	Weeder Technologies14
Converters, LTD.74	M2L Electronics50	RF Parts25	Western Test Systems32-33
Corporate Systems Center69	MCM Electronics51	Roger's Systems Specialist118	White-Star Electronics14
Creative Micro Electronics, Inc.44	MDM Radio, Ltd.17	S & N Cellular70	Wholesale Cable103
Cruising Equipment Co.7	Media-Tech International29	Scott Edwards Electronics75	Xandi Electronics, Inc.86
Cunard Associates16	Metric Equipment Sales, Inc.24	Shreve Systems110	
		Sinaco Electronic110	

ADVERTISER'S INDEX

**FIND
WHAT YOU NEED
by product/category.**

AMATEUR RADIO & TV

Abacom Technologies	83
Aljon Technologies, Inc.	69
MDM Radio Ltd.	17
Milestone Products	51
USI Corp.	16

BATTERIES/CHARGERS

Battery-Tech, Inc.	23
Cruising Equipment Co.	7
Cunard Associates	16
E.H. Yost & Co.	35
Mr. NiCd	35
Solutions Cubed	111
TNR Technical, Inc.	75
Vision and Motion Surplus	88

BUYING ELECTRONIC SURPLUS

ABC Electronics	69
Bell Electronics	23
C and H Sales Company	91
Dexis	50, 111
Metric Equipment Sales, Inc.	24
MHZ Electronics, Inc.	7
MWK Industries	17
Skycraft Parts & Surplus, Inc.	5

CABLE TV

Basic Electrical Supply & Warehousing Corp.	36
Converters, LTD.	74
Digicom Communications, Inc.	16
Direct Cable Supply	112
Foss Warehouse Distributors	110
Greenleaf Electronics	61
I.S.E., Inc.	6
Kable Works, Inc.	104
KDE Electronics Corp.	98
Kimtronix	83
Media-Tech International	29
Modern Communications	18
Modern Electronics	47
Mo-Tech Dist.	5, 105
Novaplex, Inc.	98
One Stop Supplier	11
Plazac Sales, Inc.	70
Quality Electronics	29
Televue Distributors	60
The Filter Company	103
Timeless Products	10
U.T.S. Wholesalers	92
Visual Concept	24
White-Star Electronics	14
Wholesale Cable	103

CB/SCANNERS

Optoelectronics	119
Index Publishing Group, Inc.	11
USI Corp.	16

CCD CAMERAS/VIDEO

All Phase Video-Security, Inc.	18
Creative Micro Electronics, Inc.	44
Detection Dynamics	111
Polaris Industries	70
Resources Un-Ltd.	106
Spy Outlet	111

COMPONENTS

Abacom Technologies	83
BrownDog Prototypes	110
Capital Electronics, Inc.	37, 104
Javanco	103
RF Parts	25
Skycraft Parts & Surplus, Inc.	5
Surplus Sales of Nebraska	75
The M.O.O. Corp.	10
Unicom Electronics	85

COMPUTER

Hardware

Allison Technology Corporation	31, 110
Alltech Electronics Co.	62
APC net	105
BCD Electro	110
Bisme Computer, Inc.	10
Corporate Systems Center	69
Earth Computer Technologies	18
EPS	111
General Device Instruments	9, 110
Halted Specialties Co.	3
La Paz Electronics Int'l.	18
Midwest Electronics	16
Prime Electronic Components, Inc.	67
Shreve Systems	110
Techniks, Inc.	110

Software

Pioneer Hill Software	92
Software Clearance Outlet	51
Virtual Reality Publishing	23

Microcontrollers / I/O Boards

Advanced Educational Systems	29
Base2 Computer Corp.	7
Bisme Computer, Inc.	10
Earth Computer Technologies	18
EMAC, Inc.	83
J & M Microtek, Inc.	6
Micromint, Inc.	2
Motron Electronics	25
NovaTech Industries, Inc.	19
Ohio Automation, Inc.	110
Parallax, Inc.	Back Cover
ParaMax, Inc.	104
Prairie Digital, Inc.	111
Reboot Electronics, Inc.	7
R.E. Smith	110
Scott Edwards Electronics	75
Square 1 Electronics	6
Technological Arts	110
VersaTech Electronics	11

Printer Supplies

Chenesko Products, Inc.	47
H.T. Orr Computer Supplies	104

DESIGN/ENGINEERING/ SERVICES

BrownDog Prototypes	110
Capital Electronics, Inc.	37, 104
V&V Mach. & Equipment, Inc.	111

EDUCATION

Advanced Educational Systems	29
EMAC, Inc.	83

EVENTS/SHOWS

ACP Super Store	24
Koll-Dove	76

The Greater Baltimore Hamboree and Computerfest	15
Tropical Hamboree	9

KITS

C & S Sales, Inc.	68, 94
Electronic Rainbow Ind., Inc.	46
Gateway Electronics, Inc.	82
Ramsey Electronics, Inc.	58
Scott Edwards Electronics	75
Unicom Electronics	85
Weeder Technologies	14
Xandi Electronics, Inc.	86

LASERS

Information Unlimited	30
MWK Industries	17
Resources Un-Ltd.	106

MISC/SURPLUS

Aljon Technologies, Inc.	69
All Electronics Corporation	57
Alltech Electronics Co.	62
Alltronics	45
Axin Financial Services, Inc.	5
Brigar Electronics	77
C and H Sales Company	91
Consumertronics	39
Creative Micro Electronics, Inc.	44
Cruising Equipment Co.	7
Electronic Rainbow Ind., Inc.	46
Fertik's Electronics	111
Gateway Electronics, Inc.	82
Halted Specialties Co.	3
Information Unlimited	30
Javanco	103
MCM Electronics	51
MDM Radio Ltd.	17
Prime Electronic Components, Inc.	67
Ramsey Electronics, Inc.	58
Resources Un-Ltd.	106
Roger's Systems Specialist	118
Shreve Systems	110
Skycraft Parts & Surplus, Inc.	5
Surplus Traders	110
Unicom Electronics	85
Viking International	91
Vision and Motion Surplus	88
Visitect, Inc.	69
Weeder Technologies	14

PROGRAMMERS

Andromeda Research	9
Electronic Engineering Tools	110
General Device Instruments	9, 110
ICE Technology, Inc.	111
Intronics, Inc.	24
M ² L Electronics	50
microEngineering Labs	81
Sinaco Electronic	110

PUBLICATIONS

Antique Radio Classified	111
Baylin Publications	15
Consumertronics	39
Index Publishing Group, Inc.	11
Jade Products, Inc.	110
Mouser Electronics	31
Netcom	17
Square 1 Electronics	6
Synergetics	89

Virtual Reality Publishing	23
----------------------------	----

ROBOTICS

OWI	31
-----	----

SATELLITE

Baylin Publications	15
---------------------	----

SECURITY

All Phase Video-Security, Inc.	18
American Innovations, Inc.	5
Ar ² Communications Products	15
CEPCO	105
Polaris Industries	70
Spy Outlet	111
Street Smart Security	8
Visitect, Inc.	69

SOLAR EQUIPMENT

Solar Electric Inc.	111
---------------------	-----

TELEPHONE/CELLULAR

AAA Trading/Audiopaging, Inc.	92
American Innovations, Inc.	5
Ar ² Communications Products	15
CA Grapevine	9
Cellular Technology Group	93
Consumertronics	39
Electronic Service & Supplies	83
Jectech	110
M.F.M. Communications	74
S & N Cellular	70
Technical Advisory Group	76
Weeder Technologies	14

TEST EQUIPMENT

ABC Electronics	69
Alfa Electronics	56
Allison Technology Corporation	31, 110
Bell Electronics	23
C & S Sales, Inc.	68, 94
C and H Sales Company	91
Danbar Sales Company	59
Dexis	50, 111
Electro Tool, Inc.	47
MCM Electronics	51
Metric Equipment Sales, Inc.	24
MHZ Electronics, Inc.	7
Phelps Instruments	25
R & S Surplus	8
Test Equipment Plus	29
Test Equipment Sales	24
Test Lab Co.	15
Western Test Systems	32-33

TOOLS

Electro Tool, Inc.	47
MCM Electronics	51
PATCO Service, Inc.	35
Roger's Systems Specialist	118
White-Star Electronics	14

WIRE/CABLE & CONNECTORS

Global Connections	85
Javanco	103
PATCO Service, Inc.	35
Roger's Systems Specialist	118
The RF Connection	81

Use this index-by-product to find what you need FAST!

Roger's Systems Specialist

800-366-0579

"We Have Great Connections"

Internet Catalog Online! <http://www.rogerssystems.com>

Cables ★ Connectors ★ Accessories

Computer • Telecommunications • Network • Audio • Video

Stereo Headphones

Digital CD Quality, Lightweight, exceptional sound

9' cord-3.5mm stereo plug
Sensitivity: 102dB/mW at 1KHz
Freq. Resp: 20-20,000 Hz
Impedance: 32




#TM-170 \$5⁰⁰ each
10/\$4.00 each

Centronics Adaptors

DB25 male to 36 pin female Centronics
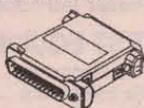
#CA-180
\$2⁰⁰ each
20/\$1.60 each
50/\$1.20 each



12" Gooseneck Microphone


Condenser style 3.5mm, Stereo plug
Fits any sound card or voice modem
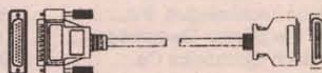
#TM-MIC-3
\$4⁰⁰ each



I-EEE-1284 Printer Cable

10' Bi-Directional
DB25 Male to Mini Centronic 36
A.K.A type "A" - "C"



#CC-PR6-BIMIN
\$5⁰⁰ each
20/\$3.00 each

12v DC Fan

3 1/8" x 1" Ball Bearing type
Standard replacement fan for
PC/AT mini-tall towers

#TM-FAN
\$3⁰⁰ each
20/\$2.50 each



Mini Stereo Extension

6ft. 3.5 mm male-female



#AC-559
\$1⁰⁰ each
50 & up .75¢

SCSI Cable


36" 50 pin 2 device


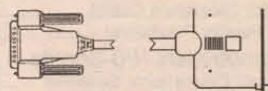
#CC-344
\$3⁰⁰ each
20/\$2.60 each 50/\$2.30

SCSI Cable


IBM or MAC Controller to devise
DB25 to 50 pin Centronics male to male


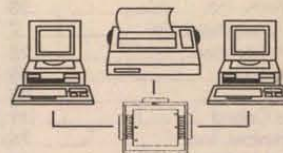
#CC-669
3 foot \$3⁰⁰ each
20/\$1.75 each

2 Computers to 1 Parallel Printer

Manual/Auto Switch • Easy to install and operate
All DB25 female connections



#DS-201P \$8⁰⁰ each

TV/VCR Cables

Quick connect "F" to "F"

Heavy duty 24K gold connectors
Double shielded
Double insulated
Clear jacket
Limited Quantity!
Professional quality




6 Foot #VC-6FF-QG

\$1⁰⁰ each

Computer Power Cord

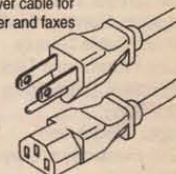
standard 6' power cable for
computer, printer and faxes



#CC-PWC \$1⁵⁰ each
20/\$1.25 each

SCSI 1 to SCSI 1 Cable


50 pin Centronics male to male

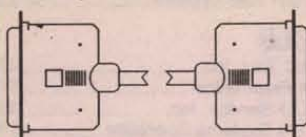

#CC-676-E
6 foot \$3⁰⁰ each 20/\$2.00

AT Modem Cable

DB25 male to DB9 Female

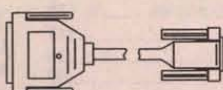

Close out
9 foot #CC-906 \$1⁵⁰ each

10' Bi-Directional Printer cable


DB25 male to standard 36 centronics


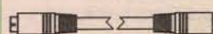
#CC-PRI-1284 \$10⁰⁰ each

S-Video Cable

4ft cable
Oxygen-Free wire
4 pin mini
male to male



#VC-735-4
\$1⁰⁰ each
50/\$.75

Computer Power Center

Five outlet-Surge Protected
Phone/Fax/Modem
3 M.O.V. protection model
EMI /RFI filters
U.L. & CSA listed
Ultra slim housing
Computer beige color
15 amp circuit breaker
Heavy duty 14/3 cord



#TM-201
\$22⁰⁰ each 5/\$19.50 each

Heat Sink with Fan - New Low Price!

Easy power hook-up! Works with ZIF Socket. Clips to Chip.


Sleeve Bearing

#TM-FAN-2 486 CPU \$5⁰⁰ each

#TM-FAN-90 Pentium CPU, 75-150 MHz \$6⁰⁰ each

Ball Bearing

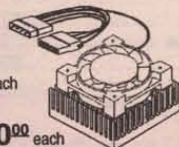
#TM-FAN-90BB Pentium CPU, 75-150 MHz \$10⁰⁰ each



DB25 Null Modem Adaptor

for serial printer and plotters
male to female

#CA-134
\$2⁰⁰ each
20/\$1.60 50/\$1.40

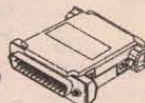

10 Base-T Cables

Category 5

\$2⁵⁰ 3ft #TE-038-L5

\$3⁰⁰ 7ft #TE-068-L5

\$4⁰⁰ 14ft #TE-128-L5

\$6⁰⁰ 25ft #TE-258-L5

\$12⁰⁰ 50ft #TE-508-L5

\$20⁰⁰ 100ft #TE-108-L5

805-288-2288 Remember, We Have Great Connections...For You! Fax 805-288-2293

\$10.00 minimum order required • Add \$4.50 shipping for pre-paid orders
California residents add 8.25% tax • eMail Sales@RogersSystems.com
Call for quantity discounts • No out of state checks accepted • Most orders shipped same day
21021-504 Soledad Canyon Road, Santa Clarita, CA 91351

Some items limited to
stock on hand.

Drawings are
representations only.



**NEW
Xplorer**

It's a receiver

a counter, a recorder, a decoder...



U.S. Patent No. 5,971,402



•Two-Line LCD display, first line displays frequency. Second line switches between either CTCSS, DCS, DTMF, Signal Strength, or Numerical Deviation.

NMEA-0183 GPS Interface, Connect your GPS to the Xplorer for Mapping applications. (GPS and Mapping Software not included)

The New Xplorer Test Receiver. Ideal for any two-way communications testing or monitoring. The Xplorer is a value packed performer integrating the functions of a CTCSS, DCS, and DTMF Decoder, Frequency Recorder, Nearfield Receiver and more into one hand-held unit. No more guessing when programming a frequency for monitoring-the Xplorer captures nearfield frequencies off the air from 30MHz - 2GHz in less than 1 second. The New Xplorer; providing the power of handheld portability with state of the art functionality and performance.



•Built-in Speaker. All frequencies received are demodulated for instant monitoring.

and the last instrument you will ever **NEED.**

Features & Specifications

- Frequency Lock Out, Manual Skip, and Auto or Manual Hold
- Internal Speaker, Audio Earphone/Headphone Jack
- Built-in PC Interface, PC Connection Cable and Download Software included
- Relative ten segment Signal Strength Bargraph
- Optimum Maximized Sensitivity for increased nearfield distance reception
- Tape Control Output with Tape Recorder Pause control relay and DTMF Encoder for audio data recording
- High speed FM Communications Nearfield Receiver, sweeps 30MHz - 2GHz in less than 1 second
- Two line LCD displays Frequency and either CTCSS, DCS, DTMF, Deviation or Signal Strength
- NMEA-0183 GPS Interface provides tagging data with location for mapping applications
- Frequency Recording Memory Register logs 500 frequencies with Time, Date, Number of Hits and Latitude/Longitude. (Latitude & Longitude coordinates are only displayed in memory when used with GPS)
- Real-Time Clock/Calendar with lithium battery back-up
- Built-in Rapid Charge NiCad Batteries with 5 hour discharge time and Power Supply included
- Numerical Deviation Display with 1-10kHz and 10-100kHz ranges
- Telescoping Whip full range Antenna included



•Easy touch control pad. F1 & F2 keys control all Xplorer functions. Hold, Skip, Store and Lockout all enabled through the keypad.

Introductory Price
\$899

FACTORY DIRECT ORDER LINE 800-327-5912
OPTOELECTRONICS

5821 NE 14th Avenue • Ft Lauderdale, FL • 33334 • Tel: 954-771-2050 • Fax: 954-771-2052
Visa • MasterCard • C.O.D.

Prices and Specifications are subject to change without notice or obligation
* Contact Optoelectronics for mapping software available

Check Out Our Web Site:
optoelectronics.com

BASIC STAMP[®] COMPUTERS

Tiny computers run PBASIC[™] programs

BASIC Stamps are component-sized computers that run PBASIC programs. They have 8 or 16 I/O lines, which can be used for a variety of digital and analog purposes. And their language is both familiar and extensive; the language includes FOR...NEXT, IF...THEN, and GOTO, as well as XOUT, SHIFTOUT, DTMFOUR, and other special commands.

If you've heard about BASIC Stamps, but never took the plunge, now you can do so for less. We now offer a "Starter Kit" for just \$79. The kit contains everything you need to get your feet wet.

**New
BASIC Stamp
Starter Kit for \$79!**
Contains our original
BASIC Stamp rev. D,
plus software, cable,
and manual.



FaxBack
#6002

BS1-IC Module **\$49**
16 I/O lines
500 instructions max.
4000 instructions/sec.
50k baud serial I/O
24-pin DIP module

Same I/O instructions as BS1, plus touch-tones, frequency generation, pulse counting, serial shift registers, X-10 powerline control, etc. I/O functions common to both modules have a higher resolution on the BS2-IC, due to its faster clock speed.



FaxBack #6004

BS1-IC Module **\$34**
8 I/O lines
80 instructions max.
2000 instructions/sec.
2400 baud serial I/O
14-pin SIP module

I/O instructions for pushbuttons, potentiometers, pulse measurement, PWM, serial I/O, sound, etc.

Programming Package **\$99**
Contains items needed to program BASIC Stamp modules; includes cables, PC software, manuals, and free technical support.

Carrier Boards **\$15-\$20**
Provide small prototyping area, 9-volt battery clips, and programming connector. Not absolutely necessary, but recommended to make programming and experimentation easy.

New! 4-line Serial LCD **\$109**
New 4-line serial LCD display is fun and useful for projects that require interaction with people. The display only takes one I/O line to operate, and can be controlled using simple SEROUT instructions in your BASIC Stamp programs.



Charles Walsh and his students in Great Falls, Montana, use BASIC Stamps in robotics projects.



Marvin Green and his students in Hillsboro, Oregon, use BASIC Stamps to make small robots.



John McLean uses BASIC Stamps to gather data in Lechugulla Cave (America's deepest cave, located in Carlsbad Caverns National Park).



Isaac Kurtz and John Bishop use BASIC Stamps in artificial hands at the Bloorview MacMillan Centre in Toronto, Canada.

Although it may be difficult to see here, that's a BS1-IC next to the white wires.

BASIC Stamp discussion list on the Net!

The list works like this: lots of people (currently 900) subscribe to the list, and then all questions and answers to the list are distributed to all members. It's a fun, fast, and free way to discuss BASIC Stamp issues.

To subscribe to the list, send email to majordomo@parallaxinc.com and write **subscribe stamps** in the body of the message.

PARALLAX

3805 Atherton Road, #102 • Rocklin, CA 95765 • USA • Toll-Free Sales: (888) 512-1024 • Office/tech. support: (916) 624-8333 • Fax: 624-8003
FaxBack: 624-1869 • E-mail: info@parallaxinc.com • Ftp: <ftp://ftp.parallaxinc.com> • <http://www.parallaxinc.com>

Australia +61 39 720 5344, +61 67 722 777 • Austria +49 241 918 90 0 • Belgium +32 4 377 5151 • Bulgaria +359 2 72 77 50 • Brazil +55 11 453 5588, +55 11 801 0045 • Canada (514) 336-9426 • Czech Republic +42 49 5813 252 • Finland +358 31 266 1885 • France +33 3 20 52 98 52 • Germany +49 241 918 90 0 • Greece +30 1 902 0115 • Hong Kong +852 2720 0255 • Hungary +36 1163 2879 • India +91 422 232 561 • Ireland +44 1 977 683 665 • Israel +972 3 498 543 • Italy +39 0542 55400 • Japan +81 3 3251 1779 • Netherlands +31 10 450 4949 • New Zealand +61 39 720 5344, +61 67 722 777 • Poland +48 34 648 882 • Singapore +65 746 8182 • Slovak Republic +42 7 580 2574 • South Africa +27 11 493 6242 • Sweden +46 70 576 14 54, +46 431 41 00 88 • Switzerland +49 241 918 900 • Taiwan +886 2 647 1978 • United Kingdom +44 1 977 683 665 • United States (800) 344-4539 (Digi-Key), (800) 831-4242 (Jameco), (800) 538-5000 (JDR)

PBASIC, BS1-IC, and BS2-IC are trademarks and BASIC Stamp & the Parallax logo are registered trademarks of Parallax, Inc. • Prices do not include shipping and applicable sales tax • Features and prices subject to change without notice. Prices are U.S. prices only; prices in other countries may vary.

0996NVSL

Write in 194 on Reader Service Card.

NUTS & VOLTS MAGAZINE
430 PRINCELAND COURT
CORONA, CA 91719

ADDRESS CORRECTION REQUESTED

BULK RATE
U.S. POSTAGE
PAID
V.Q.S.
ENTERPRISES