



**BOTH SINGLE AND DUAL DRIVE  
MODELS AVAILABLE.**

**MULTIMEDIA PROCESSOR  
ACCELERATES DUPLICATION.**

**EXTERNAL SCSI-II PORT WORKS  
LIKE A STANDARD CD WRITER  
FOR CREATING CUSTOM DISKS.**



**TOTALLY SELF CONTAINED,  
NO CONNECTION TO A PC  
IS REQUIRED.**

**INTERNAL A/V HARD  
DRIVE STORES DISK IMAGES  
FOR MULTIPLE COPIES, AND  
CUSTOM AUDIO DISKS.**

**ADVANCED FORMAT  
DETECTION PRODUCES  
PERFECT DUPLICATES ON  
STANDARD CD-R MEDIA.**

# COPY ANY CD INSTANTLY. NO PC REQUIRED.

## **CD DUPE-IT!**

Instantly duplicate CD-ROM disks for software distribution. Make backup copies of your favorite software on rugged, permanent media. Produce disks quickly and economically. No mastering or multimedia experience is required.

Insert your original disk and press "start." The multimedia processor quickly copies any disk to the internal A/V hard drive. Insert blank disks and make as many copies as you like. You'll produce identical, bit-for-bit duplicates. The system is totally self contained—no connection to a PC or Mac is required. Just

**BUY MANUFACTURER DIRECT: \$995  
408 330-5542**

plug in the power cord and press "start"—it's that easy.

You can even make your own custom audio disks without a PC! Insert your original CD's, select the tracks you want, and CD Dupe-It will copy them to the internal hard drive. Then insert a blank CD, and you'll have a custom audio disk with just the songs you want.

With the included CD mastering software, CD Dupe-It will work overtime as your personal CD mastering system. Just attach a SCSI

cable to your PC or Mac, and you're ready to design and create your own original CD's. Similar systems used in duplication houses cost over \$10,000. Now you can easily copy disks yourself for a fraction of the price.



**CORPORATE SYSTEMS CENTER**  
3310 WOODWARD AVE., SANTA CLARA, CA 95054  
[WWW.CORPSYS.COM](http://WWW.CORPSYS.COM)

Software publishers—ask about our high-volume multi-drive duplication systems.  
CD Dupe-It is sold and intended for backup and in-house design purposes only. Copyright laws must be observed.

...brings you a potpourri of high-tech goodies for the techno-tinkerer! For thirty years we have been your source for Silicon Valley exotica!

## CyberEye Color Video Camera!



- High-quality (nice looking too!) composite color camera
- 1/4 inch CCD sensor w/auto white balance control
- Resolution: NTSC 542 x 492 (250,000 pixel)
- Manual focus knob/ring, 5mm to infinity
- Power: 5.0 VDC @ 180 mA. Supply from PC or keyboard power...no external adapter needed!
- Now, also available as a kit with PCI video capture card!

HSC#17535 Camera alone **\$69.00**  
HSC#17702 Kit with camera, card **\$99.00**

## ATX Pentium Motherboard

- Support for Intel Pentium 90-200, 166-200 MMX CPU's
- Also supports Cyrix/IBM 6x86 P, PR 150 & 166 CPU's
- Also supports AMD K5, and, with special VRM, K6 CPU's
- 4 PCI slots, 4 ISA slots (one shared), 16-bit stereo sound
- 4 DIMM RAM sockets, parity or non-parity, ECC, EDO, FP
- On-board 2 x IDE, 2 x 16550 Serial ports, 1 parallel port
- New, 90-day warranty (CPU not included)



HSC# 80437 **\$49.95**  
ATX style Midtower case, fits above motherboard  
"Netpower" logo on front, never used, 90-day warranty  
HSC# 17517 **\$29.95**

## Workhorse Hard Drives!

- Seagate with SCSI interface full-height drives
- Good, Reliable drives for many applications
- Choose from 670 or 330 MB size
- With 90-day warranty!



HSC#17556 ST4766N **\$35.00**  
HSC#17557 ST4385N **\$29.00**

## Video-hacker Dream!

- Logitech Videoman Video-conference camera & interface
- These units were sold with Hewlett Packard S-700 workstations for videoconference capability
- We do not have technical data, software or manuals
- All we have is cameras with stand, and SCSI-II interface
- The camera is on a weighted stand that extends from 13" tall to over 20" tall, and has a stereo microphone
- Color camera is digital output only (not NTSC) as far as we can tell -- but who knows?
- Interface box has two SCSI-II ports on back, and a DC power input (we do not have the adapter), and on the front it has a mic, out jack, composite video out (BNC), and the connector for the camera cable.
- Note: HP and Logitech will provide no information on these



HSC#17503 **\$39.95**


## Drive-bay Amp & Equalizer

- Made by NEC, fits into standard 5.25" drive bay
- 5-Band equalizer has 4 channels, 6 watts RMS/channel
- 25 watts RMS total power output
- Headphone jack on front panel
- Connects to drive power connector
- No special software or drivers req'd!
- Compatible with any sound card
- Brand new, 90-day warranty



HSC#17534 **\$19.95**

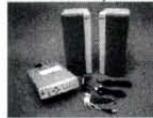- Also available, amplifier kit with matching speakers
- Same amplifier unit as above
- NEC Speakers are 11" tall, 4.5" wide
- Speakers have 4" 40-watt woofer, 1" dome tweeter
- Includes all cables, hookup accessories
- New in plain brown box, 90-day warranty



HSC#80462 **\$39.95**

## Fujitsu 1 GB Drives

- Model #s M1606S, M2694E \$ M2932SA
- SCSI Interface - 3.5" size, includes 5.25" brackets
- Tested good and DOS formatted
- Used - w/90-day warranty!



HSC#17555 **New Price!! \$69.00**

## RAID Server Chassis

- Trimm H420 Super Server rack-mount chassis will accommodate a high-end multiprocessor system board with a PCI RAID controller.
- Slots for eight RAID drives on removable slides
- Space for two CD-ROM or tape drives
- Three hot-swappable power supplies (300W) included
- Environmental processor and LCD display
- Supports ATX motherboard (not included)
- Can also accommodate Alpha or SPARC system boards
- Three 95 CFM fans and one 17 CFM blower
- Measures 17.75" high, 19" wide, 17" deep
- New in box, with rack slides, 90-day warranty



HSC#80463 **\$395.00**

## Corel Office Professional 7

- Great Software Bundle -- Amazing Value!
- Includes Corel Wordperfect 7, Corel Quattro Pro 7, Paradox 7, Corel Presentations 7, CorelDRAW 6, CorelFLOW 3, Sidekick 95, Netscape Navigator, Dash board 95, 1000 fonts, 10000 clip-art images, more!
- For Windows 95, Windows NT 3.51 and Windows NT 4.0
- Distributed on CD-ROMs, with hefty manual pack
- New, shrink-wrapped in box, 90-day warranty

HSC#80436 **\$47.50**

## PCI-Bus 56K Modem!

- Genica PCI-Bus 56K Modem at unheard-of price!
- Data, FAX, voice, full V.90 compatibility
- Voice from handset
- Windows 95/98 or NT only (Not Win 3.1 compatible)
- Uses latest Lucent chipset, comes with Lucent drivers
- New retail box, with Trio application software on CD
- 90-Day Warranty



HSC#17532 **\$39.95**

## Laptop Carrying Cases

- Two sizes, 12" x 9.5" x 1.5" and 12.5" x 10" x 2" inside dim.
- Both have velcro-sealed outer pouch, padded shoulder strap with heavy-duty swivel hooks, zipper closure.
- Handsome black vinyl "leather-grain" exterior
- Cushiony plush interior protects your laptop's case

HSC#17662 Large size case **\$22.50**  
HSC#17663 Small size case **\$17.50**

## CRT Test/Rejuvenator

- B & K Dynascan Model 470
- Tests color and B & W CRT's
- Test emission, leakage, life, tracking (color tubes) - manual included
- Rejuvenates cathodes, cleans and balances guns, removes shorts
- New in box, 90-day warranty



HSC#17617 **\$49.95**

## PCMCIA Sound Card!

### Media Vision PCMCIA Sound Card

- Great for Portables, Laptops with PCMCIA Slot
- External pod has joystick port, mic, input, line in & line out jacks, volume control.
- Install software, inst. included.
- Win 3.x, W95 compatible
- New in OEM pkg (no box), 90-day HSC warranty
- We had these before at \$39.95 and they went fast!



HSC#17036 **\$29.95**

## Viewsonic SVGA Monitor

- Great monitor for a great price! Viewsonic model E641
- 14" SVGA Multifrequency up to 1024 x 768 resolution
- Microprocessor-based push-button controls
- 28 mm dot pitch, Energy Star power management
- New in box, 90-day warranty



HSC#17690 **\$109.95**

## Take Your Pick of Floppies!

- Teac 1.44MB 3.5" Floppy Drive
- Industry standard floppy drive, beige face plate
- New OEM Pack, 90-day warranty



HSC#17654 **\$19.95**

- Citizen W1D 1.44 MB floppy measures only .43" thick!
- Interface is 26 conductor 1mm pitch printed ribbon cable
- Short (1.25") ribbon cable included
- Black bezel -- New OEM Pack, 90-day warranty
- Sorry, we do not know which laptops will accept this drive!



HSC#17587 **\$25.00**

- Teac FD-05 HF 230-U 1.44 MB Laptop floppy - same specs as Citizen



HSC#17694 **\$29.00**

## CD-ROM Writer/Readers!

- Ricoh RS-1060C CD Recorder/Player System
- SCSI Interface, 2x4 (2-speed write, 4-speed read)
- External type, case is 9.75" x 2" x 11" deep
- Caddy type, includes caddy, power cord, driver disk
- New in OEM box with manual, 90-day warranty




HSC#17567 **\$199.00**

- Also available (only a few!) internal IDE type 2 x 6 speed
- Sony CDU29E (factory refurb), caddy type, \$169.00

## Pentium-Pro Power!
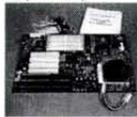
### High quality Micronics motherboards using the Intel Pentium-Pro chip at incredible savings!

- DE-IN "Invader" AT motherboard has 4 PCI, 3 ISA slots
- Built-in Primary & Secondary IDE controller, floppy controller, IR port, 2 SIO ports, 1 PIO port
- Comes with tested 150 MHz CPU installed
- Supports up to 384MB memory (72-pin SIMMs)
- Comes with instruction book, I/O Cables & bracket
- New in box, 90-day warranty



HSC#17629 **\$119.00**

- W6-LI "Lightning" dual CPU board has 4 PCI, 2 ISA slots
- Dual Processor motherboard, can use 1 or 2 CPU chips
- Comes with one tested 150 MHz CPU installed
- Voltage Regulator Module for second CPU included
- Built-in Primary & Secondary IDE controller, floppy controller, 2 USB ports, IR port, 2 SIO ports, 1 PIO port
- Also has Adaptive "Ultra-SCSI" fast SCSI Bus Mastering controller with 50-pin port and 68-pin ultra-wide port!
- Also has Creative Labs "Vibra 16CL" sound on board!
- Supports up to 512K memory (168-pin DIMMs)
- Full Manual & Disk set (SCSI, sound, etc.), I/O Cables
- ATX-style motherboard, new in box, 90-day warranty



HSC#17624 **\$199.00**

## Ludicrous Laser Pointer!

- How can we do this!...we don't even know!...
- Small, handy laser pen keychain pointer.
- 5 mW, bright red laser with tight beam
- Brushed gold finish with spring-loaded clasp
- Brand new, with batteries and instructions
- 90-day warranty.



HSC#17383 **\$12.50!**

## Briefcase of Goodies!



- These handsome hardshell cases were used to carry a laptop-computer estimating system (laptop not included)
- They were used with a Compaq LTE laptop, and provided a SCSI port for a CD-ROM drive with battery back-up
- Large Nicad pack has 10 Sanyo Cadnica cells.
- Built-in 19VDC power supply for battery charging
- Tiny piggy-back PC board seems to be a SCSI interface
- Case measures 18" x 14" x 7", with several compartments
- SCSI II to CENS0 SCSI cable, many great parts inside!
- Buy either the whole assembly, or just the parts you want!
- Not guaranteed to function with laptops -- for parts only!

HSC#17180 Complete Laptop Case **\$29.95**

HSC#17182 Empty Hardshell Case **\$15.00**

HSC#17181 Nicad Pack, 12.5VDC, 5AH **\$17.50**

HSC#17179 SCSI II Cable, 1 ft. long **\$12.50**



## Visit HSC's Website!


- Pay us a virtual visit on the World Wide Web!
- Simply point your browser to <http://www.halted.com>
- Site is constantly being revised, please visit often!
- Check out the amazing "Gizmo of the Week" feature!

## HSC Catalog online!

- That's right, get HSC's catalog on the World-Wide Web!
- Simply go to [www.halted.com](http://www.halted.com) and follow the big red link.
- Adobe .PDF files are available for download and viewing.
- Or drop on by and pick one up...we'd love to see you!

# It's our 20th year, and we're ready to ...

# CELEBRATE<sup>©</sup>

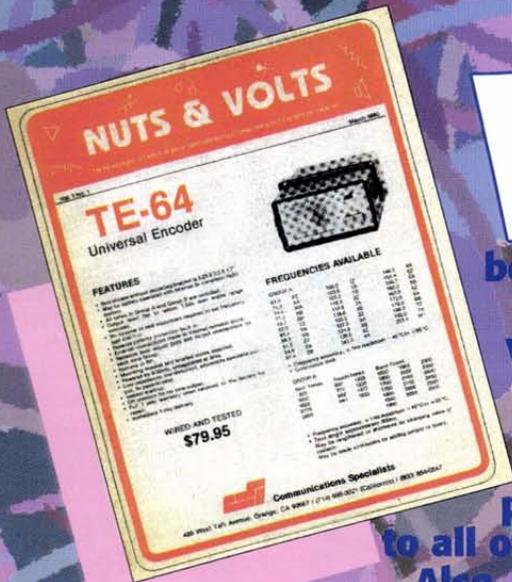

**W**e're looking forward to a stellar year in 1999, and we hope you'll be a part of it. We'll be implementing a lot of new programs this year for both the magazine and the website, plus we'll be giving existing features a face-lift.


For example, our website will be undergoing various changes over the next several months, and we will be offering things like a subscriber-only section, an extensive search engine for our index of articles, an electronics chat-room, plus we plan on having links from our website to all of our display advertisers.

Also, each month we will be having a prize drawing in which paid subscribers are automatically entered (see page 64). Prizes are provided by our display advertisers and will include both merchandise and gift certificates.

Plus, we will be starting up some new editorial and reader-interactive features, so we'll be on the look-out for new contributors to these sections. And, we'll be having some special "20th Year" promotional offers, so stay tuned for those.

We hope you'll be a part of the excitement. As we head toward the millenium, it will be increasingly important to stay on the cutting edge.

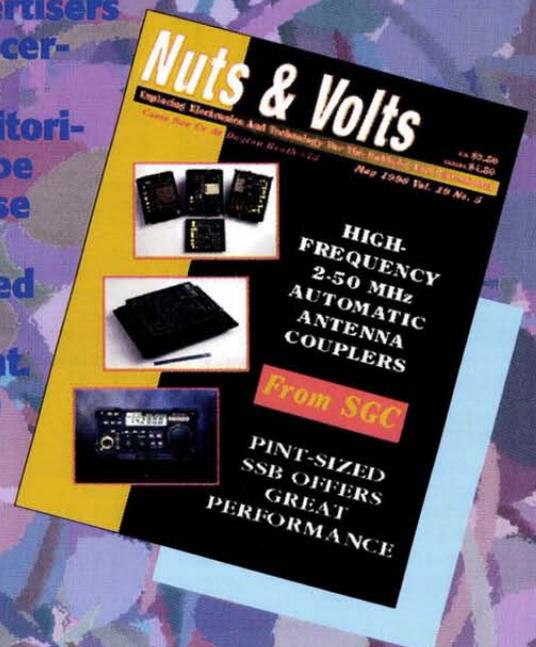And that edge is where *Nuts & Volts* plans to be!!




# Articles ...



Page 10



Page 89

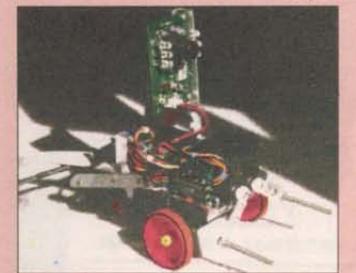

Page 76

## YOUR HOTTEST TOOL MAY BE ICE!

Been drooling over the thought of owning your own In Circuit Emulation tool? Here's one for under \$130.00!

Tim Deagan ... Page 6

## INEXPENSIVE DIGITAL TIMER

Never ruin another circuit board again with this handy device that shuts off the exposure time automatically.

Raymond C. Buck ... Page 10

## MORE WAYS TO USE LOW-COST DIGITAL METERS

If you like things that are cheap and simple but do the job, then check out these imported panel meters for under \$10.00!

John Sharp ... Page 30

## CURI vs. CAT

Integrating robots into real-world applications — in a "catty" kind of way.

George Katz ... Page 76

## (Mostly) TUNED AND TESTED

Check out these down-to-earth reviews on some "truly trick" ham equipment.

Gordon West ... Page 78

## PIC-BASED DATA ACQUISITION SYSTEM CHARACTERIZES LASER DIODES

With the huge success of CD-ROM technology, semiconductor diode lasers have become readily available and inexpensive. But now there's a new, more exciting semiconductor laser ...

Lawrence Foltzer ... Page 83

Published Monthly By  
T & L Publications, Inc.  
430 Princland Court  
Corona, CA 91719  
(909) 371-8497  
FAX (909) 371-3052

E-Mail  
editor@nutsvolts.com  
URL  
http://www.nutsvolts.com

Subscription  
Order ONLY Line  
1-800-783-4624

**PUBLISHER**  
Jack Lemieux N6ZTD  
**EDITOR**  
Larry Lemieux KD6UWV  
**MANAGING EDITOR**  
Robin Nelson KD6UWS  
**ON-THE-ROAD EXHIBIT  
COORDINATOR**  
Audrey Lemieux N6VXW  
**SUBSCRIPTIONS**  
Abby Madain  
**CLASSIFIED ADS**  
Natalie Sigafus

Copyright 1999  
by T & L Publications, Inc.  
All Rights Reserved

All advertising is subject to publisher's approval. We are not responsible for mistakes, misprints, or typographical errors. Nuts & Volts Magazine assumes no responsibility for the availability or condition of advertised items or for the honesty of the advertiser. The publisher makes no claims for the legality of any item advertised in Nuts & Volts. This is the sole responsibility of the advertiser.

Advertisers and their agencies agree to indemnify and protect the publisher from any and all claims, action, or expense arising from advertising placed in Nuts & Volts. Please send all subscription orders, correspondence, UPS, overnight mail, and artwork to: 430 Princland Court, Corona, CA 91719.

Nuts & Volts Magazine is published monthly for \$19.00 per year by T&L Publications, Inc., 430 Princland Court, Corona, CA. POSTMASTER: Send address changes to Nuts & Volts Magazine, 430 Princland Court, Corona, CA 91719.

## DEPARTMENTS

Advertiser's Index ... 70  
Classified Ad Info ... 70  
Dealer Directory ... 88  
Events Calendar ... 26  
New Product News ... 92  
News Bytes ... 29  
NV AdMart ... 68-69  
Reader Feedback ... 13  
Tech Forum ... 46

## CLASSIFIED AD INDEX

10. Ham Gear for Sale .....41  
20. Ham Gear Wanted .....41  
30. CB/Scanners .....41  
40. Music & Accessories .....42  
50. Computer Hardware .....42  
60. Computer Software .....43  
70. Computer Equip. Wanted .....43  
80. Test Equipment .....43  
85. Security .....50

90. Satellite Equipment .....51  
95. Military Surplus Electronics .....52  
100. Audio/Video/Laser .....52  
110. Cable TV .....53  
115. Telephone/Fax .....52  
120. Components .....55  
125. Microcontrollers .....55  
130. Antique Electronics .....56  
135. Aviation Electronics .....56  
140. Publications .....56

145. Robotics .....56  
150. Plans/Kits/Schematics .....57  
155. Manuals/Schematics  
Wanted .....58  
160. Misc. Electronics For Sale .....58  
170. Misc. Electronics Wanted .....59  
175. BBS & Online Services .....60  
180. Education .....60  
190. Business Opportunities .....60  
200. Repairs/Services .....61

## Columns ...

### AMATEUR ROBOTICS NOTEBOOK

Robotic goals for the new year, what it takes to go from point A to point B, and an alternative to optical encoders.

Robert Nansel ... Page 36

### ELECTRONICS Q & A

TJ Byers ... Page 16

### OPEN CHANNEL

Some interesting circuits: a "universal" IF amplifier and a logarithmic amplifier.

Joe Carr ... Page 21

### RESOURCE BIN

A look at some medical electronics.

Don Lancaster ... Page 72

### STAMP APPLICATIONS

Back to the BASICS ... find out what lies ahead for "Stampers" in the upcoming year.

Lon Glazner ... Page 28

### THE COMPUTER-CONTROLLED WORLD

Three convenient sizes of graphic LCD displays offer complete display solutions for most embedded and PC applications.

Ryan Sheldon ... Page 89

VOLUME 20  
NO. 1  
JANUARY 1999



# Your Hottest Tool May Be ICE !!

by Tim Deagan KC5QFG

**T**o a professional microcontroller developer, few tools are as useful as In Circuit Emulation, or ICE. The ability to test code while connected to the hardware it will run is a tremendous time-saver. Traditionally, ICEs can cost \$10,000.00 and up. Hobbyists on a micro-budget may drool at the thought of owning one, but that's about all.

Even though the PIC world has brought ICE prices down, \$500.00 is still considered low-cost. Nevertheless, an ICE exists that you can buy today, for under \$130.00! It's the PIC ICE II from Leading Edge Technology Ltd.

Operating from Malta (yes, the island in the Mediterranean), Leading Edge is not well known in the United States. They have one distributor in the UK — Crownhill Associates. Yet other than the web sites of those companies, there is almost no information to be found about the PIC ICE II. Still, the information you can find is very enticing!

First and foremost is the price, £59.95 (GBP) + £6.50 (GBP) shipping. In November '98, that came out to \$112.51 (US)! Even with big fluctuations in the exchange rate, that's an incredible price.

But what do you get for one-fifth the price of any other ICE? The web site lists an impressive feature set:

- Emulates all 18 and 28 pin PICs.
- Works from a standard printer port.
- On board four-channel A/D with A3 ref or VCC ref and a conversion rate of 17µS.
- OSC2 output.
- RTCC input.
- Text Editor, Assembler, Disassembler, and Simulator/Tracer.
- Single step, Go with Breakpoints, Change any register at any time, and Go without Breakpoint.
- A speed command in the editor assembler allows fine tuning, (measure OSC2 output for real-world speed calculations).
- Full 12-month guarantee.

*Let's look at these features, all of which are true, but perhaps not in the way you might expect ...*

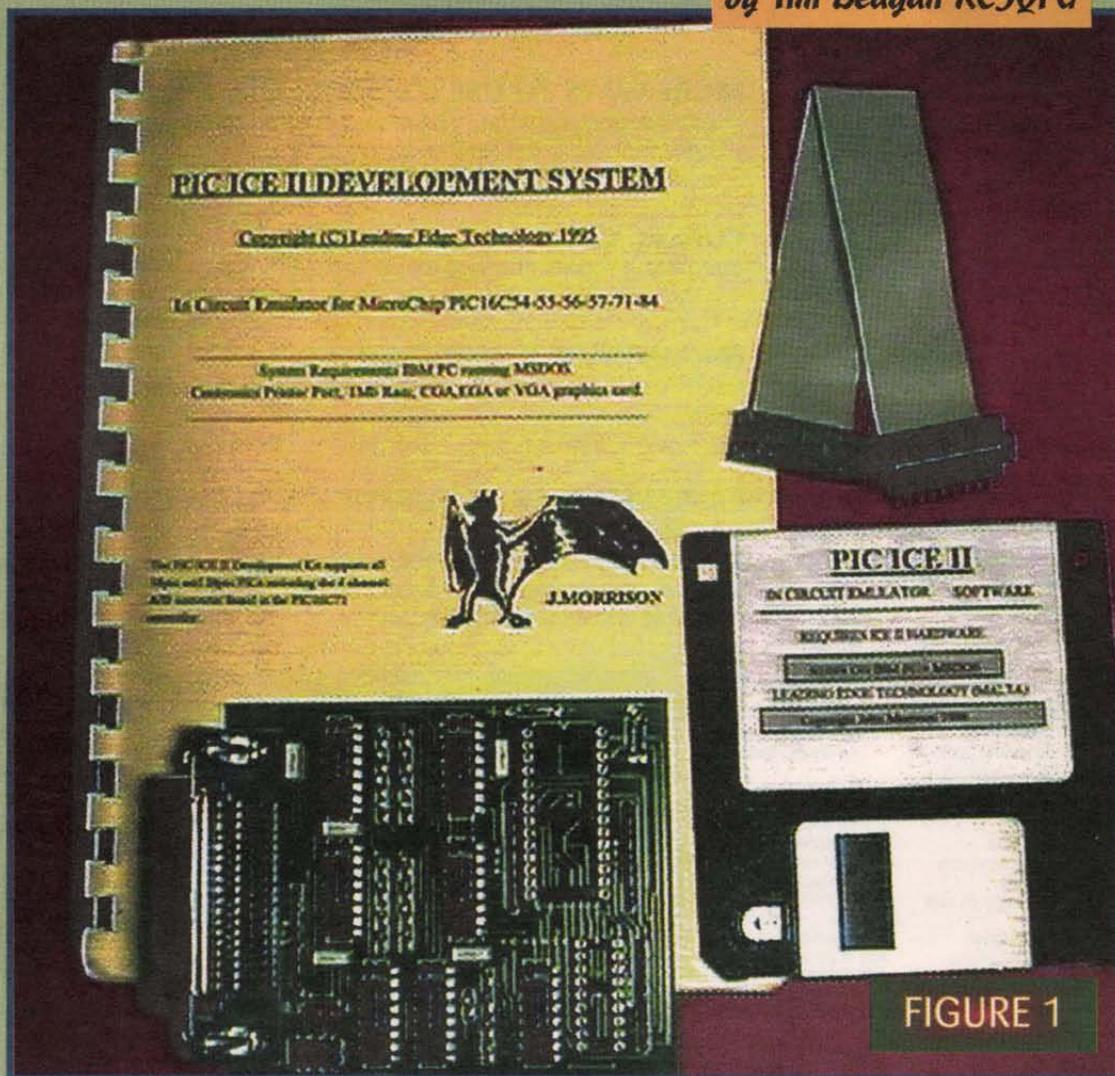


FIGURE 1

## The Components

International delivery of the PIC ICE II took three weeks. When it arrived, the envelope contained a manual, printed circuit board, 18-pin ribbon cable, and a floppy disk.

The manual consists of six front-sided pages of ICE information and three schematics for PIC circuits. Like many technical product documents, 'terse' would be an accurate description. While all the information needed to successfully use the PIC ICE II is provided, it may take a few reads through to figure this out. Luckily, the brevity makes it easy to reread a number of times.

The printed circuit board has a standard female Centronics plug for connection to a parallel port. Two DIP sockets — an 18-pin and a 28-pin — allow connection through a ribbon cable to the test

circuit. These ribbon cables have male DIP connectors on each end, allowing you to plug into the sockets where your PIC would go. The ribbon cable for the 18-pin was included, but the 28-pin cable was missing. Surprisingly enough, none of the major supply houses (Mouser, Digi-Key, JDR, Jameco) carry 28-pin DIP ribbon cable headers or pre-made cables. Somewhere this part, or its components, is available for a couple of bucks. But without it, the ICE is not usable for emulating the 28-pin PICs. Leading Edge has been E-Mailed about the cable omission, but had not replied as of this writing.


The diskette contains the main program in two versions: DEV54 for the 12-bit PICs and DEV71 for the 14-bit PICs. OBJ2BIN is included to convert a standard (Intel INHX8M) Hex file to the binary

image format the software uses. Some test, conversion, and assembly examples are also included.

## Using the PIC ICE II

The first thing that will slow down a lot of users is the speed. The PIC ICE II does not use a bond-out chip, i.e., a PIC with extra circuitry to return information about the processor internals. Instead, the PIC ICE II is a software simulator that extends its I/O out the parallel port. This design is quite clever and accounts for the low cost of the unit. However, it also means that the PIC ICE II runs at a speed dependent on the computer to which it is attached. This gives it a max speed of 7.12 KHz on a 16-MHz 386SX and 15.52 KHz on a 100-MHz 486.

The manual suggests using a

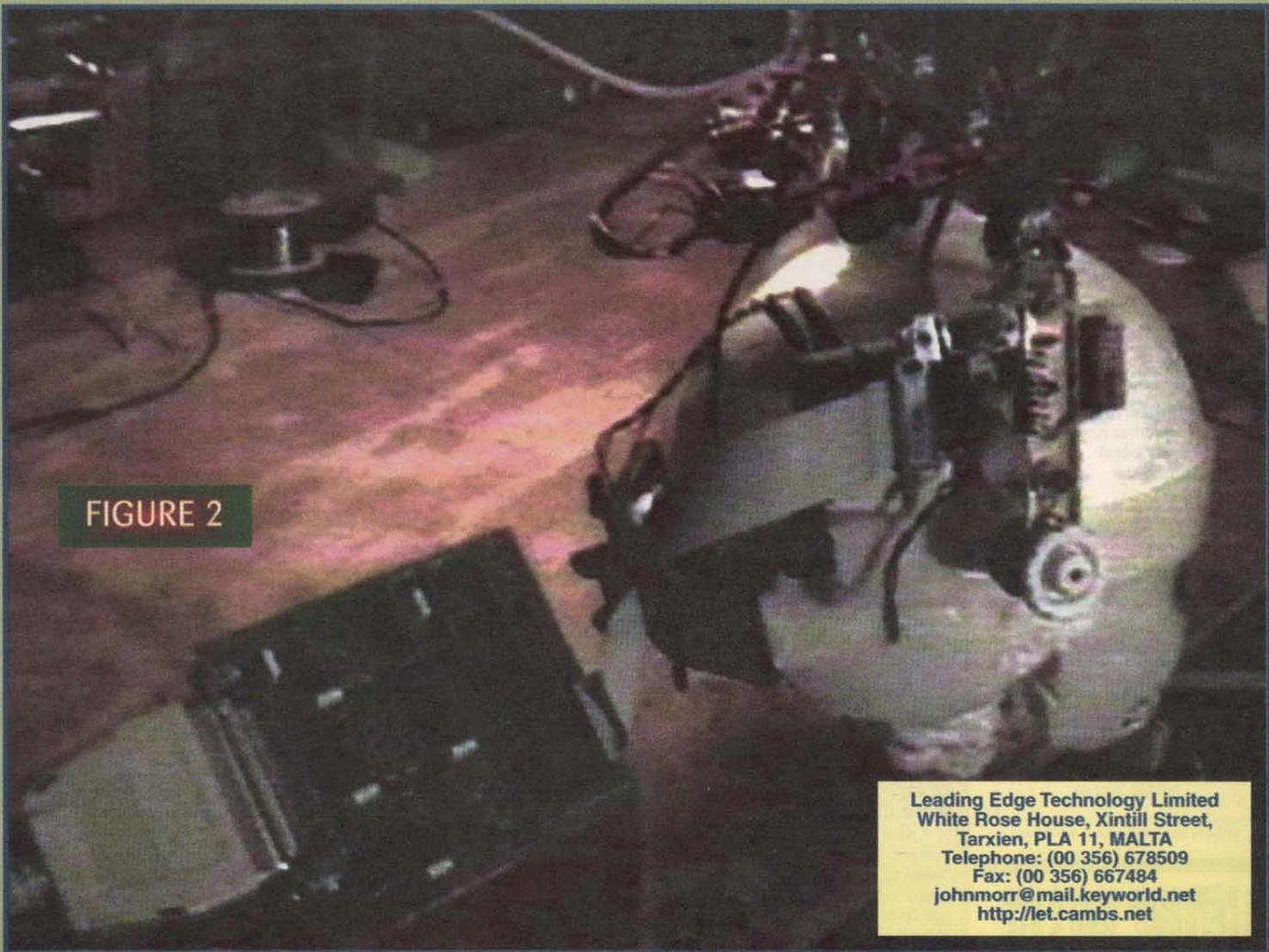

**FIGURE 2**

**Leading Edge Technology Limited**  
 White Rose House, Xintill Street,  
 Tarxien, PLA 11, MALTA  
 Telephone: (00 356) 678509  
 Fax: (00 356) 667484  
 johnmorr@mail.keyworld.net  
 http://let.cambs.net

stand-alone printer port card and adjusting the port clock speed in BIOS if available, but it's unlikely that even 1 MHz is attainable. This alone will dissuade many potential buyers. Nevertheless, it's worth pausing for a moment and thinking about what this really impacts. It means that real-time and serial port applications are tricky, if not completely impossible. Any timing-dependent project will take a lot of thought. The OSC2 does output at 1/4 the clock speed and software allows you to modify (slow down) the 'clock,' so synchronization is not completely out of the question.

Power is another area to note. The PIC ICE II is powered by the circuit under test. Any difference between the VCC in your circuit and the VCC from your parallel port can cause problems. Since parallel ports use a VCC of 5V, your circuit must provide 5V. The documentation goes on to note that 5.5V or 3.6V will not work. Many PICs have operating ranges that allow operating voltages of other than 5V.

These circuits are not candidates for the PIC ICE II.

With a few exceptions, PIC microcontrollers can source either 20 or 25mA and sink 25mA per I/O pin. When used as outputs, the PIC ICE II sources 15-20mA per

pin, but can only sink 2mA. Greater sink currents are achieved by adding pull-down resistors to the test circuit. This is described as a feature, not a bug, to keep novice users from damaging the PIC ICE II by port contention. Warning that

it will void the warranty, directions are given on how to replace specific diodes with shunts and achieve greater sink currents. Using the I/O pins as inputs requires pull-up resistors tied to 5V to achieve a logic level 1.

```

Line : 00009      Char: 01      Memory : 01051      PIC-DEV16C71/84 Version 5.06
F1 Help Esc quit.      lights71.asm      (C) John Morrison 1994/5.

-----
- Running
Demo for P
LEDS conne
Use 3mm Le
-----
rlcc
porta
portb
time_temp
wait_counter
:
begin

ADDLW (W+k)->W
ADDWF (W+f)->d
ANDLW (W & k)->W
ANDWF (W & f)->d
BCF bit clr f.b
BSF bit set f.b
BTFSZ skip if f(b)=0
BTFSF skip if f(b)=1
CALL addr
CLRF 00->f
CLRW 00->W
CLRWD 00->wdl
COMF /f,d
DECF (f-1)->d
DECFSZ (f-1)->d, skip if 00
GOTO addr
INCF (f+1)->d
INCFSZ (f+1)->d, skip if 00
IORLW (W or k)->W
IORWF (W or f)->d
MOVLW k->w
MOVE f->d
MOVWF W->f
NOP no op
OPTION W->Option
RETFIE Tos->Pc.gie
RETLW k->W.Tos->pc
RETURN Tos->pc
RLF Left shift f
RRF Right shift f
SLEEP tired?
SUBLW (k-W)->W
SUBWF (f-w)->d
SWAPF f,d
TRIS f
XORLW (W xor k)->W
XORWF (W xor f)->d
-----
: jc.jnc.jz.jnz.jmp
-----

```

**FIGURE 3**

## GPS Headquarters

### Trimble

#### Placer GPS400

**\$59.95 w/Antenna**

- 6 Channel
- Active Antenna
- RS232 / 1 pps Output

### Trimble

#### SVeeSix - CM / 3

**\$89.95**

- 6 Channel Module
- Mag. Active Antenna
- 1 pps Output
- Differential

Call for Latest List

GEOTEK GPS Equipment  
Mapping - Antennas

### Communications Surplus

4212 Mt. Vernon Houston, TX  
713-526-8000 or 1-877-878-6GPS  
Fax to 713-522-6309  
lshafer@flash.net  
Look for our ad in the  
AdMart Section

Write in 29 on Reader Service Card.

## ELECTRONIC TOOLS ETC.

### TWEEZERS, FORCEPS, SCISSORS

### \* PROBES (DENTAL PICKS)

### \* DREMEL TOOLS, ROTARY TOOL EQUIPMENT

### \* OPTICAL AIDS (MAGNIFIERS)

### \* SCREWDRIVERS, TIPS, BITS

### \* PLIERS, ALL SHAPES, SIZES

### \* NEW, HARD TO FIND TOOLS EVERYDAY

TOLL FREE: 1-888-UTOPIA-2

SAVE  
\$  
HERE!



**UTOPIA  
TOOLS**

CALL OR WRITE  
3889 BARNARD DR.  
APT. #619  
OCEANSIDE CA  
92056

CALL:  
(760) 439-6882  
FAX:  
(760) 439-6882

CALL NOW FOR FREE CATALOG

Address	Op	Op	Op	Op	File Bin	Hex	File Bin	Hex
0000	3000	begin	movlw	00				
0001	1683		bsf	03.5	00	00000000	00	18 00000000 00
0002	0085		movwf	porta	01	00000001	01	19 00000000 00
0003	0086		movwf	portb	02	00000011	03	10 00000000 00
0004	1283		bcf	03.5	03	00111000	38	18 00000000 00
0005	3040		movlw	040	04	00000000	00	1C 00000000 00
0006	0086		movwf	portb	05	00000000	00	1D 00000000 00
0007	0085		movwf	porta	06	11111111	FF	1E 00000000 00
0008	201F	right	call	wait	07	00000000	00	1F 00000000 00
0009	0C86		rff	portb	08	00000000	00	20 00000000 00
000A	1C03		btfs	03.0	09	00000000	00	21 00000000 00
000B	2808		jmp	right	0A	00000000	00	22 00000000 00
000C	0086		rff	portb	0B	00000100	04	23 00000000 00
000D	201F	left	call	wait	0C	00000000	00	24 00000000 00
000E	0086		rff	portb	0D	00000000	00	25 00000000 00
000F	1C03		btfs	03.0	0E	00000000	00	26 00000000 00
0010	280D		jmp	left	0F	00000000	00	27 00000000 00
0011	0C86		rff	portb	10	00000000	00	28 00000000 00
0012	0A85		incf	porta	11	00000000	00	29 00000000 00
0013	1D03		btfs	03.2	12	00000000	00	2A 00000000 00
0014	2808		jmp	right	13	00000000	00	2B 00000000 00
0015	3005		movlw	05	14	00000000	00	2C 00000000 00
Status: P1 P0 To Pd Z Dc C Option					15	00000000	00	2D 00000000 00
WrkF: 00000000 00 00000000 0000 11111111					16	00000000	00	2E 00000000 00
					17	00000000	00	2F 00000000 00

FIGURE 4

The analog-to-digital converter performs as advertised, working the same as it would on a 16C71. Voltage reference is either VCC or the voltage on the A3 pin. According to the datasheet, a 16C71 can have a minimum conversion time of 2mS. The PIC ICE II can convert with a minimum time of 17mS.

The software is DOS-based, running under DOS versions 3-6.2. Starting up, the text editor is the first window. Users can write assembly language programs (Microchip mnemonics) and then run them in the Trace window. Previously saved files can be opened and edited as well. The commands for editing are somewhat obscure. A full range of features (i.e., cut and paste, search, delete line) exist, but constant referral to the manual is necessary. Little things like the home key always taking you to the top of the file instead of the beginning of the line are frustrating at first. While it does claim to cover all 18- and 28-pin PICs, the software was all written before 1996. The bottom line is that any program using the 16C84 or 16C54 instruction sets is supported.

Somewhat more challenging is the implementation of the assembler directives and formatting. Hex values require a leading zero (0FA) rather than a zero-x (0xFA) or trailing h (0Fah.) Instructions must be preceded on a line by either a space or a tab, equations must not. In addition, many assemblers refer to registers in the second code page with an address like 0x86 (TRISB). This is not legal in the PIC ICE II assembler. Addresses in the second code page require switching the code page bit and then referring to that address as 0x06.

While all of these are minor annoyances, no piece of assembler code that I had previously written or acquired elsewhere would assemble without some modification. It wouldn't take much to write a PERL script or QBASIC program that would convert the files, but it's not out there at the moment. A brief line in the manual states "We recommend using the internal text editor."

However, this does not mean integration is impossible. The software has the capacity to import a binary image file created elsewhere. This allows the internal disassembler to rebuild the source in a manner it is happy with. The down side is that there is no provision for importing symbol tables. Symbols can be added manually, and saved with the disassembled .asm file. Stock listings of standard EQU statements can be block-imported in the text editor as well; more opportunities for a utility that would strip and reformat symbols from a .lst or symbol file.

The real core of the product is the Trace screen. Usage is straightforward, you can change registers, single step, step over, run to a breakpoint, or run continuously. Symbols replace hex values in the assembler listing, so code maintains some readability. It's really exciting to watch internal registers change as your hardware interacts with the code. RISC code is easy to follow in this environment, since the changes per instruction are relatively small. The software does not provide any trace buffers or history features.

A list file from an assembler or compiler becomes tremendously valuable when running imported code. Code produced using the OBJ2BIN utility occasionally gets corrupted in the first couple of bytes. Careful comparison of the addresses of code routines helps

in catching this quickly. Listings also preserve comments that do not show up in the Trace screen, making code more understandable. It's also worth noting that having an ICE doesn't lessen the value or importance of pure software simulation as a first step.

### Tool or Toy?

We've covered a lot of ground, identified a number of caveats about the product, and hopefully started some thinking about the PIC ICE II. For myself, I went through stages with the product. First, excitement and curiosity about what I might get for this really low price. Then, after it arrived, I went through a stage of frustration. It took some time to understand how to use the ICE in relation to the other tools in my environment. I went back to basics, plugging the ICE into a breadboard with LEDs and simple circuits, and just experimented.

That's when the fun started. I began to play and get comfortable with the software. After a couple more attempts to import code, I managed to get a working system. I'm now positively excited about the PIC ICE II. Sure, the software could be brought up to date with a host of improvements, but the basic functionality is all there. It's worth considering that if you bought a parallel port extension card with a programmable oscillator, multiple digital I/O lines, and four A/D channels for about \$100.00, it would be a reasonable deal. Toss in an integrated PIC emulator, disassembler and assembler and, even if you can't use it on every project, it's still a very cost-effective addition to your toolbox. The PIC ICE II is solid value for the money, opening up the ability to test code in-circuit to the hobbyist on a budget. NV

# The U.S. Government always knows exactly what time it is...do you?

New clock from Arcron uses radio signals from the U.S. Atomic Clock in Colorado to display the precise time, within a billionth of a second.


by Jake Prine



These days, timing is everything. Between meetings and appointments, deadlines and conference calls, my schedule requires that I know the time down to the minute. Even on weekends, I've got Little League games to coach, shows to tape and planes to catch. If I'm late, I'm sunk. The problem is that it's hard to be prompt if my clocks aren't correct. Even digital clocks can be inaccurate. Power outages, dead batteries, time changes...any of these can cause a clock to be inaccurate. The next thing you know, you're strolling into that important conference...an hour late. Now there's no need to worry, because advanced radio technology has produced a clock which gets the time directly from the U.S. Atomic Clock in Fort Collins, Colorado, the standard for time-keeping the world over. The Atomic Clock by Arcron is the most accurate, reliable and convenient timepiece you can buy.

**The most accurate clock on Earth.** Every morning at 1:00 a.m., this "smart" clock tunes in to the radio time signal emitted by the U.S. Atomic Clock in Colorado and automatically resets itself to the exact hour, minute and second. The U.S. Atomic Clock is accurate to ten billionths of a second per day. Using molecular technology, it measures the vibration rate of atoms—a constant—to calibrate time. This means that the clock deviates less than one second over a one million year period! The Atomic Clock even adjusts automatically for daylight savings time, so you don't have to remember to "spring forward" or "fall back." This clock is the only atomic clock with an internal calibrator that creates "intelligent" adjustments based on the latest signal readings. The desktop model is the only clock that will not lose time with low power or when you change its batteries.

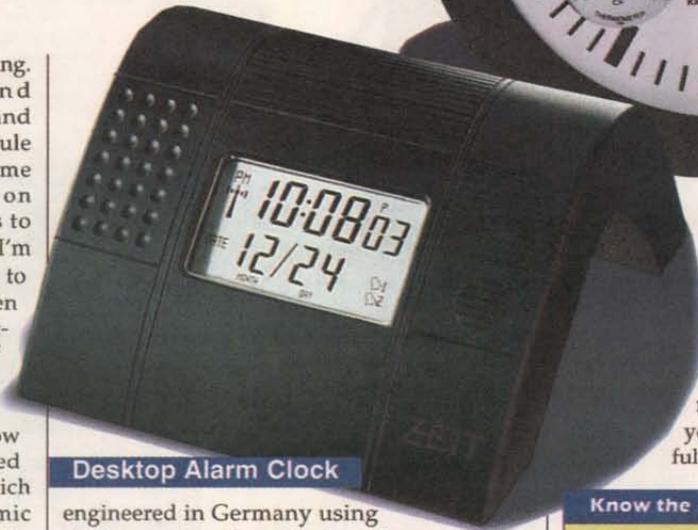**An easy time.** The most accurate clock in the world is of no use if it is difficult to operate. The Arcron Atomic Clock is



Desktop Alarm Clock


engineered in Germany using the latest scientific technology. It comes in two styles, the wall clock and the executive desktop model. Both are designed to be functional and easy to use.

The desk clock's display features the exact time (in hours, minutes and seconds), month and date, or you can choose to display any two U.S. or world time zones. It features a sleek, European design, and, at only eight ounces, is the perfect travel clock. It also has dual alarms, perfect for couples, and one-touch illumination for nighttime viewing.


The handsome wall clock comes with temperature and humidity gauges. After you install the batteries, watch the hands spin at 20 times their normal rate, until the clock has adjusted to the precise time. Both the executive desktop and the

wall model have an internal antenna for superior reception sensitivity, without unattractive wires.

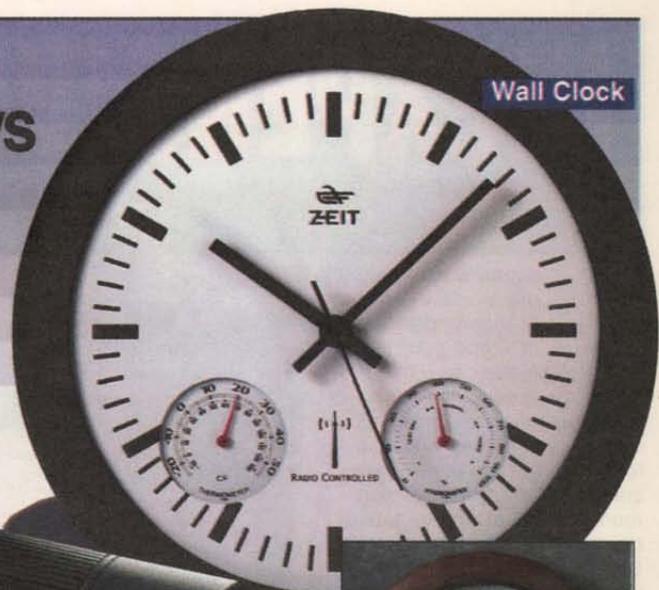**The time to buy is now!** Act now and you can own the world's most precise timepiece. Both the executive desktop and the wall model come with a one-year manufacturer's limited warranty and Comtrad's risk-free home trial. If you are



Wall Clock

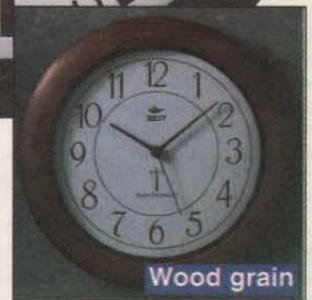

Wood grain

not completely satisfied, return your purchase within 90 days for a full, "No Questions Asked" refund.

**Know the exact time...anywhere you go**

The precise radio-controlled technology of the Atomic Clock is now available in these attractive wrist watches. Their internal receivers automatically display the exact time, and they are both rugged and comfortable. The attractive analog versions feature hardened mineral lenses and elegant leather straps. The new digital sports watch features a rubber wristband, blue backlighting and a stopwatch. It's even water-resistant to 100 feet. Now, for an affordable price, you can own a watch that's more precise than the most expensive watch in the world.



- Atomic Wall Clock . . . . . \$99 S8 S&H
  - Atomic Wall Clock (wood grain) . . . . . \$99 S8 S&H
  - Atomic Desktop Alarm Clock . . . . . \$99 S8 S&H
  - Atomic Digital Sports Watch . . . . . \$99 S8 S&H
  - Atomic Wrist Watch . . . . . \$199 S8 S&H
- Please specify black or white face when ordering.

Please mention promotional code 4022-14957.

For fastest service, call toll-free 24 hours a day

**800-992-2966**

To order by mail, send check or money order for the total amount including S&H. To charge it to your credit card, enclose your account number and expiration date.

Virginia residents only—please add 4.5% sales tax.

**comtrad industries**  
2820 Waterford Lake Dr, Suite 102  
Midlothian, Virginia 23112

Every morning at 1:00 a.m., this "smart" clock tunes in to the radio time signal emitted by the U.S. Atomic Clock in Colorado and automatically resets itself to the exact hour, minute and second. The U.S. Atomic Clock is accurate to ten billionths of a second per day.



# INEXPENSIVE DIGITAL TIMER

by Raymond C. Buck

Anyone whose hobby is electronics will probably decide at some point to make a circuit board for one of their projects. Or, if their projects use EPROM parts, they will need to erase the parts as their software undergoes development. Each of these tasks needs to be accurately timed. Usually you will plug the exposure frame or UV eraser into a wall socket and set an audible alarm for the length of time required. When the alarm sounds, you can unplug the device from the wall and proceed with the next step.

This is the way I have performed these two operations for years. However, there have been times when I was distracted and failed to hear the alarm go off. This results in overexposure of the circuit board. There is no harm done in the case of the EPROM other than shortening the life of the UV bulb.

I had been planning for a long time to build a timer that would automatically remove power at the end of the timing cycle. However, I never seemed to have enough time to design the circuit board with the display and write the necessary software for the microcontroller.


One weekend I was shopping at Walmart and happened to pass through the kitchen appliance area. I noticed a digital timer that cost less than \$10.00. I began to wonder if I could somehow use it as part of my timer project. So, I purchased one and brought it home to do some testing.

I opened the timer case and connected the piezo speaker leads to an oscilloscope and set the alarm off. The output was a slightly modified sinewave of around 2.5 volts. This was more than enough output voltage to use in the timer project. I just needed to develop the interface circuit between the digital timer and the AC line



in the parts list. If you prefer to program your own part, the source code and hex code listings are available from the *Nuts & Volts* website. The file name is timer.exe and it is a self-extracting executable. Copy the file to a separate directory and run it from the DOS prompt to extract the code listings.

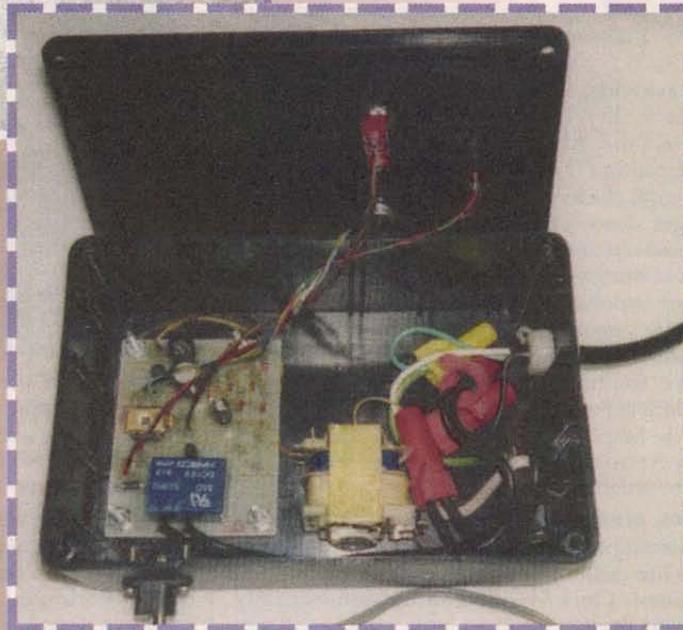The operation of the circuit is easy to understand. Diodes D1-D4 rectify the 2.5 volt AC signal from the digital timer. Capacitor C2 provides a slight amount of filtering to produce a DC voltage which is detected by pin 4 of IC1. Resistor R2 is used to pull the DC voltage rapidly to



circuit.

Figure 1 shows the final circuit design. As you can see, the circuit uses only a handful of components and is very simple. The heart of the design is the Microchip PIC 12C508 microcontroller. This is a complete microcontroller in an eight-pin DIP package. It has 512 bytes of user programmable memory and a total of six I/O lines. It operates at 4 MHz using a built-in oscillator and is perfect for this type of application. I started the original design using discrete components. However, when I got up to about a dozen parts and three ICs, I knew there had to be a better way.

That is when I decided to let the PIC make all of the logical decisions. You can purchase the preprogrammed PIC from the source shown

ground when the AC voltage (beeping) is removed. This allows you to initiate a timing period as short as two seconds.

Pin 5 of IC1 drives R3 which turns on Q1 and operates relay RL1 to apply power to the device that is plugged into J1. The AC voltage from T1 is rectified by bridge rectifier BR1. This

## BUY • SELL • CONSIGN

### WANTED

- Electronic Test Equipment
- Electronics Inventory
- Scientific Equipment
- Mfg. Shop Equip.
- Data/Telco
- Memory

# DEXIS

9749 Hamilton Road  
Eden Prairie, MN 55344

We Sell  
Nationwide!  
Call our Fax-On-Demand System, or our

Internet site for current availability.  
Visit our 25,000 sq. ft. showroom warehouse  
M-F 9 to 6; Sat 9 to 5

PHONE: (612) 944-7670

INTERNET: WWW.GO2DEXIS.COM

FAX: (612)942-9712 • FAX-ON-DEMAND: 1-800-547-4636 X 300

## PRINTED CIRCUIT BOARDS

**QUALITY PRODUCT**  
**FAST DELIVERY**  
**COMPETITIVE PRICING**


- \* UL approved
- \* Single & Double sided
- \* Multilayers to 8 layer
- \* SMOBC
- \* LPI mask
- \* Through hole or SMT
- \* Nickel & Gold Plating
- \* Routing or scoring
- \* Electrical Testing
- \* Artwork or CAD data
- \* Fast quotes

**PROTOTYPE THROUGH PRODUCTION**

# PULSAR, INC

9901 W. Pacific Ave.  
Franklin Park, IL 60131  
Phone 847.233.0012  
Fax 847.233.0013  
Modem 847.233.0014

www.pulsar-inc.com

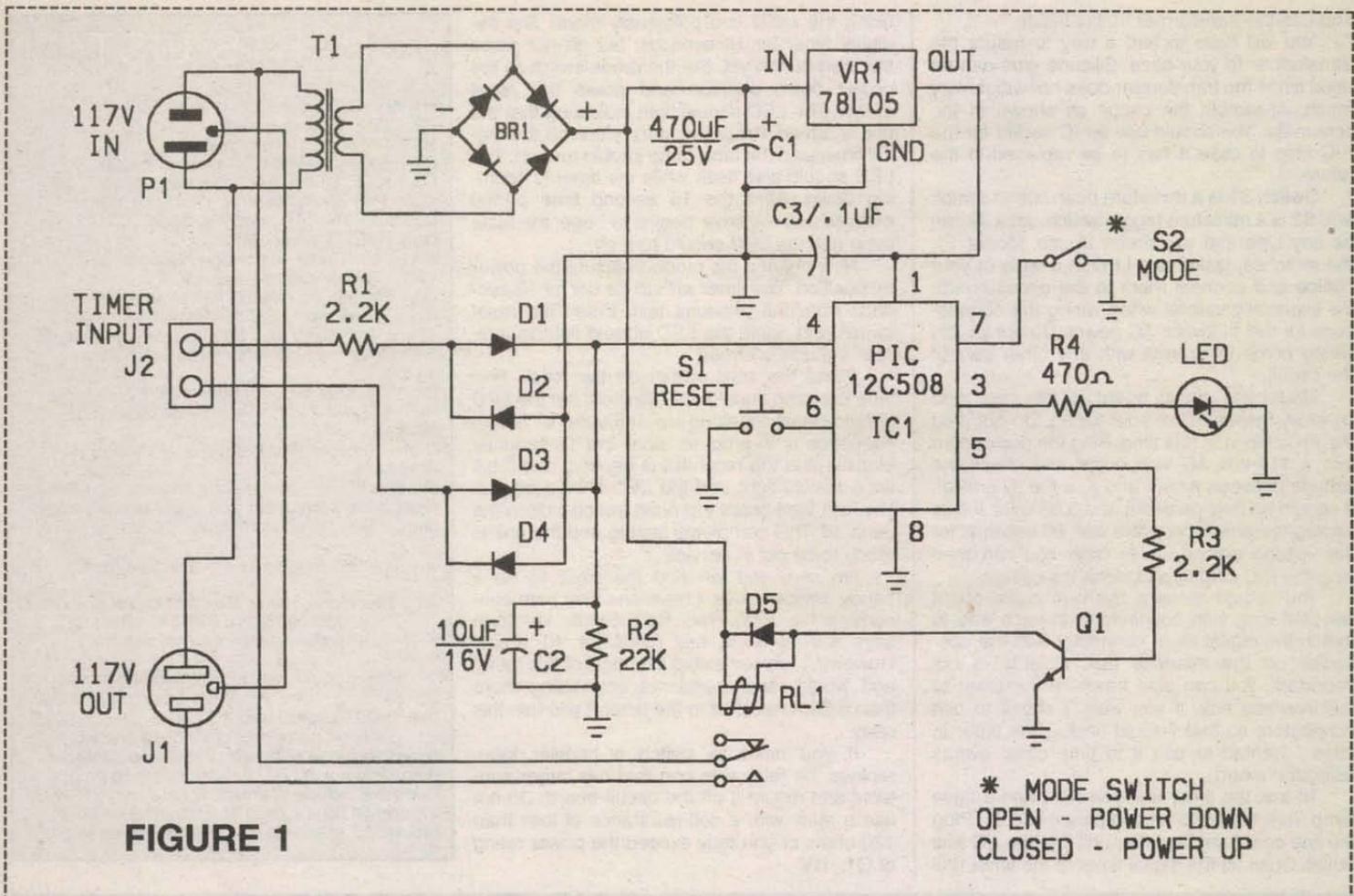

voltage is smoothed by C1 and applied to the five-volt regulator VR1 to supply power for IC1.



The timer can operate in two different modes. It can be used to power a device up or to power it down when the timing period elapses. In the power down mode, pressing the start button on the digital timer applies power to the device and power is automatically removed when the timing period is over. When used in the power up mode, power is applied when the timing period expires and you have to manually power the device down by pressing the reset button. The digital timer from Walmart has a maximum timing period of 99 minutes and 59 seconds.

Figure 2 shows the PCB layout looking through the board from the component side. Figure 3 shows the component layout. The circuit is simple enough to build using perfboard construction if you don't want to make the PCB. The board layout matches the RadioShack relay specified in the parts list.

Begin construction by modifying the digital timer. Remove the back cover from the timer. Solder two six-inch pieces of 30-gauge insulated wire to the piezo speaker terminals. Route them through the speaker opening on the back of the timer and reassemble the timer. Cut the wires so that about two inches remain and connect them to a two position .100" Molex type KK series female connector. Glue the connector to the back of the timer so that it is even with the edge of the timer. You can use any type of

miniature connector that you happen to have on hand. The Molex type is convenient because its rectangular plastic body is easy to glue to the timer case.

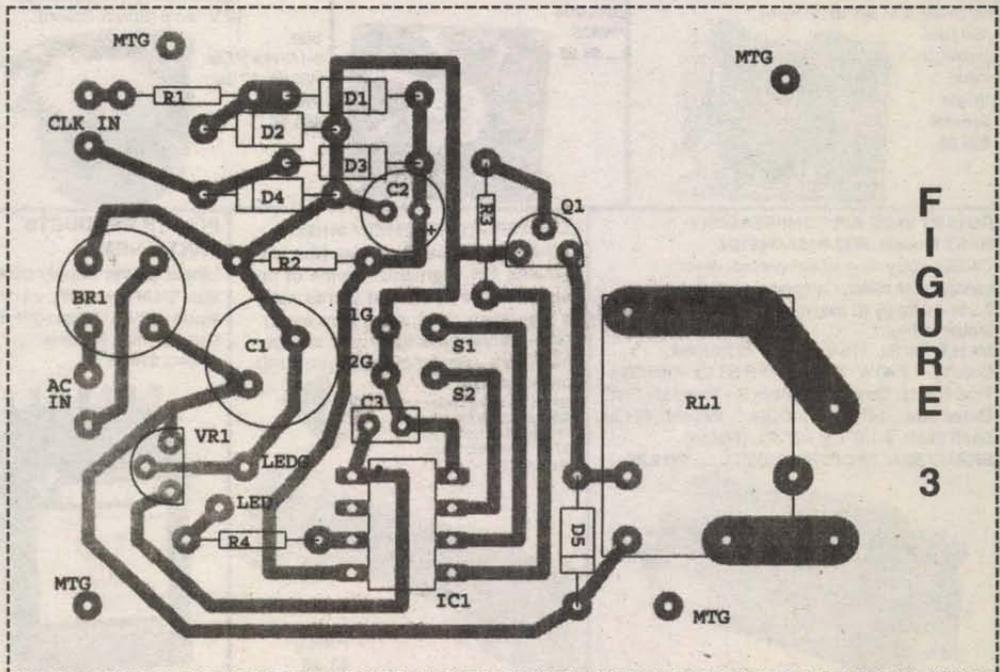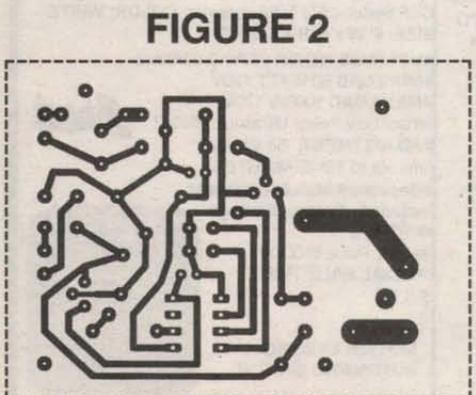Transformer T1 should be a 9- or 10-volt transformer. Do not use a 12-volt transformer as the DC voltage will be excessive for the relay. Any transformer with a 100 mA rating or greater will be sufficient. If you can't find a suitable chassis mount transformer, purchase a 12-VDC wall transformer. Break the case open



and use the transformer that is inside.

You will have to find a way to mount the transformer to your case. Silicone glue can be used since the transformer does not weigh very much. Assemble the circuit as shown in the schematic. You should use an IC socket for the PIC chip in case it has to be replaced in the future.

Switch S1 is a miniature push button switch and S2 is a miniature toggle switch. Jack J2 can be any type that you prefer to use. Mount T1, the switches, jacks, and LED in a case of your choice and connect them to the circuit board. Be especially careful when wiring the connections for the 117 volts AC power. Do not let this wiring come in contact with any other part of the circuit.

Mount the circuit board in the case and carefully inspect all of your wiring. Do not plug the PIC chip in at this time. Plug the power cord into a 117-volt AC wall outlet and check the voltage between pins 1 and 8 of the IC socket. It should be between 4.85 and 5.25 volts. If it is, unplug the power cord and wait 30 seconds for the voltage across C1 to drop. You can then plug the PIC chip in and close the case.

You should make a two-wire cable about two feet long with connectors on each end to match the digital timer connector and the connector on the interface box. Polarity is not important. You can also hardwire the timer to the interface box, if you wish. I chose to use connectors so that I could unplug the timer in case I wanted to use it to time other events using the alarm.

To test the timer unit you will need a table lamp. Turn the lamp on and plug it into J1. Plug the line cord from the timer unit into the AC wall outlet. Connect the digital timer to the timer unit

using the cable you previously made. Set the digital timer for 15 seconds, but do not press the start button yet. Set the mode switch to the power down position and press the reset switch. The LED should light indicating that the unit is armed. Press the start button on the digital timer and the table lamp should turn on. The LED should also flash while the timer is counting down. After the 15 second time period elapses and the timer begins to beep, the table lamp and the LED should turn off.

Now change the mode switch to the power up position. The timer will still be set for 15 seconds from the previous test. Press the reset switch and again the LED should light to indicate the unit is armed.

Press the start switch on the timer. This time the lamp should not come on, but the LED should start flashing to indicate a timing sequence is in process. After the 15 seconds elapses and the timer starts beeping, the table lamp should light and the LED should go out. You can then press the reset switch to turn the lamp off. This completes testing and the unit is ready to be put in service.

I'm sure you will find the timer to be a handy device to use. I have one final note concerning the relay. The RadioShack literature says the contacts are rated for 10 amps. However, I am somewhat skeptical of this rating and would recommend not connecting more than a 500-watt load to the timer if you use this relay.

If you need to switch a heavier load, replace the relay with one that has larger contacts and mount it off the circuit board. Do not use a relay with a coil resistance of less than 120 ohms or you may exceed the power rating of Q1. **NV**

## PARTS LIST

R1, R3 - 2.2K, 1/4 watt resistor.  
 R2 - 22K, 1/4 watt resistor.  
 R4 - 470 ohm, 1/4 watt resistor.  
 C1 - 470uF, 25-volt electrolytic capacitor.  
 C2 - 10uF, 16-volt electrolytic capacitor.  
 C3 - .1uF, 25-volt ceramic disc capacitor.  
 D1 - D4 - 1N4148 switching diode.  
 D5 - 1N4003 silicon diode.  
 BR1 - 50, 1 amp volt bridge rectifier.  
 VR1 - 78L05 voltage regulator.  
 Q1 - 2N3904 or 2N4400 NPN transistor.  
 IC1 - Microchip 12C508/P04 microcontroller.  
 T1 - 9 VAC or 10 VAC transformer (see text).  
 S1 - Miniature N.O. miniature push button switch.  
 S2 - Miniature SPST toggle switch.  
 RL1 - 12-volt SPDT relay (RadioShack 275-248).  
 Digital Timer - West Bend model #40035 (Walmart).  
 Misc.: LED, AC power cord, chassis mount AC receptacle, timer input jack, eight-pin IC socket, plastic case, misc. hardware.

The following parts are available from:

**ATC Electronics, P.O. Box 43033, Phoenix, AZ 85080-3033; Ph. 602-516-2926; <http://www.atcelectronics.com>**

Preprogrammed 12C508 microcontroller \$3.50 12-volt relay with three amp contacts that matches PC board layout \$1.50.

Kit of all parts except for case and PC board. Includes relay with three amp contacts. Also includes J1, P1, J2 and matching plug. Does not include Walmart digital timer, \$18.00. Include \$4.00 shipping and handling on all orders. AZ residents include 6.8% sales tax.

# BRIGAR ELECTRONICS

7-9 ALICE ST.  
 BINGHAMTON, NY 13904

SEND FOR FREE CATALOGUE

Open 7:30 To 4:30 PM  
 Monday thru Friday  
 Saturday 7:30 Am to Noon

PHONE: (607) 723-3111  
 FAX: (607) 723-5202  
 E-MAIL: BRIGAR2@aol.com  
 Web address: <http://members.aol.com/brigar2/brigar.html>



**WELDEX Video camera # WDPR-2000**  
 1/3" CCD Board camera B&W Pinhole lens compact 30mm x 30 mm (Approx 1" sq.)  
 High performance & picture quality of a full featured camera on a compact board.  
 0.03 Lux min. illumination - RCA connectors for power & Video connections.  
 430 lines resolution.  
 input.  
 Brigar Special  
**\$85.95**

**NMB 12 VOLT DC FAN 28 CFM**  
 Model # 3110KL-04W-B17  
 size: 80mm x 25mm 0.13 Amp  
 7 blade - Phenolic Blade & housing  
 DC Brushless - Ball bearing -  
 12" wire leads - UI & CSA - 25 dba  
**BRIGAR PRICE**  
 .... \$4.25

**120 VOLT AC 10 AMP TOROID ISOLATION TRANSFORMER**  
 Mfg: BANNER MAGNETICS # 159257  
 INPUT: 120VAC (Blk, Gry)  
 Output: 70v 12 amp (Red, Red)  
 120vac 10amp (Violet, White)  
 12 V 1amp (Brown, Brown)  
 Size:  
 3-1/2"H x 5"Dia.  
 Weight: 12 lbs.  
**PRICE...**  
**\$59.95**

**AC TO DC WALL TRANSFORMER**  
 MFG: AUDIOVOX PART# CNR405  
 INPUT: 120VAC 60Hz 11W  
 Output: 12 VDC 300mA  
 Polarity: Center pos. with 6' zip cord 2.5 mm Female receptacle. UL & CSA  
**SALE PRICE \$1.50**

**INTEL # P8052AH**  
 40 PIN  
 CPU 8 BIT 256  
 BYTES RAM,  
 Timer/counter and  
 I/O **PRICE... \$1.75**

**ROTARY VANE AIR COMPRESSOR**  
**GAST Model# 0522-P167-G451DX**  
 Oil-less rotary vane air compressor directly connected to motor. Compressor rated at 3.2 to 4 Cfm @ 10 psig max.  
 Motor rating:  
 3/4 H.P. 60 Hz 115 Vac 1 PH 1725 RPM  
 Code H - 7.40 A - SF 1.00 - FR 56 Cz Amb 50 c  
 Time Rating: Cont. Insul Class B - Thermally Prot.  
 Motor Size: 14"L X 6-1/2"Dia. Weight: 40 Lbs.  
 Shaft Size: 2-1/8"L x 5/8"dia. (Flated)  
**BRAND NEW FACTORY BOXED ..... \$119.95**

**LCD DISPLAY ASSEMBLY #HG416**  
 4 DIGIT 16 Segment display (the lcd contains 126 segments - some of the segments are fixed with words such as play, scan, loud, rdm, pgm etc...) 9 vdc - white back light with orange characters. Smart display with SMD components.  
**DISPLAYS COMES COMPLETE WITH 3.5" DISKETTE, FILES CONTAIN 89HC11 PROGRAM, LIST OF COMMANDS AND SCHEMATICS**

**PRICE**  
**\$3.95**

**POWER PRODUCTS PART # HE381**  
 Linear power supply module.  
 Size: 2-1/4" w x 4-3/4" L x 1-1/2" D  
 Input: 115vac 50/60hz 271 ma.  
 Output: 5vdc 5000ma.  
 Price... \$19.95 ea.

**ULTRASONIC LIGHT SWITCH MFG: LITRONIC**  
 Replaces existing wall switch - Great for home alarm systems or controlling lights & small appliances, ON-OFF Switch-LED TRIP Indicator **COLOR: WHITE**  
**SIZE: 5"W x 5"H X 1-3/8"D**  
 ● VOLTAGE 120 OR 277VAC 50/60HZ  
 ● MIN LOAD 80 WATT 120V  
 ● MAX LOAD 1000W 120V  
 Sensor Low Power Ultrasonic 25KHZ  
 ● ADJUSTMENT: Sensitivity & Time out (0 TO 25 MINUTES)  
 ● Documentation & schematic included. Energy Savings 30 TO 60%  
 ORIGINAL PRICE \$100.00  
**SPECIAL SALE PRICE \$6.95**

**SALE**

**MOTION SENSING AUTOMATIC SWITCH**

# reader FeedBack

An otherwise good article by Gerald Roylance was somewhat marred by his incorrect reference to the derivation of the 'N' connector nomenclature (page 96, Dec. '98 N&V).

You may inform your readers that the 'N' in 'N' connector stands for Neill. This is the name of the guy who invented this popular threaded and high-performance RF connector. A similar, but bayonet-style connector, the 'C' connector, was invented by a fellow named Concelman. Their joint efforts yielded the familiar TNC (threaded Neill-Concelman) and the BNC (bayonet Neill-Concelman) connectors.

To the best of my knowledge, these gentlemen both worked for Bell Labs.

The following was extracted liberally from various, mostly RSGB sources...

Up to the 1930s, the lead-in feed between the antenna and the rig was constructed by parallel wires with spreaders and binding posts. When the first RF coaxial cable was marketed, the UHF connectors PL259 were introduced.

During WW2, RADAR sets required a better connector than the PL259 then in popular use, and two designs followed. The first was to make a connector look like a piece of 50 ohm cable as near as possible and this was designed by Mr. Paul Neill at the Bell Laboratories and known as the type 'N' connector.

A Mr. Carl Concelman, apparently also of the Bell Telephone Laboratories, however realized that there was a small bit of inductance where the center pins of the N connector meet. By changing the position of the dielectric used to fill the connector, he was able to introduce some reactive cancellation, and this type 'C' connector allows it to be used well into the GHz range. Shortly after this, Neill and Concelman co-operated on the design of a miniature bayonet locking connector. This combined Neill's mechanical design with Concelman's reactive dielectric and his twist-on "bayonet style" locking ring. The Bayonet Neill Concelman (BNC) connector had arrived.

Later, for some airborne use, they produced a threaded version, the Threaded Neill Concelman (TNC). For preci-

sion microwave use, a series of sub-miniature connectors were developed 'A', 'B,' and 'C.' Of these, the 'A' type — or Sub-Miniature A (SMA) — is most popular.

**Steve Jackson**  
Technical Editor  
*Home Automator Magazine*

First, thanks for including my circuit tip in the November '98 issue of N&V magazine on page 32 in the Q & A column.

Unfortunately, several additions have been added to the original schematic that I submitted to you, resulting in two major problems.

First, the text no longer agrees very well with the schematic shown.

Specifically, the voltage supply circuitry in the upper left was not on the original, and so is not described in the text, and its purpose in the ckt is not clear. And, in fact, I cannot even find a MAX1021-5 listed anywhere in the data-books. Had I put a regulator in my ckt, I would have used a cheap 78L05 instead of an expensive Maxim part anyway.

My original intent, as described in the text, was that the +5V for the ckt would come from the processor board on which the ckt was built, and the ckt would then draw no local power when not connected to a host PC.

I guess some of this confusion probably stems from my text saying "the circuit 'steals' its power from the host serial port", whereas it should more appropriately said "... 'steals' its negative voltage ...".

Second, and much worse, is the addition of the DB9 connector to my original schematic. It is located on the WRONG side of the circuit!

As described in the text, the TxD and RxD lines go to the host serial port, while the TD and RD lines (originally labelled Tc and Rc) go to the local CPU. This has caused a lot of confusion with some people who have E-Mailed me about the ckt.

So I think we need to publish some kind of correction to straighten things out. Other than this, thanks for publishing the circuit.

Best regards,  
**Dan Michaels**  
Oricom Technologies

## Credit Card FINANCING

2 Easy Payments of **\$29!** 97 Edition

2 Payments of **\$29!** Publisher **\$195** back issue, Perfect for Service & Experimenter

**\$115** Publisher 2 Easy Payments of **\$75!!** 97 ICM CD

**\$235** Publisher

**2 Easy Payments Any Product**

2 payments of **\$29** 97 EEM CD

2 payments of **\$44** 98 EEM CD

2 payments of **\$75** 97 ICM CD for Moderate Design Work

2 payments of **\$65** 97 ICM Books

2 payment of **\$52** 96 ICM Books for Service or Life Design

2 payments of **\$99** 98 ICM CD for Advanced Design Work

### Save Time with "REFEREE"

#1 Choice of Service Centers

## CROSS REFERENCE & SPEC

Quarter Million Transistors, ICs & Diodes

A Specialist in "Hard to Cross House Numbers" **Easy, Powerful & Fast.** The Most Comprehensive Software Sold.

A selection yields Device Specifications & 75 to 250 Potential Replacements!

Replacement Numbers are Totally Global including Domestic, Asian, European, House Branded, as well as ECG, NTE, SK & GE. Displays Case Drawings, Lead Configuration & Pin-outs for many Devices. Coverage of Replacement Numbers is Very Impressive. 7 Disk Set. (17 Meg decompressed) For DOS, Win3.1 & 95 Latest Version 7.11 Includes Many Helpful Conversion Utilities, Tables & Formulas.

Includes: 4 HUGE Consumer Electronics Industry Directories  
1-Consumer Electronics Parts Sources (Service) 2-Consumer Electronics Manufacturers  
3-The Entire Computer Industry 4-Semiconductor Manufacturers

Perfect for Service, Engineering and Purchasing.

2 Easy Payments of **49!**

Shop the way the Pro's do, Use Their Tools!

These are the books that find the "Gold". For many years they've been used by the Sharpest Purchasing Agents. Look under every rock...they're impossible to find at ANY price, let alone a great deal like this. Find: Distributors, Manufacturers and Service providers for Products, Services or ANY Component Parts imaginable. Sources for Everything from Gears to Semiconductors to Foreign Assembly Services.

Single payment of **\$25**

**Parts Sources Library**  
Best Kept Secrets  
Complete Library Huge

WOW 2 easy payments of **\$282!**  
0% Financing! On Credit Cards only

the Perfect Gift Only a few left!

2 Payments of **\$282** Compaq 486 DX4-100 16m-710m-10.4"ds-W95-PCMCIA

2 Payments of **\$379** Compaq Pentium 90 16m-810m-9.4"Active-PCMCIA

may differ slightly from illustration

All Cards & COD Int'l orders email: netcomd@aol.com FAX 516-826-7776  
Netcom 800-733-3733 ext 6300 516-826-1808 10-9 EST 7Days

# Pacific Test Equipment



## BLOWOUT SALE

	<b>HP 8657A Synthesized Signal Generator</b> 0.1 - 1040 MHz with 10 Hz Resolution, +12 to -143.5 dBm 50W Reverse power protection, internal AM/FM Modulation Note: RF Connectors on rear panel (opt. 002)	Retail \$9,995 Regular \$5,900 <b>Sale \$2,375</b>
	<b>HP 8656B Synthesized Signal Generator</b> 0.1 - 990 MHz with 10 Hz Resolution, +13 to -127 dBm 25W Reverse power protection, internal AM/FM Modulation Note: RF Connectors on rear panel (opt. 002)	Retail \$7,900 Regular \$4,250 <b>Sale \$1,875</b>
	<b>HP 8656A Synthesized Signal Generator</b>	<b>Sale \$1,050</b>
	<b>HP 5334B Universal Counter</b> 0 to 100MHz, 9 digit per second resolution, rise/fall time, pulse-width, ac/dc voltage measurement. Frequency, period, ratio and time interval. Front and rear inputs in parallel. HP-IB	Retail \$2,305 Regular \$1,000 <b>Sale \$195</b>
	<b>HP 3457A Digital Multimeter</b> 3-1/2 to 6-1/2 Digit with extended resolution to 7-1/2 digits. dcV, acV, dcI, acI, Ohms, frequency and period. 1350 readings/sec. at 3-1/2 digits. HP-IB	Retail \$3,260 Regular \$2,495 <b>Sale \$1,380</b>
	<b>Tektronix 2445A 150MHz Oscilloscope</b> Auto-setup, 4 channel, 1M and 50 Ohm input impedance, dual time base, CRT readout with cursors. 2mV sensitivity.	Regular \$3,200 <b>Sale \$1,895</b>

Above items come with a 90 Day warranty, standard accessories, and FREE UPS Ground shipping within the continental U.S.

We accept VISA, MC and prepayment in advance. Sorry no C.O.D.'s. Quantities are limited to stock on-hand. 20% restocking fee on returns.

**We Buy Late Model Test and Measurement Equipment**  
 by HP, Tektronix, Fluke, R&S, Wavetek, Anritsu, and others.

(408) 441-7341 or fax (408) 441-8049

We also carry Brand New Iwatsu/LeCroy - Topward - LG Precision

<b>Iwatsu/LeCroy</b> <b>LA314/SS-7840</b> 400 MHz, 4 Channel Cursor, High-Speed Auto Setup, TV Trigger <b>\$7,200</b>	<b>Topward</b> Single Output Model Meter Output Price 3603D Digital 60V/3A \$495 Triple Output Model Meter Output Price 6603D Digital 60V/3A X 2 \$875 5V/5A Fixed Others Available - Call	<b>LG Precision</b> <b>OS-5100RB</b> 100 MHz, 4 Channel Cursor, Auto Setup CRT Readout <b>\$1,595</b>
--	--	--



**Pacific Test Equipment Corp.**

1450 Koll Cir. #111 • San Jose, CA 95112

(408) 441-7341 • Fax (408) 441-8049

For a free catalogue

or inquires on other equipment call

(408) 441-7341 M-F 9-6 (PST)

Ask for Erwin Talavera

Excellence  
since  
1934

**H&R**  
COMPANY

# HERBACH AND RADEMAN

Products for Science and Industry  
**THIS MONTH**

OUR CATALOG IS LIMITED ONLY BY YOUR IMAGINATION ...



## RUNNING TIME METER

6 Digits Non Reset  
115 VAC 60 Hz

0 to 99,999.9 Hours and Repeat



Curtis# 12729-76...Panel mount 115 VAC/60 Hz 0.1 Watts. Mounts in a 1.77" Square Cutout (supplied with mounting bracket) 0.250 QC Terminals for Conn., Size 1.90" Square x 2-3/4" Deep. New. Shpg. Wt. 1 Lb.

TM93MET2549 ----- \$14.95

## 6 WATTS PHOTOVOLTAIC SOLAR PANEL

Rated 22 Volts DC open circuit  
Size 12 x 18



Amorphous silicon resin, glass encapsulated. Operating voltage 12 Volts at rated current of 0.5 Amps in bright sunlight with short circuit current of 0.55 Amps. Ideal for storage battery charging, running small motors and many other applications. Clips supplied. Indoor/Outdoor use. New. Wt. 5.5 lbs. TM98SED3224 ----- \$39.95

## COLOR WHEEL ASSEMBLY


5 Volt, 3-phase disc-drive motor powers a 4-quadrant color wheel. A reflective silver strip is positioned on the wheel which is used for timing with a printed circuit mounted sensor. Unit is metal and black in color. The wheel diameter is 4-1/4". Overall assembly sz: 1-1/4" x 4-3/4" x 6". The sensor cable (3 leads) is approx 9-1/2" long. Excellent condition. Shpg wt 1 lb.



TM98OPT3211 ----- \$7.95
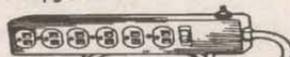
## Outlet Strip / Surge Protector

Gemini VG307... Max Rating 15 Amps, 1875 Watts, 125 VAC. 6 outlets, 3 wire grounded, illuminated on/off switch. Neutral colored plastic case. Size 12-3/8 x 2-1/2 x 1-1/2". Shpg Wt 2 lbs.



\$6.95 EA.

5 @ \$5.95 EA.


TM98MAC3171 ----- 10 @ \$5.50 EA.

## MODERN TOUCH-TONE TELEPHONE for DESKTOP or WALL

Technitron #T2200... Slim line handset is pulse / tone switchable, desk or wall mount. Black in color, the unit features: PEST CALL BLOCKER; HANDS FREE DIALING; HOLD FEATURE WITH 15 SECOND REMINDER; REDIAL; 17 NUMBER MEMORY STORAGE AND SLIDE-OUT DIRECTORY. Both cords, battery and handbook are supplied with unit. Size 8-1/2" x 5" x 1-1/2". New. Shpg wt. 2 lbs.



TM98COM3183 ----- \$17.95

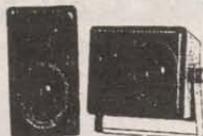

## 3-WAY HI-POWER BASS REFLEX SPEAKER SYSTEM

Shielded magnets for Audio/Video Use

Speco #DMS-6... 45 Watts RMS per channel, 60 watts max. Features include: Hi-temp voice coil; 5", 20 oz. excursion woofer; 2" wide dispersion cone tweeter and 1" dome tweeter; Frequency response 55 to 20,000 Hz compatible 4 and 8 ohms. High impact plastic with wire mesh grille, quick connect terminals, ported for max bass response. Speaker wire included. Size: 8-7/8"H x 6-1/8"W x 5-1/4"D. New. Shpg wt. 13 lbs. REGULAR RETAIL PRICE \$105.95.

TM98ADV3186 ----- FOR THE PAIR ----- \$34.95

## ANALOG DIGITAL CONVERTER

INTERFACES TO ANY IBM/CLONE  
PARALLEL PRINTER PORT



Simultaneously monitors 8 sensors including - Voltage, Current, Pressure, Vacuum, Water level and Audio signals.

The Analog Digital Converter is computer powered by a Y-adapter cable. The PC-XT type Y-adapter plugs into your keyboard port, then just plug your keyboard into the adapter. Each analog input channel can be independently programmed for one of four input ranges. This converter is capable of 50,000 samples per second (if you write and compile the code). Comes assembled and tested with circuit diagram, and QBASIC source code.

### Features:

- Eight 12-bit analog input channels
- Four software-selected input ranges per channel
- ±15V Fault protection circuitry
- LED "Power On" indicator
- Includes QBASIC source code (which is highly commented)
- Analog inputs accessed by standard male DB25 plug

Eight uni-polar analog inputs of 0 to +2.5V or 0 to +5V. Four bi-polar analog inputs of ±2.5V or ±5V.

TM98TLE3255 ----- \$99.50

Eight uni-polar analog inputs of 0 to +5V or 0 to +10V. Four bi-polar analog inputs of ±5V or ±10V.

TM98TLE3256 ----- \$99.50

## 40 Watt Switching Power Supply




Kyosan # KCT040FJ6... Input 90 to 127 VAC, 3 outputs: +5 VDC @ 4 Amps, +12 VDC @ 1 Amp, -12 VDC @ 400 mA. Size 14-1/8 x 2-1/4 x 1-3/4. New. Shpg wt. 2 lbs.

TM98PWS3254 ----- \$3.95
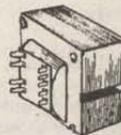
## DUAL INPUT TRANSFORMER

120/240 VAC 50/60Hz

MCI #4-07-8512 has 10 VAC @ 6 Amps, 12 VAC @ 5 Amps and 25 VAC @ 3 Amps. Features .187 QC solder terminals. O/A Size: 3" Long x 2-9/16" Wide x 2-1/4" High with four through holes on laminates for mounting. For micro-processor power supply, added schematic to convert to DC supplied. UL Listed. New. Wt, 3 Lbs.




TM94XFR2684 ----- \$7.95

## HER is a distributor for hurst Motors

### GEARED STEPPING MOTORS - SERIES SAS

Input 8 Watts, Winding resistance 36 Ohms.

Wt. each, 2 lbs.

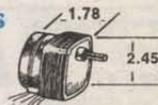

Reduction	Step Angle (degrees)	Output Speed 200 p/s (rpm)	Torque 200 p/s (oz-in)**	H&R NO.	PRICE EACH
600	0.0125	0.42	200*	H2-100	\$67.40
300	0.0250	0.83	200*	H2-101	\$67.40
75	0.100	3.33	200*	H2-102	\$63.70
30	0.250	8.33	97	H2-104	\$55.40
15	0.500	16.67	52	H2-105	\$55.40
10	0.75	25.00	35	H2-106	\$49.10
2	3.75	125.00	7	H2-107	\$53.40

\*Maximum gear train loading

\*\*Torque measured at nominal voltage with L/R drive.

VISA

ORDER TOLL FREE 24 HRS at 1-800-848-8001

or fax us at 609-802-0465

MasterCard

To receive our 100+ page CATALOG call 609-802-0422

or e-mail us at sales@herbach.com

Discover

\$25.00 minimum; additional shipping and handling charges apply  
Prices subject to change

**H&R**  
COMPANY

16 Roland Ave. Mt. Laurel NJ 08054  
INTERNET <http://www.herbach.com>

# ELECTRONICS

## Q & A


With TJ Byers

In this column, I answer questions about all aspects of electronics, including computer hardware and software. This column doesn't replace the Tech Forum that you've grown to love and support. Instead, it will supplement it, so feel free to participate as always with your questions and answers. You can reach me on America Online at TJBYSERS, on the Internet at TJBYSERS@aol.com, or by snail mail at Nuts & Volts Magazine, 430 Princland Ct., Corona, CA 91719.

### Sun To PC Monitor

**Q.** Recently I bought a used Sun Sparc 2 computer. It's complete except that I didn't buy a monitor for it. I have a Sony Multiscan 17sf II, which I use for my IBM PC compatible that I'd like to connect to the Sun system. Can you advise me on how to do this?

**Howard Lee  
via Internet**

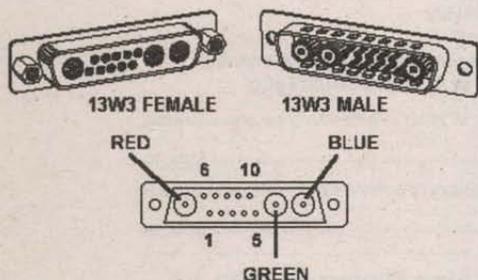

**A.** This isn't a big problem if your Sparc's graphics card uses a standard 13W3 connector. The 13W3 is an unusual connector combining a 10-pin D-shell with three analog video conductors.


### Sun Sparc 13W3 Connector

Pin	Function
1	GND*
2	Vertical sync*
3	Sense #2
4	Sense GND
5	Composite sync
6	Horizontal sync*
7	GND*
8	Sense #1
9	Sense #0
10	Composite GND

\* Considered obsolete, may not be connected.

You can buy ready-made adapter cables from **Sun Cables (732-435-1484; <http://www.sun-cables.com>)** and **System Integrators (1-800-547-2349; <http://www.si87.com>)** for about \$30.00. Or, you

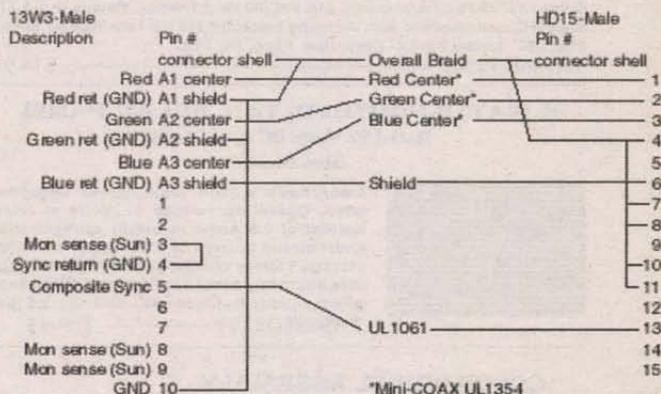can make your own using the schematic below. While the "perfect" interface calls for mini coax cables (usually of the orange-covered variety) for the video interfaces, you can use twisted pairs if you keep the cable length to six inches, or so.



For those readers who don't have the Sony monitor mentioned (or its equivalent), be aware that the Sony Multiscan 17sf II supports separate sync, composite sync, and sync-on-green, as do many PnP (Plug-n-Play) monitors. Check your monitor's specs before trying this patch. Otherwise, it won't work without further signal processing.

### CPU "Upgrade" Conversion Adapters

**Q.** I have a 486 GIO-VT2 motherboard made by FIC, and I'm looking for an adapter (daughterboard?) that drops the voltage from 5 volts to 3.3 volts. Do you know of any such device or have any ideas that might be helpful?

**Jim Madden  
via Internet**

**A.** Ah, you want to upgrade the CPU, but the new processor needs a 3.3-volt source. Bear in mind that it needs a 5-volt source, too, so you can't simply change the whole system over to 3.3 volts. Fortunately, all you need is a CPU adapter socket made by **Aries Electronics (<http://www.arieselec.com>)**, which is available from **Digi-Key (1-800-344-4539; <http://www.digikey.com>)**. The CPU adapter contains a 3.3-volt voltage regulator that powers the two (or four) 3.3-volt pins of the new CPU and passes the 5-volt source to their original destinations. To make the upgrade, simply remove the old CPU, plug in the adapter, then install the new CPU according to its instructions. These adapters will even let you plug surface-mount CPU chips into a

## EPROM+

A device programming system for design, repair and field service

- ◆ EXCEPTIONAL POWER FOR THE PRO
- ◆ EASY-TO-USE FOR THE NOVICE

**Here's what you get:** A rugged, portable programming unit including the power pack and printer port cable both of which store inside the case. A real printed user and technical manual which includes schematic diagrams for the programming unit plus diagrams for all technology, family adapters\*. Comprehensive, easy-to-use software which is specifically designed to run under DOS, Windows 3.1, 95 and 98 on any speed machine. The software has features which let you READ, PROGRAM, COPY and COMPARE plus much more. You have full access to your system's disk including LOADING and SAVING chip data plus automatic processing of INTEL HEX, MOTOROLA S-RECORD and BINARY files. For detailed work the system software provides a full screen buffer editor including a comprehensive bit and byte tool kit with more than 20 functions.

**Broad device support:** Including FIRST GENERATION EPROMS (2708, TMS2716\*, 25XX etc.) SECOND GENERATION EPROMS (2716-27C080)(8 MEG), 40 and 42 PIN EPROMS\* (27C1024-27C160)(16 MEG) EPROMS (2816-28C010) PLUS ERS901, FLASH EPROMS (28F, 29C, 29EE, 29F)(32 MEG), NVRAMS (12,20,XX210)(12) 8 PIN SERIAL EPROMS\* (24, 25, 35, 93, 95, 80011A) PLUS ERI400/MS8657\* BIPOLAR PROMS\* (74S/82S), SERIAL FPGA CONFIGURATORS (17CXXX) MICROS\* (874X, 875X, 87C5X, 87C75X, 89C) ATMEL MICROS\*(89S, 90S)(AVR) PIC MICROS\* 8, 18, 28, 40 PIN (12CXXX, 16C5X, 6X, 7X, 8X PLUS FLASH & 17C) MOTOROLA MICROS\* (68705P3/U3/R3, 68HC705C/C/D/P/9, 68HC711E9/D3)

\$289

\$5.00 SHIPPING • \$5.00 C.O.D.  
 □ 1 YEAR WARRANTY - 30 DAY MONEY BACK GUARANTEE  
 \*REQUIRES SNAP-IN ADAPTER (ORDER FACTORY DIRECT OR BUILD YOURSELF) VISA • MASTERCARD • AMEX

**ANDROMEDA RESEARCH, P.O. BOX 222, MILFORD, OHIO 45150**  
(513) 831-9708 FAX (513) 831-7562  
website - [www.arlabs.com](http://www.arlabs.com) email - [arlabs@worldnet.att.net](mailto:arlabs@worldnet.att.net) MADE IN THE U.S.A.

### 5 Axis Robotic Arm Kit

### \$195.00 Plus S&H

We make it easy!

**You can build this Robotic Arm!**  
Impressive, fast, accurate, and repeatable motion. Any computer capable of sending 2400 or 9600 baud serial data can control the arm, even a Basic Stamp. This arm makes a great foundation for AI and motion control experiments. Position the arm in an X, Y, Z, grid with a joystick or keyboard using the new RoboMotion for Windows. The kit includes the hardware, structural components, Hitec servos, pre-assembled SSC servo controller, DOS and Windows software, and an illustrated assembly manual. Camouflage paint not included.

**We have many more cool robots, check out our web page or ask for our free catalog!**  
**3 Axis Version \$155.00 • Mobile Version \$250.00 • Mobile Robots Book \$48.00**

Lynxmotion, Inc.  
104 Partridge Road  
Pekin, IL 61554-1403 USA  
<http://www.lynxmotion.com>


Tel: 309-382-1816  
Fax: 309-382-1254  
[sales@lynxmotion.com](mailto:sales@lynxmotion.com)  
[tech@lynxmotion.com](http://tech@lynxmotion.com)

"bed-of-nails" (PLCC) or Quad Flat Pack (QFP) socket.

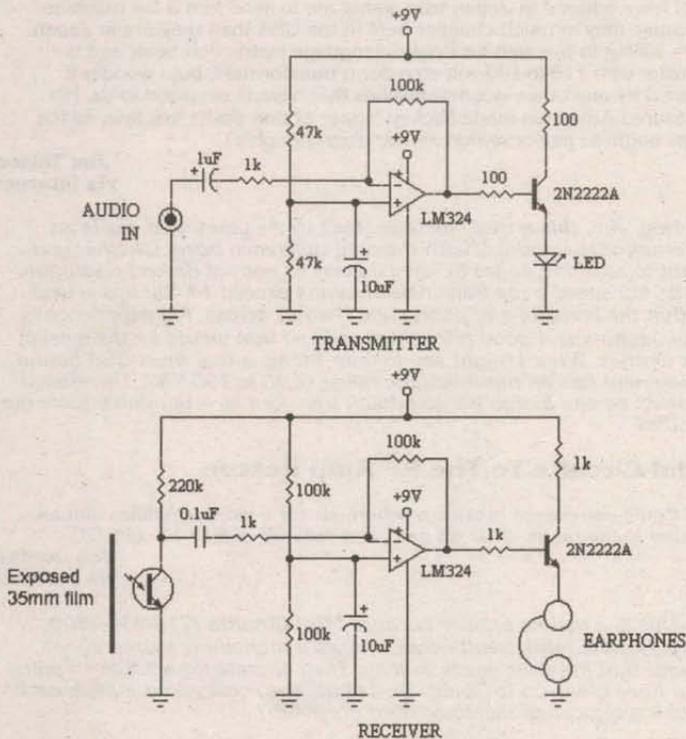**Wireless**

**Q.** I'm looking for a device that will broadcast the sound from my TV to my earphones so that I alone can hear the sound. Can you help me?  
**Bob Miskowic via Internet**

**A.** Sure! You can find what you're looking for from *UnWired*. The model you want is 3000IR, which is an infrared wireless headphone for private television listening. They sell for \$29.99 and can be found at Target stores, Fry's Electronics, J&R Computer, or directly from the company at their web site (<http://www.laral.com/unwired>). Now, if you'd like to make your own wireless IR link, play with the circuit below.



As you can see, it's divided into a transmitter and a receiver (what else?). Both circuits are basically identical, with an op amp driving either the LED transmitter or receiver earphones. The gain of the amplifier is set at 100 (this is determined by the ratio of the 1K input resistor to the 100K feedback resistor). Notice that the op amp's non-inverting input (+) is tied to a resistor divider (47K for the transmitter and 100K for the receiver) to permit unipolar (one battery) operation. For best performance, the LED and phototransistor should be matched. I used RadioShack's 276-142 optical pair and was able to receive up to 30 feet away. However, overhead lights tend to swamp the phototransistor and fluorescence create a 60-Hz buzz. The solution is to place a piece of exposed 35mm film over the phototransistor; it blocks the visible light while letting the infrared emissions pass freely.


Want to have more fun? Play with the RF data modules from **Abacom Technologies** (416-236-3858; <http://www.abacom-tech.com>). See their ad on page 59. They are AM transmitters and receivers operating in the 418 MHz range which sell for about \$25.00 total and don't have the ambient light shortcomings of the IR devices.

**Push My Button**

**Q.** I have a 5000 EXL gasoline generator with a button-actuated battery starter. Do you know how to convert it so that it will start unattended? Do you also know of a source that sells parts or will convert it to run off LP (propane)/natural gas (methane)?

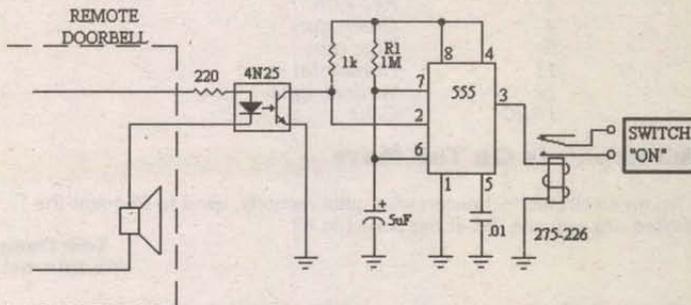**Howard Epstein via Internet**

**A.** Well, the remote starter is easy; the LP conversion harder. You are aware that you can buy remote devices that can start automobiles via remote control, aren't you? Check out *Pep Boys* or similar auto parts house in your local phone book. However, this is a DIY (do-it-yourself) magazine, isn't it, so let me take a shot at it. To start the generator remotely, I'd use a remote doorbell that you can buy from RadioShack or any hardware store. Then I'd do something like this.



The one thing these remotes have in common is that they activate a buzzer or a speaker when the button is pressed. We will use this signal to engage a starter relay by inserting an optical coupler in series with the speaker leads. I'm assuming your starter battery is 12 volts. When the "bell" rings, the 4N25's LED lights which, in turn, triggers the 555 monostable circuit. The values selected are for about a one second crank time. Repeated pushing of the "doorbell" will crank the starter one more time. The cranking time is controlled by the 1M and 5 uF capacitor; i.e., increasing the 5 uF cap to 10 uF will result in a two second "starter." I've built this circuit and it may need some fine tuning. For example, the polarity of the 4N25 LED may have to be reversed, and the cranking time depends on your generator and its tune-up. As for unattended starting, I don't recommend it, although it's easily done using a mechanical timer you can buy from any hardware store. My concern is that gasoline and nonchalance don't go together. Finally, the LP and/or natural gas conversion: Don't do it yourself! First, you need a new carburetor, plus a new fuel tank. Only a professional can provide both. Again, don't try it yourself unless you've set a track record at the Daytona. Check the Yellow Pages under "propane" or call your local gas company (as in PG&E). Expect to pay about \$500-\$1500 for the conversion.

**Out With The Old Monitor, In With The New**

**Q.** I have an old Amiga (Commodore 1084S-P) monitor that I haven't used for quite some time. Now I'm making an IBM clone for my kids and

**SOLUTIONS TO YOUR CABLING NEEDS**

Cat.5 -- Enhanced Cat.5 -- USB -- IEEE1284 / 488 / 1394  
Firewire -- High-End Monitor -- Manual & Auto Switches  
Apple -- Custom Ribbon Cables -- Premise Wiring -- more!  
**HUGE SELECTION OF SCSI CABLES & ADAPTERS**

Category 5 Patch Cables:

2 feet.....\$2.50	7 feet.....\$3.70	14 feet.....\$5.85	35 feet.....\$10.20
3 feet.....\$2.70	10 feet.....\$4.70	20 feet.....\$7.25	50 feet.....\$14.50
5 feet.....\$3.35	12 feet.....\$5.25	25 feet.....\$8.70	100 feet.....\$25.20

**Place Your Order Online 24 hrs./day**

No minimum order, same day shipping on most orders, A+ and CET technician available to answer your questions.

Northwest Cable & Connector Co.  
[www.nwcable.com](http://www.nwcable.com)  
Phone: (360) 754-3606 Fax: (360) 754-0825

Write in 98 on Reader Service Card.

**DIGITAL SATELLITE TV REVOLUTION!**

**KNOWLEDGE is POWER!**

- A clear explanation of all aspects of digital satellite TV
- Communication fundamentals and standards
- Digital compression, MPEG-2, DVB, error correction
- Uplink, satellite and receive system operation
- Internet operation and satellite delivery of data
- Installing fixed and tracking dishes
- Retrofitting older systems and mobile systems
- Conventional and IF distribution systems
- Troubleshooting and repair ... and much more ...

[www.baylin.com](http://www.baylin.com)  
or... call 800-483-2423

ORDER via Internet or Send \$60 plus \$4 s/h to:

Baylin Publications, 1905 Mariposa, Boulder, CO 80302  
MASTER, VISA & AMEX / COD orders accepted



486 pages, 8-1/2" x 11"

**JUST PUBLISHED!**

Telephone: 303-449-4551  
FAX: 303-939-8720

**FREE CATALOG - Satellite TV books, videos and software**

Write in 99 on Reader Service Card.

would like to make use of this monitor. Is there any way I could drive this monitor from a VGA or SVGA video card? I may have a clouded memory, but I always thought it was a pretty good monitor, capable of displaying 16 million colors. Any information on the conversion (if it can be done) or plug pinouts would be appreciated.

Harry  
via Internet

**A.** Yeah, back in those days this was an incredible monitor — because it was the first of the analog monitors and could display 16 million colors as opposed to IBM's digital limit of 64 colors. Unfortunately, the horizontal scan rate of this monitor is fixed at 15.75 KHz — the same as that of a color TV. (Its companion computer was designed to work with a TV, too, which explains the scan rate.) Bottom line: it won't work with VGA. My suggestion is to buy an NEC Multisync C400 14-inch monitor from Egghead Online (<http://www.egghead.com>) for just \$99.99 (Egghead has surplus monitors for as little as \$79.00, too). Now before the letters from Amiga aficionados come pouring in, here's the pinout of the monitor.

**Amiga 500, 1000, 2200, 2500, 3000, 3500, 4000 Video Pinout**

Pin	Function
3	Red gun
4	Green gun
5	Blue gun
11	Horizontal sync
12	Vertical sync
16-20	GND

**FAQ Repair Is On The Move**

**Q.** I'm an electronic technician who, until recently, used to frequent the repairfaq.org web site. What happened to it?

Tom Dang  
via Internet

**A.** The new official web site is <http://ftp.cised.unina.it/pub/electronics/REPAIR>. The original site has changed to <http://www.repairfaq.org/~fillpg>, V2.60 (10/5/97), which spotlights Samuel M. Goldwasser's "Notes on Troubleshooting and Repair of..." series of comprehensive repair guides for consumer electronics

equipment and other household devices. There is also a great deal of other information of interest to the electronics hobbyist, experimenter, technician, and engineer — and the official FAQ (frequently-asked questions) of the sci.electronics.repair newsgroup.

Unfortunately, several portions of the <http://www.repairfaq.org/~fillpg> site are being phased out — so download the files now. The best way to do this is to bring up the HTML text on the screen, highlight it using the mouse, copy it using Edit Copy or the keyboard Alt, E, C command, and paste (Alt, E, P) it into a blank word processor page, then save it. I use Winword 6.0 (Windows Word 6.0). If you need a schematic, take a screen shot using SnagIt, Paint Shop Pro, or similar screen-capture utility. This site won't last long, and it's not being updated, so time is of the essence.

**Fax Machines In Japan**

**Q.** I have a friend in Japan who wants me to send him a fax machine because they're much cheaper here in the USA than they are in Japan. He's willing to live with an English-language instruction book and is familiar with 110-to-100-volt step-down transformers, but I wonder if there'd be any other incompatibilities that haven't occurred to us. His treasured American-made Mickey Mouse phone works just fine, so the lines ought to be somewhat similar. Any thoughts?

Jim Tolson  
via Internet


**A.** Hey, Jim, this a trick question, isn't it? As you know, fax is an international standard, with the only difference being whether you want to send the pages in fine (slower) or normal (faster) resolution. At its top speed a fax transmission won't exceed 14,400 bps — well within the limits of any phone line I've run across. My experience is that Japan has a good phone network, so that would be the least of his worries. What I might say to your friend is that most USA-bound equipment has an input voltage range of 90 to 130 VAC. Therefore, I suspect he can forego the stepdown transformer — but don't quote me on that.

**Mini-Circuits To The RF Amp Rescue**

**Q.** Could you please provide a schematic for a video amplifier with an output in the range of 10 dB gain, and runs off of 5 to 12 volts DC?

Bob Jordan  
via Internet

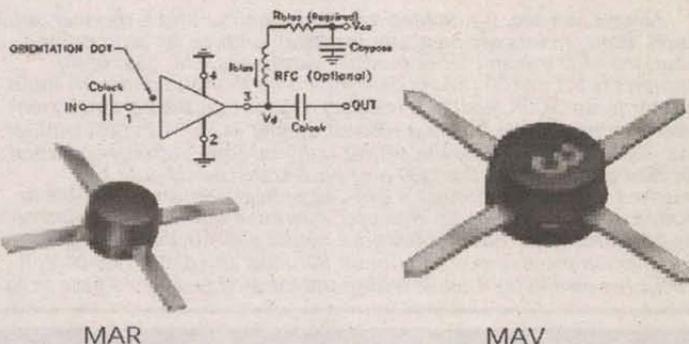**A.** This is a real no-brainer because **Mini-Circuits (718-934-4500; <http://www.minicircuits.com>)** makes a monolithic four-terminal device that fits your needs exactly. They operate from 3.5 to 15 volts, and have gains up to 26 dB. Best of all, they cost about a buck each! Here's a typical application using the MAR-7.



This device sells for \$1.05, requires just five volts, has a bandwidth of 8 GHz, and a gain of 13.5 dB. The Mini-Circuits MAR and ERA series of amplifiers are monolithic devices using gallium arsenide HBT (heterojunction bipolar transistor) technology. The internal circuit configuration is a Darlington pair, embedded in a resistor network. The resistors determine the DC operating point of the transistors, and provide feedback to set RF gain, bandwidth, and input and output impedance to optimum values.

Blocking capacitors are needed at the input and output ports. They should be of a type having low ESR (effective series resistance), and should have reactance low enough not to affect insertion loss or VSWR adversely at low frequency. The blocking capacitors must be free of parasitic (parallel) resonance up to the highest operating frequency. Use of a bypass capacitor at the connection to the DC supply is advised to prevent stray coupling to other signal processing components.

But this is just one of many Mini-Circuits RF amplifiers. Check them out — they'll be happy to send you their RF/IF Designer's Handbook (for free) which is jam-packed with data sheets, tips, and design information. (Damn, I hate it when I have to be this terse. A

Source Code:810NV Sale Ends: 12/15/98

[www.spysite.com](http://www.spysite.com)

**COVERT SURVEILLANCE: Protect Your Assets**

				EXIT SIGN CAMERA EX-985 \$295
				EMERGENCY LIGHT CAMERA EL-985 \$325

**All "985" Series Color Cameras Feature:**

- Sensor: 1/3" Sharp® Color CCD
- Resolution: Over 380 TV lines
- Sensitivity: Super Low, 2 Lux
- Built-In Backlight Compensation
- Lens: 3.7 mm Pinhole
- Viewing Angle: 92 FOV
- Video Output: Female RCA
- Power: 5V DC (included)

**CLOSEOUT**

**Color Camera Kit:**

- 1/2" Sony Color CCD
- 400 TV line Res.
- 2 lux Sensitivity
- Backlight Compensation
- 4 mm Standard Lens
- Wall Mounting Kit
- 5V Power Transformer

SONY-1002 \$175

**Counter Surveillance: Protect Your Privacy**

**Protect Yourself From:**

- Telephone Taps
- Room Transmitters
- Body Wires



Built-In White Noise Generator

AI-5500 \$380

**Detects Concealed:**

- Tape Recorders
- Video Cameras
- Body Transmitters
- Room Transmitters

LED and Vibration Alert

TRVD-900 \$450

Your Payment Options: Credit Card, Cashier's Check, or Money Order

**AMERICAN INNOVATIONS, Inc.**

119 ROCKLAND CENTER ~ Suite 315 NANUET, NY 10954  
Voice: (1) 914-735-6127 Fax: (1) 914-735-3560

feature article would be better, but only to a select few. Still check it out, and gather what you can.)

**Great Web Sites To Visit**

WinFiles.com (<http://www.winfiles.com>), formerly known as Window95.com, is the premier site on the web devoted exclusively to Windows 3.1, Windows 95, Windows 98, Windows NT, and Windows CE with great 32-bit shareware, drivers, tips, and information. Need an updated driver for your mouse? You'll find it here. Worried about Y2K? No sweat, there's a library of BIOS upgrades as well. There's a wealth of other information at this site, too. Cobsys Computers "Windows 95 Tips & Tricks" has all the dirt you'll ever want on Windows 95. FREE access to over 200 Tips & Tricks, listed in seven different categories, plus "System Optimization" Scott Wainner's incredible site with every performance and system optimization trick, hardware and software, you could ever hope to find!

Need datasheets on new and obsolete ICs? Look no further than QuestLink (<http://www.questlink.com>). This site has links to every major semiconductor vendor, including some rather obscure ones like Peregrine Semiconductor. In addition to tons of datasheets and more than 4,000 application notes there's a semiconductor supermarket where you can buy ICs one at a time! Better yet, the minimum purchase is just \$10.00. While targeted at the design engineer, it's an excellent source of parts for the hobbyist with an opening bid much lower than the \$25.00 minimum imposed by Digi-Key, Newark, et al.

In the meantime, what evidence did the dinosaurs leave behind besides bones? Find out here <http://www.emory.edu/GEOSCIENCE/HTML/Dinotraces.htm>. I think dinos are cool, and I have a really neat dino CD called "Eyewitness Virtual Reality Hunter Dinosaur Hunter" that "pits your wits against the past." Trust me, it's fun. Contact DK Multimedia at <http://www.dk.com> for a free romp.

Finally, check out the Modem Speed Test Page at <http://www.toast.net/~leslie/testpage.htm>. It will tell you whether or not your old POTS (Plain Old Telephone System) phone lines and modem can carry on a 56K conversation with our — soon to be new — revised web site (<http://www.nutsvolts.com>).

**Have a Happy New Year!**  
TJ Byers  
Q & A Editor

**MAILBAG**

The advice in Oct. '98 Electronics Q & A about quiet 2-MHz clocks missed the mark in several places. First, dithering the clock oscillator for a 20-bit ADC is a mistake because it introduces errors into the conversion. To maintain 20-bit (1 ppm) resolution in amplitude, you must also maintain about 1 ppm resolution in time. For a 50-KHz sample rate, the clock should be stable to 20 picoseconds.

Second, the original question is misleading. There are a couple of interpretations. The literal interpretation is the 20-bit ADC is working fine except that the 2-MHz clock causes a lot of radio interference to other equipment. In this interpretation, the column's advice about quieter clocks makes sense, but lacks some better advice. Shielding is very effective at killing 2-MHz radiated noise — a 1/16 inch aluminum shield provides more than 150 dB of absorption loss. Filtering the power supply and using bypass capacitors are also important.

A second (and more reasonable) interpretation is the 20-bit ADC outputs a lot of noise and the analog signals show a lot of sharp edges that coincide with the 2-MHz clock. In other words, Steve's project doesn't have the performance he wants. This interpretation is more likely, and it means there is nothing wrong with the 2-MHz clock. The clock and its harmonics are out of the ADC's input band. In this interpretation, the problem is inadequate isolation between the

digital and analog parts of the circuit.

For good performance, the analog and digital circuits must be isolated. Otherwise digital currents flowing in the analog parts of the circuit will create IR voltage drops that look like noise. The circuit design needs separate analog and digital supplies, separate analog and digital ground planes, and a single point ground connection between the two systems. The ground plane cuts need careful thought. In addition to isolating the supplies, the designer must also minimize electrostatic and electromagnetic coupling.

In particular, you must keep the digital signals away from the analog signals. Assume that an output bit of the ADC toggles at 16 KHz. If that bit is close to an analog node, say close enough to have 1pF of coupling capacitance, then the capacitive impedance between the two nodes is 10 megohms. Finally, if the analog node impedance is 10K, then the 5-volt digital signal will couple 5mV of noise to the analog node. That 20-bit ADC (whose LSB is about 5 microvolts) just became a 10-bit ADC. To kill the noise, separate the analog and digital traces and use guard rings or other shields to minimize coupling capacitance. (Use low impedance circuits (10K is too large).

Gerald Roylance  
Mountain View, CA

**JFETS**

ULTRA LOW NOISE  
LS843 - 3nV/Hz typ

TIGHT MATCHING  
LS843 - 1 mV max

- ◆ N & P Channel
- ◆ Duals & Singles
- ◆ Custom Screening
- ◆ Die, SMT, Thru-Hole
- ◆ No Order Minimum
- ◆ COD's Accepted

Second Source for Domestic & Foreign JFETS & Bipolars

Full Service U.S. Manufacturer of Specialty Linear Products

**LINEAR SYSTEMS**

4042 Clipper Court  
Fremont, CA 94538  
510-490-9160/510-353-0261 (Fax)  
E-mail: 3623671@MCIMAIL.COM

Write in 103 on Reader Service Card.



**K  
D  
E**

**ALL CABLE NEEDS  
SE HABLAN ESPAÑOL  
CONVERTERS  
ALL BRANDS WITH REMOTE**

**TOLL FREE ORDER LINE:  
1-800-361-4586**

ALSO

**HOOK-UP HELP LINE:  
1-847-233-0621**

**COMPETITIVE PRICING**

**PARENTAL LOCKOUT AVAILABLE**

**HOURS: Mon. thru Fri.  
9-6, Sat. 10-2  
30-DAY MONEY BACK GUARANTEE  
1 YEAR WARRANTY**

**NO ILLINOIS SALES**





**KDE ELECTRONICS CORP.**  
P.O. BOX 1494, ADDISON, IL 60101

Write in 101 on Reader Service Card.



The RF Connection  
213 North Frederick Ave.  
Suite 11NV  
Gaithersburg, MD USA  
20877

<http://www.therfc.com/>

Complete Selection of MIL-Spec Coax, RF Connectors and Relays

UG-21B/U N Male for RG-213/214.....	\$5.00
UG-21D/U N Male for RG-213/214.....	\$3.25
<b>N Connectors for 9913/Flex14XL/9096</b>	
UG-21B/9913.....	\$6.00 Pins Only.....\$1.50
UG-21D/9913.....	\$4.00 Extra Gasket......75
Amphenol 83-1SP-1050 PL-259.....	\$0.90
UG-176/U Reducer RG-59/8X .25 or 5/\$1.00	
UG-176/U Reducer RG-58/58A .25 or 5/\$1.00	
Silver Teflon PL-259/Gold Pin.....	\$1.00 or 10/\$9.00

MIL-Spec Coax Available (Teflon, PVC IIA)

New Product: Belden 9913F. 9913 with High Density PE Foam dielectric, stranded center cond. and Duobond III Jacket.....  
..... .80/ft or \$76.00/100ft

Also New: 9092, RG8X with Type II Jacket Intro Price.....\$23.00/100ft

Call for Specials of the Month

Full Line of Audio Connectors for Icom, Kenwood, and Yaesu

8 Pin Mike Female.....	\$2.50
8 Pin Mike Male Panel.....	\$2.50
13 Pin DIN for Kenwood.....	\$2.75
8 Pin DIN for Icom.....	\$1.00
8 Pin DIN for Kenwood.....	\$1.50

Prices Do Not Include Shipping

Orders	800/783-2666
Info	301/840-5477
FAX	301/869-3680

Write in 102 on Reader Service Card. 19




### RCA 39-BUTTON REMOTE CONTROL

This "semi-universal" unit works on several products and brands. Just press desired function button and enter the 3-digit code provided. Requires four AAA batteries (not included). Unused.  
**97V010 \$9.95 each**


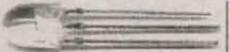
### DIODE GRAB BAG

Thousands of diodes of all kinds, including Zeners, Power, Schottky, Signal, etc.  
**94S007 One-Pound Mix - \$14.95**



### "SEMI-JUMBO" BICOLOR LED

Red/green, water clear, 7.5mm, common anode. 30° viewing angle with internal reflector. Approx. 1.8V @ 20mA (requires external resistor/s.) Shown actual size.  
**SE80124 99¢ each**



### 115V FAN

Size 3-1/8" sq. x 1". Corair/Rotron model SU2B5.  
**98F002 \$4.95 each**



### PENTIUM COOLING FAN

12VDC, 0.8A, with heatsink. Sanyo Denki #109P6612H2036.  
**98F003 \$15.00**

### 2000 GAUSS SUPER MAGNET

Black rectangular magnet, 2.5" long x 1.125" wide by 0.375" deep. These will definitely hold your calendar up!  
**98N013 \$5.95 each**

### UNIPOLAR STEPPERMOTOR DRIVER IC

UCN5804. Drives a unipolar stepper in one of three operating modes: single phase, two phase or half step. Up to 1.25 Amps per phase. Step and direction input. Drive with a 555 timer, parallel port, etc. Build your own robot, anything that requires precision positioning.  
**93I002 \$4.50 each**

### AIRPAX PULSE MOTOR


7.5"/step, 48 s/rev., 12VDC, 6-wire. Airpax #LA82407, with spec sheet.  
**92M010 \$3.95 each**

### COMBO PACK!

One 93I002 IC and 92M010 motor (both shown above) with schematics.  
**93I003 \$7.95/set**


### 10WATT STEREO SPEAKERS

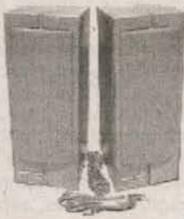11.75"H x 4.5"W x 4.75"D. With RCA cables. Non-powered.  
**98V009 \$14.95/Pair**



### 12VDC MINI FAN

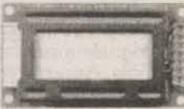2.375" square by 0.75" thick.  
**94F004 \$4.95 each**



### LCD DISPLAY

1 Row, 8 characters, with backlit face 1-3/8" x 9/16". Standard 14-pin interface with pinout sheet.  
**97L001 \$7.95 each**

### RED GLYPTAL INSULATING VARNISH

2-oz. bottle.  
**94Z034 \$1.99 each**



### PC MOUNT TRANSFORMER

Primary: 115/230V, 50/60Hz, 180/90mA. Secondary: 15/30VCT, 14VA. Wiring diagram printed on unit.  
**98N010 \$4.95 each**



### POWERSONIC AUTOMATIC CHARGER

For 12V gel cell. Input: 120VAC, 60Hz, 0.11A. Output: 12VDC @ 0.3A.  
**98E025 \$9.95**

### 12VDC 2A BRICK POWER SUPPLY

**98E026 \$4.95 each**



### SMALL BUZZER

6VDC, 5/8" x 5/8" x 1".  
**97V007 \$1.49 each**



### BNC Female

Single-hole chassis-mount type.  
**CB125A 69¢ each**



### 6 METER FSK RECEIVER

Crystal controlled on 50.675 receive frequency. Superhet with 10.7MHz IF. Three ICs and one transistor. Not a kit! New, with schematics and spec sheet for major components.  
**92A067 \$9.95 each**



### MOTOR RACK ASSEMBLY

Motor runs on 12VDC @ approx. 150 mA. Pinion and gears operate nylon rack for approx. 3". Several bells, whistles, switches, etc., attached. Approx. 7.75" L x 1.5" W x 1" H.  
**97M003 \$9.95 each**




### SHAPE-MEMORY ALLOY LINEAR ACTUATOR

One inch-pound actuator made of Tinel. Applications include robotics, doors, valves, toys, shutters, security devices, manipulators. Operated by temperature or electricity. De-energized length: 100mm. Energized length: 75mm. Self-activating temperature: 165°F. Spec sheets included.  
**95T001 \$7.95 each**
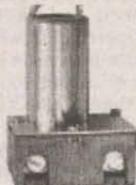
### ROBOTICS RELAY

Control circuits up to 2500 Watts with a DC pulse. This 12-30V latching relay will stay in position until it receives a second pulse. Control the unit from a simple SPDT-NO switch or from logic. Ideal for robotics, power control, remote control or controlling a load from several locations. Application notes included.  
**94B010 \$7.95 each**



### TRANSPARENT 3-BUTTON MOUSE

Watch your mouse in action! Selectable 2- or 3-button operation. Fully compatible with Mouse Systems and Microsoft. 300 DPI opto-mechanical encoder. Six-ft. cable with DB-9 connector. FCC approved. Easy-to-follow instructions and software on 5.25" floppy disk.  
**MUS3C \$7.95 each**



### RECHARGEABLE BATTERY

For 9V service (7.2V nominal value).  
**97E008 \$1.49**



### 50' LONG PHONE CORD

Fifty feet of 4-conductor black cable with 6-position plugs for use from telephone to wall jack.  
**98W020 \$2.95 each**



### 14-DAY PROGRAMMABLE TIMER

Originally used to control a satellite receiver through its IR port. Time on/off for eight distinct events. Modify it for your needs or dismantle it for its parts. Programmable with a 2732 EPROM in a removable "personality" module, the unit may be modified to control any IR device through its IR port. Contains Z80 CPU, clock display and associated parts. Operates from 9VDC 500 mA wall transformer which is included.  
**92V014 \$9.95 each**



### EMERGENCY SURVIVAL COMMUNICATIONS

How to Build and Power Your System Keys to survival news. Shortwave radio. World of amateur radio. Scanning. CB/Citizens Band. Personal communications systems. Satellite radio and guide. Alternate power sources. Free playing radio. Weather information. Radio antennas. Source lists. paper, 182pp, 8.5 x 11.  
**98X008 \$9.95**



### PIEZO FAN

A very unique fan. Made up of two piezo-electric strips mounted in a plastic case. When AC voltage is applied the strips vibrate causing a fanning action. Optimum output at 110VAC. Will work down to 20VAC at decreasing output. 3.75" x 2" x 1.125". With specs.  
**92F015 2 for \$9.95**

### STEREO HEADPHONE

Dynamic type speakers. Frequency response: 20-20,000Hz. 3.5mm stereo plug. Weighs less than 2 oz.  
**98V008 \$4.95**



### BREVEL DC GEAR MOTOR

Model "H." 110VDC @ 1A full load. Operates from 120VAC - full wave rectified. Output shaft 300 RPM. Motor 3"D x 4"L. Gearbox 1.5"D x 2.5"W x 3.5"H. Shaft 0.375"D flattened x 2.25"L.  
**92M029 \$19.95 each**



### HIGH VOLTAGE PROBE

This high-voltage probe meter offers extreme reliability and user safety. Voltage measurements up to 40,000 Volts are performed accurately and quickly. The probe is factory calibrated and should never need recalibration. Accuracy at 25kV is ±2% and ±3% at full scale. The core magnet type meter is unaffected by common outside magnet fields and is highly shock resistant. The probe body is molded of high-impact ABS plastic for maximum insulation and lightest weight. Supplied with two interchangeable tips: one conventional round needle type and one specially designed flat spring type for easy access to CRT anode.  
**95Z003 \$44.95 each**

### BOOM MIKE

Electret condenser type. This versatile microphone may be wired for handy-talkie, sound card, telephone, base station, aircraft radio, CB radio, motorcycle intercom, etc. An earphone or miniature speaker may be installed in either or both muffs. The microphone unit can be easily removed and installed on another headset or helmet.  
**92A001 \$4.95 each**



# ALLTRONICS


2300-D Zanker Road - San Jose, CA 95131-1114

World Wide Web: <http://www.alltronics.com>

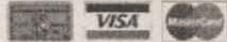(408) 943-9773 - Fax (408) 943-9776

Send \$2.00 For Our Latest Catalog!

\$4.00 Foreign. Refundable on First Order.



Store Hours: 9-6 M-F & 10-3 Sat. - Pacific  
Visa, M/C, AmEx Accepted.

All Sales Final.  
California Residents Add Sales Tax.  
Shipping Additional on All Orders.  
Prices Good 60 Days from Date of Publication



# Tiny FBasic Computer



(Shown 85% Actual Size - 40 pin DIP)

The Tickit 62 module is like a Parallax Basic Stamp® II, but has 4 times the program space installed (expandable to 64K). It also has 4 times the variable space (96 bytes), and uses a modern structured language similar to BASIC only more powerful.

- Only tool you need is a PC
- Inexpensive \$45/module, \$16/IC
- Development Kit only \$45
- Huge library of I/O function
- Structured FBasic Language
- Easy to learn and use
- Powerful enough for large projects

ASK ABOUT OUR STAMP COMPATIBLE PERIPHERAL COMPONENTS

## VersaTech

Electronics

PHONE: (303) 828-9156, FAX: (303) 828-9316

e-mail: versatech@csn.net


Web: //www.csn.net/versatech

11170 Flatiron Drive, Lafayette, CO 80026

Basic Stamp is a registered trademark of Parallax, Inc.
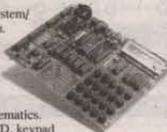
## Learn MICROCONTROLLERS EMBEDDED SYSTEMS and PROGRAMMING...

with the AES learning system/ embedded control system. Extensive manuals guide you through your development project. All programming and hardware details explained. Complete schematics. Learn to program the LCD, keypad digital, analog, and serial I/O. for your applications.



THREE MODELS AVAILABLE. Choose from an Intel 8051, Intel 8088, or Motorola 68HC11 based system. All models come with:

- 32K Byte ROM, 32K Byte RAM • 2 by 16 Liquid Crystal Display • 4 by 5 Keypad • Digital, Analog, and Serial I/O • Interrupts, timers, chip-selects • 26 pin expansion connector • Built-in Logic Probe • Power Supply (can also be battery operated) • Powerful ROM MONITOR to help you program • Connects to your PC for programming or data logging (cable included) • Assembly, BASIC, and C programming (varies with model) • Program disks with Cross Assembler and many, well documented, program examples • User's Manuals: cover all details (over 500 pages) • Completely assembled and ready to use • Source code for all drivers and MONITOR • Optional Text Book

Everything you need. From \$279

Money Back Guarantee

Call for Free Info Pack, or see

WEB at <http://www.aesmicro.com>

714-550-8094, FAX 714-550-9941

Call 1-800-730-3232

### AES

Advanced Educational Systems

AES 575 ANTON BLVD., SUITE 300, COSTA MESA, CA 92626, USA

## Open Channel

ponents in Figure 1 except the voltage regulator (U3) and C6, which will be off-board or elsewhere in the system. If you don't wish to etch your own printed circuit board, then use the guy I had make mine: FAR Circuits (18N640 Field Court, Dundee, IL 60118). Send Fred a copy of Figure 2A so that he can identify it in his files. He has a lot of my designs on file, so may find it perplexing to figure out just which one you mean. Judging from FAR's rates, I suspect that about \$7.00 ought to buy this board, but you might want to check with them for current pricing.

Figure 3 shows two views of the completed project. The view in Figure 3A is the printed circuit board (Figure 2A) with components assembled. (Note: This photo was taken before C8 was installed.) The box shown in Figure 3B is one of the SB "Lab" series made by SESCOM, Inc. (2100 Ward Drive, Henderson, NV 89015-4249). This company makes a number of really interesting boxes for RF and other builders. I've bought quite a number of them because they are "tighter" for RF than some of the other aluminum and steel construction boxes on the market ... and that means better shielding (which is all important in RF work).

The connectors for input and output can be any coaxial connector. I used RCA phono connectors because of space constraints in the project that this IF amplifier will be used in. At 10.7 MHz, the loss of RCA phono connectors (which are normally used at audio) is negligible, so ought not pose any problem. At higher frequencies, I recommend BNC connectors, SMC connectors, or SO-239 "UHF" connectors (if you've got lots of room!).

The power and gain control connections are bought through the aluminum box wall through 1000 pF feedthrough capacitors (also in the SESCOM catalog, plus other sources). Two kinds are available: one solder-in and the other screw thread mounted. For aluminum boxes, the screw thread is needed because it is difficult to solder to aluminum. Both types are available in either 1000-pF or 2000-pF values, either of which can be used in this application. If you elect to use some other form of connector, then add disk ceramic capacitors (0.001 µF) to the connector, right across the pins as close as possible to the connector.

There are several ways to make this circuit work at other frequencies. If you want to use a standard IF frequency up to 45 MHz or so, then select one with the configuration shown in

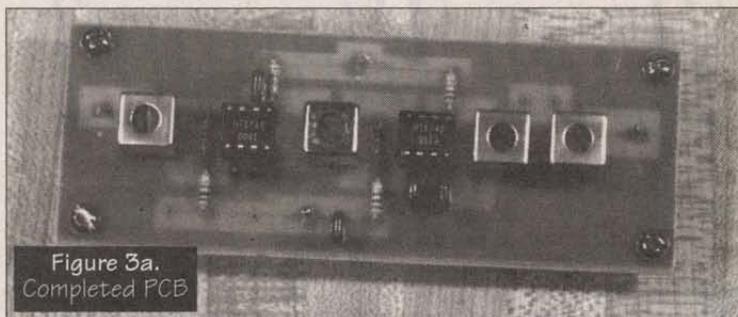


Figure 3a. Completed PCB

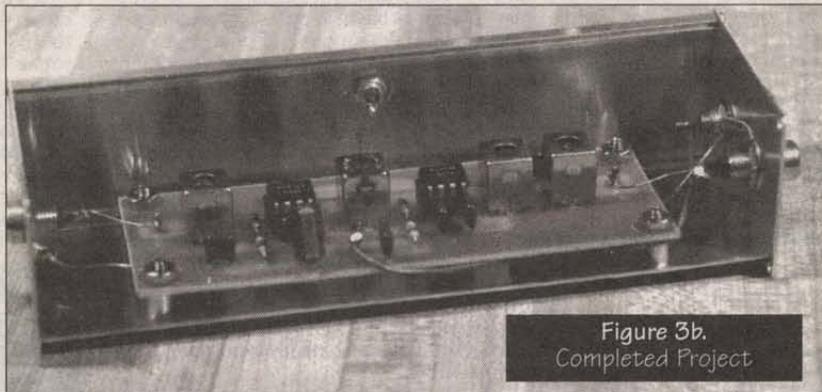


Figure 3b. Completed Project

Figure 1 (these are standard).

If you want to make the circuit operate in the HF band on a frequency other than 10.7 MHz, then it's possible to use the 10.7 MHz transformer. If the desired frequency is less than 10.7 MHz, then add a small value fixed or trimmer capacitor in parallel with the tuned winding. It will add to the built-in capacitance, reducing the resonant frequency. I don't know how low you can go, but I've had good results at the 40-meter amateur band (7-7.3 MHz) using additional capacitance across a 10.7 MHz IF transformer.

On frequencies higher than 10.7 MHz, you must take some more drastic action. Take one of the transformers, and turn it over so that you can see the pins. In the middle of the bottom header, there will be an indentation containing the tuning capacitor. It is

a small tubular ceramic capacitor (you may need a magnifying glass to see it well if your eyes are like mine). If it is color coded, then you can obtain the value using your knowledge of the standard color code. Take a small screwdriver and crush the capacitor. Clean out all of the debris to prevent shorts at a later time. You now have an untuned transformer with an inductance right around 2 µH (I measured values between 1.8 µH and 2.6 µH using the inductance function of my DMM). Using this information, you can calculate the required capacitance using:

$$C = \frac{2.53 \times 10^{10}}{f^2 L_{\mu H}} \text{ picofarads}$$

where:

C is the capacitance in pico-

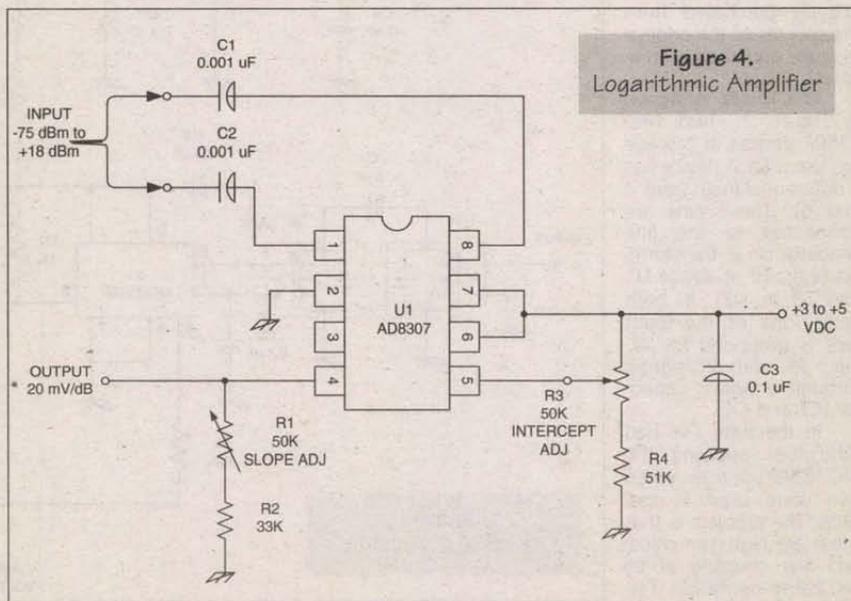


Figure 4. Logarithmic Amplifier

farads  
f is the desired frequency in KiloHertz (KHz)  
LμH is the inductance in microhenrys

Equation (1) is based on the standard L-C resonance equation, solved for C, and with all constants and conversion factors rolled into the numerator. If you know the capacitance that must be used, and need to calculate the inductance, then swap the L and C terms in Equation (1).

If the original capacitor was marked as to value or was color-coded, then you can calculate the approximate capacitance needed by taking the ratio of the old frequency to the new frequency, and then square it. The square of the frequency ratio is the capacitance ratio, so multiply the old capacitance ratio to find the new value. For example, suppose a 110 pF capacitor is used for 10.7 MHz, and you want to make a 20.5 MHz coil. The ratio is  $(10.7 \text{ MHz}/20.5 \text{ MHz})^2 = 0.272$ . The new capacitance will be about  $0.272 \times 110 \text{ pF} = 30 \text{ pF}$ .

For other frequencies, you might consider using homebrew toroid inductors. The PCB pattern of Figure 2A can still be used, but you will have to run the wires from the toroid core coils to the correct holes.

A variation on the theme is to make the circuit wideband. This can be done for a wide portion of the HF spectrum by removing the capacitors from the transformers, and not replacing them with some other capacitor.

In the example above, I used a frequency of 20.5 MHz (i.e., 20,500 KHz) to make the calculation. The reason is simple: it is a prime radio-science observing frequency for finding natural radio signals from Jupiter (see my book *RadioScience Observing Volume 1*). It is possible to build a tuned radio frequency (TRF) receiver for that frequency using this circuit, but re-tuned to 20.5 MHz.

**Logarithmic RF/IF Amplifier**

A logarithmic amplifier produces an output signal that is proportional to the logarithm of the input signal. There are a number of applications for these amplifiers. Some of them take advantage of the range compression that takes place, making it easier to get a large dynamic range. In other cases, log amps are used to convert linear signal levels to the logarithmic decibel (dB) scale. The AD8307 log amp (Figure 4) will fit a lot of these uses, including radio-science observing receivers. It has a 92 dB dynamic range from -75 dBm to +17 dBm, and operates over the range DC to 500 MHz with  $\pm 1$  dB linearity. It produces a slope of 25 mV/dB and an intercept of -84 dBm, but this can be trimmed to other values using the SLOPE ADJ and INTERCEPT ADJ potentiometers shown in Figure 4. The DC power requirements

are +2.7 VDC to 5 VDC at 7.5 mA. If you want to see the entire spec sheet for the AD8307, then go to the Analog Devices web site (<http://www.analog.com>). The data sheet is available in \*.PDF format, so you will need Adobe Acrobat Reader to display and print it. The device can be purchased for around \$18.00 from Newark Electronics and other Analog Devices distributors.

**RadioScience Observing**

Amateur scientists can often make contributions to "real science" by careful recordkeeping and observation. One of the more popular amateur science activities is radio-science observing (judging from my mail and E-Mail it is also very popular with *Nuts & Volts* readers). At one time, amateur radio operators and shortwave listeners kept log books as standard practice, but that habit seems to have fallen away in recent years. But there is a real good reason to do so if you are a radio-science observer.

Here's the reason. On August 27, 1998 at about 1022 UTC (GMT to us old guys), the earth was struck by a very large burst of gamma rays. It appears to have initiated from a neutron "magnetar" star (catalog number SGR 1900+14). Solar detectors on the sun-lit side of earth missed the event, so data is lacking. According to a report in *Popular Communications*, a researcher at the National Radio Astronomy Observatory (NRAO) is looking for any data from people who were monitoring the radio bands on Thursday morning (0322 PDT or 0622 EDT), August 27th, 1998. Send reports via E-Mail to Mr. Paul Harden at [pharden@nrao.edu](mailto:pharden@nrao.edu). Include your location (latitude and longitude if you know it), the station that you were listening to, and the frequency. This was an extremely rare natural event, and the scientists have a lot less data than they need!

Note: If, like many radio-science observers, you have paper strip charts or computer records of signal strengths, you might want to offer them to the scientists.

I first heard of this event from my E-Mail. I subscribe to the Public Seismic Network list server. The first indication of an event was a fellow who was trying to get his instruments working, but found them pegged to full-scale. A number of "helpful" suggestions on circuit and local interference causes were offered. Pretty soon, however, a number of E-Mail messages were submitted to the list server indicating a lot of sites saw the same pegged condition. Later that day, a television news report told the story of the August event. **NV**

**Connections ...**

I can be reached by snail mail at P.O. Box 1099, Falls Church, VA 22041, or via E-Mail at [CARRJJ@AOL.COM](mailto:CARRJJ@AOL.COM).

**AST GLOBAL ELECTRONICS**

24529 STATE HWY. 408, CAMBRIDGE SPRINGS, PA 16403  
VOICE 814-398-8080 • 1-888-216-7159 • FAX 814-398-1176

VIEW COMPLETE LISTING AT:  
<http://www.astglobal.com>

IF WE DON'T CARRY IT ... WE'LL FIND IT  
QUICKLY ... AT REASONABLE PRICES.

B&K 3030, Sweep/Function Generator, 2MHz (Sine, Square, Triangle).....	\$175	HP 8294A, Power Supply, 0-60V @ 1A (metered).....	\$275
Dranetz 626, Universal Disturbance Analyzer, Frame only w/Power Supply & Communication Plug-in.....	\$375	HP 8011A, Pulse Generator, 1Hz-20MHz.....	\$175
EIP 545, Microwave Counter 18GHz.....	\$650	HP 8013B, Pulse Generator, 1Hz-50MHz.....	\$275
ESI DP1311, Variable Resistor, 100K max 1K/Step.....	\$100	HP 8015A, Pulse Generator, 1Hz-50MHz 30V.....	\$425
ESI RV726, Decade Voltage Divider.....	\$375	HP 8091A, Rate Generator (1GHz) w/8092A Delay Generator (1GHz) w/8093A Output Amp w/1500A & 15400A.....	\$2,000
Fluke 332B, DC Voltage Standard.....	\$475	HP 8165A, Programmable Sig Source, 1mHz-50MHz.....	\$650
Fluke 335A, DC Voltage Standard.....	\$375	HP 8180A, Data Generator.....	\$425
Fluke 382A, Voltage/Current Analyzer.....	\$625	HP 8410B, Network Analyzer Mainframe.....	\$275
Fluke 540B, Transfer Standard w/AS4-2 Voltage Plug-in.....	\$625	HP 8414A, Polar Display.....	\$325
Fluke 721A, Lead Compensator.....	\$275	HP 8443A, Tracking Generator, 10Hz-10MHz.....	\$325
Fluke 760A, Meter Calibrator.....	\$450	HP 8444A, Tracking Generator for 14T1 System, 5-1900MHz.....	\$750
Fluke 845AB, Null Detector/Micro Voltmeter 1uV-1000VDC.....	\$375	HP 8445B, Auto Prescaler, 1.8-18GHz.....	\$550
Fluke 845AR, Null Detector/Micro Voltmeter 1uV-1000VDC.....	\$375	HP 8553B, RF Plug-in (for 140 Series Mainframes), 1KHz-110MHz.....	\$425
Fluke 893A, AC/DC Differential Voltmeter 0 to 1100 Volts, AC/DC, 0.1%DC, 0.5%AC, 1uV Resolution.....	\$100	HP 8553L, RF Plug-in (for 140 Mainframes), use with 8552A, 1KHz-110MHz.....	\$125
Fluke 3330B, Constant Current/Voltage Calibrator.....	\$475	HP 8601A, Sweeper Generator, 1-110MHz.....	\$425
Fluke 5100B, Multifunction Calibrator, Opt. 0305.....	\$3,250	HP 8614A, Signal Generator, 800-2400MHz, AM/FM Leveled.....	\$475
Fluke 5100B, Multifunction Calibrator.....	\$2,700	HP 8616A, Signal Generator LHF, 1.8-4.5GHz, +10-126dB, AM/FM.....	\$475
Fluke 5200A, Programmable AC Calibrator.....	\$1,250	HP 8624D, RF Plug-in, 5.9-9.0GHz.....	\$350
Fluke 5215A, Precision Power Amp.....	\$950	HP 8640B, Signal Generator, 5-105MHz, Opt. 002001 or 003.....	\$1,800
Fluke 6011A, Synthesized Signal Generator, 10Hz-11MHz.....	\$550	HP 8648B, Signal Generator, 5-512MHz, Opt. 001 or 003.....	\$950
(7-digi).....	\$550	HP 8743A, Reflection Test Set, 2-12.4GHz.....	\$175
Fluke 8060B, Synthesized Signal Generator 10KHz-105MHz.....	\$1,800	HP 8901A, Modulation Analyzer.....	\$1,000
Fluke 8070A, Synthesized RF Signal Generator 200KHz-520MHz.....	\$1,500	HP 89303A, D/A Converter.....	\$175
Fluke 8000A, DMM 3-1/2 Digit.....	\$75	HP 89501A, HP-IB Isolated D/A Converter.....	\$125
Fluke 8050A, DMM 4-1/2 Digit w/Battery Pack.....	\$145	Huntun Tracker 2000, w/140 Switcher (rice).....	\$1,000
Fluke 8050A, DMM 4-1/2 Digit w/Battery Pack.....	\$145	Kepco ATE15-50M, Power Supply, 0-15V @ 50A (metered).....	\$650
		Kepco ATE55-5M, Power Supply, 55V @ 5A (metered).....	\$425
		Kepco BVP100-4M, Bi-Polar Power Supply, 0-100V @ 4A.....	\$520
		Kepco JCE 36-15MWPT, Power Supply, 0-36 @ 15A (metered).....	\$275
		Kepco JCE 36-3MWPT, Power Supply, 0-36 @ 3A (metered).....	\$175
		Krohn-Hite 3302R, Dual Channel Tunable Filter, 20KHz-2MHz, High Pass, Low Pass Band Reject.....	\$275
		Polarad SPNH, Signal Generator, 20KHz-20KHz.....	\$450
		Polarad SPNL, Signal Generator, 1Hz-600KHz.....	\$350
		Recold Dana 9303, True RMS RF Level Meter.....	\$550
		Rockland 1022F, Dual HiLo Filter.....	\$150
		Rockland 5100, Synthesizer, DC-2MHz, .001 Hz Resolution.....	\$325
		Sencore SC61, Scope (100MHz) w/No Probes, Dual Trace.....	\$750
		Sencore SC61, Scope (100MHz) w/No Probes, Dual Trace.....	\$600
		Sencore SC3100, Waveform Analyzer (like new).....	\$1,900
		Sencore TV92, TV Video Analyzer.....	\$1,100
		Sorsonator DCR-80-5A, Power Supply, 80V @ 5A (metered).....	\$475
		SRL 112B, PLO/PRF Synthesizer.....	\$125
		Tek DC503, Plug-in Counter Universal, 100MHz.....	\$150
		Tek DMS01A, Plug-in DMM, 4-1/2 Digit.....	\$175
		Tek DMS02, Plug-in DMM, 4-1/2 Digit.....	\$150
		Tek FG501, Plug-in Function Generator, 0.01Hz-1MHz.....	\$175
		Tek FG504, Plug-in Function Generator, 0.01Hz-40MHz.....	\$450
		Tek PG501, Plug-in Pulse Generator, 5Hz-50MHz.....	\$175
		Tek P5501-1, Plug-in Power Supply.....	\$175
		Tek P5503A, Plug-in Power Supply Triple.....	\$175
		Tek OIG-502, Plug-in Optical Impulse Generator (unused).....	\$950
		Tek T922, Scope (15MHz), Dual Trace, rice.....	\$125
		Tek TMS03, Power Module, 3 Slot.....	\$125
		Tek TMS04, Power Module, 4 Slot.....	\$150
		Tek TMS07, Power Module, 6 Slot.....	\$200
		Tek T102B, Digitizer.....	\$100
		Tek T716A, Plug-in (225MHz), Single Trace Amp.....	\$175
		Tek T718, Plug-in (75MHz), Dual Trace Amp.....	\$75
		Tek T719, Plug-in (600MHz), Single Trace Amp.....	\$150
		Tek T726, Plug-in (200MHz), Dual Trace Amp.....	\$150
		Tek T780A, Plug-in (150MHz), Time Base.....	\$125
		Tek T785A, Plug-in (100MHz), Dual Time Base.....	\$75
		Tek T787B, Plug-in (200MHz), Time Base.....	\$150
		Tek T7892A, Plug-in (500MHz), Dual Time Base.....	\$200
		Tek T7D11, Plug-in Digital Delay.....	\$125
		Tek T7D13, Plug-in DMM 3-1/2 Digit.....	\$175
		Tek T7D15, Plug-in Counter/Timer, DC-225MHz.....	\$225
		Tek T7L1, 1.5-60GHz Spectrum Analyzer.....	\$1,700
		Tek T7S11, Plug-in Sampling Unit.....	\$175
		Tek T13A, Current Probe Amp.....	\$100
		Tek 453, Scope (60MHz), Dual Trace.....	\$175
		Tek 465, Scope (100MHz), Dual Trace.....	\$425
		Tek 465B, Scope (100MHz), Dual Trace.....	\$475
		Tek 466, Scope (100MHz storage), Dual Trace.....	\$475
		Tek 475, Scope (200MHz), Dual Trace.....	\$675
		Tek 475A, Scope (250MHz), Dual Trace.....	\$625
		Tek 475DMM4, Scope (200MHz), Dual Trace w/DMM.....	\$675
		Tek 485, Scope (350MHz), Dual Trace.....	\$650
		Tek 520A, NTSC Vectorscope.....	\$575
		Tek 2213, Scope (60MHz), Dual Trace.....	\$275
		Tek 2215, Scope (60MHz), Dual Trace.....	\$450
		Tek 2235, Scope (100MHz), Dual Trace.....	\$650
		Tek 2236, Scope (100MHz) w/Counter/Timer/DMM (unused).....	\$900
		Tek 2336, Scope (100MHz) Dual Trace.....	\$550
		Tek 2445, Scope (150MHz), 4-Channel Cursor Readout.....	\$1,700
		Tek 2465, Scope (300MHz), 4-Channel Cursor Readout.....	\$2,400
		Tek 7104, Scope (1GHz), Dual Trace.....	\$1,750
		Tek 7603, Scope Mainframe (100MHz).....	\$200
		Tek 7704A, Scope Mainframe (250MHz).....	\$200
		Tek 7854, Scope (400MHz), Dual Beam w/Waveform Calculator.....	\$625
		Tek 7904, Scope Mainframe (500MHz).....	\$275
		Wavelek 145, Pulse/Function Generator, 0.001-20MHz.....	\$350
		Wavelek 185, Lin Log Sweep Generator, 0.001Hz-5MHz.....	\$425
		Wavelek 288, Synthesized Function Generator, 20Hz-20MHz.....	\$650
		Wavelek 3000, Signal Generator, 1-520MHz.....	\$625
		Wavelek FC3B, Sweep/Function Generator 2Hz-100KHz (unused).....	\$375



• 60-DAY WARRANTY  
• 10-DAY RIGHT OF RETURN  
• SATISFACTION GUARANTEED

# We've Got It!

# MCM Electronics®

Prices effective  
January 4 through  
February 12, 1999.

To take advantage of special pricing on the items listed, please provide this code: **NVM22**

## 32 Piece Security Bit Set


Ideal for all of those difficult service applications including computer monitors, cable, telephone and vending equipment. Removes most types of security screws including security hex, torx, spanner and tri-wing. Regular price \$15.39.



Order #  
#22-1875  
\$9.99

## Aluminum Tool/Equipment Case

**Clarke**

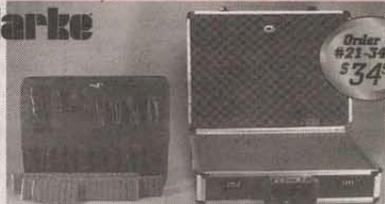

Order #  
#21-3462  
\$34.95

Includes one tool pallet and pre-cut foam bottom. Ideal for carrying test equipment with small hand tools and accessories. Black finish, measures approximately 19" x 14" x 6". Regular price \$51.50.

## Multiple DC Outlet Strip

Valuable accessory to any benchtop power supply. Eight pairs of RF bypassed binding posts allow easy connection and disconnection of multiple accessories. Features analog voltmeter, power switch, built-in fuse and 15A capacity.



Order #  
#111-2974  
\$44.95

## 12V/2.3 AH Sealed Lead Acid Battery Pack

**Panasonic**

Original Panasonic battery is commonly used in bag phones, full size camcorders and all types of portable equipment. Uses standard clip, such as MCM #28-3135.



Order #  
#P-PV-EP08A/1H  
\$38.95

## DMM With Logic Function

**TENMA®**

3½ digit DMM measures AC/DC voltage from 200mV-600V, resistance to 2000Mohm, capacitance to 20µF, transistor hFE gain and audible continuity test. Requires 9V battery (#290-080) not included. Dimensions: 2½" (W) x 5½" (H) x 1½" (D). Regular price \$65.95.



Order #  
#72-4025  
\$39.95

**FREE Catalog**



**Same Day Shipping!**

In stock orders received by 5:00 p.m. (YOUR TIME), are shipped the same day.

**MCM is the leading supplier to the consumer electronics service industry. Additionally, hobbyists, educators and even manufacturers have looked to MCM for all of their component needs. Call today for your free catalog!**

## Multi-Voltage Power Supply

Fully regulated supply provides up to two amps, at the following selectable voltages: •3 •4½ •6V •7½V •9V •12V. Regular price 16.95.



Order #  
#28-2200  
\$9.95

## Nickel-Metal Hydride Cells

Get NiMH performance in a standard "AA" or "AAA" cell. Performance is 50% over that of Ni-Cad batteries of the same size. Sold individually.

AS LOW AS  
\$2.99



Order #	Size	(1-9)	(10-49)	(50-up)
29-2615	"AA"	\$3.59	\$3.29	\$2.99
29-2620	"AAA"	4.19	3.89	3.59

## Micro PC Board Camera

**DEFENDER SECURITY**

B/W CCD camera measures only 1½" x 1¼" x 1". Provides NTSC composite video output. Built-in 3.6mm lens provides viewing angle of 92°. Requires 12VDC, 300mA. (#58-3330 AC adaptor). Regular price \$64.95.



Order #  
#82-2880  
\$49.00

## Color PC Board Camera

**DEFENDER SECURITY**

Ideal for any observation, multimedia or security application. Provides NTSC composite video output. Features automatic white balance, 330 lines of horizontal resolution and AGC. Requires 12VDC, 240mA. Regular price \$199.00.



Order #  
#82-3015  
\$149.00

## RF Modulator

Outstanding price on this popular audio/video/surveillance accessory. Accepts standard A/V signal and places it on channel three or four. RCA type inputs, "F" type output. Requires 117VAC. Regular price \$25.75.



Order #  
#33-1480  
\$19.95

## Wide-Band Radio Scanner for Your PC

**WINRADIO™**

Integrates advanced radio receiver technology and the power of a personal computer. Tune continuously from 500kHz ~1.3GHz (cellular blocked), FM (wide and narrow), AM and SSB. Hear virtually all police, fire, government, military, overseas broadcasts, HAM radio, citizens band broadcast AM, FM, and television audio. Requires Windows 3.1 or higher (including 95 and NT) and vacant slot for 16 bit ISA card. Regular price \$499.00.



Order #  
#111-6000  
\$399.00

## 8" Rubber Surround Polypropylene Woofer

**MCM AUDIO SELECT™**

Popular woofer design is the foundation of many home and auto speaker systems. 70W/100W RMS/peak capacity, frequency response 30Hz-3.5KHz. 8ohm. Other sizes available. Regular price \$13.50.



Order #  
#55-1190  
\$9.99

## 6½" Shielded Magnet Woofer

**MCM AUDIO SELECT™**

Great for use in home theater applications. Shielded magnet allows use near TV and computer monitors. Features polypropylene cone and rubber surround. 45W/60W RMS/peak capacity, frequency response 40Hz-5KHz. 8ohm. Other sizes available. Regular price \$14.25.




Order #  
#55-1186  
\$9.99

## Pre-Assembled Circuit Modules

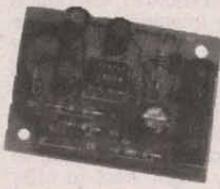**CEBEK**

Ideal for repairing old equipment, prototype work or your latest project. These well constructed PC boards are fully assembled, tested and ready to use. Supplied with application instructions and technical specifications. All operate from a single 12VDC source. Call your MCM Sales Representative for more information on over 120 available modules.



Order #	Description	Reg.	Sale
28-4795	1W audio amplifier	\$7.49	\$5.99
28-4796	5W audio amplifier	13.95	11.15
28-4800	5W x 2 stereo amplifier	24.95	19.96
28-4801	15W x 2 stereo amplifier	39.95	31.96
28-4851	88-108MHz FM transmitter	24.95	19.96
28-5115	Flip-flop relay	14.95	11.96
28-4825	VOX relay	17.95	14.36
28-4815	Electric guitar preamplifier	8.95	7.16

For complete ordering information on the items listed, or a free catalog, Call...

**1-800-543-4330**  
www.mcmelectronics.com

SOURCE CODE: NVM22

# COMPUTER CIRCULATION CENTER, Inc.

dba: Alltech Electronics

2618 Temple Heights Drive.  
Oceanside, CA 92056  
Phone Order Hours 9AM - 5:30PM Mon-Fri

Phone Orders  
760/724-2404

\$25 -Min. Order -



9350 Clairemont Mesa, San Diego - 619/573-0411  
1401 El Camino Real, Oceanside - 760/721-0093  
1300 E. Edinger, Santa Ana - 714/543-5011  
2018 W. Lomita BLVD, Lomita - 310/539-2260  
We buy surplus & excess computer inventory  
as well as scrap electronics related inventory.

## Mitsubishi DJ-1000 Digital Camera



### Pocket Size

Holds up to 15 images  
320 x 240 or 504 x 378  
PCMCIA Required for image  
downloading.  
Windows 3.1/95 Compatible  
See the web for more details

\$79


Be sure to check  
our Web Site for  
more information  
on these and other  
products!

www.allelec.com

Save on your Point of Sale systems with these refurbished and new components.

9" Monochrome VGA NEC "NEW" 640 x 480	.....\$79.00
10" SVGA COLOR View Magic .26 dp Refurb (upto 1024 x 768)	.....\$139.00
10" SVGA Color (Open Frame - Build a custom enclosure)	.....\$119.00
Fujitsu Cash Drawer NEW w/tilt, 24VDC Trigger for drawer	.....\$79.00
Cash Drawer - Epson Printer - 9" Mono VGA	.....\$199.00
Cash Drawer - Epson Printer - 10" Color SVGA .26 dp	.....\$299.00
Compact footprint 83 Key keyboard - PS/2 Type	.....\$14.95
Epson TMS300PD Parallel Receipt Printer (2 Color) Refurb	.....\$89.99

## Point of Sale Hardware

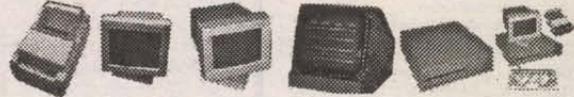

## NEC Mini 486



Mini footprint  
3.5" x 11.5 x 13  
486 SX 25 CPU  
4MB On board  
2 ISA Slots  
IDE, FD, 2  
COM, 1 LPT &  
512K VGA  
UPGRADABLE  
to DX2/66

Need a Linux Box?  
\$29.00



Light to lt-medium  
duty usage.  
360 degree swivel  
with locking  
brake. Smooth  
rolling action.

8 for \$20

1.75" Dia. Lt Wt Wheel

## Intergraph 4MB PCI Intense 3D 100


\$35.00

Rendition  
V1000e




3D Accelerated  
Video Card for  
Windows 95/NT  
See Web for  
more details

## 3D Sound Cushion

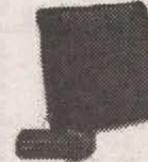

\$39.95

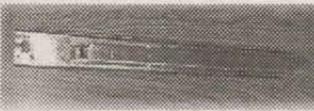Bring Life to  
your games  
and music  
experience.  
See the web for  
more info.



6 pair for  
\$29.00

Extends to 2'  
past. Two slide  
telescopic  
extension

## Ball Bearing Drawer Slide

## 10" Color SVGA!

Up to 1024 x  
768 pixels  
110V AC  
operation.

## ViewMagic



Refurb:  
\$139.00



\$9.95

## Small DC Motor w/gear box & Wheel

Robotic  
Attachments?  
Arms, etc?  
With rubber o-  
ring on 5" dia.  
disc.

## External SCSI Cases

\$29.00 & Up



5.25" Closed HH \$29.  
5.25" Open HH . \$35.  
5.25" Open FH . \$45.  
3.5" Open for Zip,  
Syquest, etc . . . \$29.  
3.5" Lunchbox . \$19.  
All cases have two 50  
pin centronics  
connectors.

## Small 105V 40 RPM Motor. 2.7W

\$9.95

Motor with spin-  
dle. Items can be  
press fit. Shaft  
has a through  
hole with a rod  
stuck in it.



## Motorola Flip Phone Data Adapter




\$39.00

RJ-11 (Dial Tone)  
Generator and Ring  
Generator. Use any  
standard land line  
device with your cell  
phone. Modem, credit  
card terminal,  
answering machine...

Large AC Motor.  
Use for robotic  
drive or ??  
Has 5" disc  
attached with a  
rubber O-Ring.

\$9.95

## Reversible 110V AC Motor with brake

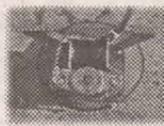

\$69.00  
24 pcs

Used 3" Dia. Wheels

360 degree  
rotatable. Ball  
Bearing for  
durability.  
These were  
from heavy  
duty mobile  
storage units

## CPUs

486SX 25/33	.....\$3.00	..\$5.00
486SX2-66	.....	\$8.00
486DX25/33	.....\$5.00	..\$8.00
486DX2-50/2-66	.....\$14.00	..\$19.00
486DX4-100	.....	\$39.00
Pentium 75/90	.....\$39.00	..\$49.00
Pentium 100 / 133	.....\$59.00	..\$69.00
Pentium 166	.....	\$79.00

Upgrade  
Your  
System



## EPROMS

2716 /2732	.....\$1.25
2764 /27128	.....\$1.25
27256 /27512	.....\$1.50
1Meg	.....\$2.50
2 Meg	.....\$2.50



\$39.00

## Macintosh 2MB PCI ATI Mach64 Video Card

Supports both  
Macintosh and  
SVGA Monitors.  
Upgradable to  
4MB

## IDE Hard Drives

420 Meg	.....\$49.00
320 Meg	.....\$39.00
270 Meg	.....\$29.00
120 Meg	.....\$20.00
80 Meg	.....\$15.00
40 Meg	.....\$10.00



## PC Oldies but Goodies

EGA/CGA Card -or- ISA Super I/O	.....\$14.95
2 Meg AT Memory Card - or - Parallel/Mono Card	.....\$9.00
Floppy Controller -or- Serial / Parallel Card	.....\$6.95
VLB 1 Meg VGA Card - or - 386 Motherboard w/2 Meg	.....\$19.95
16 Bit (ISA) VGA w 256/512/1 Meg	.....\$9.00 / \$12.00 / \$14.95
VLB Super I/O	.....\$12.95
8 Bit VGA Card - or - XT Motherboard w/640K	.....\$9.95

See Our Website for  
for more details on these  
industrial surplus items.

Robot Competition? Feeling  
creative? Build something!

## CD ROM & Sound Cards

4x IDE Internal	.....\$19.00
8x IDE Internal	.....\$29.00
24x IDE Internal with Yamaha Sound Card (ISA)	.....\$49.00
4x SCSI Internal	.....\$25.00
4x SCSI External	.....\$49.00
Universal Audio Cable (CD ROM to Soundcard)	.....\$4.95

HTTP://WWW.ALLELEC.COM  
VISIT OUR WEB PAGE DAILY FOR SPECIALS & MORE INFO. ON THESE ITEMS

# Events

# CALENDAR

## JANUARY 1999

### JANUARY 2

**CA - SANTEE** - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052.

**TN - MORRISTOWN** - Hamfest & Computer Show. Talley Ward Recreation Bldg. Talk-in: 147.303+ & 53.030-. Lakeway ARC, Perry Hensley N4PH, 423-828-4848. E-Mail: n4ph@juno.com. Kemp Lawson KF4AGB, 423-587-3320. E-Mail: kemplawson@aol.com. Web: www.usit.net/mfawbush/larc.html

### JANUARY 9

**CA - FONTANA** - Inland Empire ARC Amateur Radio & Electronics Swapmeet. A B Miller High School. Bill 909-822-4138 eves

**CO - LOVELAND** - Superfest. Larimer County Fairgrounds, 700 Railroad Ave. 9am-3pm. VE Exams. Talk-in: 145.115- or 146.85-. Northern CO ARC, Jeanene Gage N0YHY, 970-351-7327 or 970-352-5304

**NE - KEARNEY** - Hamfest. Midway ARC, Bob Mayo KB0YTO, 308-236-7320

**NY - MARATHON** - Hamfest. Skyline ARC, Patrick Dunn KC2BQZ, 315-468-5909

**SC - GREENWOOD** - Hamfest & Computer Show. Greenwood Civic Center, 1610 Hwy. 72 E. 9am-5pm. FCC exams. Talk-in: 147.165+ (open) alternate: 146.52 simplex. Greenwood ARS, Frank Kolar WA9FWO, 864-229-5639. Web: http://www.w4gwd.org

**WI - WAUKESHA** - Hamfest. Waukesha County Expo Center Forum. 8am-2pm. West Allis RAC, Phil Gural W9NAW, 414-425-3649

### JANUARY 9-10

**FL - FT. MYERS** - Hamfest. Sat: 9am-3pm, Sun: 9am-2pm. Talk-in: 146.880. FL Meyers ARC, Colleen Sammons KQ4TR, 941-936-1431. E-Mail: csammons@juno.com

### JANUARY 10

**IN - SOUTH BEND** - Hamfest. The Century Center, US 33 N. at Jefferson Blvd. 8am-3pm. Talk-in: 145.290-. Michiana Valley Hamfest Assn., Bob Dennison KA9WNR, M-F 7-10pm EST. 219-291-0252

**FL - LANTANA** - Flea Market. Next to Pizza Hut, 6170 S. Congress Ave. 7am-12pm. Talk-in: 146.67. The Major Armstrong FM Assn., Jeff Beals WA4AW, 561-586-5120. Al West W4SDC, 561-641-8244

**MI - FLINT** - Hamfest. AR & Youth, Clay KF8UI, 810-233-7889. E-Mail: clay@iavbbs.com

**MO - ST. JOSEPH** - Hamfest. Ramada Inn, I-29 @ Frederick Ave. 8am-3pm. Talk-in: 146.85 and 444.925. Missouri Valley ARC & Ray Clay ARC, John Winkler WBOVRA, 816-424-6484. Gaylen Pearson, E-Mail: WBOW@IBM.Net

### JANUARY 13

**PA - PHILADELPHIA** - Auction. Phil-Mont Mobile RC, Russ Stafford W3CH, 610-631-3401 Ext 902. Web: http://www.phil-mont.org

### JANUARY 16

**CA - SANTEE** - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052

**LA - HAMMOND** - Hamfest. University Center, University Dr. Southeast Louisiana ARC, Jack

The Events Calendar is a free service for publicizing electronic events such as amateur radio hamfests, flea markets, etc. If your organization is sponsoring an event and would like a free listing, contact us at least 60 days in advance. Include your flyer, estimated attendance, name of the person to contact, and phone number.

Complimentary issues are available upon request for distribution to your attendees. A street address for UPS is required.

While we strive for accuracy in our calendar, we can not be responsible for errors or cancellations. The information contained in this column is for the use of the readers of *Nuts & Volts* and may not be republished in any form without the written permission of T & L Publications, Inc.

All listing information should be sent to:

**Nuts & Volts Magazine**

**Events Calendar**

430 Princland Court

Corona, CA 91719

Phone 909-371-8497

Fax 909-371-3052

E-mail [events@nutsvolts.com](mailto:events@nutsvolts.com)

## COMPUTER SHOWS

**AGI Shows**, 317-299-8827.

E-Mail: [info@agishows.com](mailto:info@agishows.com)  
http://www.agishows.com

**Blue Star Productions**

612-788-1901  
http://www.supercomputersale.com

**Computers And You**, 734-283-1754.

www.al-supercomputersales.com

**Computer Central Shows**

847-412-1900 & 1-888-296-6066.  
E-Mail: [compcent@meginet.net](mailto:compcent@meginet.net)  
www.computercentralshows.com

**Five Star Productions**

810-890-0988 E-Mail: [jeff@fivestar.com](mailto:jeff@fivestar.com)  
www.fivestars.com

**Georgia Mountain Productions**

706-838-4827.  
E-Mail: [gamtpro@blrg.tds.net](mailto:gamtpro@blrg.tds.net)  
[georgiamountain.com](http://georgiamountain.com)

Comm. RAs, Donald Motz N9NYX, 630-665-7757.

E-Mail: [donlin@xnet.com](mailto:donlin@xnet.com) http://www.w9ccu.org/  
Pat Byrne K9JAI, 630-545-9950.

E-Mail: [k9jau@juno.com](mailto:k9jau@juno.com)

**OH - DOVER** - Hamfest. Tusco ARC, Howard Blind KD8KF, 330-364-5258

### JANUARY 29-30

**MS - JACKSON** - Hamfest. Jackson ARC, Ron Brown AB5WF, 601-956-1448 or 601-982-0101.

E-Mail: [ab5wf@juno.com](mailto:ab5wf@juno.com)

Web: http://www.jxnarc.org

### JANUARY 30

**AL - GREENVILLE** - Hamfest. Butler & Pike County RACES, Jerry McCullough KE4ERO, 334-382-7644. E-Mail: [w4mpq@alaweb.com](mailto:w4mpq@alaweb.com)

**FL - ARCADIA** - Hamfest. DeSoto ARC, Doug Christ KN4YT, 941-494-5070 or 941-993-4834.

E-Mail: [kn4yt@cyberstreet.com](mailto:kn4yt@cyberstreet.com)

**Gibraltar Trade Center, Inc.**

734-287-2000. Taylor, MI.

**Gibraltar Trade Center, Inc.**

810-465-6440. Mt. Clemens, MI.

**MarketPro, Inc.**, 201-825-2229

http://www.marketpro.com

**MarketPro, Inc.**, 301-984-0880.

E-Mail: [md@marketpro.com](mailto:md@marketpro.com)

http://marketpro.com

**Narisaam Computer Show**

770-663-0983.

E-Mail: [narisaam@aol.com](mailto:narisaam@aol.com)

Web: http://www.shownsale.com

**Northern Computer Shows**

978-744-8440

E-Mail: [inquiries@ncshows.com](mailto:inquiries@ncshows.com)

Web: [ncshows.com](http://ncshows.com)

**Peter Trapp Computer Shows**, 603-

272-5008. Web: [www.petrtrapp.com](http://www.petrtrapp.com)

**MO - NEVADA** - Hamfest. Nevada ARC, Dennis

Kimrey. E-Mail: [dkimrey@ipa.net](mailto:dkimrey@ipa.net)

E-Mail: [k0cb@ipa.net](mailto:k0cb@ipa.net)

Web: http://www.users2.ipa.net/~dkimrey

**NM - ALBUQUERQUE** - Albuquerque Winter

Tailgate Swapfest, Tom Ellis K5TEE, 505-291-

8122. E-Mail: [k5tee@qsl.net](mailto:k5tee@qsl.net)

**NY - LOCKPORT** - Auction. Lockport ARA,

Albert Gritzmacher AE2T, 716-433-3396.

E-Mail: [lockportara@juno.com](mailto:lockportara@juno.com)

Web: <http://hamgate1.sunyerie.edu/~lara/auction.html>

### JANUARY 31

**CA - SANTA ANA** - Swapmeet. ACP parking lot.

Mary Russo 714-558-8813

**MD - ODENTON** - Hamfest. Maryland Mobileers

ARC, Bill Ziegler KA6TY, 410-987-2384. E-Mail:

[ka6ty@juno.com](mailto:ka6ty@juno.com). Bill Hampton N3WGM, 410-

766-2199. E-Mail: [diamondb@space4less.com](mailto:diamondb@space4less.com)

Web: <http://www.space4less.com/usr/mmrc>

**Professional 10 HOUR RECORDER** Factory Direct

"BUILT LIKE A BATTLESHIP"

- Heavy duty commercial recorder - NOT improvised from consumer models
- 12, 14, and 16 hour models also available
- BUILT-IN voice activation (add \$30)
- Applications information included
- Dimensions: 11.5 x 7.0 x 2.75"

**SPECIAL Nuts & Volts Price..**

**\$159**

FREE 40-PAGE SPECIAL EQUIPMENT CATALOG!

COD's OK. Sorry, no credit cards. Free catalog USA only; other countries \$5. Price includes UPS to 48 States on Pre-Paid Orders

**Viking International** 150 Executive Park Blvd. #4600 San Francisco, CA 94134  
Phone: (415) 488-2086 • Fax: (415) 488-2087 • Web: [www.vikingint.com](http://www.vikingint.com)

## Do You Repair Electronics?

For only \$7.95 a month, you'll receive a wealth of information:

Repair data for TV, VCR, monitor, audio, camcorder, & more

Over 100,000 constantly updated problem/solutions plus...

- TechsChat live chat room.
- Private user discussion forums.
- Automated email list server.
- UL/FCC number lookup.
- Hot tips bulletin board.
- Manufacturer information.

To access RepairWorld, direct your internet browser to <http://www.repairworld.com>

# RepairWorld.com

Electronix Corp. 1 Herald Sq. Fairborn, OH 45324 (937) 878-9878

# Events CALENDAR

## FEBRUARY 1999

### FEBRUARY 1

**AZ - PHOENIX** - Auction. St. Clement of Rome Catholic Church Social Hall, 15800 Del Webb Blvd. Talk-in: 147.30+ West Valley ARC, Ralph WODNO, 602-582-8208.  
E-Mail: w0dno@worldnet.att.net

### FEBRUARY 6

**AR - WEST MEMPHIS** - Hamfest. Eugene Woods Civic Center, 212 W. Polk. 9am-4pm. VE Exams. Talk-in: 147.150+ 444.775+. Dixie AR Group, Kellye Farris KB5RCE, 870-732-8724.  
E-Mail: kb5rce@media-two.com  
E-Mail: dixiefest@media-two.com  
Web: http://www.media-two.com/DARG

**CA - SANTEE** - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052

**IA - MONTOUR** - Hamfest. Jerry Morrison NOLEM, 515-484-6036. E-Mail: NOLEM@WOCXX-I.A.USA.NA E-Mail: lmonster@pcpartner.net

**KS - MOGND CITY** - Hamfest. Mine Creek ARC, Bill VanKirk W0PT, 913-795-2080.  
E-Mail: bvkirk@kanza.net

**SC - NORTH CHARLESTON** - Hamfest. Stall High School. 8:30am-4pm. VE Exams. Charleston ARS, Jenny Myers WA4NGV, 843-747-2324.  
E-Mail: brycemyers@aol.com  
E-Mail: wa4usn@amsat.org

### FEBRUARY 6-7

**FL - MIAMI** - Tropical Hambooree. Fair Expo Center, S.W. 112th Ave. & Coral Way. VE Exams. Talk-in: 146.925, 146.76, 444.525. Dade Radio Club of Miami, Evelyn Gauzens. 305-642-4139.  
E-Mail: edg@elink.net. 305-226-5346. E-Mail: wd4sf@bellsouth.net. Web: www.hambooree.org

### FEBRUARY 7

**OH - LORAIN** - Hamfest. Northern Ohio ARS, Mike Willemin W8EJ, 440-324-4574

**PA - LATROBE** - Hamfest. American Legion, 1811 Ligonier St. 8am-1pm. Talk-in: 145.150 (-600). Chestnut Ridge ARC, William Demosky K3AFS, 724-539-1552

### FEBRUARY 12-13-14

**FL - ORLANDO** - Hamfest. Northern FL Section Conv., Tim Starr AE4NJ, 407-850-9258.  
E-Mail: AE4NJ@aol.com  
Web: http://www.oarc.org/hamcat.html

### FEBRUARY 13

**CA - FONTANA** - Inland Empire ARC Amateur Radio & Electronics Swapmeet. A B Miller High School, Bill 909-822-4138 eves

**MA - MARLBOROUGH** - Hamfest. Marlborough Middle School, Rt. 85. 10am-2pm. Algonquin ARC, Ann Weldon KA1PON, 508-481-4988

**MI - NEGAUNEE** - Swap & Shop. Township Hall. Talk-in: 147.27. Hiawatha ARA, Bob Serfas NBPKN, 906-226-9782. John Veight N8RSE, 906-228-9417

**NY - WESTFIELD** - Hamfest. Westfield Exempt Volunteer Fireman's Assn., 75 Bourne St. 8am-3pm. Talk-in: 145.350 (-). Chautauqua County RAs, Eric Kroon N2PCQ, 716-595-3220.  
E-Mail: ekroon@netsync.net

**PA - OBERLIN** - Hamfest. Oberlin Fire Co., Fire Hall. VE Exams. Talk-in: 146.76. HRAC 717-939-4825. E-Mail: n3njb@juno.com

### FEBRUARY 14

**IL - ROCK ISLAND** - Hamfest. QCCA Expo Center, 2621 4th Ave. Talk-in: W0BXR 146.28/88 and 146.04/64. Davenport ARC, Kent Williams K9UQI, 309-796-0718, 4-9pm only. E-Mail: k9uqi@arc-support.com E-Mail: k9uqi@netexpress.net Web: http://www.arc-support.com/drac

**OH - MANSFIELD** - Mid\*Winter Hamfest & Computer Show. Richland County Fairgrounds. Talk-in: call W8WE on 146.34/94. InterCity ARC, Inc., Pat Ackerman N8YOB, 419-589-7133 after 2pm EST.

### FEBRUARY 20

**AR - RUSSELLVILLE** - Hamfest. AR River Valley AR Foundation, Margaret Alexander KC5MCS, 501-968-7270. E-Mail: ealexand@cswnet.com

**CA - SANTEE** - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052

**FL - BROOKSVILLE** - Hamfest. Spring Hill VFW Post 10209, Spring Hill Dr. between US 41 & Mariner Blvd. Talk-in: 146.715. Hernando County ARS, Ralph Wilson AF4FC, 352-754-9653. Jim Angello KE4SZP, 352-688-5214.

E-Mail: jangello@fiber-net.com  
Web: www.fiber-net.com/pub/hcara/index.htm

**MN - BLAINE** - Hamfest. Robbinsdale ARC, Jerry Dorf N0FWG, or Harriet Johanson 612-537-1722.  
E-Mail: jerryd@skypoint.com

**OR - RICKREALL** - Hamfest. Polk County Fairgrounds, 520 S. Pacific Hwy. W. Talk-in: 146.86. Salem Repeater Assn. and Oregon Coast Emergency Repeater, Evan Burroughs N7IFJ, 503-585-5924 before 8pm.  
E-Mail: n7ifj@teleport.com  
Web: http://sra.goldcom.com/sraflyer.htm

**TX - SMITHVILLE** - Hamfest. Bastrop County ARC, Lynn Fisk K5LYN, RR 2 Box 198B, Smithville, TX 78957-9551

### FEBRUARY 21

**MI - FARMINGTON HILLS** - Swap 'n Shop. William M. Costick Activities Center, 28600 Eleven Mile Rd. 8am-3pm. Talk-in: 145.350-repeater and 146.52 simplex. Livonia ARCs, 734-261-5486. E-Mail: swap@larc.mi.org  
Web: www.larc.mi.org

**NC - ELKIN** - Hamfest. Briarpatch & Foothills ARCs, Jimmy Holbrook KB4GKI, 336-957-3820.  
E-Mail: kb4gki@aol.com Web: http://members.aol.com/kb4gki/kb4gki.html

**NY - FREEPORT** - Hamfest. Armory, 63 Babylon TnPk. 8:30am-1pm. Talk-in: 146.850 (136.5 PL). LIMARC, 516-520-9311. E-Mail: hamfest@limarc.org Web: http://www.limarc.org

### FEBRUARY 27

**GA - DALTON** - Hamfest. Dalton ARC, James Jordan K4FLG, 706-278-0630 evenings

**KY - CAVE CITY** - Hamfest. Mammoth Cave ARC, 502-651-2363. E-Mail: lbrumett@glasgow-ky.com Web: http://www.scrct.blue.net/mcsrc

**ND - BISMARCK/MANDAN** - Hamfest. Central Dakota ARC, Dennis Murphy K0GRM, 701-258-6747. Web: http://www.gsl.net/cdarc


**VT - MILTON** - Hamfest and Convention. Milton High School, Rt. 7. 8am-3pm. Talk-in: 145.15. RAs of Northern VT, Mitch Stern W1SJ, 802-879-6589. E-Mail: w1sj@vbmail.champlain.edu  
Web: http://www.ranv.together.com

### FEBRUARY 27-28

**OH - CINCINNATI** - Convention. Cincinnati Gardens, Exhibition Center. Great Lakes Div.  
Continued on page 67

## IndustroLogic™

Fast, friendly project development!

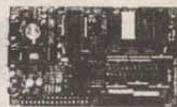

**SBC-1 80C51 Single Board Computer \$179**

Menu based monitor and BASIC in ROM. 50 I/O, A/D, RTC, serial, I/O rack interface, up&download to EEPROM. Includes software.



**SMD-12 Stored Message Display \$179**

Display & enter messages with switch closure or serial port. 12 messages of up 32 characters. 6"W x 3"H x 6"D Steel case.



**SIO-1000 RS-232 Data Acquisition Interface Board \$179**

8 TTL in, 8 TTL out, dual 12 bit A/D & D/A channels. counter in, frequency out, WINDOWS/DOS software, cable, case & supply. 4.25" x 6.5" x 1.5" high. 12 oz.

Industrologic, Inc.  
3201 Highgate Lane  
St. Charles, MO 63301

(314) 707-8818  
9AM-5PM Central

Full technical info on the Web!

www.industrologic.com

Write in 92 on Reader Service Card.

## MICRO VIDEO CAMERAS

**MB-750U & MB750P Video Cameras your Choice \$89.95**

- 1.25" sq.
- .1 LUX
- 420 TV Line

The Best, Smallest, Micro Cameras on the Market Today!  
Call and Compare! We Match or Beat All Prices!

## WIRELESS VIDEO CAMERAS

### NIGHT VISION

**Night Vision Scope w/ Illuminator**  
Fun to use, Low cost.  
3.6 x 85mm F1.6  
MI-PR100 - \$399.95

### GFT-1001

**GFT-1001 \$189.95**  
Gives any camera the ability to be Wireless.

### Compatible with AC or Battery

**GFR-1001 Receiver \$249.95**  
Transmits Over 1000 ft.

### FREE Product Catalogs

American Express, VISA, MasterCard

Wireless Observation System's  
GFS-1001 (900MHz) - \$499.95  
GFS-1001c (900MHz) - \$599.95  
(1.2 Ghz system available)

Wireless 4-Channel B/W & COLOR Cameras Available!  
Plug and Play Readiness

1-800-752-3571

Visit Polaris Ind. Web Site at:  
http://www.polarisusa.com

Polaris Industries 470 Armour Drive NE • Atlanta GA 30324 • Tech Info: 404-872-0722 • FAX 404-872-1038

## Panasonic Color Camera Sale

**MB-950c Panasonic Camera Sale \$99.95 was \$299.95**  
Sale Ends 12/31/98

**Micro Color MB-45cB: \$99.95**

- Wide Voltage Range, 5-14 Volts!
- Small Footprint!
- Self contained ultra small package design for various applications.
- MCM PCB design for minimizing the size and improve durability.

**Specifications: MB-45cB Color Camera**

Pick-up device	1/4" Interline transfer
Effective Pixels	512 (H) x 496 (V)
Scanning System	2:1 Interface
Frame per second	525 lines - 60 fields
Synchronization	30 frames
Video output	Internal
Horizontal Res.	VBS. 1vpp 75 Ohms
Min. Required Illumination	More than 330 lines
AGC	40 LUX @ F2.8
White Balance	On fixed
Operating Temperature	ATW fixed
Ambient conditions	32°F to 104°F
Lens	Indoors

Size: 1.25 x 1.25 sq. w/ Footprint

## AFFORDABLE LIPSTICK CAMERAS


These cameras are supplied with a PCM-1 Video/Power cable.  
The BNC connection is for standard video connection to a Monitor or VCR.

**LP-850i \$129.95**  
Length: 1.9" Diameter: .91"

**LP-850p \$139.95**  
Length: 1.37" Diameter: .87"

# STAMP APPLICATIONS

by Lon Glazner

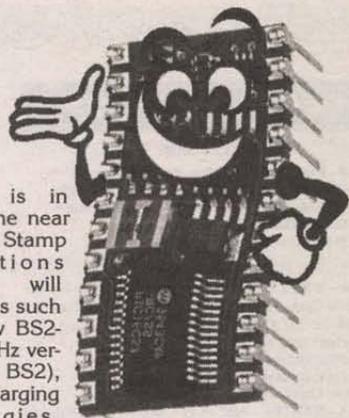

## Putting the Spotlight on BASIC Stamp Projects, Hints, and Tips

### Back To The Basics (Stamps, That Is!)

So here I am, sitting down at the computer, and asking myself, "What do people want to know about BASIC Stamps?" More importantly, "What do I have to share?"

At Solutions Cubed, we handle all aspects of embedded control design. In other words, I've got technical experience. But technical know-how does not a good article make.

Like most engineers, I spend an inordinate amount of time perusing dry engineering manuals. While informative, I think most of us can agree that data sheets are a far cry from good literature. I think the real power in BASIC Stamps is derived from the way they allow us to interact with technology. This interaction is what I hope to explore.

The first time I completed serial communication between a microcontroller and a computer, I felt like I had cracked some secret code. Yeah, so the secret code was well-documented and everyone else already knew it, I felt a sense of accomplishment anyway. I still find myself thinking "This is pretty cool!" when I see MY data splashing across a computer screen.

BASIC Stamps can be many things to many people. To the inexperienced, they allow a successful foray into the world of embedded control.

To the experienced engineer, they are a powerful tool in an ever-expanding tool box.

It is my hope that experienced BASIC Stamp users will find good technical information in my upcoming columns. It is my desire that a number of beginners will experience the sense of accomplishment that understanding technology has brought to me.

Why does the Stamp Applications column exist? Probably because BASIC Stamps are being used by students, teachers, hobbyists, and engineers worldwide. In an educational setting, they can provide months of discussion and learning. To a hobbyist, they may represent a home-lighting solution, or a tachometer for the hot-rod in the garage. As an engineer, I often use them to test various aspects of my electronic designs.

The BASIC Stamp is a powerful and ubiquitous design tool. They're also inexpensive, well-documented, and Parallax provides excellent technical support.

Designing with BASIC Stamps can be described as 50% software and 50% hardware. At times, it will seem like there is an additional 50% that revolves around figuring which part just evaporated in a cloud of smoke, and why.

Certain design techniques help to reduce guesswork and allow the designer to foresee potential problems. These techniques will be the meat and potatoes of my future articles.

What is in store for the near future? My Stamp Applications columns will cover topics such as the new BS2-SX (a 50MHz version of the BS2), battery charging technologies, implementation of user interfaces, and data logging. We'll also get into testing techniques for BASIC Stamp based systems.

I'm looking forward to writing this column and hope that you will find something worthwhile in the pages to come. See you next month! NV

Lon Glazner is a partner and engineer at Solutions Cubed. Solutions Cubed is an innovative group of design engineers who specialize in embedded control design. They also produce a line of BASIC Stamp compatible products called Miniature Engineering Modules.

#### CONTACT:

Lon Glazner — Partner  
Solutions Cubed  
3029 Esplanade Suite F  
Chico, CA 95973  
E-Mail: lon@solutions-cubed.com  
Phone: 530-891-8045  
Fax: 530-891-1643

## INTERNET SECURITY CELLPHONE/CORDLESS GUIDE STOPPING POWER METERS MANY MORE TITLES!

The latest tricks and methods hackers use on the Net to pirate software (warez), and hack websites. Includes examples, countermeasures, password defeats, Packet-Switched Networks, UNIX, Sprintnet, X.25, anonymous FTP, brute force techs, lots of tips. *More!* \$29. EWC=29.4K

**INTERNET TRACKING & TRACING:** Scammers, spammers, stalkers, infectors, and others hide behind the Internet's anonymity to commit serious offenses. Learn from master hackers best methods to track, trace IDs and origins, and to protect your own privacy. *More!* \$29. EWC=17.0K

**INTERNET FRAUDS DATABASE:** Internet cons, scams and related frauds now rake in \$2+ Billion annually! Most are done anonymously with impunity. Details how they're done, how to ID them, how to protect yourself. *More!* \$25. EWC=18.9K

**THE COOKIE TERMINATOR:** Many websites track your every move! Browser cookie, history and cache files contain personal data readily accessible to Internet predators, scammers, spammers and snoops. Your financial, medical, political, habits, lifestyle, future plans data is exposed to the world! Step-by-step how to remove and stop cookies from destroying your privacy. \$25. EWC=8.4K  
Any 2 for \$49, 3 for \$64, all 4 for \$79!

**PBX SECURITY**  
PBXs hacking losses of \$5-\$10 Billion/yr! Detailed vulnerabilities (especially for out-dial), countermeasures. Exclusive author interview in Forbes! \$24. EWC=17.4K

**ATM SECURITY**  
100+ ATM crimes, abuses, vulnerabilities, defeats exposed - TEMPEST, mag stripes, false fronts, supercool. *More!* Case histories, labeled internal photos, figures. \$39. EWC=41.0K

**TOP SECRET**  
Full Web Catalog: [www.tsc-global.com](http://www.tsc-global.com) Special Projects: .../spaf-spp.html

**CONSUMERTRONICS** CATALOG \$1 WITH ORDER, \$3 W/O  
2430 Juan Tabo, NE, #259, ABQ, NM 87112  
P.O. Box 23097 ABQ, NM 87192  
Fax: 505-292-4078 (all hours orders only) Voice: 505-237-2073 (9-7 M-S)

Established in 1971 by John Williams, MSEE, former DOD weapons engineer and NIH physicist. Featured on CBS "60 Minutes", Forbes, New York Times. Add \$5 total S/H (US, Canada). Postal MO is fastest! VISA, MC OK. No CODs. 10% OFF All Orders over \$100; \$2.00 OFF All New Orders over \$20 placed by Mail or Fax. EWC=Estimated Word Count Sold for legal educational purposes only. Some publications are controversial! We take no responsibility for anything we publish. See Catalog for LIMITED WARRANTY, SPECIAL PROJECTS and all other applicable policies.

How cellphones operate; mods. Vulnerabilities to hack attack; countermeasures. Cloning details for NAMs, ESNs, etc, control data formats, computing encoded MINs, ESNs, SIDHs, Op Sys, PROMs, forcing ACK, test mode and resets, cable diagrams, scanning, tracking, scanner restorations, freq allocations, roaming, step-by-step to keypad-reprogram 100+ popular cellphones. One FREE database search. Plus much on Cordless phones. *More!* \$49. EWC=80.2K

**PAGER (BEEPER) MANUAL:** How Pagers work, different types and uses, freqs, advantages over and uses with cellphones, and tips and tricks. How phreaks hack Pagers; countermeasures. Plus plans for a Personal Pocket Paging System (xmitter and receiver). *More!* \$29. EWC=11.4K  
Both for only \$69!

**CALLER ID & ANI SECURITY**  
How they work and the many vulnerabilities of Caller ID, ANI, \*69, \*57, Call Blocking, \*67, et al. Describes ESS, SS7, CNA, CAMA, DNR, Diverters, Centrex! \$25. EWC=15.2K

**FAX MACHINE SECURITY**  
All known methods used to hack faxes and countermeasures. Includes computer fax modems, crimes, interceptions, fax servers, fax-on-demand, protocols, parameters, compression, encryption, and fax surveillance-type mods. *More!* \$29. EWC=28.7K

**VOICE MAIL SECURITY**  
VMSs are hacked to penetrate PBXs to make outgoing calls, get free VMB usage, secretly read/change/delete messages, control or damage the VMS (or its PBX) itself. Details how hackers do it, countermeasures. A must for users, sysops, security personnel! \$29. EWC=14.2K

**COMPUTER SECURITY**  
Describes in detail how computers penetrate each other, and how VIRUSES, TROJAN HORSES, WORMS are implemented. Dozens of computer crime and abuse methods and countermeasures. Includes disk filled with hacker text files and utilities, and the legendary FLUSHOT+ protection system. Internet advice, password defeats, glossary - much more! Manual + PC Disk! \$39. EWC=54.7K

**BEYOND VAN ECK**  
Plans for remote eavesdropping of TV video signals. Range up to 1 KM. Describes how van Eck systems work, and are also used in surveillance of computer systems. \$29. EWC=10.6K. Van Eck Demo Tape is \$29. (15 min). Both for only \$49!

**As reported on "60 MINUTES"!** 6th Edition! Details devices that can slow down (even stop) power meters while loads draw full power - great science projects! Devices plug into one outlet and normal loads into other outlets. Describes meter creep, overload droop, pole meters, etc. \$29. EWC=10.4K

**SPM THE VIDEO:** Now its easier to learn about KW-HR Power Meters than ever before! This educational video shows you how they work and their anatomy. Demonstrates SPMEM device and external magnetic methods used to slow and stop meters! Hosted by a top expert in the field. From the novice to the pro, an excellent source of info on these exciting devices! Great in combo with our SPM-related manuals! \$29. (20 min)

**THE I.G. MANUAL:** Details external magnetic ways (applied to meters) outlaws use to slow down and stop power meters while drawing full loads. \$25. EWC=4.9K

**KW-HR METERS:** How watt-hour energy meters work, calibration, error modes (many), ANSI Standards, etc. Demand and Polyphase Meters. Experimental results to slow, stop power meters by others. \$25. EWC=24.2K  
Any 2 for \$49, 3 for \$64, all 4 for \$79!

**COMPUTER SECURITY**  
Describes in detail how computers penetrate each other, and how VIRUSES, TROJAN HORSES, WORMS are implemented. Dozens of computer crime and abuse methods and countermeasures. Includes disk filled with hacker text files and utilities, and the legendary FLUSHOT+ protection system. Internet advice, password defeats, glossary - much more! Manual + PC Disk! \$39. EWC=54.7K

**THE HACKER FILES:** Expose 3 HD PC disks filled with choice raw, colorful, highly informative hacker, phreaker text files covering many topics! \$39. Both for only \$69!

**BEYOND VAN ECK**  
Plans for remote eavesdropping of TV video signals. Range up to 1 KM. Describes how van Eck systems work, and are also used in surveillance of computer systems. \$29. EWC=10.6K. Van Eck Demo Tape is \$29. (15 min). Both for only \$49!

**THE DIRTY-2 DOZEN!**  
24+ Hot Hack Phreak Expose Disks!  
See CATALOG!  
SPECIAL PROJECTS  
We will design & build just about anything electronic!  
Hardware done as SPECIAL PROJECTS.  
See Catalog for details and SP Application Form, else:  
[www.tsc-global.com/spaf-spp.html](http://www.tsc-global.com/spaf-spp.html)

# Newsbytes

## Announcing the Steganos Contest — Keep Your Secrets a Secret and Win!

Washington, DC - CenturionSoft announced a contest to promote their new security utility Steganos. Steganos — for Windows, 95, 98 and NT — is a utility that not only provides a high 2048 bit level of encryption but also allows the user to hide their encrypted data in normal looking image, sound, and text files.

Why both hiding and encrypting? When only encryption methods are used, data may be unreadable, but it is obvious that there is sensitive data — that there is a secret. By combining two powerful ways to protect data: **Cryptography** — to make data unreadable to anyone who does not know the password — and **Steganography** — which hides the existence of data, files being hidden and encrypted by Steganos can be neither read nor detected easily.

To enter the Steganos contest one needs only to go to the CenturionSoft website — <http://www.centurionsoft.com> — and follow the instructions for downloading both the free 30-day evaluation copy of Steganos and the contest image. The contest image contains a secret message on how to enter the contest which can be unhidden and decrypted using Steganos.

Prizes will be awarded weekly beginning December 15th, 1998. The grand prize will be awarded on March 31st, 1999. Prizes include a round-trip ticket to Europe, a color TV, and free copies of Steganos. For complete terms and conditions, please see the CenturionSoft website.

Steganos' benefits include:

\* *Protect your sensitive E-Mail.* Sending E-Mail is like sending a postcard, it is easily accessible by many people before it reaches the recipient. Sending sensitive information both encrypted and hidden in normal looking attachments ensures that your sensitive information won't be seen by anyone else, and you can send these attachments directly from Steganos! Recipients can use the free Steganos Decryptor to unhide and decrypt the information if they don't own Steganos.

\* *Protect sensitive information on your laptop.* Laptops can and do get stolen. While the cost of your laptop is probably insured, what about your sensitive information? What is the cost if sensitive company data gets into the hands of your competitors? Steganos can be used to protect this invaluable data.

\* *Protect sensitive information on your desktop.* Networks and the Internet allow you to access information easily and quickly, but they also make your desktop vulnerable to unwanted prying eyes. Passwords can be broken. Steganos ensures that the sensitive data on your desktop remains confidential.

Steganos, which began shipping on September 30th, 1998, has an estimated street price of \$39.95.

Centurionsoft — a Washington, DC based software company — specializes in Windows utilities for productivity and security.

### Centurionsoft

2000 P Street NW Suite 305

Washington, DC 20036

[WWW.CENTURIONSOF.COM](http://WWW.CENTURIONSOF.COM)

## Look Ma, No BASIC Stamp\*

### PicBasic Compiler - \$99.95

Put BASIC Stamp I programs right into a PIC microcontroller - no BS1 module necessary! The programs run faster and can be longer. You also get more variables and extra instructions. For mid-range PIC12C67x, 16C55x, 6xx, 7xx, 8x, 9xx.

### PicBasic Pro Compiler - \$249.95

PicBasic Pro is BASIC Stamp II compatible, and like the standard compiler above, eliminates the need for a BS2 module. Pro adds built-in LCD support, interrupts in BASIC, arrays, program size to 8K, real if..Then..Else and I/O to any PIC pin. For mid-range PIC12C67x, 16C55x, 6xx, 7xx, 8x, 9xx.

\*BASIC Stamp is a trademark of Parallax Inc.

### EPIC Plus PIC Programmer - \$59.95



Programs PIC12C50x, 67x, 16C55x, 6xx, 7xx, 8x, 9xx. Optional ZIF adapters for DIP, SOIC, MQFP, PLCC. Runs off two 9-volt batts or optional AC adapter. Includes programming software and assembler.

### PICProto Prototyping Boards

Get it wired quicker! High-quality blank prototyping boards for PICmicros. Holds 5V reg, caps, osc, DB9-25, large proto area. \$8.95 - \$17.95



### microEngineering Labs, Inc.

Box 7532 Colorado Springs CO 80933  
(719) 520-5323 (719) 520-1867 fax

<http://www.melabs.com>

email: [info@melabs.com](mailto:info@melabs.com)

Write in 218 on Reader Service Card.

## Miniature Transmitters and Receivers

### 2 Button / 3 Channel Transmitter



#### RF300T

1....\$22.95  
5....\$19.95 ea  
10...\$16.95 ea

#### RF300XT

1....\$25.95  
5....\$22.95 ea  
10...\$19.95 ea

- 300' (XT), 150' (T) Range
- Frequency: 318 MHz
- 59,049 Settable Security Codes
- 12 Volt Battery and Keychain Included
- Current Draw: 4.8 ma
- Fully Assembled in Case
- Dimensions: 1.25" x 2.0" x .5"
- Push both buttons for the 3rd Channel
- Slide Button Cover Included

### 4 Button / 15 Channel Transmitter



#### RF304XT

1....\$27.95  
5....\$24.95 ea  
10...\$21.95 ea

- 250' Range
- Frequency: 318 MHz
- 6,561 Settable Security Codes
- 12 Volt Battery and Keychain Included
- Current Draw: 4.6 ma
- Fully Assembled in Case
- Dimensions: 1.35" x 2.25" x .5"
- Push combination of buttons to achieve up to 15 channels

### 2-4 Data / 3-15 Channel Receivers



#### RF300RL RF300RM

1....\$27.95  
5....\$24.95 ea  
10...\$22.95 ea

#### RF304RL RF304RM

1....\$29.95  
5....\$26.95 ea  
10...\$23.95 ea

- Compatible with 300/4 Transmitters
- 11-24 volts DC Operating Voltage
- 13 ma. Current Draw
- Latching (L) or Momentary (M) Output
- Kits Available (subtract \$5.00 ea.)
- Dimensions: 1.25" x 3.75" x .5"
- 2 (300) / 4 (304) Output Data Lines
- Binary to Dec / Hex Converter can achieve up to 15 channels

- Alarm Systems
- Garage / Gate Openers
- Lighting Control

- Magic Props
- Medical Alert
- Monitoring Systems

- Industrial Controls
- Surveillance Control
- Motor Control

- Schematics Available
- Receiver Board Layout Available
- Custom Design Consulting Available

Visitect Inc.

(510) 651-1425 Fax: (510) 651-8454  
P.O. Box 14156, Fremont, CA 94539

Email: [Support@Visitect.Com](mailto:Support@Visitect.Com)  
Visa / Mastercard, COD

Write in 217 on Reader Service Card.

ELECTRONIC COMPONENTS



Visit our web site!  
[www.mouser.com](http://www.mouser.com)

Subscribe, download, or  
view catalog online!

- Over 78,000 Products
- More than 145 Suppliers
- Same Day Shipping
- No Minimum Order

800-992-9943

817-483-6828 Fax: 817-483-6899  
[catalog@mouser.com](mailto:catalog@mouser.com)

**MOUSER**  
ELECTRONICS

958 North Main St., Mansfield, TX 76063

Write in 218 on Reader Service Card. 29

**T**raditionally, digital panel meters have been sort of a premium item. They're accurate and easy to read, but they tend to be fairly expensive, with prices starting at about \$40.00 in single quantities. Recently, a series of parts imported from China has changed that situation dramatically. You can now buy a single 3-1/2 digit job with LCD display for under

well. The display is reasonably sized and, though not backlit, very readable in typical room lighting or outdoors. The accuracy and stability are plenty adequate for most applications; certainly better than even fairly expensive analog meters. So, what's the catch?

### The Problem

To help clarify the problem,

of 0V to + or -200mV whose common or ground is the same as the power supply ground. However, the chip was primarily intended for handheld, battery-operated multi-meters. It internally generates a 'common' level that's about 2.8V below the positive supply voltage. For battery operation, the signal common line is tied to this internal common, as shown in Figure 2. That's what the designers of these panel meters have done.

by John Sharp

source, it works fine. If you use the meter wholly within an instrument or device, though, you'll usually be measuring signals in the same circuit that powers the meter.

Most often, the voltages you want to measure will be referenced to ground. But if you feed the meter with, say, +10V on the positive supply input and circuit ground on the negative, the signal input common will need to be at about +7.2V. That's why the vendors have started putting notes in their ads like "Cannot measure own power source" or "meter power must be isolated."

What can you do about this? One solution might be to modify the meter so that you can use the circuit in Figure 1. In practice, this means ripping the thing apart and doing a whole bunch of trace cutting and jumpering. If that's not enough to stop you, consider that disassembling the plastic housing from the circuit board pops the LCD display module loose; those of you who have tried to reinstall an LCD with conductive elastomeric connectors after they've picked up some dust or skin oils need no further warning.

Fortunately, there's a couple of other fairly simple solutions. You can power the meter with a ground referenced supply and then shift the signal voltage to where the meter wants it; or you can power the meter from an isolated supply so that it doesn't care where the signal is.

### Circuit #1: Level shifter

Figure 3 shows a circuit that allows the panel meter to measure a voltage in relation to its own supply ground. The opamp is configured as a differential amplifier with a gain of 0.01 (1/100), which scales a 20V signal referenced to circuit ground down to a 200mV signal referenced to the meter's common input. Note that even though the meter and opamp are both powered from +7 to +12 volts, the measured voltage can be ±20V.

Differential amplifiers (and their kin — instrumentation amplifiers) are often used to pick up a relatively small signal that's 'riding' on a higher voltage that may be fluctuating or noisy. The idea is to amplify the signal between the inputs without

# More Ways To Use Low-Cost Digital Meters

\$10.00! That's cheaper than all but the very crudest analog movements.

There's not much clue as to

let's first look at how these meters work. They're based on a clone of the classic Intersil ICL7106 integrated circuit, which is a complete

So, if you run the panel meter from an isolated source like a battery, and measure a voltage that has no connection to the power

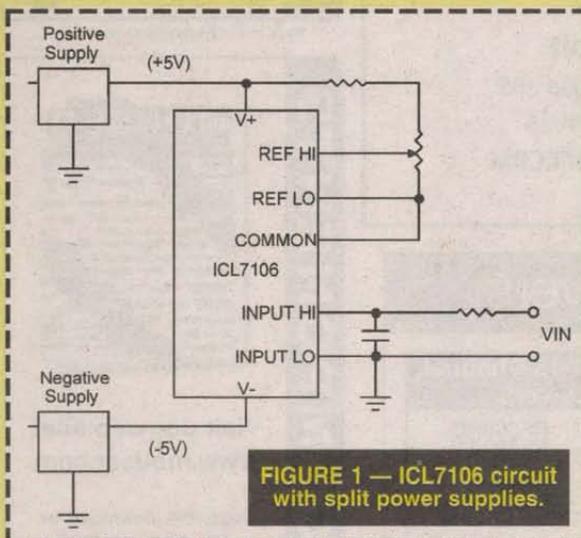


FIGURE 1 — ICL7106 circuit with split power supplies.

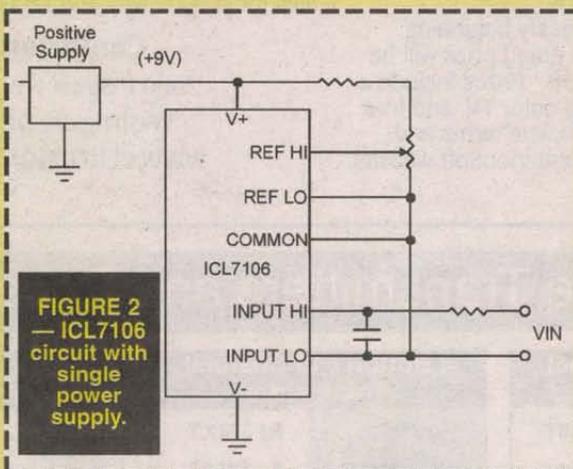


FIGURE 2 — ICL7106 circuit with single power supply.

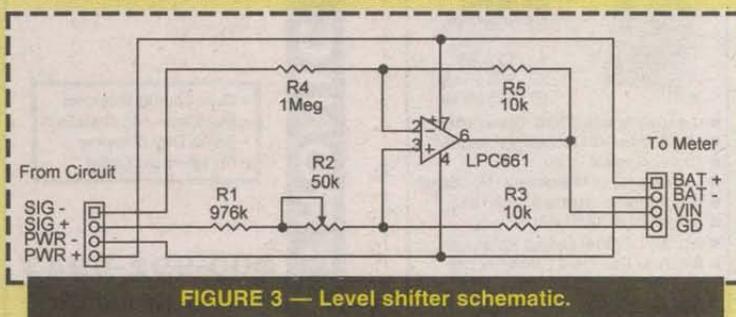


FIGURE 3 — Level shifter schematic.

who actually built these meters; the packaging is simply marked "C & C Digital Panel Meter," with a part number PM-128. Nonetheless, they work pretty

analog-to-digital converter with LCD display drivers. When fed with 'split' positive and negative power supplies as shown in Figure 1, it will measure a signal

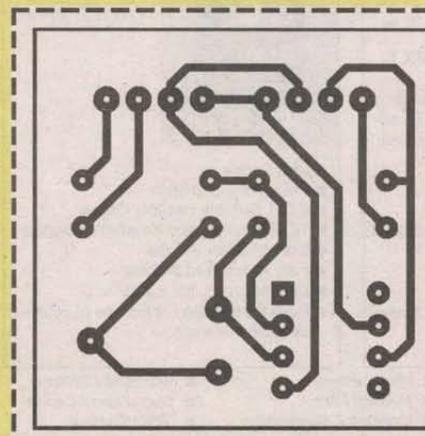


FIGURE 4 — Level shifter PC artwork.

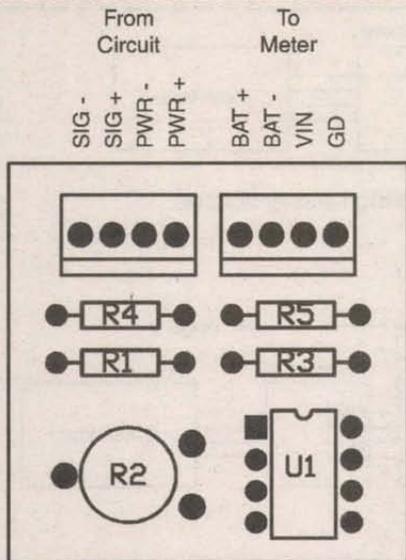


FIGURE 5 — Component layout for level shifter board.

amplifying the voltage to ground that's common to both inputs. They have a reputation as a 'high performance' type of circuit, requiring parts with tight tolerances and low drift and usually still needing careful tweaking.

The application here is a lot less demanding for two reasons. One is that instead of amplifying a small signal, we're attenuating a larger one. The second reason is that while the signal is offset from the meter input level, that offset changes very little.

So, this scheme will work fine for fairly large voltage ranges (2V or more) that have a fixed reference, like circuit ground.

## MATERIAL SUPPLIERS

### Module Parts

**Digi-Key**  
P.O. Box 677  
Thief River Falls, MN 56701  
1-800-344-4539  
(218) 681-3380 Fax  
[www.digikey.com](http://www.digikey.com)

**Mouser Electronics**  
958 North Main St.  
Mansfield, TX 76063-4827  
1-800-346-6873  
(817) 483-0931 Fax  
[www.mouser.com](http://www.mouser.com)

### Panel Meters

**All Electronics**  
P.O. Box 567  
Van Nuys, CA 91408-0567  
1-800-826-5432  
(818) 781-2653 Fax  
[www.allcorp.com](http://www.allcorp.com)

**Circuit Specialists**  
P.O. Box 3047  
Scottsdale, AZ 85271-3047  
1-800-528-1417  
(602) 464-5824 Fax  
[www.cir.com](http://www.cir.com)

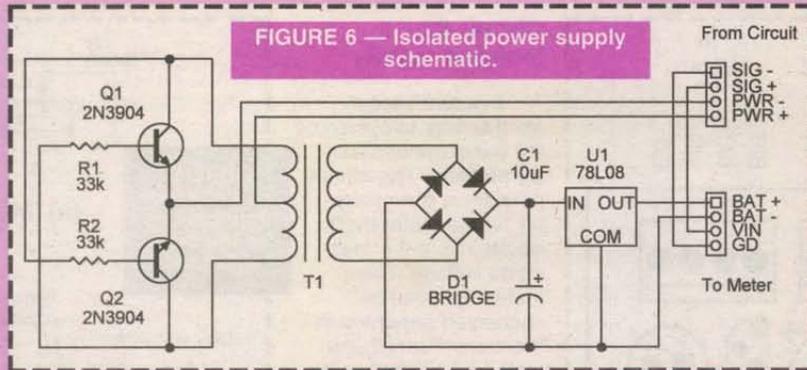


FIGURE 6 — Isolated power supply schematic.

Examples would be monitoring the battery voltage in a portable instrument, or tracking the output voltage of a variable power supply (see sample connections in Figure 9). It won't work well at all for small voltages whose reference changes. For

example, to measure the current of your variable supply, you'd put a shunt resistor on the output, as in Figure 9(c). The voltage across the shunt will only be a couple of hundred millivolts at most, but the voltage from the shunt to ground will vary from zero to 10s of volts. For this kind of measurement, check out the 'isolated supply' trick later in this article.

The LPC661 opamp works well in this circuit for several reasons. One is that it will operate with very low supply voltage, so we can feed it from the meter's power supply. It also draws very little supply current, so this circuit is great for battery-operated equipment. Finally, this opamp's

inputs take extremely low current, so we can use high value resistors to avoid loading the circuit we're measuring.


Use 1% resistors for R1, R3, R4, and R5. A single turn trimmer is fine for R2. The values shown are for a 20V full scale input range; you can scale that up to 200V by making R3 and R5 1 Kohm resistors, or down to 2V by using 100K parts.

Figure 4 is the artwork for a single-sided printed circuit board. It's reproduced at twice normal size so you can copy or scan with better resolution; reduce it 50% when printing to toner-transfer material or to a transparency for photoresist processes. To check on the accuracy of your copier, printer, or scanner, the board outline is 1.25" square. Note that the pattern appears as if you are looking down through the PC board from the com-

ponent (top) side; the final copper pattern, seen looking at the bottom of the board, will be a mirror image of this. This image orientation is required for the toner-transfer process (i.e., you can't get it backwards).

If you use a photoresist,


FIGURE 7 — Printed circuit artwork for isolated supply board.

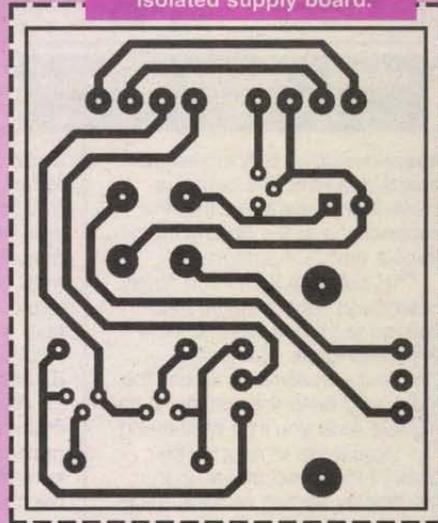

## MORE POWER!

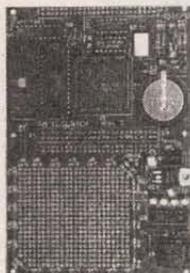
### 68HC11, 80C51 & 80C166

AM Research supports over 30 of the most popular Embedded controllers with both *hardware* and *software*.



- ✓ More Microcontrollers
- ✓ Faster Hardware.
- ✓ Faster Software.
- ✓ More Productive.
- ✓ More Tools & Utilities.
- ✓ IIC Peripherals.
- ✓ Single Chip Capable.
- ✓ Outstanding Support.
- ✓ Custom designs.

Call or email for a free full line brochure

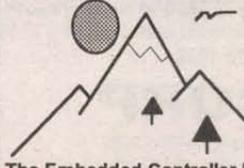
 Orders (800) 949-8051  
 Info (916) 652-7472  
 fax (916) 652-6642  
[www.amresearch.com](http://www.amresearch.com)  
**AM Research, Inc.**  
 PO Box 43  
 Loomis, CA 95650  
**The Embedded Controller Experts**

## PIC'n Books

### LEARN ABOUT PIC MICROCONTROLLERS

#### EASY PIC'n - Beginner \$29.95

- Programming techniques
- Instruction set, addressing modes, bit manipulation, subroutines, loops, lookup tables, interrupts
- Using a text editor, using an assembler, using MPLAB
- Timing and counting (timer 0), interfacing, I/O conversion

#### PIC'n Up The Pace - Intermediate \$34.95

- Serial communication - PIC to peripheral chips and PIC-to-PIC
- Serial EEPROMS
- LCD interface and scanning keypads
- D/A and A/D conversion - several methods
- Math routines

#### PIC'n Techniques - Intermediate \$34.95

- 8-pin PICs
- Timer 1, timer 2 and the capture/compare/PWM (CCP) module
- Talking to a PIC with a PC using a terminal program
- Test equipment and data logger experiments


See Table Of Contents: <http://www.sq-1.com>

+ \$4 s/h in US for 1 book, \$5 for 2 books, \$6 for 3 books  
 VISA, MC, AMEX, MO, Check

CA residents please add 7.25% CA sales tax  
 PIC and MPLAB are trademarks of Microchip Technology Inc.

### SQUARE 1 ELECTRONICS

P.O. Box 501, Kelseyville, CA 95451  
 Voice (707) 279-8881 FAX (707) 279-8883  
<http://www.sq-1.com>  
 E-Mail [sqone@pacfic.net](mailto:sqone@pacfic.net)

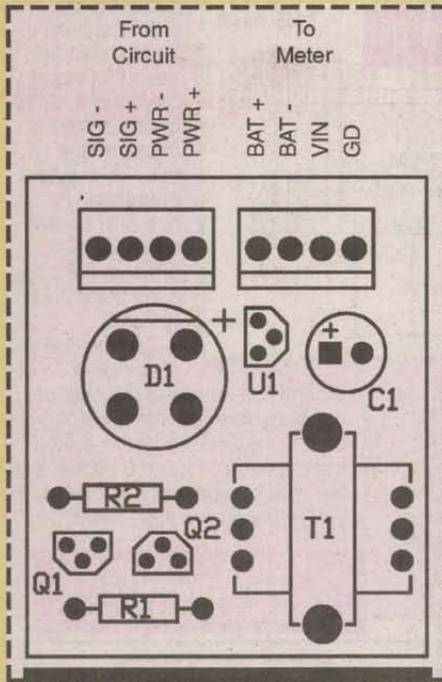

**FIGURE 8 — Isolated power supply component layout.**

board design or building on perf-board, just keep the resistors close to the opamp so that the connections to the opamp inputs (pins 2 and 3) are short.

To calibrate the circuit, apply power and set the signal input voltage to zero. Adjust R2 until the panel meter reads zero. Connect a multimeter across the input, and raise the voltage to the highest level you'll be measuring.


Adjust the trimpot on the back of the panel meter so that the display agrees with the multimeter.

### Circuit #2: Isolated supply

Figure 6 shows another way to overcome the panel meter's supply problem. This circuit provides a power supply for the meter that's isolated from the measured voltage. The meter input can be connected anywhere in the 'parent' circuit; the meter will behave as if powered by its own battery. This is especially useful when you're switching the meter input to various parts of the circuit, for example using the same panel meter to display both voltage and current.


The circuit is a simple DC-to-DC converter. The transistors form a multivibrator that creates a squarewave of several hundred Hertz, which passes through an inexpensive audio frequency coupling transformer to a rectifier and filter. This is followed by a low power voltage regulator IC that keeps the output constant and removes most of the remaining noise and ripple. The circuit as shown will take a power input from 7 to 12 volts and put out a clean, isolated 8 volts for the meter.

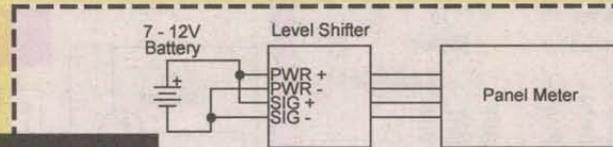We can get away with this crude approach because the meter needs only very modest current, less than 1 mA. You can buy ready-made DC-DC converters that are smaller, more effi-




(a) Monitoring battery voltage

**FIGURE 9 — Examples of applications for the meter modules.**

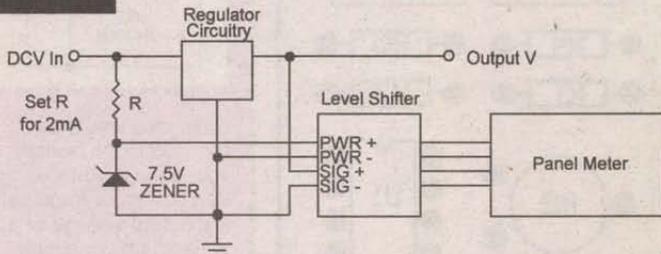

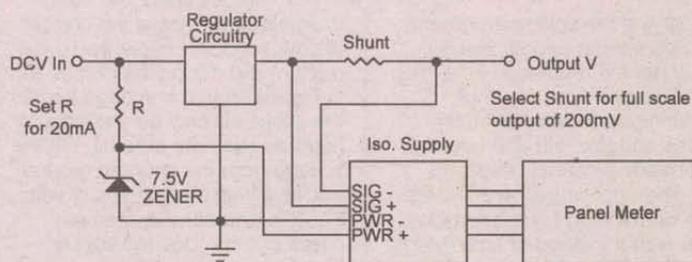(b) Measuring output voltage of variable power supply



(c) Measuring output current of variable power supply

cient, and handle more power. Unfortunately, their cost starts at around \$10.00 each. The parts for this circuit should run less than a third of that.

T1 is simply the cheapest


600-ohm coupling transformer I could find. Most anything similar you can dig up should function. C1 should be a tantalum electrolytic since they work a little better at high frequencies than the aluminum capacitors. If you have two meters to run, a dual secondary (600:600/600) transformer with a bridge, capacitor, and regulator on each output will keep them both isolated.

Figure 7 is the printed circuit board artwork. As for the level shift circuit, it's reproduced at twice normal size. The actual board outline is 1.25" by 1.5". Figure 8 shows the top side component placement. Layout isn't critical in this circuit. The location and wiring of the input and output connectors is identical to the level shift board.

When you first power up the module, double check the output voltage under load to make sure it's at approximately 8 volts. Note that the circuit simply passes the measured signal through the board. If you are using the meter's 200mV range, no further calibration is necessary (assuming the panel meter was correctly adjusted at the factory).

If you need a higher range (2V, 20V, or 200V), follow the instructions packed with the meter to create a simple resistive divider on the meter board. Set
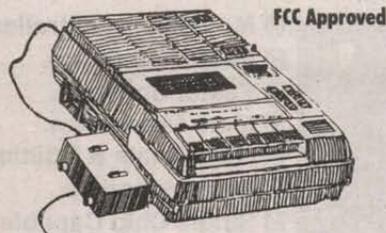
## TELEPHONE LISTENING DEVICE WITH 12 HR. RECORDER



Record telephone conversations in your office or home. Starts automatically when phone is answered, records both sides of phone conversation. Recorder stops when phone is hung up. \$99.95 + \$7 shipping. For telephone listening device separately \$19.95 + \$2 ship.

For comprehensive 50 page catalog of Micro Video, VHF transmitters, Surveillance, and Counter-surveillance and much more! Send \$3.00


Call 407-725-1000

### USI CORP

P.O. Box N2052 Melbourne, FL 32902  
COD'S OK
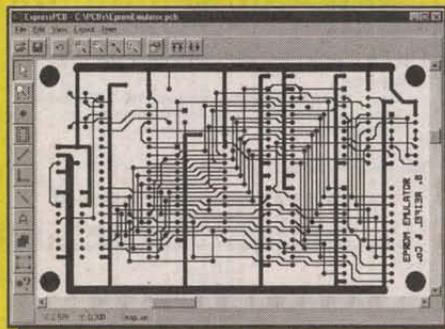
## PCB LAYOUT Software For Win95 - FREE

- 1 Download our board layout software
- 2 Design your 2 sided plated-through PCB
- 3 Send us your layout over the Internet
- 4 In 2-3 business days, UPS delivers your boards, often under \$100



[www.expresspcb.com](http://www.expresspcb.com)

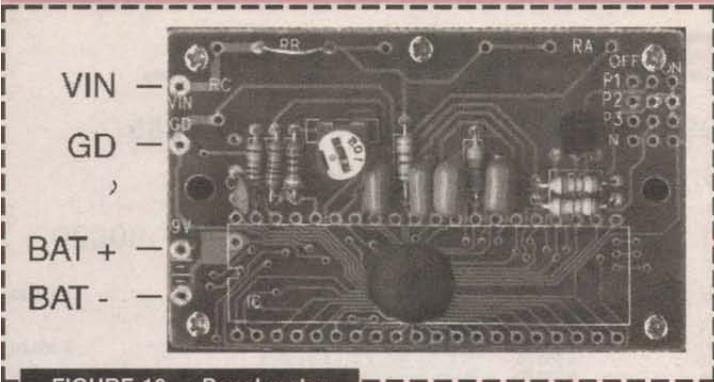


FIGURE 10 — Panel meter connections.

the voltage to be measured near its maximum level and monitor it with a multimeter. Adjust the trim-pot on the back of the panel meter so that the display agrees with the multimeter. The panel meter doesn't require any calibration for the zero input condition.

### Conclusion

As you can probably tell from

the tone of this article, I tend to like things that are cheap and simple, but do the job, and that pretty well describes these imported panel meters. I hope the ideas shown here will help you use them in your own projects.

Perhaps on your next one, you can skip scrounging around the surplus bins for an electro-mechanical antique and design in a nifty digital readout instead!  
**NV**

## Parts List for Panel Meter Modules

### Level Shift Circuit

- R1 - 976 Kohm, 1/4 watt, 1% tol.
- R2 - 50 Kohm, horizontal trimpot (most 8mm open-frame trimmers fit)
- R3,R5 - 10 Kohm, 1/4 watt, 1% tol. (for 20V full scale input; use 1 Kohm for 200V, 100 Kohm for 2V)
- R4 - 1 Megohm, 1/4 watt, 1% tol.
- U1 - National Semiconductor LPC661 opamp IC, DIP pkg. (Digi-Key P/N LPC661IN-ND)

### Isolated Supply Circuit

- C1 - 10uF, 25V, tantalum electrolytic, radial lead
- D1 - 1.5 Amp, 50V or higher, bridge rectifier
- Q1,Q2 - 2N3904 transistor, TO-92 plastic case
- R1,R2 - 33 Kohm, 1/4 watt, 5% tol.
- T1 - 600:600 ohm audio transformer (Mouser P/N 42TL016)
- U1 - LM78L08 type 8V regulator IC (Mouser P/N 513-NJM78L08A)

Connectors (optional) - Both boards are laid out for Waldom/Molex KK-100 series four-pin connectors, available from Mouser or Digi-Key:  
 Header (goes on PC board) - Molex P/N 22-23-2041  
 Housing (goes on wires) - Molex P/N 22-01-3047  
 Contact pins for housing - Molex P/N 08-50-0114

# www.gatewayelex.com

(Electronically Speaking, Gateway's Got It!)



MAIL ORDERS CALL TOLL-FREE 1-800-669-5810

# WESTERN TEST SYSTEMS

# WE BUY AND SELL

Inquiries 303-438-9662 • Fax 303-438-9685

Orders only 800-538-1493

530 Compton St., Unit #C, Broomfield, Colorado 80020

## OSCILLOSCOPES & ACCESSORIES

### TO 100 MHz

TEK SC502 15 MHz Dual Trace Oscilloscope, TM500 series \$ 375.00

### ABOVE 100 MHz

TEK 2465 300 MHz 4-channel Oscilloscope \$ 2,500.00  
TEK 7104 1 GHz Oscilloscope, with 7A29, 7A29-04, 7B10, 7B15 \$ 4,500.00  
TEK 7844 400 MHz Dual Beam Oscilloscope \$ 900.00  
with 7A24, 7A26, 7B80, 7B85  
TEK 7904 500 MHz Oscilloscope, with 7A24, 7A26, 7B80, 7B85 \$ 900.00  
TEK 7A42 4-Channel Logic Triggered Vertical Amplifier \$ 500.00

### PROBES

HP 1122A Probe Power Supply \$ 150.00  
TEK 1101 Accessory Power Supply, for FET probes \$ 200.00  
TEK P6046 100 MHz Differential Probe \$ 750.00  
TEK P6150 9 GHz 10X/3 GHz 1X 50 Ohm Probe, SMA(m) output \$ 400.00  
TEK P6201 300 MHz 1X/10X/100X FET Probe \$ 450.00  
TEK P6202A 500 MHz 10X FET Probe \$ 300.00  
TEK P6203 1 GHz 10X Active Probe, for 11000 series \$ 375.00  
TEK P6701-opt.02 O/E Converter, 450-1050 nm/0-1 mW; DC-700 MHz, ST conn. \$ 175.00

### CALIBRATION

TEK SG503 Level Generator, 250 kHz-250 MHz, TM500 series \$ 600.00

## WAVEFORM GENERATORS

### FUNCTION

HP 3310A 5 MHz Function Generator \$ 250.00  
HP 3310B 5 MHz Function Generator, monocyte & var. phase trigger \$ 325.00  
HP 3312A 13 MHz Function Generator \$ 600.00  
HP 3325A 21 MHz Synthesized Function Generator, HPIB \$ 1,000.00  
HP 3325A-002 21 MHz Function Generator, high voltage output option \$ 1,500.00  
HP 8165A-002.003 Prog. Signal Source, 1 mHz-50 MHz, log sweep, rear out \$ 900.00  
TEK AWG5102 Arb. Waveform Gen., 20 MS/s, 12 bits, 50ppm synthesis <1MHz \$ 1,250.00  
TEK AWG5105-opt.02 Arbitrary Waveform Generator, dual channel option \$ 275.00  
TEK DD501 Digital Delay & Burst Gen., for function & pulse gen's \$ 225.00  
TEK FG501 1 MHz Function Generator, TM500 series \$ 300.00  
TEK FG502 11 MHz Function Generator \$ 250.00  
TEK FG503 3 MHz Function Generator, TM500 series \$ 225.00  
TEK RG501 Ramp Generator, TM500 series \$ 300.00  
WAVETEK 185 5 MHz Lin/Log Sweep/Function Generator \$ 750.00  
WAVETEK 288 20 MHz Synthesized Function Generator, GPIB

### PULSE

BERKELEY NUCLEONICS 7085B Digital Delay Generator, 0-100 mS, 1 nS res., 5 Hz-5 MHz \$ 750.00  
HP 8007B 100 MHz Pulse Generator \$ 650.00  
HP 8012B 50 MHz Pulse Generator, variable transition time \$ 600.00  
HP 8015A-002 50 MHz Dual Output Pulse Generator, gated burst option \$ 750.00  
HP 8080A/81A/83A/84A 300 MHz Word Generator \$ 800.00  
HP 8080A/91A/92A/93A 1 GHz Single Channel Pulse Generator \$ 950.00  
HP 8111A 20 MHz Pulse / Function Generator \$ 1,000.00  
HP 8115A 50 MHz Dual Channel Pulse Generator, HPIB \$ 2,750.00  
TEK PG502 250 MHz Pulse Generator, <1nS, TM500 series \$ 600.00  
TEK PG505 100 kHz Pulse Generator, 80 V peak, TM500 series \$ 275.00  
TEK PG508 50 MHz Pulse Generator, TM500 series \$ 500.00  
WAVETEK 802 50 MHz Pulse Generator \$ 300.00

## VOLTAGE & CURRENT

### VOLTMETERS

FLUKE 845AR High Impedance Voltmeter / Null Detector \$ 400.00  
HP 3456A 6-1/2 Digit Voltmeter \$ 700.00  
HP 3478A 5-1/2 digit Multimeter, HPIB \$ 700.00  
KEITHLEY 181 6-1/2 digit Nanovoltmeter, 10 nV sensitivity, GPIB \$ 900.00  
SOLARTRON 7081 8-1/2 digit Voltmeter \$ 3,250.00  
TEK DM501A 4-1/2 digit Multimeter, TM500 series plug-in \$ 225.00

### CALIBRATION

FLUKE 510A AC Reference Standard, 10 VRMS, 0-10 mA \$ 450.00  
FLUKE 515A Portable Calibrator, DC/AC/Ohms, line & battery power \$ 900.00  
FLUKE 5220A Transconductance Amplifier, DC-5 kHz, 0-20 A \$ 3,000.00  
FLUKE 720A 7-decade Kelvin-Variety Voltage Divider \$ 1,250.00  
FLUKE 731B DC Reference Standard \$ 400.00  
FLUKE 732A DC Voltage Standard \$ 1,750.00  
HOLT 11 AC Thermal Converter Set, 0.5-1200 V, 20 Hz-30 MHz \$ 1,000.00  
VALHALLA 2703 AC Volt. Std., 0-120V/10 Hz-100 kHz; 120-1200V/10 Hz-1 kHz \$ 1,750.00

### VOLTAGE SOURCES

HP 6115A Precision Dual Range Power Supply, 50V 0.8A / 100V 0.4A \$ 850.00  
KEITHLEY 228 Programmable Voltage/Current Source \$ 2,500.00

## CURRENT METERS & SOURCES

HP 1414B Picoammeter / DC Voltage Source, without test fixtures \$ 2,000.00  
HP 6177C DC Current Source, to 50V, 500mA \$ 500.00  
HP 6181C DC Current Source, to 100 V, 250 mA \$ 500.00  
HP 6186C DC Current Source, to 300V, 100mA \$ 750.00  
KEITHLEY 225 Current Source, 0.1 uA-100 mA, 10-100 V compliance \$ 500.00  
KEITHLEY 227 Current Source, 1 uA-1 A, 0-50 V compliance \$ 800.00  
KEITHLEY 261 Picoampere Source \$ 375.00  
HP 64303 Current Probe, DC-15 MHz, 100 A max., for use with AM503 \$ 1,000.00  
TEK AM503/AM302/TM501 AC/DC Current Probe System \$ 1,000.00  
TEK CT-5 -opt.05 High Current Transformer for P6021/A6302, to 1000A meter, 2-2000 uH \$ 300.00  
TEK P6021/A6302, to 1000A meter, 2-2000 uH \$ 550.00

## IMPEDANCE & COMPONENT TEST

### L.C.R.

BOONTON 62AD 1 MHz Inductance \$ 650.00  
BOONTON 72BD 1 MHz Capacitance Meter, 3-1/2 digit display \$ 650.00  
GR 1689-M 5 digit LCR Meter, 12 Hz-100 kHz \$ 1,900.00  
HP 4262A-101 3-1/2 digit LCR Meter, 120 Hz/1 kHz/10 kHz test, HPIB \$ 1,750.00  
HP 4275A-001 5-1/2 digit LCR Meter, 10 kHz-10 MHz, 0-35 V int. bias \$ 5,000.00

### STANDARDS

E.S.I. DB62-11K 6-Decade Resistor, 0-11,111.10 Ohms, 0.01 Ohm res. \$ 300.00  
E.S.I. SR1010 Resistance Transfer Standards, 1 Ohm-100 K/step \$ 550.00  
E.S.I. SR1050-1M Resistance Transfer Standard, 1 Megohm/step \$ 2,000.00  
GR 1404-A 1000 pF Reference Standard Capacitor \$ 700.00  
GR 1406 Standard Air Capacitors, GR900 connector, 0.1% acc. \$ 375.00  
GR 1432-U 4-Decade Resistor, 0-111.10 Ohms, 0.01 Ohm resolution \$ 100.00  
GR 1433-G 7-Decade Resistor, 0-1,111.10 Megohms, 0.1 Ohm res. \$ 275.00  
GR 1433-J 4-Decade Resistor, 0-11,110 Ohms, 1 Ohm resolution \$ 150.00  
GR 1433-K 4-Decade Resistor, 0-1,110 Ohms, 0.1 Ohm resolution \$ 150.00  
GR 1433-L 4-Decade Resistor, 0-111,100 Ohms, 10 Ohms resolution \$ 150.00  
GR 1433-N 5-Decade Resistor, 0-11,111 Ohms, 0.1 Ohm resolution \$ 200.00  
GR 1433-X 6-Decade Resistor, to 111,111.0 Ohms, 0.1 Ohm res. \$ 250.00  
GR 1482-series Standard Inductors \$ 200.00  
VALHALLA 2724A Programmable Resistance Standard, 0-11 Gigaohms, GPIB \$ 1,250.00

### HI & LO RESISTANCE

HP 4328A Milliohmeter \$ 1,200.00

### CURVE TRACERS

TEK 577D1/177 Storage Curve Tracer, with standard test fixture \$ 2,250.00  
TEK 577D2/177 Curve Tracer, with standard test fixture \$ 1,850.00

### T.D.R.

TEK 1502-opt.04 Time Domain Reflectometer, 0-2-000 feet, chart recorder \$ 1,400.00  
TEK 1503-opt.04 Time Domain Reflectometer, 0-50,000 feet, chart recorder \$ 1,400.00

## POWER SUPPLIES

### SINGLE OUTPUT

HP 6002A-001 0-60 V/ 0-10 A/ 200 Watts max. Autoringing Power Supply \$ 750.00  
HP 6011A Autoringing 0-20 V/ 0-120 A Power Supply, 1000 W max \$ 1,400.00  
HP 6200B Dual Range Supply, 0-20 V 0-1.5 A/ 0-40 V 0-750 mA CVCC \$ 200.00  
HP 6201B 0-20 V 0-1.5 A CV/CC Power Supply \$ 175.00  
HP 6207B 0-160 V 0-200 mA CV/CC Power Supply \$ 200.00  
HP 6256B 0-10 V 0-20 A CV/CC Power Supply \$ 300.00  
HP 6260B-027 0-10 V 0-100 A CV/CC Power Supply, 208 VAC line \$ 675.00  
HP 6261B-027 0-20 V 0-50 A CV/CC Power Supply, 208 VAC line \$ 675.00  
HP 6263B 0-20 V 0-5 A CV/CC Power Supply \$ 400.00  
HP 6266B 0-40 V 0-5 A CV/CC Power Supply \$ 400.00  
HP 6267B 0-40 V 0-10 A CV/CC Power Supply \$ 500.00  
HP 6269B-028 0-40 V 0-50 A CV/CC Power Supply, 230 VAC line \$ 900.00  
HP 6271B 0-60 V 0-3 A CV/CC Power Supply \$ 400.00  
HP 6281A 0-7.5 V 0-5 A CV/CC Power Supply \$ 175.00  
HP 6284A 0-20 V 0-3 A CV/CC Power Supply \$ 200.00  
HP 6289A 0-100 V 0-750 mA CV/CC Power Supply \$ 200.00  
HP 6384A 4-0-5 V 0-5 A CV/CC Power Supply \$ 125.00  
HP 6434B 0-40 V 0-25 A CV/CC Power Supply \$ 800.00  
HP 6443B 0-120 V 0-2.5 A CV/CC Power Supply \$ 450.00  
KEPCO ABE-1500M 0-1500 V 10 mA CV/CL Power Supply \$ 125.00  
KEPCO ATE 36-30M 0-36 V 0-30 A CV/CC Power Supply \$ 900.00  
KEPCO ATE 36-8M 0-36 V 0-8 A CV/CC Power Supply \$ 375.00  
SORENSEN DCR 20-25B 0-20 V 0-25 A CV/CC Power Supply \$ 550.00  
SORENSEN DCR 40-40B 0-40 V 0-40 A CV/CC Power Supply \$ 700.00  
SORENSEN DCR 600-0.75B 0-600 V 0-750 mA CV/CC Power Supply \$ 600.00  
SORENSEN SRL 20-12 0-20 V 0-12 A CV/CC Power Supply \$ 400.00  
SORENSEN SRL 60-8 0-60 V 0-8 A CV/CC Power Supply \$ 600.00

TEK PS501-1 Power Supply, 0-20 V, 2 mV res., 400 mA, TM500 series \$ 175.00

### MULTIPLE OUTPUT

HP 6205C Dual Output Supply, 0-40 V 300 mA or 0-20 V 600 mA \$ 300.00  
HP 6227B Dual 0-25 V 0-2 A CV/CC Power Supply \$ 500.00  
HP 6228B Dual 0-50 V 0-1 A CV/CC Power Supply \$ 450.00  
HP 6236B Triple Output Supply, to +/-20 V 0.5 A & 0-6 V 2.5 A \$ 375.00  
HP 6237B Triple Output Supply, to +/-20 V 0.5 A & 0-18 V 1 A \$ 375.00  
HP 6253A Dual 0-20 V 0-3 A CV/CC Power Supply \$ 500.00  
HP 6255A Dual 0-40 V 0-1.5 A CV/CC Power Supply \$ 500.00  
LAMBDA LPT-7202-FM Triple Output Power Supply \$ 450.00  
TEK P55010 Programmable Triple Power Supply, TM500 series \$ 750.00  
TEK P5503A Dual Power Supply, TM500 series \$ 200.00

### MISCELLANEOUS

ACME PS2L-500 Programmable Load, 0-75 V / 0-75 A / 500 Watts max. \$ 400.00  
ELGAR 1751B/461 AC Power Source, 0-135 VAC, 1750 Watts, fixed freq. osc. \$ 2,000.00  
HP 53501B HPIB Isolated DAC/Power Supply Programmer \$ 175.00  
HP 6825A Bipolar Power Supply/ Amplifier, +/- 20 V 2 A \$ 800.00  
HP 6827A Bipolar Power Supply/ Amplifier, +/- 100 V 0.5 A \$ 800.00  
KEPCO BOP 20-20M Bipolar Op Amp/ Power Supply, to 20 V 20 A \$ 675.00  
KEPCO BOP 36-5M Bipolar Op Amp/Power Supply, to 36 V 5 A \$ 400.00  
KEPCO BOP 50-2M Bipolar Op Amp/Power Supply, to 50 V 2 A \$ 400.00  
TRANSISTOR DEVICES DAL-50-15-100 Programmable Load, 0-50 V, 0-15 A, 100 Watts max. \$ 200.00

## TIME & FREQUENCY

### UNIVERSAL COUNTERS

HP 5315A-001 100 MHz/100 nS Universal Counter, TCXO reference option \$ 450.00  
HP 5315B 100 MHz/100 nS Universal Counter \$ 500.00  
HP 5316A 100 MHz/100 nS Universal Counter, HPIB \$ 600.00  
HP 5316A-001, 003 100 MHz/100 nS Univ. Counter, HPIB, TCXO, 1 GHz C-ch. \$ 750.00  
HP 5316B 100 MHz/100 nS Universal Counter, HPIB \$ 750.00  
HP 5334A 100 MHz Universal Counter, HPIB \$ 200.00  
HP 5334A-010,030,050,100 MHz Univ. Counter, OCXO, DVM, 1.3 GHz C-ch., rear in \$ 750.00  
HP 5334B-010,060 100 MHz Universal Counter, HPIB, OCXO \$ 250.00  
HP 5335A 200 MHz Universal / Statistical Counter \$ 500.00  
TEK DC5004 Programmable 100 MHz/100nS Counter/Timer, TM5000 series \$ 250.00  
TEK DC5009 Programmable 135 MHz Univ. Counter/Timer, TM5000 series \$ 400.00  
TEK DC5010 350 MHz / 3.125 nS Universal Counter, TM5000 series \$ 1,200.00  
TEK DC503A 125 MHz/100 nS Universal Counter, TM500 series \$ 275.00  
TEK DC509 135 MHz/10 nS Universal Counter, TM500 series \$ 275.00  
5315A-003 100 MHz/100 nS Univ. Counter, 1 GHz C-channel option \$ 550.00

### FREQUENCY COUNTERS

EIP 575 18 GHz Source Locking Counter, GPIB \$ 1,500.00  
FLUKE 7220A-010,131,351 1.3 GHz Counter; battery power, OCXO, and res. mult. \$ 500.00  
HP 5340A 18 GHz Frequency Counter \$ 450.00  
HP 5342A 18 GHz Frequency Counter \$ 500.00  
HP 5342A-001,011 18 GHz Frequency Counter, OCXO reference & HPIB \$ 600.00  
HP 5342A-003 18 GHz Freq. Counter, +22 dBm, -20 dBm dynamic range \$ 600.00  
HP 5342A-01,04,05,24 GHz Frequency Counter, OCXO, DAC \$ 650.00  
HP 5343A-001 26.5 GHz Frequency Counter, OCXO reference \$ 3,500.00  
HP 5345A/5355A/5356B 26.5 GHz CW/Pulse Frequency Counter \$ 4,000.00  
HP 5384A 25 MHz Frequency Counter, HPIB \$ 500.00  
TEK DP501 1.3 GHz Prescaler, divide by 16, TM500 series \$ 225.00

### STANDARDS

HP 105B Quartz Oscillator, 0.1 / 0.5 MHz, battery power \$ 1,500.00  
HP 5087A-4 11/018 12x4 Dist. Amp., eight 5 MHz outputs, four 10 MHz outputs \$ 1,500.00  
HP 5087A-opt.033 Distribution Amplifier; 12 outputs at 10 MHz \$ 1,750.00

## AUDIO & BASEBAND

### SPECTRUM ANALYSIS

HP 3586C Selective Level Meter, 50 Hz-32.5 MHz, 50 & 75 ohms \$ 1,500.00  
TEK 7L5L3/R7603 Spectrum Analyzer, 20 Hz-100 kHz, 10 Hz min. res., w/frame \$ 1,500.00

### DISORTION ANALYZERS

HP 339A Distortion Analyzer, built-in low distortion osc. \$ 750.00  
HP 8903A-001 Audio Analyzer, 20 Hz-100 kHz, rear panel input \$ 1,500.00  
HP 8903B-001,013,051 Audio Analyzer, 20 Hz-100 kHz, C-message, CCITT \$ 1,750.00  
TEK DA4084 Programmable Distortion Analyzer \$ 750.00

### RMS VOLTMETERS

FLUKE 8920A True RMS Voltmeter, 180 uV-700 V, 10 Hz-20 MHz \$ 450.00  
FLUKE 8922A True RMS Voltmeter, 180 uV-700 V, 2 Hz-11 MHz \$ 450.00

### OSCILLATORS

HP 209A Sine/Square Wave Generator, 4 Hz-2 MHz, 5 VRMS max. \$ 225.00



HP 3336C Synthesizer/Level Generator, 10 Hz-21 MHz	\$ 1,400.00
TEK SG5010 Programmable Oscillator, 10 Hz-163.8 kHz	\$ 2,750.00
TEK SG502 Sine/Square Osc., 5 Hz-500 kHz, 70 dB step atten., TMS00	\$ 200.00

### RF & MICROWAVE

#### SPECTRUM ANALYZERS

HP 3575A-001 Phase-Gain Meter, 1 Hz-13 MHz, dual display option	\$ 850.00
HP 461A Amplifier, 20/40 dB, 1 kHz-150 MHz, 0.5 V/50 Ohms	\$ 125.00
KROHN-HITE 3103 High/Low Pass Filter, 10 Hz-3 MHz, 24 dB/octave	\$ 350.00
KROHN-HITE 3202 Dual HP/LP/BP/BR Filter, 20 Hz-2 MHz, 24 dB/octave	\$ 450.00
KROHN-HITE 3342R Dual HP/LP Filter, 0.001 Hz-99.9 kHz, 48 dB/octave	\$ 900.00
KROHN-HITE 3750 LP/HP/BP/BR Filter, 0.02 Hz-20 kHz, 61/12/18/24 dB/oct.	\$ 600.00
KROHN-HITE DCA-10R 10 Watt Amplifier, 20 dB gain, DC-1 MHz, 600-1000 Ohms	\$ 450.00
ROCKLAND 852 Dual Highpass/Lowpass Filter, 0.1 Hz-111 kHz	\$ 1,000.00
TEK AM502 Differential Amplifier, 0.1 Hz-1 MHz, TMS000 series	\$ 475.00
HP 11517A/18A/19A/20A Mixer Set, 12.4-40.0 GHz, for HP 8555A/8569A	\$ 600.00
HP 11970A WR28 Harmonic Mixer, 26.5-50 GHz	\$ 1,100.00
HP 11970K WR42 Harmonic Mixer, 18.0-26.5 GHz	\$ 1,100.00
HP 11970Q WR22 Harmonic Mixer, 33-50 GHz	\$ 1,400.00
HP 11970U WR19 Harmonic Mixer, 40-60 GHz	\$ 1,400.00
HP 8444A-059 Tracking Generator, 0.5-1500 MHz, for 8554, 8568, etc.	\$ 1,250.00
HP 853A-001 Spectrum Analyzer Display, bench/track mount config.	\$ 1,250.00
HP 8556A-100 Spectrum Analyzer, 10 MHz-22 GHz, 100 Hz min. res.	\$ 4,500.00
HP 8556B Spectrum An., 100 Hz-22 GHz, HP calibration certificate	\$ 25,000.00
HP 8556R Spectrum Analyzer, 10 MHz-22 GHz, 100 Hz min. res. bw.	\$ 7,500.00
TEK 7L14-039/7603 Spectrum Analyzer, 1 kHz-2.5 GHz, 30 Hz min. res. bw.	\$ 2,500.00
TEK TR502 Tracking Generator, 0.1-1800 MHz, for Tek 7L12/13/14	\$ 950.00
TEK TR503 Tracking Generator, 0.1-1800 MHz, for 4322/4516	\$ 850.00
TEK WM782V WR15 Harmonic Mixer, 50-75 GHz	\$ 1,500.00

#### NETWORK ANALYZERS

HP 08748-60010 8748A Reference Plane Extension Cables (set of 6)	\$ 3
HP 08748-60011 8748A-H26 Reference Plane Extension Cables (set of 3)	\$ 250.00
HP 35676A Reflector/Transmission Test Kit, 5 Hz-200 MHz	\$ 1,000.00
HP 8405A Vector Voltmeter, 1-1000 MHz	\$ 450.00
HP 85020A Directional Bridge, 10-4300 MHz, N(f) test port	\$ 650.00
HP 85021A Directional Bridge, 0.01-18 GHz, APC7 test port	\$ 1,000.00
HP 85021C Directional Bridge, 0.01-18 GHz, N(f) test port	\$ 1,000.00
HP 8502A-H26 Reflector/Transmission Test Set, 4-2600 MHz	\$ 600.00
HP 8504A Reflection/Transmission Test Set, 300 kHz-3 GHz	\$ 1,500.00
HP 85046A S-Parameter Test Set, 300 kHz-3 GHz, for HP 8753A/B/C	\$ 3,750.00
HP 8753A Network Analyzer, 300 kHz-3 GHz	\$ 7,500.00
HP 8756A Scalar Network Analyzer	\$ 2,500.00
HP R85026A WR28 Detector, 26.5-40 GHz, for HP 8757 series	\$ 1,200.00

#### SIGNAL GENERATORS

FLUKE 6060A Synthesized Signal Gen., 0.1-1050 MHz, 10 Hz res., GPIB	\$ 2,500.00
FLUKE 6060A/AN Synthesized Signal Gen., 10 kHz-520 MHz, 10 Hz res., GPIB	\$ 1,750.00
FLUKE 6062A Synthesized Signal Gen., 0.1-2100 MHz, 10 Hz res., GPIB	\$ 5,000.00
GIGATRONICS 1018 Synthesized Signal Gen., 50 MHz-18 GHz, 1 MHz res.	\$ 4,500.00
GIGATRONICS 60910-18 Synthesized Source, 10-18 GHz, 1 MHz res., GPIB	\$ 2,500.00
GIGATRONICS 60916-12 Synthesized Source, 6-12 GHz, 1 kHz res., GPIB	\$ 2,500.00
GIGATRONICS 875/50 Levelled Multiplier, x4, 50.0-75.0 GHz output, -3 dBm	\$ 2,500.00
GIGATRONICS 875/86 Levelled Multiplier, 26.5-40.0 & 50.0-75.0 GHz outputs	\$ 3,750.00
GIGATRONICS 900/2-8 Synthesized Signal/Sweep Gen., 2-8 GHz, 1 MHz res., GPIB	\$ 2,500.00
HP 11720A Pulse Modulator, 2-18 GHz, 80 dB on/off ratio	\$ 450.00
HP 85100V Frequency Mult., 10-15 GHz in / 50-75 GHz out >0 dBm	\$ 3,750.00
HP 8640B-001 Signal Generator, 0.5-512 MHz, AM, FM, var. audio osc.	\$ 1,000.00
HP 8640B-002 Signal Generator, 0.5-1024 MHz, AM, FM, reverse power prot.	\$ 1,750.00
HP 8656B-001 Synth. Signal Gen., 0.1-990 MHz, 10 Hz res., COXO ref.	\$ 2,500.00
HP 8657A-002 Signal Generator, 0.1-1040 MHz, 10 Hz res., HP1B	\$ 3,250.00
HP 8660C/8660B-002 Synth. Sig. Gen., 1-1300 MHz, FM / Phase mod. w/86635A	\$ 3,000.00
HP 8660C/8660A-002 Synthesizer, 1-2600 MHz, FM / Phase mod. w/86635A	\$ 4,250.00
HP 8672A Synthesized Signal Generator, 2-18 GHz	\$ 6,000.00
HP 8673G-004 Synth. CW Signal Generator, 2-26 GHz, >+8 dBm output	\$ 12,500.00
HP 8684B Signal Generator, 5.4-12.5 GHz, AM, WBFM, Pulse	\$ 3,500.00

#### SWEEP GENERATORS

HP 8350A/83545A-002 Sweep Oscillator, 5.9-12.4 GHz, 70 dB step attenuator	\$ 4,000.00
HP 83545A RF Plug-in, 5.9-12.4 GHz, +17 dBm levelled	\$ 1,750.00
HP 8601A Generator/Sweeper, 0.1-110 MHz, +20 dBm levelled	\$ 400.00
HP 8620C Sweep Oscillator Frame	\$ 550.00
HP 8752D-002 RF Plug-in, 10-2400 MHz, +13 dBm levelled, 70 dB atten.	\$ 1,500.00
HP 86230B RF Plug-in, 1.8-4.2 GHz, +10 dBm unlevelled	\$ 400.00

HP 86235A-001,002 RF Plug-in, 1.7-4.3 GHz, +14 dBm levelled, 70 dB atten.	\$ 600.00
HP 86240C RF Plug-in, 3.6-8.6 GHz, +16 dBm levelled	\$ 700.00
HP 86241A-001 RF Plug-in, 3.2-6.5 GHz, +8 dBm levelled	\$ 300.00
HP 86242D-004,008 RF Plug-in, 5.9-9.0 GHz, +10 dBm levelled	\$ 300.00
HP 86250D RF Plug-in, 8.0-12.4 GHz, +10 dBm levelled	\$ 500.00
HP 86260A RF Plug-in, 12.0-18.0 GHz, +10 dBm levelled	\$ 500.00
HP 86260A-H04 RF Plug-in, 10.0-15.0 GHz, +10 dBm unlevelled	\$ 500.00
HP 86290A RF Plug-in, 2.0-18.0 GHz, +7 dBm levelled	\$ 1,750.00
WAVETEK 962 Sweep Generator, 1.0-4.0 GHz, markers, -12 dBm unlvld.	\$ 1,250.00
WILLTRON 6619A Sweep Generator, 2-8 GHz, +10 dBm levelled	\$ 1,500.00

#### POWER METERS

ANRITSU MA728 Power Sensor, -20 to +20 dBm, 0.01-18 GHz	\$ 200.00
ANRITSU MP-81B/ML-83A Power Meter, 75-110 GHz (WR10), -20 to +20 dBm	\$ 2,500.00
BOONTON 4200-01A,03B-4A X2 Dual Channel Microwattmeter, w/(2) 1 MHz-7 GHz sensors	\$ 1,500.00
BOONTON 42B/41-4B Analog Power Meter, with 1 MHz-12 GHz sensor	\$ 375.00
BOONTON 42B/41-4E Analog Power Meter, with 1 MHz-18 GHz sensor	\$ 500.00
GENERAL MICROWAVE 476/4240A Power Meter & Sensor, 0.01-18 GHz, -35 to +10 dBm	\$ 300.00
HP 435B/8482B Power Meter, 0 to +43 dBm, 100 kHz-4.2 GHz	\$ 1,800.00
HP 435B/8482H Power Meter, 0.1-4200 MHz, -10 to +34 dBm	\$ 950.00
HP 8477A Power Meter Calibrator, for HP 432 series	\$ 500.00
HP K486A WR42 Thermistor Mount, 18.0-26.5 GHz, for 432 series	\$ 350.00
HP Q8486A Power Sensor, 33.0-50.0 GHz, WR22, for 435/67/8	\$ 1,500.00
HP R486A WR28 Thermistor Mount, 26.5-40 GHz, for 432 series	\$ 350.00
HP R8486A WR28 Power Sensor, 26.5-40 GHz, for HP 435/67/8	\$ 1,500.00

#### RF MILLIVOLTMETERS

BOONTON 92B-opt.05 RF Millivoltmeter, 10 kHz-1.2 GHz, 75 Ohms scale	\$ 500.00
RACAL 9303 TRMS Level Meter, 10 kHz-2 GHz, -77 to +23 dBm, GPIB	\$ 875.00

#### AMPLIFIERS, MISCELLANEOUS

AMPLIFIER RESEARCH 1W1000 Amplifier, 30 dB gain, 1-1000 MHz, 1 Watt output	\$ 650.00
BOONTON 82AD-opt.01A Modulation Meter, AM, FM, 10-1200 MHz, GPIB	\$ 750.00
HP 415E SWR Meter	\$ 200.00
HP 465A Amplifier, 20/40 dB, 5 Hz-1 MHz, 1/2 Watt/50 Ohms	\$ 125.00
HP 8447A Amplifier, 20 dB, 0.1-400 MHz, 5 dB return loss	\$ 375.00
HP 8447E Amplifier, 22 dB, 0.1-1300 MHz, +13 dBm output	\$ 750.00
HP 8447F Preamp/Power Amplifier, 0.1-1300 MHz	\$ 1,200.00
HP 8901A Modulation Analyzer, 150 kHz-1300 MHz	\$ 2,500.00
HP 8901B-1,2,3 Modulation An., 0.15-1300 MHz, rear input, COXO, ext.LO	\$ 3,500.00
HP 8970A Noise Figure Meter	\$ 5,000.00
HUGHES 1177H02F000 TWT Amplifier, 4.0-8.0 GHz, 10 Watts output	\$ 1,500.00
MICROWAVE SEMI-CORP MC5112 Noise Source, 25.5 dB ENR, 1.0-12.4 GHz, N(m), +28 VDC	\$ 175.00
ROHDE & SCHWARTZ ESHZ Test Receiver, 3 kHz-30 MHz	\$ 5,000.00

### COAXIAL & WAVEGUIDE

AMERICAN NUCLEONICS AM-432 Cavity Backed Spiral Antenna-LHC, 2-18 GHz, TNC(f) *NEW*	\$ 95.00
AVANTEK AMT-400X2 WR28 Active Doubler, 13-20 GHz +10 dBm in, +10 dBm out	\$ 450.00
CONTINENTAL MW. RAE28-K-M WR28 x K(f) Envelope Adapter	\$ 225.00
FXR/MICROLAB S3-02N Triple Stub Tuner, 200-1000 MHz, 100 Watts max., N(m/f)	\$ 125.00
GR 874-LTL Constant Impedance Trombone Line, 0-44 cm, DC-2 GHz	\$ 400.00
GR 900-Q GR900 14mm Interseries Adapters	\$ 125.00
HP 11590A-001 Bias Network, 1.0-18.0 GHz, APC7	\$ 450.00
HP 11612A Bias Network, 45 MHz-26.5 GHz, APC3.5	\$ 550.00
HP 11692D Dual Directional Coupler, 22 dB, 2-18 GHz	\$ 800.00
HP 33321K Programmable Step Attenu., 0-70 dB, DC-26.5 GHz, 3.5mm	\$ 475.00
HP 33327L-006 Programmable Step Attenuator, 0-70 dB, DC-40 GHz, 2.9mm	\$ 1,200.00
HP 774D Dual Directional Coupler, 20 dB, 215-450 MHz	\$ 275.00
HP 777D Dual Directional Coupler, 20 dB, 1.9-4.1 GHz	\$ 275.00
HP 778D-011 Dual Dir. Coupler, 20 dB, 100-2000 MHz, APC7 test port	\$ 450.00
HP 8431A 2-4 GHz Band Pass Filter, N(m/f)	\$ 150.00
HP 8470B Crystal Detector, 10 MHz-18 GHz, neg. pol., APC7	\$ 250.00
HP 8472A Crystal Detector, 10 MHz-18 GHz, neg. pol., SMA	\$ 150.00
HP 8472B Low Barrier Schottky Det., 10 MHz-18 GHz, neg. pol., SMA	\$ 200.00
HP 8494A-001 Step Attenuator, 0-11 dB, DC-4 GHz, N(f)	\$ 350.00
HP 8494B-002 Step Attenuator, 0-11 dB, DC-18 GHz, SMA(f)	\$ 450.00
HP 8494G-002 Programmable Step Attenuator, 0-11 dB, DC-4 GHz, SMA	\$ 350.00
HP 8495G-002 Programmable Step Attenuator, 0-70 dB, DC-4 GHz, SMA	\$ 300.00
HP 8495H-002 Programmable Step Attenuator, 0-70 dB, DC-18 GHz, SMA	\$ 400.00
HP 8496B-002 Step Attenuator, 0-110 dB, DC-18 GHz, SMA(f)	\$ 450.00
HP 8497K-004 Programmable Step Attenuator, 0-90 dB, DC-26.5 GHz	\$ 750.00
HP K382A WR42 Direct Reading Attenuator, 0-50 dB, 18-26.5 GHz	\$ 2,900.00
HP K422A WR42 Flat Broadband Detector, 18.0-26.5 GHz	\$ 350.00
HP K532A WR42 Frequency Meter, 18.0-26.5 GHz	\$ 450.00
HP K870A WR42 Slide Screw Tuner, 18.0-26.5 GHz	\$ 275.00
HP K914B WR42 Moving Load, 18.0-26.5 GHz	\$ 350.00
HP Q752D WR22 Directional Coupler, 20 dB, 33-50 GHz	\$ 650.00
HP R382A WR28 Direct Reading Attenuator, 0-50 dB, 26.5-40 GHz	\$ 2,000.00

HP R532A WR28 Frequency Meter, 26.5-40 GHz	\$ 500.00
HP R752A WR28 Directional Coupler, 3 dB, 26.5-40 GHz	\$ 450.00
HP R914B WR28 Moving Load, 26.5-40 GHz	\$ 300.00
HP V365A WR15 Isolator, 25 dB, 50-75 GHz	\$ 900.00
HP V752D WR15 Directional Coupler, 20 dB, 50-75 GHz	\$ 650.00
HP X870A WR90 Slide Screw Tuner	\$ 150.00
HUGHES 45111H-2000 WR28 Isolator, 25 dB, 26.5-40 GHz	\$ 450.00
HUGHES 45712H-1000 WR22 Frequency Meter, 33-50 GHz	\$ 900.00
HUGHES 45721H-1000 WR28 Direct Reading Attenuator, 0-50 dB, 26.5-40 GHz	\$ 900.00
HUGHES 45732H-200 WR22 Level Set Attenuator, 0-25 dB, 33-50 GHz	\$ 250.00
HUGHES 45772H-1100 WR22 Thermistor Mount, -20 to +10 dBm, 33-50 GHz	\$ 400.00
HUGHES 45775H-1100 WR12 Thermistor Mount, -20 to +10 dBm, 60-90 GHz	\$ 800.00
HUGHES 47316H-1111 WR10 Tunable Detector, 75-110 GHz, positive polarity	\$ 600.00
HUGHES 47323H-1211 WR19 Flat Broadband Detector, negative, 40-60 GHz	\$ 650.00
HUGHES 47974H-1000 WR15 SPST PIN Switch, 250 MHz speed, 60-62 GHz response	\$ 375.00
KAY 442D Step Attenuator, 0-101 dB, 75 ohms, BNC	\$ 100.00
M/A-COM 3-19-300/10 WR19 Directional Coupler, 10 dB, 40-60 GHz	\$ 450.00
MIDWEST MICROWAVE 3537 DC Block, 0.1-12.4 GHz, SMA(m) *NEW*	\$ 40.00
MINI-CIRCUITS ZFDC-20-4 Directional Coupler, 19.5 dB, 1-1000 MHz, SMA(f)	\$ 25.00
MINI-CIRCUITS ZHL-42 Amplifier, 30 dB gain, 0.7-4.2 GHz, +28 dBm, 15V, SMA	\$ 400.00
NARDA 3000-SERIES Directional Couplers	\$ 150.00
NARDA 3024 Bi-Directional Coupler, 20 dB, 4-8 GHz	\$ 300.00
NARDA 3090-SERIES Precision High Directivity Couplers	\$ 225.00
NARDA 366B/NM Coaxial High Power Load, 500 Watts, 2.0-18 GHz, N(m)	\$ 500.00
NARDA 369B/NF High Power Termination, 175 Watts, 0.7-18 GHz, N(f)	\$ 325.00
NARDA 3752 Coaxial Phase Shifter, 0-180 deg./GHz, 1-5 GHz	\$ 1,000.00
NARDA 3753B Coaxial Phase Shifter, 0-55 deg./GHz, 3.5-12.4 GHz	\$ 1,000.00
NARDA 4000-SERIES SMA Miniature Directional Couplers	\$ 75.00
NARDA 4245-10 Directional Coupler, 10 dB, 4-12 GHz, SMA(f)	\$ 100.00
NARDA 4799 Level Set Attenuator, 0-15 dB, 4-18 GHz, SMA(f)	\$ 135.00
NARDA 5070-SERIES Precision Reflector Couplers	\$ 300.00
NARDA 765-10 10 dB Attenuator, 50 Watts, DC-5 GHz, N(m/f)	\$ 135.00
NARDA 792FF Variable Attenuator, 0-20 dB, 2.0-12.4 GHz	\$ 375.00
NARDA 794FM Direct Reading Variable Attenuator, 0-40 dB, 4-8 GHz	\$ 375.00
OMNI-SPECTRA 2085-6010-00 Crystal Detector, 1-18 GHz, negative polarity, SMA(m/f)	\$ 50.00
PALTECH KY1014 WR42 Junction Circulator, 18.0-26.5 GHz	\$ 250.00
SONOMA ENG. S-4901 WR15 Junction Isolator, 57-59 GHz, 30 dB isolation	\$ 125.00
SONOMA ENG. S-4906 WR15 Junction Isolator, 60-62 GHz, 30 dB isolation	\$ 125.00
SONOMA ENG. S-4907 WR15 Junction Isolator, 62-64 GHz, 30 dB isolation	\$ 125.00
SONOMA SCIENTIFIC 21A3 WR42 Circulator, 20 dB, 20.6-24.8 GHz	\$ 75.00
SPACE LABS DQ-1 WR22 Flat Broadband Detector, 33-50 GHz	\$ 400.00
SPACE LABS K-2X Frequency Doubler, 1.0-13.25 GHz in / 18.0-26.5 GHz out	\$ 350.00
SPACE LABS KA-3X Frequency Tripler, 8.83-13.33 GHz in / 26.5-40.0 GHz out	\$ 350.00
TRANSCO 705C90100 Latching DPDT Transfer Switch, DC-26.5 GHz, 28 V	\$ 150.00
TRG B528 WR22 Direct Reading Phase Shifter, 0-360 deg., 33-50 GHz	\$ 1,250.00
TRG V551 WR15 Frequency Meter, 50-75 GHz	\$ 600.00
TRG W551 WR10 Frequency Meter, 75-110 GHz	\$ 750.00
WAVELINE 100080 WR28 Terminated Crossed Couplers, 30 dB	\$ 200.00
WEINSCHEL 1515 Power Divider, 2-Way, DC-18 GHz, SMA(m/f)	\$ 125.00
WEINSCHEL DS109 Double Stub Tuner, 1-13 GHz, N(m/f)	\$ 150.00
WEINSCHEL DS109LL Double Stub Tuner, 0.2-2.0 GHz, N(m/f)	\$ 150.00

### COMMUNICATIONS

HP 3762A/3763A BER Test System, 1 kHz-150 MHz	\$ 1,250.00
HP 4935A-003 Transmission Test Set, 20 Hz-110 kHz, battery power	\$ 600.00
HP 59401A HP1B Bus Analyzer	\$ 700.00
TEK 1410R NTSC Gen., w/SPG2 sync generator, TSG7 color bars	\$ 800.00
TEK 1411R PAL Gen., w/SPG12 sync, TSG11 color bars, TSG13 linearity	\$ 750.00
TEK 1411R PAL Test Gen., w/SPG12, TSG11, TSG13, TSG15, TSG16	\$ 1,000.00
TEK 1411R PAL Test Gen., w/SPG12, TSG11, TSG12, TSG13, TSG15, TSG16	\$ 1,100.00
TEK 1411R-opt.04 PAL Test Gen., w/SPG12, TSG11, TSG11, TSG13, TSG15, TSG16	\$ 1,400.00
TEK 147A NTSC Test Signal Generator, with noise test signal	\$ 600.00
TEK 147A NTSC Test Signal Generator, with noise test signal	\$ 800.00
TEK 148 PAL Insertion Test Signal Generator	\$ 700.00
TEK 520A NTSC Vectorscope	\$ 750.00
TEK 521A PAL Vectorscope	\$ 750.00

#### MISCELLANEOUS

P.A.R. 5206-95.98 Two-Phase Lock-in Amp., 2 Hz-100 kHz, GPIB	\$ 1,500.00
P.A.R. 5209 Lock-in Amp., 0.5 Hz-100 kHz, 1	

# AMATEUR ROBOTICS

# NOTEBOOK

by Robert Nansel

Though it's barely past Thanksgiving as I write this, it will be January by the time you read this column, so Happy New Year to all you gearheads out there. Even if you didn't get that digital storage scope you've been lusting after, 1999 is going to be a great year for building robots.


Also, I didn't want to present yet another version of Breadbot's figure-eight test software (only this time in PIC assembler). I want to actually make Breadbot do something worth doing, and that's going to take some real work. Which left me in a quandary: what should Breadbot do?

As any mobile robot builder will

mobile robots. In its current form, Breadbot doesn't do this very well because it doesn't have feedback to tell it how straight it's steering or what distance it has traveled. So, one goal for the coming year is to explore ways to make Breadbot and its descendants go in straight lines.

This will require wheel encoder

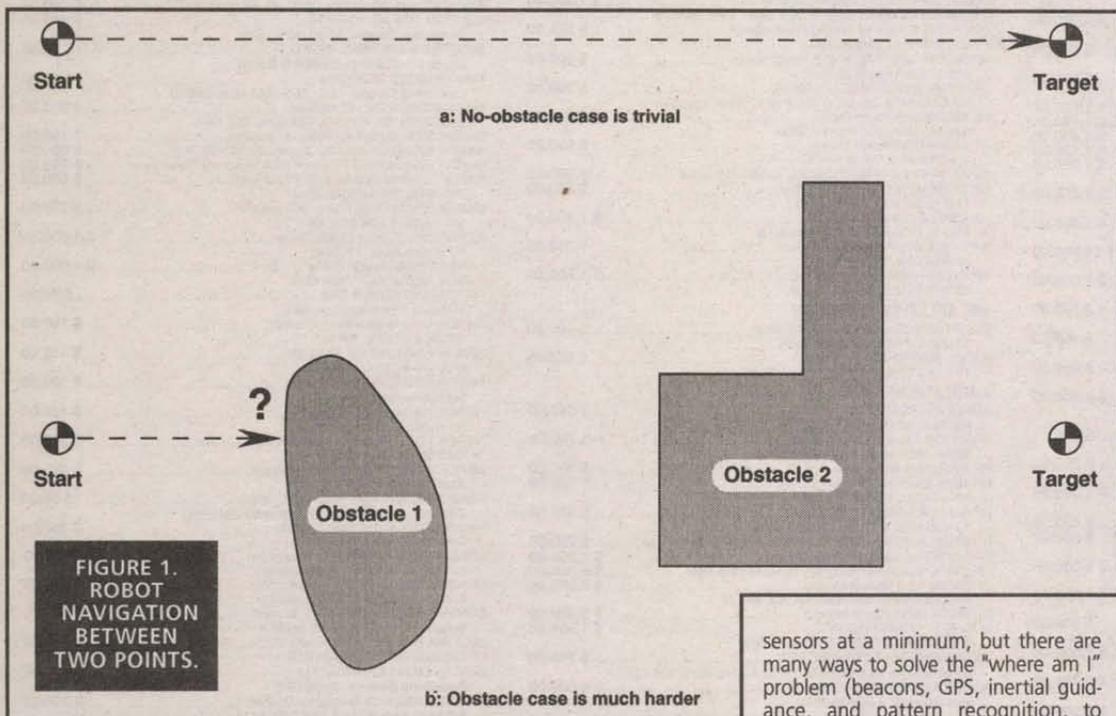avoidance and navigation, things become really interesting. The problem is so complex that even people sometimes have problems solving it, and very few amateur roboticists even attempt it with their machines. Call it hubris, but this year I'm going to give it a shot.



This month, I was going to show how to use the DonTronics DT101 SIMMStick as a high-performance brain for Breadbot, but I got to thinking about the New Year and what I want to accomplish in robotics in 1999, and I decided to postpone the actual brain transplant in favor of outlining some of those larger goals.

say, it should be, well, mobile. But mobile in an interesting way.

### Where am I?

A robot's whole reason for being is to autonomously go from point A to point B, and it is this ability that ultimately separates RC toys from true

sensors at a minimum, but there are many ways to solve the "where am I" problem (beacons, GPS, inertial guidance, and pattern recognition, to mention a few). Most wheel encoders are optical, but this month I'll touch on one new part that will give optical encoders a real run for their money (more on this later).

Just going from point A to point B isn't all that interesting in and of itself, though. When there can be obstacles in the path between A and B, when the robot has to do obstacle

### Is there Software in that Land?

Another area that I want to work on is development tools. So far, I've avoided the issue with the various incarnations of Breadbot; PBASIC provided a convenient — if not exactly high power — development environment, and that was that.

Now as I'm venturing into the land of assembly language, I know that, although I am comfortable with assembly language, many of you out there won't be. Assembly language, for all its speed, is not the ideal language to illustrate the general principles of AI programming; with the availability of good compilers for embedded processors, using a high-level language such as C makes sense for all programming but the lowest-level I/O.

I've used Forth and, while I admire its lean, elegant style and power, most people find Forth code nearly impossible to read. C and its offspring — like it or not — are what the majority of folks are most comfortable programming in. C can be pretty obtuse, too, of course, but good programming practices can alleviate most of that.

### Get Real Time

Another area that I want to investigate in the coming months is the use of a Real Time Operating System (RTOS) to simplify the task of writing the code more complex robots will require. Robots are inherently multi-

**\$\$\$ We Can Save You Money \$\$\$**

Computers	PCB Manufacturing	PCB Assembly Services	Full Line Of Electronic Components
Custom Built PC's at the Lowest Prices Computer Accessories	Single & Double Sided	Board Stuffing Wave Soldering Acquisition of Parts	IC's Semiconductors Capacitors Resistors Sockets Relays Transistors & More
Call <b>Chaffin Electronics</b> Toll Free at <b>(800) 442-2330</b>			
<b>WE WANT YOUR BUSINESS!!! BIG OR SMALL</b>			
Phone (800) 442 2330	Fax (740) 354-9462	Email ccinc@zoomnet.net	Internet www.chaffinelectronics.com

## USB Relay Module

**Model JSB-210**


*Controls 8 to 16 "form C" relays over the USB (Universal Serial Bus). Program the module with simple commands in any program language that supports USB Communications. Driver and sample code provided*

**J-Works, Inc**  
12328 Gladstone St., Unit 4  
Sylmar, CA 91342  
(818) 361-0787 Voice (818) 270-2413 Fax

**Other Products**  
RS-485 Remote I/O  
ISA Waveform Generator  
RS-485 to DS-1820  
RS-485 Temperature I/O  
DS-1820 Probe

Visit our Web site for Information on all our products  
<http://www.j-works.com>  
E-mail [sales@j-works.com](mailto:sales@j-works.com)

**FIGURE 2.**  
ROBOT PATH WITH  
BUG 1 ALGORITHM.

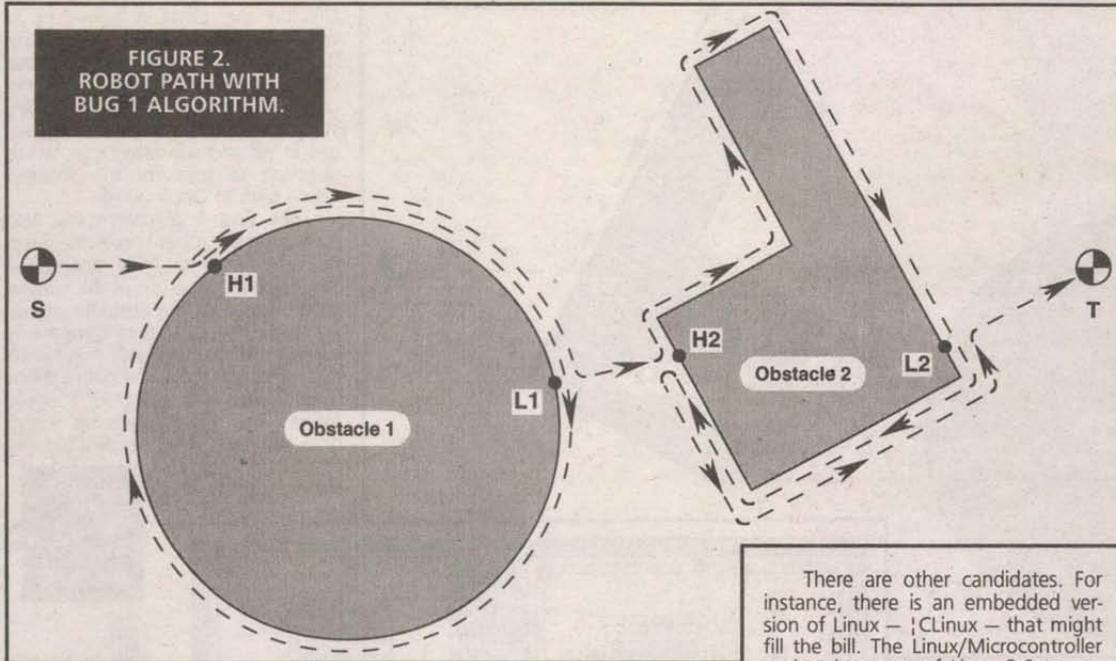

tasking creatures since motion control, sensing, and planning must occur simultaneously while the robot is in motion. The idea is to incorporate reflex actions that can be triggered by certain conditions — say, bumping into a wall — without having to explicitly code every possible exception (which would be mostly impossible in any case).

There are hundreds of RTOS systems out there for every processor you can imagine. Most are expensive, proprietary systems that aren't of much interest to amateur robot builders, but there are a number of free systems around. One I'm looking at is *!C/OS* (pronounced "micro-see OS") by Jean Labrosse. This is a portable, ROMable, scalable, preemptive real-time, multi-tasking kernel for microprocessors and microcontrollers. The RTOS is described in Labrosse's book *!C/OS*,

*The Real-Time Kernel* which also includes a diskette with all the source code. *!C/OS* manages up to 63 user tasks, and its performance is comparable with many commercially available kernels. Because *!C/OS* was designed from the outset to be as processor-independent as possible, it's written in C with an absolute minimum of assembly language. Altogether, it seems ideal for hacking into a robot OS.

Labrosse has just published a new book with a new version of *!C/OS* called (of course) *!C/OS-II*. I haven't seen this book yet, but it's available for \$69.95 hard cover, with disk (560 pp, 8" x 10", ISBN 0-87930-543-6). I think I'll wait for the paperback version. The latest version of the original *!C/OS* source code — V1.11 — is available for free download from his website (see sidebar).

There are other candidates. For instance, there is an embedded version of Linux — *!CLinux* — that might fill the bill. The Linux/Microcontroller project is a port of Linux 2.0 to systems without a Memory Management Unit. There's even a version that runs on the 3Com PalmPilot, which would make a dandy robot controller. The nice thing about this RTOS is that it's all published under the GNU Public License, as are all the development tools. That means they are free. I haven't looked at this port yet, so I'll let y'all know how it looks in coming months. One thing for sure, though, is this one won't run on a PIC.

Finally, this year I want to look into networking processors together to make sophisticated robots. There are many network technologies to choose from (I2C, CAN-Bus, USB, etc.), but I want to concentrate on the network software architecture first. I favor a publish/subscribe architecture where any processor node that has data to announce "publishes" it to the network without explicitly addressing

it to any particular node, in turn, any node that needs certain data will send a "subscribe" notice to the network, informing any nodes that publish that information. This makes for a robust, easy-to-program system since neither publisher nor subscriber nodes need be aware of each other.

## Bug Algorithms

What is the simplest possible algorithm for a mobile robot to autonomously navigate from a starting point S to a target point T? If there are no obstacles between S and T, the obvious solution is for the robot to follow the straight line segment connecting the two points. Even though the robot may use position feedback (say, from wheel shaft encoders), this approach is fundamentally open loop because no allowance is made for obstacles.

A more interesting — and useful — problem to solve, then, would allow arbitrary obstacles to exist between S and T. Because the mechanical elements needed for planar mobility are well understood and can be considered "off-the-shelf" items, the question really boils down to "what are the simplest sensing schemes and motion control algorithms required to deal with arbitrary obstacles between S and T?"

For any robot navigating in a domain with unknown obstacles, the simplest sensor is the bumper contact sensor. There are many electro-mechanical possibilities for bumper sensing. As proof of the utility of bumpers, consider that every animal in nature has some form of tactile collision sense, even those animals that possess incomparably more sophisticated senses such as vision or sonar. Some animals — insects in particular — have almost no other sense than the tactile sense. Assuming we can build

As always, if you have suggestions for improving Breadbot, if you've built a Breadbot, or if you have questions or comments about amateur robotics topics, you can reach me at:

**Robert Nansel**

69 S. Fremont Ave. #2  
Pittsburgh, PA 15202

E-Mail: [bnansel@nauticom.net](mailto:bnansel@nauticom.net)

### BUG 1 & 2 algorithms:

Lumelsky, V. J. and Stepanov, A. A. "Path-Planning Strategies for a Point Mobile Automaton Moving amidst Unknown Obstacles of Arbitrary Shape." *Algorithmica*, 1987, pp 403-430.

### !CLinux web page:

[ryeham.ee.ryerson.ca/u/CLinux/](http://ryeham.ee.ryerson.ca/u/CLinux/)

### !C/OS web page:

[www.ucos-ii.com/](http://www.ucos-ii.com/)

### R&D Books:

(Labrosse's *!C/OS* book, and other embedded programming titles)

6600 Silacci Way  
Gilroy, CA 95020

Tel: 1-800-500-6875, (408) 848-8294

Fax: (408)-848-5784

[www.rdbooks.com](http://www.rdbooks.com)

### Melexis, Inc.

15 Sutton Rd. Box 837  
Webster, MA 01570

Tel: (508) 943-9430  
Fax: (508) 943-0487

[www.melexis.com](http://www.melexis.com)

## EZ-EP DEVICE PROGRAMMER - \$169.95

Check Web!! -- [www.m2l.com](http://www.m2l.com)

**Fast** - Programs 27C010 in 23 seconds

**Portable** - Connects to PC Parallel Port

**Versatile** - Programs 2716-080 plus EE and flash (28, 29) to 32 pins

**Inexpensive** - Best for less than \$200

● Correct implementation of manufacturer specified algorithms for fast, reliable programming.

● Easy to use menu based software has binary editor, read, verify, copy, etc. Free updates via bbs or web.

● Full over current detection on all device power supplies protects against bad chips and reverse insertion.


● Broad support for additional devices using adapters listed below.

### Available Adapters

EP-PIC (16C5x, 61, 82x, 71, 84)	\$49.95
EP-PIC84 (16C62-5, 72-4)	\$30.95
EP-PIC12 (12C50x)	\$39.95
EP-PIC17 (17C4x)	\$49.95
EP-51 (8751, C51)	\$39.95
EP-11E (89HC11 E/A)	\$59.95
EP-11D (89HC11 D3)	\$39.95
EP-16 (160x EPROMs)	\$49.95
EP-28 (28A02, 3, 4, 5, 7, 8)	\$39.95
EP-SEE2 (93x, 24x, 25x, 85x)	\$39.95
EP-750 (87C750, 1, 2)	\$59.95
EP-PEEL (IC22x10, 18x6)	\$59.95
EP-1051 (89C1051, 2051)	\$39.95
EP-PLCC (PLCC EPROMs)	\$49.95
EP-SOIC (SOIC EPROMs)	\$49.95
EP-TSOP (TSOP EPROMs)	\$59.95
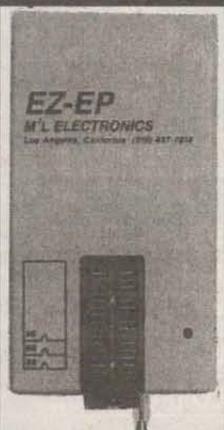
### M<sup>2</sup>L Electronics

970/259-0555  
Fax: 970/259-0777  
361 S Camino Del Rio #119  
Durango, CO 81301  
CO orders please add 7%  
sales tax.  
<http://www.m2l.com>



Write in 65 on Reader Service Card.

## Motron Electronics

PO Box 2748  
Eugene OR 97402-0280

(541) 687-2118  
<http://www.motron.com/>


The Auto-Kall® AK-32 Radio Telemetry/Control Boards are designed for remote control applications where direct wiring is impractical. By implementing a radio interface, the AK-32 offers both a wireless and economical solution. The AK-32 boards work in pairs and can be used for bi-directional control and contact monitoring applications. The AK-32 will work with any FM Communications or Amateur Radio transceiver (Appropriate licenses required.) The AK-32 features 16 inputs and 16 open-collector outputs designed to control 12V relays. Outputs can be connected to any of the MoTron line of Relay Boards. Programming the boards is accomplished with any DTMF source, and will retain the data in the EEPROM until reprogrammed. For additional information, visit our website, or call us at (541) 687-2118.



Visa, MasterCard, American Express, Discover and Government Purchase Orders accepted.  
S/H: \$8 USA; \$11 Canada; \$16 Foreign.  
Se Habla Español. Pida Por Don Moser.

Info: (541) 687-2118 **Orders: (800) 338-9058** Fax: (541) 687-2492


**\$249.00**  
plus shipping

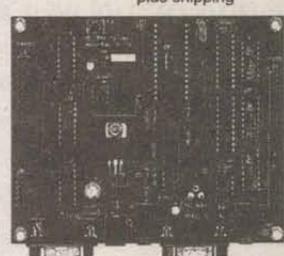

**Auto-Kall® AK-32**  
Radio Telemetry/Control Board



**FIGURE 3. ROBOT PATH WITH BUG 2 ALGORITHM.**

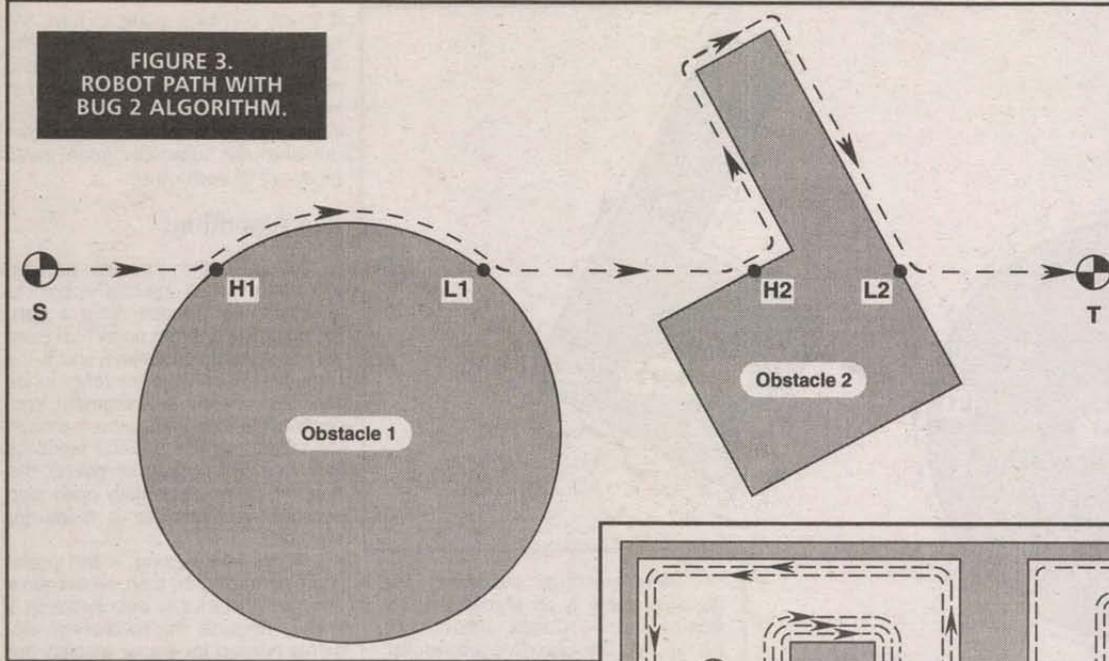

suitable bumpers, can we program a robot "bug" using bumper sensors to successfully negotiate unknown obstacles?

In short, yes. Two simple algorithms created over a decade ago by Vladimir Lumelsky satisfy the obstacle avoidance needs of a robot attempting to travel from any initial position to any target position regardless of the obstacles in between. These algorithms are called, appropriately enough, BUG 1 and BUG 2. If a path exists, these algorithms will find it, and though the path won't necessarily be optimum, it will usually be good enough.

Assuming no prior knowledge of the obstacles that might be in its way, a robot with only bumpers for sensors can deal with an obstacle only by running into it and then attempting to skirt around it. Without knowledge of the obstacle's shape or size, the robot has no way of knowing which way to turn is the "best," so an arbitrary direction to turn must be chosen.

To keep things simple, pick one direction and stick with it. This preferred direction is called the "local direction." If the robot always turns left when it bumps into an obstacle,

then it is using a "left local direction" rule. Where the robot first hits an obstacle is designated a "hit point" and where the robot leaves the obstacle to continue on toward the target is called a "leave point." Now that the terminology is out of the way, let's look at the Bug algorithms.

### BUG 1

1. From point  $L_{i-1}$  (with  $L_0 = S$ ), move toward T along the straight line segment (S,T) until one of the following happens:


- (a) T is reached; flag success and exit.
- (b) An obstacle is encountered and a new hit point  $H_i$  is defined; go to step 2.

2. Using the accepted local direction, follow the obstacle boundary. If during this process T is reached, flag success and exit. While traversing the boundary, store the coordinates of the current point  $Q_m$  located the closest to T. After traversing the whole boundary (and returning to  $H_i$ ), define a new

$Q_m$  on the obstacle boundary at which the distance to T is a minimum; R2 integrates the length of the obstacle boundary starting at  $H_i$ ; R3 integrates the length of the boundary starting at  $Q_m$ . The smaller of the values in R2 and R3 determines which direction to turn for the shortest return path to  $Q_m$  from  $H_i$ .

The Bug 1 algorithm will also function if the robot knows the direction and range to T. By storing the minimum distance  $D_m$  of the current point instead of the absolute coordinates, the robot can then compare its current distance to T with that stored in R1. Figure 2 shows the path a robot programmed with the BUG 1 would follow. The robot begins at S and goes straight toward T until it hits the first obstacle at  $H_1$ . Arbitrarily, this

**FIGURE 3B. BUG 2 PATH IN A MAZE.**

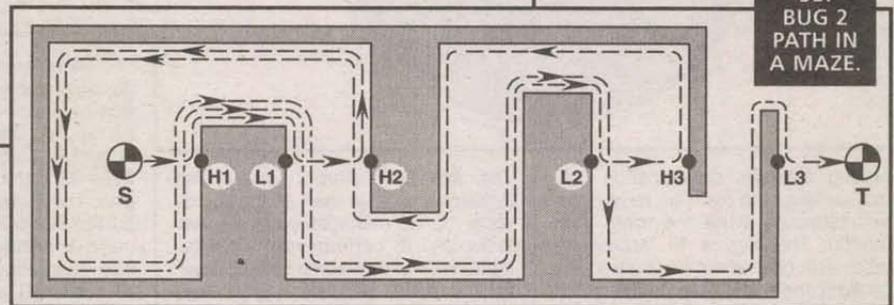

leave point  $L_i = Q_m$  and go to step 3.

3. If the straight line segment between  $L_i$  and T crosses the obstacle at point  $L_i$ , stop because the target is completely enclosed by the obstacle and is thus unreachable; flag failure and exit. Otherwise, follow the shorter path along the boundary back to  $L_i$ , set  $i=i+1$ , and go to step 1.

The Bug 1 algorithm should be executed at every point along a continuous path. The procedure can be implemented with only three registers: R1, R2, and R3 to store intermediate information between hit points. When a new hit point is reached, all three are reset to zero. R1 holds the current X, Y coordinates of the point

robot is a left local direction robot, which means that it turns left each time it encounters an obstacle. Following the BUG 1 algorithm, it circumnavigates Obstacle 1, all the while keeping track of how far around the perimeter it has come, how far it currently is from T, and how far it has come from  $Q_m$ , the most recent closest point to T.

Once it reaches  $H_1$ , it then compares the total perimeter distance with the distance travelled since the point  $Q_m$  ( $L_1$ ) is closest to T. In this case, the shortest distance between  $H_1$  to  $L_1$  is in the clockwise direction, so the robot continues on its path around the obstacle until it reaches  $L_1$ , then it makes another attempt to

ABC ELECTRONICS 315 7TH AVE N. MPLS. MN. 55401  
(612)332-2378 FAX (612)332-8481 E-MAILSURP1@VISI.COM  
WE BUY TEST EQUIPMENT AND COMPONENTS.  
VISIT US ON THE WEB AT WWW.ABCTEST.COM

HP 54501A 100MHZ DIGITIZING SCOPE	\$1300.00	HP 4935A TRANS IMPAIRMENT TEST SET	\$900.00
HP 54201D 300MHZ DIGITIZING SCOPE	\$1000.00	HP 5006A SIGNATURE ANALYZER	\$150.00
HP 54201A 300MHZ DIGITIZING SCOPE	\$1000.00	HP 86602B 1MHZ-1300MHZ RF PLUG	\$400.00
HP 54200A 50MHZ SCOPE/WAVEFORM ANALYZER	\$700.00	EIP 575 MICROWAVE COUNTER	\$1500.00
HP 3312A 13MHZ FUNCTION GENERATOR	\$250.00	FLUKE 95 50MHZ SCOPEMETER	\$550.00
HP 5370A 100MHZ U.T.I. COUNTER	\$400.00	LECROY 7200 400MHZ O-SCOPE	\$1000.00
HP 3586C LEVEL METER	\$750.00	TEK 475 200MHZ O-SCOPE	\$500.00
HP 436A POWER METER W/O SENSOR&CABLE	\$500.00	TEK 465 100MHZ O-SCOPE	\$400.00
HP R350B SWEEP OSCILLATOR MAINFRAME	\$2000.00	TEK 496P 1KHZ-1.8GHZ SPEC ANALYZER	\$3500.00
HP 3437A 3 SDIGIT SYSTEM VOLT METER	\$250.00	TEK 1240 LOGIC ANALYZER	\$750.00
HP 3455A DIGITAL MULTIMETER	\$250.00	TEK TDS320 100MHZ DIGITAL O-SCOPE	\$1400.00
HP 3456A DIGITAL MULTIMETER	\$400.00	TEK 11401A 500MHZ PROG O-SCOPE FRAME	\$750.00
HP 3336C SYNTHESIZER/LEVEL GENERATOR	\$800.00	TEK 7854 400MHZ OSCILLOSCOPE FRAME	\$500.00
HP 3325A SYNTHESIZER/FUNCTION GENERATOR	\$1000.00	TEK 7904 400MHZ OSCILLOSCOPE FRAME	\$250.00
HP 5335A 200MHZ COUNTER	\$600.00	TEK 7A26 200MHZ VERTICAL PLUG	\$75.00
HP 8165A PROGRAMMABLE SIGNAL SOURCE	\$1100.00	TEK 7A24 400MHZ VERTICAL PLUG	\$150.00
HP R558B181 100K-1500MHZ SPECTRUM ANALYZER	\$1000.00	TEK 7B80 400MHZ TIME BASE	\$75.00
HP R559B183 10MHZ-21GHZ SPECTRUM ANALYZER	\$3000.00	TEK 7B92A 500MHZ DUAL TIME BASE	\$125.00
HP 1790A 100MHZ OSCILLOSCOPE	\$250.00	TEK 7S12 SAMPLING PLUG	\$250.00
HP 6034A 60VDC-10A POWER SUPPLY	\$750.00	TEK 7L14 10KHZ-1.8GHZ SPEC. ANALYZER	\$1000.00
HP 6269B 40VDC-50A POWER SUPPLY	\$800.00	TEK AMS03 CURRENT PROBE AMPLIFIER	\$250.00
HP 6553A 40VDC-12.5A POWER SUPPLY OPT J01	\$1200.00	WAVETEK 145 20MHZ PULSE/FUNCTION GEN.	\$400.00
HP 6632A 20VDC-5A POWER SUPPLY	\$500.00	WAVETEK 182A 4MHZ FUNCTION GEN.	\$150.00
HP 6648A 45VDC-4.3A POWER SUPPLY OPT J03	\$750.00	WAVETEK 955 7.5-12.4GHZ MICROSOURCE	\$1100.00

## ❖ ATTENTION CABLE VIEWERS ❖

CABLE VIEWERS... get back to your **BASIC** Cable Needs

Call 1-800-577-8775

For information regarding all of your **BASIC** cable needs.

5 GOOD REASONS TO BUY OUR FAR SUPERIOR PRODUCT

- ❖ PRICE
- ❖ EFFICIENT SALES AND SERVICE
- ❖ WE SPECIALIZE IN 5, 10 LOT PRICING
- ❖ ALL FUNCTIONS (COMPATIBLE WITH ALL MAJOR BRANDS)
- ❖ **ANY SIZE** ORDER FILLED WITH SAME DAY SHIPPING

We handle **NEW** equipment **ONLY** - Don't trust last years **OBSOLETE** and **UNSOLD** stock!  
COMPETITIVE PRICING - DEALERS WELCOME



**BASIC**  
**ELECTRICAL**  
**SUPPLY &**  
**WAREHOUSING**  
**CORPORATION**

P.O. BOX 8180 · BARTLETT, IL 60103-8180 · 847-584-2099

go straight toward T.

If obstacle 2 were not in the way, it would be home free, but it collides with the second obstacle at H2 and the whole process repeats. In this case, however, once the robot has circumnavigated the obstacle perimeter, the shorter distance from H2 to L2 is in the counterclockwise direction, so the robot turns around to go that way. Once at L2, it again resumes a straight line path toward T, which it will reach with no further difficulty.

In the worst case, the robot will have to travel 1.5 times the perimeter of each obstacle before resuming its travel toward the target point. This may seem wasteful, but BUG 1 assumes no prior knowledge about the obstacles that might be encountered. BUG 1 could work very well in conjunction with a separate algorithm that creates an occupancy grid map of the environment so that the next time a particular obstacle is encountered, a more efficient route around it can be picked (but that's a topic for another column).

A less conservative algorithm would not require a complete circumnavigation of every obstacle. For simple, mostly convex obstacles, BUG 2 can usually produce more efficient paths than BUG 1 (see Figure 3).

## BUG 2

1. From point Li-1 (with  $L0 = S$ ), move toward T along the straight line segment (S,T) until one of the following happens:

(a) T is reached; flag success and exit.

(b) An obstacle is encountered and a new hit point Hi is defined; go to step 2.

2. Using the accepted local direction, follow the obstacle boundary until:

(a) T is reached; flag success and exit.

(b) The robot crosses line segment (S,T) at Qm where the distance Dq from Qm to T is less than the distance from Hi to T, and the line segment (Qm,T) does not cross the current obstacle at the point Qm. Define leave point Li=Qm, set  $i=i+1$ , and go to step 1.

(c) The robot completes the boundary traversal and returns to Hi without having defined the next leave point Li; flag failure and exit because

the obstacle boundary completely encloses T.

Again, I've arbitrarily chosen a left local direction for the robot. Notice how much shorter the path is for the robot when it encounters the first obstacle at H1. Even a right local direction robot, which would follow the perimeter of obstacle 1 in a counterclockwise direction, would still have a shorter total path than the BUG 1 algorithm could produce. With the second obstacle, it's a toss-up which direction would be better, but either would still be shorter than the BUG 1 path.

Both the BUG 1 and BUG 2 algorithms are guaranteed to find a path if one exists, though it's important to remember that the path may be quite long. Bug 2 is a bit less conservative than Bug 1 and will often give shorter total paths, but note that Bug 2 is especially poor at handling mazes (see Figure 3b). Both algorithms are at their best when dealing with simple convex obstacles. Both algorithms put a premium on the robot knowing where it is and how far it has come, so accurate odometry and straight-line motion control are essential.

## What's all this Navigation stuff?

This takes us right to the leading edge of robotics and beyond. Rather than attempt to formulate some all-inclusive (and impractical) definition of the autonomous navigation problem, I'll break it down into a hierarchy of subproblems (see Figure 4).

There is no one "navigation problem" just as there is no one "problem of driving to LA." For a robot driving to Los Angeles, there are a variety of problems to be overcome in different phases and at different scales.

In order for a robot to find its way from a start position to a target position, it must plan the path to take and it does this by using a software agent called a Path Planner. If the robot starts in Seattle, the path plan it would use to get to LA could be "drive south on Interstate 5 until you get to LA." Driving from Boston, the plan would be slightly more complicated: "Go west on I90 until you reach Seattle; at Seattle go south on I5 until you reach LA."

These are both examples of glob-

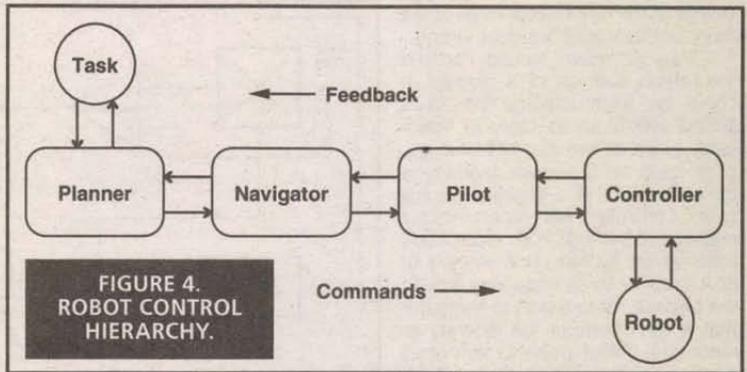


FIGURE 4. ROBOT CONTROL HIERARCHY.

al path planning. By global, I don't mean paths must be a thousand miles long to qualify, but that the Planner agent is concerned only with the "big picture." Details about freeway entrances and exits, traffic signals, detours, and scenery along the way are not the concern of Planner.

The path plan itself must be executed by a Navigator Agent. The Navigator is responsible for two things. The first is translating the vague path plans Planner cooks up into detailed itineraries. I'll get to the second of the Navigator's duties later.

To translate Planner's plans into viable itineraries, Navigator must be able to do some planning of its own, though of a more local nature. Local plans deal with the immediately perceivable environment and unfold sequentially.

## How far is LA?

Our Bostonian robot on the road to LA would have a local planning area as far as it could see, which might be as little as half a block in downtown Boston, or as much as 20 miles to the horizon in South Dakota. A robot exploring the asteroid belt would still be doing local path planning as long as those paths remain within the range of its radar, the limits of its perception. Local planning for a robot with nothing but bumpers for sensors (as with the Lumelsky Bugs) would operate within the area defined

by the reach of those bumpers.

Navigator decomposes the global path plan into a series of local path plans. Navigator would translate the Seattle/LA drive into something like "drive one mile west on Northgate Way, turn right at the southbound I5 entrance, merge into traffic, drive south; every 350 miles or so stop to gas up and charge batteries, until you reach LA."

Navigator will turn this itinerary over to another agent called Pilot to do the actual driving. Pilot is responsible for generating and executing point-to-point trajectories, for local obstacle avoidance, and for sensing "free space" (that is the safe zone for the robot to move within). The Navigator's itinerary is still a fairly general plan, reflecting perhaps that our robot has never been further south than Portland, but it's enough for Pilot to do its job.

Pilot assumes the robot is ideal, that it accepts drive and steer commands, and returns position and heading without error. Real robots come in a variety of mechanical configurations, so a lower-level agent is needed to translate Pilot's universal robot commands into the actual actuator velocities and positions. This agent is known as Controller. Controller isolates the rest of the command chain from the specific details of making the robot perform as commanded. Pilot gives commands and Controller makes it so. Controller is in

**Equipment Management Technology**  
From Acquisition to Disposition

**BUY \* RENT \* SELL**  
Quality  
Test and Measurement Equipment

We inventory HP, Tektronix, Fluke, Anritsu, Wiltron, Iwatsu, Wavetek, GenRad and many other manufacturers. Our product lines include RF & microwave, oscilloscopes, generators, supplies, communications, voltage and frequency standards. Call us now for a quote!

Tel 650-631-1700 \* Fax 650-631-1200 \* email sales@emt1.com

**Weeder Technologies** ON-LINE CATALOG **Pro-Kit**  
www.weedtech.com

PO Box 2426, Ft. Walton Beach, FL 32549 Voice/Fax 850-863-5723

<p><b>Stackable RS-232 Kits</b></p> <p>Digital I/O - 12 I/O pins individually configurable for input or output. DIP switch addressable; stack up to 16 modules on same port for 192 I/O points. Turn on/off relays. Sense switch transitions, button presses, 4x4 matrix decoding using auto-debounce and repeat. <b>\$32</b></p> <p>Analog Input - 8 input pins. 12-bit plus sign self-calibrating ADC. Returns results in 1mV steps from 0 to 4095. Software programmable alarm trip-points for each input. DIP switch addressable; stack up to 16 modules on same port for 128 single-ended or 64 differential inputs. <b>\$49</b></p> <p>Home Automation (X-10) - Connects between a TW523 and your serial port. Receive/transmit all X-10 commands with your home-brewed programs. Full collision detection with auto re-transmission. <b>\$39</b></p> <p>Caller ID - Decodes the caller ID data and sends it to your serial port in a pre-formatted ASCII character string. Example: "12/31 08:45 850-863-5723 Weeder, Terry &lt;CR&gt;". Keep a log of all incoming calls. Block out unwanted callers to your BBS or other modem applications. <b>\$35</b></p> <p>Touch-Tone Input - Decodes DTMF tones and sends them to your serial port. Keep a log of all outgoing calls. Use with the Caller ID kit for a complete in/out logging system. Send commands to the Home Automation and/or Digital I/O kits using a remote telephone. <b>\$34</b></p>	<p><b>Phone Line Transponder</b></p> <p>7 individual output pins are controlled with buttons 1-7 on your touch-tone phone. Automatically answers telephone and waits for commands. Monitor room noises with built in mic. "Dial-Out" pin instructs unit to pick up phone and dial user entered number(s). Password protected. <b>\$49</b></p>
<p><b>IR Remote Control Receiver</b></p> <p>Learns and responds to the data patterns emitted by standard infrared remote controls used by TVs, VCRs, Stereos, etc. Lets you control all your electronic projects with your TV remote. 7 individual output pins can be assigned to any button on your remote, and can be configured for either "toggle" or "momentary" action. <b>\$32</b></p>	<p><b>DTMF Decoder/Logger</b></p> <p>Keep track of all numbers dialed or entered from any phone on your line. Decodes all touch-tones and displays them on a 16 character LCD. Holds the last 240 digits in non-volatile memory. Connect directly to radio receiver's speaker terminals for off-air decoding of repeater codes, or numbers dialed on a radio program. <b>\$55</b></p>
<p><b>Telephone Call Restrictors</b></p> <p>Two modes of operation; either prevent receiving or placing telephone calls (or call prefixes) which have been entered into memory, or prevent those calls (or call prefixes) which have "not" been entered into memory. Use touch-tone phone to program.</p> <p>Block out selected outgoing calls. Bypass at any time using your password. <b>\$35</b></p> <p>Block out selected incoming calls. Calls identified using Caller ID data. <b>\$46</b></p>	

charge of the robot's actions all of the time. Unless something goes wrong.

Suppose down around Portland the robot's path on I5 is blocked. It could be from construction or a stalled vehicle in its lane, in which case, a lane or two may still be open, or it could be the whole highway is closed because of a landslide. In any case, Controller will report sensor readings deviating from acceptable limits as set by Pilot. It is the job of Pilot to either try to find a way around the obstacle, or to report to Navigator that it can't perform the itinerary as requested. If Pilot is able to shift lanes on its own, then all is well. But if the obstacle is more extensive (the landslide), then Pilot will report failure to Navigator.

At this point, Navigator must adjust its itinerary. Navigator might be able to choose another route visible locally, perhaps following detour signs. This is the second capability Navigator should have, that of mapping its surroundings, determining position, and recognizing features of interest. Of all robotics AI topics, this is the most difficult and in need of the most research because this is where idealized planning collides with the real world.

Supposing Navigator fails to find an alternate local route, then Navigator must, in turn, report failure to Planner. Planner would then create a new global path plan that takes the new obstacle into consideration (perhaps it would divert to I405).

## The Chain of Command

At each level in the hierarchy from Planner to Navigator to Pilot to Controller, commands from the agent above and status information from the agent below control the behavior of that particular agent. There are many fine algorithms available to implement Planner, as well as Pilot and Controller.

The BUG 1 and BUG 2 algorithms address the purely local problem of obstacle avoidance; they are therefore properly Pilot-level algorithms. The

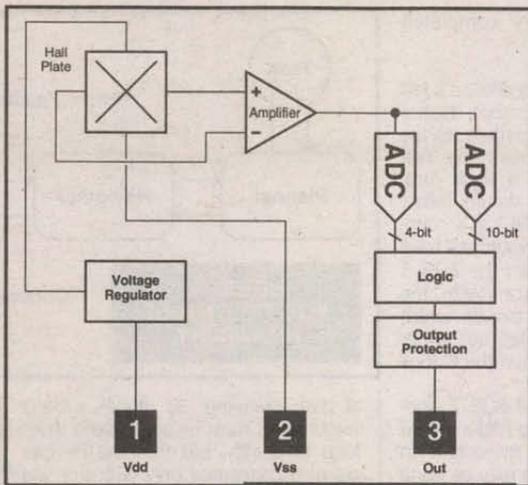


FIGURE 5. MLX90217 HALL-EFFECT GEAR TOOTH SENSOR.

general autonomous navigation problem involves issues of sensor processing, local path planning, position resolution, and error recovery, which are all the domain of Navigator.

Navigator is the tough nut to crack. Creating software that can perform all the functions required of the Navigator agent is an on-going research problem in universities around the world. My goal for this year is to demonstrate some of the simpler algorithms already out there.

## Another Turn of the Wheel

Okay, I'm just about out of space, but I promised I would talk about an alternative to optical encoders. The "part of the month" is the Melexis MLX90217, a Hall-Effect gear tooth Sensor (Figures 5 and 6).

The MLX90217 is a digital output gear tooth position sensor designed for automotive camshaft sensing, as well as sensing gear teeth. It's designed to be used with a bias magnet as shown in Figure 6 with the south pole facing the back of the sensor (if you put the magnet the other

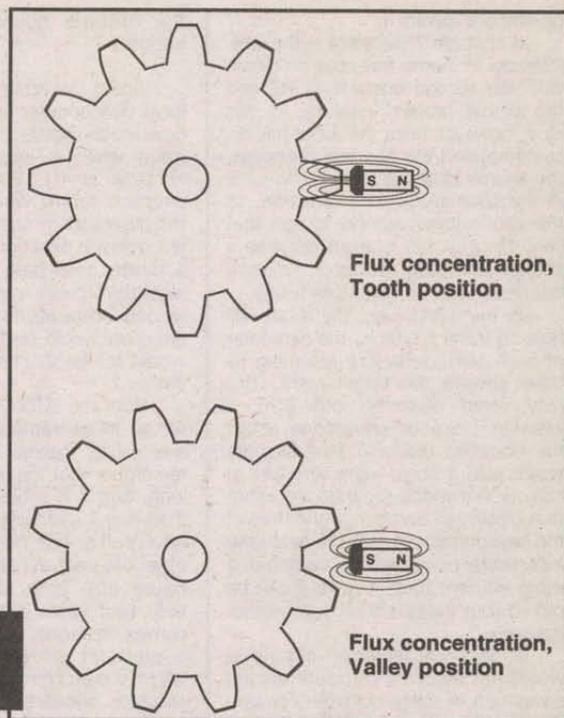


FIGURE 6. HALL-EFFECT GEAR TOOTH SENSOR.

way, the part goes into a special test mode).

The nifty thing about this part is that it has an on-chip 10-bit A/D converter and logic that acts as a digital sample and hold. A separate four-bit converter provides a fixed amount of hysteresis. The output will turn ON after the magnetic flux has reached its peak and has decreased by the amount equal to the hysteresis; likewise, the output will turn OFF after the flux has reached a minimum and increased by the hysteresis amount. This makes for a nice, clean signal even when individual gear tooth profiles are worn, a sort of Schmitt Trigger for magnetic flux.

This baby comes in a three-pin, TO-92-size package (a bit slimmer, actually), and will run from a wide voltage supply range, 3.5 to 24V. At 12V, it draws 3 mA. The bandwidth of the chip is 15 KHz. How would you use

this chip? Well, the output gear on one popular Dayton gear motor is a 67-tooth steel gear. There's plenty of space inside the metal gear box to put a couple of these sensors, along with their bias magnets and, with a little logic or software, they would provide  $67 \times 4 = 268$  counts per revolution, along with direction information. This would be a very rugged setup, one I intend to try soon. The MLX90217 is \$5.13 each in 10 pc. quantities, and \$2.33 each in 100 pc. quantities, three weeks ARO from the factory.

## Next Time

I'll get back to that promised SIMMStick brain transplant, try out simple encoders for Breadbot's wheels, and review a new robot kit. Until then, keep your soldering irons warm. This is going to be a heckuva year. NV



### ROOM GUARDIAN™ ALARM

The Room Guardian™ Alarm features advanced microprocessor controlled circuitry to protect your home or office. This unit is able to detect intruders using Passive Infrared Motion (PIR) detection and intrasonic forced entry detection. The PIR sensor has a 30 foot, 360° range. The intrasonic sensor detects shock waves produced by an intruder breaking a window or forcing entry through a door, etc. When the unit detects an intruder, it activates its loud (100-decibel) built in alarm for 30 seconds. The unit is armed by a handheld (keychain) infrared remote control. The remote has approximately a 30 ft. range of operation. In addition, a 4 position dip switch on the remote and a 4 position dip switch in the alarm can be used to create a custom "electronic address" for your unit (there are 16 combinations possible). There are three indicator LEDs on the top of the unit. The Yellow LED indicates low battery/test mode, the Red LED indicates arm/disarm status, and the Green LED indicates AC power. This unit operates from a 9VDC AC adapter (included) or a 9-volt battery (not included). Size of Room Guardian™ Alarm: 4 1/16" x 3 1/16" x 1 3/8". Brand new in retail box with complete instructions.

G9884 \$14.95 ea.

Sale \$8.95 ea.

SALE

G9884 \$14.95 ea.

### ULTRA HEAVY DUTY BUHLER MOTOR

This heavy duty high torque motor can power a large robot platform. Its body size is about 3 5/8" L x 1 7/8" Dia. with a 7/32" Dia. shaft. The shaft protrudes 1 1/8" on one end and it protrudes 3/8" on the other end. Rated for 24VDC, however it works fine on 12VDC. Prime Buhler quality - made in Germany. Part #147-0070-01. Brand new! Worth many times our blowout price.

G9934 \$6.95 ea.

NEW

G9934 \$6.95 ea.

### HEAVY DUTY MOTOR WITH TACH DISK

Heavy duty motor with optical speed tach disk features a 1 1/4" long 3/16" Dia. shaft. Overall body size is about 4" L x 1 1/2" Dia. with a 2 5/16" Dia. optical encoding unit attached to one end. Operates from 6VDC up to 24VDC. New made by SHIHANO KENSHI Co LTD of JAPAN. Model DX058-018. Has 4 wires for the optical encoder and 2 wires for the motor.

G9933 \$3.95 ea.

### HEAVY DUTY MOTOR WITH TACH DISK

This is similar to the G9933 motor however it has a body length of 3 5/8" L x 1 1/2" Dia. and a 3/16" Dia. "D" shaft about 1/2" L. Operates from 6VDC up to 24VDC. This motor has a smaller optical encoder disk compartment and therefore is more compact than the G9933 motor. Has 4 wires for the tach encoder and of course 2 wires for the motor.

G9932 \$4.25 ea.

NEW



### MINI TV CAMERA AND LENS

Tiny digital camera board complete with a Chinon KL-120 lens. These are small 1 5/16" x 1 1/8" imager PCA Model TV04 TV cameras that have an eleven pin connector for hookup. We do know that the board was designed to operate from 12VDC, however except for that fact we have no schematics, hookup info, or data on these. Units are brand new and come packed with the lens in a box. Note that the lens was not designed to attach to the board but it was designed to go into some case that the board mounted to. Very high quality items—no rejects or used. If you can figure them out you'll save a bundle! The lens alone is worth more than our price for the set.

G9913 \$21.95 ea. or 5 for \$99.00

### KODAK GIANT IR FILTER

Type 87C by Kodak Wratten gelatin filter is 75mm square and black in color. Restricts visible light but allows IR energy to pass. Great for making large IR illuminators, IR light sources, IR vision applications etc. New in foil sealed Kodak envelopes.

G9935 \$3.49 ea. 10 for \$32.00

### LTE-2872 JUMBO HIGH OUTPUT INFRARED (IR) LED

TI 3/4 jumbo water clear case IR LED features a narrow 16° viewing angle and high (12mWsr) output. Wavelength is 940nm. Vt typical is 1.2V@20ma. Great for IR projects where you need a small diameter intense IR energy source. Prime, first quality units with long leads.

G8312 5/\$1.00 100/\$18.00 1,000/\$150.00

### OMRON MAG STRIPE CARD READER

Brand new credit card reader by OMRON type 3S4YR-HSR4.01. These are only 4" L x 1 1/16" X 1 1/8". We have no info/schematics except that we do know they operate on 5VDC and have a 5 lead ribbon cable connected to the circuit board. Check the Nov. issue of Nuts and Volts for an interesting article about interfacing a magnetic stripe reader (however it was not an OMRON). Prime, but no data!

G9937 \$5.95 ea.

WE ALSO OFFER OVER 150 DIFFERENT ELECTRONIC KITS.

**ELECTRONIC GOLDMINE**  
PO Box 5408  
Scottsdale, AZ 85261

<http://www.goldmine-elec.com>

NOTE: All items subject to prior sale. All prices expire 2-31-99

For Phone Orders Call: 800-445-0697  
or Fax Your Orders to: (602) 661-8259  
For a Free Catalog Call: (602) 451-7454  
Foreign catalog request: send \$5.00

Minimum Order: \$10 (plus min. \$5 Shipping and Handling). We accept MasterCard, Visa and personal checks, however, we cannot accept personal checks on orders outside the U.S. Minimum Foreign Order Amount: \$50 (plus a minimum \$10 S&H)

**HEAVY DUTY DC AIR PUMP**  
Made by VDO of Germany for ASF Thomas Company. Part # 70120012. These are about 4 1/2" L x 3" H black enclosed case air pump. The outlet fitting has a removable protective cap and is designed for 1/4" dia. hoses. Operates from about 12VDC up to 30VDC but is designed for 24VDC. Very nice precision made unit. Brand new Prime!

G9927 \$8.95 ea.

**BOURNS 10 TURN PRECISION 5K POT**  
Linear taper type 3540S-1502 features 5K resistance and linearity of ±0.25%. Has standard 3/8" bushing and panel mounting nut. Shaft is 1/2" long and 1/4" diameter. Prime Bourns quality.

G9936 \$3.95 ea.

## Lowest Dealer Price Available

	5+	10+	20+
Refurb. Panasonic 145	\$45	\$40	\$35
Panasonic 175	\$70	\$68	\$65
Regal w/Remote	\$38	\$35	\$30
BC4535 86 Channel	\$30	\$28	\$25
Oak Sigma 99 Channel	\$45	\$40	\$35
75 Channel Converter	\$18	\$18	\$18
Zenith ST1600 w/Remote	\$75	\$70	\$65

Call us today to satisfy all your cable equipment needs!

## SAM'S ELECTRONICS

### 1-405-631-1856

All Cable Equipment is unmodified.

## HAM GEAR FOR SALE

**WANTED: ROCKWELL-Collins HF-80** equipment, 851S-1, 237B-3 log periodic, Collins literature. Jim Stitzinger 805-259-2011, 805-259-3830 (fax), bfl-jfs@smartlink.net

**HAM EQUIPMENT** repair or overhaul Collins, Drake, Swan, Astro, Yaesu, Kenwood, etc. 20 years experience with former Slep Electronics Co. Same excellent service, same reasonable rates, satisfaction guaranteed. Brooks Electronics, 828-349-3503. E-Mail: rwbrooks@dnet.net

**MILITARY COMPONENTS** wanted. Capacitors, resistors, diodes, transistors, semiconductors, ICs. Electronic Material Industries, 818-769-1002, FAX: 818-769-1084.



**CELLWAVE 4** channel cavity, ferrite transmitter combiners. 870MHz combiners will tune down to 860MHz. Cellwave model no. 505980. Dimensions: 13x18x13 inches. Weight: 50 lbs. \$300. Cellwave power monitor ZRB101 with DSG-2 sensor \$150. Test Equipment, 1412 S. Central Park Ave. #D, Anaheim, CA 92802. 714-778-5151. Fax 714-778-0312.

**LML RADIO UHF GRMS** repeater 15W programmable 256 channels \$120. 2 meter mobile amp 60 watt \$30, Harris HF receiver \$150. Free catalog 909-873-1319. Fax on demand 24 hr. 909-820-1885. Web catalog <http://members.aol.com/hrh6> Write 424 E. Shamrock, Rialto, CA 92376.

**NEW PRODUCTS FROM S & S: UPGRADE YOUR OLD RIGS!** Digital dial (counter) has 10Hz resolution HF, 100Hz VHF and frequency range 50KHz to 230MHz; kit \$99.95; assembled \$149.95. **NEW Digital VFO** with 1Hz resolution to 54MHz; kit \$169.95; assembled \$219.95. S&S \$7 (Continental US). **GUARANTEED TO WORK.** For info send **SASE.** Call/write to order: S & S Engineering, 14102 Brown Rd., Smithsburg, MD 21783. 301-416-0661, E-Mail: N3SAD@aol.com or see <http://www.xmetric.com/sseng>

**KB6KQ ANTENNAS:** Antennas for 10M, 6M, 2M, 222 & 432 MHz. Mobil, base and CC & R applications. Need custom mast-ing? Call Norm at 702-885-7885.

**POWER SUPPLIES** Pyramid, simply the best durable power supply on the market for value! Ideal for radio use, amps, or bench work. 13.8 VDC from 3 amps to 52 amps available with surge protection. Some models available with cigarette plug socket. Factory packed in retail display boxes. All come factory new with one year warranty. Lowest prices on any quantity. Wholesale/distributors welcome. Gentry Communications 507-332-2788.

**KK4JK NEEDS** to sell Ten-Tec, Mini D transceiver. Not used after factory refurbish. Paid \$800, sell for \$475. Wife ill. 803-534-6868.

## HAM GEAR WANTED

**MILITARY COMPONENTS** wanted. Capacitors, resistors, diodes, transistors, semiconductors, ICs. Electronic Material Industries, 818-769-1002, FAX: 818-769-1084.

## CB - SCANNERS

**SALES, SERVICE:** CB equipment, radios, modifications, power mice, echo-verb boxes, kits, meters, filters, antennas, noise toys, mounts, hard-to-find items. Partial list \$1, complete list \$4. D&R Electronics, 10 Park St., Thomaston, CT 06787. 860-283-9492.



**ULTIMATE MODIFICATION BIBLE.** Mind boggling is the only way to describe this 220 page book. Modification of CBs, channels, power, sliders, talk back and more. 10 meter radios, HAM RADIO, scanners, toys, meters, and more. Only \$29.95 + \$3.25 shipping. Phone orders 1-800-256-9895 (MC-Disc-Visa) No CODs.

**"CB MODIFICATION SECRETS,"** new 200-page guide by author of "CB Radio Hacker's Guide." More easy AM/SSB CB upgrades & enhancements: Cobra, Realistic, Uniden, President, etc. Freq. expansion, VFO, clarifier unlock, VOX, Roger Beep, anti-theft device, receive preamp, more. Only \$21.95, plus \$5 S/H (\$7 to Canada). CRB Research, Box 56, Comstock, NY 11725. NYS res. add \$2.22 tax. Visa/MC orders call: 516-543-9169.


# Digital Storage Oscilloscopes

From \$189?

ATC modules connect to your PC printer port and transform it into a full-function DSO, spectrum analyzer, logger, & DVM. Units DC to 25MHz



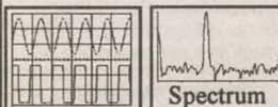Captured Waveforms  
Pico Tech  
ADC-200 in  
Windows



O-Scope II  
in DOS



ATC proudly announces the addition of Pico Technology Ltd. products to our product line. Pico is based in Britain and offers a variety of data logging and virtual instrument modules.



**O-Scope Ip (ST 50KHz).....\$189**  
**O-Scope II (DT 500KHz).....\$349**  
**ADC-100 (DT 12bit 50KHz)..... \$449**  
**ADC-200/20 (DT 10MHz).....**  
**ADC-200/50 (DT 25MHz).....**

**CALL**


Loggers 1-22 ch. (8-16 bit) from \$99  
Shipping UPS \$7.50 grnd, \$11.50 (2 day)

**800-980-9806**  
**Allison Technology Corporation**  
2006 Finney Valley Rd., Rosenberg, TX 77471  
Fax: 281-239-8006 Technical: 281-239-8500  
E-Mail: [atc@accesscomm.net](mailto:atc@accesscomm.net)  
<http://www.atcweb.com>

## Turn Your Multimedia PC into a Powerful Real-Time Audio Spectrum Analyzer
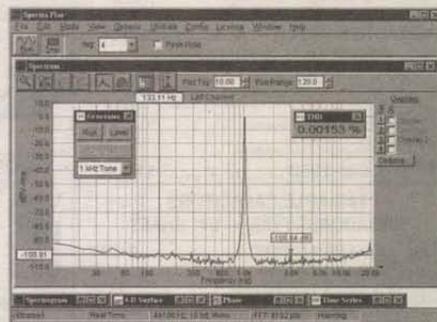
### Features

- 20 kHz real-time bandwidth
- Fast 32 bit executable
- Dual channel analysis
- High Resolution FFT
- Octave Analysis
- THD, THD+N, SNR measurements
- Signal Generation
- Triggering, Decimation
- Transfer Functions, Coherence
- Time Series, Spectrum Phase, and 3-D Surface plots
- Real-Time Recording and Post-Processing modes



### Applications

- Distortion Analysis
- Frequency Response Testing
- Vibration Measurements
- Acoustic Research

### System Requirements

- 486 CPU or greater
- 8 MB RAM minimum
- Win. 95, NT, or Win. 3.1 + Win.32s
- Mouse and Math coprocessor
- 16 bit sound card

**Priced from \$299**

(U.S. sales only - not for export/resale)

**DOWNLOAD FREE 30 DAY TRIAL!**

[www.spectraplus.com](http://www.spectraplus.com)

**PHS** Pioneer Hill Software  
24460 Mason Rd.  
Poulsbo, WA 98370

a subsidiary of Sound Technology, Inc.

Sales: (360) 697-3472

Fax: (360) 697-7717

e-mail: [pioneer@telebyte.com](mailto:pioneer@telebyte.com)

**Spectra Plus**  
FFT Spectral Analysis System

**SCANNING USA:** monthly magazine 100% scanning. All the news and product reviews from the writers you trust. Get more from your scanner. Subscriptions \$24.95, samples \$3. Call 1-800-651-0922 your Visa or MasterCard, or write 2054 Hawthorne, Joliet, IL 60435

**ANTRON 101 CB 10 METER** base station antenna with isolation network, no bleedover, no splatter, no TVI tuning sleeve technology 3 piece fiberglass \$69.99. **Twin-Tronics, Inc.** PO Box 2571, Youngstown, OH 44507-0571. Send \$1 for literature, refundable. Ph 330-788-9693. Fax 330-788-7709.

**CB RADIO EQUIPMENT:** Selling all kinds of equipment! For details E-Mail: [rushead1@juno.com](mailto:rushead1@juno.com)

**KONNEX DISTRIBUTING.** Call 1-888-777-7874. PO Box 451372, Los Angeles, CA 90045. CBs, antennas, meters, transistors. Best prices. Credit card acceptable.

**CB MODIFICATIONS!** Frequencies, books, kits, high-performance accessories, plans, repairs, amplifiers, 10-meter conversions. The best since 1976! Catalog \$3. CBCI, Box 1898NV, Monterey, CA 93942. [www.cbciint.com](http://www.cbciint.com)

**240+ CHANNEL CB/HAM/COMMERCIAL** radios: AM/FM/SSB/CW export/domestic: RCI, Motorola, Uniden, Cobra, Alinco, Kenwood. Mics, antennas, linears, meters, books, night scopes, and tons more stuff! Catalog \$3. MAXTECH, Box 8086, New York, NY 10150. 718-547-8244.

**SUPERSTAR, GALAXY, Mirage, Uniden, Cobra, microphones, power supplies, scanners hard-to-find products, picture price sheets.** \$1 to cover postage (REFUNDABLE). Galaxy, Box 1202, Akron, OH 44309. Over 10 yrs. in business.

## MUSIC & ACCESSORIES

**FOR SALE:** Military H-251-U headsets new \$15 ea. 10 or more \$12.50. Steve Bartkowski 708-863-3090.


## COMPUTER HARDWARE

**START YOUR OWN TECHNICAL VENTURE!** Don Lancaster's newly updated **INCREDIBLE SECRET MONEY MACHINE II** tells how. We now have autographed copies of the Guru's underground classic for \$18.50. Synergetics Press, Box 809-K, Thatcher, AZ 85552. 520-428-4073. VISA/MC.

**WE CARRY** a variety of cables, switch boxes, accessories, and adapters to connect PCs, printers, Mac's, networks, telecommunications, and audio/video equipment. We offer: custom cables, free catalogs, and same day shipping on most orders. Visit our website at [www.rogerssystems.com](http://www.rogerssystems.com) or call 1-800-366-0579.

**CRTs CHEAP.** Buy direct from the manufacturer. Save money. Mfg. all CRT types since 1950. **3 year warranty.** Reg-Flex 19" tubes \$75; 25" \$100; hi-res 13" tubes from \$80. We specialize in **hi-resolution video/computer CRTs.** T.M.C. 215-226-0749/215-223-0388.
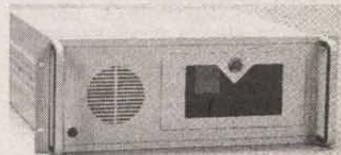
<http://www.pccables.com> **PC CABLES and PARTS.** 100s of hard-to-find new cables and parts, free technical information, low prices, fast online ordering & browsing.



**19" RACKMOUNT PC chassis:** Heavy duty, 4U, for standard 7 slots ATX motherboard. Optional 8, 12, 14 slots back panels available. Four (three hidden) 3.5"/two 5.25" drive bays, 4.625" front panel fan, power supply not included, \$189 with this ad! Monitor chassis \$269, keyboard chassis \$139. 8255-8253 I/O card with prototyping area \$69, 12-bit ADDA card \$89. **Computronics Technology, 972-242-8087.**

**LOOKING FOR cheap clone PC parts that actually work?** Call UTWE for CD-ROMs, hard drives, disk controllers, video cards, mainboards CPUs, etc. For example, **NEW Clone-o-matic mainboard** with 4 PCI, 3 ISA, 256K cache, I/O built on board with 200MHz AMD \$90, 2 meg PCI S3 video board \$20. 486 "all in one" mainboard (video and IDE I/O) \$35 ea. Multitech V90 56K flex modem internal \$30. Remember, today we have, tomorrow we don't! For all the latest deal sheets E-Mail: [dealsheets@utwe.com](mailto:dealsheets@utwe.com) Call 626-930-1121 (10am-5pm Pacific) or fax 626-930-1123. E-Mail: [sales@utwe.com](mailto:sales@utwe.com)

**EVERYTHING NEW w/warranty!** P300MHz MMX \$165, 1.28 gigabyte HD \$65. 15"/17" SVGA monitors \$145/235. Pentium systems from \$350. Also multimedia kits, hard drives, scanners, printers, SCSI adapters \$25. Memory, cases, etc. Call for monthly specials. CCI 714-778-0450. E-Mail: [cci@net999.com](mailto:cci@net999.com)

**P300 MHz Multimedia systems, fully loaded, liquidation \$495.** Laser printers \$175, color Inkjets \$95, Notebooks \$350, closeout prices on software. Call 714-778-0450.

**COLORADO BACKUP** tape drives, 350MB, internal, \$35; Summagraphics digitizing tablets, \$95; thermal wire stripers, \$25. 334-889-4637.

# OCEAN STATE ELECTRONICS

**CALL, WRITE OR FAX FOR OUR FREE 104 PAGE CATALOG 1-800-866-6626**

Step back into the past and build a Vintage tube type receiver or transmitter. Each kit comes with all the necessary components to get you on the air vintage radio style. A great opportunity to learn to build, troubleshoot and operate vintage tube type equipment.

### THE CAKEPANION RECEIVER KIT 2 TUBES GENERAL COVERAGE REGEN



- Receives Am, SSB, and CW
- Regenerative Receiver Design
- Uses two 6AQ5 Tubes
- Continuous coverage 500 KC - 10MHz using pre-wound plug in coils as in old fashioned regenerative receivers (Coils sold below)
- Smooth Vernier Dial Tuning (No Logging Scale)
- J fet front end isolates the antenna and adds RF gain.
- Solid frequency stability.
- Ultra sensitive reception.
- Hi Fi quality audio into 8 ohms. Enough to drive a small speaker (not included)
- Headphone Jack
- Audio clipper circuit eliminates key clicks and heavy static.
- Solid state power supply
- Complete punched and drilled chassis (tuning caps and solder lugs are pre-installed)
- Well written detailed assembly instructions include color pictorials. Manual included
- Assembly time approx. 6 hours
- Measures 9" Wide x 9" Deep x 2" High • Weight approx. 5 lbs.

ASSEMBLE A COMPLETE QRP STATION. THE CAKEPANION RECEIVER MATES PERFECTLY WITH OUR CPCW-5 TUBE TRANSMITTER

Part No.	Description	Price
CPR-1	2 Tube Receiver Kit	\$119.95
CPR-B	Broadcast Band Coil 500kHz-1800kHz	\$14.95
CPR-160	160 Meter Coil 1.5 MHz-3.0MHz	\$9.95
CPR-80	80 Meter Coil 2.9MHz-7.5MHz	\$9.95
CPR-40	40 Meter Coil 4.00MHz-10MHz	\$7.75

### DIGITAL LCR METER — ALSO MEASURES VOLTS, AMPS & FREQUENCY

At Last! An LCR meter that everyone can afford. Now you can measure coils, transformers, chokes from 1µH to 40H. Capacitors from 1 pfd to 400 mfd and resistors from 1 ohm to 40 meg ohms. DCV to 1000 V. ACV to 750V. Freq. 1Hz to 4MHz. Great price for this instrument.

LCM-1950 ..... \$79.95

### VARIABLE CAPACITORS BROADCAST TYPE — 1/4" SHAFT

- 1 GANG 14-365PF ..... \$10.95
- 2 GANG 10-400/10-400/PF ..... 19.95
- 3 GANG 15-500PF/SEC ..... 12.95

Many more types available from small air trimmers to large 4KV tuner types.

### 6146W POWER TUBE

Rugged version of popular 6146B used in many transmitters. MFG. GE

\$17.95 EA. or \$37.00 MP

12BY7A Driver ..... \$15.95

CALL US FOR ALL YOUR TUBE NEEDS.

### LEARN COMPUTER THEORY BY BUILDING THIS KIT DIGITAL TRAINER MODEL MM-8000

Starting from scratch you build a complete computer system. Our Micro-Master trainer teaches you to write into RAMs, ROMs and run a 8085 microprocessor. You will write the initial instructions to tell the 8085 processor to get started and store these instructions in permanent memory in a 2816 EPROM. Teaches you all about input and output ports, computer timers. Build your own keyboard and learn how to scan keyboard and display. No previous computer knowledge required. Simple easy to understand instruction teaches you to write in machine language. Upon completion of this course you will be proficient in computer technology.

- Uses the 8085 Microprocessor
- Uses the 2816 EPROM, electrically erasable programmable ROM
- Uses the 8156C, 2048 Bit static MOS RAM with I/O ports and timer
- Memory expandable option
- Built in 5V power supply
- 28 key keyboard
- Complete with lesson manual, instructions and experiments

All this for only ..... \$79.95

### QRP CW TRANSMITTER KIT 2 TUBES, 3 BANDS



- 3 Band CW Coverage — 160, 80, 40 meters using prewound plug in coils (sold below)
- Crystal Control
- 5 Watts Output into 50 OHMS
- Single Antenna operation with built in TR Switch
- LED Output Power Indicator
- Cathode Keying Circuit
- Solid State Power Supply
- Tube Line Up 6CA Crystal OSC. 6AQ5 Final
- Complete with Pre Wound 80 Meter Coil Included
- Complete Instruction and Color Pictorials
- Use with any Receiver or Transceiver
- Includes 2 Crystals for 80 Meters — 3.64MHz & 3.70MHz
- Complete Punched and Drilled Chassis
- Measures 9" W x 9" D. Weight approx. 5 lbs.
- Assembly time approx. 6 hours

BE UNIQUE! GO QRP VINTAGE RADIO STYLE!

Part No.	Description	Price
CPCW-5	2 Tube Transmitter	\$109.95
CPC-160	160 Meter Coil	\$9.95
CPC-80	80 Meter Coil (included)	\$9.95
CPC-40	40 Meter Coil	\$7.95
CY1812	160 Meter Crystal 1.812MHz	\$9.65
CY3560	80 Meter Crystal 3.560MHz	\$9.65
CY7040	40 Meter Crystal 7.040MHz	\$9.65

OTHER CRYSTAL FREQUENCIES IN STOCK. PLEASE INQUIRE.

### DELUX CODE KEY

Adjustable, heavy duty brass base with ball bearing pivots. Designed for hard usage. 3/16" plated contacts.

\$16.95

### CODE PRACTICE OSCILLATOR & MONITOR

3" Speaker, Headphone Terminal, Volume & Tone Controls. Uses 1 9V Battery Kit ..... \$19.95  
Wired ..... \$24.95

### SIGNAL INJECTOR/ TRACER

This handy tester is both a signal generator and receiver. As a generator use it to check out an amplifier, stage by stage. Also tests AM radio IF and RF stages. As a receiver you can pin point where a defective part exists. Will transmit and receive simultaneously.

Kit ..... \$18.95  
Assembled ..... \$24.95

### NEW! PC-DATA™ SOFTWARE

FOR MAKING PRINTED CIRCUIT BOARDS ON ANY WINDOWS 95 OR MS-DOS IBM COMPATIBLE PC!

- Make single or double sided PCB Board artwork, up to 30" x 30"
- Print your artwork on any PostScript™ Laser Printer
- Produces a 1X positive, ready to use with pre-coated board. No other artwork required.
- Produce industry standard solder mask and component layout for silkscreen art.

PC-DATA™ is supplied on one 3.5" diskette with a quick start manual. The full user's manual is larger and must be printed by the user (dot matrix printer ok); approximately 75 pages in length.

The **NEW PC-DATA™** software lets you create PCB boards ranging from prototypes to hobby projects, and on a par with the pro's. You may do the complete printed circuit board layout artwork on your own PC, at a fraction of the cost of other programs. Print the layout on any PostScript™ compatible printer, either on regular paper to be photographed for a positive or negative, or on clear film to be used directly as a positive with other Datak products.

ALL THIS FOR ONLY ..... \$29.95

**TO ORDER CALL  
1-800-866-6626**

## Ocean State Electronics

P.O. Box 1458 6 Industrial Drive  
Westerly, RI 02891

Phone: 401-596-3080 Fax: 401-596-3590

Mail in orders please include \$5.00 shipping.  
CANADA \$10.50 OVERSEAS \$16.00  
Minimum order \$10.00 (before shipping)

R.I. Residents add 7% Sales Tax

VISA & MASTERCARD ACCEPTED

### VERNIER DIALS

- 1-1/2" Diameter 0-10 Marking ..... \$11.95
- 1-1/2" Diameter 0-100 Marking ..... \$12.95
- 2" Diameter 0-100 Marking ..... \$13.25

### VERNIER DRIVE

American made 6.1 vernier drive. Has dual plate mounting flange with two tapped holes (2.56) for dial mounting. Input & output mate with 1/4" shaft.

\$9.95

### SIGNETICS NE602AN

Balanced Mixer/OSC. Popular IC among experimenters for building DC and super-het receivers.

\$2.49

### MINI-CIRCUITS SBL-1 DIODE RING MIXER

Double Balanced Mixer  
LORF — 1-500 MHz  
RF DF — 500 MHz

OTHER MINI-CIRCUIT PRODUCTS IN STOCK

### AM RADIO RECEIVER ON A CHIP (TYPE ZN414)

In a tiny (TO-22) transistor size case, a ten transistor tuned RF circuit that requires no setup or alignment. Nearly a complete circuit, add battery (1 to 1.5 volts), tuning coil and capacitor and crystal earphone. Data sheets with circuit examples included.

ZN414 ..... \$7.95

### FERRITE "LOOP-STIK" ANTENNA

Now to find Loop-Stik Antenna. HARD IN STOCK!  
For radio receivers. Tunes the broadcast band, 540KHz-1600KHz.

Measures 1/2" Dia. x 3 1/2" Long. Includes mounting bracket. Q-25, L=788µH.

LA-540 ..... \$2.25

### PLUG IN COIL FORMS

Wind your own coils with these plug in coil forms. Made from Grade XX Phenolic. Equipped with rim, making it easy to insert and pull out. Coils measure 1 1/4" Dia. by 2 1/4" H. Exclusive of the pins. These are like the coil forms used in all the early receivers and transmitters. Hard to find! Must mount in a 4, 5 or 6 pin tube socket

PART NO.	PINS	PRICE
CF-4	4	\$6.90
CF-5	5	\$6.90
CF-6	6	\$6.90

### MAGNET WIRE

Enamel coated solid copper. For winding coils, transformers and toroids. Prices for 1/4 lb. spools.

#14 \$4.00	#24 \$4.25	#34 \$6.25
#16 4.00	#26 4.25	#36 6.45
#18 4.00	#28 4.85	#38 6.95
#20 4.00	#30 4.85	#40 7.85
#22 4.25	#32 4.85	

### TOROIDS

IRON	FERRITE
T-25-2 \$ .40	FT-37-43 \$ .70
T-25-6 \$ .40	FT-37-61 \$ .70
T-37-2 \$ .55	FT-37-77 \$ .70
T-37-6 \$ .55	FT-50-43 \$ .85
T-50-2 \$ .65	FT-50-61 \$ .85
T-50-6 \$ .65	FT-50-77 \$ .85
T-50-6 \$ .65	FT-82-43 \$ 1.30
T-68-0 \$ .90	FT-82-67 \$ 1.30
T-68-2 \$ .90	FT-82-68 \$ 1.30
T-68-6 \$ .90	FT-114-61 \$ 2.30
T-80-2 \$ 1.20	FT-140-43 \$ 3.50
T-200-2 \$ 6.00	FT-240-61 \$ 8.75

WE STOCK A COMPLETE LINE OF TOROIDS AND BEADS.

### FM RADIO IC TDA 7000

Ideal for small mono FM receivers. Features an RF input stage, mixer I/O, IF amplifier stage, phase demodulator and muting circuitry. Also useful in LAN, data and SCA receivers. Data Sheet Included.

TDA7000 ..... \$9.95

**HARD DRIVE** liquidation 1,280 megabytes \$60. 8.00 gigabyte \$155. Mouse \$1.95, SVGA monitors \$135, flatbed scanners \$75, 56K modems 45, 386SX40 \$25, 1.2/1.44 floppy \$20, Adaptec SCSI controllers \$45, memory 1.25/megabyte. 714-778-0450.

**CNC SYSTEMS!** Write: motivity, Attn. Pam, PO Box 428, Rocklin, CA 95677. Call: 916-349-8757. Info/pictures at [www.motivityusa.com](http://www.motivityusa.com) A great place to buy CNC.

**DEC EQUIPMENT WANTED!!!** We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), DSD, Datability, Dilog, other DEC compatibles, and Computer Output Microfilm (COM) units. Please call for a quote or fax us your equipment list. We buy, sell, and trade. **KEYWAYS, INC.**, 937-847-2300 OR fax 937-847-2350.

**HEWLETT PACKARD:** Deskjet 500 printer (qty.), \$79. HP 7475A plotter (8.5x11"), \$79 QMS Laser 810 printer (8 pg./min), \$275. COMPAQ or NEC SVGA 14" monitor, \$89. VIEWSONIC SVGA 20" monitor, \$790. Call for other 17", 19" & 21" SVGA monitors. Accept Visa, MC, AMEX. Call Maple Data 908-964-7070.

**TRS-80** models 1, 3, 4, 100, pocket computer, COCO. #10 SASE, 55¢ stamp, for list to: TRS-80 Again, 2073 Co. Rd. 127, Fort Payne, AL 35967. E-Mail: [www.simology.com/trs80again](mailto:www.simology.com/trs80again)

**RISOGRAPH GR1700** digital printer. 130 prints per minute. \$8,500 last year, asking \$1,600. Dye Sublimation Proofing Printer PTR 200, 1995, \$1,000. FOB San Diego. 619-350-0989.

**WANT: BUYERS,** telecommunications suppliers. Seller of used Tadiran sys. Coral I, II, III, Tadex, 60/124, 1A Z key eq. ITT, AT&T, GTE. Parts: USB, hubs, category 5 product 110 blocks & connectors, adaptors, cable, assemblies network, modular, cable tester, computer printer cable, video, accessories, wallplates, ITT, multiline phones, Western Electric IA 2 phones 2500 w/tap M/W \$4,900 each. Ohio Service Supply Co., PO Box 8802, Canton, OH 44711. 330-456-8177.

## COMPUTER SOFTWARE

**FREE IBM DISK CATALOG** of quality Shareware and CD-ROMs. **MOM 'N' POP'S SOFTWARE** <ASP>, PO Box 15003-N, Springhill, FL 34609-0111. 352-688-9108. [momnpop@gate.net](mailto:momnpop@gate.net)

**LINUX & FREEBSD & LINUX & FREEBSD** Linux and FreeBSD distributions on CD-ROM for as low as \$1.99. See our full range of Linux products and books at **incredible prices**. Use our secured shopping cart system at [www.cheapbytes.com](http://www.cheapbytes.com) Visa and MasterCard gladly accepted. E-Mail: [sales@cheapbytes.com](mailto:sales@cheapbytes.com) fax: 209-367-8518. CheapBytes, PO Box 2714, Lodi, CA 95241.

**MOD CHIPS for Sony PlayStation.** Now your backups will work. Only \$9.95 ea. + \$3 shipping. Call 1-888-467-6150, all major credit cards accepted. Computers & components at wholesale prices. [www.cconusa.com](http://www.cconusa.com)

**MAKE \$\$\$** giving away our software! Business kit \$10 (refundable). RASCOM, 860 E. Carson St. #118-89, Carson, CA 90745.

**CAM & MOTION SW/HW:** Z-trace, PCB toolpath. Plotcam motion control, step drivers. [cmheater@juno.com](mailto:cmheater@juno.com) MSG/FAX 407-452-7197, 407-459-2729. [www.megabits.net/ddt](http://www.megabits.net/ddt)

**LIQUIDATION WIN 95/98,** Office97, WindowsNT, 10 PACK CDs \$25, DOS \$25, Lotus Smartsuite \$10, Wordperfect Suite \$35. Antivirus \$5. Call 714-778-0450.

## COMPUTER EQUIPMENT WANTED

**DEC EQUIPMENT WANTED!!!** We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), DSD, Datability, Dilog, other DEC compatibles, and Computer Output Microfilm (COM) units. Please call for a quote or fax us your equipment list. We buy, sell, and trade. **KEYWAYS, INC.**, 937-847-2300 OR fax 937-847-2350.

**WANTED: FOR** historical museum, pre-1980 microcomputers, magazines, and sales literature. Floyd, VA 24091-0341 (540-763-3311/540-382-2935).

**HP CALCULATORS** wanted: models 10, 70, calculator watch, others for private collection. Cash paid. Bob Morrow, 765-855-2348, [rkmorrow@aol.com](mailto:rkmorrow@aol.com)

**WANTED: TERMINALS + PRINTERS:** DEC, Wyse, IBM, ADDS, Okidata, Data South, Epson, C.I.TOH, etc. Call for quote on any surplus computer equipment. Call Jeremy, 603-673-8077.

## TEST EQUIPMENT

**DESOLDER STATIONS:** own pump, Pace PPS100A/SX25, \$175; MBT 200A desolder/solder, \$350; MBT 250A, \$750; SX25 handpiece, \$75; Ungar 4024, \$200; Weller DS1000 digital readout, \$350; DS100, \$200; Mesei hot tweezers, \$50; soldering: Weller EC2000 digital adj. temp. \$100; WTCP \$45u, \$60nu; EC1301 pencil \$40u, \$60nu; 1 lb. solder, \$8. 310-515-2058.

## Congratulations Richard Hight - Winner of our November drawing!

27pc•kit

\$12.95

K2637  
**MINIATURE AUDIO AMPLIFIER KIT**  
Big sound from a small unit!  
Small PCB with both pre- and power amp  
Short circuit protected  
Input sensitivity: 20mV  
Max. output power: 2.5W  
Power supply: 4.5 to 15VDC



28pc•kit

\$12.95

K1771  
**FM OSCILLATOR KIT**  
Use for home broadcasts, baby monitoring, security  
Frequency range: 100-108MHz  
Microphone input  
No coils to wind  
Power supply: 9-12VDC



17pc•kit

\$9.95

K1803  
**UNIVERSAL MONO PRE-AMPLIFIER KIT**  
Boost any audio signal up to 40dB (x100)  
Max input signal: 40mV  
Frequency range: 20Hz to 20KHz  
Power supply: 10-30VDC/10mA



19pc•kit

\$19.95

K5300  
**STROBOSCOPE KIT**  
Stage effects at home  
Adjustable flash rate: 2-20 flashes/second  
Powerful flash tube  
Supply voltage: 110-125V AC



36pc•kit

\$18.95

K4304  
**10 LED VU METER KIT**  
Visualise any audio level  
Line or speaker inputs  
DOT or BAR mode. Range: -20 to +3dB  
Front-panel included. Vertical or horizontal mounting. Power supply: 10-15VDC



27pc•kit

\$24.95

K5002  
**HALOGEN LAMP DIMMER KIT**  
Light control at the touch of a button  
Suitable for loads up to 3A  
Can control small motors with brushes  
Push button operation  
Add any number of buttons  
Power supply: 110-125V AC



16pc•kit

\$14.95

K6708  
**IR REMOTE CONTROL KEY CHAIN TRANSMITTER** For K6709 Kit  
Range: Up to 24 feet  
LED operation indicator  
8748 different code settings  
Power supply: 12V battery



66pc•kit

\$24.95

K6709  
**IR REMOTE RECEIVER**  
For K6708 Kit  
The easy way to add a remote control  
10A relay with momentary or pulse changeover contact  
Allows control of alarm systems, garage doors, outdoor lighting, garden pumps, etc  
LED reception indicator  
Accepts multiple transmitters K6708  
Power supply: 2x9VAC or 12 to 16VDC



12pc•kit

\$12.95


K1823  
**1 AMP POWER SUPPLY**  
Just add a transformer  
Adjustable output voltage  
1.5V to 35V/1A max  
Short circuit and thermal protection  
Max input voltage: 37VDC  
Max dissipation: 15W



18pc•kit

\$14.95

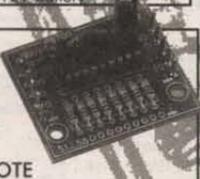K6700  
**2-WIRE REMOTE CONTROL TRANSMITTER**  
Transmitter For K6701 Kit  
Control up to 16 devices\*, with only 2 wires! Remotely control 8 (\*16 with 2 units) devices up to 160 feet away. Transmitter is powered over the data wires. Simple operation by means of switches (not included)  
Transmitter can drive multiple receivers



46pc•kit


\$24.95

K6701  
**2-WIRE REMOTE CONTROL RECEIVER** For K6700 Kit  
8 open collector outputs (max 200mA)  
LED output status indication  
Daisy chain 2 units for 16 outputs  
Power supply: 6-16V DC

18pc•kit

\$14.95

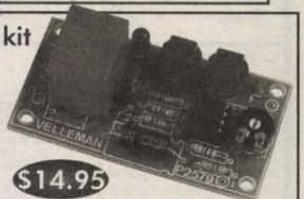K2579  
**UNIVERSAL START STOP TIMER KIT**  
0-15 Minutes Adjustable Delay  
3A changeover relay contact  
Start and Stop button included  
LED function indicator  
Can be modified for longer delays  
Power supply: 12V/55mA



# velleman

7415 Whitehall Street Suite 119  
Fort Worth, TX 76118  
(817) 284-7785 F: (817) 284-7712  
[www.velleman.be](http://www.velleman.be) email: [velleman@earthlink.net](mailto:velleman@earthlink.net)

Questions ? Contact us for a list of US distributors or to get your **FREE** catalogue

**NEW HEWLETT-PACKARD 141T CRTs \$195 EACH.** We have quantities available. These are double boxed, unopened with late 80's date code, guaranteed. Fits all Kentronix. 732-681-3229 or FAX 732-681-3312. Mailing: Kentronix, PO Box 2444, Farmingdale, NJ 07727 or E-Mail: brian@kentronix.com

**EQUIPMENT MANUALS** we have 1000's of service and operators manuals for all types of test and measurement equipment from 1950 to present. All test equipment manufacturers are represented. Call, write, or fax your want list. Please include mfg.'s manual P/N unit serial numbers if known. **Manuals Plus**, Box 549, TAD #601, Tooele, UT 84074. 435-862-7188, FAX 435-882-7195.

**POOR MAN'S** Spectrum Analyzer/Monitor Receiver Kit. 2 to 1,700 MHz. Basic kit only \$78. Now available with switched resolution filters, tracking generator and direct digital frequency readout. Works with ANY scope or IBM compatible computer. Send stamped envelope for details. Science Workshop, Box 310B, Bethpage, NY 11714. <http://www.science-workshop.com>

**KENTRONIX TEST EQUIPMENT SPECIALS.** Check our WEB site at <http://www.kentronix.com> for monthly specials. We are also looking to buy test equipment, coaxial and waveguide components, manuals, etc. Contact Brian at 732-681-3229 or FAX 732-681-3312. E-Mail: brian@kentronix.com

**WE BUY electrical power systems test equipment.** This includes the following manufacturers: **Multi-Amp** (now AVO Multi-Amp), **Biddle** or James G. Biddle (now AVO Biddle), **Megger** (now AVO Megger), **Associated Research, AEMC, EIL, Programma** or any other test equipment used for testing high voltage equipment and components. The test equipment that we are looking for is used for testing high voltage transformers, circuit breakers, cables, and protective relays. FAX 972-564-9139 or phone 1-800-261-9139 for quote. **Phase-3 Power Test Equipment.**

**SPECTRUM ANALYZER** in a probe. \$249. View thru your inexpensive scope. [WWW.spectrumprobe.com](http://WWW.spectrumprobe.com)

**TEST EQUIPMENT FOR SALE:** Wiltron 560A scalar network analyzer, \$1,500; HP 8620C sweep oscillator, \$500; Wiltron 560-7A50-1 RF detector, N-connection, \$500; Wiltron 560-7A50-1 RF detector, SMA-connection, \$500; Tenma 72-4015 NTSC generator, \$300; HP spectrum analyzer 141T display section, 8555A RF section, 8552B IF section, \$2,875; Tenma 72-6055 waveform monitor/vectorscope/oscilloscope, \$2,500; HP 7044A XY recorder, \$475; Bird 43P thru-line watt meter, \$400; watt meter plug 250B, 50-125MHz, \$45; watt meter plug 250C, 100-250MHz, \$45; watt meter plug 250E, 400-1000MHz, \$45; watt meter plug 1000E, 400-1000MHz, \$45; watt meter plug 433-163, 2500-2600MHz, \$45; watt meter plug 433-164, 2600-2700MHz, \$45; EIP 545A frequency counter 18GHz, \$2,400; Bird dummy load 150W CW, \$150; -30dB directional coupler at 3-4GHz, \$400; -20dB directional coupler at 3-4GHz, \$400; Bird 43P carrying case, \$30. Contact 813-503-4300.

**24 Hr. Shipping**

To Order Call 1-800-292-7711 Fax: (847) 541-9904

## Quality Kits for Hobbyist and Students

All Kits include PCB, all parts, and detailed assembly manuals.

### XK-700 Digital / Analog Trainer

Elenco's newest advanced designed Digital / Analog Trainer is specially designed for school projects. It is built on a single PC board for maximum reliability. It includes 5 built-in power supplies, a function generator with continuously sine, triangular and square wave forms. 1560 tie point breadboard area. Tools and meter shown optional (Mounted in a professional tool case made of reinforced metal).

**XK-700**  
Assembled and Tested  
**\$189.95**

**XK-700-SEMI KIT**  
w/ Fully Assembled PC Board  
**\$174.95**

**XK-700K - Kit**  
**\$159.95**



Made in the USA

### SOLDERLESS KITS **NEW**

#### TALKING CLOCK KIT

**\$14.95 AK-220**



- Dual analog/digital
- Rooster crows every hour.
- Easy-to-build No Soldering Required

#### 35mm Camera Kit

**AK-540 \$14.95**

Learn all about Photography



No Soldering Required

#### ELECTRONIC KEYBOARD KIT

**AK-900**

**\$24.95**

- 37 mini-size keys
- 8 tempo rhythms
- 4 custom drums



#### REMOTE CONTROL CAR KIT

**AK-870**

- 7 functions
- Remote control included

**\$24.95**

No Soldering Required



Call for a **FREE** 64 page catalog! (800) 445-3201

#### Hobbyist Tool Kit

**TK-1000**

All the tools you'll need to build these kits. 25 tools contained in a heavy-duty carrying case.

**\$39.95**



#### Stereo Cassette Player Kit

**\$14.95 AK-200**

- Transparent Case
- Belt Clip
- High Resolution
- Includes Head-phones



#### M-1005K

#### Digital Multimeter Kit

Low cost, 3 1/2 digit LCD, 18 ranges, transistor test, diode test, overload protection and pocket-size.

**\$19.95**



#### AM/FM-108K

AM/FM Radio Kit and Training Course 14 Transistors and 5 Diodes

**\$29.95**




AM Radio Kit and Training Course 7 Transistors and 1 Diode **\$19.95**

#### FO-30K

#### Fiber Optics Technology with Training Course

Learn the basics of fiber optics data communications while you build this exciting kit. Comes complete with all necessary components.

**\$24.95**

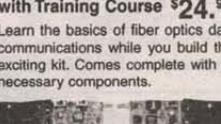

#### Telephone Kit

**Model AK-700**

Build this high-tech see-thru plastic telephone. Learn theory on how telephones work and then proudly show off your work with the transparent phone case. Complete with all parts and manual. Neon lamps flash when the phone rings.


**\$15.95**



#### AR-2N6K

2 meter / 6 meter Amateur Radio Kit

**\$34.95**

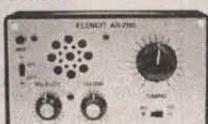

#### AK-300 Digital Roulette Kit

This Digital Roulette Kit is just like the real thing. With a push of a button, the LEDs spin round and round. Where they stop is anybody's guess. It's unique design includes "pop out" chips of different values. Enjoy hours of fun with this game of chance. Requires one (1) 9V battery.

**\$14.95**



#### Sound Activated Switch

**Model K-35**

Clap and the light comes on, clap again and it goes off.



#### Telephone Bug

**Model K-35**

Size of a dime, yet transmits both sides of a phone conversation to any FM radio. No battery needed.



**\$7.95**

#### Strobe Light Kit

**Model AK-520**

You will have fun building this kit and learn how strobe lights work. Complete with all parts and case.

**\$54.95**



#### Motion Detector Kit

**Model AK-510**

Simple and fun to build. Compact, portable, and adds safety to your home or office. Requires one (1) 9V battery.



**\$14.95**

**Guaranteed Lowest Prices**

**C&S SALES, INC.**

UPS SHIPPING: 48 STATES 5%  
OTHERS CALL FOR DETAILS  
IL Residents add 8.25% Sales Tax

150 W. CARPENTER AVENUE  
WHEELING, IL 60090  
FAX: (847) 541-9904 • (847) 541-0710  
[http://www.elenco.com/cs\\_sales](http://www.elenco.com/cs_sales)



**15 DAY MONEY BACK GUARANTEE**  
**FULL FACTORY WARRANTY**

PRICES SUBJECT TO CHANGE WITHOUT NOTICE



**ENGINEER TESTED:** Spectrum analyzers, frequency counters, frequency standards, meters, scopes, generators, curve tracers, temperature, time, weight, light, sound, distance, etc., measurement instruments. **VISA, MASTERCARD, AMEX.** "Performance tested." NIST calibrated. Warranted. New & used. Gary NgZD. [HTTP://TECH-SERVICES.COM](http://TECH-SERVICES.COM)

**TERRIFIC VALUES:** HP 8116A/001 50MHz pulse/function generator with burst, logarithmic sweep, \$4,400; HP 8111A/001 20MHz pulse/function generator with burst, \$2,300; HP 54100D 1GHz digitizing oscilloscope featuring automatic measurements, \$3,100; Tek AM 503, A6302 current probe, amplifier \$825; HP 83522A .01 to 2.4GHz plug-in \$3,750; HP 83570A 18 to 26.5GHz plug-in \$4,500; HP 3488A mainframe \$650 (cards available); HP 8161A/020 100MHz dual channel pulse generator \$2,750; Stanford Research SR 510 lock-in amplifier \$950; HP 8410C, 8410B, network analyzer mainframes \$625, 450; HP 8411A/018, 8411A harmonic frequency converters \$395, 295; HP 8743B/018, 8743A test sets \$575, 300. All in excellent condition with warranty. Pepper Systems (<http://home.earthlink.net/~peppersys>) 214-353-0257 (Fax 214-902-9511). E-Mail: [peppersys@earthlink.net](mailto:peppersys@earthlink.net)


**TEKTRONIX SALE:** 465B, \$446, 4 available; 465B DM44, \$497, 2 available; 475, \$525; 475A DM44, \$565. As new 453 man, cover, \$175; 5223 as new, \$150; Tek 466, \$300; 7104 1GHz frame, \$1,000; bright CRTs, \$975; 7A13, \$100 LED; 7A18, \$45; 7A19, \$100; 7A26, \$60; 7B53A, \$60; 7B80/7B85, \$65 either one; 7B92A, \$125; 7D15, \$175; DC504, \$100; PG-507, \$200; PG-508 \$250; P6046 probe \$200; all with money back warranty. **Psitech Plus**, 707-745-4804, [www.psitech-plus.com](http://www.psitech-plus.com)

**AFFORDABLE HP** power sensor repair! Most 8481As repaired for \$260 or less. We also handle 478As and many others. Call or fax for more information. Willamette RF, Inc., 541-754-7226, FAX 541-753-4629.

**WANTED: WESTERN** electric test equipment. Tube-type only please. Freq. measuring sets, oscillators, amplifiers, parts, tubes, etc. 1-800-251-5454.

**TEST EQUIPMENT** repair or overhaul Tektronix, HP, Wavetek, Boonton, etc. 20 years experience with former Slep Electronics Co., same excellent service same reasonable rates, satisfaction guaranteed. Brooks Electronics 828-349-3503. E-Mail: [rwbrooks@dnnet.net](mailto:rwbrooks@dnnet.net)

**NON-DESTRUCTIVE testing:** Ardrex penetrant kit, \$125; Uniwest/Nortec hole probes, PWA54280, PWA44295, \$35; Automation Industries/Tektronix EMC-3300/5110, \$190; Magnaflex H-100, inop, \$45; ratio transformers: Astrosystems TF-384/U, \$55; Eaton RT-20A, \$60; Gertsch RT-2, \$50; Gertsch RT-7, \$55. Military test sets: SA-ALC/MMIREB computer (lightweight) AN/AJB-7, \$60; Hazeltine transponder simulator AN/APM-245, \$75; Fluke voltmeter ASM-340, \$50; Hartman aural signal generator AN/ASM-397A, \$75; Westinghouse laser energy monitor AN/ASM-498, \$150; Simpson DMM AN/PSM-45, \$60; Multronics PRC-25 ckt card tester AN/GRM-55A, \$45; Van Norman freq. meter AN/TSM-16, \$70; Struthers wattmeter AN/URM-120, \$70; Spedcor freq. meter AN/USM-159A, \$60; Bendix F15 LVPS test selector unit 2143204-2, \$40; Boeing electronic control amp ASK-39/F37U-9, \$75; Capehart range simulator TS-38A/UPM-11A, \$50; Collins amp 878L-1, \$60; Datamatric printer (p/o TTU-485/E) 112610-100, inop, \$40; General Precision computer tester TS-783/UPM-35, \$60; Montair/Rosemount AOA/stall warning simulator 6078, \$125. G&G 210-674-8771, fax 210-674-8775.

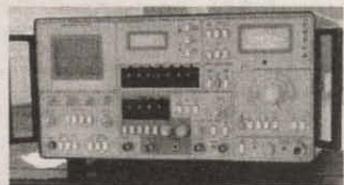

**CT SYSTEM, Inc. service monitor:** model 3000B, \$800, good working condition. Frequency range 400KHz to 1GHz, RF output 0.03UV to 316MV, receive sensitivity 2UV, RF sweep generator, tone generator/decoder, FM marker at 600Hz and 5KHz, internal wattmeter, internal distortion analyzer, oscilloscope. Tel: 714-778-5151 Fax: 714-778-0312.

**BRUEL & KJAER BUY, SELL, BEST PRICES. EXCALIBUR ENGINEERING,** 3198-C AIRPORT LOOP DRIVE, COSTA MESA, CA 92626. 714-540-0169, FAX 714-540-5417.

**HEWLETT PACKARD SALE:** as new 4262A digital LCR meter with 16062A test lead/adaptor, \$1,075; 8175A opt 002,003 complete, \$1,500; 3314A function generator in Cal, \$1,750; 1630G logic analyzer with all pods, \$450; 1630D, \$300; 3325A synthesizer function generator, \$650; 5335A opt 20,40, \$325; 3336C opt 004 synthesizer/level generator, \$800; as new 1980B osc. meas. sys., \$500, all with money back warranty. Psitech Plus, 707-745-4804, www.psitech-plus.com

**CAPANALYZER 88** finds bad caps in-circuit with 100% accuracy. Checks both ESR and DCR, auto-discharge feature. Money back guarantee. www.ed-inc.com 561-487-6103.

**LEAKSEEKER 82A** tracks a shorted or leaky component to the EXACT location on the PCB. Range: zero to 150 ohms. Money back guarantee. www.ed-inc.com 561-487-6103.

**WANTED: ELECTRONIC estates.** Ham, broadcasting, military, test, public address, tubes, transformers, telex equipment. The bigger the pile, the more worthwhile. We fly anywhere. Sumner McDanel 1-800-251-5454.

**BEST PRICES** on guaranteed test equipment. Oscilloscopes, Tektronix 305, 454, 475, SC 504, 2225, 2246, & others. Huntron Tracker 2000, Fluke, HP and other fine used test equipment. Check us out at: [www.lonemtn.com](http://www.lonemtn.com)

**SPECTRUM ANALYZER:** IFR A-7550, frequency range: 100KHz to 1GHz. Optional features FM/AM receiver, battery and carrying case. Good condition, low time. \$4,900 frm. Tel 1-888-584-6284 ask for Cal.

**WANTED: RADIO** service monitors, IFR, Motorola, HP, Marconi, also late model HP equipment. 716-763-9104 or Fax 716-763-0371. <http://www.amtronix.com>

**TEST EQUIPMENT** for sale/wanted: RF, Microwave, video and fiber optic. Cable TV, Broadcast TV, satellite and related industries. Wavetek, Tektronix, Hewlett Packard and other manufacturers. Spectrum analyzers, signal level meters, sweep systems, TDRs, OTDRs, and much more. PTL Test Equipment, Inc. Phone 561-747-3647 FAX 561-575-4635.

**KEPCO BOP** 72-6m, opamp/pwr. sup. ±75V, ±6 amp. Mint cond., \$750 (new, \$2,800). Keith, 541-726-1512, after 6pm.

**NEW: POCKET TESTBENCH,** tiny, portable, RS-232 instrument. Scope, logic, spectrum, counter, generator modes. Oricom Technologies, 303-449-6428 [www.sni.net/~oricom](http://www.sni.net/~oricom)

**DATA RECORDS.** Teac XR-5000 14 channel SVHS format \$5,000. Sony PC-204 portable 4 channel DAT format \$900. John 973-591-0523.

**FEITEK PROVIDES** repair, calibration and traceable certifications of test equipment. Free estimates. We buy, sell and trade all makes of test equipment. Visa and MasterCard accepted. Check out our inventory and specials at [WWW.FEITEK.COM](http://WWW.FEITEK.COM) 2752 Walton Road, St. Louis, MO 63114, 314-423-1770.

**TEKTRONIX FG504,** \$350; SG504, excellent, late, w/leveling head, \$2,000. Also available: SG503, TG501, and PG506, all new style in excellent condition. 732-445-4915, or see [www.test-equipment.net](http://www.test-equipment.net) for details, pictures, and more Tek goodies.


**HP 3336B,** \$450; 3586B, \$450; 8518B optical attenuator, \$1,800. 732-445-4915 or see [www.test-equipment.net](http://www.test-equipment.net) for details and more HP goodies.

**LARGE ASSORTMENT** of used test equipment for sale. Request catalog or visit our website. Stevenson Equipment Company, 609-888-2846, Fax: 609-888-2847. Website: <http://www.stevensonlabs.com>
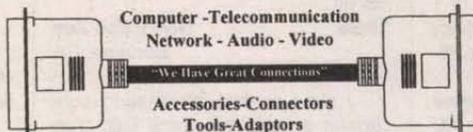
## Roger's Systems Specialist

We accept Purchase Orders:


- Government
  - Schools
  - Firms\*
- (\*w/approved credit)



We now offer discounts to members of PC User Groups!
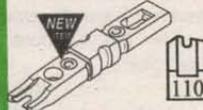
### HARRIS


110 punchdown tool blades for network punch blocks.



#Special ..... \$2.50 each or 5/\$10.00
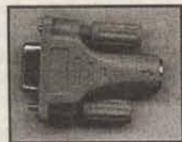
### Mouse Adaptor

PS/2 F to DB9 F  
For using a PS/2 mouse with a serial port.



<http://www.rogerssystems.com/main/items/at-ser-mou-adaptors.html>

#CA-610 ..... \$5.00  
3/\$1.00 20/\$5.00

### 7' Category 5


crossover network cable computer to computer



TE-068-L5X  
Retail Price..... \$9.00  
Roger's Price..... \$1.00
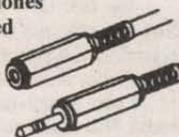
### 20' Audio Cable

Stereo extension cables, for speakers and headphones  
3.5mm, gold plated male to female, shielded, 20 ft.




[www.rogerssystems.com/main/items/stereo-exten-audio.html](http://www.rogerssystems.com/main/items/stereo-exten-audio.html)

#AC-560..... \$4.50 each
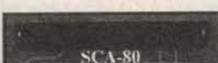
### SCA 80 Adaptor

SCA 80 to SCSI 50 pin and SCSI HD68

Includes active termination and power connector.



<http://www.rogerssystems.com/main/items/sca-adaptors.html>

#CA-051 ..... \$22.00 each



Headphone with high quality microphone, used for net meetings, and voice dictation.

Stereo Headphone w/mic (TM-165)

Roger's Price..... \$6.00 ea  
QTY. 100+..... \$4.50 ea

Mono Headphone w/mic (TM-165-MONO)

Retail Price..... \$30.00 ea  
Roger's Price..... \$3.50 ea  
QTY. 100+..... \$2.00 ea

[www.rogerssystems.com/main/items/ster-head-micro-audio.html](http://www.rogerssystems.com/main/items/ster-head-micro-audio.html)

### MAC Touchpad

ALPS Portable Glidepoint for MAC.  
3 Programable Buttons  
4 pin ADB Connector



<http://www.rogerssystems.com/main/items/glidepoint/alps%20glidepoint%20detail.htm>

Roger's Systems Specialist  
24895 Avenue Rockefeller  
Valencia, Ca 91355

1-800-366-0579  
[www.rogerssystems.com](http://www.rogerssystems.com)

Local  
805-295-5577  
FAX  
805-295-8777

\$20.00 minimum order required • Add \$4.50 shipping for pre-paid orders • Prices subject to change without notice.  
All major credit cards accepted. • Special offers only valid on items in stock • California residents add 8.25% tax • eMail [sales@rogerssystems.com](mailto:sales@rogerssystems.com) Call for quantity discounts • No out of state checks accepted • Most orders shipped same day! • Not responsible for errors in typesetting. Trademarks are the property of their respective companies.  
All photographs are for illustration purposes only and may not be a true representation of actual products.

# TECH FORUM

This is a READER TO READER Column. All questions AND answers will be provided by *Nuts & Volts* readers and are intended to promote the exchange of ideas and provide assistance for solving problems of a technical nature. All questions submitted are subject to editing and will be published on a space available basis if deemed suitable to the publisher. All answers are submitted by readers and **NO GUARANTEES WHATSOEVER** are made by the publisher. The implementation of any answer printed in this column may require varying degrees of technical experience and should only be attempted by qualified individuals. Always use common sense and good judgement!

## QUESTIONS

Send all material to **Nuts & Volts Magazine**, 430 Princeland Court, Corona, CA 91719. OR fax to (909) 371-3052. OR E-Mail to [forum@nutsvolts.com](mailto:forum@nutsvolts.com)

I am looking for a design using modern ICs that will allow me to output a selected frequency in the range of 100 MHz to 1 GHz with steps of 1 MHz. I would like to set the frequency using a computer interface (like RS-232, I2C, SPI, USB, or similar).

**1991** **Gus Calabrese**  
Denver, CO

I have an application where I need to control two 12-volt, 5-amp DC motors via a digital microcontroller module. However, the microcontroller appears to malfunction when the motors are started. I am suspecting some sort of interference generated by the motors. Should I employ filtering? I've seen motors with capacitors soldered across the leads. Do I need something like this? If so, what size capacitors should I use?

**1992** **Ken Delahoussaye**  
via Internet

I have used a 33.6 modem for some time and when I received a call while online, it would hang me up and allow the call to come through (I have call waiting). Now that I have a 56K modem, it no longer allows the calls to come through and I am missing important phone calls. Please let me know if you have any ideas how I can still get my calls through. Please don't tell me I need another line.

**1993** **Bill Ulster**  
via Internet

I would like to see a schematic for a simple UPS which uses power MOSFETs in its output stages. I have several which are not repairable due to the lack of a schematic and, which I might convert to a useable unit with a schematic.

**1994** **C. Mills**  
via Internet

I have a Galaxy 2100 transceiver that when the frequency counter is on, a tone is heard on the speaker. It's not very loud, but I would like to get rid of it. How do I go about doing this?

**1995** **Herman Atkinson**  
Venus, TX

Is there a simple circuit to detect 60 Hz and light an LED? And also,

add another LED to light before 60 Hz, and go out at 60 Hz? And another LED to light at 62 Hz with the others off?

**1996** **Henry Van Zee**  
Stevens, PA

I need to find information concerning a magnetic force field that could lift approximately 100 lbs., if possible. I am working on a new type of "Hover-Cam" design. I also need information on anti-gravity that I might be able to use for this same design.

**1997** **Don Camman**  
Cameron, MO

I think I understand the cause of ghosts on TV pictures. But what causes vertical dark and light bands on some channels? Can anything be done about them?

The two UHF channels (28 and 34) are plagued by bands, share a common tower, and are about 10 miles away across flat urban terrain.

I use a high-gain antenna on a rotor. The signal strength seems satisfactory, but the bands are quite annoying. Any suggestions?

**1998** **Paul Tucker**  
Columbus, OH

I am okay with a single timer, but I can't figure out how to make a three-stage timer. I want to use the timer on a traffic light. Also, each stage must be adjustable from 5 seconds to 30 seconds, approximately.

The problem I have is how do I make the end of one timing cycle start the next, and then at the end of the third cycle start all over again?

**1999** **Ray Samples**  
Fayetteville, NC

I have been using a Magnavox MC3510-AL01 monitor system, CCTV system for about two years now. When mounting one of the cameras, I bumped it hard and a solder joint must of broke inside the camera's picture tube. It left a crooked line on the screen.

I would like to replace the picture tube in the camera, but Magnavox does not supply parts for this camera. So, I would like to get a replacement tube. The number on the tube is Matsushita-4848. Can anyone tell

me what replacement tube will work and where I can get one?

**19910** **Furman Hendrickson**  
Washington Crossing, PA

I have an analog device AD2038 digital temperature meter for which I would like to have the pinout.

There is a description of this device in the 1987 ad, short form selecting guide.

I ordered some sensors for it several years ago, but both the ad and their distributor disclaimed any technical information. Through experimentation, I have discovered some information, but a pinout would be much simpler.

**19911** **Kenneth Keck**  
Via Internet

I want to build a light display using 100 lamps or LEDs, 10 columns x 10 rows. The display is sort of like the lights you would see on a Ferris wheel with endless patterns and designs.

I repair pinball machines for a living and the machines have a Materix display, except the Materix system is embedded with a switch Materix and EPROMs.

Is there anything simpler to build or is my imagination expecting too much?

**19912** **Ray Samples**  
Fayetteville, NC

I have on occasion, a need to make a 1/2 inch tape with my video equipment. What I need are the pinouts to construct an adapter to go from 14-pin female to 10-pin male, both EIAJ.

**19913** **Matthew Augugliaro**  
Smiths Creek, MI

I'm trying to find a way to use a BASIC Stamp and display, or laptop to communicate with my Jeep Cherokee's onboard computers. This way I can tie into the data stream to check all of the engine diagnostics. Any ideas?

**19914** **Joe**  
Via Internet

I heard that it was possible and inexpensive to make an adapter so that an oscilloscope would act like a Huntron Tracker.

## ANSWER INFO

- Include the question number that appears directly below the question you are responding to.
- Payment of \$25.00 will be sent if your answer is printed.
- In most cases, only one answer per question will be printed.
- Your name, city, state, and E-Mail address, (if submitted by E-Mail), will be printed in the magazine, unless you notify us otherwise with your submission.
- Due to space limitations, we can not reprint the original questions with the answer. The question number and the issue it appeared in are printed above the answer.
- Unanswered questions from a past issue may still be responded to.
- Comments regarding answers printed in this column may be printed in the Reader Feedback section if space allows.

## QUESTION INFO

### TO BE CONSIDERED FOR PUBLICATION

All questions should relate to one or more of the following:

- 1) Circuit Design
- 2) Electronic Theory
- 3) Problem Solving
- 4) Other Similar Topics

### INFORMATION/RESTRICTIONS

- No questions will be accepted that offer equipment for sale or equipment wanted to buy.
- Selected questions will be printed one time on a space available basis.
- Questions may be subject to editing.

### HELPFUL HINTS

- Be brief but include all pertinent information. If no one knows what you're asking, you won't get any response (and we probably won't print it either).
- Write legibly (or type). If we can't read it, we'll throw it away.
- Include your Name, Address and Phone Number. Only your name will be published with the question, but we may need to contact you.

A Huntron Tracker is a device that gives the waveform of a component such as a diode curve or a capacitor and resistor.

I used one for testing components to see if they are failing or noisy, etc.

**19915** **Joe Farley**  
Via Internet

I just bought a new CMOS camera for my RC car and I'm now stuck with the dilemma of finding a good compact video transmitter.

I have seen some transmitters

# TECH FORUM

on the market, but I need something that can go further than 1,000 feet.

Does anyone know of any kits or circuit schematics out there for a black and white (audio would be nice) video transmitter? The smaller and less power, the better.

19916  
Gregg  
Via Internet

I am looking for a circuit that would enable one to switch between a regular PC mouse (i.e., Microsoft or Logitech typical mouse), and a PC touchpad mouse (i.e., Cirque glide-point control).

I believe the complication comes from either the software or initialization of the hardware.

19917  
Derek Koonce  
San Jose, CA

## ANSWERS

### ANSWER TO #12988 - DEC. 1998

Use a 74193 or 74LS193 four-bit up-down counter to count down. You did not specify whether your preset of 2-12 is a constant or changeable.

The starting number is wired to the DCBA inputs with an optional 10K resistor to +5V on each input, which is then unconnected for a binary 1 or shorted to ground by a switch for a binary 0.

You will need to supply a pulse on the DOWN pin for each count. If this is to come from a switch, you must debounce it. Use a 7404 hex inverter and a SPDT switch.

**7404 Wiring:** +5V to pin 14 (power) ground to pin 7 and switch common (ground of inverter and logic 0 input). Connect pin 2 (notA) to pin 3 (inputB) and to normally closed SPDT switch section. Connect pin 4 (notB) to DOWN of 7493 (clock pulse out) and pin 1 (inputA) and normally open switch.

**7493 Pinout:** Inputs: D,C,B,A initial count = 9,10,1,15  
LOAD counter=11  
CLEAR=14  
DOWN=4  
UP=5  
Power: +5V=16  
GND=8  
Outputs: BORROW=13  
CLEAR=14  
CARRY=12  
D,B,C,A outputs={7,6,2,3}

**7493 Wiring:** +5V to pins 5 and 16 (no UP counting, and supply voltage). Ground to 8 and 14 and through four switches to {9, 10, 1, 15} (ground, no clear, initial count). Connect pin 11 to 13 (to reload each count down past 0, or a momentary switch from ground to pin 11) to manually load your count. Connect your trigger (high to low edge) to pin 4 (clock down count). Output the end of count on pin 13 (borrow out from counter after 0 count). Leave output

### ANSWERS TO #129821 - DEC. 1998

HiJaak Pro from Inset Systems, supports a Dr. Halo .CUT format — created with Dr. Halo III. Uses run length compression to store images with 256 colors (eight bit).

CUT images store color palette information in a separate palette file with a .PAL extension. It also supports Lotus .PIC format — I don't know if that's any relation to the Dr. Halo .PIC format.

Inset Systems is at 71 Commerce Dr., Brookfield, CT 06804; 203-740-2400 FAX 203-775-5634.

HiJaak Pro should be available from software retailers.

Carlos Hidalgo  
Brookfield, CT

### ANSWERS TO #129821 - DEC. 1998

I have located two programs which I have used for graphic format conversion. Both of these claim to convert Dr. Halo II files to many formats (actually from many formats to many formats). However, both refer to .CUT files not the .PIC which you mention.

Can you resave them in .cut? If you can display the file in your Dr. Halo program, perhaps you can use a screen capture program to get a new format.

1. *icovert.zip* (short for I convert.com — version 1.49 — 1988) is an old DOS program available on <http://www.filepile.com/nc/start>. I have used this program to convert many odd file formats. You must use the "setver" DOS command to set the version to 3.3 or lower as the program does not recognize later versions.

2. *Graphic Workshop Professional Version 2.0A* Copyright 1998 by Alchemy Mindworks, Inc. — <http://www.mindworkshop.com/alchemy/alchemy.html>. I have used this program slightly, only to test a few conversions. There is a registration fee (after you try it and like it) of \$40.00. This program also has

counts D, C, B, A=(pins 7, 6, 2, 3) unconnected.

The input count can be four DIP switches or a rotary HEX thumb wheel switch with the common tied to ground and the four outputs tied to inputs DCBA.

Example: ground C and B to load 1001 binary. This will take nine pluses of down to count to 0 and one more to trigger the borrow for a count of 10.

Barry Cole  
Sunnyvale, CA

### ANSWER TO #129823 - DEC. 1998

You don't need to bypass the monitor at all — the motherboard doesn't need to have a monitor attached.

The keyboard is checked during the POST (Power On Self Test), so you will need to have a 'keyboard' attached.

Vetra Systems sells a "Phantom Keyboard" that "Allows PC boot-up and operation without keyboard." It's a small plug that replaces the key-

board plug at the motherboard connector.

Bob Rutledge  
via Internet

### ANSWERS TO #129821 - DEC. 1998

Graphic Workshop, by Alchemy Mindworks, Inc., will read and convert Dr. Halo images to just about any other common format. The program is available for evaluation or purchase at <http://www.mindworkshop.com>. HiJaak PRO by Quarterdeck Corp. is another excellent converter, but it's a little pricey compared to Graphic Workshop, and is probably overkill for your needs.

Scott Miller  
via Internet

### ANSWERS TO #129821 - DEC. 1998

The Dr. Halo format is probably the same as Lotus .PIC format. PIC was used by Lotus to display graphs in their 1-2-3 spreadsheet, and many programs adopted the file format for simple pictures. David C. Kay and John R. Levine describe the format in their book, *Graphics File Formats*, McGraw Hill 1992.

A current version of Lotus may offer some form of conversion, but I

don't know. Excel 97 claims to read these files if they belong to a set of Lotus files, but it will not convert them.

The documentation for Corel Draw 7 claims to read and write these files, but the program disagrees. Corel may have removed the filter because the .PIC extension conflicts with the extension commonly used for Macintosh PICT files. Corel Draw 8 may have ironed this out, but we are getting pricey.

An old version, Corel Draw 4, does read these files and will output the converted file in almost any format you want. If you can find a copy, it will be cheap. The program was bundled with some video cards for a while, and I've seen copies for \$40.00.

Lotus PIC is a simple vector format file, so when you convert the files, you should convert them to another vector format. A Windows metafile can do vectors. If you convert the file to a bitmap file (BMP, PCX, or TIF), then you've turned the lines and text into pixels. Bitmap files are larger than vector files, and they are more difficult to edit.

Gerald Roylance  
Mountain View, CA

Hauppauge, NY

ANSWER TO #129819 - DEC. 1998

Check out the ad on page 47 of Dec. '98 *Nuts & Volts*. This vendor (Pikul & Assoc.) carries two inexpensive monitor adapters that may do

board plug at the motherboard connector.

Vetra Systems is at 275-J Marcus Blvd., Hauppauge, NY 11787; 516-434-3185 FAX 516-434-3516. E-Mail: [vetra@mail.idt.net](mailto:vetra@mail.idt.net)  
Carlos Hidalgo

# LASERS & ACCESSORIES

## HELIUM NEON LASERS

- Complete Systems
- Plasma Tubes
- Power Supplies

## ACCESSORIES

- Optics
- Electro-Optics
- IR Viewers
- Books & More



MEREDITH  
INSTRUMENTS

Phone: 602-934-9387 • Fax: 602-934-9482

## DIODE LASERS

- Visible / IR
- Complete Modules
- Collimating Optics
- Drive Circuits

## FREE CATALOG

WEB SITE:  
[www.mi-lasers.com](http://www.mi-lasers.com)

Write in 141 on Reader Service Card.

screen capture ability, but I have not used it.

Bob Rutledge via Internet

ANSWERS TO #129821 - DEC. 1998

The Dr. Halo format is probably the same as Lotus .PIC format. PIC was used by Lotus to display graphs in their 1-2-3 spreadsheet, and many programs adopted the file format for simple pictures. David C. Kay and John R. Levine describe the format in their book, *Graphics File Formats*, McGraw Hill 1992.

A current version of Lotus may offer some form of conversion, but I

don't know. Excel 97 claims to read these files if they belong to a set of Lotus files, but it will not convert them.

The documentation for Corel Draw 7 claims to read and write these files, but the program disagrees. Corel may have removed the filter because the .PIC extension conflicts with the extension commonly used for Macintosh PICT files. Corel Draw 8 may have ironed this out, but we are getting pricey.

An old version, Corel Draw 4, does read these files and will output the converted file in almost any format you want. If you can find a copy, it will be cheap. The program was bundled with some video cards for a while, and I've seen copies for \$40.00.

Lotus PIC is a simple vector format file, so when you convert the files, you should convert them to another vector format. A Windows metafile can do vectors. If you convert the file to a bitmap file (BMP, PCX, or TIF), then you've turned the lines and text into pixels. Bitmap files are larger than vector files, and they are more difficult to edit.

Gerald Roylance  
Mountain View, CA

Hauppauge, NY

ANSWER TO #129819 - DEC. 1998

Check out the ad on page 47 of Dec. '98 *Nuts & Volts*. This vendor (Pikul & Assoc.) carries two inexpensive monitor adapters that may do

board plug at the motherboard connector.

Vetra Systems is at 275-J Marcus Blvd., Hauppauge, NY 11787; 516-434-3185 FAX 516-434-3516. E-Mail: [vetra@mail.idt.net](mailto:vetra@mail.idt.net)  
Carlos Hidalgo

Mr. NiCd

**JANUARY SUPER SPECIALS!**

THE BEST BATTERIES IN AMERICA!

<b>Packs &amp; Charger for YAESU FT-50R / 40R / 10R:</b>		<b>For ICOM IC-2SAT / W2A / 3SAT / 4SAT etc:</b>	
FNB-40xh (5w) (NiMH)	7.2v 650mAh \$41.95	BP-93 pack	7.2v 600mAh \$23.95
FNB-47xh (5w) (NiMH)	7.2v 1800mAh \$49.95	For ICOM 02AT etc & Radio Shack HTX-202 / 404:	
FNB-41xh (5w) (NiMH)	9.6v 1000mAh \$49.95	BP-8h pack	8.4v 1400mAh \$32.95
<b>For YAESU FT-51R / 41R / 11R:</b>		BP-202S pack (HTX-202)	7.2v 1400mAh \$29.95
FNB-38 pack (5w)	9.6v 700mAh \$39.95	For KENWOOD TH-79A / 42A / 22A:	
<b>For YAESU FT-530 / 416 / 816 / 76 / 26:</b>		PB-32xh pack (NiMH)	6.0v 1000mAh \$29.95
FNB-26 pack (NiMH)	7.2v 1500mAh \$32.95	PB-34xh pack (5w) (NiMH)	9.6v 1000mAh \$39.95
FNB-27S (5w) (NiMH)	12.0v 1000mAh \$45.95	For KENWOOD TH-78 / 48 / 28 / 27:	
<b>For YAESU FT-411 / 470 / 73 / 33 / 23:</b>		PB-13 (original size)	7.2v 700mAh \$26.95
FNB-11 pack (5w)	12.0v 600mAh \$24.95	For KENWOOD TH-77, 75, 55, 46, 45, 26, 25:	
FBA-10	6-Cell AA case \$14.95	PB-6x (NiMH w/rotp) pack	7.2v 1200mAh \$34.95
<b>Packs for ALINCO DJ-580 / 582 / 180 radios:</b>		Mail, phone, & Fax orders welcome! Pay with Mastercard / VISA / DISCOVER / American Express	
EBP-20ns pack	7.2v 1500mAh \$29.95	<b>Call 608-831-3443 / Fax 608-831-1082</b>	
EBP-22nh pk (5w)	12.0v 1000mAh \$36.95	<b>Mr. NiCd - E. H. Yost &amp; Company</b>	
EDH-11	6-Cell AA case \$14.95	2211-D Parview Road, Middleton, WI 53562	
<b>For ICOM IC-21A / T22-42A / W31-32A / T7A:</b>		<b>CALL OR WRITE FOR OUR FREE CATALOG!</b>	
BP-180xh pk (NiMH)	7.2v 1000mAh \$39.95	Cellular / Laptop / Videocam / Commercial & Aviation packs too!	
BP-173 pack (5w)	9.6v 700mAh \$49.95	E-mail: <a href="mailto:ehyost@midplains.net">ehyost@midplains.net</a>	
<b>For ICOM IC-W21A / 2G/XAT / V21AT (Black or Grey):</b>			
BP-132S (5w) (NiMH)	12.0v 1500mAh \$49.95		


**Great Books for Hobbyists,  
Students, Engineers . . .**

**Simple, Low-Cost Electronics  
Projects**

by Fred Blechman

Learn electronics with Fred Blechman's exciting new book. Begin with simple designs and progress to more sophisticated projects. Each project comes with a complete discussion of circuit theory and parts list, as well as information on troubleshooting and testing. Build voltmeters and multimeters, inductance and semiconductor testers, variable frequency audio oscillators, a photoelectric counter, and much more!

1-878707-46-9/224 pages/\$19.95

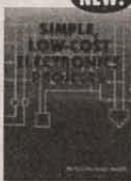


**Controlling the World with Your PC**

by Paul Bergsman

PC Disk Included! Connect your computer to the real world and make it do useful work like controlling stepper motors, turning appliances on and off, or monitoring fluid levels. PC disk contains software files in ready-to-use form.

1-878707-15-9/208 pages/\$35.00

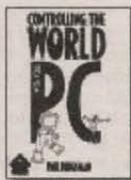

**The Forrest Mims Engineer's  
Notebook**

by Forrest Mims III

This revised edition of Forrest's classic book includes hundreds of useful circuits built from integrated circuits and other parts available from convenient sources.

1-878707-03-5/156 pages/\$19.95




**The Integrated Circuit Hobbyist's  
Handbook**

by Thomas R. Powers

Covers the major types of integrated circuit devices—linear, TTL, and CMOS—and provides complete details and theory about their operation. Contains lots of useful application circuits—an essential reference for every hobbyist.

1-878707-12-4/256 pages/\$19.95

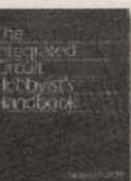

Order on the Web!

For these and other great books on electronics, visit:  
[www.LLH-Publishing.com](http://www.LLH-Publishing.com)

or call 1-800-247-6553 to use a major credit card, or send check or money order to:



LLH Technology Publishing  
3578 Old Rail Road  
Eagle Rock, VA 24085

**TECH FORUM**

the trick.

One converts VGA to RGB + Sync and one converts VGA to R G/Sync B. They may be able to tell just which one you need for your particular monitor. Their phone number is 314-937-0335.

John McMichael  
Laramie, WY

**ANSWER TO #129813 - DEC. 1998**

The stripes in the new currency are used as a measure against counterfeiting. These stripes cannot be scanned from outside your home to see how much money you have in your possession.

Mark Hanz  
Houston, TX

**ANSWERS TO #129820 - DEC. 1998**

The "Apple II Emulator Resources Guide" found at: <http://www.faqs.org/faqs/apple2/emulators-faq/part1/> is the best resource for Apple II emulator and interface information.

I am not sure if it's possible to directly connect an Apple II drive to a PC, because PC drives and Apple drives use different encoding techniques. There are a number of methods available to transfer the information from an Apple II diskette to a ROM image for use with an emulator.

It is possible to transfer disk images "on the fly," in which an Apple II will simultaneously create and send images via null-modem cable to a host computer. The easiest method for creating disk images on the Apple II and transferring them to the PC is by using "Ap222PC" by Clay Chang (found at [ftp://ftp.apple.asimov.net/pub/apple\\_utility/ap222pc.zip](ftp://ftp.apple.asimov.net/pub/apple_utility/ap222pc.zip)). AP222PC will transfer disk and

**ANSWER TO #129812 - DEC. 1998**

The adapter you need to connect your video camera to a TV can be purchased at RadioShack. It is called a video RF modulator (cat. #15-1283) and is priced at \$29.99. This unit will convert the line-level video from your video camera to TV channel 3 or 4.

Depending on the plug style on your camera's video output cord, you may also need to buy an adapter to connect to the video RF modulator. RadioShack should also have such an adapter if you need one.

John McMichael  
Laramie, WY

**ANSWER TO #129811 - DEC. 1998**

Although you should follow the

sequential text files between the PC and Apple using the Apple game I/O port and a PC parallel port.

In-depth details of all facts of Apple II emulators can be found in the above listed resource guide.

Joe Grand

**ANSWERS TO #129820 - DEC. 1998**

Mr. Reynolds indicated that he wants to interface an Apple II floppy drive directly to his PC to create disk images, but I believe there is a much simpler way. Why not just interface the entire Apple II computer to your PC to transfer the disks and create images?

I will assume that you have access to an Apple II with floppy drive and serial port. I believe the //c and //gs came with a serial port already installed, and controller cards for others models are readily available from several sources.

You can connect your Apple II and PC together with a null modem

manufacturer's recommendations for charging batteries, you do not have to be a fanatic. Understanding what's going on will show the reasoning behind charging profiles and how and why they may be modified.

For reference, I recommend a book by Gates Energy Products, *Rechargeable Batteries Applications Handbook*, Butterworth-Heinemann 1992.

There is also T. R. Crompton, *Battery Reference Book, Second Edition*, Society of Automotive Engineers, 1996.

Batteries are recharged by running a current through them. The larger the current, the more quickly the battery will reach full charge. Battery design determines how large

cable, and run some free software to transfer disks.

Check out <http://geta.life.uiuc.edu/~badger/files/ad120.zip> (Apple Disk Transfer 1.20) for the software needed to create/transfer the disk images. The program is well documented and even contains pinouts for the null modem cable, in case you need to construct one.

According to the program documentation, the program will create 140K disk images that are compatible with the ap12em Apple emulator. Overall, this solution should be less costly and time consuming than designing and constructing an interface to the floppy drive itself.

It's nice to see people still supporting such a great computer. For additional Apple II references, take a look at <http://geta.life.uiuc.edu/~badger/apple2.html> and <http://www.apple2.org>.

Jason Plumb  
Lubbock, TX

**ALFA ELECTRONICS**  
HIGH QUALITY TEST EQUIPMENT

Visit [www.alfaelectronics.com](http://www.alfaelectronics.com) for complete info  
Call 1-800-526-2532 for Order and Free Catalog

DMM	TOP/COUNTER	TRIPLE	SPECIALTY
<p><b>DMM-895</b> (\$179.00): true rms, AC/DC (V,A), <math>\Omega</math>, bar graph, freq, capac, dBm, logic, diode</p> <p><b>DMM-23T</b> (\$99.95): 4 1/2 digit, true rms, high resol (10pV, 10nA, 10m<math>\Omega</math>), hFE, diode, contin.</p> <p><b>DMM-20</b> (\$74.95): AC/DC (V, A), Freq, cont., Capac, Induct, <math>\Omega</math>, hFE, diode, duty cycle</p> <p><b>DMM-122</b> (\$59.95): DC/AC(V,A), <math>\Omega</math>, hFE, diode, capacitance, freq, logic, continuity</p> <p><b>DMM-123</b> (\$44.95): DMM + capacitance, DC/AC(V,A), <math>\Omega</math>, hFE, diode, continuity</p> <p><b>DMM-10</b> (\$19.95): 3 1/2 digit, DC/AC (V, <math>\Omega</math>, hFE, diode, signal output (+3V, -0.5Vsq, 50% duty)</p>	<p><b>CAP-15</b> (\$49.95): 3 1/2 digit, 0.1pF-20mF, 9 Ranges, 0.1pF resolution, zero adjustment</p> <p><b>LCR-24</b> (\$179.95): 0.1pH-200H, 0.1pF-2000pF, 0.01G-20M<math>\Omega</math>, diode test, New Model</p> <p><b>LCR-131D</b> (\$219.95): autorange, 0.1uH-10kH, 0.1pF-10mF, 1m<math>\Omega</math>-10M<math>\Omega</math>, Q Factor, serial/parallel, 120Hz/1kHz testing mode</p> <p><b>FC-1200</b> (\$129.95): 1.25GHz Handheld, 8 digit display, 10ppm accuracy, sensitivity 5mV (130-350MHz), 30mV (400MHz)</p>	<p><b>PS-303</b> (\$159.00) 30V/3A</p> <p><b>PS-801</b> (\$239.95) 30V/5A</p> <p><b>PS-1830</b> (\$198.95) 18V/3A</p> <p><b>PS-1850</b> (\$214.95) 18V/5A</p> <p><b>PS-1830D</b> (\$214.95) 18V/3A</p> <p><b>PS-1850D</b> (\$244.95) 18V/5A</p>	<p><b>AC Current Probe</b> \$34.95</p> <p><b>DC/AC Current Probe</b> \$79.95</p> <p><b>Mini AC Clamp</b> \$59.95</p> <p><b>AC Clamp w/temp</b> \$89.95</p> <p><b>DC/AC Clamp</b> \$109.95</p> <p><b>Thermometer</b> \$69.95-\$89.95</p> <p><b>IR Thermometer</b> \$189.95</p> <p><b>Sound Level Meter</b> \$169.95</p> <p><b>Tachometer</b> \$169.95-\$219.95</p> <p><b>EMF Tester</b> \$69.95</p> <p><b>Pressure Meter</b> \$299.95</p> <p><b>Watt Meter</b> \$129.95</p> <p><b>High Voltage Probe</b> \$59.95</p> <p><b>pH Meter</b> \$79.95</p> <p><b>Light Meter</b> \$79.95-\$89.95</p>
<p><b>Single Output DC Power Supplies</b></p> <ul style="list-style-type: none"> <li>Constant current, constant voltage mode</li> <li>Short Circuit and overload protected</li> </ul>		<p><b>Triple Output</b></p> <ul style="list-style-type: none"> <li>Independence of Tracking operation</li> <li>Parallel to double current output (PS-8102 &amp; PS-8103 only)</li> </ul>	
<p><b>Audio/RF/FUNCT. GEN.</b></p> <ul style="list-style-type: none"> <li>RF Generator • <b>SG-4160</b> (\$124.95) 100kHz-150MHz sinewaves in 8 ranges</li> <li><b>SG-4162AD</b> (\$229.95) with 6 digit counter</li> <li>Audio Generator • <b>AG-2601</b> (\$124.95) 10Hz-1MHz, 0-8Vpp sine, 0-10Vpp squarewave</li> <li><b>AG-2603AD</b> (\$229.95) with 6 digit counter</li> <li>Function Generator • <b>FG-2108A</b> (\$154.95) 0.2Hz-2MHz, 5mV-20Vpp</li> <li><b>FG-2103</b> (\$329.95) Sweep 0.5Hz-5MHz</li> </ul>			

GWINSTEK <sup>®</sup> DC POWER SUPPLIES				FUNCTION GENERATOR	BENCHTOP DMM	
20 MHz Scope	Cursor Readout	Triple Output	Single Output	Programmable		
<p><b>OS-620</b> \$324.95</p> <ul style="list-style-type: none"> <li>Most economical scope</li> <li>Dual CH/X-Y operation</li> <li>1 mV/div sensitivity</li> <li>Z-axis input, CH1 output</li> <li>TV syn. ALT trigger</li> <li>2 probes (x1, x10)</li> </ul>	<p><b>OS-626G</b> \$599.95</p> <ul style="list-style-type: none"> <li>Readout a Cursor means</li> <li>Dual CH / Delay sweep</li> <li>Built-in delay line</li> <li>ALT trigger, Hold-Off</li> <li>Z-axis input, CH1 output</li> <li>2 probes (x1, x10)</li> </ul>	<ul style="list-style-type: none"> <li>2 variable out 0-30V, 0-3A</li> <li>One fixed 5V, 3A output</li> <li>Auto track, serial, parallel</li> <li>Const. volt, current mode</li> <li>4 analog or 2 digital display</li> </ul> <p><b>PC-3030</b> (\$499.95)</p> <p><b>PC-3030D</b> (\$549.95) digital</p>	<ul style="list-style-type: none"> <li>Const voltage, current mode</li> <li>Voltage regulation &lt;0.01%</li> <li>Current regulation &lt;0.2%</li> </ul> <p><b>PS-1830</b> (\$198.95) 18V/3A</p> <p><b>PS-1850</b> (\$214.95) 18V/5A</p> <p><b>PS-1830D</b> (\$214.95) 18V/3A</p> <p><b>PS-1850D</b> (\$244.95) 18V/5A</p>	<ul style="list-style-type: none"> <li>Auto serial/parall (PPT ser)</li> <li>Auto track (PPT series), IEEE-488.2 and SCPI compatible command set</li> </ul> <p><b>PPS-1860G</b> (\$1,149.95) 18V/6A</p> <p><b>PPS-3630G</b> (\$2,199.95) 36V/3A</p> <p><b>PPT-1830G</b> (\$1,499.95) 18V/3A</p> <p><b>PPT-3630G</b> (\$2,499.95) 36V/3A</p>	<p><b>FG-8020G</b> (\$209.95)</p> <ul style="list-style-type: none"> <li>0.02Hz-2MHz w/pulse</li> <li>Sine/Sqr/Tri/w/comp Ramp</li> </ul> <p><b>FG-8020G</b> (\$209.95)</p> <ul style="list-style-type: none"> <li>0.02Hz-2MHz w/counter</li> </ul> <p><b>FG-9050</b> (\$149.95) Sweep 0.05Hz-5MHz w/counter <p><b>INT/EXT AM/FM</b> w/counter </p></p>	<p><b>DM-8034</b> (\$179.95) 3 1/2 digit</p> <ul style="list-style-type: none"> <li>AC/DC(V,A), <math>\Omega</math>, diode</li> <li><b>DM-8048</b> (\$339.95) 3 1/2 digit</li> <li>ACV to 50kHz, true rms</li> <li><b>DM-8055G</b> (\$889.95) 5 1/2 digit</li> <li>0.006% accuracy, GPIB -d, dBm, auto REL, min/max</li> </ul>

**ALFA ELECTRONICS** P.O. BOX 8089 PRINCETON, NJ 08543-8089  
**TEL: (800) 526-2532 / (609) 897-1135**  
**FAX: 609-897-0206**  
**E-mail: [sales@alfaelectronics.com](mailto:sales@alfaelectronics.com)**  
 Call / Write / Fax / Email for FREE CATALOG  
 Visa, MC, AMEX, COD, PO Accepted. OEM Welcome.  
 1 Year Warranty (2 Years for GWIN/Instek)

# TECH FORUM

the charging current may be — and for how long.

The major limitation occurs when the battery is recharged but is still receiving a recharge current — the condition is called overcharge.

Near full charge in modern sealed batteries, the charging current produces oxygen at the positive plate, and this oxygen increases the pressure inside the cell. Ideally, this oxygen migrates to the negative electrode where it harmlessly recombines with some extra cadmium hydroxide.

The recombination releases the heat that makes the cell temperature rise, and this heat balances the electrical energy of the charging current. The migrating oxygen allows a battery to handle some overcharge current, but how much overcharge current depends on the cell design. If the overcharge current is too large, then the pressure becomes too high and the cell vents through a safety valve. Venting causes a sealed cell to lose capacity and shortens its life. Consequently, cells should not be overcharged beyond their design specifications.

There are three common battery types: standard charge, quick charge, and fast charge.

The capacity of a battery is rated in ampere-hours, and the charging rates are commonly specified as a fraction of C, which is the battery capacity divided by one hour.

A D-size battery might have a 4 ampere-hour rating. The standard charge rate is 0.1 C, so it should be recharged at 400mA (or less). The charging process isn't perfect, so it takes about 14 hours to recharge a battery at the 0.1 C rate — about 40% longer than expected. The battery should not be damaged by a 0.1 C overcharge that lasts for days.

Quick charge batteries can be charged at up to 0.33 C, so they reach full charge within four to five hours.

Although the cell is designed to withstand this high rate, it should not be left on the charger indefinitely.

For example, my Black and Decker drill wants the charge stopped after five hours.

Some chargers will use the quick charge rate for a few hours and then switch to rate less than 0.1 C. Such a charger will not damage a cell that is left in the charger.

Fast charge cells can be charged at rates as high as 4C, so they can recharge a battery in 20 minutes, but the charging current must be reduced before the cell is fully charged.

To fast charge a cell, you need a charger that senses when the cell nears full charge and adjusts its charging rate. The charger can tell it is near full charge when the battery temperature rises.

Many batteries are trickle

charged [0.05 to 0.1 C] to keep them fully charged during long periods of inactivity.

Gerald Roylance  
Mountain View, CA

## ANSWER TO #12984 - DEC. 1998

The GP1U52X IR receiver is manufactured by Sharp, and is also sold by RadioShack as part #276-0137. You can find a copy of the data sheet at [http://support.tandy.com/support\\_supplies/17533.htm](http://support.tandy.com/support_supplies/17533.htm).

Also, if you're trying to build transmitter and detector circuits with this device, you may find the following URLs useful: <http://www.wirz.com/tutorial/IR/index.html> and <http://www.seattlerobotics.org/guide/infrared.html>.

Another good source for IR circuits in general is <http://godot.tuniv.szczecin.pl/~mjaskula/tomi/opto.html>

Mark Winters  
Orem, UT

## ANSWER TO #12981 - DEC. 1998

I don't know where you can get a copy of IDE, but getting the USB spec is very easy — you can download the spec from [www.usb.org](http://www.usb.org).

Gerald Roylance  
Mountain View, CA

## ANSWER TO #12982 - DEC. 1998

Everyone should connect a pair of VU meters to his stereo system!

When my brother and I were in our teens, we saved up our money until we could afford to do it. It must have done something good, because we both became broadcast engineers.

A quick check of the 1969 Allied Electronics catalog shows a 4.5" Simpson "Wide-Vue" VU meter for \$32.10 ... pretty pricey in terms of 1969 allowance dollars!

If you have a pair of true VU meters, consider yourself lucky.

Nowadays, these have been largely replaced by DC voltmeter movements that are driven by an electronic buffer circuit. A true VU meter is typically a 200-microampere D'Arsonval movement, with an internal resistance of 3900 ohms. A fullwave diode bridge inside the meter case converts the audio (AC) into DC to drive the meter. The meter is intended to be used to measure a 600-ohm audio circuit.

Of course, a diode will not conduct below a certain threshold voltage, and as the meter diodes switch between non-conduction and conduction, this slightly changes the amount of current that the meter draws from that 600-ohm audio line, and introduces a slight amount of distortion to the sound. To reduce this distortion, the standard 3900-ohm VU meter was intended to be used with a 3600-ohm series resistance, bringing the total resistance to 7500 ohms.

## Top Quality Reconditioned Electronic Test Equipment

Hewlett-Packard • Tektronix • Fluke • Wavetek

Buy • Sell • Rent • Trade

Shop our On-Line Catalog

<http://www.bellelect.com>

650-579-1711 • Fax 650-579-5777

Corporate Offices: Seattle WA 425-251-6653  
1479 Rollins Road 285 S.W. 41st Street  
Burlingame CA 94010 Renton WA 98055



### Looking for Test Equipment Manuals?

Contact: Manuals Plus (435)882-7188 • Fax (435)882-7195

<http://www.manualsplus.com>

Write in 138 on Reader Service Card.

With this series resistance, the meter would read zero VU, or 100%, with 1.228 vRMS [+4 dBm] applied.

A further need for the series resistance is so that the meter will have the proper ballistic characteristics ... when a signal is applied, the needle will rise at the proper rate, and will come to rest without excessive overshoot and "bouncing around."

A standard VU meter has been designed to have proper ballistics when fed through that 3600-ohm resistance, and if you change or eliminate that resistance, the ballistics will suffer.

How do you connect the VU meter to the speaker wiring of your stereo system? The simplest hook-up is to connect one terminal of the meter to the "common" speaker terminal, and connect the other meter terminal, through a 3600-ohm series resistor, to one channel's "hot" speaker terminal. Connected that way, the meter will read zero VU when 1.228 VRMS is present across the speaker. If you assume your speaker has an eight-ohm impedance, that will actually be a power

level of 188 mW.  $P = E^2/R; [1.228]^2/8 = 0.188 W$ .

That's pretty quiet, by most listeners' standards.

In fact, this measurement will be only approximate, for two reasons.

First, a VU meter reads accurately only with a steady-state sinewave input. With a complex waveform, such as music or speech, the meter indicates somewhere between the average and peak values of the waveform.

Second, the impedance of the loudspeaker varies with frequency. So even if the meter is measuring a steady sinusoidal tone, you would need to know the speaker's actual impedance at that frequency, and then re-calculate the actual power delivered.

Unless you listen at exceedingly low audio levels, you'll probably want to add some attenuation to your meter circuit.

For ballistic reasons, always keep that 3600-ohm resistance in series with the meter, and connect the attenuation between the loudspeaker terminals and the resistance. *Continued on page 63*

## WHOLESALE CABLE

### COMPLETE LINE OF CABLE PRODUCTS

- Quality merchandise by brand name manufacturers
- Satisfaction guaranteed  Free gift on first order
- Technical support
- 2 year warranty on new converters
- COD shipping & overnight shipping by request
- Experience where it counts  Volume pricing

PLAIN CONVERTERS: ZENITH, OAK, PANASONIC, PIONEER, EAGLE, HAMLIN, STARGATE, PLUS MORE.

REMOTE CONTROLS: ALL MAJOR BRANDS, INCLUDING 2-4 FUNCTION UNIVERSAL REMOTES

WHOLESALE CABLE M-F 11am-6pm EST (800) 909-4333  
(718) 262-0900 • FAX (718) 657-4015 • (718) 297-9221

No NY sales. Federal and local laws provide criminal and civil penalties for unauthorized use. Check with your cable providers for permission to use equipment. Must be paying for all services you receive. Order by model number only. Some equipment refurbished as new.

Tell us the best price you were offered, where you got it from, and let us try to beat it.



**TEST EQUIPMENT cont.**

**DEC EQUIPMENT WANTED!!!** We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), DSD, Datability, Dilog, other DEC compatibles, and Computer Output Microfilm (COM) units. Please call for a quote or fax us your equipment list. We buy, sell, and trade. **KEYWAYS, INC.**, 937-847-2300 OR fax 937-847-2350.

**YIG OSCILLATORS** wanted from old HP, Tek, WJ, Advantek, etc., products. Paying between 50 and 150 dollars typical. Please fax list to 804-794-8284 or E-Mail: avcom@richmond.infi.net


**OTHER TEST equipment** Racal Dana 9303 true RMS level meter with head as new, \$375; Fluke 8921A true RMS volt-meter, \$300; Phillips PM 6654 high resolution programmable timer counter, \$350; Wavetek 178 programmable waveform synthesizer, \$825. Psitech Plus, 707-745-4804, www.psitech-plus.com.

**HP 8640B**, 001,002,003, manual, \$1,195; **HP 8660A/86602A/86633B**, \$1,695; **TEK 465M**, \$349; **Wavetek 1001A**, \$149; **HP 334A**, \$100; **TEK AM 502**, \$100; **HP 6006A**, \$149; **HP 8620C**, 5.9-9GHz, \$249; **TEK 7844**, opt. 3.22,78, \$139. Technologies West, 541-267-6064.

**HP 54602B** 4 ch. 150MHz digital oscilloscope, opt 5 (enhanced video trigger), benchlink module/software (RS232 out), training kit probes, transferable HP warranty til 9/99, normally priced at \$5,000, sale price as new at \$2,500. Sorenson DCR-115B DC PS, 0-20V, 0-115A, CVCC, dual meter 220 input, \$800. 201-796-1405.

**CESIUM/RUBIDIUM** repairs, free estimates. 13 Tektronix catalogs 1967, 70s, most 80s, \$120; GR1412BC capacitance decade, \$100; Fluke clamp on ammeter 80I-410, \$50; Rubidium modules, \$425; Quartz modules, \$175-\$250. Corby Dawson, 805-736-0288.

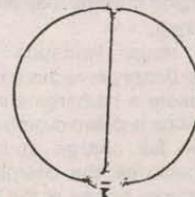**USM 338 HP 1700B/300**, \$150; Heathkit frequency counter SM2420 0-512MHz \$29; Tek 191 sig-gen \$50; Call 909-873-1319.



**WANTED: LOOP ANTENNA 10509A** from Hewlett Packard 117A any condition. Call Greg after 7pm EST 305-261-0929.

## Tired of Expensive Inkjet Cartridges ? Save 90% on Inkjet Inks !

Printer	# of Refills		Cost/Refill		Kit Price	
	Black	Color	Black	Color	Black	Color
HP 500 Series, 400, Officejet 300, 350, Fax	7	14	4.71	2.85	32.95	39.95
HP 600 Series, Officejet 500, 570, 600	7	14	4.71	3.21	32.95	44.95
HP 800 Series, 1000C, 1150C, Copier 120, 210	6	10	6.67	4.00	39.95	39.95
HP 720C, 722C, 890C, 1120C	6	10	6.67	4.50	39.95	44.95
Canon BJ-10, 200, 210, 240, 250 Apple SWriter 1200, 1500	14	20	2.15	2.00	29.95	39.95
Canon BJC-4000 Series, C2500, C3000, C3500, C5000	60	60	0.50	0.67	29.95	39.95
Apple StyleWriter 2400, 2500						
Canon BJC-600, 610, 620 Apple SWriter Pro	20	13	1.50	3.07	29.95	39.95
Epson Stylus Color, Color Pro, Pro XL	12	12	2.50	3.33	29.95	39.95
Epson Stylus Color II, IIs	15	15	2.00	2.66	29.95	39.95
Epson Stylus Color 500, 200	20	17	1.50	2.35	29.95	39.95
Epson Stylus Color 400, 600, 800, 850, Photo	20	17	1.50	2.65	29.95	44.95
Lexmark JP 1000, 1020, 1100, ExecJet II, IIC, Medley 4C	10	17	3.00	2.35	29.95	39.95
Lexmark JetPrinter 5700, 5000, 7000, 7200	10	17	4.00	2.35	39.95	39.95
Xerox Home Center 450C, XJ6C Inkjet	22	12	1.36	3.33	29.95	39.95

## SAVE 30 - 50% on New Compatible Cartridges!

Printer	BLACK CARTRIDGE	COLOR CARTRIDGE
Canon BJC-4000 Series, C2500, C3000, C3500, C5000	\$5.50	\$12.95
Apple StyleWriter 2400, 2500	\$5.50	\$12.95
Canon BJC-600, 610, 620 Apple StyleWriter Pro	\$4.95 (9cc)	\$4.95 @ (9cc)
Hi-Capacity Canon BJC-600, 610, 620	<b>\$5.95 (15cc)</b>	<b>\$5.95 @ (12cc)</b>
Canon BJC-70, BJC-80	\$9.95 (3-pak)	\$14.95 (3-pak)
Epson Stylus Color, Color Pro, Pro XL	\$12.00	\$19.00
Epson Stylus Color II, IIs	\$14.00	\$19.00
Epson Stylus Color 500, 200	\$14.00	\$19.00
Epson Stylus Color 400, 600, 800, 850, 1520, Photo	<b>\$14.00</b>	<b>\$19.00</b>


- **BULK Inks, Refill Accessories**
- **Glossy card stock & Coated Paper**
- **School & Government PO's Welcome**
- **2 - 3 Day Shipping**

**Quality Inks for:**  
HP • Epson • Lexmark  
Canon • Apple • DEC

**Call or see us online!**

Monday - Friday  
7:30 - 4:30 PST 10:30 - 7:30 EST

**Inkjet Southwest**

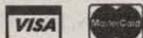

**www.inkjetsw.com**

(602) 668-7334 Fax

**1-800-447-3469**

(602) 668-0959

## SECURITY

**SURVEILLANCE EQUIPMENT** wanted. Audio, video, RF, telephonic, countersurveillance, communications, any other professional equipment. Fax 410-836-1190. E-Mail to Sales@swssec.com Voice 410-879-4035. www.swssec.com/used.html.



**FACTORY SALE! QVS 104:** 4 BNC/RCA 12 pixels, 256 scale. 8.5" (W) x 2" (H) x 5.5" (L). \$169 @ 5 pcs., \$149 @ 10 pcs. Also available: 8-1 video auto-switcher, \$65 @ 5 pcs., \$58 @ 10 pcs. Distributors welcome. Matco, Inc., 1-800-440-0299 Fax: 630-350-9546. E-Mail: sales@matco.com Web site www.matco.com

**8 CAMERA DUO-QUAD DISPLAY BLOW-OUT.** 8 camera B+W 2 page hires. real-time quad w/2 video outputs. Selectable display quad/sequencer or both. These units are brand new discontinued American Dynamics AD1475A. Similar units in this magazine are twice the price. Not a China imitation. Industrial unit. Our reg. price \$350, **NOW \$175 EA.** While they last! Pro-Vid Sys. 781-933-0827. E-Mail: RicksVideo@MSN.COM



**FACTORY SALE! PS 102:** Built-in pin hole CCD, lens size: 1.2mm. 5-1/2" (D) x 1.7" (H). \$69 @ 5 pcs., \$65 @ 10 pcs. Distributors welcome. Matco, Inc., 1-800-440-0299 Fax: 630-350-9546. E-Mail: sales@matco.com Web site www.matco.com




**FACTORY SALE! CNL100, CNP101:** 1/3" CCD, 430 line horiz., 12V/100mA, lens and pin hole types, lens 3.6mm/F2.0, 1.27" (W) x 1.27" (L) x 1" (H). \$43 @ 5 pcs., \$38 @ 10 pcs. Distributors welcome. Matco, Inc., 1-800-440-0299 Fax: 630-350-9546. E-Mail: sales@matco.com Web site www.matco.com

**MILITARY COMPONENTS** wanted. Capacitors, resistors, diodes, transistors, semiconductors, ICs. Electronic Material Industries, 818-769-1002, FAX: 818-769-1084.

**ALARM CATALOG** of panels, motion detectors, contracts, CCTV & more. Equipment that only the professionals can buy. Send \$2 to HES Electronics, POB 183, Brick, NJ 08723. Mention this ad and get a \$10 off certificate! Visit [www.heselectronics.com](http://www.heselectronics.com)



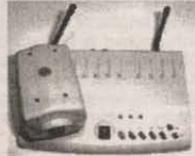**FACTORY SALE!** IC 113: PIR motion detector w/ NO/NC alarm output. CCD camera with audio can be turned on by detector. 5-1/4" (L) x 2-3/4" (W) x 2" (D). \$89 @ 5 pcs., \$82 @ 10 pcs. Matco, Inc. 1-800-440-0299 Fax: 630-350-9546. E-Mail: [sales@mat-co.com](mailto:sales@mat-co.com) Web site [www.mat-co.com](http://www.mat-co.com)



**FACTORY SALE!** AS 1000, 2.4GHz transmitter & receiver. Capable handling total of 4 wireless cameras, range: >300'. Built-in camera, 380 TV line. \$189 @ 5 pcs., \$179 @ 10 pcs. Additional camera \$99 @ 10 pcs. Matco, Inc. 1-800-440-0299 Fax: 630-350-9546. E-Mail: [sales@mat-co.com](mailto:sales@mat-co.com) Web site [www.mat-co.com](http://www.mat-co.com)

**FREE FULL COLOR CATALOG.** Hidden cameras in lamps and teddy bears ready for use, personal alarms, and many other personal protective and safety devices. Send request to: GTH3 Computers, PO Box 4434, Oceanside, CA 92052-4434 or [gth3@mailcity.com](mailto:gth3@mailcity.com)

## SATELLITE EQUIPMENT

**USED SATELLITE EQUIPMENT.** You name it, we have it. LNAs, downconverters, drives, receivers. Working condition guaranteed. Call 765-385-2305.



**BEST PRICING** on 18" satellite TV systems for home and RV. DSS, DISH Network programming, multi-room viewing options, accessories. [www.skyvision.com](http://www.skyvision.com) Call 1-800-543-3025.

**FREE SATELLITE TV CATALOG.** Tech books, installation videos, analysis software 1-800-843-2425 or [www.baylin.com](http://www.baylin.com)

**L BAND** quadrifilar T/R antenna, 55 dB LNA, 20 watt HPA, works great for remote GPS. Info at [afstar.com](http://afstar.com)



**FREE BIG dish catalog.** Low prices! Systems, upgrades, parts, and "4DTV." Skyvision, 1010 Frontier Dr., Fergus Falls, MN 56537. [www.skyvision.com](http://www.skyvision.com) Call 1-800-543-3025.

**MILITARY TRANSISTORS & DIODES & INTEGRATED CIRCUITS WANTED.** ELECTRONIC MATERIAL INDUSTRIES 818-769-1002, FAX 818-769-1084.

**1998 DSS SOFTWARE COOKBOOK 700+ CD-ROM COLLECTION**  
CLONING REVERSE-ENGINEERING, PPV, ADULT, EMULATORS, DIAGRAMS, SCHEMATICS, PATCHES, PLANS, MUCH MORE. (SPECIAL: 1ST 500 ORDERS GET 500+ ADDITIONAL PROGRAMS!) WHOLESALE ONLY \$22 (BUY 2, GET 1 FREE!!!). DSS TEST-CARD INFO SOURCE MANUAL \$10. VISA/MC/AMEX/COD/CHECKS/MO. BRINKER ENGINEERING LABS, USA. CALL NOW 352-429-5496.

**WHAT! YOU** don't have TELECODE's NEW 1998-9 "HACKER CATALOG," yet! 125+ items. Call 520-726-2833. Surf online at <http://www.hackerscatalog.com>

**SATELLITE EQUIPMENT** available: Receivers \$25 and up; 20-25 LNB \$30; C-KU feed horns \$65. Call 757-599-4408.

**FREE SATELLITE TV INSTALLATION TOOLS AND EQUIPMENT CATALOGUE:** for complete installation. Consumers, dealers, distributors and technicians welcome. 1-800-646-8665 or [www.natropolis.com](http://www.natropolis.com) or fax 651-641-1898. Natropolis, Int'l, PO Box 14115, St. Paul, MN 55114.

**DSS AUTOMATIC LNB cutoff.** Very low noise, no adjustments, works with all models. \$60 each, plus shipping charges. 10% discount for 10 or more. Call 703-764-5118 to place an order.

**SATELLITE RADIO BOOK AND GUIDE.** New book covers all Audio Services, SCPC, Subcarriers, FM Squared, Facsimile, Press Services, Weather Services. Simple how-to-receive instructions. \$16.95 plus \$3 Priority Mail. UNIVERSAL ELECTRONICS, 4555 GROVES ROAD, #12, COLUMBUS, OH 43232. 614-866-4605.

**THE BEST** is back to stay. Master code recovery. 16c5x, 16c62x, PALS, GALS, other microcontrollers, etc. Check out our web page at [www.acdinc.com](http://www.acdinc.com) for details or call 703-764-5361 or write Advanced Circuit Designs, Inc., 5765-F Burke Centre Parkway, Suite 317, Burke, VA 22015.

# RAINBOW KITS

**FAN CONTROLLER**  
Use this kit to control cooling fans, or any device that is temperature activated. Output is 100mA. For a 3 Amp application use the Relay kit RP-1 or the new Micro-controlled Relay PRC-1 kit. Temperature probe included. Operating voltage: 7.5 to 18v DC. Size: 1.5" x 1.2"

(Temperature Range 32° - 200°F)

FC-1 KIT \$14.95

**FLASHING SAFETY LIGHT**  
• Push ON / Push OFF switch.  
• Flashes 3 weeks on 2 AAA batteries.  
• Great for kids, bike riders and joggers.  
• Keep in car for emergencies.  
• Tough ABS case with belt clip.  
• Size: 1 3/8" x 2 1/4" x 1 1/8"

BFL-3 BUILT \$6.95  
2 for \$9.95

**WIDE BAND PRE-AMP** Uses PCB and surface mount technology for better performance. Use this for scanners, HT's, Frequency counters, Satellite Receivers. It amplifies low-level (weak) signals. If the signal is extremely low two amplifiers can be used in a series.

• 1MHz to 2.5 GHz 2.8dB NF  
• 1dB compression=0dBm  
• Gain: 1MHz- 20dB to 2.5GHz-6dB  
• Power requirement: 12v @ 6mA

WBA-6 BUILT \$19.95

**KEY CHAIN LASER PEN**  
Comes with 4 extra heads  
• Smiley face • I Love You • Hearts • Skull (all different) 2 1/2" Long 4mm/650 nm

LP-4 BUILT \$12.95

**TV NOTCH FILTERS**  
FOR CHANNELS 2 thru 22 ONLY  
Our TV filters eliminate unwanted TV channels or interference that alters both sound and video with a BEEP BEEP BEEP. Works on cable channels (2 thru 22) only.

NOTE: All TV Filter Kits are sold for educational purposes only. You must obtain permission from your local cable company before using these filters on your cable system.

DF-222 KIT \$14.95

**FM STEREO TRANSMITTER** Have your own FM radio station. Any stereo signal you plug into the FMST-100 transmitter kit will be transmitted to any FM radio tuneable from 76 to 108MHz FM. Plug in your CD player, tape deck and have a wireless link to any FM radio, within 200 ft. Listen to your CD while mowing the lawn. Transmit from your car to your camper, or through an auditorium. Transmit music on one channel sing on the other. Compatible with any audio system. Clarity is excellent, approx. 40dB stereo separation. Length of antenna determines distance of transmission. Comes complete with left & right input level control as well as a crystal for left & right stereo separation. ANTENNA NOT INCLUDED 9v Battery operation.

FMST-100 SIZE: 1.5" x 1.6" KIT \$29.95  
Cabinet SIZE: 1.5" x 2.5" x 3" \$8.95

**RAINBOW MINI-LIGHT Super Bright Flashlight**  
• LED's don't burn out!  
• Battery lasts for years!  
• If you have your keys, you'll have a flashlight.  
• Replaceable battery!  
• Better buy 2, your wife is going to take yours!

Lights up a complete bedroom at night

Red MLR \$9.95 each  
Yellow MLY  
Blue MLB  
White MLW \$12.95 each  
Infrared MLI

Extra batteries \$2.95  
SHOWN ACTUAL SIZE

**LIE DETECTOR**  
This kit can be great fun at parties. When you lie, generally your hands will sweat and the more you sweat the louder the tone. This kit allows you to measure these changes, only a slight amount of change will cause the tone to increase in frequency. Power requirement: 6 to 12v DC. SIZE: 8" x 1.2"

LD-1 KIT \$9.95

**BUSY PHONE LIGHT**  
Add this little kit to any or all of your telephones. When one phone is used a red LED will light on the other extension. This lets everyone know when your computer modem is in use. Power requirement 9v DC. SIZE: 1.1" x 6"

TEL-LITE KIT \$9.95

**DC VOLTAGE MONITOR**  
If battery status is important, you need this kit. This kit uses 7 LEDs to monitor 12v DC in 1v, 1/2v, or 1/4v steps. Monitor 8v or 5v in 1/4v steps. Great for boats, motor homes, model planes or race car ni-cads. All parts and instructions are included. SIZE: 1.3" x 2.7". If you want to switch more power see our Triac (TP-1).

VM-1 KIT \$7.95  
For 110 AC VM110 KIT \$10.95

**WATER ALARM**  
Don't ever get stuck with a flooded basement or over fill your water bucket. When the liquid level reaches the sensor it automatically turns the pump on or off. The Water Alarm supplies you with 100 mA of output that activates a relay (that you supply). This relay can turn on a sump pump, or in applications where you are filling a area with liquid it turns off the pump. Sensor included. Size 1.4" x 2"

WA-2 KIT 17.95

**VOICE ACTIVATED SWITCH**  
This VOX circuit can be used to operate a tape recorder, ham radio, CB radio, or turn on an alarm. The VOX-1 kit has 100MA of output that operates a relay, light, motor, ? What could you do with a sound activated switch? Power requirement 7.5 TO 18v DC. SIZE: 1.5" x 1.3"

If you want to switch more power see our Triac (TP-1) or Relay (RP-1) Power kit.

VOX-1 KIT \$6.95

**PHONE RECORDING SWITCH**  
This phone line powered switch is small enough to be installed anywhere. Every time the phone is picked up the recorder will record both sides of the conversation automatically. Use it in your office to record all phone calls so you don't lose important information. SIZE: 1" x 6"

If you want to switch more power see our Triac (TP-1) or Relay (RP-1) Power kit.

TEL-SW1 KIT \$12.95

**WIRELESS FM MICROPHONE**  
Small but mighty this little jewel will out perform most units many times its price. It really stomps out a signal. The WM-2 kit is a buffered wireless mike that operates from 80MHz to 120MHz FM, the frequency of any broadcast FM radio. Includes a mini-electret mike. 6 to 12v DC. SIZE: 1.25" x 1"

WM-2 KIT \$14.95

**16 TONE DECODER**  
Sweet 16 tone decoder operates great over phone lines, radios or scanners.

• 16 TTL Level Outputs  
• DTMF Decoder Decodes 16 different touch tones using the phone, radios, or scanners.  
• One relay & driver circuit on board.  
• 9v battery powered. Size: 2.34" x 2 1/8"

TT-16 KIT \$34.95

**AUDIO PREAMP**  
Boost your microphones output up to line level!  
Plug your mic into our AP-1 and drive your amp, to full capacity. Connect an AP-1 to a pair of amplified speakers, plug your mic in and you have an instant PA system. Requires 6 to 12v DC. Size: 1.75" x 1"

AP-1 KIT \$9.95

**STROBE LIGHT**  
Do you need an attention getter, warning light, or flashing light for model airplanes? Then this kit is for you. Use it as an emergency light for your auto, radio tower, even use it on your bicycle. Has a variable flash rate. Power requirement 6 or 12v DC. Size: 3.5" x 1.9"

ST-1 KIT \$11.95

**SUPER SNOOPER BIG EAR**  
Listen through walls, hear conversations across the room. Add a parabolic reflector and hear blocks away. The BIG EAR can be hidden about anywhere. Makes an ultra sensitive intercom. Can be used as a 1.5W AMP. We supply a mini-electret mike in the kit. Power requirement 6 to 12v DC. SIZE: 1.25" x 1"

AA-1 BUILT \$29.95 KIT \$10.95

**INDUCTANCE METER**  
This is the kit everyone has been asking for. Turn your digital volt ohm meter into an inductance meter. It will read inductors 3uH to 7MH. Power requirement 9v DC. SIZE: 1.75" x 2.5"

IA-1 CABINET KIT \$14.95  
IA-1 KIT \$8.95

**DIGITAL THERMOMETER**  
The DT-3 kit will turn your digital volt ohm meter into an accurate digital thermometer with .1 degree resolution. Measure temperatures from -40° to 250°F. The remote sensor is .25" sq. and can be mounted many feet from the meter. Power requirement 9V DC. SIZE: 2" x 1.35"

DT-3 KIT \$8.95

**CAPACITANCE METER**  
This kit will turn your digital volt meter into a capacitance meter. Turn that junk box of unmarked capacitors into a fortune of usable parts. Measure capacitors from <math>2.2pF</math> to 2.2uF. Power requirement 9V DC. SIZE: 1.80" x 2"

CA-1 KIT \$12.95

**KEY BOOK \$14.95**  
This Manual contains schematics, parts lists & P.C. board layouts for many of the Rainbow Kits. Use your own parts to construct your kits.

Write in 41 on Reader Service Card.

Nuts & Volts Magazine/January 1999 51

## MILITARY SURPLUS ELECTRONICS

MILLIONS \$\$\$ in "scrap gold" from old computers and electronics junk. Message; 603-645-4776 or [www.tiac.net/users/quiksand/goldtek.htm](http://www.tiac.net/users/quiksand/goldtek.htm)

## AUDIO - VIDEO - LASERS

WANTED: PRO video equipment, VCRs, switchers, cameras, etc. Advanced Media 702-874-1911.

**SYNC-A-LINK UNIVERSAL VIDEO SYNC GENERATOR** restores all horizontal & vertical sync lines, DC level, compensates for inverted video, color phase, from standard or distorted analogue video-type formats. Comes complete with operations manual & 90-day warranty. \$160. 918-479-6451 or write to Sync-A-link Communications, PO Box 4, Locust Grove, OK 74352.

**START YOUR OWN TECHNICAL VENTURE!** Don Lancaster's newly updated **INCREDIBLE SECRET MONEY MACHINE II** tells how. We now have autographed copies of the Guru's underground classic for \$18.50. Synergetics Press, Box 809-K, Thatcher, AZ 85552. 520-428-4073. VISA/MC.



**ANTIQUE VIDEO TRANSFER SERVICE:** transfer of any 2" quadruplex video tapes. Quad TV spots, features, medical, corporate, military, government, and university tape libraries **TRANSFERRED TO VHS.** Affordable. Phone/fax 415-821-7500. If no answer call 415-821-3359 or pager 415-245-8700.

**MOD CHIPS for Sony PlayStation.** Now your backups will work. Only \$9.95 ea. + \$3 shipping. Call 1-888-467-6150, all major credit cards accepted. Computers & components at wholesale prices. [www.cconusa.com](http://www.cconusa.com)

**BROADCAST VIDEO** equipment wanted: all types, new or old. Please call, Jon with info. 1-800-539-2859.


**FREE LASER CATALOG.** Helium-Neon, Argon, ruby, visible laser diode modules, lightshows, holography, laser pointers. Lowest prices. Midwest Laser Products, PO Box 262, Frankfort, IL 60423. 815-464-0085 [www.midwest-laser.com](http://www.midwest-laser.com)

**CREATE 3-D video images with the Visual Eyes Video system.** Phone or fax 918-479-6451 or write to Sync-A-Link, PO Box 4, Locust Grove, OK 74352.

**LASER POINTERS** hottest novelty craze! Bullet style, metal cased, keychain pointers (not the cheap plastic styles). Highest quality, brightest laser for legal US use. Each packed in brilliant display case with batteries. All factory new and sealed with full one year warranty. We wholesale with the lowest prices on any quantity. Gentry Communications 507-332-2788.

**SONY PLAYSTATION MODCHIPS.** Allow you to play CDR backups & imports. \$10 ea. + \$3 shipping. Quantity discounts. 619-590-9320.

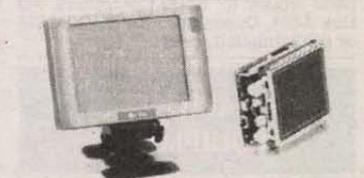**8x8 PORT video/stereo audio switch.** Electronic wideband patch panel eliminates complex wiring of your video and audio components. Easy signal routing via front panel controls using the MMCS-10. Call Communications Systems Labs at 1-800-529-9483 or check our web site at [www.commsyslabs.com](http://www.commsyslabs.com) for this and more.



**TFT COLOR LCD monitor:** 12VDC power, NTSC video input. Display for car, boat, navigation, instrument, security. 4" panel \$149. 5" monitor \$315. 6.4" monitor \$480. TV tuner, AV switches, antenna, 6.4" monitor, remote control, video sources for car CCD camera, tracking, etc. Call 1-800-266-5706 PCT. Website: [mobil-e-tech.com](http://mobil-e-tech.com)

## TELEPHONE/FAX

**TELEPHONE CATALOG** 160 pages including office automation, voice mail, and all phone accessories. Send \$10 to HES Electronics, POB 183, Brick, NJ 08723. Mention this ad and get a 10% off certificate! Visit [www.heselectronics.com](http://www.heselectronics.com)

**NEW: MEMORECS** system, provides most important features your answering machine is missing. Oricom Technologies, 303-449-6428. [www.sni.net/~ori.com](http://www.sni.net/~ori.com)

**WHAT! YOU don't have TELECODE's** new 1998-9 "HACKER CATALOG," yet! 125+ items. Call 520-726-2833. Surf online at <http://www.hackerscatalog.com>

**PHONE SYSTEMS WANTED!!!** We buy AT&T MERLIN, SYSTEM 25/75/85 and other AT&T phone systems. Please call for a quote or fax us your equipment list. **KEYWAYS, INC.**, 937-847-2300 or FAX 937-847-2350.

**Sell Nuts & Volts** in your store and earn \$\$\$! Contact us for details. 909-371-8497 E-Mail [distributors@nutsvolts.com](mailto:distributors@nutsvolts.com)

# Quality Reconditioned TEST EQUIPMENT

Visit us at our website [www.danbar.com](http://www.danbar.com)

**General Radio 1482  
Standard Inductors  
Special \$250.00**

Available in 1482B, 1482D, 1482E, 1482F, 1482L, 1482J, 1482K, 1482L, 1482M, 1482P, 1482Q.

**Bird 4380A-488  
\$300.00**

IEEE-488 Interface.

**Bird 4410A  
\$300.00**

Wattmeter, Frequency range 0.2 to 2300 MHz, 0.002 to 10,000 Watt. Elements are not included.

**Bird 61  
\$175.00**

Wattmeter, .5/ 2.5 Watts. Elements are not included.

**Bird 611  
\$175.00**

Wattmeter, 15/60 Watts. Elements are not included.

**EIP 545  
Special \$750.00**

Microwave Frequency Counter, 10 Hz to 18 GHz frequency range (3 bands), 12 digit LED display, time base: 10 MHz, aging rate <math>3 \times 10^{-7}</math>/month, 50Ω input.

**EIP 545A  
Special \$895.00**

Microwave Frequency Counter, 10 MHz to 18 GHz frequency range (3 bands), 12 digit LED display, time base: 10 MHz, aging rate <math>3 \times 10^{-7}</math>/month, 50Ω input.

**Avcom PSA35A  
Special \$995.00**

Portable Spectrum Analyzer, low bands 10 MHz to 1750 MHz; high bands 3.7 to 4.2 GHz. 60 dB dynamic range.

**Hewlett-Packard 5335A  
Special \$695.00**

200 MHz Universal Counter, built-in automatic risetime, duty cycle & pulse width.

**Hewlett-Packard 3312A  
Special \$575.00**

Function Generator, 0.1 Hz to 13 MHz in 8 decade ranges, AM/FM, sweep, trigger, gate and burst.

**Hewlett-Packard 3325A  
\$1250.00**

Synthesizer/Function Generator, 1 uHz to 21 MHz, 11 digit resolution.

**Hewlett-Packard 3488A  
\$550.00**

Switch Control Unit, up to 50 channels, dc to 300 MHz signal switching, can hold up to 5 modules in the 444XX series.

**Hewlett-Packard 8350B  
Special \$2,500.00**

Sweep Oscillator Mainframe, 10 MHz to 40 GHz (dependent on plug-in used), 10 mW output power to 26.5 GHz.

**Hewlett-Packard 83522A  
Special \$3,500.00**

Sweep Oscillator Plug-In, 0.01 to 2.4 GHz, leveled output >13 dBm. Has opt 004, rear panel RF output.

**Hewlett-Packard 83525A  
Special \$4,500.00**

Sweep Oscillator Plug-In, .01 to 8.4 GHz, +13 dBm output. Opt 002, adds 70 dB step attenuator.

**Hewlett-Packard 83545A  
\$3,900.00**

Sweep Oscillator plug-in 5.9 to 12.4 GHz frequency range, 50 mW max leveled power, complete HP-IB programmability.

**Hewlett-Packard 83592B  
\$10,950.00**

Sweep Oscillator Plug-In, .01 to 20.0 GHz, +13 dBm internally leveled output.

**Hewlett-Packard 83594A  
\$14,700.00**

Sweep Oscillator Plug-In, 2 to 26.5 GHz, +4 dBm internally leveled output. Opt 002, adds 70 dB step attenuator.

**Tektronix 2213A  
Special \$600.00**

60 MHz Oscilloscope, 2mV sensitivity, 5 nS/div sweep speed, advanced trigger system. Includes 2 probes.

**Tektronix 2220  
Special \$895.00**

60 MHz Oscilloscope, digitizing rates 20 MS/s at 5 uS/div and faster to 20 samples/s at 5 s/div, digital storage/non-storage, single timebase, 4 k record length.

**Tektronix 2430A  
Special \$3,750.00**

150 MHz Digital Oscilloscope, 100 MS/s digitizing rate, simultaneous acquisition on 2 channels, envelope mode with 2 ns glitch capture. Has Opt. 05 & 11.

**Tektronix 466  
Special \$575.00**

100 MHz Storage Oscilloscope, dual trace, 5 mV/div, stored writing speed of 3000 div/μs variable persistence. Includes 2 probes.

**Tektronix 465  
Special \$550.00**

100 MHz Oscilloscope, dual trace, 5 mV/div sensitivity, 5 nS/div sweep rate. Includes 2 probes.

**Tektronix 468  
Special \$1,150.00**


Digital/Analog Storage Oscilloscope, 100 MHz nonstorage bw, 10 MHz storage bw, cursors for time/voltage measurements. Includes 2 probes.

**Tektronix 475  
Special \$750.00**

200 MHz Oscilloscope, dual trace, 2 mV/div sensitivity. Includes 2 probes.

**Tektronix 485  
Special \$895.00**

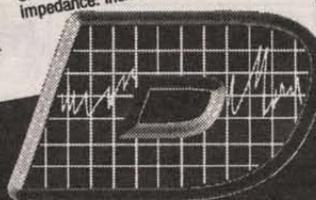350 MHz Oscilloscope, dual trace, 5 mV/div sensitivity, 1 nS/div sweep rate, 3.0 div/ns writing speed, selectable input impedance. Includes 2 probes.



**WANTED  
USED TEST  
EQUIPMENT**

(602) 483-6202  
Fax (602) 483-6403  
14455 North 79th Street, Unit #C • Scottsdale, Arizona 85260

**DANBAR  
SALES COMPANY**

## CABLE TV


**DEALERS:** NEW VM8000 cable converter. Sharp tuner, 800MHz. 125 channels. Call for lot pricing. NTS 1-888-355-6687.

**UNMODIFIED JERROLD 212** converter \$50. 97.5, 106.5, 108.5, AB filters \$12 ea. 100dB deep. Digital 125 ch PRO converter \$150. Call for the best you can buy! Toll free 1-888-561-4796 M-F 10-6pm. <http://bbctech.hypermart.net>



**NOTCH FILTERS** 110, 108.5, 106.5, 97.5 75dB deep notch. \$19.95 ea., 1-5 qty. \$15.95 ea., 6-10 qty. \$11.95 ea., 11-20 qty. \$9.95 ea., 21 or more qty. Call 24 hr. order and information hot line 516-389-3536.

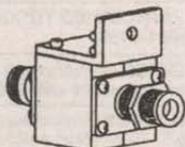**NEW! CABLE** converter electronic service equipment and supplies for most cable converter boxes. Highest service, lowest prices. Call Ken Erry Electronics. 24 hr. order and information hot line 516-389-3536.



**EXPLOSIVE CABLE TV GRAB!** BRINKER ZAPPER/SNOOPER STOPPER combo module all in one! Buy wholesale factory-direct, no middleman. Let others get fined + zapped instead. 100% COMPATIBLE. Your order shipped NATIONWIDE immediately! LIFETIME GUARANTEE! VISA/MC/AMEX/COD/MO/CHECKS. ONLY \$10 (SPECIAL: 3/\$20 plus FREE DESCRAMBLER PLANS!). SUPER ZAPPER MODULES ONLY \$16! (3/\$33) Use SUPER ZAPPERS if you have COX, TCI, WARNER in: CA, TX, FL, NY, PA, MI. DESCRAMBLER PLANS (4=\$5, 20=\$15) 130+ DESCRAMBLER SOURCES (\$5). FREE SHIPPING. OPEN 24 HOURS! 352-429-5496. BRINKER ENGINEERING LABS, USA.

**ADEAL4U WHOLESALES BIG SAVINGS \$\$\$ BEST QUALITY - NO CHEAP CLONES** 888-387-1248 [www.adeal4u.com](http://www.adeal4u.com)

**JERROLD UNMODIFIED CONVERTERS FOR SALE.** CALL FOR BEST PRICES. NO DESCRAMBLER SALES. CALL BRLD ELECTRONICS 1-800-322-6316.

**PICS, GALS READ** if you've lost your masters. Programming service available. Call for info. Network Sales, 616-683-0500.

**125 CHANNEL** Digital Pro converter with audio & video \$82 each. Panasonic TZ-PC175DG2-7 converter with volume control \$135 each. The best converters you can buy! Please call 1-888-561-4796.

**UNMODIFIED CABLE CONVERTERS.** Zenith ST1600, ST1086, ST300, Panasonic 175, 145 vol. & non-vol. Regal RR-92 & RC 83, DP5, DP7, DRZ, 5503 VIP, SA 8580. Guaranteed low prices. Please call for more converters 405-631-1856.

**WANTED PIONEER 6110, 6310 CONVERTERS, RAW, TOP CASH, LOTS 5 OR MORE.** 702-642-0325.

**UNMODIFIED ST 1000 and ST 4000,** \$20 ea. Bill 419-385-3100.

# BIG POWER LOW COST



Dominoes are rugged, miniature encapsulated controllers that combine lots of analog and digital I/O with a fast control-oriented floating-point BASIC to provide a one-stop computation and control solution for cost-sensitive control tasks. Used stand alone or connected via RS-232/RS-485, Dominoes are true plug-and-go control.

### Domino 1 features:

- Full floating-point ROMed BASIC
- 32-KB SRAM and 32-KB EEPROM
- 12 bits of parallel I/O
- 2 PWM outputs
- PC bus
- 2-channel 12-bit ADC
- Serial port: 19.2-kbps RS-232A, RS-422, or RS-485
- +5 V @ 15 mA

### Domino 2 has:

- everything in Domino 1 plus
- 16 more bits of high-current parallel I/O
- Hardware clock/calendar
- Wide-range power operation
- Hardware PWM output

**\$99 to \$139**

Visit our Web site for complete datasheets

[www.micromint.com](http://www.micromint.com)

To Order Call: **1-800-635-3355**

4 Park St., Vernon, CT 06066  
(860) 871-6170



Write in 43 on Reader Service Card.

## World Passing You By?

Are you interested in Microprocessors & Embedded Control Systems? If not you should be! Look around, just about everything these days has an embedded microprocessor in it, TVs, cars, radios, traffic lights & even toys have embedded computers controlling their actions. The Primer Trainer is the tool that can not only teach you how these devices operate but give you the opportunity to program these types of systems yourself. Examples & exercises in the Self Instruction manual take you from writing simple programs to controlling motors. Start out in Machine language, then move on to Assembler, & then continue on with optional C, Basic, or Forth Compilers. So don't be left behind: this is information you need to know!



### Examples Include:

- Measuring Temperature
- Using a PhotoCell to Detect Light Levels
- Making a Waveform Generator
- Constructing a Capacitance Meter
- Motor Speed Control Using Back EMF
- Interfacing and Controlling Stepper Motors
- Scanning Keypads and Writing to LCD/LED Displays
- Bus Interfacing an 8255 PPI
- Using the Primer as an EPROM Programmer
- DTMF Autodialer & Remote Controller (New!)

The PRIMER is only \$119.95 in kit form. The PRIMER Assembled & Tested is \$169.95. This trainer can be used stand alone via the keypad and display or connected to a PC with the optional upgrade (\$49.95). The Upgrade includes: an RS232 serial port & cable, 32K of battery backed RAM, & Assembler/Terminal software. Please add \$5.00 for shipping within the U.S. Picture shown with upgrade option and optional heavy-duty keypad (\$29.95) installed. Satisfaction guaranteed.

**EMAC, inc.**  
11 EMAC WAY, CARBONDALE, IL 62901  
618-529-4525 Fax 457-0110 BBS 529-5708  
World Wide Web: <http://www.emacinc.com>

1985 - 1998  
OVER  
**12**  
YEARS  
OF SERVICE

Write in 44 on Reader Service Card.

**PIONEER 6110, 6310s, READY TO GO, SATISFACTION GUARANTEED, SORRY NO NEVADA SALES, LESS BUSTERS ELECTRONICS, 702-642-0325, WEB: WWW.LESSBUSTERS.COM**

**FREE CABLE DESCRAMBLER PLANS!** For details write: Sierra Publishing, 909 E. Yorba Linda Blvd., Suite H-181, Dept. NVK, Placentia, CA 92870.

**AS-IS** converters Oak Sigma, \$20; Zenith, \$7; genuine unmodified DPV5, \$10. Call John 419-243-7856.

**CBTV REPAIR.** We specialize in all converters, including Zenith. Give us a call: 405-634-1535.

**UNMODIFIED, POWER-UP,** Pioneer BA: 6110, \$75; 5135 \$45; 5125 \$25; Jerrold DP5, channel 2: \$19, DPBB 7312, \$95; S/A 8590-757 (11 button) \$95. Minimum 10-lot. 405-631-5153.

**CABLE PARTS!** Computer parts. Call for great prices or visit us on the Web: [HTTP://WWW.CB-Electronics.com](http://WWW.CB-Electronics.com) or call 1-800-436-8630.

**TOCOM UNMOD.** 5503 cable converters \$6 each. Call 706-398-2100. 10 lot min.

**ONE STOP** shop. We carry a full line of CBTv equipment for all your cable needs. Also a wide variety of converter parts and accessories. Call for free catalog: 405-631-5153, FAX: 405-631-4788.

## FOR THE BEST PRICES ON PROFESSIONAL TOOLS, CALL ELECTRO-TOOL



**platt** - Case - Deluxe Polypropylene. Chemical Resistant. Tools by CooperTools and others. 800T Case, complete with tools ... \$419.95  
800T Case Only ... \$121.80




**platt** - Case - Cordura Exterior. Two exterior pockets & one literature pocket. 660ZT Case, complete with tools ... \$223.00  
660ZT Case Only ... \$59.45  
Optional Sperry meter #DM6510 as shown ... \$65.00



**Weller WCC100** - Electronically controlled station, temperature adjustable from 350°F-850°F, Zero voltage circuit-safe for sensitive components, 40 Watt pencil ... \$97.90

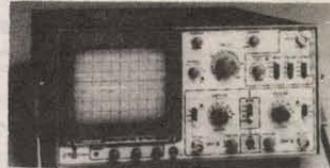**OptiVISOR** - Superior magnification, Optical Glass Prismatic lenses (not plastic). Select any one of (6) magnifications ... \$24.00



**GoldStar** - 20 MHz Dual Trace Oscilloscope OS-9020A-Large 6" rectangular, high sensitivity: 1mV/div, high accuracy: ±3%, stable, low-drift design, 8 divisions of displayed dynamic range and accurate, distortion-free waveform measurements ... \$372.00

## Electro Tool, Inc.

9103 Gillman, Livonia, MI 48150  
Customer Service: (734) 422-1221  
ORDERS ONLY: 1 (800) 772-3455  
FAX: (734) 422-3432



"Tools American Made."

**SA UNMODIFIED** all makes and models. Call for best prices 706-398-2100.

**SONY PLAYSTATION MODCHIPS.** Allow you to play CDR backups & imports. \$10 ea. + \$3 shipping. Quantity discounts. 619-590-9320.

**TOCOM UNMOD.** 5503 cable converters \$6 each. Call 706-398-2100. 10 lot min.


**PANASONIC TZPC175-3DG2:** the original 175 with volume, parental control, and channel 3 output. Ideal for all your projects. \$50 each/10 lot. With remote! All units fully guaranteed, RAN, and repacked. We are the lowest priced wholesaler of Panasonic equipment. Gentry Communications. 507-332-2788.

# LOWEST COST LCD'S ON EARTH


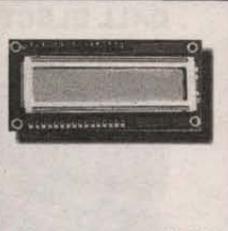
## VIDEO LCD

4 Inch Video NTSC \$150  
Sharp P/N 4LU4E  
Composite NTSC & RGB Input  
12:00 OR 6:00 Viewing Angle  
Integrated Backlight & Inverter  
Extended Temp: -10 to +60 C  
Brightness: 260 nits  
Power Consumption: 4.3 Watts  
Contrast: 50 to 1



## CHARACTER LCD

OPTREX DMF-5005N-EW  
240 x 64 Graphic EL Backlit STN \$30  
OPTREX DMF-5005N  
240 x 64 Graphic Reflective STN \$30  
SANYO DM2023-7G1  
2 x 20 Character Reflective STN \$8  
SHARP LM20A21  
2 x 20 Character Reflective STN \$8  
VIKAY 2035TNLD NOTW-D  
2 X 16 Character LED Backlit STN \$8




## LCD MONITOR

10.4" DSTN or 12.1" TFT  
Analog SVGA Input  
Autosync  
Auto Sizing  
Automatic Expansion of VGA  
images to SVGA (On 12.1")  
Very Aggressive Pricing  
Starting under \$500!


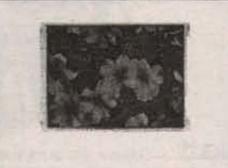
## TOUCH MONITOR


EarthVue 10.4  
10.4" VGA TFT  
Analog VGA Input  
105 Nit Brightness  
RS-232 Touch Screen Option  
Only 9.9"W x 7.7"H x 1.5"D  
Ideal For Factory Automation  
Fully Articulating Ball Mount  
Only \$1095 With Touch



## LCD DISPLAYS

6.3" Mono STN	\$60
9.4" Mono Reflective	\$60
8.4" TFT	\$250
9.4" DSTN	\$150
10.4" TFT	\$350
10.4" DSTN	\$240

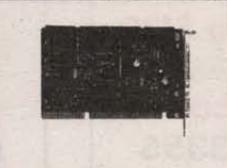NoteBook Screens  
340 Models in Stock  
Obsolete Screens Stocked  
Hard To Find LCD? Call!



## CONTROLLERS

ISA  
PCI  
PC/104  
NTSC  
Analog VGA  
Complete LCD Kits with LCD,  
Controller & Cable Starting  
under \$200



# EARTH

Computer Technologies


"The World Leader In LCD Recycling"

Ph: (949) 361-2333 Fax: (949) 361-2121

<http://www.flat-panel.com>

Write in 71 on Reader Service Card.

## The Pocket Programmer

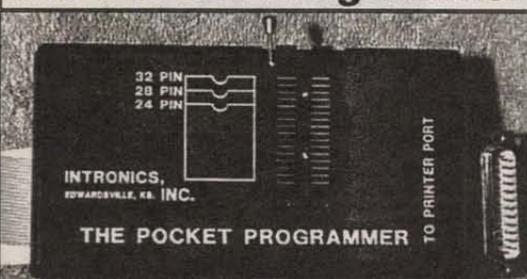

The portable programmer that uses the printer port of your PC instead of an internal card. Easy to use software that programs E(E)prom, Flash & Dallas Ram. 27(C)/28(C)/28F/ 29F/29CXXXX & 25XX series from 16K to 8 Megabit with a 32 pin socket. Adapters available for Pic, MCU's 874X, 875X, 40-Pin X 16 & Serial Eprom's, PLCC, 5-Gang, 82/74 Prom's and Eprom Emulator to 32K X 8.  
Only \$129.95

Same Name, Address & Phone Number for 16 Years....  
Now isn't that Amazing ?

### Intronics, Inc.

Box 13723 / 612 Newton St.  
Edwardsville, KS 66113 Add \$5.00 COD  
Tel. (913) 422-2094 Add \$4.00 Shipping  
Fax (913) 441-1623 Visa / Master Charge / Amex

54 January 1999/Nuts & Volts Magazine

**SCHEMATIC DIAGRAMS** is what we have. 200+ cable items. 100+ satellite items. We tear down, reverse engineer, and draw schematics for items we are sent by companies or individuals who can't get prints from manufacturers. Latest draws: MM2000, HT2000, cable boxes, Hird-A2 satellite receiver. Send \$5 and request television catalog, or check our web site for our other 20 catalogs. **Bomarc Services**, Box 1113, Casper, WY 82602. 307-234-3488 [ROLLO@TRIB.COM](mailto:ROLLO@TRIB.COM) **BOMARC.ORG**

**ATTENTION: YOU'VE** tried the rest, now go with the best. **UNICORN ELECTRONICS** where our valued customers **ALWAYS** come first. **CABLE CONVERTERS AND ACCESSORIES. WE** beat all competitors prices **GUARANTEED**. All **UNITS** in **STOCK** for **IMMEDIATE SHIPMENT. FREE** batteries and coax cable. **FREE** bullet protection with every unit purchased. **FREE** shipping with a \$500 purchase or more. **NO** COD charges. **ALL** products come with a 1 year warranty and a 30 day money back guarantee. Please give us a call **TOLL FREE 1-888-738-8181** 9am to 6:30pm EST. **VISA, M/CARD, DISCOVER, COD. UNICORN** Electronics does not advocate unauthorized use or theft of cable services.

**MOD CHIPS** for Sony PlayStation. Your backups will work. Only \$9.95 ea. + \$3 shipping. Call 1-888-467-6150, all major credit cards accepted. Computers & components at wholesale prices. [www.cconusa.com](http://www.cconusa.com)

**LOW COST** plain converters: Pioneer BC 4135, Hamlin CR-6000, DRZ-3, they're all 450MHz, 70 channel comes with new remote, 1 year warranty for only \$15 each. Panasonic: TZPC-170, 450MHz with volume, \$25 each; TV-86, \$25. Minimum 10-lot. Call 405-634-1535.

**GENUINE UNMODIFIED JERROLD DPBB 7312. 1-800-804-8655. E-MAIL: CLEWIS7298@AOL.COM**

**CABLE PARTS & EVERYTHING.** Parts & accessories. Best prices & quantity discount. **WE DON'T SELL BOXES. 1-800-MODULE-0.**

**TOCOM UNMOD.** 5503 cable converters \$6 each. Call 706-398-2100. 10 lot min.

**FOR ALL YOUR CABLE NEEDS:** Call Images Electronics, for the best quality parts at the lowest prices. **909-982-2482** or visit our web site at <http://members.aol.com/ImagesCo>

**ZENITH ST1600** unmodified \$60 each. Call 706-657-4445. 10 lot min.

**PANASONIC TZPC145-3:** the original 145 with parental control and channel 3 output. \$45 each/10 lot. With remote! All units fully guaranteed, RAN, and repacked. We are the lowest wholesaler of Panasonic equipment. Gentry Communications. 507-332-2788.

**CONVERTERS WHOLESALE** Regal CR83 \$35 each/10 lot. Panasonic 145-3 \$45 each/10 lot. Panasonic 175-3 \$50 each/10 lot. We also stock TV86, Timeless, RA550E, and Trivisions. Large selection of replacement remotes and batteries. Lowest prices on any quantity. Wholesale/distributors welcome. Gentry Communications. 507-332-27

**WANTED: GENUINE RAW UNMODIFIED CABLE TV CONVERTERS. TOP CASH PAID. CALL 708-715-6118.**

**BATTERIES WHOLESALE.** Heavy duty AA and AAA batteries. These are ideal for remotes, toys, and small electronics. 24 batteries per box. Cells start at 12¢ each! Fully guaranteed in factory packed boxes. Wholesalers and distributors call for case quantities. Gentry Communications. 507-332-2788.

**GENUINE UNMODIFIED TOCOMS VIP. CALL 717-401-3438.**

**SA UNMODIFIED** all makes and models. Call for best prices **706-398-2100.**

**FILTERS IN STOCK,** limited supply. 110, 108.5, 106.5, 97.5 MHz notch. Round and square types. \$14 to \$20 each. Highest quality. **407-676-2530.** Mention ad number F100.

**BOARD R US,** for all your cable needs or computer software, programming service available. 4 MHz resonators 3 pins as low as 34¢. For info call 909-948-3736 or visit us at our web site <http://members.aol.com/BoardRUs>

**GENUINE UNMODIFIED JERROLD DPBB7312 FOR SALE 10 LOT MIN. CALL 708-715-6118.**

**UNMODIFIED CABLE CONVERTERS: JERROLD, SCIENTIFIC ATLANTA, PIONEER, ZENITH, TOCOM. MIN 10 LOT. CALL 708-715-6118**

**CABLE TV.** Panasonic TZPC 175DG2, brand new, \$80 w/volume, 1 year warranty, minimum 10 pcs. any qty., plus all major brands available. **Lowest price new/field pulls. E-Mail: OCALA@BELLSOUTH.NET phone: 1-800-929-1549 fax: 305-220-9396**

**UNBELIEVABLE PRICES.** We carry a full line of cable tools and equipment for all your cable needs. Also a wide variety of electronic parts & accessories, tools, diagrams, converters, step-by-step instructions, no raw parts. **Full technical support.** 12pm-7:30pm EST. **1-800-562-8442.**

**THE BEST** is back to stay. Master code recovery. 16c5x, 16c62x, PALS, GALS, other microcontrollers, etc. Check out our web page at [www.acdinc.com](http://www.acdinc.com) for details or call 703-764-5361 or write Advanced Circuit Designs, Inc., 5765-F Burke Centre Parkway, Suite 317, Burke, VA 22015.

**TOCOM UNMOD.** 5503 cable converters \$6 each. Call 706-398-2100. 10 lot min.

**PLAYSTATION MOD** chips. Works with all models up to 750x. Color instructions. Five wire hook up, comes with wire. \$5 each, plus shipping charges. 10% discount for 10 or more. Call 703-764-5118.

**ZENITH ST1000** unmodified \$16 each. Call 706-398-2100. 10 lot min.

**WANTED: TV** digital cable converters. Fax 954-961-7577.

# PRINTED CIRCUIT BOARDS

*Since 1969*

## Prototype to Production

**Quick • Quality • Service • Price**

- Single Sided
- Double Sided
- Multi-Layer

- Surface Mount
- Punch Press Capability
- LPI

**QUICK TURN AROUND  
COMPLETE IN-HOUSE CAPABILITY**

### CIRCUIT ETCHING TECHNICS

*Since 1969*

700 Lee Street Phone: 847-228-1722  
Elk Grove Village Fax: 847-228-1816  
Illinois 60007 Modern: 847-228-6549  
Toll Free: 888-657-3827

*Please call Jim, Barb, or Babu for more information and/or quote.*

Write in 72 on Reader Service Card.

**SA UNMODIFIED** all makes and models. Call for best prices 706-398-2100.

**CABLE STOP**, one stop for all your cable needs. Quality parts at a low price. 1-800-562-8442 12pm-7:30pm EST

**ZENITH ST1000** unmodified \$16 each. Call 706-398-2100. 10 lot min.

## COMPONENTS

**DON LANCASTER'S ACTIVE FILTER COOKBOOK** is back in print. Autographed copies of the seventeenth(!) classic printing \$28.50. **SYNERGETICS PRESS**, Box 809-N, Thatcher, AZ 85552. 520-428-4073. Visa/MC.

**MILLIONS \$\$\$** in "scrap gold" from old computers and electronics junk. Message: 603-645-4776 or www.tiac.net/users/quiksand/goldtek.htm

**PHOTOMULTIPLIER TUBES**, radiosondes, electro-luminescent panels, electronic parts, test equipment. [www.lonemtn.com](http://www.lonemtn.com)

**MILITARY TRANSISTORS & DIODES & INTEGRATED CIRCUITS WANTED. ELECTRONIC MATERIAL INDUSTRIES** 818-769-1002, FAX 818-769-1084.



**FACTORY SALE!** CNL100, CNP101: 1/3" CCD, 430 line horiz., 12V/100mA, lens and pin hole types, lens 3.6mm/F2.0, 1.27" (W) x 1.27" (L) x 1" (H). \$43 @ 5 pcs., \$38 @ 10 pcs. Distributors welcome. Matco, Inc., 1-800-440-0299 Fax: 630-350-9546. E-Mail: sales@mat-co.com Web site www.mat-co.com

**OLD ICs & TRANSISTORS WANTED: HIGHEST PRICES PAID** please FAX your list with part number, quantity & condition of any semiconductors to Rick @ ESI, 5363 Broadway Ave., Cleveland, OH 44127. 216-441-8500 FAX 216-441-8503. Since 1946! [www.electronic surplus.com](http://www.electronic surplus.com)




**AMAZING! 35¢ ALL TOGGLE SWITCHES.** Brand new. Rated 6A/125V. Hardware included. 1/4" panel hole. SPDT or DPDT on-on, or on-off-on. Minimum 100pcs/package. Add \$6 freight. Gateway Products Corporation, PO Box 936397, Margate, FL 33093, 954-974-6864, Fax: 954-974-6818, VISA/MC, no COD.

**WANT TO Buy:** ICs, military & aircraft relays, diodes, transistors, Cannon, TRW, Amp, Burndy, Deutsch, Bendix connectors, electronic test equipment & most components. Hoff Electronic Ent., 818-718-1165, FAX 818-341-5506.

**RF TRANSISTORS, TUBES**, 2SC2879, SD1446, MRF455, MRF454, 3SC1969, 2SC2166, 2SB754, TA7222AP, 2SC1419, 2SC1947, 2SB688, 2SD880, MRF422, MRF448, MRF247, MRF317, SAV7, SAV17, 3-500ZG 4CX250B, 572B, 3CX3000A7, 4CX400A silver mica caps, resistors, electrolytics, etc. Westgate 1-800-213-4563.

## MICROCONTROLLERS

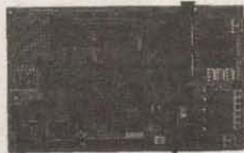

**PICBOT AUTOMATION** controller. Single PCB with extensive I/O and sensory for home & office automation, robot-

ics, and light industrial applications. Includes 20MHz 8-bit RISC MCU, up to 512K SRAM & FLASH, dual H-bridge motor drivers, dual serial COM ports, stereo digital audio, 14 Darlington drivers, 6 high-current drivers, 8 LED drivers, IR remote sensor, and user prototype area with 10 PIC I/O (A/D) lines and SMT pads. Includes an object-oriented stack-based interpreter that runs applications from any text file on a PC. Runs off any DC power source from +6V to +24V, and connects directly to PC COM port for easy programming and configuration. **Single PCB solution for mobile robot projects.** Prices from \$199 quantity 1. Web Technology, 408-690-9660. Fax 408-279-3211 [www.webotechnology.com](http://www.webotechnology.com)

**PICWISER LOW cost development system.** Rapid prototyping system contains PIC16F84, integrated programmer and solderless breadboard. Write software on PC, program PIC16F84 using parallel port, and test circuits fast. Send \$59 plus \$6 shipping to: Emicros, 25759 Ridgewood, Farmington, MI 48336. 248-477-6639, [www.emicros.com](http://www.emicros.com)

**ATMEL 90S1200/89C2051 PROTOTYPE BOARD.** High quality 2x3 board with 1x2 prototype area. Supports RS-232 interface, regulated power supply, connectors. Includes schematics for board and interactive programmer. Send check or money order for \$15.50 to: 2051BC, 1826 Lambeth Way, Carmichael, CA 95608. 916-487-2513. [WWW.2051BC.COM](http://WWW.2051BC.COM)



## EDLIE THE KIT KING

Presents New-Do-

It Yourself Kits from Datak



Each Kit comes complete with an educational explanation of the circuit.

Build these useful kits and have! Fun Too! Each kit comes with its own PC Board

### Voice Changer (80-1051)

Your voice can be changed to add a vibrato, like those used to disguise secret witnesses. Or you may change your voice upward or downward: women sound like men and vice versa. Includes a very ROBOT voice as well. A microphone and speaker are included on the PC board; all that you need to add is a 9V transistor battery. This is a very novel and entertaining circuit. **\$12.95**

### 4 Train Sound Effects (80-9101)

This Cob project will produce 4 very realistic user selectable sound effects that are ideal for model railroad. Throw any of switches to produce a train whistle blowing 3 times, a train chugging along, a level crossing bell & the "clickety clack" of a train crossing a bridge. Kit includes all parts including speaker Easy to assemble. operates on 2.4 to 6VDC. **\$7.95**

### Light Alarm (80-0801)

Detects very small amounts of light and sounds a piezo alarm. Put in your cash box or cupboard. Uses Darlington photo transistor MEL2 & 14011 I.C. A very educational kit. **\$8.50**

### Universal Timer (80-1061)

Another novel circuit, that might be useful for special theatrical effects, or, if you are simply a practical joker! The circuit can produce sounds such as the tick-tock of a grand father's clock, a heart monitor (as ins the hospital) water on a tin roof, a motor boat, cricket, etc. Requires a 9-Volt battery. Includes its own speaker. **\$8.95**

### Stereo Preamplifier (80-1041)

Amplify any tiny audio signals about 50 times & deliver them to a power amplifier cleanly and undistorted. An AGC control eliminates pops or distortion. This circuit will be useful in boosting the output from tape heads, microphones or a magnetic cartridge etc. For input to an audio amplifier. Requires a 12VDC power supply at about 100mA peak **\$9.50**

### 2 Stage FM Transmitter

This is an extremely sensitive and powerful FM bug; transmits to upper part of FM band. A two stage, three transistors FM transmitter. It operates on a 9V battery. The most sensitive & powerful that you can legally buy. The circuit employs an Electret microphone for added sensitivity. Unit can run on 6 volts, greatest output at 12V use. Use 9 volts and the short antenna wire included staying legal in U.S. **(80-3201) \$9.50**

### Sound Activated FM Transmitter (80-2801)

A sound activated switch and hybrid sound turns on the transmitter. Sound switch activation level is user settable. Two-state transmitter has excellent range. When no sounds present the transmitter is powered down to save power **\$10.95**

### Infrared Toggle Switch

**(80-5801)** Control just about any device using the remote control from just about any TV set. The circuit switches an on-board SPDT relay: Turn it on with the remote, and turn it off with another signal. The relay contacts are rated 1A at 125 V.A.C. The circuit operates any DC supply from 8 to 15V; use as an old calculator supply etc. This circuit can have some very practical Applications, such as turning on a light by an invalid. Your imagination is the limit. **\$15.95**

### Sound Effects Generator

**(80-103)** Another novel circuit, that might be useful for special theatrical effects, or, if you are simply a practical joker. The circuit can produce sounds such as the tick-tock of a grand father's clock, a heart monitor (as in the hospital) water on a tin roof, a motor boat, cricket, etc. Requires a 9-Volt battery. Includes its own speaker **\$7.95**

### Suction Cup Phone Pick-Up with Amplifier (80-5501)

No electrical connection to the telephone is Required. Attach a suction cup to the handset & turn on the amplifier. This project permits group listening to phone calls, or you can monitor any other oscillating electrical field Dual IC's provide a good quality amplifier. The circuit runs on 6VDC. Everything is included except batteries. **\$10.95**

### Variable Power Supply (80-6801)

This is a basic adjustable voltage power supply with a range of about 1.5VDC to 35VDC set by a potentiometer. It is capable of 2 Amps if you add a simple heat sink. Circuit includes short circuit protection. **\$13.95**

### Photo Sensor with Control Relay (80-1031)

The most popular usage for this kit is to make your own night light. But you could switch just about any appliance either on or off with either darkness or daylight. Light sensitivity is adjustable over quite a range. The relay can handle up to 10 Amp A.C.. You need to add a 9-Volt transistor battery or a 9V. 25mA supply **\$8.95**

*Edlie Has been in business for 52 years. Visit our Store*

Call or Write for a

**Free**

76 page Catalog  
800-516-645-4722  
Outside the US Please send  
\$3.00

Mail your orders to  
**Edlie Electronics Inc**

2700 Hempstead Tpke.  
Levittown, N.Y. 11756

Order Toll Free

800-516-645-4722  
IN NYS 516-735-3330

Checks, or Money orders are Accepted by mail No C.O.D. Shipping & handling charge \$5 For the continental United States For all Others Including Canada, Hawaii, Alaska, & P.R. must pay full shipping charges

We accept MC, Visa, & AE



To order by Fax Call 516-731-5125  
For Info Call 516-735-3330

## ANTIQUE ELECTRONICS

**ANTIQUE RADIO CLASSIFIED.** Free sample copy! Antique radio's largest-circulation monthly magazine. Old radios, TVs, ham equip., 40s & 50s radios, telegraph, books & more. Ads & articles. Free 20-word ad monthly. Subscribe today. Six-month trial: \$19.95. Yearly rates: \$39.49 (\$57.95 by 1st Class). Foreign: write. ARC, PO Box 802-G23A, Carlisle, MA 01741. Phone: 978-371-0512; Fax: 978-371-7129; Web: www.antique-radio.com

**TELEGRAPHY INSTRUMENTS, KEYS SOUNDBERS, RELAYS, METERS, VIBROPLEX'S, PRACTICE SETS, INSTRUCTOGRAPHS, CALL BOXES, ETC. GOODMAN 217-345-6771.**

**CRYSTAL SETS.** Parts, plans, books, kits. Largest source in the world. Catalog \$2. MIDCO, PO Box 222288, Hollywood, FL 33022.

**WESTERN ELECTRIC WANTED:** 1927-1960s. Amplifiers, speakers, tubes, etc. Free offer. 1-800-251-5454.

**WANTED: FOR** historical museum, pre-1980 microcomputers, magazines, and sales literature. Floyd, VA 24091-0341 (540-763-3311/540-382-2935).

**WESTERN ELECTRIC WANTED:** 1920's-1960's. Amplifiers, mixers, pre-amps, speakers, tubes, etc. FREE OFFER 1-800-251-5454.

**MILITARY TRANSISTORS & DIODES & INTEGRATED CIRCUITS WANTED. ELECTRONIC MATERIAL INDUSTRIES 818-769-1002, FAX 818-769-1084.**

**2 NOS Sony 1/2" Reel to Reel VTR's.** Portable model 3450, camera model 3400, power supply, Sony 19" monitor. Also model AV3600. All cords still in plastic. Includes AV3600 for parts. Asking \$1,000 for all, or will separate. 919-363-9510.

**RADIO TUBES** and phono. needles. 870-347-2281.

## AVIATION ELECTRONICS

**BUY, SELL,** trade, avionics equipment, Collins, King, Sperry; test equipment, IFR, Litton LTN series INUs. 941-625-3222 P. 941-625-0494 F. E-Mail: avionics@afcon.net

**SYNCHRO RESOLVER** test sets, system analyzers, test equipment. www.lonemtn.com

**MILITARY TRANSISTORS & DIODES & INTEGRATED CIRCUITS WANTED. ELECTRONIC MATERIAL INDUSTRIES 818-769-1002, FAX 818-769-1084.**

## PUBLICATIONS

**START YOUR OWN TECHNICAL VENTURE!** Don Lancaster's newly updated **INCREDIBLE SECRET MONEY MACHINE II** tells how. We now have autographed copies of the Guru's underground classic for \$18.50. Synergetics Press, Box 809-K, Thatcher, AZ 85552. 520-428-4073. VISA/MC.

**THE CASE AGAINST PATENTS.** Don Lancaster's tested and proven alternatives that work in the real world. \$28.50. Synergetics Press, 3860 West First Street, Box 809, Thatcher, AZ 85552. 520-428-4073. synergetics@tinaja.com VISA/MC.

**MILITARY COMPONENTS** wanted. Capacitors, resistors, diodes, transistors, semiconductors, ICs. Electronic Material Industries, 818-769-1002, FAX: 818-769-1084.

**COLLECT COMPUTERS?** Sure! Start now before it's too late. Buy a Guide to Collecting Computers and Computer Collections. Send \$22 (includes S&H & taxes) to Unusual Systems, 220 Samuel, Kitchener, ON N2H1R6. 519-744-2900. kstumpf@unusual.on.ca

**WHAT! YOU** don't have TELECODE's NEW 1998-9 "HACKER CATALOG," yet! 125+ items. Call 520-726-2833. Surf online at http://www.hackerscatalog.com

**HOW WILL HIGH DEFINITION TV** implementation plans affect you? Send \$5 for detailed newsletter/report. Communications Systems Labs, Dept. HDTV, 95-132 Lokih Street, Suite A, Millilani, HI 96789.

**NEW SURVIVAL COMMUNICATIONS BOOK.** How to build complete home communications systems. Covers all needs: shortwave radio, amateur radio, citizens band, scanners, federal, weather, alternate news, satellite radio, equipment sources. How to build and use alternate emergency power sources, solar, generators, backup batteries. 200 pages. \$24 Fast delivery Priority Mail. MC or Visa. Call Universal Electronics 1-800-241-8171.

## ROBOTICS

**ROBOT BOOKS.COM** visit our web site for reviews of robotics books, plus robot kits, toys, movies, and magazines! www.robotbooks.com

**H-BRIDGE MOTOR** controllers, 12VDC, 35A average, 50A peak PWM out. Forward, reverse, ramp-up and ramp-down on acceleration/deceleration. Current foldback when hot, reverse polarity protected, conformal coated, regenerative braking, compact, approx. 3.75"x5.5". \$25 & S&H. 717-735-5053. http://members.tripod.com/~divelec

# ALL ELECTRONICS CORPORATION

QUALITY PARTS

FAST SHIPPING

DISCOUNT PRICING

CALL, WRITE, FAX or E-MAIL For A Free 96 Page CATALOG. Outside the U.S.A. send \$3.00 postage.

### Interact ProPad GAME CONTROLLER


Interact Game Products # SV-230 PC ProPad works with hundreds of PC games. Very similar to Super Nintendo controllers, it has a four-way direction button on the left, A and B buttons on the right and speed controls and auto-fire controls in the middle. 15 pin D-sub connector plugs into the sound card on most Windows based computers.



**\$3.00** each CAT # SV-230  
2 for \$5.00
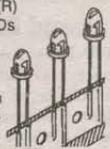
### 3000 MCD ULTRA-BRIGHT RED LED

Everlight # 383URC-2/TR1-C(R) Red, "Ultra-bright" T 1 3/4 LEDs now at our lowest price ever. Due to a special purchase of "tape-and-reel" parts we are able to offer these LEDs at an incredibly low price when purchased on the reel. These are 5 mm diameter water-clear LEDs that light bright red at 20 ma.



CAT # LED-50  
**2 for \$1.00**  
100 for \$35.00  
1000 for \$250.00 (25¢ each)


### S-VHS Tape (Used)

Super VHS tape users! Save a bundle on name-brand S-VHS, T-120 tapes. These tapes were used for a brief period, then bulk erased. The record-protect tabs have been broken out, so you will have to cover the notch with a piece of tape, but they work great and cost a fraction of the "new" price.

CAT # S-VHS **\$3.00** each  
10 for \$28.00 • 100 for \$250.00
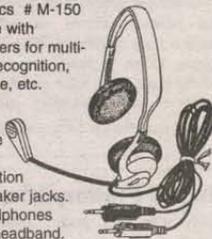
### STEREO HEADSET with Electret Mike

Andrea Electronics # M-150 Designed for use with personal computers for multimedia, speech recognition, internet telephone, etc. Stereo headset and boom mike has two separate 3.5mm stereo plugs for connection to mike and speaker jacks. Lightweight headphones with adjustable headband. 6' cord.



CAT # PHN-15 **\$8.75** each

### 10K THERMISTOR

Semitec # 103AT-2 10K ohm (± 1 %) @ 25 deg. C. Rated 10 mW. Time constant: 15 sec. 2 mm x 3mm. 2.5mm lead spacing. CAT # THR-20

**\$1.00** each  
10 for \$8.50  
200 for \$130.00

### 250 uh PANEL METER

Good-looking 1.65" x 1.68" panel meter. Matte-black frame with a 1.43" x 0.84" viewing window. Scale calibrated from 1 to 10, divided into green (1-4), yellow (4-6) and red (6-10) areas. Logo, "The Seeker" is written under the scale.



**\$1.50** each CAT # MET-51  
10 for \$12.50

### Encased Piezoelectric Element

0.82" DIAMETER X 0.15" AVX/Kyocera # PCRT21BGX Black plastic front, vented metal back. Solder loop terminals. Louder than non encased piezo elements. Requires external signal to produce sound. CAT # PE-38



**3 for \$1.00**  
100 for \$25.00  
1000 for \$125.00

### BIG Flashing LED

Big, bright red flashing LED. 10 mm diameter. Red diffused lens. Great for attention getting displays. Operates on 3-12 Vdc. Flash rate approx. 2 times per second.



CAT # LED-60  
**2 for \$1.50**  
10 for \$6.50  
100 for \$50.00

### UV Blacklight

New black-light lamps designed by Avon Cosmetics to highlight dry skin. They have a built-in timer that shuts-off the lamp after approximately one minute. Ideal for lighting fluorescence in black-light posters, gemstones, hand stamps and US currency. 5" lamp, F4T5BLB, is housed in a lightweight plastic case. 7" x 3.25" x 2.3" high. Powered by a 12 Vdc, 500 ma wall transformer (included). Individually boxed.



CAT # UVL-1 **\$10.00** each

F4T5-BLB Replacement lamp for above fixture. CAT # BLB-5 \$3.00 each

### 470 Mfd 450 Vdc

Nichicon #LGQ2W471MHSC 1.375" dia x 2" high. 0.4" lead spacing. CAT # EC-4745



**\$3.00** each  
10 for \$22.50

### "Hi-8" Video Cassette

SONY Hi-8 Top quality, metal particle 120 minute video cassettes. Used for a short time, then bulk-erased. Each cassette has its own plastic storage box.



CAT # VCU-8 **\$3.00** each  
10 for \$28.00 • 100 for \$250.00

ORDER TOLL FREE

**1-800-826-5432**


MAIL ORDERS TO:  
ALL ELECTRONICS CORP.  
P.O. BOX 567  
VAN NUYS, CA 91408-0567

FAX (818) 781-2653 • INFO (818) 904-0524  
INTERNET <http://www.allcorp.com/>  
E-MAIL [allcorp@allcorp.com](mailto:allcorp@allcorp.com)



NO MINIMUM ORDER • All Orders Can Be Charged to Visa, Mastercard, American Express or Discover • Checks and Money Orders Accepted by Mail • Orders Delivered in the State of California must include California State Sales Tax • NO C.O.D. • Shipping and Handling \$5.00 for the 48 Continental United States • ALL OTHERS including Alaska, Hawaii, P.R. and Canada Must Pay Full Shipping • Quantities Limited • Prices Subject to change without notice.

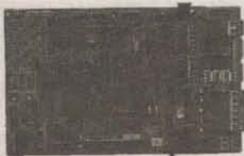MANUFACTURERS - We Purchase EXCESS INVENTORIES... Call, Write, E-MAIL or Fax YOUR LIST.



**PICBOT AUTOMATION** controller. Single PCB with extensive I/O and sensory for home & office automation, robotics, and light industrial applications. Includes 20MHz 8-bit RISC MCU, up to 512K SRAM & FLASH, dual H-bridge motor drivers, dual serial COM ports, stereo digital audio, 14 Darlington drivers, 8 high-current drivers, 8 LED drivers, IR remote sensor, and user prototype area with 10 PIC I/O (A/D) lines and SMT pads. Includes an object-oriented stack-based interpreter that runs applications from any text file on a PC. Runs off any DC power source from +6V to +24V, and connects directly to PC COM port for easy programming and configuration. **Single PCB solution for mobile robot projects.** Prices from \$199 quantity 1. Webo Technology, 408-690-9660. Fax 408-279-3211 www.webo.com

**CNC SYSTEMS!** Write: motivity, Attn. Pam, PO Box 428, Rocklin, CA 95677. Call: 916-349-8757. Info/pictures at [www.motivityusa.com](http://www.motivityusa.com) A great place to buy CNC.

**www.futurerobots.com ROBOTS** are soon coming to our homes. Most of the technology is now here and their need is also here. Come see the real future of home robots.

## PLANS - KITS - SCHEMATICS

**HOBBY CATALOG:** Broadcasting and microbroadcasting transmitters, amplifiers, antennas. **Start your own radio station books.** Audio, TV, ham, CB, surveillance, science projects, and more. **PAN-COM International,** Box 130-V, Paradise, CA 95967. [www.panaxis.com](http://www.panaxis.com)



**CIRCUIT BOARDS.** Totally new! Low cost, precision-milled PC boards from your Gerber/NC Drill files. Single and double sided. Full details at <http://www.pcbmilling.com> E-Mail: [feedback@pcbmill.com](mailto:feedback@pcbmill.com) FAX: 703-818-0071.

**HEATHKIT COMPANY** is selling photocopies of most Heathkit manuals. Only authorized source for copyright manuals. Phone: 616-925-5899, 8-4 ET.



**BROADCAST FARTHER!** 75-110MHz amplifier connects to stereo transmitters. Produces 2-15 watts. Requires 50-150mW drive. Complete plans with part source and antenna information only \$14 + \$2 S&H. **Progressive Concepts,** PO Box 586, Streamwood, IL 60107. 630-736-9822.

**BUILD THE MENDOCINO MOTOR.** This fascinating device is a solar powered, magnetically levitated motor. It will delight and amaze you and your friends. The 27 page plans book includes a list of parts suppliers. The motor uses readily available parts. Plans are \$15 plus \$2.50 S&H. Write to: St. Elmo's Fire, PO Box 141, Stow, MA 01775. E-Mail: [tcv@genrad.com](mailto:tcv@genrad.com)

**ELECTRONIC KITS,** projects and supplies for prototyping, designing or hobby. Call 1-888-GO-4-KITS for catalogs or send \$3 to Quality Kits, 49 McMichael St., Kingston, ON, K7M 1M8. <http://www.qkits.com>

**AWESOME KITS:** voice changers, levitators, lasers, solar robots, and more! Catalog \$1. **LNS Technologies,** PO Box 67243, Scotts Valley, CA 95067. [www.ccnnet.com/~lnstech](http://www.ccnnet.com/~lnstech)

**200+ ELECTRONICS PROJECTS.** Build for pleasure or make 100% (or more) profits reselling printed plans. \$1 (refundable) for catalog & dealer info. **MATCO-A5,** PO Box 509, ROSEVILLE, MI 48066-0509.



**TERRIFIC TIMEPIECES!** LED binary clock. LED digital clocks, other kits! Free catalog! **WPC,** 805-339-0702. [www.west.net/~wpc](http://www.west.net/~wpc)

**TEST EQUIPMENT** kits. If you liked Heathkit, you will love Technology Systems, 4 Prospect Pl., Torrington, CT 06790.

**MOD CHIPS for Sony PlayStation.** Now your backups will work. Only \$9.95 ea. + \$3 shipping. Call 1-888-467-6150, all major credit cards accepted. Computers & components at wholesale prices. [www.cconusa.com](http://www.cconusa.com)

**MILITARY COMPONENTS** wanted. Capacitors, resistors, diodes, transistors, semiconductors, ICs. **Electronic Material Industries,** 818-769-1002, FAX: 818-769-1084.


**KITS, PROTOBOARDS,** telephone electronics, pocket testbench, RS-232 instrumentation PIC monitor chips. **Oricom Technologies,** 303-449-6428, [www.sni.net/~oricom](http://www.sni.net/~oricom).



We call them the 'Cubes'... Perfect video transmission from a transmitter you can hide under a quarter and only as thick as a stack of four pennies—that's a nickel in the picture! Transmits color or B&W with fantastic quality - almost like a direct wired connection to any TV tuned to cable channel 59. Crystal controlled for no frequency drift with performance that equals law enforcement models that cost hundreds more! Basic 20 mW model transmits up to 300' while the high power 100 mW unit goes up to 1/4 mile. Audio units include sound using a sensitive built-in mike that will hear a whisper 15 feet away! Units run on 9 volts and hook-up to most any CCD camera. Any of our cameras have been tested to mate perfectly with our Cubes and work great. Fully assembled - just hook-up power and you're on the air!

- C-2000, Basic Video Transmitter Cube.....\$89.95
- C-3000, Basic Video and Audio Transmitter Cube.....\$149.95
- C-2001, High Power Video Transmitter Cube.....\$179.95
- C-3001, High Power Video and Audio Transmitter Cube.....\$229.95

## Super Pro FM Stereo Radio Transmitter

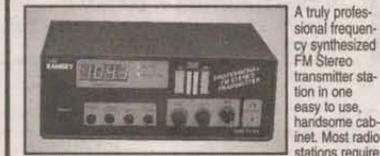

A truly professional frequency synthesized FM Stereo transmitter station in one easy to use, handsome cabinet. Most radio stations require a whole equipment rack to hold all the features we've packed into the FM-100. Set frequency easily with the Up/Down frequency buttons and the big LED digital display. Plus there's input low pass filtering that gives great sound no matter what the source (no more squalls or swishing sounds from cheap CD player inputs!) Peak limiters for maximum 'bunch' in your audio - without over modulation. LED bargraph meters for easy setting of audio levels and a built-in mixer with mike and line level inputs. Churches, drive-ins, schools and colleges find the FM-100 to be the answer to their transmitting needs, you will too. No one offers all these features at this price! Kit includes cabinet, whip antenna and 120 VAC supply. We also offer a high power export version of the FM-100 that's fully assembled with one watt of RF power, for miles of program coverage. The export version can only be shipped outside the USA, or within the US if accompanied by a signed statement that the unit will be exported.

- FM-100, Professional FM Stereo Transmitter Kit.....\$299.95
- FM-100WT, Fully Wired High Power FM Transmitter.....\$429.95



Ramsey AM radio transmitters operate in the standard AM broadcast band and are easily set to any clear channel in your area. Our AM-25 'pro' version, fully synthesized transmitter features easy frequency setting, DIP switches for stable, no-drift frequency control, while being jumper settable for higher power output where regulations allow. The entry-level AM-1 uses a tunable transmit oscillator and runs the maximum 100 milliwatts of power. No FCC license is required, expected range is up to 1/4 mile depending upon antenna and conditions. Transmitters accept standard line-level inputs from tape decks, CD players or mike mixers, and run on 12 volts DC. The Pro AM-25 comes complete with AC power adapter, matching case set and bottom loaded wire antenna. Our entry-level AM-1 has an available matching case and knob set for a finished, professional look.

- AM-25, Professional AM Transmitter Kit.....\$129.95
- AM-1, Entry level AM Radio Transmitter Kit.....\$29.95
- CA1, Matching Case Set for AM-1.....\$14.95

## CCD Video Cameras



If you're looking for a good quality CCD board camera, stop right here! Our cameras use top quality Japanese Class X CCD arrays with over 440 line resolution, not the off-spec arrays that are found on many other cameras. You see, the Japanese suppliers grade the CCDs at manufacture and some manufacturers end up with the off-grade chips due to either cost constraints or lack of buying 'clout'. Also, a new strain of CMOS single chip cameras are entering the market, those units have about 1/2 the resolution and draw over twice the current that these cameras do - don't be fooled! Our cameras have nice clean fields and excellent light sensitivity, you'll really see the difference, and if you want to see in the dark, the black & white models are super IR (Infra-Red) sensitive. Our IR-1 Illuminator kit is invisible to the human eye, but lights the scene like a flashlight at night! Color camera has Auto White Balance, Auto Gain, Back Light Compensation and DSP! Available with Wide-angle (80°) or super slim Pin-hole style lens. They run on 9 VDC and produce standard 1 volt p-p video. Add one of our transmitter units for wireless transmission to any TV set, or add our IB-1 Interface board for audio sound pick-up and super easy direct wire hook-up connection to any Video monitor, VCR or TV with video/audio input jacks. Cameras fully assembled, including pre-wired connector.

- CCDWA-2, B&W CCD Camera, wide-angle lens.....\$99.95
- CCDPH-2, B&W CCD Camera, slim fit pin-hole lens.....\$99.95
- CCDPH-2, Color CCD Camera, wide-angle lens.....\$149.95
- IR-1, IR Illuminator Kit for B&W cameras.....\$24.95
- IB-1, Interface Board Kit.....\$24.95

## FM Stereo Radio Transmitters



Microprocessor controlled for easy frequency programming using DIP switches, no drift, your signal is rock solid all the time - just like the commercial stations. Audio quality is excellent, connect to the line output of any CD player, tape deck or mike mixer and you're on-the-air. Foreign buyers will appreciate the high power output capability of the FM-25; many Caribbean folks use a single FM-25 to cover the whole island! New, improved, clean and hum-free runs on either 12 VDC or 120 VAC. Kit comes complete with case set, whip antenna, 120 VAC power adapter - easy one evening assembly.

- FM-25, Synthesized FM Stereo Transmitter Kit.....\$129.95

A lower cost alternative to our high performance transmitters. Offers great value, tunable over the 88-108 MHz FM broadcast band, plenty of power and our manual goes into great detail outlining aspects of antennas, transmitting range and the FCC rules and regulations. Connects to any cassette deck, CD player or mixer and you're on-the-air, you'll be amazed at the exceptional audio quality! Runs on internal 9V battery or external power from 5 to 15 VDC. Add our matching case and whip antenna set for a nice finished look.

- FM-10A, Tunable FM Stereo Transmitter Kit.....\$34.95
- CFM, Matching Case and Antenna Set.....\$14.95
- AC12-5, 12 Volt DC Wall Plug Adapter.....\$9.95

## RF Power Booster

Add some serious muscle to your signal, boost power up to 1 watt over a frequency range of 100 KHz to over 1000 MHz! Use as a lab amp for signal generators, plus many foreign users employ the LPA-1 to boost the power of their FM Stereo transmitters, providing radio service through an entire town. Runs on 12 VDC. For a neat, professionally finished look, add the optional matching case set.

- LPA-1, Power Booster Amplifier Kit.....\$39.95
- CLPA, Matching Case Set for LPA-1 Kit.....\$14.95
- LPA-1WT, Fully Wired LPA-1 with Case.....\$99.95

## Treasure Finder Kit



Search for buried treasure at the beach, backyard or park. This professional quality kit can detect metal at a depth of up to 6 inches. Easy to use, just listen for the change in tone as you 'sweep' the unit across the surface - the larger the tone change - the larger the object. Has built-in speaker or earphone connection, runs on standard 9 volt battery. Complete kit includes handsome case, rugged PVC handle assembly that 'breaks down' for easy transportation and shielded Faraday search coil. Easy one evening assembly. This nifty kit will literally pay for itself! That guy in the picture looks like he found something - what do you think it is - gold, silver, Rogaine, Viagra? You'll have fun with this kit. **TF-1, Treasure Finder Kit.....\$39.95**

## Binocular Special

We came across these nice binoculars in an importers close-out deal. Not some cheap in-line lens jobs, these beauties have roof prisms, a super nice rubber armored housing over light weight aluminum. 10 x 25 power with fully coated optics. Includes lens cleaner cloth, neck lanyard and nice carry case. For extra demanding use in bright sun, choose the EX model with ruby coated Objective lens. First quality at a close-out price! We've seen the exact same units with the 'Bushnell' name on them being sold for \$30 more!

- BNO-1, Binoculars and case.....\$24.95
- BNO-1EX, Ruby Coated Lens Binoculars and case.....\$29.95

## Speech Descrambler

Decode all that gibberish! This is the popular descrambler / scrambler that you've read about in all the Scanner and Electronic magazines. Speech inversion technology is used, which is compatible with most cordless phones and many police department systems, hook it up to your scanner speaker terminals and you're in business. Easily configured for any use: mike, line level and speaker output/inputs are provided. Also communicate in total privacy over telephone or radio, full duplex operation - scramble and unscramble at the same time. Easy to build, all complex circuitry contained in new custom ASIC chip for clear, clean audio. Runs on 9 to 15VDC. Our matching case set adds a professional look to your kit.

- SS-70A, Speech Descrambler/Scrambler Kit.....\$39.95
- CSS, Custom Matching Case and Knob Set.....\$14.95
- SS-70AWT, Fully Wired SS-70A with Case.....\$79.95
- AC12-5, 12 Volt DC Wall Plug Adapter.....\$9.95

## Call for our Free Catalog!

See our complete catalog and order on-line with our secure server at [www.ramseyelectronics.com](http://www.ramseyelectronics.com)

**RAMSEY ELECTRONICS, INC.**  
793 Canning Parkway Victor, NY 14564

**Order Toll-free: 800-446-2295**  
Sorry, no tech info, order status at this number

**Technical Info, Order Status**  
**Call Factory direct: 716-924-4560**  
Fax: 716-924-4555

ORDERING INFO: Satisfaction Guaranteed. Examine for 10 days, if not pleased, return in original form for refund. Add \$6.95 for shipping, handling and insurance. Orders under \$20, add \$3.00. NY residents add 7% sales tax. Sorry, no CODs. Foreign orders, add 20% for surface mail or use credit card and specify shipping method.

# WE BUY & SELL!

# C and H

## SALES COMPANY

2176 E. Colorado Blvd.  
Pasadena, CA 91107

**50 YEARS IN BUSINESS**

Take advantage of our special purchase on TEST EQUIPMENT

### HIGH PRECISION DIGITAL MULTIMETER

FLUKE, Model 8810A. LED readout. 5-1/2 digit auto-ranging multimeter. Has ohms converter and true rms options. Accuracy AC volts 0.1% to 0.5%, AC rms 0.2% to 0.4%, DC volts 0.01%, ohms 0.02% to 0.2%. Max input voltage 1000 VDC or peak AC. Input impedance to 1 to 1000 meg ohms depending on range. Power input voltage 115 VAC 50/60 Hz. Has built-in carrying handle that can be used as a tilting base. Dimensions: 9-1/4" wide x 14-1/2" deep (including carrying handle) x 3-1/4" high.



Stock #TE9805 **\$295.00**

### 3-1/2 DIGIT DIGITAL MULTIMETER

FLUKE, Model 8000A. LED readout. Classic digital multimeter. Ideal companion to our Stock #TE9800 counter. Measures AC/DC volts/milliamps plus ohms. Input range 0-200 mV to 1200 volts, 0-200 uA to 2000 mA, 0 to 2000 K ohms. Portable unit with carrying handle which also can be used as a tilt stand. Input impedance 10 meg ohms. Max. input voltage 1200 VDC or rms. Accuracy DC volts 0.1% of input +1 digit. AC volts 0.5% of input +2 digits 45 Hz to 10 KHz. Input power 115 VAC 50 to 400 Hz 5 watts. Dimen.: 8-1/2" wide x 12" deep (including carrying handle) x 2-1/2" high.



Stock #TE9801 **\$75.00**

### MILLIOHMETER

HEWLETT PACKARD, Model 4328A. Designed to measure very low resistances. Measurement range 1m ohm to 100 ohms. Resolution 20 u ohms. Analog meter readout. Ideal for measuring contact resistance of switches or relays. This unit is also useful for measuring the resistivity of semiconductor devices. (Requires special 4 terminal probes which are not supplied, but probably are available from Hewlett Packard.) Power input: 115-230 VAC 48-66 Hz, 5 VA max. Dimensions: 5-1/8" wide x 11-1/2" deep x 6-1/2" high.



Stock #TE9812 **\$200.00**

### 200,000 COUNT DIGITAL MULTIMETER, FLUKE,

Model 8800A. LED readout. 6-digit, autoranging multimeter. Basic accuracy  $\pm .005\%$ . 15 ranges DC volts:  $\pm 200$  mV to  $\pm 1200$  in 5 ranges accuracy  $\pm .008\%$  or better. AC volts: 2 VAC to 1200 VAC in 4 ranges. Accuracy  $\pm 1\%$  or better depending on frequency and range. Resistance 200 ohm to 20 meg ohms in 6 ranges. Accuracy  $\pm .02$  or better. Input impedance: 1000 meg ohms or more on DC ranges, 2 meg ohms on AC ranges. Has complete overload protection and isolated inputs. Power input 110/230 VAC 50/60 Hz 8 watts. Built-in carrying handle that also acts as a tilt-up base. Dimensions: 3-1/2" high x 9" wide x 12-1/2" deep.



Stock #TE9815 **\$100.00**

### 3600 RPM DC MOTOR WITH OPTICAL ENCODER PACIFIC SCIENTIFIC, #4VM82-

004-4. 30 volts nom. Input voltage. Permanent magnet, reversible servo motor. Has Hewlett Packard optical encoder. Ball bearings. No load speed at 30 VDC input is 4600 rpm. No load current 0.75 amp at 60 oz-in load rpm is 3600, current is approx. 6.6 amps. Torque constant is 9.1 oz-in per amp. Rotor inertia 0.0007 oz-in-sec<sup>2</sup>. Terminal resistance 0.89 ohm. Optical encoder is similar to "HEDS 6000" series. Encoder has 1024 counts per revolution, two channel quadrature output. Outputs are TTL compatible. Encoder requires 5 VDC input at less than 50 mA input current. Dual shafts: front shaft is 3/8" dia. x 3/4" long. This shaft is tapped on the end 8X32 tpi. Rear shaft is 1/4" dia. x 7/16" long. This shaft has dual flats that measure approx 3/16" across. Motor has four 8X32 tpi tapped mounting holes on front. A 3-3/16" dia. centering pilot is also provided on the front face. Dimensions: 4" dia. x 5-1/2" long (excluding shafts.)



Stock #DCME9850 **\$79.50**

Call us first if you have surplus inventories of electronic, optical, or mechanical items for disposal

Master Charge  Visa  American Express  Discover

**TOLL FREE: 1-800-325-9465**

Write in 45 on Reader Service Card.

Subscribe to Nuts & Volts and be automatically entered in our monthly prize drawing!!



## P.S. Technology

Tel: (800) 326-8103 Fax: (800) 878-7083



- ◆ IC's & Semiconductors
- ◆ Telephone & Cellular Accessories
- ◆ Amplifiers & Audio Equipment
- ◆ 35mm Cameras
- ◆ Universal Remote Controls
- ◆ Batteries (all brands)


- ◆ Computer Products
- ◆ Recordable CD's & Tapes (top brands)
- ◆ Indoor TV Antennas
- ◆ Security Systems
- ◆ CB Radios
- ◆ Fuses & Switches







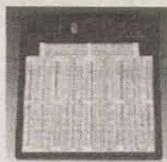**DAZZLING HOLIDAY LIGHT DISPLAY.** Build a spectacular light show for the holidays driven to the tempo of your favorite music. Plans for a state-of-the-art color organ \$15. Call Communications Systems Labs at 1-800-529-9483 or check our web site at [www.commsyslabs.com](http://www.commsyslabs.com) for this and more.



**SOLDERLESS BREADBOARD SB-147:** 3260 tie points, 4 binding posts. **\$29.95 plus \$2.60** (2% of subtotal plus \$2) UPS ground delivery. Call 972-242-8087 for 10+ prices. Mail check to: CTI, 1301 West Beltline #105, Carrollton, TX 75006.

**WIRELESS DOORBELL!** Includes battery-operated transmitter and receiver. 200 FT ranges. Plans for interfacing external hardware. \$26.95 + \$3 S&H. Pine Valley Technologies, Inc. W4117 Pine Valley Rd., Belleville, WI 53508. 608-424-3836.

**NEW: SOLAR** electric helium helicopter airship. Plans for 200 lb. 1 pilot version, \$100. Plans for radio-controlled model, \$50. Rose Aircraft, POB 7589, Chula Vista, CA 91912.

## MANUALS - SCHEMATICS WANTED

**MILITARY COMPONENTS** wanted. Capacitors, resistors, diodes, transistors, semiconductors, ICs. Electronic Material Industries, 818-769-1002, FAX: 818-769-1084.

**CASH FOR** your test equipment manuals in good condition for most Tektronix, HP, Fluke, and other test equipment. E-Mail your list and best price to: [manu@lonemtn.com](mailto:manu@lonemtn.com)

**CONSTRUCTION MANUAL 1975** DeVry scope. Delahoyde, Box 33063, Phoenix, AZ 85067-3063.

## MISCELLANEOUS ELECTRONICS FOR SALE

**MILITARY TRANSISTORS & DIODES & INTEGRATED CIRCUITS WANTED.** ELECTRONIC MATERIAL INDUSTRIES 818-769-1002, FAX 818-769-1084.



**SOLAR-POWERED FAN HAT.** Baseball type hat with solar powered fan. Great for sports fans, golfers, etc. Available in red or blue. \$19 plus \$2.00 shipping. CA residents add 7.75% sales tax. Visa/MC/Disc/Amex OK. H.T. Orr Computer Supplies, 249 Juanita Way, Placentia, CA 92670. 714-528-9822, 1-800-377-2023, FAX 714-993-6216.

**HIGH QUALITY TOOLS AND STAINLESS STEEL HARDWARE.** European and American screwdrivers, nut-drivers, pliers, hex- keys, balldrivers, and more! Wiha, Bondhus, and Knipex. Stainless cap screws, machine screws, nuts, washers, U-bolts, and eyes. Free catalog. Robert Mink Import-Export, Box 6437V, Fair Haven, NJ 07704. Telephone or fax 732-758-8388. E-Mail: [w2tv@csi.com](mailto:w2tv@csi.com)

**CALL FOR a free electronics catalog** or visit our web site at [www.bgmicro.com/](http://www.bgmicro.com/) B.G. Micro, PO Box 280298, Dallas, TX 75228. Order line 1-800-276-2206.



**ANAHEIM WIRE PRODUCTS. DISTRIBUTOR OF ELECTRICAL WIRE AND CABLE** since 1973. Items available from our stock: Hook up wire, Automotive primary wire, GXL, SXL, Plenum cable, Teflon wire, Multi-conductor cable, Irradiated PVC, SO-CORD, Mil-Spec wire, Building wire, Welding cable, Battery cable, Telephone wire, Shrink tubing, Cable ties, Connectors cut & strip to spec. If interested, please call 1-800-626-7540, FAX: 714-771-5043. Visa/MC/Amex. SEE US ON THE INTERNET: <http://www.anaheimwire.com> OR E-Mail: [info@anaheimwire.com](mailto:info@anaheimwire.com)

**HIGHEND SURPLUS 203-744-4101. OK INDUSTRIES DEMO BLOWOUT.** If it is not listed just give us a call, chances are we have it! **SOLDER STATIONS:** total rework, forced convection, hot air. MTR5000 (retail \$4,595) sell \$2,350; MTR4000 (retail \$3,995) sell \$1,750; MTR3000 (retail \$2,495) sell \$1,250; BTR2000 (retail \$1,595) sell \$775; FCR2000 (retail \$1,850) sell \$950; BTR1000 (retail \$825) sell \$400; SMT1160 (retail \$1,000) sell \$450; SA2000 (retail \$395) sell \$185; SA1000 (retail \$295) sell \$150; SA500 (retail \$225) sell \$75. **PUR-AIR:** Fume extractors. EP101 (retail \$1,695) sell \$475; EP051 (retail \$595) sell \$225. **JEM:** Batch ovens JEM310 (retail \$7,995) sell \$3,600; JEM210 (retail \$4,995) sell \$2,200. **PICK & PLACE:** Chip placers, vacuum pencils, fluid dispensers. SMT8001 (retail \$4,000) sell \$1,750; SMT880 (retail \$2,200) sell \$950; FD1000 (retail \$395) sell \$175; VP100 (retail \$395) sell \$175. **BOARD ETCHER:** SSP-75A (retail \$995) sell \$400. **ALWAYS BUYING: VIDEO, RADIO, PHONE SYSTEMS, COMPUTERS, STEREO, AND BROADCAST EQUIPMENT.**

# RF Data Modules



## AM TRANSMITTER

- Small size: 17.78 x 11.43mm
- CMOS/TTL input
- No adjustable components
- Low Current, 4mA typical
- 418MHz or 433.92MHz OOK
- Simple to integrate - simply add antenna, data and power
- Range up to 250ft.
- Wide supply range, 2-14Vdc
- SAW controlled - stability
- Also available in DIL package

AM-RT5 ..... \$12.10

## AM RECEIVER

- Compact size: 38.1 x 13.7mm
- On-board data recovery, CMOS
- Low current, 2.4mA typical
- 2kHz data rate, CMOS/TTL output
- 5Vdc operation
- On 418MHz or 433.92MHz (4xx)
- No adjustable components
- Patented Laser Trimmed component
- High stability
- Sensitivity: -105dBm
- Available also in 0.8mA version

AM-HRR3-4xx ..... \$10.95

## FM TRANSCIEVER

- Only 23 x 33 x 11mm
- Up to 40k bps data rate
- 19200 baud with ASCII
- Up to 500ft. range
- 5v operation
- 0.25mW into 50
- 418 or 433MHz FM
- Fast 1ms enable
- Direct interface to 5V CMOS
- Auto TX/RX changeover

BIM-4xx-F ..... \$87.36

## RS232 TRANSCIEVER MODULES



- 4,800 to 38,400 bps half duplex
- 3-wire RS232 interface
- $\mu$  Controller with user EEPROM
- RS232 interface protected to  $\pm 15kV$
- Data packetizing performed by user
- Auto TX/RX changeover
- 418 MHz and 433MHz versions
- Range up to 500ft. (0.25mW ver.)
- 0.25mW & 10mW versions
- Reset switch and status LED's
- 7.5-15V dc via DB9 connector, 20mA

BIM-4xx-RS232 .... \$139.30



Transceiver.....  
Transmitter.....  
Receiver.....

- Up to 19,200 bps half duplex
  - 3 wire RS232 interface
  - Range up to 500ft
  - Transparent data packetizing
  - Supports 8 or 9 bit protocols
  - Self test function
  - Reset Switch & Status LED's
  - 1/4 wave wire antenna on board
  - Available in a Simplex Tx/Rx pair. (RTcomTX & RTcomRx)
  - 7.5V-15Vdc operation
- RTcom-4xx..... \$247.90  
RTcomTx-4xx..... \$ 87.15  
RTcomRx-4xx..... \$105.52



**ABACOM**  
TECHNOLOGIES



Tel: (416)236-3858  
Fax: (416)236-8866  
www.abacom-tech.com  
abacomtech@compuserve.com


<http://www.pccables.com> PC CABLES and PARTS. 100s of hard-to-find new cables and parts, Free technical information, low prices, fast online ordering & browsing.

**L BAND** quadrifilar T/R antenna, 55 dB LNA, 20 watt HPA, works great for remote GPS. Info at [afstar.com](http://afstar.com).

**FREE FLYER** on cable TV, phones, credit cards info, schematics, project boards, other misc. items. Bill 1-800-879-9657.

**NUCLEAR ELECTRONICS** (NIM, CAMAC), PMTs, optics, high vacuum, and high voltage components and equipment. Guaranteed quality at reasonable cost. OE Technologies, Box 703, La Madera, NM 87539. Ph: 505-583-2482, Fax: 505-583-9190, E-Mail: [oetech@newmexico.com](mailto:oetech@newmexico.com) <http://www.oetech.com>

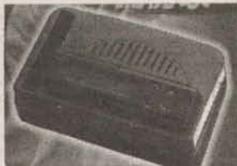**NEW, USED,** and "as is" Radio Shack items. Software, printers, computers, books, parts for R/C cars, etc. Free list. B and B Enterprises, 208 S. Pulaski St., Baltimore, MD 21223. 410-566-5388.



**Z64 GAME** recorder: self-contained computer with 32meg RAM, ZIP. Plug into N64 station. Unlimited game storage, saving \$375. N64 is a Nintendo trademark. 1-800-266-5706 PCT. Website: [mobil-e-tech.com](http://mobil-e-tech.com)

**TOROIDAL ISOLATION TRANSFORMER**, 120V TO 120V @ 450 watts with mounting bracket & hardware. \$30 each, 2 for \$50 or 10 for \$200, includes S&H. List price over \$100, 70 pcs. available. Call GS&E, 716-338-7001. VISA & MC NO COD.

**WANTED TO buy:** Heathkit ID-5001 weather station. Will consider non-working units. 847-683-1032 74742.1570@compuserve.com

**CNC MILLING MACHINE** as-is for parts or rebuild. 1994 Precision Automation PA1000. Accepts DXF files: MasterCAM v5.5 for Windows w/postprocessor. Remote PC console. Anaheim Automation drivers, stepper motors. 5'x10'x7" bed w/heavy duty aluminum frame, vacuum table, \$2,000 OBO. Consultant available for repair and training. Call Showman Fabrications 718-935-9899 or [showfab@AOL.com](http://showfab@AOL.com)

## MISCELLANEOUS ELECTRONICS WANTED

**MILITARY TRANSISTORS & DIODES & INTEGRATED CIRCUITS WANTED. ELECTRONIC MATERIAL INDUSTRIES 818-769-1002, FAX 818-769-1084.**

**TESTERS WANTED:** Immediate offers made for Ultrasonic, Magnetic Particle, Eddy Current, X-Ray and Borescopes, 24hrs. Leave detailed message with make/model. 1-800-530-3371.

**WANTED: ELECTRON** tubes, ICs, semi-conductors. Summit, PO Box 1850, Linden, NJ 07036. Call 1-800-526-4052.

**WANTED: TUBE** HiFi/commercial amps, preamps, corner/horn speakers. Altec, Marantz, McIntosh, Western Electric, etc. 405-737-3312 fax 405-737-3355.

**OLD ICs & TRANSISTORS WANTED: HIGHEST PRICES PAID** please FAX your list with part number, quantity & condition of any semiconductors to Rick @ ESI, 5363 Broadway Ave., Cleveland, OH 44127. 216-441-8500 FAX 216-441-8503. Since 1946! [www.electronic surplus.com](http://www.electronic surplus.com)

# SURPLUS TEST EQUIPMENT

## HEWLETT PACKARD

11729B, Carrier Noise Test Set.....	\$3500
11975A, Amplifier, 2-8GHz.....	\$2000
214B, Pulse Generator, 10Hz-10MHz.....	\$1000
3310A, Function Generator.....	\$250
3312A, Function Generator, 1Hz-13MHz.....	\$700
3325A, Synthesizer/Function Generator.....	\$1000
3325A/01/02, Synthesizer/Function Generator.....	\$1500
3335A, Frequency Synthesizer, 200Hz-81MHz w/Opt. 01.....	\$5500
334A, Distortion Analyzer.....	\$250
339A, Distortion Analyzer.....	\$1000
3456A, Digital Multimeter, 6.5 Digits.....	\$800
3478A, Digital Multimeter.....	\$700
3488A, Switch Control.....	\$600
3551A, Transmission Test Set.....	\$600
3562A, Dynamic Signal Analyzer.....	\$6000
3575A, Phase Gain Meter 1Hz-13MHz.....	\$1000
3577A, Network Analyzer w/35677A Test Set.....	\$10,500
3580A, Spectrum Analyzer, 5Hz-50kHz, Opt. 2 & 3.....	\$1000
3581C, Selective Voltmeter.....	\$800
3585A, Spectrum Analyzer, 20Hz-40.1MHz.....	\$5500
3586B, Selective Level Meter.....	\$750
3589C, Selective Level Meter.....	\$700
4192A, LF Impedance Analyzer w/16097A Kit.....	\$11,000
4193A, Vector Impedance Meter.....	\$6500
4342A, Q-Meter.....	\$1800
435B, Power Meter.....	\$500
436A, Power Meter w/Opt. 022.....	\$1000
44472A, Dual 4-Channel VHF Switch Module (new).....	\$275
44478A, 1.3GHz, 50 Ohm Multiplexer Module (new).....	\$350
4815A, RF Vector Meter.....	\$1200
4935A, Transmission Impairment Test Set w/Opt. 001.....	\$1500
5314A/01/02, Universal Counter.....	\$225
5316B, Universal Counter.....	\$1000
5328B, Universal Counter.....	\$1000
5335A, Frequency Counter, Opt. 10/20.....	\$850
5340A, Frequency Counter, 10Hz-18GHz.....	\$800
5340A, Frequency Counter w/Opt. 01/02/011.....	\$1000
5342A, Microwave Frequency Counter, 10Hz-18GHz.....	\$900
5350B, 20GHz Frequency Counter.....	\$3000
5355A, Frequency Converter.....	\$1000
5386A, Frequency Counter, 10Hz-3GHz.....	\$2000
54100A, Digitizing Oscilloscope.....	\$2500
54100D, 1GHz Digital Oscilloscope.....	\$2700
54110D, 1GHz Color Digitizing Oscilloscope.....	\$2500
54120A, Digitizing Oscilloscope Mainframe.....	\$5750
54121A, Four Channel Test Set.....	\$6500
54201D, Digitizing Oscilloscope.....	\$2650
6011A, Autorange Power Supply, 20V/120A, 1000 Watt.....	\$1200
8011A, Pulse Generator.....	\$400
8011A, Pulse Generator w/Opt. 001.....	\$500
8012B, Pulse Generator.....	\$750
8013B, Pulse Generator.....	\$750
8082A, Pulse Generator, 1KHz-250MHz.....	\$1350
8112A, 50MHz Pulse Generator.....	\$4000
8116A, 50MHz Pulse/Function Generator, Opt. 001.....	\$4000
8160A, Programmable Pulse Generator, 50MHz.....	\$2000
8165A/002, Programmable Signal Source w/AM.....	\$2200
8347A, RF Amplifier, 100KHz-3GHz.....	\$3000
8350A, Sweep Oscillator Mainframe.....	\$1500
8350B, Sweep Oscillator Mainframe.....	\$2000
83522A, Sweeper Plug-in, -01-2.4GHz, w/Opt. 02.....	\$4500
83540A, RF Plug-in, 2.0-8.4GHz.....	\$2000
83540A/002, RF Plug-in, 2-8.4GHz.....	\$2500
83545A, Oscillator Plug-in, 5.9-12.4GHz.....	\$1750
8411A/018, Frequency Converter, 11 to 18GHz.....	\$500
8494H, Programmable Attenuator (unused).....	\$800
8495H, Programmable Attenuator (unused).....	\$600
8501A, Storage Normalizer.....	\$1000
8505A, Network Analyzer w/8501A & 8503A.....	\$4000
8511A, Harmonic Frequency Counter.....	\$6000
8554B, RF Spectrum Analyzer Plug-in, 500KHz-1250MHz.....	\$800
8559A, Spectrum Analyzer Plug-in, 01-21GHz.....	\$2650
8564A/B, Spectrum Analyzer, 100Hz-22GHz.....	\$2200
8569B, Spectrum Analyzer, 10MHz-22GHz.....	\$7000
8640A, Signal Generator, 0.5-512MHz.....	\$700
8640B, Signal Generator, Opt. 002, 5-1024MHz.....	\$2100
8640B, Signal Generator, Opt. 1, 2.....	\$2200
8654A, Signal Generator, 10-520MHz.....	\$450
8656A, Signal Generator, 100KHz-990MHz.....	\$1700
8660D, Synthesized Signal Generator.....	\$7000
8672A, Synth. Signal Gen., 2.0-18.0GHz.....	\$6000
8748A, S-Parameter Test Set w/Opt. 026.....	\$1350
8754A, Network Analyzer w/8748A Test Set.....	\$2000
8756A, Scalar Network Analyzer.....	\$1500
8757A, Scalar Network Analyzer, 10MHz-60GHz.....	\$4000
8901B, Modulation Analyzer.....	\$4000
8904A, Multifunction Synthesizer w/Opt. 002.....	\$2500
8970A, Noise Figure Meter.....	\$4500

## TEKTRONIX

1502, TDR Cable Tester w/Opt. 04 Recorder.....	\$1700
1503, TDR Cable Tester w/Opt. 04 Recorder.....	\$1550
2215, 60MHz Oscilloscope.....	\$900
2236, 100MHz Oscilloscope w/Counter/Timer/DMM.....	\$1000
2246, 100MHz Oscilloscope.....	\$1600
2247A, 100MHz Oscilloscope w/Counter/Timer/Voltmeter.....	\$2500
2337, 100MHz Oscilloscope w/DMM.....	\$1650
2430A, 150MHz Digital Oscilloscope.....	\$2850
2432A, 300MHz Digital Storage Oscilloscope.....	\$3000
2445, Four Channel 150MHz Oscilloscope.....	\$1500
2445A, 150MHz Four Trace Oscilloscope.....	\$1850
2465, Four Channel 300MHz Oscilloscope.....	\$2500
2465B, Four Channel 400MHz Oscilloscope.....	\$4500
2754P, 10KHz-21GHz Spectrum Analyzer.....	\$9000
465B, 100MHz Oscilloscope.....	\$450
466, 100MHz Storage Oscilloscope w/DM44.....	\$800
475, 200MHz Oscilloscope.....	\$650
475A, 250MHz Oscilloscope.....	\$800
485, Oscilloscope, 350MHz.....	\$900
576, Curve Tracer.....	\$2750
577/02, Curve Tracer, Non-storage w/177 Fixture.....	\$1500
7020, Programmable Digitizer.....	\$400
7L5/L3, Spectrum Analyzer, 20Hz-5MHz, w/Opt. 025 Tracking Generator.....	\$1850
7L12, Spectrum Analyzer, 100KHz-1.8GHz.....	\$1500
7L13, Spectrum Analyzer, 1KHz-1.8GHz.....	\$1800
7L18, Spectrum Analyzer Plug-in, 1.5-18GHz, Capable of 60GHz with Mixers.....	\$2500
7512, TDR/Sampler.....	\$450
AFG5101, Arbitrary Function Generator.....	\$1500
CG5001, Programmable Calibration Generator.....	\$4000

VISIT OUR WEBPAGE AT  
[WWW.RSSURPLUS.COM](http://WWW.RSSURPLUS.COM)

PG506, Calibration Generator Plug-in.....	\$600
R2246, 4 Channel Oscilloscope, 150MHz.....	\$1500
SG5010, Programmable Oscillator.....	\$3000
SG504, Leveled Sinewave Generator.....	\$1800
TM5003, Three Slot Power Mainframe.....	\$450
TM5006, Six Slot Power Mainframe.....	\$550
TR503, Tracking Generator for 492/4/5/6.....	\$850

## MISCELLANEOUS

Acme Elect. PS2L1000, Electronic Load.....	\$850
California Inst. 4500L/M3, AC Power Source.....	\$4000
California Inst. 4503L, AC Power Source.....	\$4000
Eaton 2052B, Amplifier, 100-512MHz.....	\$800
EIP 545A, Microwave Frequency Counter.....	\$800
EIP 548A, Frequency Counter, 10Hz-26.5GHz.....	\$2000
EIP 548B, Frequency Counter, 10Hz-26.5GHz.....	\$3250
EIP 578, Source Locking Frequency Counter.....	\$2500
ENI 1140LA, Power Amplifier, 9KHz-250KHz.....	\$3500
ENI 310L, RF Amplifier, 50dB, 250KHz-110MHz.....	\$2000
ENI 325LA, Power Amplifier, 250KHz-150MHz, 25 Watts.....	\$1850
ENI 503L, RF Amplifier, 40dB, 2-510MHz.....	\$800
Fluke 5100B/03/05, Multifunction Calibrator.....	\$3000
Fluke 5101B/03, Calibrator.....	\$3000
Fluke 5200A, AC Voltage Calibrator.....	\$2000
Fluke 732A, DC Standard.....	\$1850
Gigatronics 910, Frequency Synthesizer, .05-26GHz.....	\$9500
Kikusui PAD16-10L, Power Supply, 16V, 10A.....	\$300
Kikusui PLZ700W, Electronic Load.....	\$850
Krohn-Hitt 3202R3202, Tunable Filter/Rack Version.....	\$500/\$350
LeCroy 9424, 350MHz Oscilloscope.....	\$3500
Marconi 2019A, Signal Gen., 80KHz-1040MHz.....	\$2200
Philips 6652C, Prog. High Res. Counter/Timer, 8 Digit, 120MHz.....	\$1300
Philips PM3394, 200MHz Oscilloscope.....	\$2250
Sorensen DCS40-25, DC Power Supply, 40V/25A.....	\$750
Trans. Devices DLR400 15 3500A, Dynamic Load.....	\$1500
Trans. Devices DLP 50-60-1000A, Electronic Load.....	\$800
Trans. Devices DLPV 130-110-1000 Electronic Load.....	\$950
Trans. Devices DLPV 50-120-1000 Electronic Load.....	\$1000
Valhalla 2703, AC Voltage Standard.....	\$2350
Varian VZL6942G5JM, Amplifier, 1-2GHz, 100 Watt.....	\$8000
W & G SNA5, 50Hz-3.2GHz Spectrum Analyzer.....	\$6000
Wavetek 178, Automatic Synthesizer.....	\$1850
Wavetek 3000, Signal Generator, 1-520MHz.....	\$900
Wavetek 3000-200, Signal Generator.....	\$900
Wavetek 3001, Signal Generator 1-520MHz.....	\$1000
Wavetek 801, Pulse Generator, 5Hz-50MHz.....	\$800
Wiltron 561, Scalar Network Analyzer.....	\$2500



## R & S Surplus

1050 E. CYPRESS STREET, COVINA, CA 91724

(626) 967-0846 • FAX (626) 967-1999



# NEWYEAR SPECIALS

## SUPER SAVING UPGRADE KIT

M/BOARDS WITH CPU, 8MB AGP & SOUND:	
K6-2 300 MHz MMX	\$199
K6-2 333 MHz MMX	\$229
K6-2 350 Mhz MMX	\$259
Pentium II Celeron 300	\$199
Pentium II Celeron 300 w/128Kcache	\$209
Pentium II Celeron 333 w/128Kcache	\$229
Pentium II 266 MMX	\$299
Pentium II 300 MMX	\$369
Pentium II 333 MMX	\$359
Pentium II 350 MMX	\$369
Pentium II 400 MMX	\$495
Pentium II 450 MMX	\$675

CASES WITH POWER SUPPLIES	
MED TOWER CASE PREMIUM.....	\$29
ATX MED TOWER CASE PREMI..	\$49

## FLOPPY

1.44 Mitsumi.....	\$ 16.95
-------------------	----------

## MONITORS

14" 28 108 N-I, Low Radiation.....	\$119
15" 28 1024x768 N-I, Low Rad.....	\$145
17" 28 1280x1024 N-I, Low Rad.....	\$239

## KEYBOARDS

104 Keyboard.....	\$10
Keytronic.....	\$19
Focus 2000.....	Scall

## VGA CARDS

SVGA 1MB ISA.....	\$35
PCI 1MB/2MB/4MB.....	\$14/25/39
PCI OR AGP 4MB, TV OUT, OPTI.....	\$39
PCI OR AGP VGA 8MB.....	\$69
BANSHI 16MB.....	\$119
WOODO II 12MB W/incoming & G-Police.....	\$119
ANY OTHER VGA CARDS.....	SCALL

## CONTROLLER SCSI

DIAMOND FIRE PORT 40.....	\$95
Adaptec 2940/2940UW/2940U2W.....	\$149/169/379

## MODEM/ FAX MODEM

33.6K Voice Modem/ Fax Modem.....	\$26
56K Voice Modem/ Fax Modem.....	\$29
US ROBOTIC 56K Modem...V90.....	\$89
ISDN.....	SCALL



## 36X CDROM..\$45

### Orders & Price

Tel:(800) 899 6430

### 36X Bundle

**\$69**

36X Speed CD  
16 Bit Sound Card  
with Wavetable.  
Amplified Speakers 80W

For ALL kinds of Drives, Sound Cards  
Speakers and CD Titles: SCALL

## HARD DRIVES SPECIALS

4.3GB..\$136 6.4GB..\$155 8.4GB..\$185 11GB..\$255

13.5GB..\$295 16GB..\$395 21GB..\$555 any other CAL

## IBM 6X86

### 333 MMX

Motherboard  
CPU, 8MB AGP  
VGA & SOUND

**\$199**

### All Systems carry

5 years Parts &

5 years Labor

Warranty.

Lifetime Tech

Support

## Simm Memory

### LOW \$\$\$

Will beat any price

Resellers

Dealers

Welcome

us out

No Minimum Charge.No Hidden Charge.

Prices subject to change without notice.

15% Restocking fee for Non Defective Items.

Orders of \$950 or more, ground shipping free,

except for Cases, Monitors, Keyboards and F/Drives.

## AMD K6-2

### 350 MMX

Motherboard  
CPU, 8MB AGP  
VGA & SOUND

**\$249**

## CREDIT CARDS OK

MasterCard, Visa, Discover, American Express

\*Govt.P.O.\* C.C.O.D.

## EVERYDAY LOW PRICES

[www.bisme.com](http://www.bisme.com)

**BISME COMPUTERS OUTLET** 906 N Carpenter Rd, Suite A, Modesto, CA 95351

Write in 47 on Reader Service Card.

**WANT USED** or surplus DC motor controls or adjustable frequency AC drives, 1/2 HP and up. DC motors fractional to 3 HP. C. Woodruff, 5507 55th Ave. S., Seattle, WA 98118. Voice/Fax 206-723-8487.

**WANTED: TUBES**, radios, transmitters, receivers, gyros, bearings, connectors, relays, lamps, synchros. Hyness Company, 709B Delair Road, Cranbury, NJ 08512-4212. Phone: 609-395-1116, FAX 609-395-1117.

**WANTED: BALANCING** machines & vibration analyzing equipment manufactured by the following: Spectral Dynamics, Hofmann, Bentley Nevada, Schenck, IRD Mechanicals, Gishott. Contact Mike Park at E.T. Balancing, 12823 Athens Way, Los Angeles, CA 90061. 310-538-9738, FAX: 310-538-8273.

**RADAR/MICROWAVE** equip: Aviation, marine, fire control. Like TPS 21, APS 10, 42 APG 30. Parts, TM's, etc. Radar, Box 10215, Pittsburgh, PA 15232.

**WANTED: AVIONICS** test equipment, IFR, 600A, 401L, others, Collins, King, Sperry, North Atlantic, Litton INUs LTN series, rate and tilt tables, air data test sets, 941-625-3222 P, 941-625-0494 F, E-Mail: avionics@afcon.net

**WESTERN ELECTRIC** audio equipment wanted. 1927-1960's. Amplifiers, "preamps," speakers, transformers, tubes, etc. 1-800-251-5454.

**WESTERN ELECTRIC WANTED:** 1920's-1960's. Amplifiers, mixers, preamps, speakers, tubes, etc. FREE OFFER 1-800-251-5454.

**WANTED: ELECTRONIC** estates. Ham, broadcasting, military, test, public address, tubes, transformers, telex equipment. The bigger the pile, the more worthwhile. We fly anywhere. Sumner McDanel 1-800-251-5454.

**ELECTRON TUBES**, transistors-RF aircraft radar & comm. Sold or bought. ARS Electronics, 7110 De Celles Pl., Van Nuys, CA 91406. 1-800-422-4250, fax 818-997-6158.

**WANTED: GR1630AV; GR1620;** power resistors (carbon tube, heatsink wv preferred, 50wt); AC capacitors (60 out, .1uF-50uF). 610-932-4019.

**DEC EQUIPMENT WANTED!!!** We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), DSD, Datability, Dilog, other DEC compatibles, and Computer Output Microfilm (COM) units. Please call for a quote or fax us your equipment list. We buy, sell, and trade. **KEYWAYS, INC.**, 937-847-2300 OR fax 937-847-2350.

## BBS & ONLINE SERVICES

**VISIT DON** Lancaster's GURU'S LAIR website at <http://www.tinaja.com> PICs, pseudoscience, PostScript, patents, Tinaja quests, flutterwumpers, book-on-demand, magic sinewaves, money machines, Navicubes, tramways, wavelets, and Webmastering. Online reprints, consultants net, forums, annotated hot links, surplus bargains, great heaping bunches more.

**MOD CHIPS** for Sony PlayStation. Now your backups will work. Only \$9.95 ea. + \$3 shipping. Call 1-888-467-6150, all major credit cards accepted. Computers & components at wholesale prices. [www.cconusa.com](http://www.cconusa.com)

## EDUCATION

**START YOUR OWN TECHNICAL VENTURE!** Don Lancaster's newly updated **INCREDIBLE SECRET MONEY MACHINE II** tells how. We now have autographed copies of the Guru's underground classic for \$18.50. Synergetics Press, Box 809-K, Thatcher, AZ 85552. 520-428-4073. VISA/MC.

**DON LANCASTER'S ACTIVE FILTER COOKBOOK** is back in print. Autographed copies of the seventeenth(!) classic printing \$28.50. **SYNERGETICS PRESS**, Box 809-N, Thatcher, AZ 85552. 520-428-4073. Visa/MC.

**GRAND UNIFIED THEORY MADE EASY.** 110 page book explains a new theory linking gravity, electronics & magnetism. Explores universe mysteries, goes beyond relativity & quantum theory. \$9.95. To order: send check or M/O to American Science Innovations, PO Box 155, Clarington, OH 43915.

## BUSINESS OPPORTUNITIES

**START YOUR OWN TECHNICAL VENTURE!** Don Lancaster's newly updated **INCREDIBLE SECRET MONEY MACHINE II** tells how. We now have autographed copies of the Guru's underground classic for \$18.50. Synergetics Press, Box 809-K, Thatcher, AZ 85552. 520-428-4073. VISA/MC.

**THE CASE AGAINST PATENTS.** Thoroughly tested and proven alternatives that work in the real world, \$28.50. **SYNERGETICS PRESS**, Box 809-N, Thatcher, AZ 85552. 520-428-4073. Visa/MC.

**MILITARY COMPONENTS** wanted. Capacitors, resistors, diodes, transistors, semiconductors, ICs. Electronic Material Industries, 818-769-1002, FAX: 818-769-1084.

**MILLIONS \$\$\$** in "scrap gold" from old computers and electronics junk. Message: 603-645-4776 or [www.tiac.net/users/quiksand/goldtek.htm](http://www.tiac.net/users/quiksand/goldtek.htm)

**WHAT! YOU** don't have TELECODE's NEW 1998-9 "HACKER CATALOG," yet! 125+ items. Call 520-726-2833. Surf online at <http://www.hackerscatalog.com>

**ACP's 89th GIANT COMPUTER SWAP★MEET**

Orange County's Original

All Day Sunday 8am-2pm

**Jan 31st**

FREE Admission & Parking Shop 100's of Sellers

in ACP's Giant Parking Lot !!!

Advanced Computer Products, Inc.

**ACP SUPER★STORE**

Since 1976

1310 E. Edinger Santa Ana, CA 714-558-8813

**CABLE TV CONVERTER**

R-860V, 135 Ch, Volume Control Converter

135 channel volume control converter, with remote control, ch-3/4 output, audio/video output, parental lock, MFT(manual fine tuning)& Memory, HRC/Std, sleep timer, 117VAC

R-550E, 85 Ch, Plain Converter

85 channel converter with remote unit, ch-3 output, parental lock, HRC/Std, sleep timer

Call or Fax us for free brochures and price list

**PCW CO** TEL : (310)515-5085/756-7710(FAX)

HOME PAGE:  
www.hamboree.org



# ARRL HAMFEST OF THE AMERICAS & 39TH ANNUAL TROPICAL HAMBOREE® AMATEUR RADIO & COMPUTER SHOW

FEBRUARY 6-7, 1999

## FAIR EXPO CENTER

S.W. 112 AVENUE & CORAL WAY (S.W. 24 ST.)  
MIAMI, FLORIDA

TALK IN:  
146.925, 146.76  
444.595  
Information Loop:  
147.555

E-MAIL:  
edg@elink.net  
wd4stg@bellsouth.net

INTRODUCTION TO AMATEUR RADIO DISPLAY • VHF TRANSMITTER HUNT • TECH TALKS ON APRS  
ANTENNAS • DXPEDITIONS • AMATEUR SATELLITES • YOUTH FORUM • ARRL FORUM  
DX FORUM • COMMERCIAL EXHIBITS • 900+ SWAP TABLES • ON-SITE EXAM SESSIONS  
FIELD CHECKING FOR DXCC AND CQ AWARDS  
ALTERNATIVE INTEREST PROGRAMS AND DEMONSTRATIONS  
NUMEROUS "FREE AWARDS" PLEASING TO ALL

## NEW FOR 1999

COMPUTER SEMINARS AND DEMONSTRATIONS  
HINTS ON "BASIC COMPUTER MAINTENANCE" • "GETTING CAUGHT BY THE INTERNET" AND MORE

AIR-CONDITIONED FACILITY • ON-SITE CAMPING FOR 300 RV'S  
FREE PARKING FOR 15,000 VEHICLES • WHEELCHAIR & STROLLER RENTALS  
ON-SITE REFRESHMENT AREAS • ATM IN MAIN BUILDING FOR THOSE "SPECIAL SALE PURCHASES"

Registration: \$5.00 Advance (deadline Feb. 5th) - Door: \$7.00, Tax included  
Campsites: 3 days (Fri., Sat., Sun.) \$54.00 • 4 days (Thur., Fri., Sat., Sun.) \$72.00  
Check out with Camp Committee by 5:00 P.M. Sunday for mail refund of Sunday fee.

### Exhibit Fees for Two Days of Show

10' x 10' Booth: \$250.00, includes company sign, power, undraped tables, chairs & tickets  
Additional booths: \$200.00 per 10' space  
Area "C" Tables: \$60.00 per draped table (min. 4 tables), includes power & tickets  
Swap Shops "A and B": \$33.00 per table plus power @ \$10.00 per user & tickets.  
Telephone lines to booths or tables @ \$115.00 per line.  
(Request exhibit reservation form by e-mail, fax or postal mail prior to sending payment)

HEADQUARTERS HOTEL: AIRPORT FAIRFIELD INN SOUTH: \$72.00 single, double + 12.5% tax  
Location: Marriott Complex, 1201 N.W. LeJuene Road (N.W. 42 Ave.)  
Telephone: 800-228-2800 (Only 100 rooms available at special rate)  
Mention "Tropical Hamboree" • Cutoff date is January 15, 1999

CHECKS AND/OR MONEY ORDERS FOR TICKET, CAMP, EXHIBIT FEES SHOULD BE  
PAYABLE TO DADE RADIO CLUB OF MIAMI, INC.

Mail to: Evelyn Gauzens, W4WYR, 2780 N.W. 3 St., Miami, FL 33125-5059

BOOTH & TABLE INQUIRIES: Email: edg@elink.net, Tel: 305-642-4139, Fax: 305-642-1648  
wd4stg@bellsouth.net, Tel: 305-226-5346

⇒ CHECK OUT OUR HOMEPAGE: www.hamboree.org ⇐

INTERNET DISTRIBUTORS wanted.  
The nation's largest privately-held ISP  
needs distributors in all areas. E-Mail:  
rgobel@navix.net for free information.

## REPAIRS - SERVICES

ENGINEERING CONSULTING. Product  
development from conceptual to  
manufacturing stages. Digital, analog,  
and RF expertise. Microcontroller  
designs for HC05xx, HC11xx, and PIC  
families. Software design for IBM PC.  
XILINX and Altera FPGA design. In-  
house schematic capture and PWB.  
Hicks Electronic Design, PO Box 7366,  
Loveland, CO 80537-0366. Toll Free 1-  
888-849-6792 E-Mail: steve@hickseng  
ineering.com website: www.hickseng  
ineering.com

PINBALL MACHINES! Books,  
Magazines, Manuals, Diagrams,  
Supplies, Parts. \$2 catalog, Marco  
Specialties, 5290-N Platt Springs Rd.,  
Lexington, SC 29073-9252. 803-957-  
5500. FAX 803-957-6974. E-Mail:  
tilt@ix.netcom.com http://pinball  
machine.com

SCRATCH REMOVER for antique or  
new radios, TVs and other electronic  
pieces. Works with any color. 100% guar-  
anteed. Send \$10 to: Scratch Out, 1922  
Cassowary Lane, Apex, NC 27502. 1-  
888-363-9510.

When Visiting Disney World And Sea World...  
Come To The World Of Electronic Surplus!

## SKYCRAFT

PARTS & SURPLUS, INC.  
ORLANDO, FLORIDA



Located At The Intersection Of I-4  
And Fairbanks Avenue.

Self-Service Retail Outlet Featuring Commercial  
And Government Electronic Surplus Including:

- ★ WIRE
- ★ SWITCHES
- ★ RESISTORS
- ★ TRANSISTORS
- ★ TRANSFORMERS
- ★ TEST EQUIPMENT
- ★ NI-CAD BATTERIES
- ★ COAX
- ★ RELAYS
- ★ HARDWARE
- ★ CAPACITORS
- ★ PANEL METERS
- ★ CIRCUIT BOARDS
- ★ INTEGRATED CIRCUITS.

### HOURS:

Monday - Friday 8:30-6:00  
Saturday 8:30-5:00

★ ★ ★ ★ ★ ★ ★ ★  
We Buy Surplus  
Electronic Parts -  
FAX your list.

FAX 407/647-4831

PH 407/628-5634

P.O. BOX 536186

ORLANDO, FLA. 32853-6186



## REFILL INKS FOR INKJET PRINTERS

Refill your old cartridge and save. All refill kits come with instructions and  
needed materials for refilling inkjet cartridges. Success guaranteed.

Available for the following:

CANON BC-01, BC-02 CANON BJI10e, APPLE STYLEWRITER, BJ-200  
Single Black Refill \$8.00; Triple Refill \$19.00. CANON BJC-600 (BC-201)  
Single Black or Single Colors (3 refills) \$8.00. CANON BJ-130/300/330  
& IBM Exec Jet (Cart #BJI-481 & BJI-642) Black - 3-bottle kit \$22.00.  
CANON BJC-210/240 (BC-05 Cart) 3-color kit (3 refills each color for BC-  
05) \$24.00. CANON BJC-4000 and Apple Stylewriter 2400 Black 3-bottle  
kit (3 refills BC-20, 9 refills BCI-21 black, 30 refills BCI-11 black, 10 refills BCI-10) \$19.00. CANON  
BJC-4000/BJC70 and Apple Stylewriter 2400 Tri-color kit - 6 refills each color for BCI-21 or 15  
refills each color for BCI-11 \$24.00. CANON BJC-800/820/880 3-bottle kit (for BJI-643B) \$19.00.  
CANON BJC-800/820/880 3-bottle tri-color kit (Cart #BJI-643CMY) \$24.00. EPSON STYLUS  
COLOR PRINTER - (Cart S020034) Single Triple black \$19.00; Tri-color kit (Cart S020036) 2 refills  
each color \$24.00. EPSON STYLUS COLOR II - (S020047) Triple Black \$19.00 (S020049). Tri-color  
(2 refills each color) \$24.00. EPSON STYLUS COLOR 400, 500, & 600 (S020093) Triple black (7  
refills total) \$19.00; EPSON STYLUS COLOR 200, 500 (S020097) Tri-color 3 refills each color  
\$24.00. EPSON STYLUS COLOR 400, 600, 800, 1520 Tri-color (S020089) 3 refills each color  
\$24.00. EPSON STYLUS 800/1000 (S020025) 3-refill kit, black, \$19.00. HP DESKJET  
500/550/560 (51608A, 51633A, 51626A) Black single refills \$8.00. HP DESKJET  
500/550/560. Black 3-bottle kit \$19.00. HP DESKJET 500C/550C/560C. Tri-color kit (5 refills  
each color) \$24.00. HP DESKJET 1200C, DESIGNJET 650 (Cart #HP 51640B) Black Three pack  
(3 refills) \$19.00. HP DESKJET 1200C/1600C, DESIGNJET 650 (Cart #HP 51640 C,M,Y). Tri-  
color kit (one refill each color) \$24.00. HP DESKJET 600/660 (HP 51629A) Black three pack  
\$19.00. HP DESKJET 600C/660C. (HP 51649A) Tri-color (5 refills each color) \$24.00. HP  
DESKJET 855C/1600C (HP 51645A) Black three pack \$19.00. HP DESKJET 855C (HP 51641A)  
Tri-color kit (2 refills each color) \$24.00. HP DESKJET 720, 722, 890, OFFICE JET 1170 & 1175  
(C1823A) Tri-color kit (2 refills each color) \$24.00. HP PAINTJET and PAINTJET XL (51606A) Black  
3-bottle kit \$19.00. HP PAINTJET and PAINTJET XL (51606C) Tri-color kit \$24.00. HP PAINTJET  
XL300 (C1645A & C1656A) Black 3-refill kit \$19.00. HP PAINTJET XL300 Tri-color kit (1 refill  
each color) HP 51639C,M,Y \$24.00. HP THINKJET, QUIETJET, KODAK DICONIX 150 (51604A  
or 92261A) black 5 refills \$9.00. IBM/Lexmark/Execjet/4076 (1380620) black 3-refill kit \$19.00.  
IBM/Lexmark ExecJet IIc, WinWriter 150 C (Cart #1380619) 4 refills each color \$24.00. SNAP  
AND FILL SYSTEM - Permits refilling HP 51626A (black for HP 500-series) and HP 51629A (black for  
HP 600-series) cartridges without making a hole in the cartridge. Consists of special cartridge holder,  
syringe, plastic tubing, and directions. STARTER KIT - with ink for 3 refills \$28.00. EXTRA INK FOR  
SNAP & FILL SYSTEM (black only) 4-oz. bottle \$18.00; 8-oz. bottle \$34.00. Specify whether for HP  
51626A or HP 51629A.



## HARD-TO-GET PRINTER RIBBONS

Gorilla Banana, Commodore 1525 \$8.00; Adam Coleco \$12.00; TI-850/855  
\$6.00; Centronics 700 Zip Pack \$5.00; C. Itoh Prowriter Jr., Riteman C+/F+  
\$6.00; Riteman Infomuser \$8.00; Commodore MPS-801 \$5.00; MPS-803 \$7.00; Decwriter LA30/36 \$4.00;  
Apple Scribe \$4.00; Mannisman Tally Split 80, Commodore 1526 \$5.00; Epson JX-80 4-Color \$14.00.  
Printonix P-1013 \$11.00; Star SJ144 color 3-pack \$29.00.

ALSO HEAT & TRANSFER RIBBONS AND PAPER FOR PRINTING T-SHIRTS.

Over 300 different ribbons in stock. All ribbons new, not re-inked. Fully guaranteed.

Order directly or send SASE for complete list.

Add \$4.00 per order shipping. California residents add 7.75% sales tax.  
On ribbon orders over \$50.00 deduct 10% discount.

## H.T. ORR Computer Supplies

249 Juanita Way, Placentia, CA 92870-2216

714-528-9822 • 800-377-2023 • FAX 714-993-6216

http://www.extremeplay.com/occomp/orr.htm

Write in 48 on Reader Service Card.

## WHOLESALE CABLE BOXES

## CONVERTERS • FILTERS




Call Us To  
Satisfy All Of Your Cable  
Equipment Needs!

WE CARRY ALL  
THE MAJOR  
BRAND NAMES!

THE BEST  
DEALER  
PRICING!

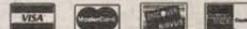30 DAY MONEY BACK  
GUARANTEE!  
1 YEAR WARRANTY



Call Now and Take Advantage!!!

## MODERN ELECTRONICS

1-800-906-6664

2609 S. 156TH CIRCLE • OMAHA, NE 68130

VISIT OUR WEB SITE: http://www.modernelectronics.com

E-MAIL: modern@modernelectronics.com

Write in 50 on Reader Service Card.

January 1999 61

**(E)PROM PROGRAMMING** done quickly and economically. One day turn around typical. Simple copy \$3 per device. Also prototyping, design, and consulting services available. Call or send SASE to: **Luzer Electronics, 4023 North Bayberry, Wichita, KS 67226. 316-687-2127, FAX 316-687-3103.**

**PICS, GALS READ** if you've lost your masters. Programming service available. Call for info. Network Sales, 616-683-0500.

**PLAYSTATION MOD chips.** Works with all models up to 750x. Color instructions. Five wire hook up, comes with wire. \$5 each, plus shipping charges. 10% discount for 10 or more. Call 703-764-5118.

**WELD ALUMINUM WITH PROPANE!** EZ, INEXPENSIVE, STRONG. DETAILS: WEEKS, 36 CAROLINA ST., TAYLORS, SC 29687. 1-800-547-WELD(9353) FAX 864-244-6349. <http://www.dura-fix.com>

**PC BOARDS REPAIRED.** Prices start at \$5. Minimum 5 of one type. Network Sales, 616-683-0500.

**PROFESSIONAL PRINTED** circuit design on CAD, over 30 years experience. All types of designs: conventional, multilayer, downhole, fine line. Prototype and production boards fabricated. Reverse engineer existing two layer boards. Quick service with affordable cost. Call now for your quote. Tel 713-952-8623, Fax 713-952-8624.

**REPAIR PERSON NEEDED:** to repair my SAE500A analog impulse noise reduction device. It once removed clicks & pops from records during replay, but no longer works at all. No schematic available as far as I know and the company appears to be out of business. Want to give it a try? [wardzone@sprynet.com](mailto:wardzone@sprynet.com)

**CABLE CONVERTER REPAIR:** Quality repair service for all name brands. If you're tired of the runaround you're getting from the company you purchased it from, or they're out of business. Give us a call for fast and courteous service. Have model and problem ready. Sorry no box, chip, or IL repairs. **Highview Engineering 815-245-3735 or E-Mail: HIGHENG1@AOL ask for George.**

# Unlock a World of Performance!

## ACE COMPUTERS

Delivering Power and Performance for Less Since 1983

1425 East Algonquin Road  
Arlington Heights, IL 60005

(847) 952-6900

(847) 952-6901 FAX

Call Toll-Free

1-877-ACE-COMP

[www.acecomputers.com](http://www.acecomputers.com)



"The Ace GamePro 2000 is a great gaming system with a price you'll like as much as the games you'll play"  
- Computer Buyer's Guide and Handbook, October, 1998  
"A Power User's Delight"  
- Computer Buyer's Guide, Summer 1998  
"Ace loads its system with enough high end components to turn a power user's head."  
- Computer Shopper, August 1997

"Fast all around and affordable - an excellent value"  
- Computer Buyer's Guide and Handbook, July 1998  
"Top 100 Direct Vendor"  
- PC Computing, February 1998  
"BEST BUY - Ace has put together a system that's sure to please just about any consumer."  
- Computer Buyer's Guide & Handbook, May 1998

"High quality components, Fast speed and Reasonable price - A real business workhorse!"  
- PC Today, June 1998  
"A fine system that would be valuable to any business - A great value!"  
- PC Today, July 1998  
"2 TIME BEST BUY - The right blend of nice touches - a computer worth seriously thinking about when it's time to buy."  
- Computer Buyer's Guide and Handbook, August, September 1998

Pro Series Notebooks	GamePro 2000
<b>TRACER/TRAVELER</b>	<b>Intel Pentium® II Processor w/512K Cache</b>
• Intel Pentium® 233MHz/Pentium® II Processor	• 64 Megs SDRAM/ 6.5GB Ultra DMA Drive
• 12.1" or 14.1" Active Matrix Screens	• Creative Labs DVD Drive Kit/1.44M Floppy
• 20X or 24X CD-ROMs and 1.44M FDD	• US Robotics 56KB V.90 Fax/Modem
• 64 Megs SDRAM	• Matrox G100 AGP with 8M SGRAM
• 3 or 4 GB Hard Drive	• Diamond Monster II w/12M SGRAM
• 56KB Fax/Modem	• Iomega 100 MB Zip Drive
• 3D Sound with speakers	• 20" (18.8" Viewable) SVGA Monitor
• Touchpad Mouse	• Diamond Monster MX200® PCI Sound
• Full Travel Keyboard	• Pro SW-12 Subwoofer w/4 Satellite Speakers
• Carrying Case Included!	• Microsoft Ergonomic Style Mouse/104 Kb
• Windows 98 Included!	• Mini-Tower Case w/6 Bays
• 1 Year Warranty	• Windows 98 Installed
TRACER with PENTIUM® 233 MMX® (12.1", 3GB, 20X CD-ROM) - \$1499	PENTIUM® II 300 - \$2249
TRAVELER with PENTIUM® II - 266 (14.1", 4GB, 24X CD-ROM) - \$2649	PENTIUM® II 333 - \$2279
	PENTIUM® II 350 - \$2329
	PENTIUM® II 400 - \$2479
	PENTIUM® II 450 - \$2679

Intel FINANCIAL Leasing Available!  
Custom Configurations Available!  
Options on-site warranties available on all systems!  
We accept all major credit cards. We accept Fortune 1000, Government, and Educational Institution Purchase Orders. We respond to invitations for commercial and educational open bids. Business leasing available to qualified applicants. Prices, appearance, and specifications subject to change without notice. 17" monitors are 15.9" VHS or better, 19" monitors are 18.8" VHS or better. Certain models may include upgraded components. All custom configurations are available. 15% restocking fee on returns of custom-built systems. 30 day return policy does not include shipping charges, incurred damages, or service charges. All returns must include original packaging, accessories, and documentation in as-new condition. Monitors may be manufactured by third parties. Viewable sizes of monitors vary. The Intel inside logo and Pentium are registered trademarks of Intel Corp.

Enhanced IDE & SCSI2 Hard Drives	Memory - SIMMs/DIMMs	Microprocessors	Motherboards for Pentium Processors
2.14 Gig Seagate/Western Digital 10 ms access \$119	72 Pin SIMM Modules	Pentium® II-XEON 450/400 w/512K/1279/1934	BCM 575-AT-430TX.P75-233PCI w/512K, DIMM, MMX \$89
2.55 Gig Seagate/Mediatek 10 ms access \$125	4M NonParity/ECC/Parity \$104/10/19	Pentium® II-450/400/350 \$629/449/1299	Tyan Tomcat 4, Dual CPU, w/8 SIMMs, 512K \$159
3.2 Gig Seagate/Western Digital 11 ms access \$135	8M NonParity/ECC/Parity \$181/18/25	Pentium® II-333/300/266 \$249/229/199	Tyan Turbo-2 ATX AT, Intel 430TX w/8 SIMM/2 DIMM \$129
4.3 Gig Seagate/Western Digital 10 ms access \$145	16M NonParity/ECC/Parity \$354/34/48	Celeron® 333/300A/300/266MHz \$179/148/99/95	SuperMicro P55M380-Intel 430TX, 512K \$159
5.1 Gig Quantum Ultra DMA, 9 ms \$159	32M NonParity/ECC/Parity \$69/65/83	Pentium® 233 MMX/200 MMX \$139/110/9	Quicktrak, P75-20 w/Adaptac 2940UD SCSI2, 512K Ppa. \$159
6.4 Gig Seagate/Western Digital, Ultra DMA, 9 ms \$179	64M ECC/Parity \$109/112/9	Pentium® 200 Mhz/166 MMX \$149/89	ASUS T9917/ATX, AT-430TX.P75-233PCI w/512K \$89
8.4 Gig Quantum Fireball, Ultra DMA, 9 ms \$199	168 Pin DIMM Modules	Pentium® 166 Mhz/133MHz \$85/79	<b>Motherboards for the Pentium® II Processor</b>
8.6 Gig Seagate Mediatek, 9 ms \$199	16M SDRAM 10x \$20	AMD K5-300/266/233 MHz \$109/89/79	BCM 600 - 150-200 MHz, Intel 440FX Chipset, PCIIISA \$179
9.1 Gig Seagate Mediatek Pro 7200 RPM, Ultra DMA \$259	32M SDRAM 10x w/PC100 \$39/45	989/79/69	Supernova AT or ATX - Intel 440FX, PCIIISA \$179
10.1GB Western Digital, 5400 RPM, Ultra DMA \$239	64M SDRAM 10x w/PC100 \$85/89	1279/1278	Tyan Titan Pro - Single/Dual Processor PCIIISA, AT or ATX \$149/124/9
11.5GB Maxtor Diamondmax, 5400 RPM, Ultra DMA \$259	128M SDRAM 10x w/PC100 \$175/185	ALL PROCESSORS COMPLETE WITH FULL WARRANTY!	Intel PR440FX - Dual Pro, UW SCSI, 10/100 LAN, Audio, ATX \$429
13.6GB Maxtor Diamondmax, 5400 RPM, Ultra DMA \$319			<b>Motherboards for the Pentium® III Processor</b>
16.6GB IBM Deskstar, 5400 RPM, Ultra DMA \$439			BCM 632 - Intel 440FX Chipset, PCIIISA/AGP/AMBIOS \$109
			BCM 634 - Intel 440FX, PCIIISA/AGP, 10/100 LAN \$139
			Intel AL440X - Intel 440FX, PCIIISA/AGP, DIMMs, Audio, ATX \$169
			Intel SE440BX - Intel 440BX, 100 Mhz Bus, CPU \$169
			Intel SE440LX/IR440LX - Adaptac, LAN, Audio, 2 CPU \$449
			Intel N440BX/TA40BX - Adaptac, LAN, Dual/Single \$579/379
			Asus P2B - Intel 440BX, PCIIISA/AGP, ATX \$119
			ABIT LB - Intel 440X, PCIIISA/AGP, ATX \$119
			ABIT BH-6 - Intel 440BX, PCIIISA/AGP, ATX \$119
			Soitek SL81B - Intel 440LX, PCIIISA/AGP/AT, SIMM/DIMM \$129
			Soitek - Intel 440BX, 100 Mhz Bus, AGP/PCI w/ SCSI \$119/129
			Soitek - Intel 440X, PCIIISA/AGP, ATX, 100 Mhz \$149
			SuperMicro P55L310S-440X, One/Dual P2, PCIIISA/AGP/SCSI \$219/229
			Supermicro P60B1-440BX, Dual P2, PCIIISA/AGP/SCSI \$299
			Supermicro P65B1-440BX, Single P2, PCIIISA/AGP/SCSI \$299
			Supermicro P55A1-440X, PCIIISA/AGP, ATX, 100 Mhz \$149
			Tyan Titan - Intel 440X/PCIIISA/AGP/AT Term Factor \$159
			Tyan Tiger II - AGP V, Dual Processor, ATX \$189
			<b>Boards for the Pentium® III Processor Processor</b>
			<b>Closely boards for the Xeon® Processor IN STOCK!</b>
			GGI P75-200, 256K Cache, 430FX \$49
			BCM 591593 - P75-200, 256K Cache, 430VX \$49
			BCM 594 - P75-200, MMX, 512K Cache, 430VX \$49
			BCM 594 - P75-200, MMX, 512K Cache, 430VX \$49
			Supermicro P5CMS - Intel 430FX, 256K Cache \$59
			Tyan Tomcat II - Intel 430FX, Dual Processor \$89
			Tyan Titan II - Intel 430FX, 5 ISA/4 PCIIISA, 256K Cache \$59

Don't see what you want listed? Just call us or see our Web site for a full catalog of fine quality products!  
[www.acecomputers.com](http://www.acecomputers.com)

**Discovery Station**

- Intel Pentium® II Processor w/512K Cache
- 32 Megs SDRAM/4.3GB Ultra ATA Hard Drive
- 32X Speed CD-ROM Drive/1.44M Floppy Drive
- 56KB USR Fax/Modem w/Voice Mail
- AGP Video with 4M RAM
- 17" Monitor - 0.28 Dot Pitch
- Yamaha 3D Sound with Desktop Speakers
- Microsoft Intellimouse Mouse/104 Keyboard
- Mini-Tower or Desktop Case w/6 Bays
- Windows 98 or Windows NT 4.0(Add \$99 for NT)
- 3 Year Complete Warranty Included

PENTIUM® II 266 - \$1279 • PENTIUM® II 350 - \$1379  
PENTIUM® II 300 - \$1299 • PENTIUM® II 400 - \$1549  
PENTIUM® II 333 - \$1329 • PENTIUM® II 450 - \$1749  
Business/Personal lease as low as \$47/Mo, 36 Months

**Home/Office Pro +**

- Intel Pentium® II Processor w/512K Cache
- 64 Megs SDRAM/ 6.4GB Ultra ATA Hard Drive
- 32X Speed CD-ROM Drive/1.44M Floppy
- US Robotics 56KB Fax/Modem
- Matrox Productiva G100 AGP with 8M RAM
- Goldstar 17" Monitor - 0.26 Dot Pitch
- Sound Blaster 128 PCI with Subwoofer Speakers
- Microsoft Ergonomic Style Mouse/104 Keyboard
- Mini-Tower or Desktop Case w/6 Bays
- Windows 98 or Windows NT 4.0(Add \$99 for NT)
- Office 97 Included!
- 3 Year Complete Warranty Included

PENTIUM® II 266 - \$1529 • PENTIUM® II 350 - \$1629  
PENTIUM® II 300 - \$1549 • PENTIUM® II 400 - \$1799  
PENTIUM® II 333 - \$1579 • PENTIUM® II 450 - \$1999  
Business/Personal lease as low as \$61/Mo, 36 Months

**Dreamed System**

- Intel Pentium® II Processor w/512K Cache
- 64 Megs SDRAM/ 16.4GB Ultra ATA Hard Drive
- Creative Labs DVD-ROM Drive/1.44M Floppy
- US Robotics 56KB Fax/Modem
- Matrox G200 AGP with 8M RAM
- 20" SVGA Monitor with 1600 x 1280 Resolution
- Sound Blaster Live! PCI with Subwoofer Speakers
- Microsoft Ergonomic Style Mouse/104 Keyboard
- Mini-Tower Case w/6 Bays
- Windows 98 or Windows NT 4.0(Add \$99 for NT)
- Office 97 Included!
- 3 Year Complete Warranty Included

PENTIUM® II 300 - \$2569 • PENTIUM® II 400 - \$2599  
PENTIUM® II 350 - \$2449 • PENTIUM® II 450 - \$2849  
Business/Personal lease as low as \$85.5/Mo, 36 Months

**ACE PowerWorks® Server 2400**


- Single or Dual Intel Pentium® II or Xeon® Processors
- 128 or 256 Megs ECC SDRAM/Expandable to 2 Gigs
- 3 - 4.5GB Ultra Wide SCSI2 RAID Hot Swappable Drives
- (3 - 9.1GB Ultra Wide SCSI2 RAID Hot Swappable Optional)
- 1.44M Floppy/32X SCSI2 CD-ROM Drive
- Integrated Intel PCI 10/100 Network Interface
- Microsoft Ergonomic Style Mouse/104 Keyboard
- Certified Server Chassis w/RAID Capability ("Cube Style for Xeon Processor")
- Remote Monitoring
- Windows NT Server 4.0 with 10 Client Licenses
- 4 Year National Onsite Parts and Labor Warranty Included!
- Professionally Tested with Novell, Windows NT & SCO Unix

CPU/128M/3-4.5GB Drives 2 CPUs/256M/3-9.1GB Drives

PENTIUM® II 266 - \$3679 • PENTIUM® II 266 - \$4549  
PENTIUM® II 300 - \$3729 • PENTIUM® II 300 - \$4649  
PENTIUM® II 333 - \$3779 • PENTIUM® II 333 - \$4749  
PENTIUM® II 350 - \$3899 • PENTIUM® II 350 - \$4999  
PENTIUM® II 400 - \$4049 • PENTIUM® II 400 - \$5299  
PENTIUM® II 450 - \$4249 • PENTIUM® II 450 - \$5699  
XEON® 400 - \$4799 • XEON® 400 - \$6349  
XEON® 450 - \$5149 • XEON® 450 - \$6999  
Business/Personal lease from \$121/Mo, 36 Months

You Win  
with  
Nuts & Volts  
Subscribe today and be automatically entered in our new DRAWING!!  
We now offer a three-year subscription for only \$51.00!  
(USA delivery only)

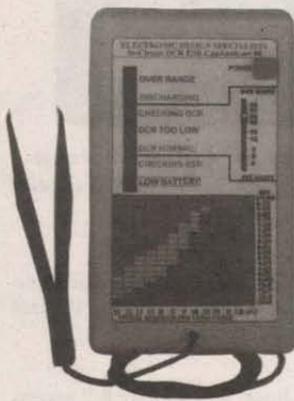
**CHECK CAPACITORS  
IN-CIRCUIT WITH  
100% ACCURACY**



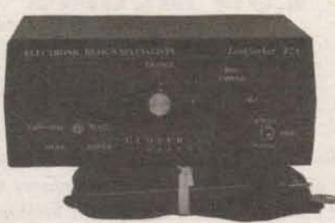**CapAnalyzer 88 \$179**

- Automatically discharges cap;
- Checks for low DCR and shorts;
- Checks high-frequency ESR and displays on 20-segment LED meter
- 3-color chart shows typical values.
- Includes gold-plated tweezer probe
- Portable... Batteries included!

**LOCATE ANY SHORTED  
or LEAKY COMPONENT  
TO THE EXACT SPOT**



**LeakSeeker 82A \$179**

Locates shorted & leaky parts to the exact spot on the PCB without cutting up the board or unsoldering any parts!

• **60 DAY SATISFACTION  
OR MONEY BACK  
GUARANTEE**

• **AVAILABLE AT YOUR  
FAVORITE DISTRIBUTOR**



**ELECTRONIC DESIGN SPECIALISTS**

4647 Appalachian St, Boca Raton, FL 33428 561-487-6103 www.eds-inc.com  
we make test equipment designed to make you money.

Write in 136 on Reader Service Card.

**TECH FORUM**

Continued from page 49

One solution would be a simple potentiometer, I'd suggest a value of 1000 ohms. If you assume you have eight-ohm speakers, and you're powering them with 100 watts, that means there's 28.28 volts across the speaker terminals.  $P = E^2/R$ ; so  $E = (P \cdot R)^{.5}$ ; so  $(100W \cdot 8 \text{ ohms})^{.5} = 28.28$  volts. Now calculate the amount of power drawn by the 1000-ohm pot: again  $P = E^2/R$ , so  $(28.28)^2/1000 = 0.8$  watts. That means you'll need at least a one-watt pot, and a higher power rating would be even safer.

Connect two identical circuits, one for each channel, as follows: Connect the speaker "common" terminal to the counter-clockwise end of the potentiometer, and also to one side of the VU meter. Connect the speaker "hot" terminal to the clockwise end of the potentiometer.

Connect the center terminal of the potentiometer to one end of the 3600-ohm resistor (1/2 watt is fine for the resistor's power rating).

Connect the other end of the resistor to the remaining terminal of the VU meter.

If you want attenuators that are calibrated, I suggest you look through the surplus catalogs. From time to time, you'll find someone selling stepped attenuators, with values typically 1 dB or 10 dB per step. These

are usually 600-ohm impedance. Be sure the attenuator's power rating is high enough, as shown above. Or, using Ohm's Law, you could build your own custom attenuator using 1% resistors and a two-gang rotary switch.

Greg Miller

gmiller@commedge.com

**ANSWER TO #11982 - NOV. 1998**

Either some jumpers were changed or the sound card was removed from the computer before it was sold. Windows knew about the card and can't find it, so it gives you an error message.

You may try re-installing the software for the card. From the Control Panel, click on the Add New Hardware icon and follow the on-screen directions. If the card is there Windows should find it. If it needs a disk it should tell you.

You may also want to check under Control Panel | System | Device Manager to see what the computer thinks is in your machine. Click on the Sound, Video and Game Devices icon then right click on each subsystem. Check the properties table that appears. Make sure that the hardware is selected and that there are no conflicts. Anything with a yellow question mark for an icon needs some attention.

**ELECTRONIC TEST EQUIPMENT  
BOUGHT & SOLD**

90 DAY WARRANTY PARTS & LABOR • 10 DAY RIGHT OF RETURN, OPEN ACCOUNTS

Altech 360D11, Frequency Syn., 01-2GHz	\$800	HP 86290B, RF Plug-In, 2-18GHz	\$1,400
Alltech Type 32, Precision Attenuator, 0-100dB	\$300	HP 8656B, Signal Generator, 1-990MHz, AM/FM	\$3,000
Argosystems AS210, Frequency Calibration System	\$2,000	HP 8660C, Freq Syn w/86603A & 86635A, 2.6GHz	\$2,500
Bird 4381, RF Power Analyst, Opt. 832	\$200	HP 8672A01, Signal Generator, 2-18GHz	\$5,000
Boonton 102B, Signal Generator, 45-520MHz	\$500	HP 8697A, RF Plug-In, 26.5-40GHz	\$250
Boonton 518-A4, C Standard	\$100	HP 8730A, Reflection Transmission Test Set	\$200
Boonton 82AD, Modulation Meter	\$650	HP 8734A01B, Reflection Transmission Test Set, 18GHz	\$300
Boonton 92BD, Digital RF Millivolt Meter	\$250	HP 8750A, Storage Normalizer, Includes Cable	\$250
Boonton 4200/4E, Power Meter, 18GHz	\$600	HP 8753B, Network Analyzer, 300KHz-3GHz	\$10,000
Boonton 4200/4G, Power Meter Sensors, 01-26.5GHz	\$200	HP 8755C, Network Analyzer Plug-In	\$250
Boonton 4220/51013, Power Meter, 18GHz	\$600	HP 8756A, Scalar Network Analyzer	\$1,500
Boonton 4300, Power Meter w/2-51013 Detectors, Calibrated	\$2,500	HP 8757A001, Network Analyzer, Opt. 001	\$4,000
Bruel & Kjaer 1612, Bandpass Filter	\$250	HP 8970A, Noise Figure Meter	\$4,000
Calif. Inst. 1011, AC Power Source	\$400	HP E3617A, DC Power Supply, 0-40V, 1A	\$250
Data Precision 6000/611, Waveform Analyzer	\$350	HP TMS03, Mainframe, 3 Slot	\$100
Datron 1062, Digital Multimeter	\$350	Keithley 192, Programmable DMM, 6.5 Digits, HP1B	\$600
DR Thiedig MILLI-TOZ, Ohmmeter, 1 MilliOhm-2 Termaohms	\$400	Keithley 195A, Digital Multimeter	\$300
Eaton 380K11, Frequency Synthesizer, 1-2000MHz	\$2,000	Keithley 614, Electrometer	\$700
EIP 371, Source Locking Microwave Counter, 18GHz	\$1,000	Kroh-Hite 3202, Filter, LP, HP, BP Unused	\$350
ESI 250DE, LCR Bridge	\$200	Leeds & North 1091, Capacitor Decade, .001uF-uF	\$150
ESI 296, Auto LCR Meter	\$600	Marconi 6960, Power Meter with 6920 Sensor	\$600
Fluke 515A, Portable Calibrator	\$300	Narda 5682, High Directivity Bridge, 2-18GHz	\$300
Fluke 6010A, Frequency Synthesizer, 10Hz-11MHz	\$300	Narda 5292 Directional Coupler, 1-18GHz	\$200
Fluke 6080/AVM Frequency Syn., 5-1024MHz	\$4,000	PMI 1018B, Peak Power Meter	\$200
Fluke 8922A, True RMS Voltmeter	\$200	Rascal Dana 1515, Delay Pulse Generator	\$500
Fluke 9010A, Micro-System Troubleshooter Opt. 001	\$200	Rascal Dana 1992, Frequency Counter, High Stab.	\$500
Fluke A55, Thermal Converter	\$200	Rascal Dana 9082P, Signal Gen. 1.5-520MHz	\$400
General Microwave 478A, Peak Power Meter	\$700	Rascal Dana 9303, True RMS RF Level Meter	\$500
General Radio 1433G, Decade Resistor	\$350	Rascal Dana 9515, Universal Counter, HP1B, Opt. 41	\$200
General Radio 1433G, Decade Resistor, 1.111111m.	\$300	Rohde & Schwarz SPN, Audio Generator	\$300
General Radio 1557, Vibration Calibrator	\$200	Schenck TF30, Super Cricket Transistor Tester	\$200
Gigatronics 600/6-12, Synthesized Source	\$1,000	Tek 1241A, Logic Analyzer, with Accessories	\$650
Gigatronics 600/10-18, Signal Generator, 10-18GHz	\$1,500	Tek 134, Probe Amplifier for P6021 & P6022	\$100
Guidline 9154C, Transvolt Standard Cell	\$300	Tek 1410, Sync Generator SP02, Color Bars TSG7	\$650
Guidline 9577, Precision DMM, 7.5 Digits	\$300	Tek 1420, NTSC Vectorscope	\$500
Hitachi V-212, Scope, 20MHz, Dual Trace	\$200	Tek 1470, NTSC Color Sync & Test Sig. Generator	\$500
HP 1124A, 100MHz Active Divider Probe, Unused	\$100	Tek 1502, TRD, Opt. 4, Chart Recorder	\$1,000
HP 11590A, Bias Network	\$250	Tek 1503/01/05, TDR, Scale in Meters	\$1,000
HP 11604A, Universal Extension	\$100	Tek 178, Linear IC Test Fixture, For 577	\$150
HP 11605A, Flexible Arm	\$100	Tek 2336, Scope, 100MHz, Dual Trace	\$700
HP 11638A, Calibration Kit, Type N	\$600	Tek 2432, Scope, Digital, 300MHz, 4 Channel	\$2,000
HP 11665B, Modulator	\$250	Tek 2445B/10/12, Scope, 150MHz, 4 Trace, HP1B	\$1,800
HP 11712A, Service Kit for 8670 Series Inst.	\$500	Tek 2465, Scope, 300MHz, 4 Channel	\$1,800
HP 11869A, Adaptor for Plug-In 8350A/B	\$350	Tek 305DMM, Scope, 10MHz, Dual Trace, DMM, battery	\$800
HP 16500A, Logic Analyzer System	\$2,000	Tek 4041, System Controller, GPIB	\$200
HP 16510B, Logic Analyzer Card, 16500A System	\$500	Tek 436/022, Power Meter w/8461A, Cable, GPIB	\$1,200
HP 16530A/16531A, Digital Scope Card, 16500A System	\$500	Tek 464, Scope, 100MHz Dual Trace, Storage	\$400
HP 16500A, Pulse Generator	\$1,000	Tek 465, Scope, 100MHz Dual Trace	\$400
HP 3312A, Function Generator, 1-13MHz, Sweep	\$400	Tek 491, Spectrum Analyzer w/Mixers to 40GHz	\$600
HP 3325A, Function Generator	\$1,200	Tek 492/02, Spectrum Analyzer	\$4,000
HP 3325A/01/02, Function Gen. Opt. 01/02	\$1,800	Tek 496P, Programmable Spectrum Analyzer	\$4,000
HP 3400A, RMS Voltmeter, 10Hz-10MHz	\$200	Tek 5A13N, Differential Comparator	\$250
HP 3455A, Digital Multimeter	\$300	Tek 5A20N, Differential Amp	\$100
HP 3456A, Digital Voltmeter, 6.5 Digits	\$600	Tek 604, XY Monitor	\$100
HP 3458A, Multimeter, 5.5 Digits	\$400	Tek 7020, Programmable Digitizer Pl	\$600
HP 3580A, Spectrum Analyzer, Opt. 02	\$800	Tek AA501, Distortion Analyzer	\$800
HP 4140B, Picocommeter, DC Source	\$2,000	Tek DC503, Universal Counter/Timer TMS00	\$150
HP 436A/022, Power Meter, HP1B	\$100	Tek DC504, Counter/Timer TMS00	\$100
HP 5004A, Signature Analyzer	\$100	Tek DM502A, Autoranging DMM	\$150
HP 5005B, Signature Multimeter	\$350	Tek FG502, Function Generator, 1Hz-11MHz	\$250
HP 5006A, Signature Analyzer	\$300	Tek PG046, Differential Probe	\$300
HP 5182A, Waveform Recorder, Generator	\$500	Tek PG508, Pulse Generator, 50MHz	\$300
HP 5316A, Universal Counter	\$200	Tek PS503A, Dual Power Supply	\$150
HP 5328A/021/040, Frequency Counter, DMM	\$250	Tek SC502, Scope, 15MHz, Dual Trace	\$200
HP 5334A/020, Universal Counter w/DVM	\$800	Tek SC503, Scope, 10MHz Storage	\$400
HP 5335A/010, Frequency Counter	\$800	Tek SG502, Sig. Gen. 5Hz-50KHz	\$400
HP 5335A/030, Frequency Counter, 1300MHz	\$800	Tek TG501, Time Mark Generator, New Style	\$200
HP 5340A, Frequency Counter, 18GHz	\$800	Tek THS 720, Handheld Digital Scope, 100MHz	\$1,200
HP 5350A/010/002, Microwave Frequency Counter	\$2,500	Texscan SSG2000, Freq. Syn., 100KHz-2GHz, AM, FM	\$1,800
HP 54100D, Digital Scope, 1GHz	\$2,000	Ungar 462A, Solder, Desolder Station	\$250
HP 54200A, Digital Storage Scope, Dual Trace, 200MG/S	\$1,000	Valhalla 2000, Auto Digital Watt-Ammeter	\$200
HP 6112A, Power Supply, 0-40V, 0.5A	\$200	V-DATA 5110, Semiconductor Tester, In/out Circuit	\$150
HP 8015A, Pulse Generator, 1Hz-50MHz, 30V	\$500	Wavelet 143, 20MHz Function Generator	\$200
HP 8165A, Programmable Signal Source, .0001-50MHz	\$1,600	Wavelet 1084, Signal Gen. Sweeper, 3.5-4.5GHz	\$300
HP 8350A/86290B, Sweep Oscillator, 2-18GHz	\$2,900	Wavelet 180, Sweep/Function Generator	\$200
HP 8350B, Sweep Oscillator Mainframe	\$2,500	Wavelet 185, Sweep Function Gen. 0001-5MHz	\$400
HP 83545A, RF Plug-In, 5.9-12.4GHz	\$1,200	Wavelet 186, 5MHz Phase Lock Generator	\$200
HP 83592A/02, RF Plug-In, 10MHz-20GHz	\$12,000	Wavelet 1910, XY Monitor, Dual Trace	\$400
HP 8410C/8412B, Network Analyzer w/8411A/Opt. 18, 18GHz	\$800	Wavelet 452, Filter, Dual Hi/L, 1Hz-10KHz	\$450
HP 8411A, Frequency Converters	\$250	Wavelet 7530A, FFT Spectrum Analyzer 0-100KHz	\$500
HP 8414A, Polar Display	\$300	Wavelet 907, Signal Generator, 7-11GHz	\$600
HP 8445B, Spectrum Anz., Automatic Pre-Selector	\$300	Wavelet 955, Micro Source, 7.5-12.4GHz, AM, FM, Sweep	\$1,000
HP 8496B, Attenuator, 110dB	\$250	Wiltron 560A, Network Analyzer	\$800
HP 8553B, Spectrum Anz., RF Plug-In, 1K-110MHz	\$200	Wiltron 560-97A50, SWR Autotester, .01-18GHz	\$500
HP 8554B/8552B, Spectrum Analyzer 141T, 1.2GHz	\$1,500	Wiltron 610D, Sweeper Mainframe	\$250
HP 8557A/180TR, Spectrum Analyzer, .01-350MHz	\$1,000	Wiltron 610D/8237D, Sweep Generator, 2-18GHz	\$800
HP 8559A/182T, Spectrum Analyzer, .01-21GHz	\$2,500	Wiltron 82130, RF Plug-In, 10MHz-4.2GHz	\$400
HP 8559A/853A, Spectrum Analyzer, Digital, .01-21GHz	\$3,500	Wiltron 82190, RF Plug-In, 2-8GHz	\$200
HP 8565A, Spectrum Analyzer, .01-22GHz	\$3,500	Wiltron 82230, RF Plug-In, 4-12.4GHz	\$250
HP 8566A, Spectrum Analyzer	\$20,000	Wiltron 82280, RF Plug-In, 7.9-18.5GHz	\$300
HP 86222B/H68, RF Plug-In, .01-4GHz	\$1,000	Wiltron 82275, VSWR Bridge, 10-1000MHz	\$150
HP 86241A, RF Plug-In, 3.2-6.5GHz	\$400	Wiltron 8647A-20/02/03, Programmable Sweep Generator	\$4,000
HP 86260A, RF Plug-In, 12.4-18GHz	\$400	Wiltron 8NF50, Autotester, 1-1500MHz, for 640	\$100
HP 86290A, RF Plug-In, 2-18GHz	\$1,200	Wiltron 7850, Detector, 1-1500MHz, for 640	\$100

**MONTHLY CLEARANCE SALE**

HP 54100D, 1GHz DIGITAL SCOPE  
RETAIL PRICE \$18,500 • SALE PRICE \$995

HP 8901A MODULATION ANALYZER  
RETAIL PRICE \$9,800 • SALE PRICE \$995

**HELPS INSTRUMENTS**

2631 Hillside Ave., Norco, CA 91760  
909-279-7347 • FAX 909-279-7347



# You Win with Nuts & Volts

Subscribe today and be  
automatically entered in our **new**  
**MONTHLY PRIZE DRAWING!!!**

A BEL MERIT  
DM-5050 DIGITAL MULTIMETER  
plus A \$50.00 CERTIFICATE  
TOWARDS PURCHASES AT:

January Drawing  
hosted by  
**HSC ELECTRONIC  
SUPPLY** (see page 3)

**HSC Electronic Supply**  
<http://www.halted.com>

Serving  
Silicon Valley  
since 1964!

OUR NOVEMBER WINNER:

**RICHARD HIGHT**  
of Tucson, AZ

As a special bonus, in addition  
to providing December's prize,  
**NETCOM** will be furnishing  
goodies monthly, including the  
**IC MASTER** and more ...

Our growing list of contributors  
includes ...

**Parallax  
Corporate Systems Center  
Resources Unlimited  
Timeline, Inc.  
Alltronics  
Electro Mavin  
All Electronics  
Roger's Systems Specialist  
Electronic Goldmine  
MCM Electronics**

DECEMBER PRIZE

A FOUR-VOLUME SET  
OF THE  
**IC MASTER  
REFERENCE MANUALS**  
covering  
1994 through 1997  
Furnished compliments of

**NETCOM**  
(netcomd@aol.com)  
See Page 13 this issue.

To Subscribe –  
Just fill in and mail the  
enclosed subscription card or  
call our toll free orderline at  
(800) 783-4624 with a  
Visa or MasterCard.

## ATTENTION CURRENT NUTS & VOLTS SUBSCRIBERS:

If you have a current, paid subscription to Nuts & Volts, you  
are automatically entered each month in our drawing!!

We now offer  
a three-year  
subscription  
for only \$51.00!!  
(USA delivery only)

If you do not wish to order a subscription,  
but would like to be entered in our drawing,  
simply **send or E-Mail** your name, address,  
and telephone number, to NUTS & VOLTS,  
430 Princland Court, Corona, CA 91719,  
drawing@nutsvolts.com. No phone entries  
accepted. All orders/entries must be  
received by the last day of the month to be  
included in that particular month's drawing.

Check us out on the web!  
<http://www.nutsvolts.com>

## Scott Edwards Electronics

### NEW! Graphics LCD Module with Serial Interface



The new G12864 makes it easy to display text and graphics on a  
128-by-64-pixel LCD. It interfaces with a computer through a 2400  
or 9600-baud RS-232 serial hookup.

#### Text Features

The G12864 works like a serial-receive terminal. It displays text in a  
4-line by 16-character format. Text is displayed in a large 8- by 16-pixel  
font, which can be edited to include custom symbols.

#### Graphics Features

The display lets you plot points, draw lines, and display full-screen  
graphics using easy instructions. Its flash memory stores the text font  
plus 14 screens. You can create fonts and graphics on your PC, then  
download them to the G12864 using the included software.

#### Convenience Features

A power supply and DB9 serial-port connector are built in. Connect the  
display to the (included) AC adapter; plug the (included) serial cable  
into your PC or other computer, and you're ready to go. Current draw  
ranges from 15mA (typical, backlight off) to 100mA (max, backlight on).  
For complete specifications, see our web site: [www.seetron.com](http://www.seetron.com).

Display, with starter pack: \$199    Display alone (OEM qty 1): \$179

Scott Edwards Electronics • PO Box 160 • Sierra Vista • AZ • 85636-0160  
ph: 520-459-4802 • fax: 520-459-0623 • e-mail: [info@seetron.com](mailto:info@seetron.com)  
Internet: [www.seetron.com](http://www.seetron.com)

Write in 132 on Reader Service Card.

## TECH FORUM

Often removing the offending  
device driver then running Find  
Hardware again will fix these sort of  
problems. If that doesn't help either  
buy a sound card or ask your seller  
what happened. Before you go back  
to the seller, though, open up the box  
and check for yourself to save some  
embarrassment.

Dave Sarraf

#### ANSWER TO #129814 - DEC. 1998

This timer is ideally implemented  
in a small microcontroller such as a  
PIC. The only components needed  
are a PIC, a crystal (try a 32,768Hz  
watch xtal), switch, and output  
device!

The program is so short, it can  
be written in assembler, BASIC,  
FORTRAN, or C. Sample pseudo code  
follows:

```
DO
  { WaitForSwitch
    For i:=1 to 20
      {
        Wait1Minute
        For cnt:=1 to 20
          {
            if(cnt<=i) BEEP1 else
          }
        BEEPO
        WaitHalfSec
        BEEPO
        WaitHalfSec
      }
    }
  }
```

}  
}

Wait1Minute and WaitHalfSec  
are simple decrement loops based  
on precomputed constants loaded  
into a variable or register, and being  
counted down to zero. BEEP1 and  
BEEPO turn an output bit on or off.  
The 20 second creep can be avoided  
by reducing the minute count by 20  
seconds, and always outputting 20  
beeps of which the first count writes  
1 (ON, OFF) and the remaining write  
0 (OFF, OFF). This method allows  
extremely accurate timing, easy to  
change the rules, and minimum  
parts count!

Barry Cole  
Sunnyvale, CA

#### ANSWER TO #12987 - DEC. 1998

I have played around with high  
voltage a lot, and since I do neon  
work, I have access to many high-volt-  
age transformers.

Building ion generators is fairly  
easy. Basically, all you need is a high-  
voltage transformer, rheostat, and  
an ion grid.

The rheostat controls the input  
of the transformer and the output of  
the transformer goes to the ion grid.

The ion grid is easily made. I used  
a 6" x 6" x 1/8" piece of plate-glass  
and epoxied mesh wire 4" x 4" to

# ONE STOP SUPPLIER

MILLENNIUM  
TRI 550  
PANASONIC  
JERROLD

"One call does it all!"

1-888-426-9787

REMOTES

FILTERS

A DOZEN OTHER CONVERTERS AVAILABLE!

Call for Quantity Prices

Open Monday - Friday 10:00 a.m. - 5:00 p.m. Saturdays 10:00 a.m. - 1:00 p.m.

No Florida Sales • We ship same Day • 90 Day Limited Warranty

WE BEAT ANY ADVERTISED PRICE IN THIS MAGAZINE!


Write in 135 on Reader Service Card.

## TECH FORUM

each side of the glass.

Epoxy is applied to each corner

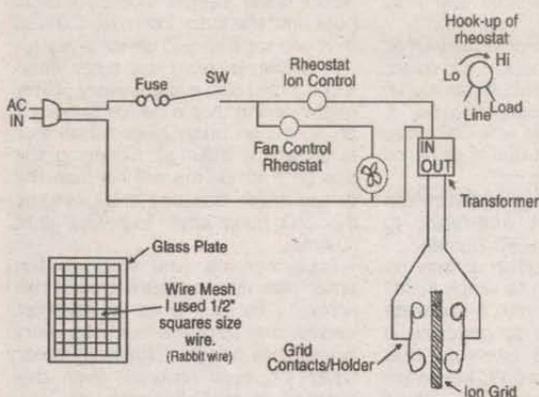of the mesh wire on both sides of the glass.



You can make some sort of a insulated stand to hold the ion grid. I built a box and added a B<sup>+</sup> computer fan and Heppa filter. The unit has two controls: One for the ion control and one for the fan speed, plus and off/on switch and fuse.

Ray Samples  
Fayetteville, NC

### ANSWERS TO #129815 - DEC. 1998

The PC timer chips have three counters. The count registers are at I/O ports 40h, 41h, and 42h, respectively. The Control Word is written to port 43h.

The timers are assigned as: Timer 0 — IRGO (timer tick); Timer 1 — DRAM refresh; Timer 2 — speaker control.

Loading a countdown value to one of the registers must be done in conformance with the Read/Load format already established for that timer. This format is set in the Control Word.

In attempting to control the speaker, three steps should occur: 1) Set the Control Word: Output B6h to port 43h. (This selects counter 2 [bits 7 & 6], establishes the counter value as 16-bit LSB then MSB order [bits 5 & 4], sets timer Mode 3 [squarewave] [bits 3-1], and sets the counter to count in binary vs. BCD [bit 0]). 2) Load the desired countdown value to port 42h, least-significant byte followed by most-significant byte. 3) Enable the speaker by setting bits 1 & 0 at port 61h. WITHOUT CHANGING THE OTHER SIX BITS AT THIS PORT ADDRESS. (Input port 61h, OR the value with 3, then Output back to 61h).

The output frequency will be 1.193182 MHz divided by the countdown value loaded into the timer's register. To get an output freq of about 10 KHz, use a countdown of 119 [decimal].

If you want interrupts to occur at this rate, you could use a special purpose card which has a pigtail to interface with the speaker connector, and use that signal to pulse another one of the IRQ lines available on the peripheral connector. You would have to install your own interrupt handling routine to service that IRQ. In this event, you would probably want to use timer Mode 2 [Control Word bits 2 & 1 set to 1 & 0, respectively].

Another way to change the interrupt rate would be to change the setting of the timer 0 countdown value, but this is involved. You would probably want to install your own IRGO interrupt handler to service each interrupt, calling the default IRGO handler at the standard "timer tick" rate, about every 54 milliseconds. I'd suggest using assembly language, to keep your IRGO handler code as tight as possible.

Larry Mistretta  
Sunnyvale, CA  
Continued on next page

## Go Wireless With Our Modules

### SILRX/TXM

SILRX — \$26.00 ea.  
TXM — \$15.50 ea.

The TXM and SILRX modules are a transmitter and receiver pair which can achieve a one-way radio data link-up to a distance of 200m over open ground.

Both units are supplied in space-saving single-in-line packages and offer SAW controlled, wide band FM transmission/reception.

The modules are particularly suited to battery-powered, portable applications where low power and small size are critical design criteria.



### TX2/RX2

TX2 — \$19.50 ea.  
RX2 — \$38.50 ea.

The TX2 and RX2 radio transmitter and receiver pair enable the simple implementation of a data link at up to 40kbit/s at distances up to 75m in-building and 300m open ground. Both modules combine full screening with extensive internal filtering to ensure EMC compliance by minimizing spurious radiations and susceptibilities. The TX2 and RX2 modules will suit one-to-one and multinode wireless links in applications including car and building security, EPOS and inventory tracking, remote industrial process monitoring, and computer networking.

Because of their small size and low power requirements, both modules are ideal for use in portable, battery-powered applications such as hand-held terminals.



900 MHz

AVAILABLE JAN '99

### RPC

RPC — \$99.00 ea.

The RPC module is an intelligent transceiver which enables a radio network link to be simply implemented between a number of digital devices. The module combines an RF circuit with processor-intensive low-level packet formatting and recovery functionality, requiring only a simple antenna and 5V supply to operate with a microcontroller or a PC.



### BiM

BiM — \$69.00 ea.

The BiM module integrates a low-power UHF FM transmitter and matching superhet receiver together with data recovery and TX/RX change over circuits to provide a

low-cost solution to implementing a bi-directional short-range radio data link.



## Lemos International Co., Inc.

65 Southbridge Street, Auburn, MA 01501

Phone (508) 798-5004 ♦ Fax (508) 798-4782

www.lemosint.com ♦ lemosint@ma.ultranet.com

All products available in either 418 or 433 MHz

Write in 134 on Reader Service Card.

## Celebrating our 16th Year Of Service !!

### COLLIMATING LENS

This economical collimating lens assembly consists of a black anodized aluminum barrel that acts as a heat sink, and a glass lens with a focal point of 7.5mm. Designed to fit standard 9mm laser diodes. Simply place diode in the lens assembly, adjust beam to desired focus, then set with adhesive.

STOCK	1-7	10-21	25-
LSLENS Lens Assembly	24.99	23.74	21.37

### DIODE/TRANSISTOR TESTER KIT

This dynamic tester allows checking of transistors and diodes in circuit. Identifies NPN or PNP transistors. Checks all types, small or large power. Identifies anode or cathode of diodes.

STOCK	1-7	10-21	25-
DT100K	24.99	23.74	21.37

### ANTI-STATIC FOAM CLEANER

A thick, foaming cleaner for use in static sensitive applications. Safe for plastics and fiberglass. Use on computer cases and all office equipment. Also cleans soft fabrics. 5 oz. aerosol can.

STOCK	1-7	10-21	25-
SB1102	1.99	1.89	1.70

### EPROMS

	1-24	25-39	100-
2716	2.99	2.84	2.56
2732	4.49	4.27	3.84
2732A-20	5.39	5.12	4.61
2764-20	5.39	5.12	4.61
2764-25	4.49	4.27	3.84
2764A-20	3.49	3.32	2.99
2764A-25	2.99	2.84	2.56
27C64-15	2.99	2.84	2.56
27256-15	4.79	4.55	4.10
27C256-15	2.99	2.84	2.56
27512-25	3.09	2.94	2.65
27C512-25	2.99	2.84	2.56
27C010-15	3.79	3.60	3.24
27C020-15	4.49	4.27	3.84
27C040-12	6.29	5.98	5.38
27C080-12	12.99	12.34	11.11

### 7400 SERIES I.C.'s

	1-24	25-39	100-
7400	.29	.28	.25
7402	.19	.18	.16
7404	.29	.28	.25
7406	.27	.26	.23
7407	.33	.31	.28
7408	.33	.31	.28
7410	.19	.18	.16
7411	.55	.52	.47
7414	.27	.26	.23
7420	.24	.23	.21
7432	.33	.31	.28
7447	.89	.85	.77
7473	.79	.75	.68
7474	.33	.31	.28

### FM MICROPHONE KIT

Transmit your voice on any FM radio. Range up to 1000'. Case included.

STOCK	1-7	10-21	25-
K30	11.99	11.39	10.25

### What Do We Have ?

- I.C.'s
- Capacitors
- Oscillators
- Connectors
- Crystals
- Trimpots
- Diodes
- Kits
- Tools
- Vias
- Laser Diodes
- LED's
- Vises
- Transistors
- Resistors
- And more!

### GADGETEER'S GOLDINE

This exciting collection of electronic projects features experiments ranging from magnetic levitation and lasers to high-tech surveillance and digital communications.

STOCK	1-7	10-21	25-
TB3360	21.99	20.89	18.80

- Order Line — (800) 824-3432 • International — (724) 495-1230 • Fax Orders — (724) 495-7882
- Technical Support — (724) 495-1231 • No Minimum Order — (Orders under \$20 subject to \$ 5 charge) • UPS 3 day, Blue, Red, & Fed. Ex. Shipping Available (Call for charges) • PA Res. Add 7 % Sales Tax • Open Mon-Fri 9:00 AM - 5:00 PM (EST) • Corporate Accounts / Quantity Discounts Available • We accept M/C, VISA, Discover & American Express with no surcharge • Call For FREE Catalog (\$2.00 Outside U.S.)
- We Carry A Complete Line Of Electronic Components • Email - unielect@aol.com

FREE SHIPPING!!  
on pre-paid orders

Unicom Electronics  
1142 State Route 18  
Aliquippa, PA 15001

# TECH FORUM

## ANSWERS TO #129815 - DEC. 1998

The 8253 timer is quite useful, but hard to program unless you know some computer architecture or have had some digital electronics experience. I'll briefly go over how the 8253 is used in a PC before going on to how to program it.

The PC real-time clock runs at 1.19318 million Hz. However, to fit the value in a 16-bit number, the 8253 is used to "step down" the counter to a 16-bit value (max of 65535). The result is the 18.2 Hz rate, or approx. 55 ms interval.

The 8253 has four "channels," but 0, 1, and 3 are used by the system (real-time clock, memory refresh, and system timeout detection, respectively), so only channel 2 is available for use, and that is usually hooked up to the speaker.

The 8253 actually has SIX different modes of operation, but for PC purposes, "mode 3" is sufficient. In "mode 3," the "latch register" is loaded with a number, which counts DOWN to 0 on every clock pulse. When the counter hits 0, the output turns on for one clock cycle, and the counter reloads the original value and starts over.

To control the timer, you need to send a one-byte command to the "command register", which is on the PC at port 0043h. Then you load the latch register with the value you selected. Once the timer gets the second value, the countdown starts.

The command register is programmed as follows:

```
bit 0: 0 if binary, 1 if BCD
1-3: timer mode, 0-5 <<< use 3
4-5: operation type
00 = move counter into latch
01 = read/write high byte only
10 = read/write low byte only
11 = read/write high byte, then low
byte <<<< use this 6-7: which channel
to set [0-3] <<<< use 2
```

Channel 2's latch is at port 0042h. To set the timer to operate at 0.1 ms, you need to determine the latch

counter value by dividing 1190000 by the frequency. 0.1 ms is 10000 Hz, so the value you need is 119. Let's declare that ... unsigned latchval=199; you will also need to turn off the link between the timer and the speaker. You do that by turning off the last two bits of command port B at 0061h, so you need `outp[0x61,inp[0x61] & 252]; // turn off sound.`

Then we initialize the command register. The bits we need are 10110110b, or 182. `outp[0x43,182]; // init cmd register`

To output 199 in two parts, we'll separate the lower and upper by using AND \$FF and shift right eight times. As 199 is less than 2^8 you can use only the lower byte, but I wrote it this way to be "compatible."

```
outp[0x42,latchval & 0xFF]; //
send low byte value
outp[0x42,latchval >> 8]; // send
high byte value
And you are done!
```

Don't forget the reset the timer when you're done ... `1190000/18.2 = 65385 (approx).`

To relink channel 2 to speaker, reinitialize with: `outp[0x61,inp[0x61]|3];`

**Kasey Chang**  
San Francisco, CA

## ANSWERS TO #129815 - DEC. 1998

Unless you modify the PC hardware, the only timer that can generate an interrupt is timer 0. The XT BIOS sets up timer 0 with this code:

```
mov al,36h ;mode 3, lsb then msb,
squarewave
out 43h,al
mov ax,0000 ;preset = 65536
out 40h,al
mov al,ah ;now send msb
out 40h,al
```

Note that it takes three output instructions to complete this preset operation, the first is the mode control byte and then this is followed by the two bytes you have just told the 8253 that you were going to send,

first the low byte of the preset value, and then the high byte of the preset value. You cannot just output a new preset value, you must go through the full fandango. The value 0000 is effectively 65,536 because it loads a 16-bit counter that first counts down and then looks to see where it is.

The interrupt rate is `int rate = 1,193,180/preset` so with `preset = 65536` we get 18,206 interrupts per second.

You have asked for an interrupt every 100 microseconds, or 10,000 interrupts per second. The preset required would then be `preset = 1,193,180/int rate` or = 119.

You should have set INT 1Ch at location 0000:0070 to point to your own interrupt handler; when you quit you should restore that vector to its original value.

The time-of-day and the floppy disk motor timeout will be messed up while you have timer 0 running at your own rate, so you should also restore the original 8253 preset value.

Also there's more. Whether you can actually get in and out of 10,000 interrupts per second and still do anything else, is a question you may explore the hard way.

That's the theory. For a somewhat more thorough discussion you might want to consult Michael Abrash: *Zen of Assembly Language, Volume 1, Knowledge*. Foresman and Company, 1990. Of course it's out of print, so you'll have to look around.

For discussion of the hardware see Lewis C. Eggebrecht: *Interfacing to the IBM PC Sams*, 1990. Sameo.

As a practical matter, it may be easier in the long run to simply install an expansion board with a separate 8253 timer set up to generate a completely separate interrupt that stays clear of the basic PC hardware and BIOS operations. This would appear to be particularly true where you are interfacing "various sensors/transducers..."

For example, **Circuit Specialists 1-800-528-1417** has a \$46.00 I/O

Prototype Development Card that comes in kit form and includes the 8253, 8255, and address decode circuits already built in. This is the kind of project that may cause you to learn why Steve Ciarcia once said, "solder is my favorite language."

**Jack Dennon**  
Warrenton, OR

## ANSWERS TO #129815 - DEC. 1998

The simple answer is do not change the timer interrupt rate. There is a lot of black magic that happens with timer interrupts, and you need to understand the impact that any changes have.

Furthermore, it is generally a bad idea to issue thousands of interrupts per second.

It takes time to service interrupts, and a lot of interrupts will bring a system to its knees.

For fast data rates, you should use buffered transfers and DMA. Keep the interrupts below 1,000 per second.

Under MS/DOS, you can change the interrupt rate, but you risk screwing up the operating system or a device driver. Device drivers will often hook onto the timer interrupt chain so they can tell if an I/O device is hung.

A driver, knowing the timer interrupts (ticks) occur about every 55ms, might decide that a device is hung if an operation takes longer than four ticks (about 200ms). Changing the tick time to 0.1ms will confuse the device driver, because it will assume the I/O hung after four fast ticks (0.4ms).

Programmers who increase the timer rate need to work around this problem, so they write an interrupt handler that fields the fast ticks; every 55ms that handler chains to other timer interrupt routines. Even this practice is risky because any program that hooks into the timer interrupt chain later gets the fast tick rate.

Under Windows, what happens is mysterious. Your `outportb()` subroutine calls manipulate a virtual timer chip (not the real one on the motherboard, but a software simulation), and then Windows may or may not change the settings on the real chip.

Under Windows you must also take special steps to page lock your interrupt routine or callback, and that requires a fair bit of Windows knowledge.

Using the Windows APIs can be even more disconcerting. Windows allows you to schedule a timer message every millisecond — but it doesn't promise to give you every one of them! Ask for 1ms messages and you may get one only every 55ms — and even then you may not get one if the system is busy doing something else.

Leave the timer interrupt alone and use the serial port for collecting the samples. Use the operating system's drivers for accessing the serial port so you don't have to write the interrupt routine. The operating system drivers will make full use of hardware FIFOs, system buffers, and ring 0 interrupt routines.

**Gerald Roylance**  
Mountain View, CA

## WE'LL MEET OR BEAT ANY COMPETITOR'S PRICE!

ALL PRODUCTS  
1 Year Warranty



**BRAND NEW**  
Wavemaster 99 Channel

• Sleep Timer • Std./HRC Switch • Parental Control

AS LOW AS \$45<sup>00</sup> COMPLETE  
CHECK US OUT!



Formerly JES, Inc.

**BEST PRICES!**

**FAST SERVICE**

**SAME DAY SHIPPING**



**Panasonic I45 & I75's**

WE STOCK  
EVERY MODEL USED.

CALL NOW FOR  
WHOLESALE PRICING

TOLL FREE: 800-322-9690



FAX: 516-246-5634

## Fixed Frequency or Workstation Monitor?

Now, use **ANY** monitor on your PC with the new **Avalanche 3D** from Worldwyde.com!



- Easiest installation of any card in its class!
- Supports all resolutions and frequencies:
  - from 320 x 200 to 1280 x 1024
  - 15KHz to 120KHz
- Available in PCI or AGP

To order, call Worldwyde.com  
**1-248-473-1182**  
 21365 Randall Street • Farmington Hills, MI 48338  
 Visit us on the web at [www.worldwyde.com](http://www.worldwyde.com)



Dealer/Quantity Discounts Available

Write in 93 on Reader Service Card.

## Events CALENDAR

Continued from page 27

Conv., William Tittle KABLAY, 513-661-1861.  
 E-Mail: [gldivconvention@juno.com](mailto:gldivconvention@juno.com)

### FEBRUARY 28

**NY - CHEEKTOGAWA** - Hamfest, Lancaster ARC, Luke Caliano N2GDJ, 716-634-4667.  
 E-Mail: [licalliano@freeweb.com](mailto:licalliano@freeweb.com) Web: <http://hamgate1.sunysie.edu/~larc/greaterbuffalointerhamf>

**NY - MELVILLE** - Hamfest, Radio Central ARC, JoAnn Colletti N2IME, 516-399-1877.  
 E-Mail: [wo2n@li.net](mailto:wo2n@li.net)

**OH - CIRCLEVILLE** - Hamfest, Teays ARC, Roy Ulko KG8EK, 740-477-8310.  
 E-Mail: [royulko@scioto.net](mailto:royulko@scioto.net)

**OH - CUYAHOGA FALLS** - Hamfest, Emidio & Sons Party Center, 48 E. Bath Rd. 8am-2pm. Cuyahoga Falls ARC, Carl Hervol N8JLQ, 330-497-7047. E-Mail: [carlh@pop.mex.com](mailto:carlh@pop.mex.com)  
 Web: <http://www.cfarc.org/hamfest.htm>

**PA - CASTLE SHANNON** - Hamfest, VFD Memorial Hall, Library Rd. (Rt. 88), 8am-3pm. Talk-in: 146.955-N3RNX repeater. N3SH ARC, Steve Lane W3SRL, 412-341-1043.  
 E-Mail: [slane@adelphia.net](mailto:slane@adelphia.net)

Web: <http://www.hky.com/~sanfordb/index.htm>  
**VA - ANNANDALE** - Hamfest, Vienna Wireless Society, Mike Toia K3MT, 703-757-5021.  
 E-Mail: [k3mt@erols.com](mailto:k3mt@erols.com)

Web: <http://www.erols.com/k3mt/vws>  
**WV - FAYETTEVILLE** - Hamfest, Plateau ARA, Juddie David Burgess KC8CON. E-Mail: [kc8con@usa.net](mailto:kc8con@usa.net) Web: <http://www.geocities.com/CapeCanaveral/Launchpad/4842>

### MARCH 1999

#### MARCH 5-6-7

**NE - NORFOLK** - State Convention. Fred Wiebelhaus N0VLX, 402-379-1929.  
 E-Mail: [fdwiebel@sufia.net](mailto:fdwiebel@sufia.net) Web: <http://members.aol.com/davidn0xnb/evarc.html>

#### MARCH 6

**CA - SANTEE** - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in, 619-561-0052.

**TN - KNOXVILLE** - Hamfest, Kerbel Temple, 315 Mimosa Ave. 8am-4pm. Talk-in: 144.83/145.43 or 146.52 simplex. Kerbel Temple, Paul Baird K3PB, 423-986-9962

#### MARCH 6-7

**FL - NEW PORT RICHEY** - Hamfest, Fred K. Marchman Technical Educational Center. Sat: 8am-5pm, Sun: 8am-3pm. Talk-in: 146.670 or 145.330. Gulf Coast ARC, Rick Brown KF4GX5, 813-842-2127. E-Mail: [richar@gte.net](mailto:richar@gte.net)

#### MARCH 7

**NY - LINDENHURST** - Hamfest, Great South Bay ARC & Suffolk County RC, 516-422-9594.  
 E-Mail: [ka2d@li.net](mailto:ka2d@li.net) Web: <http://www.gsbarc.org>

**WI - WAUKESHA** - Swapmeet, Waukesha County Expo Center, 8am-2pm. VE Exams. Talk-in: 146.82 PL 127.3. SEWFARS, John Breecher N9NWN, 414-835-7035

#### MARCH 13

**AZ - SCOTTSDALE** - Hamfest, Scottsdale ARC, Roger Cahoon KB7ZWI, 602-948-3548

**CA - FONTANA** - Inland Empire ARC Amateur Radio & Electronics Swapmeet. A B Miller High School, Bill 909-822-4138 eves

**FL - EAST ENGLEWOOD** - Hamfest, Englewood

ARS, J.R. House K9HJY, 941-475-3005. Web: <http://www.flnet.com/~crosby/ears/index.html>  
**FL - SEBRING** - Hamfest, Highlands County ARC, Phyllis Dibble KD4CQG, 941-465-8176.  
 E-Mail: [dibble@strato.net](mailto:dibble@strato.net)

Web: <http://www.strato.net/~hamradio>  
**KY - CAVE CITY** - Hamfest, Mammoth Cave ARC, Larry Brumett KN4IV, 502-651-2363.  
 E-Mail: [lbrumett@glasgow-ky.com](mailto:lbrumett@glasgow-ky.com)

Web: <http://www.scrtc.blue.net/mcsrc>  
**MO - KANSAS CITY** - Hamfest, Ararat AR Shrine Club, Steve Dowdy WJ0I, 816-941-3392.  
 E-Mail: [sdowdy@qnl.com](mailto:sdowdy@qnl.com)

**ND - WEST FARGO** - Hamfest, Red River Radio Amateurs, Mark Kerkvliet KG0FR, 701-282-4716.  
 E-Mail: [mbkerk@worldnet.att.net](mailto:mbkerk@worldnet.att.net)  
 Web: <http://www.rrra.org/>

**WA - PUWALLUP** - Hamfest, Mike & Key ARC, Michael Dinkelman N7WA, 253-631-3756 or 425-867-4797. E-Mail: [mwdink@eskimo.com](mailto:mwdink@eskimo.com)

#### MARCH 13-14

**NC - CHARLOTTE** - Hamfest & Computerfair, Charlotte Merchandise Mart, 2500 E. Independence Blvd. Mecklenburg ARC, Tim Slay WO4G, 704-382-3234 (W) or 704-948-6283 (H).  
 E-Mail: [wo4g@w4bfb.org](mailto:wo4g@w4bfb.org)  
 Web: <http://www.w4bfb.org/hamfest.html>

**LA - RAYNE** - Hamfest, Acadiana ARA, Nolan Griffith K5ARH, 318-989-9039.  
 E-Mail: [k5dpg@aisp.net](mailto:k5dpg@aisp.net)

Web: <http://www.acadiana.net/w5ddl/>

#### MARCH 14

**IN - INDIANAPOLIS** - Hamfest, Morgan County Repeater Assn., Dennis Bauernfiend WB9ZNZ, 317-996-3782. E-Mail: [dennis.bauernfiend@dfas.mil](mailto:dennis.bauernfiend@dfas.mil) Web: <http://www.eb1.com/mcra>

**IL - STERLING** - Hamfest, High School Fieldhouse, 1608 4th Ave. Talk-in: 146.25/146.85 W9MEP. Sterling-Rock Falls ARC, Lloyd Sherman KB9APW, 815-336-2434.  
 E-Mail: [lsherman@essexl.com](mailto:lsherman@essexl.com)

**OH - CONNEAUT** - Hamfest, Conneaut ARC, Jack Marttila KA8TQU, 440-593-3353

#### MARCH 19-20

**FL - FT. WALTON BEACH** - Hamfest, Playground ARC, Clyde Gowdy KE4FLC, 850-244-0624.  
 E-Mail: [parcfest@aol.com](mailto:parcfest@aol.com)

**ME - LEWISTON** - ME State Convention. Androscoggin ARC, Ivan Lazure N1OXA, 207-784-0350. E-Mail: [ilazure@gwi.net](mailto:ilazure@gwi.net)

**OK - TULSA** - OK State Convention. Green Country Hamfest Assn., Merlin Griffin WB5OSM, 918-622-2277. E-Mail: [info@GreenCountryHamfest.org](mailto:info@GreenCountryHamfest.org) Web: <http://www.GreenCountryHamfest.org>

#### MARCH 20

**CA - SANTEE** - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in, 619-561-0052

**FL - STUART** - Hamfest, Martin County ARA, David Millard KE4AMW, 561-288-7100

**MI - MARSHALL** - Hamfest, Southern Michigan ARS & Marshall HS Photo Electronics Club, Wes Chaney N8BDM, 616-979-3433.  
 E-Mail: [n8bdm@voyager.net](mailto:n8bdm@voyager.net)

#### MARCH 20-21


**TX - MIDLAND** - Hamfest, Midland ARC, Beverly Harwood KC5BNT, 915-686-1841.  
 E-Mail: [shamrock@apex2000.net](mailto:shamrock@apex2000.net)  
 Web: <http://www.lxnet/edge/midswap.htm>

#### MARCH 21

**NC - KINSTON** - Down East Hamfest, Lenoir

Continued on page 77
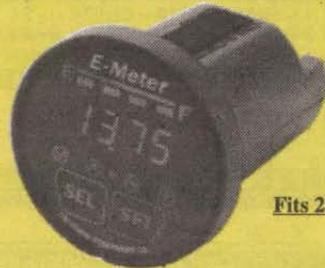
## Y2K PLANNING? USING BATTERIES? GET AN E-METER™



From \$200

OEM's: Call for free applications assistance.

Fits 2" hole

Up to 1000 Amps @500 Volts!

Here's why *every* Y2K battery bank needs an **E-Meter** - the world's most popular DC energy monitor: The multi-color bar graph shows battery status at a glance. The bright digital display reports Volts, Amps, Amp-hours, Time Remaining, - even Kilowatt-hours. Reports historical information including battery Charge Efficiency, number of discharge cycles, deepest depth of discharge and average depth of discharge. The optional Low Battery contact can optimize your generator run times for charging and RS232 output is available for remote sites.

Don't be afraid of Y2K - be ready with an E-Meter!

## Cruising Equipment

5245 Shilshole Ave. NW, Seattle, WA 98107  
 (206) 782-8100 Fax: (206) 782-4336  
<http://www.cruisingequip.com>

Write in 94 on Reader Service Card.

## ANA Instruments

Phone: 1-800-944-0495

Fax: (540) 775-9638

E-Mail: [anainstr@crosslink.net](mailto:anainstr@crosslink.net)

### Specials

- HP 141T CRTs, New in Box .....\$195.00
- HP 8657A Signal Generator .....\$4,500.00  
 100 KHz-1040 MHz
- HP 8640B Signal Generator .....\$2,100.00  
 Opt. 001, 002, 003
- Gigatronics 600 .01-8 GHz .....\$2,400.00
- HP 86222A .01-2.4 GHz .....\$1,100.00
- HP 8903B Audio Analyzer .....\$2,700.00
- HP 8901B Modulation Analyzer.....\$3,700.00
- HP 8902A Measuring Receiver .....\$17,500.00
- HP 436A Power Meter w/Cable.....\$1,400.00
- Tek 492 Opt 1,2,3 Spec. Analyzer ..\$6,200.00
- Sanders 5440C Noise Figure Meter...\$400.00  
 (new)


## Wanted

RF & Microwave Test and Measurement Equipment & Components

Electronic Test Equipment Bought and Sold  
 Visa and MasterCard Accepted
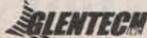
## A/D CONVERTERS with SERIAL OUTPUT

Tiny (1.75"x1.41") fully assembled and tested printed circuit board includes two 8-bit A/D converters and one digital input. Up to 16 units addressable (DIP switch setting) totalling 32 converters on a single serial port. Output is ASCII encoded bit count (0 to 255) at 2400 BPS via RJ-11 interface. Fully programmed PIC16C71 installed in IC socket. Sample software in BASIC included. Requires 8-28Vdc At 1-2mA.  
\*\$49.95\* Optional DC adapter \$19.95.  
Add \$5.00 shipping.



Tele: 847-891-2584  
Fax: 847-891-2587  
www.glentech-rf.com

## SURPLUS SALE

### 1,000,000 WALL TRANSFORMERS



3VDC/100MA .... CX099 .... \$0.75  
6VDC/100MA .... CS039 .... \$1.45  
9VDC/100MA .... CR314 .... \$1.45  
12VDC/200MA .... CS033 .... \$0.99  
13.5VAC/400MA.. CR574 .... \$1.29  
24VDC/500MA .... CR174 .... \$3.40  
Min 1000/type -- Call for other types

## SURPLUS TRADERS

PO Box 276,  
Alburt, VT 05440  
Tel: (01) 514-739-9328  
Fax: (01) 514-345-8303  
http://www.73.com/vt

## FREE CATALOG!

## Serial Problems???

Use your PC compatible desktop or laptop computer to debug serial communications problems with Serial, our test tool for serial communications.

Serial works with the standard data rates and asynchronous serial formats commonly found in modern office and industrial environments. Suitable for development, service work, and end-user problem diagnosis.

- Easy to Use
- Menu and Windows
- Highly Configurable
- Contextual Help
- Autobaud Detect
- Time Stamping
- Custom font editor for EGA/VGA Screens
- Saves Configurations
- Extensive Manual
- Block transmit ability
- CRC/LRC generation

Serial, with manual ..... \$99.95  
Cable for full duplex monitoring ..... \$49.95  
For Orders and Inquiries Call: 1-800-980-9806  
Allison Technology Corporation  
2006 Finney Valley Rd., Rosenberg, TX 77471  
281-239-8500 • 281-239-8006 FAX

## GET IT UP BEFORE WINTER!

MARCONI ANTENNA 700W 50 Ω  
THE BEST "LITTLE" LOW BAND ANTENNA

**EASY TO INSTALL.**

— 160M — 130' OVERALL \$63.95 PP  
— 80M — 67' OVERALL \$46.95 PP

**THE OCR.** AN OPTICALLY COUPLED REGEN. IS AN EXCEPTIONAL REGEN RECEIVER KIT. EASY TO ASSEMBLE.  
(SEE QST JUNE 98) ..... \$ 91.95 PP

**SEND FOR FREE CATALOG:**  
• SMART BATTERY CONTROLLER KITS ..... \$23.45 PP  
• CODE PRACTICE OSCILLATOR ..... \$23.45 PP  
• CURTIS KEYSER KIT ..... \$46.95 PP

1-800 JADE PROD (523-3776)  
www.jadeprod.com/  
email: jadeprod@jadeprod.com  
JADE PRODUCTS INC E HAMPSTEAD NH 03826-0388

## PROGRAMMERS

ADVANTECH EETOOLS NEEDNAME DATA I/O ICE TECHNOLOGY HIO SYSTEM GENERAL CHROMA MODULAR CIRCUIT TECHNOLOGY XELTEK



PROMAX EMP-20 MEGAMAX MEGAMAX4 SIMM/SIP TESTER EMUPA  
CALL ADVANTECH LABTOOL 599 EETOOLS SIMMAX  
629 ICE TECH MEGROV 795 CHROMA SIMM/SIP  
650 EETOOLS ALLMAX + 359 MOD-MCT-EMUPAR  
409 EETOOLS MEGAMAX 279 MOD-MCT-EMUPR  
509 EETOOLS MEGAMAX4 49 EPROM 1G TO 512K  
369 XELTEK SUPERPRO II 69 EPROM 1G TO 1MEG  
409 XELTEK SUPERPRO II P 99 EPROM 4G TO 1MEG  
249 XELTEK SUPERPRO L 199 EPROM 16G TO 1 MEG  
165 XELTEK ROMMASTER II 89 EPROM 1G TO 8MEG  
479 MOD-MCT-EMUPA 129 EPROM 4G TO 8MEG  
739 STAG ORBIT-32 250 EPROM 8G TO 8MEG



LABTOOLAS MICROMASTER SUPERPRO ALLMAX PLUS ROMMASTER2  
**General Device Instruments**  
Sales 916-393-1655 Fax 916-392-4949  
Web www.generaldevice.com E-Mail idovoice@best.com

## BATTERY — YUASA



Sealed Lead-Acid/Gel-Cell  
12V: 7AH \$19, 2.3/4AH \$16  
18AH \$39, 1.2AH \$13  
6V: 4AH \$9, 10AH \$13

Quantity Discounts Available  
Call for other models

## Aventrade

4518 Temple City Blvd.  
Temple City, CA 91780  
Tel. 626-286-0118 Fax 626-287-9618  
E-Mail: aventrade@aol.com

## PCB's in Minutes From LaserPrint!\*


8 1/2" x 11" Sheets \* Or Photocopy Use household iron to apply.

**PnP BLUE** or **PnP WET**  
For High Precision Professional PCB Layouts

1. LaserPrint
  2. Iron-On
  3. Peel-Off
  4. Etch
- Adds an Extra Layer of Resist for Super Fine Lines on Std. Clad Bds
- 205h \$30/405h \$50/1005h \$100/2005h \$100 (No Mix)  
Sample Pack 5 Shts Blue + 5 Shts Wet \$20  
VISA/MC/PO/CH/MO \$4 S&H — 2nd Day Mail  
Techniks Inc. P.O. Box 463 Ringoes NJ 08551  
(908) 788-8249  
100% Money Back Guarantee-Dealer Inquiries Invited
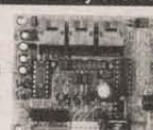
## Convert RS-232 to RS-485 or TTL/CMOS for Only \$49.00

Communicate up to 4,000 feet, at up to 1 MEGA-BPS, full or half duplex, up to 32 units on one serial link, with 31 jumper options for flexible configuration, LED indicators.



## COMMUNICATIONS CONVERTER

- FULL SCHEMATIC AND DOCUMENTATION
- FULL FAMILY OF MODULAR DESIGNS
- RS-485/RS-422 REMOTE I/O MODULE KITS
- NETWORK SOFTWARE AND SOURCE CODE
- AUTOMATIC OR RTS UNITS AVAILABLE
- RJ-11/12 CONNECTORS OR TERMINAL STRIP
- TURN YOUR PC INTO A DISTRIBUTED DATA ACQUISITION AND CONTROL SYSTEM

## R.E. SMITH

(513) 874-4796  
4311 TYLERSVILLE RD. ■ HAMILTON, OHIO 45011  
www.rs485.com

## TV 85 PJ & TV 86 CABLE CONVERTERS VOLUME & NON-VOLUME CONTROL

SALES/SERVICE  
VOICE 1-800-473-0506  
FAX 1-800-488-0525

FOSS  
WAREHOUSE  
DISTRIBUTORS  
285 Schenck St.  
N. Tonawanda, NY 14120  
www.fossw.com

**PCBS PER SQIN** **9¢**  
\$100.00 SETUP  
WE SPECIALIZE IN SINGLE SIDED, 1 OZ, PC75

**PCB LAYOUT** **59¢**  
PER COMPONENT PIN \$100.00 MINIMUM

**ENGINEERING DIAGRAMS** **39¢**  
PER COMPONENT PIN \$100.00 MINIMUM

V&V MACH. & EQUIP., INC. (HOUSTON, TX OFFICE)  
PH (281) 397-8101 FAX (281) 397-6220  
MARKETING TECH. S.A. (MEXICO/PLANT)  
PH 011 (525) 361-3351 FAX 011 (525) 361-5996

## Peltier Junction

While They Last!  
1 3/16" x 1 3/16" cooling area  
Quantity Pricing Available

WITH HEATSINK AND LEADS  
**\$10 EACH**  
OR THREE FOR \$25

**SHREVE SYSTEMS**  
**318-424-9777**  
Ask for Jake  
HTTP://WWW.SHREVEYSTEMS.COM

## RGB Color Composite Displays ON SALE!



\*refurbished with 90-day warranty  
**ONLY \$79!!**  
Excellent for studio, lab or surveillance applications  
640x480 resolution, RCA-style connectors

Returns subject to a 15% restocking fee. Prices are subject to change without notice.  
WE ACCEPT VISA, MASTERCARD, AMEX, DISCOVER  
HTTP://WWW.SHREVEYSTEMS.COM

## Telecom Hardware/Software Developers

STOP using your phone lines to test and demonstrate your telecom devices. Our affordable telephone line simulators offer authentic USA dial tone, busy signals, ringing, and exceptional speech quality.



**RING-IT! TELCO SIMULATOR**  
• Single Line (two RJ-11 Jacks)  
• LED Display  
• DTMF Operation  
• Automatic Ring-up Mode  
• \$325 (\$149 kit available)

**PARTY-LINE TELCO SIMULATOR**  
• Six Extensions  
• Caller-ID (Name/Nbr)  
• Distinctive Ringing  
• \$425 (\$199.95 kit avail)

Digital Products  
COMPANY  
134 Windstar Circle  
Folsom, CA 95630 USA  
Tel: 916-985-7219  
Fax: 916-985-8460  
http://www.digitalproductsco.com

## ADAPT-11 & ADAPT-12

Low-cost modules for HC11 & HC12 just into solderless breadboards

- Evaluate your idea instantly!
- Breadboard it, for quick hardware changes
- Program it in-circuit, for quick software changes
- Debug your application—no the basics!

ADAPT-11 Modules feature three 8-bit I/O ports, SPI, SCI, eight 8-bit analog input channels, hardware timers/counters, & interrupts. All Starter Packages include PC serial download cable, documentation, & disk of utilities & examples. Bundle ImageCrash C for Windows (OC011) with any Starter Package for an additional US\$120.00 + \$5 S&H.  
HC11 Starter Package Configurations:  
AD11-SP 2K EE256 bytes RAM US\$ 74.95 + \$5 S&H  
AD11-C75-SP 8K EE512 bytes RAM US\$ 97.00 + \$5 S&H  
AD11-C750X-SP 8K EE32K bytes RAM US\$120.00 + \$5 S&H  
AD11-SP84K ADAPT-11 w/ 32K EE/32K RAM memory expansion card & dual slot adapter (2 I/O ports total) US\$123.00 + \$5 S&H  
ADAPT-12 features 68HC12A4, 4K EE, 1K RAM, 85 I/O lines, eight high speed 8-bit analog inputs, memory expansion connector, RS232 & RS485, convenient firmware bootloader, plus support for all BDM pods. All this on a compact 2.25" x 3.25" board. Starter Package (AD012-SP) US\$99 + \$5 S&H. Add US\$125 for ICC12MNH.  
AVAILABLE SOON! ADAPT-9-12 features 68HC912B32 (32K Flash, 768 EE, 1K RAM, 56 I/O lines, 8 chan. analog), RS232 and RS485. All this and more on a compact 2.25" x 3.25" board! Starter Package (AD012-SP) US\$99 + \$5 S&H. Add US\$125 for ICC12MNH.

TECHNOLOGICAL ARTS  
voice/fax: (416) 963-8996  
www.interlog.com/techart

## HIGH PERFORMANCE ULTRA-MINIATURE PINHOLE LENS CAMERA W/ CASE

The "NEW" MiniCam1 (in a durable, metal case) is the smallest pinhole camera in the industry! It's actually smaller than the board cameras currently on the market. Comes w/ mounting bracket & power supply for easy installation • High resolution—more than 420 lines, 0.1 lux • Ultra miniature - lightweight & measures only 29mm x 29mm x 12mm. • Pinhole lens offers sharp image w/highened sensitivity • Can be easily mounted behind a 1/8" hole for any custom/cover applications. ONLY...\$79.00  
Surveillance Catalog \$5.00

**SPY OUTLET**  
2468 Niagara Falls Blvd • Tonawanda NY 14150  
(716) 695-8660 Fax 695-7380 www.spyoutlet.com

## VIDEO CHARACTER OVERLAY GENERATOR

New BOB-II superimposes up to 308 characters on standard video or generates video. 30-pin SIMM design, RS-232 interface, easy to use for:

- Video Inspection - NDT
- Home Automation Display
- ATV - CCTV Security - CATV
- Remotely Piloted Vehicles
- Gaming - Racing - Sports
- Process/Experiment Monitor
- Robotics - Electronic Signs

Single units only \$79.95

## DECADEN ENGINEERING

5504 ValView Dr. SE, Turner, OR 97392  
Tel: 503.743.3194 - Fax: 503.743.2095  
mikeh@decadenet.com - www.decadenet.com

## RESISTORS

SPECIALS FOR ENGINEERS, TECHNICIANS, HOBBYISTS, SCHOOLS, ETC.

5,000 1/4W 1-5% metal & carbon film. 50 each of 100 standard values (our selection of values) \$45.00 (less than 1¢ each).

10,000 1/4W 1-5% metal & carbon film. 50 each of 200 values (our selection of values) \$95.00 (less than 1¢ each).

OR: You select the values and the quantity of each. Minimum of each value 50 pieces. Minimum order \$50.00. 5% - 1¢ each/1-2% - 2¢ each.

Shipping and tax included. Each value clearly marked for ID. Over 500 values available from a stock of millions. Groups put your order together and then split the cost.

HYATT ELECTRONIC SURPLUS

371 N. JOHNSON AVE., EL CAJON, CA 92020  
TEL: (619) 444-2434 FAX: (619) 444-1987

## ATTENTION DEALERS

### WHOLESALE ONLY!

• ANY CABLE MFRG CONVERTERS & ACC

• BEST PRICING & SERVICE

• SHOP US NOW

PANASONIC • NOVA, ETC.

800-777-7731

## ATOMIC TIME FOR ANY COMPUTER

WWVB based time code receiver and real time clock with RS232 interface

### FEATURES

Sensitive receiver  
Direct UTC readout in ASCII  
Y2K compatible calendar  
0.1 second accuracy  
RS232 powered

Low cost

### APPLICATIONS

Remote data acquisition  
Embedded systems  
Automatic sequencers  
Tamperproof time stamping

**ULTRALINK**

702 782 9758 www.ulio.com

## EPS AS LOW AS 25¢

27C256	27C040	27C1024	87C51
27C512	27C400	28F010	8751
27C32A	27C4096	28F020	8755
27C32	574000	28F040	68705
27C128	574000	8749H	2564
27C64	27C402	8748H	2516
2716	27C020	8741	
2708	27C210	8742	
27C512-90	27C010	8744	

STATIC RAM	MEMORY	PROCESSOR
62256 & 6264 & 6116		8255
GAL16V8 & GAL22V10		8254
PIC16C54 & PIC16C56		80C31

**SPECIAL 2764**

TEL: (818) 774-9444 · FAX: (818) 774-0822  
WE BUY EXCESS INVENTORY



FREE SAMPLE COPY!  
**ANTIQUE RADIO CLASSIFIED**

Antique Radio's Leading Monthly Magazine

Articles - Classifieds - Ads for Parts & Services. Also: Ham Equip. - Books - Telegraph - 40's, 50's & 60's Radios - Early TV - Auction Reports & more...

1-Year: \$39.49 (\$57.95 by 1st Class)  
6-Month Trial - \$19.95. Foreign - Write.

A.R.C., P.O. Box 802-G23  
Carlisle, MA 01741

Call: 978-371-0512 - Fax: 978-371-7129  
Web: www.antiqueradio.com

TOGGLE SWITCHES - All sizes, all types

LEDs - 1.8mm to 10mm all colors, shapes & intensities

MINIATURE LAMPS - for all applications

HOOK-UP WIRE - 18 to 26 gauge, 10 colors

SMALL ELECTRIC MOTORS - 3 to 12 volt

SOCKETS & PLUGS

DEMAR ELECTRONICS  
P.O. Box 7215, Algonquin, IL 60102  
Toll Free 877-655-6433  
Fax 847-854-4434  
Call or Fax for Quotes  
Catalogs Available

## CUT MANUFACTURING COST!

CUSTOM METAL BOXES  
WE ACCEPT SMALL ORDERS TOO

SHEET METAL

20 GAUGE

SILK SCREEN

PRINTED

WITH YOUR CO. NAME

ALSO PCB, SMT, PROTOTYPES, ASSEMBLY, PLASTIC MOLDS, INJECTION MOLDING.

USA Office: V&V Mach. & Equip. Inc.  
Ph: (281) 397-8101, Fax: (281) 397-6220.  
Mexico Plant: Marketing Tech.  
Ph: 011 (525) 361-3351, Fax: 011 (525) 361-5996.

## CUSTOM PLASTIC PARTS

• MODELS (WOOD AND RESIN). TO EVALUATE YOUR PARTS BEFORE COMMITTING TO MANUFACTURE A MOLD.  
• MOLD DESIGN AND BUILDING.



• PRODUCTION OF INJECTION MOLDED PARTS. NO ORDER TO SMALL OR TO BIG.  
• VERY COMPETITIVE ON HIGH LABOR PARTS.

We also have manual low pressure machines for injection molding of very small runs or prototypes of parts up to 2 oz. At a surprisingly low price.

USA Office: V&V Mach. And Equip. Inc.  
Tel: (218) 397-8101, Fax: (218) 397-6220.  
Please send blue prints or samples to:  
Marketing Tech. S.A. • Alamo 53, 4 Piso • Sta. Monica, Tlal • Eco. De Mexico 54040 • Tel. 011 (525) 361-3351.  
Fax: 011 (525) 361-5996. AT: N. VICTOR M. MCENDOZA  
e-mail: marktech@fiosel.net.mx

## ASSEMBLY & ENGINEERING

Producible designs since 1970

Contract Engineering  
Embedded Microprocessors  
PCB Layout and Packaging Design  
Analog Including RF to 1 GHz  
Instrumentation  
A/D and D/A

Contract Assembly  
High-Speed Fujii Surface Mount  
Through hole  
Turn-key or Kit  
Run sizes one through thousands  
Test and burn-in available

Bilocon Corp.  
800-736-5927  
425-353-2276  
www.bilocon.com




ST241A  
Stereo microscope  
\$240.00  
New - 1 year warranty

650/367-8320  
Fax - 365-5845  
3580 Haven Avenue  
Redwood City, CA 94063-4603  
Email: jlittle@netwizards.net

## CONTROL • MEASURE • INPUT

MODEL 40-\$109

• RS-232 interface  
• 28 lines digital I/O  
• Eight analog inputs  
• PWM output  
• Three stepper ports

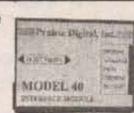

MODEL 100-\$279

• 12-bit 100KHz A/D • Four analog outputs  
• Three timer counters • 24 digital I/O



PRAIRIE DIGITAL, INC.


920 SEVENTEENTH ST., INDUSTRIAL PARK  
PRAIRIE DU SAC, WI 53578  
TEL: (608) 643-8599 • FAX: (608) 643-6754

CALLER ID PHONE  
w/ELECTRONIC ORGANIZER!  
w/1500 NUMBER  
SPEED DIALER AND  
MUCH MORE!!



\$49.95  
+ S&H  
MC/VISA  
TURNER TECHNOLOGIES  
www.turnertechusa.com  
616-475-8531


## 10 Hr. Telephone Recorder \$69

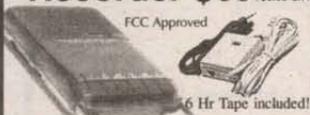


FCC Approved  
Automatically starts recording when the phone is picked up and stops when you hang up. Records both sides of the conversation!  
BEST PRICE AROUND!

FREE CATALOG  
www.mscelectronics.com

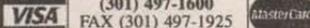MSC Electronics  
PO BOX 461 Jessup, MD 20794  
(301) 497-1600  
FAX (301) 497-1925


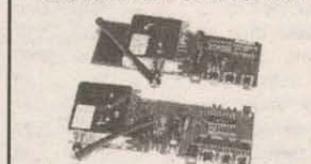
## 2.4GHZ Wireless Transmitter & Receiver



2.4GHz - 2.48GHz User Selectable  
.Over 700' Range and 4 Chl auto-scan  
.Compatible B/W & Color Video, Stereo  
.Designed for wireless security system  
\$.89/set @ 100pcs. Customization avail.

MATCO INC  
www.mat-co.com (800)440-0299

## Monarch Bar Code Equipment

8900B Power Calibrator	\$40
3400A Voltmeter	\$75
3465A Digital Voltmeter	\$275
Tek 176 Pulse Current Fixture	\$35
436A Power Meter	\$500
1715A Oscilloscope	\$150
8654 Signal Generator	\$200
905A Coaxial Slide Load	
1.8-18GHz HP	\$200
911A Coaxial Slide Load	
2.0-18GHz HP	\$200
11638A Type N Cal. KitTek	
P6045 FET probe package	\$150
Tek P6046	\$200
Tek P6201	\$150
HP 33321K Attenuator/70dB	\$150
8411A	\$70
8732B	\$50

ADDITIONAL PLUG-INS  
7A11...\$25; 7A14...\$50; 7B92...\$75; 7A13...\$50;  
7A18...\$35; 7B92A...\$75; 7B85...\$50; 7A25...\$50  
T.T.I. • 616-475-8531 • 616-475-8534 fax  
FREE CATALOG • CALL TODAY  
www.turnerequipment.com

## GPS Units

Trimble Placer 400  
6 Channel w/ 3" diam. Antenna  
\$59.95

Trimble Placer 300  
6 Channel w/ Wedge Antenna  
\$99.95

GEOTEK Units  
Call for a List of Equipment

Communications Surplus  
713-526-8000 or 1-877-878-6GPS  
lshafer@flash.net Fax to 713-522-6309

# HOW TO PLACE A CLASSIFIED AD

TYPE or PRINT your **ELECTRONICALLY RELATED** ad copy **CLEARLY** (not all caps) on a separate piece of paper. Spell out words when submitting handwritten copy. Calculate the number of words and multiply it by the appropriate rate (see RATE PER WORD section). Include any charges for bold and/or CAPPED words, any artwork costs that would be applicable, and/or costs for boxing your ad (explained below). Choose the appropriate classification for your ad(s) to appear in (see below). If no classification is indicated, it will be placed in Misc. Electronics or wherever we deem most suitable. **Enclose your name, address, phone number, and Nuts & Volts account number from your mailing label** (if available) for identification purposes. Include full payment — **CLASSIFIEDS RUN ON A PRE-PAID BASIS ONLY** — and mail your completed order to:

**NUTS & VOLTS MAGAZINE**, 430 Princland Ct., Corona, CA 91719.

## RATE PER WORD

The ad rate for **current PAID subscribers** is **60¢** per word. All others pay **\$1.20** per word. There is a **\$9.00 minimum** charge per ad per insertion.

## WORDS IN BOLD AND/OR ALL CAPS

Words to be set in **bold** or **CAPS** are each **10¢** extra PER WORD. **BOLD CAPS** are **20¢** extra per word. The first two words of each ad are bold capped at no charge. Indicate bold words by underlining. Words normally written in caps (e.g., IBM) and accepted abbreviations such as VAC or MHz are NOT charged as all cap words. Use a two-letter abbreviation for states.

## PHOTOS, DRAWINGS, AND BOXES

A photo or drawing may be run at the top of your classified ad for an additional **\$10.00** (1" depth max.) for camera-ready art. No wording is allowed in this area. Add a one-time charge of **\$5.00** to enlarge, reduce, or duplicate line

art, or **\$8.00** for halftone of photographs. To **BOX** your ad, include an additional **\$50.00** for copy-only ads, or **\$75.00** for ads with art or photos.

## FAXING IN AD COPY

You may fax in ad copy or changes before the closing date (5:00pm on the **5th**) at 909-371-3052 using MasterCard or Visa. Include credit card expiration date, the name that appears on the card, a daytime phone number, and your **Nuts & Volts** account number. Ads without credit card information will not be listed as received until payment is received in full. **WE DO NOT CALL OR FAX BACK VERIFICATION OR QUOTES OF FAXED-IN ADS.** For verification of faxed-in ads, please call 909-371-8497.

## DEADLINE

Prepaid ads received by 5:00pm on the **closing date (5th of the month)** will appear in the following month's issue. Ads postmarked through the **5th**, but received after the closing date, will be placed in the next available issue. No cancellations or changes after the 5th. Cancellations and changes must be submitted in writing.

## IMPORTANT INFORMATION

All classified ads are running copy only. No special positioning, centering, dot leaders, extra space, etc. is allowed. All advertising in *Nuts & Volts* is limited to **electronically related items ONLY**. All ads are subject to approval by the publisher. We reserve the right to reject or edit any ad submitted. We do not take ad copy or changes over the phone. We do not bill for classified ads. Repeat ads or ads run in multiple classifications within the same issue are allowed. Paid subscribers may run ads at the 60¢ rate only through their subscription expiration date. **NO REFUNDS.** Credit only. No credit for typesetting errors will be issued unless you *clearly* print or type your ad copy.

*Choose a category for your ad from the classifications listed below.*

10. Ham Gear For Sale	80. Test Equipment	120. Components	155. Manuals/Schematics Wanted
20. Ham Gear Wanted	85. Security	125. Microcontrollers	160. Misc. Electronics For Sale
30. CB/Scanners	90. Satellite Equipment	130. Antique Electronics	170. Misc. Electronics Wanted
40. Music & Accessories	95. Military Surplus Electronics	135. Aviation Electronics	175. BBS & Online Services
50. Computer Hardware	100. Audio/Video/Lasers	140. Publications	180. Education
60. Computer Software	110. Cable TV	145. Robotics	190. Business Opportunities
70. Computer Equipment Wanted	115. Telephone/Fax	150. Plans/Kits/Schematics	200. Repairs/Service

## ADVERTISER'S INDEX

Abacom Technologies .....59	Cunard Associates.....78	Lemos International Co., Inc. ....65	Scott Edwards Electronics .....64
ABC Electronics .....38	Danbar Sales Company .....52	Linear Systems .....19	Seabird Technical .....69
Ace Computers .....62	Decade Engineering .....68	LLH Technology Publishing .....48	Shreve Systems .....68
ACP Super Store .....60	DeMar Electronics .....69	Lynxmotion, Inc. ....16	Skycraft Parts & Surplus, Inc. ....61
Advanced Educational Systems .....22	Dexis .....10	M2L Electronics .....37	Spy Outlet .....68
Alfa Electronics .....48	Digital Products Co. ....68	MCM Electronics.....24	Square 1 Electronics .....31
All Electronics Corporation .....56	Earth Computer Technologies .....54	Meredith Instruments .....47	Surplus Traders .....68
Allison Technology Corporation .....41, 68	Edlie Electronics, Inc. ....55	Metric Equipment Sales, Inc. ....74	Synergetics .....72
Alltech Electronics .....25	E.H. Yost & Co. ....47	microEngineering Labs .....29	Techniks, Inc. ....68
Alltronics .....20	ELECTRO MAVIN .....74	Micromint .....53	Technological Arts .....68
American Innovations, Inc. ....19	Electro Tool, Inc. ....53	Modern Electronics .....61	Telulex, Inc. ....73
American Technologies Network Corp. ....79	Electronic Design Specialists, Inc. ....63	Motron Electronics .....37	The RF Connection .....19
AM Research, Inc. ....31	Electronic Goldmine .....40	Mouser Electronics .....29	Timeless Products .....80
ANA Instruments .....67	Electronic Rainbow Ind., Inc. ....51	Mr. NiCd .....47	Tropical Hamboree .....61
Andromeda Research .....16	Electronix Corp. ....26	MSC Electronics .....69	T.T.I. ....69
Antique Radio Classified .....69	EMAC, Inc. ....53	Netcom .....13	Turner Technologies.....69
AST Global Electronics.....23	EPS .....69	Northwest Cable & Connector Co. ....17	Ultra Link .....69
Aventrade .....68	Equipment Management Technology .....39	Ocean State Electronics .....42	Unicorn Electronics .....65
Basic Electrical Supply	ExpressPCB .....32	One Stop Supplier .....65	USI Corp. ....32
& Warehousing Corporation .....38	Foss Warehouse Distributors.....68	Optoelectronics .....94	Utopia Tools .....8
Baylin Publications .....17	Gateway .....33	Pacific Test Equipment Corp. ....14	V&V Mach. & Equipment, Inc. ....68, 69
Bell Electronics .....49	General Device Instruments .....68	Parallax, Inc. .... Back Cover	Velleman .....43
Bilcocon Corp. ....69	Glentech, Inc. ....68	PARAMAX, INC. ....77	Viking International .....26
Bismite Computers Outlet .....60	Halted Specialties Co. ....3	PCW, Inc. ....60	Visitect, Inc. ....29
Black Feather Electronics .....77	Herbach and Rademan.....15	Phelps Instruments .....63	Weeder Technologies .....39
Brigar Electronics.....12	H.T. Orr Computer Supplies.....61	Pioneer Hill Software .....41	Western Test Systems .....34-35
C & S Sales, Inc. ....44, 82	Hyatt Electronic Surplus .....69	Polaris Industries .....27	Wholesale Cable .....49
C and H Sales Company .....58	IndustroLogic .....27	Prairie Digital, Inc. ....69	Worldwyde .....67
Chaffin Electronics .....36	Information Unlimited .....81	P.S. Technology .....58	
Chenesko Products, Inc. ....79	Inkjet Southwest .....50	Pulsar, Inc. ....10	
Circuit Etching Technics.....54	Intronics, Inc. ....54	R & S Surplus .....59	
Communications Surplus.....8, 69	Jade Products, Inc. ....68	Ramsey Electronics, Inc. ....57	
Comtrad Industries .....9	James' Electronic Services, Ltd. ....66	Resources Un-Ltd. ....75	
Consumertronics .....28	J-Works, Inc. ....36	R.E. Smith .....68	
Corporate Systems Center .....2, 95	KDE Electronics Corp. ....19	Roger's Systems Specialist .....45	
Cruising Equipment .....67	La Paz Electronics Int'l. ....78	Sam's Electronics .....41	

## AMATEUR RADIO & TV

Abacom Technologies	59
Alltronics	20
Communications Surplus	8, 69
Gateway	33
Jade Products, Inc.	68
Lemos International Co., Inc.	65
Ocean State Electronics	42
Ramsey Electronics, Inc.	57
The RF Connection	19

## BATTERIES/CHARGERS

Aventrade	68
Cruising Equipment	67
Cunard Associates	78
E.H. Yost & Co.	47
Jade Products, Inc.	68
Mr. NiCd	47

## BUSINESS OPPORTUNITIES

Cheneko Products, Inc.	79
------------------------	----

## BUYING ELECTRONIC SURPLUS

ABC Electronics	38
Alltech Electronics	25
Black Feather Electronics	77
C and H Sales Company	58
Dexis	10
Earth Computer Technologies	54
EPS	69
Equipment Management Technology	39
Metric Equipment Sales, Inc.	74
Roger's Systems Specialist	45
Skycraft Parts & Surplus, Inc.	61

## CABLE TV

Basic Electrical Supply & Warehousing Corporation	38
Foss Warehouse Distributors	68
James' Electronic Services, Ltd.	66
KDE Electronics Corp.	19
Modern Electronics	61
One Stop Supplier	65
PCW, Inc.	60
Sam's Electronics	41
Timeless Products	80
Wholesale Cable	49

## CB/SCANNERS

USI Corp.	32
-----------	----

## CCD CAMERAS/VIDEO

American Innovations, Inc.	19
American Technologies Network Corp.	79
Black Feather Electronics	77
Decade Engineering	68
Herbach and Rademan	15
MSC Electronics	69
Polaris Industries	27
Ramsey Electronics, Inc.	57
Resources Un-Ltd.	75
Seabird Technical	69
Spy Outlet	68
USI Corp.	32

## COMPONENTS

Ace Computers	62
Circuit Etching Technics	54
Communications Surplus	8, 69
Electronic Goldmine	40
EPS	69
Hyatt Electronic Surplus	69
La Paz Electronics Int'l.	78
Linear Systems	19
Ocean State Electronics	42
Pulsar, Inc.	10
Skycraft Parts & Surplus, Inc.	61
Unicom Electronics	65
Visitect, Inc.	29

## COMPUTER

### Hardware

Ace Computers	62
ACP Super Store	60
Allison Technology Corp.	41, 68
Alltech Electronics	25
AM Research, Inc.	31
Bisme Computers Outlet	60
Chaffin Electronics	36
Consumertronics	28
Corporate Systems Center	2, 95
Earth Computer Technologies	54
ELECTRO MAVIN	74

General Device Instruments	68
Halted Specialties Co.	3
La Paz Electronics Int'l.	78
MCM Electronics	24
Northwest Cable & Connector Co.	17
Roger's Systems Specialist	45
Shreve Systems	68
Techniks, Inc.	68
Ultra Link	69
Worldwyde	67

### Software

AM Research, Inc.	31
Bisme Computers Outlet	60
Electronix Corp.	26
Pioneer Hill Software	41
Ultra Link	69

### Microcontrollers / I/O Boards

Abacom Technologies	59
Advanced Educational Systems	22
AM Research, Inc.	31
Bisme Computer Outlet	60
EMAC, Inc.	53
IndustroLogic	27
La Paz Electronics Int'l.	78
Micromint	53
Motron Electronics	37
Parallax, Inc.	Back Cover
PARAMAX, INC.	77
Prairie Digital, Inc.	69
R.E. Smith	68
Scott Edwards Electronics	64
Square 1 Electronics	31
Technological Arts	68
VersaTech Electronics	22

### Printers/Printer Supplies

Cheneko Products, Inc.	79
H.T. Orr Computer Supplies	61
Inkjet Southwest	50

## DESIGN/ENGINEERING SERVICES

ExpressPCB	32
Pulsar, Inc.	10
V&V Mach. & Equipment, Inc.	68, 69

## EDUCATION

Advanced Educational Systems	22
Electronix Corp.	26
EMAC, Inc.	53

## EVENTS/SHOWS

ACP Super Store	60
Tropical Hamboree	61

## KITS

Alltronics	20
C & S Sales, Inc.	44, 82
Digital Products, Inc.	68
Earth Computer Technologies	54
Edlie Electronics, Inc.	55
Electronic Goldmine	40
Electronic Rainbow Ind., Inc.	51
EMAC, Inc.	53
Gateway	33
Hyatt Electronic Surplus	69
Information Unlimited	81
Inkjet Southwest	50
Jade Products, Inc.	68
Ocean State Electronics	42
Ramsey Electronics, Inc.	57
Scott Edwards Electronics	64
USI Corp.	32
Velleman	43
Weeder Technologies	39

## LASERS

Information Unlimited	81
Meredith Instruments	47
Resources Un-Ltd.	75
Unicom Electronics	65

## MISC./SURPLUS

All Electronics Corporation	56
Alltech Electronics	25
Black Feather Electronics	77
Brigar Electronics	12
C and H Sales Company	58
Chaffin Electronics	36
Communications Surplus	8, 69
Consumertronics	28
DeMar Electronics	69
Electronic Goldmine	40
Electronic Rainbow Ind., Inc.	51
EPS	69
Equipment Management Technology	39
Gateway	33

**FIND**  
what you need . . .

**FAST**

BY PRODUCT  
OR  
CATEGORY

Halted Specialties Co.	3
Hyatt Electronic Surplus	69
Linear Systems	19
P.S. Technology	58
Resources Un-Ltd.	75
Shreve Systems	68
Skycraft Parts & Surplus, Inc.	61
Surplus Traders	68
Unicom Electronics	65
Viking International	26
Visitect, Inc.	29
Weeder Technologies	39

## PROGRAMMERS

Andromeda Research	16
General Device Instruments	68
Intronics, Inc.	54
M2L Electronics	37
microEngineering Labs	29

## PUBLICATIONS

Antique Radio Classified	69
Consumertronics	28
LLH Technology Publishing	48
Mouser Electronics	29
Netcom	13
Square 1 Electronics	31
Synergetics	72

## ROBOTICS

Abacom Technologies	59
Lemos International Co., Inc.	65
Lynxmotion, Inc.	16
PARAMAX, INC.	77

## SATELLITE

Baylin Publications	17
---------------------	----

## SECURITY

American Innovations, Inc.	19
American Technologies Network Corp.	79
Information Unlimited	81
Lemos International Co., Inc.	65
MSC Electronics	69
Polaris Industries	27
Visitect, Inc.	29

## SOLAR EQUIPMENT

Cruising Equipment	67
Herbach and Rademan	15

## STEPPER MOTORS

Alltronics	20
Herbach and Rademan	15
PARAMAX, INC.	77

## TELEPHONE

Bilocon Corp.	69
Digital Products, Inc.	68
Telulex, Inc.	73
Turner Technologies, Inc.	69
Weeder Technologies	39

## TEST EQUIPMENT

ABC Electronics	38
Alfa Electronics	48
Allison Technology Corp.	41, 68
ANA Instruments	67
AST Global Electronics	23
Bell Electronics	49
C & S Sales, Inc.	44, 82
C and H Sales Company	58
Cruising Equipment	67
Danbar Sales Company	52
Dexis	10
Digital Products, Inc.	68
Electronic Design Specialists, Inc.	63
Equipment Management Technology	39
Electro Tool, Inc.	53
Glentech, Inc.	68
Intronics, Inc.	54
J-Works, Inc.	36
MCM Electronics	24
Metric Equipment Sales, Inc.	74
Optoelectronics	94
Pacific Test Equipment Corp.	14
Phelps Instruments	63
Pioneer Hill Software	41
R & S Surplus	59
Seabird Technical	69
Telulex, Inc.	73
T.T.I.	69
Western Test Systems	34-35

## TOOLS

C & S Sales, Inc.	44, 82
Electro Tool, Inc.	53
The RF Connection	19
Utopia Tools	8

## WIRE/CABLE & CONNECTORS

Northwest Cable & Connector Co.	17
Roger's Systems Specialist	45
The RF Connection	19

# RESOURCE BIN

number eighty four

## A look at some medical electronics.

**O**ur usual reminder here that the *Resource Bin* is a two-way column. You can get tech help, consultant referrals, and off-the-wall networking on nearly any electronic, *tinaja* questing, personal publishing, money machine, or computer topic by calling me at (520) 428-4073 weekdays 8-5 Mountain Standard Time.

Be certain to frequently check out my new *Guru's Lair* web site at (where else?) [www.tinaja.com](http://www.tinaja.com).

### Some Medical Electronics Topics

This month, I thought I'd round up a bunch of resources which seem to relate to medical electronics in one way or another. But first, an obvious big disclaimer: Please do not consider what follows to be medical advice in any way, shape, or form. Do not base any critical decisions upon anything said or suggested here. At least not without careful further research.

Working with medical electronics has major hassles. Typical electronics suppliers flat out refuse to allow their components to get used in life critical applications. There's untold zillions of regulations. You might easily end up illegally practicing medicine.

The market is strictly by, for, and of big bucks and long term insiders. And betting a life on something that does not work or puts off seeking proper help until too late can obviously end up a deadly travesty.

But there is a lot of very interesting possibilities here. If you are thorough and use the available resources.

### Some Alternates

I have personally found the best of alternate medicine to be exceptionally useful in prevention and dealing with chronic problems. While a traditional medicine is by far your better choice when working with urgent repairs.

There's a lot that's very good and very bad about both routes. I also do believe that most medical

problems are your own dumb fault. Caused or made worse by lifestyle, activity, and diet considerations.

Your key secret to dealing with any problem, medical or otherwise, is to get *multiple information from several independent sources*. If you are dealing with a single source of medical info, the chances are more than good there may be hidden agendas or some cross purposes not in your best

**NEXT MONTH:  
Don looks at some of his favorite web sites.**

interest.

Second opinions are crucial. Much more on these topics can be found in DONTICK.PDF and in those alternate medicine links you can find at [www.tinaja.com/beewb01.html](http://www.tinaja.com/beewb01.html).

Essential alternate medical reading is anything by or about Dean Ornish or most books relating to the Pritikin clan. Yes, "wash it down with a steak" near-vegetarianism seems to work like a champ. At least for me.

### Medline

The definitive online research tool that all doctors and medical pros use is called *Medline*. Any time you want to know anything about any medical topic, it is just common sense to go to Medline for a second or third opinion. Sadly, Medline has been outrageously expensive. But a number of sites are now offering you free Medline access of one type or another.

One superb Medline access site is *Health World* at [www.healthy.net](http://www.healthy.net). The second is *American Health Network* at [www.ahn.com](http://www.ahn.com). Other gateway sites for medical stuff are Emory University's at [www.gen.emory.edu/medweb](http://www.gen.emory.edu/medweb) and the folks at [www.medaccess.com](http://www.medaccess.com).

Convenient click-through links to all of these and a few others are found at [www.tinaja.com/beewb01.html](http://www.tinaja.com/beewb01.html).

### Medical Electronics Products

This is one of many free "shopper" industry trade journals which address medical electronics. Here's some more journals and shoppers ...

- *Biomedical Instrumentation and Technology*
- *Medical & Biological Engineering and Computing*
- *Medical Design Technology*
- *Medical Devices Report*
- *Medical Electronics & Equipment News*
- *Medical Electronics and Medical Electronic Products*
- *Medical Electronics Manufacturing*
- *Medical Equipment Designer*
- *Medical Product Manufacturing News*

As an aside, there's a company that specializes in those antique scientific instruments from the 16th to the 19th centuries. Find them at *Early Scientific Instruments*. And scads of intriguing books on turn-of-the-century science and technology can be found through *Lindsay* at [www.lindsay.com](http://www.lindsay.com), or use his banner link on my website.

### Fun With Dentists

I may have actually found a use for dentists. Several actually.

Firstoff, they have these wonderful x-ray machines. Which are just dandy for snooping around inside of sealed modules such as telephone interface blocks or pulse monitors. Yeah, their film size is tiny and their res isn't that great. But, with practice, you can tell an awful lot about a chip simply by looking at its number of pins, its lead frame, and its die size.

Secondly, you might think of your dentist as a precision machine shop. I once needed a shaft coupling for a HP distortion analyzer. A little grinder work on a delrin rod, and a tricky-to-get item was cheaply substituted.

Dentists could be highly useful for carved shapes (such as odd connector cases or proof-of-concept plastics), to "unencapsulate," or simply for elegant mechanical design.

Some dental products may have all sorts of unintended uses. A few years ago, there was an introduction of new disposable low-cost handpieces. These were basically a small and powerful turbine that could be cut down to fit inside a plotter pen. And had all sorts of printed circuit, mini-CAD

new from  
**DON LANCASTER**

#### ACTIVE FILTER COOKBOOK

The sixteenth (!) printing of Don's bible on analog op-amp lowpass, bandpass, and highpass active filters. De-mystified instant designs. **\$28.50**

#### CMOS AND TTL COOKBOOKS

Millions of copies in print worldwide. The two books for digital integrated circuit fundamentals. About as hands-on as you can get. **\$28.50 each.**

#### RESEARCH INFOPACKS

Don's instant cash-and-carry flat rate consulting service. Ask any reasonable technical question for a detailed analysis and complete report. See [www.tinaja.com/info01](http://www.tinaja.com/info01) for specifics. **\$75.00**

#### INCREDIBLE SECRET MONEY MACHINE II

Updated 2nd edition of Don's classic on setting up your own technical or craft venture. **\$18.50**

#### LANCASTER CLASSICS LIBRARY

Don's best early stuff at a bargain price. Includes the CMOS Cookbook, The TTL Cookbook, Active Filter Cookbook, PostScript video, Case Against Patents, Incredible Secret Money Machine II, and Hardware Hacker II reprints. **\$119.50**

#### LOTS OF OTHER GOODIES

Tech Musings V or VI .....	\$24.50
Ask the Guru I or II or III .....	\$24.50
Hardware Hacker II, III or IV .....	\$24.50
Micro Cookbook I .....	\$19.50
PostScript Beginner Stuff .....	\$29.50
PostScript Show and Tell .....	\$29.50
Intro to PostScript Video .....	\$34.50
PostScript Reference II .....	\$34.50
PostScript Tutorial/Cookbook .....	\$22.50
PostScript by Example .....	\$32.50
Understanding PS Programming .....	\$29.50
PostScript: A Visual Approach .....	\$22.50
PostScript Program Design .....	\$24.50
Thinking in PostScript .....	\$22.50
LaserWriter Reference .....	\$19.50
Type 1 Font Format .....	\$16.50
Acrobat Reference .....	\$24.50
Whole works (all PostScript) .....	\$380.00
Technical Insider Secrets .....	FREE

#### BOOK-ON-DEMAND PUB KIT

Ongoing details on Book-on-demand publishing, a new method of producing books only when and as ordered. Reprints, sources, samples. **\$39.50**

#### THE CASE AGAINST PATENTS

For most individuals, patents are virtually certain to result in a net loss of sanity, energy, time, and money. This reprint set shows you Don's tested and proven real-world alternatives. **\$8.50**

#### BLATANT OPPORTUNIST I

The reprints from all Don's Midnight Engineering columns. Includes a broad range of real world, proven coverage on small scale technical startup ventures. Stuff you can use right now. **\$24.50**

#### RESOURCE BIN I

A complete collection of all Don's Nuts & Volts columns to date, including a new index and his master names and numbers list. **\$24.50**

#### FREE SAMPLES

Check Don's Guru's Lair at <http://www.tinaja.com> for interactive catalogs and online samples of Don's unique products. Searchable reprints and reference resources, too. Tech help, hot links to cool sites, consultants. email: [don@tinaja.com](mailto:don@tinaja.com)  
FREE US VOICE HELPLINE VISA/MC

#### SYNERGETICS

Box 809-NV  
Thatcher, AZ 85552  
(520) 428-4073

machine, and other flutterwumper uses. A few details appeared in HACK76.PDF. And there's great heaping bunches of light-curing plastics and other items.

One of several trade journals here is *Dental Products Report*. More on some of these mini-turbine possibilities at [www.tinaja.com/flut01.html](http://www.tinaja.com/flut01.html).

Finally, certain dentists seem to get off on all those perpetual motion and overunity energy scams so, better to let them buy those overpriced videos and books. Then, you'll borrow these

# RESOURCE BIN

## SOME MEDICAL ELECTRONICS AND RELATED SOURCES

**Berkeley Wellness Ltr**  
PO Box 420148  
Palm Coast FL 32142  
(904) 445-6414

**Biomedical Insts**  
210 S 13th St  
Philadelphia PA 19107  
(800) 962-1892

**Cardiac Alert**  
7811 Montrose Rd  
Potomac MD 20854  
(301) 424-3700

**Careers & the disabled**  
150 Motor Parkway #420  
Hauppauge NY 11788  
(516) 273-0066

**Closing the Gap**  
PO Box 68  
Henderson MN 56044  
(612) 248-3294

**Dental Prod Report**  
2 Northfield Pz #300  
Northfield IL 60093  
(847) 441-3700

**Dentistry Today**  
26 Park St  
Montclair NJ 07042  
(201) 783-3935

**Diet & Nutrition Ltr**  
53 Park Place  
New York NY 10007  
(800) 274-7581

**Disability Bookshop**  
PO Box 129  
Vancouver WA 98666  
(800) 637-2256

**Disabilities Digest**  
522 Cinti-Batavia Park  
Cincinnati OH 45244  
(513) 528-0404

**Disability Policy Jnl**  
346 North West Avenue  
Fayetteville AR 72701  
(501) 575-3656

**Disability Rag**  
PO Box 145  
Louisville KY 40201  
(502) 459-5343

**Early Sci Insts**  
PO Box 151  
Haslings NY 10706  
(914) 478-2594

**Educom Review**  
1112 16th Street NW #600  
Washington DC 20036  
(280) 872-4200

**Exceptional Parent**  
209 Harvard Street #303  
Brookline MA 02146  
(617) 730-5800

**Gale Research**  
835 Penobscot Blvd  
Detroit MI 48226  
(313) 961-2242

**Grey House Pubs**  
Pocket Knife Square  
Lakeville CT 06039  
(800) 526-2139

**Harvard Heart Letter**  
164 Longwood Avenue  
Boston MA 02115  
(800) 829-9171

**Health & Healing**  
PO Box 60042  
Potomac MD 20859  
(800) 539-8219

**Health Wisdom for Women**  
7811 Montrose Rd  
Potomac MD 20854  
(301) 762-8061

**Herb Quarterly**  
223 San Anselmo Ave #7  
San Anselmo CA 94960  
(415) 455-9540

**In Vivo Metric**  
PO Box 249  
Healdsburg CA 95448  
(707) 433-4819

**Issues in Law & Medicine**  
PO Box 1586  
Terre Haute IN 47808  
(812) 232-0103

**Lifetime Health Letter**  
PO Box 420342  
Palm Coast FL 32142  
(800) 829-9177

**Lindsay Publications**  
PO Box 538  
Bradley IL 60915  
(815) 935-5353

**Mayo Clinic Health Ltr**  
200 First Street SW  
Rochester MN 55905  
(800) 333-9037

**Medical Bio Eng & Comp**  
445 Hoes Ln  
Piscataway NJ 08855  
(908) 981-0060

**Medical Design Tech**  
275 Washington St  
Newton MA 02158  
(617) 964-3030

**Medical Electronics**  
2994 W Liberty Ave  
Pittsburgh PA 15216  
(412) 343-9666

**Medical Electronics Mfg**  
3340 Ocean Park Blvd #1000  
Santa Monica CA 90405  
(310) 392-5509

**Medical Electronic Prds**  
2994 W Liberty Ave  
Pittsburgh PA 15216  
(412) 343-9666

**Medical Equip Designer**  
29100 Aurora Rd #200  
Solon OH 44139  
(216) 248-1125

**Medical Product Mfg News**  
3340 Ocean Park Blvd #1000  
Santa Monica CA 90405  
(310) 392-5509

**Medline**  
8600 Rockville Pike  
Bethesda MD 20894  
(800) 638-8480

**Mobility International USA**  
PO Box 10767  
Eugene OR 97440  
(503) 343-1284

**Natural Health**  
17 Station Street  
Brookline Village MA 02147  
(800) 526-8440

**New Mobility**  
PO Box 8967  
Malibu CA 90265  
(800) 543-4116

**Ornish Medicine**  
900 Bridgeway #1  
Sausalito CA 94965  
(800) 64-1110

**Polar**  
99 Seaview Blvd  
Port Washington NY 11050  
(516) 484-2400

**Prevention//J/Rodale Press**  
33 E Minor St  
Emmaus PA 18098  
(610) 967-5171

**Pritikin Center**  
1910 Ocean Front Walk  
Santa Monica CA 90405  
(800) 421-9911

**Synergetics**  
Box 809  
Thatcher AZ 85552  
(520) 428-4073

**TASK**  
100 West Cerritos Avenue  
Anaheim CA 92805  
(714) 533-TASK

**Trace Center Publications**  
S-151 Waisman Cen UWI  
Madison WI 53705  
(608) 263-5408

**Women's Health Advocate**  
10310 Main St #301  
Fairfax VA 22030  
(800) 829-5876

Gotchas here include the nulls of the ferrite rod transmitter in the chest unit; making sure any other ferrites or cores used offer decent Q and good permeability at 5 KHz; and working out a suitable averaging algorithm for a stable yet current display. It would seem that a four beat running average is a pretty fair starting point.

Interesting books on this subject do include John Parker's *Heart Monitor Training for the Complete Idiot*, and Ed Burke's *Precision Heart Rate Training*. I have placed links to these and others at [www.tinaja.com/amlink01](http://www.tinaja.com/amlink01).

Tech details, sources, software, and insider info on pulse monitors can be found in HACK68.PDF. I've also got InfoPacks available on this.

### Disabilities

We looked at several disability and handicapped resources way on back in RESBN44.PDF. Chances are that if you have come up with a "solution" to some limited hearing or limited vision problem, others are likely to already have a better approach. It also seems to me that there are lots of hidden agendas in the disability "industry" that you should be aware of. Profits are also exceptionally elusive.

At any rate, one extremely useful gateway resource is Trace Center. They appear to have the definitive CD-ROM resource bases on handicapped and disability aides. A bimonthly mag on using microcomputer technology for the disabled is *Closing the Gap*. One that targets children with disabilities is the *Exceptional*

fiction works for utterly fascinating fantasy reading and viewing. Of the mesmerizingly awful.

More info on pseudoscience topics at [www.tinaja.com/pseu-do01.html](http://www.tinaja.com/pseu-do01.html).

### Pulse Monitors

There sure appears to be a bunch of interest in pulse monitors lately. I've personally found these exceptionally useful for working around some long term medical problems. Others apply them extensively for aerobics.

There are two popular types. One low-cost solution is the *pleth-*


*symograph* that clips onto a finger, a toe, or your earlobe. These operate on finger or toe capillaries, expanding and contracting on each heart beat. They often consist of an infrared LED photoreflexor.

The problem is that *motion artifacts* make these totally useless for aerobic exercise programs. Instead, the more costly EKG types can be used. Typical units are the *Polar Edge*. These consist of a chest strap that has two sensing conductors and a small transmitter. A separate "wristwatch" receiver senses and displays the pulse information.

The transmitter converts each pulse beat into a burst of roughly 35 cycles of 5 KHz sinewaves. The receiver detects the sinewave bursts and then averages and displays them.

You can think of this system as an ultra low-frequency pulsed CW radio transmitter. Or, as a loosely coupled higher-frequency audio transformer. Either way, a computer interface can be easily built. You can even sense the signal using an eight-inch loop of wire on a scope probe. Since you are very much in the near field, ranges above five feet or so will be hard to do.

## Any waveform you want!

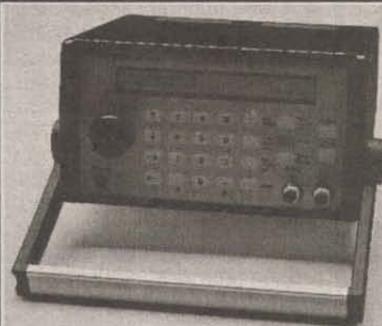

Telulex Inc. model SG-100A


- New Features:**
- ✓ 21.5 MHz
  - ✓ .01 Hz steps
  - ✓ multi-unit phaselock

### ● Synthesized Signal Generator


Clean sinewaves DC-21.5 MHz with .001% accuracy!  
.01 Hz steps. DC Offset. RS232 remote control.
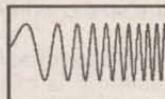
### ● Arbitrary Waveform Generator


40 Megasamples/Second. 32,768 points. 12 bit DAC




DC to 21.5 MHz linear and log sweeps

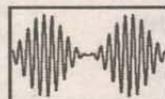


Int/Ext AM, SSB, Dualtone Gen.

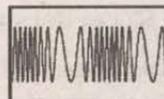


Int/Ext FM, PM, BPSK, Burst

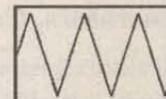


Ramps, Triangles, Exponentials

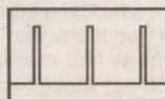

Pulse Generator

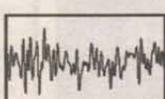

Noise

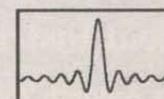

Arbitrary Waveforms




Unlimited Possibilities!

**Telulex Inc.**

2455 Old Middlefield Way S  
Mountain View, CA 94043

Tel (650) 938-0240  
Fax (650) 938-0241
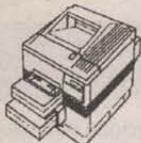
<http://www.Telulex.com>  
Email: sales@Telulex.com



## Used HP Duplex Laser Printers Blowout Price \$300.00

Hewlett Packard IID - Empty MIO Slot to Install a Jet Direct Card  
300 DPI - Can Print Double or Single Sided - Dual Letter Trays  
Can Take Letter or Legal Size - 3 Meg of Ram (Expandable to 8)  
Lease Returns, but were well maintained Under Service Contract  
No Hassle 30 Day Warranty - Uses 95A Cartridges

## Quality Computer Towers AT Style (Not ATX)

Full (260 Watt)(11 bays) \$35.00  
Mid Size (230 Watt)(7 bays) \$22.00  
Mini Size (230 Watt)(6 bays) \$17.00



## Hard Drives

New 2.1 Gig Seagate SCSI

\$80.00

New Micropolis 1.53 gig SCSI

\$50.00

New 760 Meg ESDI XT8760EH

\$40.00



Lots of MicroWave Goodies In Stock

## Brand New Wavetek 907AF Frequency Generators

Range 7-12.4 GHz \$1000.00

HP Direct Reading Frequency Meter

#R532A 26.5-40 GHz New \$500.00

SMA Attenuators - Stepper Motors



## Electro Mavin

800-421-2442 or FAX 310-632-9867

E-Mail [john@mavin.com](mailto:john@mavin.com)

Visit Our Web Site for More Info and Specials

<http://www.mavin.com/mavin.html>

# Metric

Equipment Sales, Inc.

800-432-3424

Fax: 510-264-0886  
[www.metricsales.com](http://www.metricsales.com)



Scopes, Meters, Analyzers, Power Supplies, Signal  
Generators, Counters, Recorders and more

Hewlett-Packard, Tektronix, Fluke, Dranetz, TTC, Anritsu,  
Wavetek, Keithley, and more

## Test & Measurement Instruments

Over 7000 Models • 6-Month Warranty  
Save 30-90% • 5-Day Free Trial

## Parent.

Useful newsgroups include ...

alt.comp.blind-users  
alt.disability.blind.social  
alt.discuss.disability  
alt.education.disabled  
alt.society.deaf  
alt.support.disabled  
alt.support.disabled.artists  
alt.support.learning-disab  
misc.handicap

There's all sorts of newsletters and ezines as well. Normal web searches should be able to quickly pin all these down for you.

## Brainwaves

Various *biofeedback* schemes can be based on sensing and acting upon low frequency brainwaves in that 1 to 12 Hz region. One apparently proven use is for stress management. Systems and results range the gamut from legitimate traditional medicine to far out new age hogwash.

The key source for biopotential skin electrodes seems to be *In Vivo Metric*. Additional suppliers do appear in the trade journals mentioned above.

But please think twice before you hot wire your cat.

## The Placebo Effect

A patient that wants to get better and believes they are taking positive steps towards a "cure" is often much more likely to actually do so. This is called the *placebo effect*. Placebo effects are very real and very powerful. As such, they often mask whether some process or medicine is useful.

A lot of the locals around here seem to get off on "arthritis cures" that are magical little grey electrical boxes. In some of them, a very weak electrical current gets used (literally creating a "live" or a "warm fuzzy" sub-shock). But in others, the circuitry makes no sense whatsoever.

In my opinion, there is no credible basis as to why such a device would work. Except for that overwhelming placebo effect. But the locals are sure convinced otherwise.

As before, careful and independent research is essential. When something works, fine. But don't bet on a far out (or far off) device to the point where it gets too late for traditional medicine.

And do remember that "net" is the acronym for *not entirely true*. Always seek out second and third opinions. And realize that, the further you get away from Medline, the less likely the credible or useful results.

## For More Info

There's bunches of books out there on medical electronics and medical instrumentation topics. Since there are so many of these, I have gathered them at [www.tinaja.com/amlink01.html](http://www.tinaja.com/amlink01.html).

Additional research on any med electronics topic is available per my *InfoPack* service you will find at my [www.tinaja.com/info01.html](http://www.tinaja.com/info01.html). Otherwise mentioned tutorial files are easy to find by using my website search.

I also have some new pulse monitor software I developed which appears exceptionally useful in chronic angina management and reversal. If you are a professional in this area, please do contact me for additional details. A credible co-author is being sought.

A few medical electronics bargains are at [www.tinaja.com/bargie01.html](http://www.tinaja.com/bargie01.html). A lot of other medical gear can be gotten as military surplus at very low prices. We saw more on this in RESBN81.PDF and RESBN82.PDF.

## This Month's Contest

As our contest for this month, just tell me about any useful, oddball, or unique medical electronics resource that I haven't already come across.

There'll be a dozen or more of my new *Incredible Secret Money Machine III* books going to the better entries. Plus an all expense paid *tinaja quest* for two (FOB Thatcher, AZ) going to the very best of all.


Send your written and snail-mailed entries on this contest directly to me here at *Synergetics*. Let's hear from you. NV

**M**icrocomputer pioneer and guru Don Lancaster is the author of 35 books and countless tech articles. Don maintains his no-charge US tech helpline found at (520) 428-4073, besides offering all of his own books reprints, and consulting services. Don also offers a free catalog full of his unique products and resource secrets. The best calling times are 8-5 on weekdays, Mountain Standard Time.

Don is the webmaster of his *Guru's Lair* found at <http://www.tinaja.com>. Full reprints and preprints of all Don's columns and ongoing tech support appear here. You can reach Don at Synergetics, Box 809, Thatcher, AZ 85552. Or send any messages to [don@tinaja.com](mailto:don@tinaja.com).

# WILL U & I B OK WITH Y 2 K?
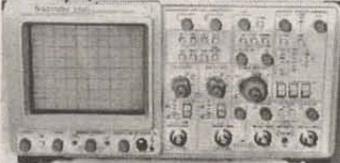
## TEKTRONIX 2465A-DM, 4 Chan., 300MHz, O'Scope, on screen waveform stats & DMM READOUT



One of the most popular & powerful scopes available at a reasonable cost. Features: 500ps/Div sweep, 2mV/Div vertical sensitivity, 1Mohm / 50-ohm input, 500Mhz trigger bandwidth, four channels. On-screen waveform cursors provide vert. & horiz. scale factors, trigger level, voltage, time, freq., phase, ratio values and mode indication. Plus complete DMM! Complete with 2 probes, pouch, cover and manual. Mint condition. 90 day warranty. **\$2695.**

## ULTRA RESOLUTION & SENSITIVITY, B/W, 1/2" CCD



Type GM-600, 425K pixels, 600 Lines res. < 0.02LUX sensitivity. Access all operating parameters from outside the camera! Adjustable shutter speed, gain, auto/man. gain, ext. sync. and gamma. 12VDC powered. Dual mounts. Sony CCD! Just the thing for astronomy, scientific or extreme low light. **SPECIAL, GM600.....\$379ea.**

## TWO MINI C-MOUNT CAMERAS, The super sensitive, GM410 or the general purpose GM412, The GM-412 specs: B&W, size 1.5"sq. X 2.4", 250,000 Pixels, 380 Lines Resolution, Sensitivity 0.3 Lux. The GM410 specs: size only 1.5" SQ. x 1.6", >270,000 Pixels, 410 Lines Res., Sens. 0.05 LUX. Both cameras are 1/3" CCD with AGC & Electronic shutter. 12V @110mA power. NTSC out. IR SENSITIVE, BNC video out. Both use std. DC pwr. jack. Aluminum housings with dual threaded top and bottom mounting. True performance not hype! These cameras will outperform ANY camera in this magazine. Multi-lens options are available to exploit their superior performance. **GM412, less lens..\$119, GM410, less lens..\$169**



Performance. **GM412, less lens..\$119, GM410, less lens..\$169**

## C-MOUNT LENS OPTIONS TO ENHANCE YOUR IMAGE: Fast Lenses for Low Light or General Purpose Normal Light


16mm, f1.6, 15' FOV.....\$39	4mm, 80' FOV.....\$24
8mm, f1.3, 40' FOV.....\$49	8mm, 40' FOV.....\$24
4mm, f1.4, 78' FOV.....\$49	12mm, 28' FOV.....\$24

## SUPER! UNDERWATER (60 ft.) "LIPSTICK" CAMERA with INTEGRAL INFRARED ILLUMINATOR!



Sleek black anodized, BRASS, housing is O-Ring sealed & WATERPROOF. Adjustable mount included. Specs: 1/3" CCD, 400 lines resolution, 0.05 Lux sensitivity, AGC, Auto Shutter. Operates on 12VDC @225mA, 3.6mm, 92° FOV lens. A real glass lens. NTSC video out. Superior construction. SENSITIVE to IR. Ultra small size only: 1.25" diam. X 2" long. With 60 ft. cable. Great for general outdoor use also. **REG. \$299, GM-300KIR.....\$219**
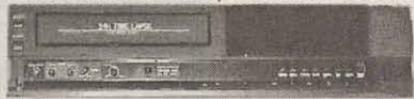
## 4 HEAD TIME LAPSE VCR, Records 24 + HOURS!



Used, refurbished, late model VICON model 424's at only 2/3 off the regular price. On screen programming, time/date stamp, audio, index search, power loss recovery and alarm inputs. Excellent, with manual. **VICON 424.... \$499**

## CLOCK RADIO COVERT CAMERA, New, Magnavox

clock radio with covert low light video camera. Specs. per GM1000A shown below. Connect to anything with a "video In" jack. via RCA style output. Also available wireless model, CRC-2W transmits to cable ready TV or VCR on cable channel 59, up to 500ft. No separate receiver req'd. **CRC-1std.. \$129.00 or CRC-2W, Wireless..\$279ea.**

## COVERT CAMERAS available with audio, 1/3" CCD, 410 Lines Res., 0.2 Lux sens., Pwr. from 9 to 12VDC @100mA, 90° FOV lens, All focus from 3 ft. to infinity. NTSC video out. SENSITIVE to IR. note: Smoke & Motion detectors not functional, Clock & Exit operate normally. Dome is 3.5" x 5.5" Diam. Covert Clock, Smoke Detector, MotionDetector or Dome Camera any model.....\$119

Exit Sign.....\$139 add \$10 for audio.



## NEW MICRO CAMERA, w/audio

1/3" CCD, 410 Lines Res., 0.3 Lux sens., AGC, Auto Shutter. Pwr. from 9 to 12VDC @100mA, 250K PIXELS, Std. model, 3.6mm, 92° FOV lens, Pinhole, 90° FOV. A real glass lens. Both focus from 10mm to infinity. Std. NTSC video out. 1/2 once! SENSITIVE to IR. Size Std: 1.25"sq. x 1.0" d. Both with 6' leads. **WARNING: Don't confuse these models with LOW RESOLUTION, HIGH LUX C-MOS CAMERAS. Six models to choose from.**

GM-1000A-STD.....\$80	GM-1000A-STD/Aud.....\$85
GM-1000A-PH.....\$80	GM-1000A-PH/Aud.....\$85
GM-1000A-CMNT.....\$80	GM-1000A-CMNT/Aud.....\$85


Micro Lenses for GM1000 series	
2.5mm, 150°.....\$22	8.0mm, f2.0.....\$22
4.3mm, 78° f1.8.....\$22	12.0mm, f2.0.....\$22
6.0mm, f2.0.....\$22	5mm, 70°-PH.....\$22

## SEE in TOTAL DARKNESS! WEATHERPROOF IR FLOOD,

48 powerful LED's project a 40 deg. FOV beam up to 45 feet. Automatic on at dusk off at dawn! 110VAC power. Rugged anodized aluminum, housing with adjustable mtg. bracket Size: 4"x5"x6.3". Commercially made. Brand New! **WPIR....\$179ea.**



## SCIENTIFIC, 1/2" COLOR CCD CAMERA

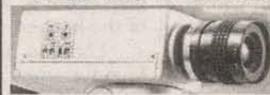

- YC/SVHS output
- 380K Pixels
- 460 Lines
- <1 lux Sensitivity

All parameters adjustable from outside camera! Perfect for microscopy, inspection, capture or surveillance. Features internal or external sync, Interlaced or N/I, Adj. shutter, 1/60 to 1/10000 Sec., Auto White balance with three steps, Auto iris output, C or CS mount, Manual/auto gain or ext. variable gain. BNC video out, 12V@250mA pwr., via std. barrel jack. The GM470-C has it all! Aluminum housing. Size: 50mm W x 50mm H x 145mm L. **New, GM470C, less lens.....\$499ea.**

## WEATHER RESISTANT Camera Enclosure

Solid, extruded aircraft aluminum. Glass window. Strain reliefs for cables. Size: 3.5" w x 3.7" h x 14" L.



Special Price.....\$59ea. with 110VHEATER...\$69ea.

## PRICE BUSTER, DSP, COLOR CAMERA,

Brand New, model GM550, Size: 1.6" x 1.6" x 1.5", 1/3" CCD with SONY CCD & DSP technology. 4mm, f1.8 glass lens, 80° FOV. Resolution >350 lines, sensitivity, 0.3lux, AWB, AGC & auto electronic shutter 1/60 to 1/10,000 sec. Pwr. 12VDC @160ma. NTSC out. Budget color surveillance. **GM550-STD.....\$149ea. GM550-PH.....\$149ea.**

## CHECK THIS! ULTRA MINI and WEATHERPROOF Our "LIPSTICK" camera sets new standards.

Sleek black anodized, aluminum, housing is O-Ring sealed & RAIN-PROOF. Adjustable tilting mount included. Specs: 1/3" CCD, 380 lines resolution, 0.3 Lux sensitivity, AGC, Auto Shutter. Operates on 9 to 12VDC @100mA, 3.7mm, 90° FOV lens, A real glass lens. NTSC video out. 1/2 once! SENSITIVE to IR. Ultra small size only: 23mm diam. X 50mm long. With 36" cable with BNC video and DC barrel jack. **GM-200KSTD...\$99 pwr. adapter..\$4.95**

## "EMBEDDABLE", PINHOLE LENS, "BULLET CAM" it's INCREDIBLE!

So tiny you can install it right into a door with merely an 0.9" diameter hole. Sleek black anodized, extruded aluminum housing. Similar construction as the lipstick camera above only smaller! 1/3" CCD, 410 lines Res., 0.3 Lux sens., AGC, Auto Shutter. Power from 9 to 16VDC @100mA, 250K PIXELS, 90° FOV Pinhole lens. A real glass lens. Std. NTSC video out. 1/2 once! SENSITIVE to IR. Size only 23mm Diam. x 35mm long. With 36" leads. Think of the places you could put this little jewel. **GM-200KPH lens, \$99**

Please fax us your list of unique surplus material.

## 6V @ 12 AH SEALED, RECHARGEABLE, LEAD ACID BATTERY



Brand new Panasonic type LCR6V12P, tough to get at a discount. Very compact. Use two for a 12V @ 12AH pack. Two top mounted 1/4" faston connectors. Perfect for robotics and other high drain applications. Size: 5.9" L x 3.7" H x 1.97" D. **REG. \$18ea. NOW 2 for \$20, or 10 for \$89**

## PRICE BUSTER, DSP, COLOR, MINI C-MOUNT, CAMERA, New, model GM859,

Size only: 2" x 2" x 2.5". Latest 1/4" CCD technology. Res. 350 lines, sens., <3lux, auto white balance, AGC. Auto iris connector. 9-12VDC @150ma power. BNC video out. Switchable gain. Superior cast aluminum housing with top and bottom mounting. Perfect for general surveillance. Less lens. **Reg. \$299, Save \$100, Special, GM859..\$189ea.**



## NEWPORT, 495A MOTORIZED, ROTARY STAGE,

Bidirectional 360° continuous rotation, 0.001° res. Integral DC motor & encoder. Load independent velocity servo. Mount in any orientation. Capacity: 55lbs. Size: 4.75"x5"x1.35" with 2" clear aperture. **Reg. \$2141, Our Price \$795**

## COMPACT 3mW ARGON LASER. Super brilliant turquoise beam.

Looks as bright as a 20mW HeNe! New, Uniphase 2202-3 with pwr. supply. The 488nm, TEM00 mode is something to see! The power is in the wavelength. This highly visible beam operates where the eye is most sensitive. Very impressive for it's size. Head only 2.5" diam. and 13" long. Plug and play operation. Standard 110VAC operation. Compact power supply and fan cooled head. Less than 1/4 the price of a new one. Photo not available at pres time. **Reg. \$3000 Our price.....\$695ea.**

## \$5000 HI-TECH SURVEILLANCE SYSTEM, NOW REDUCED 82%!

**THIS SUPER SYSTEM INCLUDES:**

- MOTORIZED, 6X ZOOM LENS
- MOTORIZED, 360° CONTINUOUS PAN
- MOTORIZED, TILT up to 90°
- PHILIPS HIGH RES. 1/2" CCD CAMERA
- OPAQUE BLACK INNER DOME
- CLEAR ACRYLIC OUTER DOME
- ZOOM LENS CONTROLLER with A/I
- PAN and TILT CONTROLLER


Walk into any major dept. store and you will see these fully integrated systems. From the same mtg. who supplied the Atlanta Olympics! These late model, new in the box systems are virtually ready to use. All you add is power. Philips B&W CCD camera, 450 lines res., 0.5 Lux sensitivity! Their best grade CCD. Anodized aluminum construction. Camera plus Pan & Tilt are powered by external 24VAC via the included Pan & Tilt controller. Motorized, Zoom, Focus and Iris Controller also included. Size of dome: 14" diam. Includes mount for drop ceiling. **COMPLETE SYSTEM SPECIAL.....\$895ea. or 2 for \$1699**

## WORLDS SMALLEST

... 100mW ...

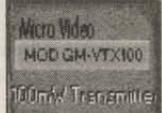
## VIDEO TRANSMITTER,

Incredibly only 0.98" x 0.8" x 0.037" in size. Transmits crystal controlled hi-res. images with 100mW output! The transmitter you've been waiting for. Shows actual size. Much smaller than the 9V battery which powers it. Draws only 35mA! Factory tuned ready to receive on cable channel 59. Will work with color & B&W cameras. UHF Bow tie antenna with balun and 3' F cable for TV included. Perfect with our GM1000A cameras. Both will fit in a cigarette pack...with the battery! The best deal anywhere. **TVX-100..\$189. with GM1000A-PH CAM...\$259.**


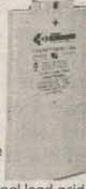
## YOU CAN NEVER BE TOO THIN or TOO POWERFUL. Unique Thinline Energy Cell from Portable Energy Products.

Their model PLA02V50. A super thin, high performance, patented technology, sealed lead acid battery. Each cell provides 2V@5AH. Their size is an amazing 3.1" x 5.3" x 0.3" thick! They can be mounted in any orientation. Can line the bottom of a briefcase or be covertly worn on the body. 30% higher energy density than conventional lead acid batteries. **Price 6 cells for \$15 or 24 for \$49**



# RESOURCES UN-LTD.

300 BEDFORD STREET, MANCHESTER, NH 03101

VISA, MC, AMEX, DISCOVER, COD. ORDER: 800-810-4070 TECH. 603-668-2499 ORDER FAX: 603-644-7825 E-MAIL unltd4u@tiac.net

Write in 85 on Reader Service Card.

Nuts & Volts Magazine/January 1999 75

# CURI vs. Cat

by George Katz

**F**or many years now, I have searched for practical uses for my robots, including my latest research project into behavioral control software that simulates a pet's behavior.

Most of my previous projects have been solutions looking for problems until last Thursday evening, when my wife and I discovered a visitor in our house. We were first alerted to the presence when I discovered a little (well not that little) cat surprise by the door. I thought this was strange because


20 seconds or so.

When the cat ran to the kitchen, I could not believe my eyes when I saw it disappear into a small hole about 4" x 5" in the kickboard of the kitchen counter.

Looking through the hole I found a small crawl space just big enough for the cat. There was no way we could reach in and grab it, the hole just was not big enough for an arm and cat to fit through. We agreed more bait would get it out.

Not wanting to drill a big hole in the cupboard, we needed a trap that would close off the hole when

Figure 1.  
CURI-4 —  
the cat  
hunter.

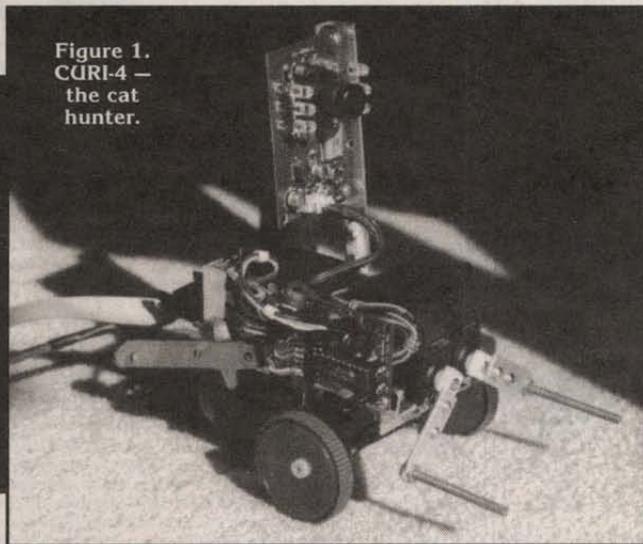

we do not have any pets. We looked through the house and could not see any signs of a cat, or whatever it was, and hoped that it was gone by now.

The next morning Amanda put a small dish of assorted food on the floor of the kitchen as a precautionary measure to see if it really was gone.

At lunch time, we came home to find that the creature liked the tuna, not hot-dogs. We opened all the doors to the outside and searched the house to find a black cat hiding by the hot air vent in the living room. Though we chased the cat into another room where the door was open to the outside, we never saw it actually leave. Needless to say, we were still a little suspicious. With lunch hour running out, we closed all the doors and put another dish of food out to see if anything would bite. What has this to do with robots? I will get to that soon enough.


In the evening when we returned home, we knew to look for the cat by the heating vent. We opened all the doors again and the chase was on! At least for the first

the cat came out. For a computer engineer, it did not take long to think of a solution involving a robot.

Just a week earlier, I finished building a small mobile robot named CURI-4, equipped with a small CCD camera and a gripper. CURI is tethered to a 486DX40 PC which is equipped with a frame grabber for capturing images. The camera is equipped with infrared LEDs allowing it to see in complete darkness for a distance of around 10 feet.

CURI's drive mechanism consists of two individually powered wheels each driven by a geared DC motor. CURI also has a servo which controls the pitch of the camera, two servos that are used by the gripper, and a fourth servo is used for a leg that allows the robot to raise or lower the gripper. The camera can be positioned so that it can see the objects the gripper is picking up. CURI's size is a mere 7.5" x 7" x 4" (20 cm x 18 cm x 10 cm), and even shorter with the camera fully retracted. Naturally, I tried to see if CURI would fit in the hole

Figure 2.  
CURI-4  
poised to  
trap the cat.

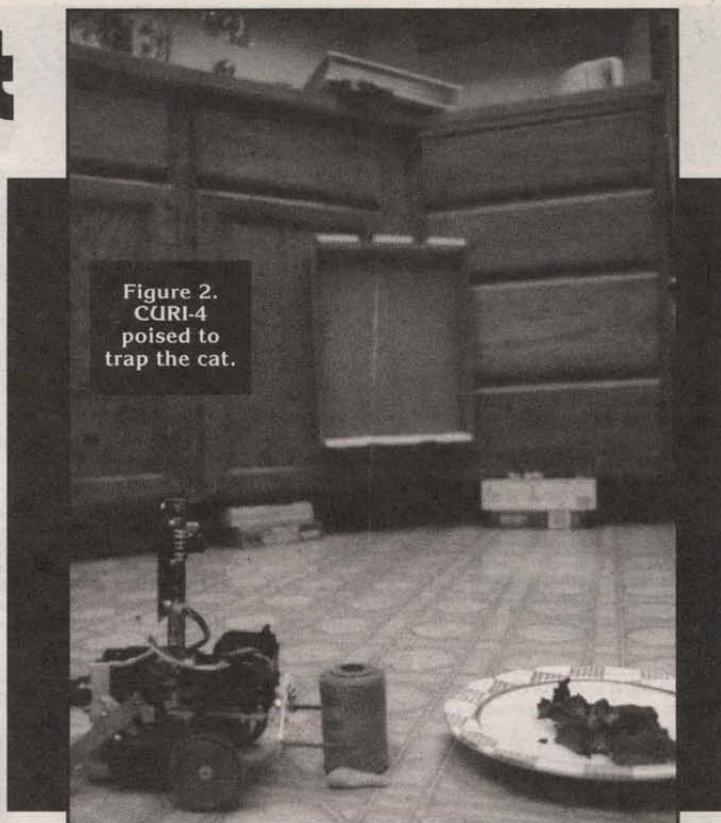

so it could drag the cat out by the tail, but the hole was just too small.


Normally, CURI's primary behavior is to play with a ball. This involves finding it, picking it up, and hiding it. For convenience, it forgets where the ball is hidden and repeats the finding/hiding behavior. Superimposed are higher priority behaviors that help CURI avoid obstacles and deal with other real-world situations. For example, if CURI hears a loud noise, it suspends the ball finding/hiding behavior and attempts to hide itself in a dark corner. After a period of silence, the original behavior resumes. All this hardware and software was about to meet its first simple, but practical test.

I recalled that about six months ago, I wrote a very sensitive motion detection program that worked with

the camera onboard CURI. In 30 minutes, CURI's behavioral software was reprogrammed to move one of her gripper arms when it detected any movement. I suspended the lid of a cardboard box above the hole by a thin thread and wound it several times around a makeshift pulley. I then led the thread to CURI, which was positioned on the floor about three feet away from the hole where CURI's camera was aimed at the third dish of food. I placed CURI so that its gripper would release the spool of thread which lowered the trap door. After several trial runs and fine tuning, the trap was set! We turned off the lights and went to bed.

As I fell asleep thinking about CURI doing battle with the cat, (CURI's behavioral software telling her to move anytime the cat did), a

Figure 3. Through the eye of CURI-4 — infrared image of food bowl taken in complete darkness.

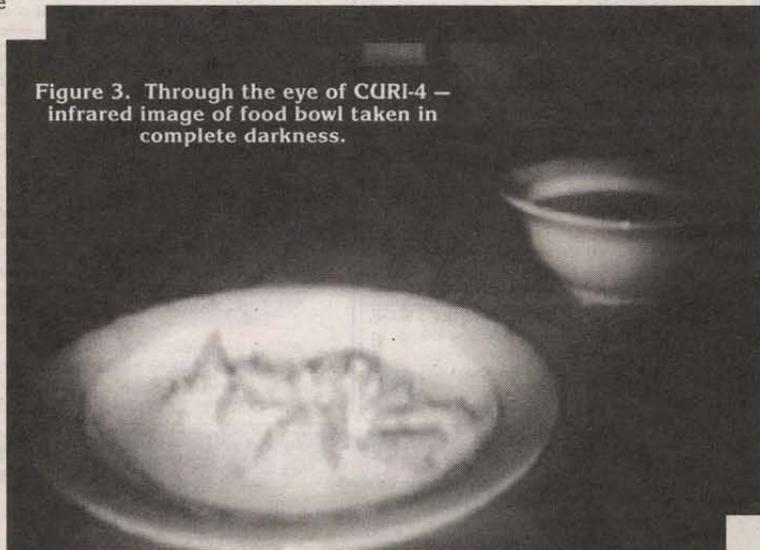

horrible thought struck me. "Hang on ... cats eat little moving things!" However, I was confident that the cat would take one look at the robot and laugh (in a cat sort of way).

Thud!! Two A.M. Amanda wakes me up and we found a vase lying on the carpet. The cat was out. I rushed to see if CURI survived the fight. CURI was sitting there, spool knocked over and trap door shut!!! I could see that CURI was happy to see me because it was moving its gripper back and forth.

"It worked!!" I shouted as Amanda pointed out that the cat was still somewhere in the house. I put a couple of paperback books over the hole and we went to the cat's favorite resting place (when it was not in the hole). Again, the chase was on. The cat did not hesitate this time, 10 seconds later it was dashing for the hole in the kitchen. We were both shocked when we saw the cat struggle with the books and manage to push them out of the way and slip back in the hole. Arrrrggghhh!!! CURI just sat there waving at us.

We decided to just wait until morning to see if the cat would come out. We put more food out, but by now the cat had more food in it than our fridge. By 7 A.M., no more food was touched and we resolved to drill a hole in the cupboard. Five minutes later Amanda reached in the new hole with thick gloves and the cat ran out through the little hole. We now placed heavy pots and pans and books and anything else not bolted to the floor over both holes. We found the cat again and with all the doors opened, it finally was last seen scrambling across the green lawn outside. Hopefully heading for another kitchen.

I guess the moral of the story is, a robot can be programmed to do something useful, but you can't teach a cat to eat hot dogs!

If you prefer fully-autonomous robots over tethered robots, check out my previous project: CURI-3 developed in 1994 for the University of New South Wales Artificial Intelligence Lab in Sydney Australia. CURI-3 is a fully autonomous mobile robot with a built-in IBM PC and stereo cameras. Currently it is being used for a number of research projects. **NV**

**For further details about the cat or any of my robots, please visit my web page:**

<http://www.geocities.com/SiliconValley/Lakes/7156>

or E-Mail me at: [gkd@rtassoc.com](mailto:gkd@rtassoc.com)

## Events CALENDAR

Continued from page 27

County Fairgrounds, Hwy. 11 S. 8am-3pm. Doug Burt W4OFO, 252-524-5724  
**NJ - TRENTON** - Hamfest. Delaware Valley Radio Assn., Darryl Foyuth N2JVP, 609-882-2240  
 E-Mail: n2jvp@amsat.org

**OH - MAUMEE** - Hamfest. Lucas County Recreation Center, 2901 Key St. 8am-2pm. Talk-in: 147.27+ or 442.85+. Toledo Mobile Radio Assn., Paul Hanslik N8XDB, 419-243-3836.  
 Web: <http://www.tmrhamradio.org>

**WV - CHARLESTON** - Hamfest. Charleston Area Hamfest & Computer Show, Jimmie Hewlett WD8MKS, 304-768-1143

### MARCH 27

**CT - WATERFORD** - Auction. Waterford Senior Center, Rt. 85. Talk-in: 146.730. RAS of Norwich, Tony Griggs AA1JN, 860-859-0162.  
 Web: [www.lms.uconn.edu/~rason](http://www.lms.uconn.edu/~rason)

### MARCH 27-28

**MD - TIMONIGUM** - Maryland State Convention. Sharon Dobson N3QQC, 410-HAM-FEST (Box 3772), 1-800-HAM-FEST (Box 3772). E-Mail: n3qqc@amsat.org Web: <http://www.gbhc.org>

### MARCH 28

**CA - SANTA ANA** - Swapmeet. ACP parking lot. Mary Russo 714-558-8813  
**OH - MADISON** - Hamfest. Lake County ARA, Roxanne, 440-256-0320

## APRIL 1999

### APRIL 2-3

**OK - MOORELAND** - Hamfest. Tri-State AR Group, Duane Henderson KC5NID, E-Mail: kc5nid@pdl.net

### APRIL 3

**CA - SANTEE** - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052

### APRIL 9-10-11

**CA - FRESNO** - Int'l DX Convention. Gordon Girtan W6NW. E-Mail: gordon@svpa.org  
 E-Mail: w6nw@amateur-radio.org  
 Web: <http://www.amateur-radio.org/ncdxc.org>

### APRIL 10

**CA - FONTANA** - Inland Empire ARC Amateur Radio & Electronics Swapmeet. A B Miller High School. Bill 909-822-4138 eve

**MN - ROCHESTER** - Hamfest. Rochester ARC, John Scott N0HZN, 507-285-6522.  
 E-Mail: n0hzn@aol.com

Web: <http://members.aol.com/rarchams/>

**NC - MORGANTON** - Hamfest & Computer Fair. Burke County Fairgrounds, Hwy. 181N (Exit 100 Eastbound, Exit 105 Westbound I40). 8am-5pm. Talk-in: 147.15 (K4VLY repeater). Catawba Valley, Tom Tayler, 704-433-6205.  
 E-Mail: kc4qpr@vistatech.net

**WA - SPOKANE** - Hamfest. Lilac City ARC,

PRODUCTS      FEATURES      ORDER      NEWS      LINKS



# Black Feather ELECTRONICS

Black Feather Electronics  
 10841 Noel St. #106  
 Los Alamitos, Ca. 90720

DIRECT DIAL: (714)236-1776 FAX: (714) 236-1778 E-MAIL: [blkfea@juno.com](mailto:blkfea@juno.com)

## WWW.BLKFEATHER.COM

WE BUY EXCESS/SURPLUS ELECTRONIC SUPPLIES

Write in 143 on Reader Service Card.

Warren Kelsey KJ7BB, 509-534-8443

### APRIL 11

**NC - RALEIGH** - RARSFest. State Fairgrounds. Raleigh ARS, Wilbur Goss WD4RDT, 919-266-9883. E-Mail: k4hf@juno.com

**WI - MADISON** - Hamfest. Madison Area Repeater Assn., Paul Toussaint N9VWH, 608-245-8890. E-Mail: n9vwh@hotmail.com

### APRIL 17

**AL - ALBERTVILLE** - Hamfest. Marshall County ARC, Buddy Smith KC4URL, 256-593-2516.  
 E-Mail: kc4url@airnet.net

**CA - SANTEE** - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052

**ID - IDAHO FALLS** - Hamfest. Eastern Idaho UHF Society, Jay Greenburg WA4VRV, 208-524-1388. E-Mail: wa4vrv@srv.net

Web: <http://www.srv.net/~wa4vrv/hamfest.htm>  
**KY - MURRAY** - Hamfest. Murray State University ARC, Pat Compton KF4FMZ, 502-762-6433.  
 E-Mail: patrick.compton@murraystate.edu Web: <http://mursuky.edu/clubs/msuarc/hamfest.htm>

**MO - JOPLIN** - Hamfest. Joplin ARC, Ray Brown KB0STN, 417-781-4967. E-Mail: raybrown@ipa.net  
 Web: <http://www.joplin-arc.org>

### APRIL 18

**CT - HARTFORD** - 1999 Trinity College Fire-Fighting Home Robot Contest. Trinity College campus. Jake Mendelsohn, 190 Mohegan Dr., West Hartford, CT 06117.  
 E-Mail: JMENDEL141@AOL.COM

Web: <http://www.trincoll.edu/~robot>

**MA - CAMBRIDGE** - Flea Market. Kendall Square area. MIT. Nick Altembernd KA1MQX, 617-253-3776. Web: <http://web.mit.edu/w1mx/www/swapfest.html>

**PA - MONROEVILLE** - Hamfest. Two Rivers ARC, Michael Kowalcheck, Jr. KV3L, 412-751-9657

### APRIL 23-24

**AR - LITTLE ROCK** - Hamfest. Jim Blackmon K5VZ, 870-246-7833. E-Mail: lrhamfest@usa.net  
 Web: <http://www.aristotle.net/~ares/hamfest/>

### APRIL 24

**IA - DES MOINES** - Hamfest. Des Moines RAA, Duane Bower WB0JCY, 515-287-6542

**NJ - HARMONY** - Hamfest. Warren County Farmers Fairgrounds, Rt. 519 N. 8am-2pm. VE Exams. Talk-in: 147.375+ 146.730. Cherryville RA II, Inc., Randy Vance N2MQZ, 908-788-4080 or 908-454-4370. E-Mail: n2mqz@aol.com

**VA - CHESAPEAKE** - Hamfest. Chesapeake AR Service, Jim Cannon KF4RQQ, 757-382-0193

**WA - VANCOUVER** - Hamfest. Clark County ARC, Luther Brisky KC7KVL, 360-896-8909 or 360-254-5082. E-Mail: lwayne@e-z.net  
 Web: <http://www.w7a.org>

### APRIL 25

**FL - GAINESVILLE** - Hamfest. Gainesville ARS, H. Walter Johnston W4TKE. E-Mail: w4tke@juno.com E-Mail: w4tke@gator.net

**IL - ARTHUR** - Hamfest. Moultrie ARK, Ralph Zancha WC9V, 217-873-5287 or 217-543-2178. E-Mail: rzancha@one-eleven.net Web: <http://home.stlnet.com/~jhudson/hamfest.html>

**OH - ATHENS** - Hamfest. Athens County ARA, Drew McDaniel W8MHV, 740-592-2106.  
 E-Mail: dmcdaniell@ohiou.edu

## MAY 1999

### MAY 1

**CA - SANTEE** - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052


**TN - NASHVILLE** - Hamfest. Nashville ARC, Bob Malone WB5ZDS, 615-865-6225

**WI - CEDARBURG** - Hamfest. Ozaukee RC, Joe Holly AA9HR, 414-377-2137

## ADDRESSABLE STEPPER MOTOR CONTROLLER

Part Number: JWP1X-1A

**\$199.95**

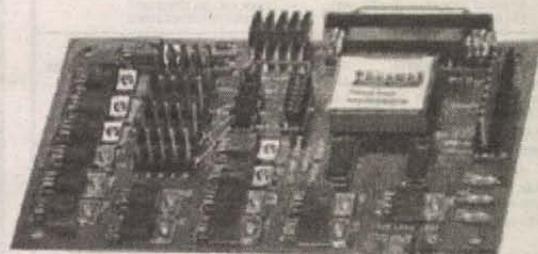

**PARAMAX INC.**

**(800) 473-8080**

Come and visit us on the internet at:

[www.paramax.net](http://www.paramax.net)

The PARAMAX stepper motor controller is a PC parallel port based addressable controller capable of simultaneous operation of 4 uni-polar stepper motors ranging in voltages from 5 to 12 volts at up to 2 amps per phase. The PARAMAX stepper motor controller includes 8 digital inputs with a data through put rate of 500k bytes per second. Using the unique PARAMAX addressing method, up to 256 controllers can simultaneously function from a single parallel port. The programming package includes libraries that allow you to create applications both under Windows and DOS. Included libraries are: C++, Pascal, Delphi, Basic and utilities for DOS and Windows.

Also available at:  
**FORD ELECTRONICS, INC**  
 (714) 521-8080



you back your bucks.

## COST-EFFECTIVE IAMBIC KEY

I love my Bencher paddle. It's nice and heavy so it won't scoot around the operating table, and it looks impressive by its exotic springs-and-things construction. Any good ham CB operator runs the Bencher paddles.

But for a day out on the road where you don't want to take along a heavy paddle to go along with your memory keyer or rig with a built-in automatic keyer circuit, for under \$20.00 you will marvel at the K9LU micro iambic key, made up of brass buttons and what appears to be office supply clip. It's all mounted on a nice piece of wood with suction cups and 30-inch pre-wired cable with 3.5mm plug.

When we tried it out, we were amazed that the feel of the key was superb. To increase or decrease the spacing between the contact points, you give a little finger pressure at the appropriate spot as detailed in the brief instructions. Same thing with tension — a little finger pressure gets you just the right feel for this unique CW sending set-up.

I'm going to order a couple more to give my CW buddies a gift that they have never seen before! The thing is darn-right cute, and works swell. They also have a memory keyer that goes along with the iambic key, too.


Look at it on the web at <http://www.qth.com/k9lu>, or phone them for a brochure at 630-443-8822 in St. Charles, IL. The electronic memory keyer is put together by W9XT, and the little paddle set from Louis Petkus K9LU. The key runs under \$20.00; and if you want to do your own with the parts they supply, it's only \$10.00! The memory keyer runs around \$80.00. Look them up on the web. A terrific gift item, even though the holidays are over.

## ICOM 706 AUTOSHIFT

I see that the new ICOM IC-706G with the added 440 capability now includes automatic offset for the VHF and UHF bands. Thank goodness. With any ICOM IC-706 Mark I or Mark II transceiver, two-meter repeater operation always requires several keystrokes to program-in the appropriate minus or plus offset. When it comes to a plus offset, it takes some extra steps to get your transmitter 600 KHz above RX as opposed to the easier minus 600 KHz. These extra keystrokes make it almost impossible to program two-meter repeaters when driving down the street.

The Autoshift 706, designed by KO6YD, will automatically set the VFO-B to the proper offset with split enabled on two meters, six meters, and even the FM repeaters on 10 meters. As you tune around with VFO-A, the split will be disabled. When you stop tuning, VFO-A will be the repeater output receive frequency, and VFO-B automatically enables split and automatically selects the offset through the ARRL band plan. And since there are several different six-meter band plans, there is a jumper that allows you to roll your own.

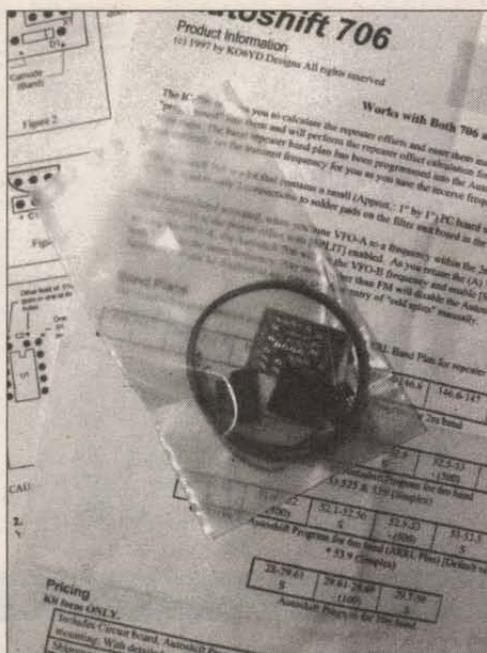
When you next tune to a simplex frequency, such as 146.520 MHz, the Autoshift 706 now puts both VFOs onto the same frequen-



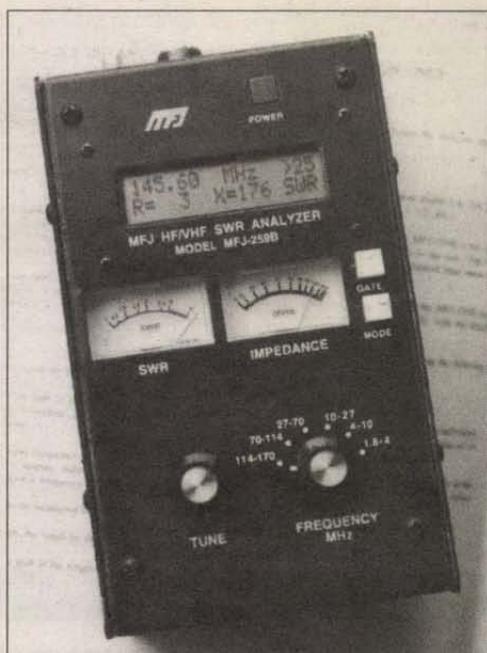**THE AUTOSHIFT 706 WORKS WITH THE ICOM 706 MARK I AND MARK II. IT ASSEMBLES IN LESS THAN AN HOUR AND WIRES IN LESS THAN 10 MINUTES!**

cy. And you can still disable the autoshift in case you want to work VFO-A and -B on a repeater odd split.

This is a kit project. But don't panic — the KO6YD designed board has all components labeled on the board, and it took one of our students only about 20 minutes to drop in the handful of components. We liked the idea of the chip socket to provide for easy installation of the Autoshift processor. "It will also allow future enhancements to be made by replacement of the processor chip," comments KO6YD Designs. "But we caution everyone to remember that the Autoshift processor is sensitive to static electricity, so please take precautions to avoid a



**THE MFJ SWR ANALYZER COMES IN MANY VARIETIES, FROM \$99.00 TO \$259.00.**

static discharge when handling the chip."

Installing the Autoshift inside the IC-706 is a simple three-wire connection. One wire goes to +8 to +15 VDC, one wire to ground, and one wire to the CI-V data connection. The actual board is mounted in the area just to the left of the optional filter modules in the front-left of the radio.

Once we got our 706 up and running with Autoshift, getting onto repeaters was a snap. Putting them into memory was also a snap. Just be sure to remember that on the IC-706 Mark II, you must drop the tone into VFO-B to encode CTCSS for proper operation. If you are a Mark II owner and you can't seem to bring up certain repeaters, chances are you probably have

## TONER CARTRIDGE RECHARGE

& Laser/Printer Supplies

**CALL NOW FOR YOUR FREE CATALOG #13!**

Instruction Manual  
Free with starter kit

Video Training Tapes  
choose from our library

Catalog #13  
100 pages  
**FREE!**

Marketing Flyers  
with customized pricing

Printer/Copier/Fax  
Cross Reference  
68 pgs-Free with any order

- Black, Color & MICR Toners
- Tools and Accessories
- Technical Support

- Cartridge Parts
- Video Training Tapes
- OPC Drums and Belts

- Ink-Jet Refill Supplies
- Graphic Black Toner Kits
- MICR Toner Kits

Visit our website at

[www.chenesko.com](http://www.chenesko.com)

for all the free tech documents, Sales Specials and the latest industry news!

Chenesko Products, Inc.  
2221 Fifth Ave., Suite 4,  
Rochester, NY 14727  
Fax: 315-457-2222  
E-Mail: [chenesko@aol.com](mailto:chenesko@aol.com)  
<http://www.chenesko.com>

800-221-3516

## ATTENTION DEALERS/DISTRIBUTORS

**BUY DIRECT FROM THE MANUFACTURER**

THESE AND OTHER VIDEO SECURITY PRODUCTS NOW AVAILABLE!!! (DEALERS/DIST. ONLY) Minimum Order.

	Qty	Qty	Qty	Qty
CCD Cameras	5	10	20	50+
B&W Board	\$57	\$52	\$47	Call!
B&W Board/sound	\$62	\$57	\$52	Call!
B&W Mini	\$65	\$60	\$55	Call!
Color - Mini	\$150	\$142	\$135	Call!

\*B&W CCDs use Sansome Chips. Color CCDs use Sony.






### CCD Camera Hidden Inside a "Magnavox" Clock

	Qty	Qty	Qty	Qty
CCD Clock	5	10	20	50+
B&W Wired	\$144	\$129	\$114	Call!
B&W Wireless	\$289	\$264	\$248	Call!
Color Wired	\$234	\$218	\$199	Call!
Color Wireless	\$387	\$362	\$345	Call!

Wireless use 2.4GHz standard transmitters and receivers.

### Call ATN Today for the Best Prices and Quality Security Products.

American Technologies Network Corp.	1(800)910-2862
20 S. Linden Ave. #1B	1(650)875-0130
S. San Francisco, CA 94080	fax: 1(650)875-0129
<a href="http://www.atncorp.com">www.atncorp.com</a>	sales@atncorp.com

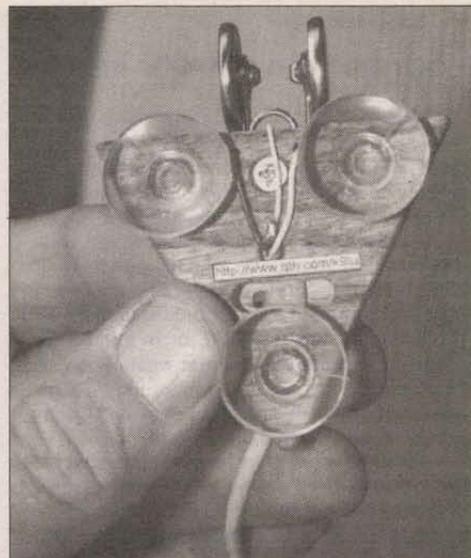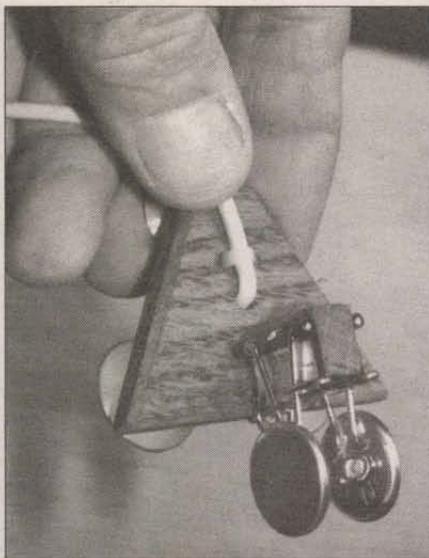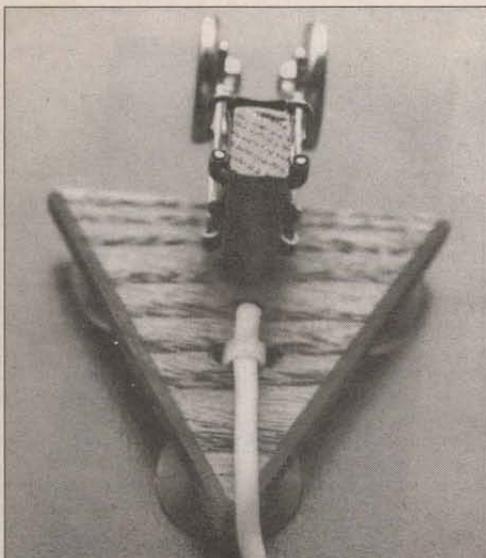

THE MICROPADDLE WORKS GREAT! A PERFECT GIFT, EVEN AFTER THE HOLIDAYS ...

encode on VFO-A, instead of where it should be on VFO-B. Check it out.

The Autoshift 706 comes with detailed assembly and operating instructions, and it is available for under \$35.00. You can look it up on the web at [www.jps.net/k06yd](http://www.jps.net/k06yd), or phone KO6YD Designs at 916-728-4539 in Elverta, CA.

#### THE MINDS AT MFJ

The company name MFJ stands for the initials of Martin F. Jue K5FLU, MFJ's president since the company started in 1977. MFJ offers hams, scanner enthusiasts, radio-computer folks, and shortwave listeners over 1,000 products, gadgets, and accessories. MFJ is also Ameritron — the linear amplifier people on HF — and Mirage — the VFH and UHF power amplifiers. They are also Vectronics — kits and finished radio equipment and accessories for the more technical radio enthusiast.

I am convinced that MFJ must allocate one day a month just for brainstorming. I can see a board room filled with half their active radio employees coming up with ideas on new products or figuring out ways to make what's already out there in the radio place more-trick and more-affordable.

The MFJ product line has matured, too. They continue to upgrade their production lines to insure all equipment going out is indeed tuned, tested, and "hot" out of the box. Richard Stubbs KC5NSZ, MFJ's customer service manager and active ham operator, backs up his claims of total customer satisfaction by being readily available on an 800 number without having to go through any arduous voice-mail key-strokes. I tried the 1-800-647-1800, and I got right through on the first ring!

The products I tried out were their new two-meter FM analyzer (MFJ-224), their new MFJ HF/VHF SWR analyzer (MFJ-259B), and their

brand new 45-amp switching power supply (MFJ-4245MV).

Starting with the switcher power supply, my big interest was whether or not it was noisy on HF and VHF frequencies. It was quiet. In fact, so quiet that you could easily listen to an AM radio station with a little portable radio inside the shack without the switcher power supply tearing things up. And I tested the switcher at full idle, as well as powering a big marine SSB with 30 amps draw.

The 45-amp switcher weighs only 5.5 pounds, making it ideal to take along into the classroom to run all sorts of ham equipment. We also tested it for shutdown in the presence of a strong RF signal — no problem. With other transformer-type power supplies, many would actually cycle off in the presence of a strong RF source. The switcher did not.

The MFJ switcher power supply lets you vary the voltage from 9 volts to 15 volts DC.

Sorry, nothing below 9. Nice three-inch meters are backlit to make it easy to monitor both your voltage, as well as load currents. A built-in fan turns on when the power supply is switched on, and runs relatively quiet.

We would have liked to have seen larger red and black binding posts for the 45-amp version of the power supply. If you're going to be running this kind of current, the red and black binding posts are tough to get the wire around unless you use lugs. But other than that, the switcher is doing just fine in the classroom.

The SWR analyzer, Model 259B, is the granddaddy of all MFJ SWR analyzers. Besides testing an antenna for minimum SWR, it can also indicate impedance, reactance, resistance, bandwidth, and resonant frequency. And if you're into doing your own antenna tuners, it puts out about 20 milliwatts which is more than enough power to tweak your output and input matching networks, along with chokes, suppressors, traps, and other tuned circuits. The output is also strong enough to let you put a signal out on the air to

## CABLE TV CONVERTERS

WILL NOT DECODE

The Best Prices and Service • In Business over 15 years!

Phone 218-346-6660 Fax 218-346-6664

### TIMELESS PRODUCTS

New! "TP 125 V"  
128 Channel Converter with Volume

Special Prices for  
TP1550PC  
Call for Details

Panasonic still available!

- REFURBISHED CONVERTERS ALSO AVAILABLE •
- QUALITY REPAIR DEPARTMENT FOR ALL YOUR TUNER REPAIRS •
- REMOTES AVAILABLE FOR MOST CABLE BOXES •

DEALERS ONLY • GREAT QUANTITY PRICES • NO DECODER SALES

adjust your receiver and antenna tuner on receive for maximum input.

I liked running the receiver on a specific frequency, and then listening for the SWR analyzer as I would zero in on the operating frequency without having to look over at the LCD readout. I suppose this is also a good check for a receiver that is either good or blown.

The MFJ 259B also has more advanced features for hams "rolling their own" to check the resonant frequency and approximate "Q" of traps and tuned circuits, plus the value and self-resonant frequencies of small capacitors.

You could also measure coax loss by hooking into the 50-ohm cable with the opposite end of the coax having an open circuit, or a short circuit, or a pure reactance. You can also calculate impedance, return loss and reflection coefficient, distance to coax fault, resonance, and efficiency. These are covered in the "advanced operation" portions of the instruction manual; and if you regularly work on antenna projects, this meter may be the one for you.

But did you know that MFJ also makes HF, as well as VHF SWR analyzers for UNDER \$100.00? They don't have the digital readout, but they work dandy in sweeping the band or bands, and indicating where the dip of SWR is found. To spot the exact frequency, simply dial around with your radio hooked up to a short piece of wire, and "spot" where the meter is indicating. The tuning dial is rather coarse, but your simple receiver can spot you right down to the Kilohertz.

We also tested the new two-meter FM analyzer. This battery-operated receiver tunes from 143.5 to 148.5 and monitors many important signal parameters found on the two-meter band. If you just want to use it as a VFO receiver, plug in a set of headphones and tune around.

Where there is a lot of two-meter activity, tune around SLOWLY. We found the big capacitor tuning circuit relatively sensitive and properly locking into a signal required the dexterity of a watchmaker. This is especially true if the weak signal you are trying to tune in is right beside a strong signal. In fact, in trying to pull out weak signals from strong signals, tune with the FM analyzer in the discriminator mode, and go for ZERO on the large front panel meter.

You can also check for field strength in dBm, as well as FM deviation in Kilohertz. But do this after you have dialed in the appropriate two-meter signal with zero offset on the discriminator.

You can also plug into the oscilloscope output to look at modulation waveforms and to measure instantaneously peak deviation.

So besides being a fun little dual-conversion, two-meter VFO-type receiver with adequate sensitivity, it's also a handy test set for working on two-meter mobile and handheld equipment.

For off-air monitoring, signal strength is calibrated in dBm, not S-units. Calibration of the scale in



FIRST, CALCULATE FREQUENCY ERROR AT EACH END OF THE TWO-METER BAND.

dBm is convenient because it allows comparisons of signal differences directly in dB. Here is how they convert dBm to sensitivity in microvolts:

Power in dBm	Microvolts
-100	3
-90	10
-80	30
-70	100
-60	300
-50	1,000
-40	3,000

We found the dBm calibration as good, but not necessarily spot-on. They tell you how to calibrate using professional equipment and adjusting the calibration trim pots back and forth until you get a good linear readout. As it came from the factory, we were close — but not quite right-on.

When we started tuning around the two-

meter band with a set of headphones, we noticed that repeaters between 147 MHz to 148 MHz were not reading out near as close on the big tuning dial as simplex and repeater frequencies at the bottom of the two-meter band. In consulting the manual, we could adjust the frequency calibration for the entire band, but there was no way to easily recalibrate or spot-on the 4 MHz frequency points on two meters.

Radio School associate-instructor Jim Ford N6JF, wires in a three picofarad capacitor between one pin of the integrated circuit and the active leg of the variable capacitor, and then adjusts between two and three picofarads in order to expand the 144 to 148 MHz range to completely fill up the dial as indicated. Once the cap is in place, you will also need to re-adjust the tuning calibration coil to get back to 146 MHz in the center of the band. From there on, it's a slight tweak of the new added cap to electronically pull out the band edges until your FM signal analyzer is right on the nose.

This is a handy piece of equipment for working on any piece of two-meter equipment, and we found the rest of the calibration right up to spec.

If you haven't seen the latest MFJ catalog, get on the web and go to [www.mfjenterprises.com](http://www.mfjenterprises.com), or call them at 601-323-5869 and order one in for your review. We think that MFJ offers extraordinary value for their low-priced products, and any small amount of time in a slight retweaking of their product will certainly "tune you in" to all that goes on in the insides.

I can't think of any company that has contributed as much to happy radio as MFJ, and most recently all of their test equipment has certainly contributed to technicians working on their own and wanting the best equipment available for the buck. NV

AMAZING PRODUCTS!

INFORMATION

VISIT OUR "ACTION" WEB SITE @  
UNLIMITED DEPT NV 0498 <http://www.amazing1.com>  
BOX 716 AMHERST, N.H. 03031

---

### PLASMA BALLISTIC GUN

SHOOTS A HIGH VELOCITY PROJECTILE

Uses New Technology to Generate High Propellant Pressure Without Chemical Reactions

Velocities Up To 3000 m/sec with 50mg Projectile!!  
Easily Scaled Up or Down  
Easy to Build-Kit and Parts Available  
Approximately .16 Caliber Bore

**PPR01 Plans, Parts Lists and Sources.....\$20.00**

Includes Our HEP Series Plans Used for RAILGUNS, COIL GUNS, EMP LEVITATION, ANTIGRAVITY, MASS WARPING, LATTICE SNAPPING etc

### BURNING LASER RAY GUN

BLASTS THRU THE HARDEST OF METALS!

All Parts Available

A FUTURISTIC CONCEPT!!

**LAGUN2 Plans.....\$20.00**

### BURNING CO2 BENCH LASER

HOTTER THAN MOST TORCHES!

Easy to Assemble

**LC7 Plans.....\$20.00**

### TAKE CONTROL!!

ELECTRONIC HYPNOSIS & MIND MACHINES

Electronic Circuitry Induces Hypnotic as Well as ALPHA Relaxed States of the Mind. Place Subjects "Under" Your Control. Enhances Hidden PSYCHIC Ability in Many People!

**MIND Plans.....\$15.00**  
**MIND2K Kit and Plans.....\$49.95**  
**MIND20 Assembled.....\$89.95**

### JACOBS LADDER

Observe a pyrotechnical display of "traveling" fiery plasma. Starts off as 1/2" arc and expands to over 3" before evaporating into space. This is an excellent attention getting display as well as a winning science project!! With arc control.

**JACK1 Plans.....\$8.00**  
**JACK1K Kit Minus Case.....\$129.95**  
**JACK10 Ready to Use.....\$249.95**

**12KVGEN20 Pwr Supply Only.....\$99.95**  
**12KVGEN2K Kit of Pwr Supply.....\$79.95**

### CYBERNETIC EAR!

Enhances Normal Hearing 3 to 4 Times; Provides That Extra "Edge" for Hunters. Trackers Nature Enthusiasts

Adjustable Volume Control  
Fits Into Either Ear  
Built In Long Lasting Batteries  
**CYBEREAR Ready to Use.....\$19.95**

### PHASOR PAIN FIELD PISTOL

Blast out rats and rodents with high power Shock Waves. Handheld and Battery Operated

**PPPI Plans.....\$8.00**  
**PPPIK Kit/Plans.....\$49.50**  
**PPPI10 Ready to Use.....\$79.50**

### TELEPHONE TAPING SYSTEM

EXTENDED X4 PLAY  
Tapes Both Sides of Phone Conversation - Check Laws!  
**TAP30X Ready to Use.....\$84.95**  
**BEEP10 Beeper Alert.....\$29.95**

### 3Mi FM VOICE TRANSMITTER

Safety Product Allows Listening to Children or Involves in Hazardous Areas, Pools, Ponds etc. Great Security Intrusion Alert! Uses FM Table Top Radio. Become the local neighborhood DJ.

**FMV1K Kit/Plans.....\$39.95**

### MICRO TESLA COIL

Lights up a 4 ft Fluorescent Tube Without Contact!!!  
Yet Only 3" Tall!

Super Magic Trick  
Low Cost Science Project  
12 VDC/15 VAC Operation  
**MTC1K Kit/Plans.....\$19.95**  
**MTC10 Ready to Use.....\$34.95**

### HOVERBOARD PLANS

Kit Soon to be Available  
28 Pages of "how to" build a magnetic force field capable of containing a column of ionized air up to several feet! Includes theory on how to build a HOVERBOARD prototype capable of lifting 200 lbs.

**HOVER Plans and Data.....\$25.00**

### TRANSISTORIZED TESLA COIL

TURNS A LIGHT BULB INTO A SPECTACULAR PLASMA DISPLAY  
Transmits Wireless Energy. Brush and Corona Discharge. Noiseless Operation. Pyrotechnic Effect.  
12 VDC/5 Amps or Battery  
115 VAC Optional Converter. Adjustable Frequency Control For Effect.

**TC15 Plans.....\$8.00**  
**TC15K Kit/Plans.....\$59.95**  
**TC150 Ready to Use.....\$109.95**  
**12DC/7 12VDC@7Amps.....\$39.95**

**1 800 221 1705 ORDERS ONLY! FAX 1 603 672 5406 INFO 9-5pm 1 603 673 4730 FREE CATALOG ON REQUEST**  
Pay by MC, VISA, Cash, Chk, MO, COD. Please Add \$5.00 S&H plus \$5.00 if COD. Overseas Please Contact for PROFORMA

Write in 62 on Reader Service Card.

Nuts & Volts Magazine/January 1999 81

**CALL TOLL FREE**  
 (800) 292-7711 orders only  
 Se Habla Español

# C&S SALES

EXCELLENCE IN SERVICE

CALL OR WRITE FOR OUR  
 NEW FREE 64 PAGE  
 CATALOG!  
 (800) 445-3201

## REPAIR SYSTEM SOLDERING AND DESOLDERING Model SL-916



**\$425.00**

Top-of-the-line repair system will handle desoldering. Temperature controlled soldering from 300°F to 790°F (150°C to 420°C), desoldering temperature range 410°F to 900°F (210°C to 480°C). The system is based on principle of vacuum absorption of the solder from the PC board.

SL-928 - Desoldering System with Digital Display also available. \$325.00

## Elenco Scopes Free Dust Cover and Probes



S-1325	25MHz		\$325
S-1330	25MHz	Delayed Sweep	\$439
S-1340	40MHz		\$475
S-1345	40MHz	Delayed Sweep	\$569
S-1360	60MHz	Delayed Sweep	\$749
S-1390	100MHz	Delayed Sweep	\$895

**DIGITAL SCOPE SUPER SPECIALS**

DS-203	20MHz/10Ms/s Analog/Digital	\$695
DS-303	40MHz/20Ms/s Analog/Digital	\$895
DS-603	60MHz/20Ms/s Analog/Digital	\$995

## Four Functions In One Model MX-9300



**\$459.95**

- Features:**
- One instrument with four test and measuring systems:
  - 1.3GHz Frequency Counter
  - 2MHz Sweep Function Generator
  - Digital Multimeter
  - Digital Triple Power Supply - 0-30V @ 3A, 15V @ 1A, 5V @ 2A

## NEW Tektronix DMMs

- 40,000 count
- High Accuracy
- Tektronix quality
- 3yr warranty



DMM 912	<del>\$169</del>	\$179
DMM 914	<del>\$239</del>	\$229
DMM 916	<del>\$265</del>	\$275

## 20MHz Sweep / Function Generator with Frequency Counter Model 4040



- 0.2Hz to 20MHz
- AM & FM modulation
- Burst Operation
- External Frequency counter to 30MHz
- Linear and Log sweep

10MHz Model 4017	\$309	<b>\$399</b>
5MHz Model 4011	\$239	

## Fluke Scopemeters



123...NEW...	\$950
92B	\$1445
96B	\$1695
97	\$1695
99B	\$2095
105B . NEW.	\$2495

ALL FLUKE  
 PRODUCTS  
 ON SALE

## Technician Tool Kit Model TK-1500



28 tools plus a DMM contained in a large flexible tool case with a handle ideal for everyone on the go.

**\$49.95**

### Fluke Multimeters

Model 28III	\$195	Model 12	\$84
Model 70III	\$85	Model 63	\$235
Model 73III	\$115	Model 85	\$269
Model 75III	\$139	Model 87III	\$299
Model 77III	\$154	Model 863E	\$475
Model 79III	\$175	Model 867BE	\$650

### B&K Precision Multimeters

Model 389	\$109	Model 388A	\$99
Model 390	\$127	Model 2707	\$75
Model 391	\$143	Model 2860A	\$79
Model 5360	\$195	Model 5370	\$219
Model 5380	\$265	Model 5390	\$295

## NEW DIGITAL LCR METER Model LCR-1810



- Capacitance .1pF to 20MF
- Inductance 1µH to 20H
- Resistance .01Ω to 2000MΩ
- Temperature -20°C to 750°C
- DC Volts 0 - 20V
- Frequency up to 15MHz
- Diode/Audible Continuity Test
- Signal Output Function
- 3 1/2 Digit Display

**\$99.95**

## B&K High Current DC Power Supply




- Variable 3-14 VDC
- Thermal Protection
- Current Limiting

Model 1686 12A	\$159
Model 1688 25A	\$239

B & K 13.8V Fixed DC/Power Supplies	
Model 1680 6A	\$39
Model 1682 15A	\$75
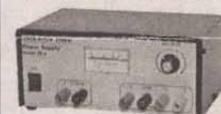
## Quad Power Supply Model XP-4

4 Fully Regulated DC Power Supplies in One Unit  
 4 DC voltages: 3 fixed - +5V @ 1A, -5V @ 250mA, +12V @ 500mA • 1 Variable 0-12V @ 500mA



**\$29.95**

## Digital Multimeter Model M-1740

**\$39.95**

Free Holster



11 functions including freq to 20MHz, cap to 20µF.  
 2 Year Warranty

## Family Radio Model FRS-14

by Standard

- 1 Mile Range
- 1/2 Watt Output, 14 Channels
- LCD Channel & Code Display
- 38 Selectable Channel Codes
- Back-Lit Display.
- No License Required!


**\$129.95 each or  
 2 for \$250.00**



## Handheld Universal Counter

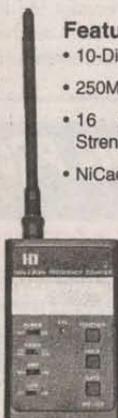**Features:**

- 10-Digit LCD Display.
- 250MHz Direct Count.
- 16 Segment & RF Signal Strength Bargraph.
- NiCad Battery Included.



## Model F-2800 1MHz - 2.8GHz

**\$99**

## B&K Spectrum Analyzers



**500MHz Series**

BK2615A	\$1250
BK2620A	\$1675

- 150KHz to 500MHz
- Dynamic Range 80dB (113dB with attenuation)
- +20dBm maximum input
- 12.5 and 400KHz resolution bandwidth
- 150KHz/hour stability
- Built-in tracking generator (Model 2620A)

**1.05GHz Series**

BK2625A	\$1925
BK2630A	\$2595

- 150KHz to 1,050MHz
- Dynamic Range 80dB (113dB with attenuation)
- AM & FM de mod included
- 20 and 400KHz resolution bandwidth
- 150KHz/hour stability
- Built-in tracking generator (Model 2630A)

## Simm Module Tester B&K Precision Model 898

- Tests 72 and 30 pin SIMMs to 36 bits.
- Stands alone and portable. No other equipment required.
- Automatically identifies width, depth and speed of SIMMs.
- 10 built-in tests identify most memory defects Pre-heat cycle prior to tests.

**\$625**



## Model XP-581

4 Fully Regulated DC Power Supplies in One Unit  
 4 DC voltages: +5V @ 3A, +12V @ 1A, -12V @ 1A  
 1 Variable - 2.5 - 20V @ 2A



**\$89.95**

## Portable Semiconductor Tester B&K Precision Model 510

- In or out-of-order circuit tests for transistor, FETs, SCRs and darlington.

**\$199**



## Satellite Finder Model SF-01

- Aligns Satellite Dishes
- Range 950-2050MHz
- Compact Size
- Self Power Check

**\$39.95**




## Dual-Display LCR Meter w/ Stat Functions B&K Model 878

**\$219.95**

Auto/manual range  
 Many features  
 with Q factor  
 High Accuracy

## Digital Audio Generator SG-9300

**\$175**

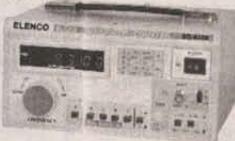

- 10Hz - 1MHz
- Low Distortion
- Sine/Square waves
- Built-in 150MHz Frequency Counter

Guaranteed Lowest Prices

# C&S SALES, INC.

15 DAY MONEY BACK GUARANTEE  
 FULL FACTORY WARRANTY

UPS SHIPPING: 48 STATES 5%  
 OTHERS CALL FOR DETAILS  
 IL Residents add 8.25% Sales Tax

150 W. CARPENTER AVENUE  
 WHEELING, IL 60090  
 FAX: (847) 541-9904 (847) 541-0710  
[http://www.elenco.com/cs\\_sales/](http://www.elenco.com/cs_sales/)



PRICE IS SUBJECT TO CHANGE WITHOUT NOTICE

# PIC-Based Data Acquisition System Characterizes LASER Diodes


by Lawrence Foltzer

cavity cousin ... two of which are its low threshold current and total operating current requirements. However, having plotted numerous laser device characteristics manually, point-by-point, to determine the optimum bias and modulation levels, I decided it was finally time to automate the task.

What I needed was a simple data acquisition system that would interface to the PC for number crunching, and provide both hard and soft copy capability, and ... it had to be easy to build so as not to

With the huge success of CD-ROM technology, semiconductor diode lasers have become readily available and inexpensive. But now a new, more exciting semiconductor laser has become available — the Vertical Cavity Surface Emitting Laser (VCSEL).

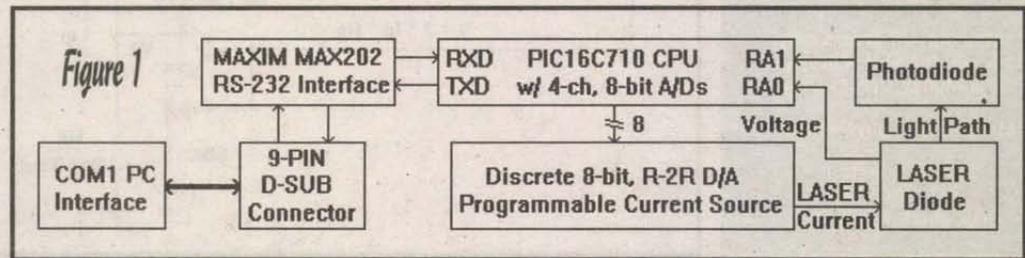The VCSEL offers many advantages over its planar Fabry-Perot



```

REM date: 10-13-98
REM QuickBasic 4.5 version
REM Plots LASER P vs I, Vf vs I
REM and Rs vs I (needs work)
REM creates bit mapped file of screen display
CLOSE: REM can't be too careful

REM vertical voltage scale fixed at 0.2 volts/div
REM then we scale power plot to match that grid and desired power/div
REM there are 13 intervals, and 14 horizontal lines
REM 480/13=36+, use 35. 256/13=19+, use 20, so scale factor is 35/20=1.75
REM so, vplot%=ymax&-ymax&*(255-Vf)/128

Xoffset%= 100: Yoffset%= 100
z%= 40
REM the following values could be switch selectable,
REM in which case you would query for values before starting run
Rd! = 100: REM value of current source resistor
Rp! = 2500: REM value of detector current sampling resistor
IDmax! = 2500 / Rd!: REM IDmax in milliamperes
dId! = 2.5 / (255 * Rd!): REM 98ua per step for Rd! = 100
IPmax! = 2500 / Rp!: REM IPmax in milliamperes

SCREEN 12: CLS
xmax& = 639: ymax& = 479: REM screen 11/12 size
xs! = xmax& / 255: ys! = ymax& / 255: REM x & y scale factors

INPUT "Enter .bmp file_name to create: ", b$
bmpfile$ = b$ + ".bmp"

INPUT "Enter source wavelength (um): ", l!
REM l! = .85
INPUT "Enter detector quantum efficiency (0-1): ", QE!
REM QE! = .6 @ .85um for BP104
PRINT "Enter drive current scan range as a % of: IDmax!: ", ma:
INPUT IDrange!
REM IDrange! = 60 => 15ma
Max% = 255 * IDrange! / 100
INPUT "Enter vertical scale increment (uw/div): ", dP!
INPUT "Enter horizontal scale increment (ma/div): ", dI!
INPUT "Enter number of scans desired: ", s%
Pmax! = 1240.7 * IPmax! / (l! * QE!)
REM Pmax! is full-scale reading in milliwatts
dPdD! = Pmax! / 256: M! = dPdD! / dP!

DIM Vf!(Max% + 4), P!(Max% + 4), Vave!(Max% + 1), Pave!(Max% + 1)
FOR l% = 1 TO Max%: Vave!(l) = 0: Pave!(l) = 0: NEXT l%

GOSUB makegrid

xz% = 0: vz% = ymax&: pz% = ymax&
Vf!(0) = 0: P!(0) = 0: Vave!(0) = 0: Pave!(0) = 0

REM open com port to talk to PIC plotter
portnum% = &H2E8: REM for 386 system, &H3F8 for pentium
OPEN "COM2:2400,N,8,2,BIN,CD0,CS0,DS0,OP0,RS,TB48:RB48" FOR RANDOM AS #1

```

## LISTING 1

```

FOR samples% = 1 TO s%

cont:
REM we do interlaced scan for faster (apparent) graphics

REM make it odd on way up
FOR d% = 1 TO Max% STEP 2
GOSUB retrieve
Vave!(d%) = Vave!(d%) + Vf!(d%)
Pave!(d%) = Pave!(d%) + P!(d%)
NEXT d%

REM now we sweep down
e% = d% - 1: REM make it even on way down
FOR d% = e% TO 2 STEP -2
GOSUB retrieve
Vave!(d%) = Vave!(d%) + Vf!(d%)
Pave!(d%) = Pave!(d%) + P!(d%)
NEXT d%

NEXT samples%

CLOSE

GOSUB makegrid

REM now we compute and display averages on screen
FOR d% = 1 TO Max%
Vave!(d%) = (Vave!(d%) / s%): REM AND &HFF
Pave!(d%) = (Pave!(d%) / s%): REM AND &HFF
NEXT d%

FOR d% = 2 TO Max%
REM Vf vs I
LINE (xs! * (d% - 1), 479 - 35 * 5 * 2.5 * Vave!(d% - 1) / 128)-(xs! * d%, 479 - 35 * 5 * 2.5 * Vave!(d%) / 128)
REM P vs I
LINE (xs! * (d% - 1), ymax& - 35 * Pmax! * Pave!(d% - 1) / (256 * dP!))-(xs! * d%, ymax& - 35 * Pmax! * Pave!(d%) / (256 * dP!))
REM dRs vs I
REM dVf! = (Vave!(d%) - Vave!(d% - 1)) * (5 / 255)
REM printout dynamic series resistance
REM dRs! = (dVf! / dId!)
REM LOCATE 5, 40: PRINT dRs!
NEXT d%

CLOSE
REM END

REM part 1 initialize monochrome .bmp file structure
RESTORE: c% = &HFF: M% = &H80: REM M is bit plot mask
a& = 1
DATA &H42, &H4D, &H9E, &HEA, 0, 0, 0, 0, 0, &H3E, 0, 0, 0, &H28, 0
DATA 0, 0, &H20, 3, 0, 0, &H58, 2, 0, 0, 1, 0, 1, 0, 0, 0
DATA 0, 0, &H60, &HEA, 0, 0, &HCE, &HE, 0, 0, &HD8, &HE, 0, 0, 0, 0
DATA 0, 0, 0, 0, 0, 0, 0, 0, 0, 255, 255, 0, 255, 255, &H5A
OPEN bmpfile$ FOR BINARY AS #1

```





photodiode. The laser drive current level is controlled by the value written to port "RB" of the processor, which together with a discrete R-2R

the drive current to lessen the chance of damage to the device if connected backwards, for example.

A photograph of the hardware is shown in Figure 3. The photo shows both the initial handwired breadboard, and the first PCB prototype that included an on-board voltage regulator. The connections

for the LASER diode and photodiode are indicated on the picture of the PCB.

You can see a laser facing upside-down toward a BP104 photodiode, just above the CA3260AE op-amp on the handwired unit.

Figure 4 shows the 1:1 artwork for the 2.25" by 5.8", second gen-

eration PCB. This version provides pads for both 1206 size surface-mount resistors and 1/4 watt through-hole resistors. Some of the power supply capacitors are double-padded as well. All of the other capacitors are 1206 size surface-mount types for better bypass characteristics, and are mounted on the foil side of the board.

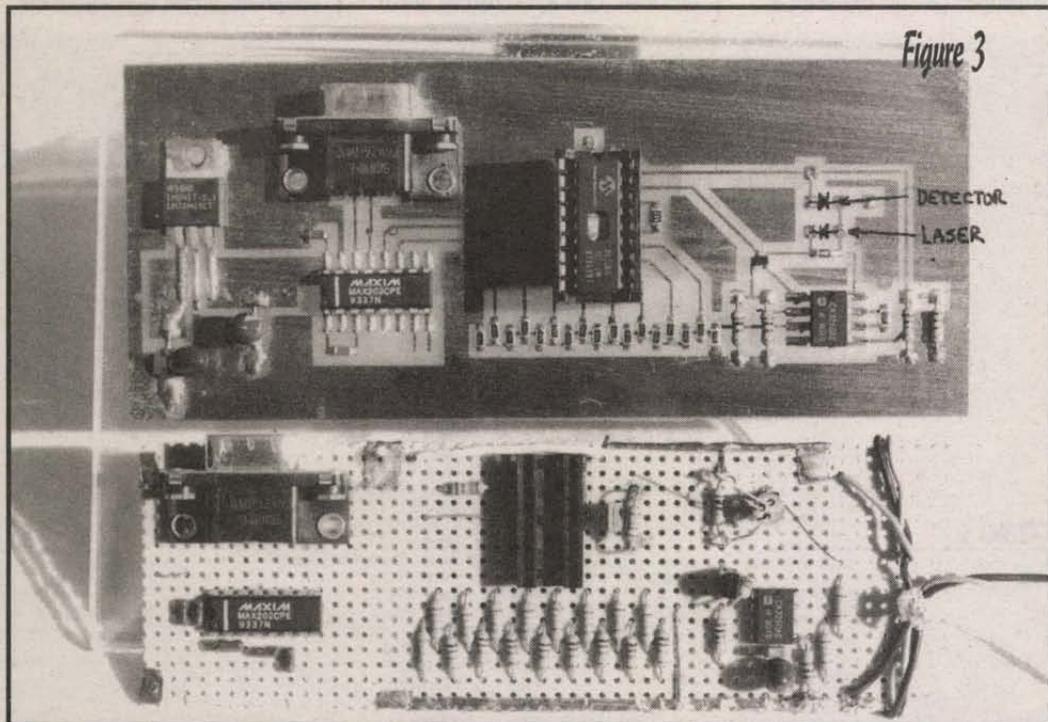


Figure 3

ladder network, makes up an eight-bit D/A converter.

The output of the R-2R ladder is then buffered by a high input impedance op-amp, which drives transistor Q1 to produce a proportional drive current through the emitter resistance. The schematic of the circuit is shown in Figure 2.

The photodiode detector (Siemens TP60P or BP104) is operated in what is called the photoconductive mode (reverse-biased). In this mode, the photodetector acts as a photon counter, generating an output current that is linear with light intensity over several decades of light intensity.

That current develops a voltage across Rsample that is then amplified and presented to the second A/D channel. As the LASER's drive current is increased, both its forward voltage and output power is measured and plotted.

Although not implemented here, one could test the forward voltage measurement against an upper limit, and limit or turn off

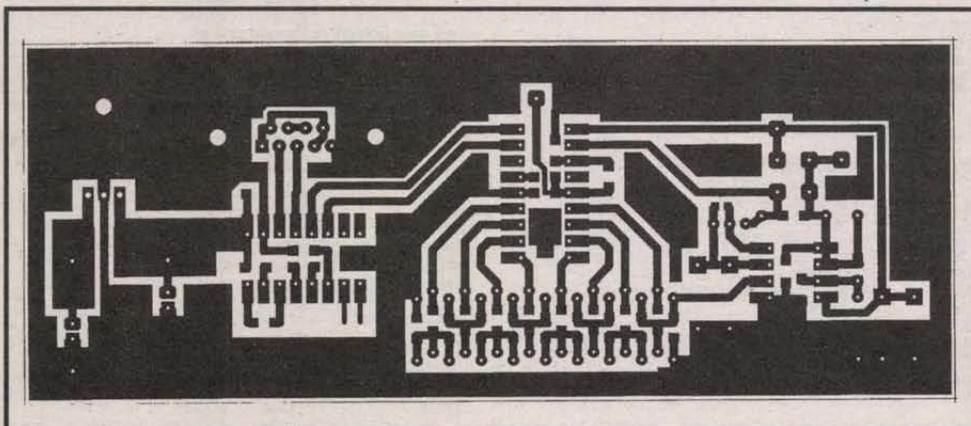


Figure 4

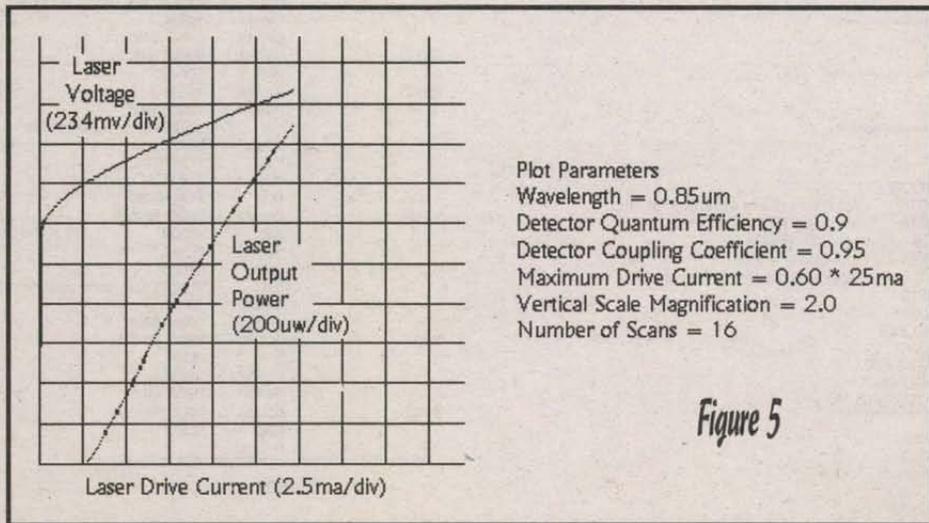


Figure 5

## The Software

The BASIC program is shown in Listing 1. The code is segmented into groups for the purpose of discussion.

Code group three contains the values of two resistors used for plotting VCSEL characteristics. Rd! establishes the maximum LASER drive current to 2.5 volts / Rd! = 25 milliamperes. Rp!'s value is set to maintain 2.5 volts reverse bias across the photodiode for the highest anticipated photocurrent, which translates to 2.5 volts drop across Rp!. For Rp! = 1000 ohms, and Vcc = 5 volts, that equates to 2.5 milliamperes, or roughly 2.5 milliwatts peak.

You may choose to change these values to better fit your particular application, or add a pair of mullet-throw switches for added flexibility. If you add switches, then you will need to add code here to accommodate the new resistor values.

The fifth section of code requests the filename where the monochrome bitmap plot data will be stored. Blocks 21 through 27, and 33 do the work of formatting the file, adding the appropriate header information and setting the appropriate bits to build a MS WINDOWS PAINT compatible monochrome image.

The sixth block of code queries the user for plot calibration information. This data is used to establish the appropriate scale factors for converting the photon count rate to optical power at the source operating wavelength.

This scaling takes into account the fact that photons are essentially energy containers, where blue containers hold more energy than red ones.

So for a given optical power (optical energy delivery rate), it takes more red containers than blue ones. And since our detector counts photons (whose energy exceeds a threshold amount), we get more current for a

watt of red light than for a watt of blue light.

Code group six also asks how many scans to perform on a device. The data collected from these scans is first displayed in raw form on the screen, and averaged to create a reduced noise bitmap PAINT file. By averaging data from multiple scans, it is possible to improve the effective resolution of the A/D beyond its basic hardware limitation.

Code groups 28 through 32 are the interface code to the PIC CPU. These blocks send a redundant drive current command, check to see if the command was properly received, retrieves the A/D data, and plots the results on the screen.

### The Firmware

Listing 2 is the PIC16C710 assembly code for the acquisition system. As you can see, it doesn't take much code (105 instruction words) to implement this functionality, which is basically that of a smart peripheral. The CPU simply examines the serial port looking for a repeated pair of current level command bytes.

When it finds a matching pair, it echoes the command to the host as an acknowledgment, and then sets the output current level as requested. The CPU then reads the two A/D channels, sending the data back to the host, and returns to

monitoring for a new command.

### Some Plot Examples

Figures 5, 6, and 7 show plots made on various VCSEL lasers, and the flexibility provided in terms of customizing plots of individual devices using the Paint program.

### Other Applications

The simple functionality of the system should not be overlooked,

for it lends itself to many other applications. An application closely related to the LASER curve plotter is the characterization of the Current Transfer Ratio (CTR) of optical isolators that contain both emitter and detector.

In fact, I tested the apparatus for the first time in this way, rather than take a chance and burn up a LASER had I wired something wrong.

Another application that comes immediately to mind is to use the

system as part of a closed-loop proportional temperature controller, where heater power is controlled by the programmable current source, and a temperature sensor, such as a thermistor goes in place of the photodiode. Still another application might be in a dark room as an exposure meter. NV

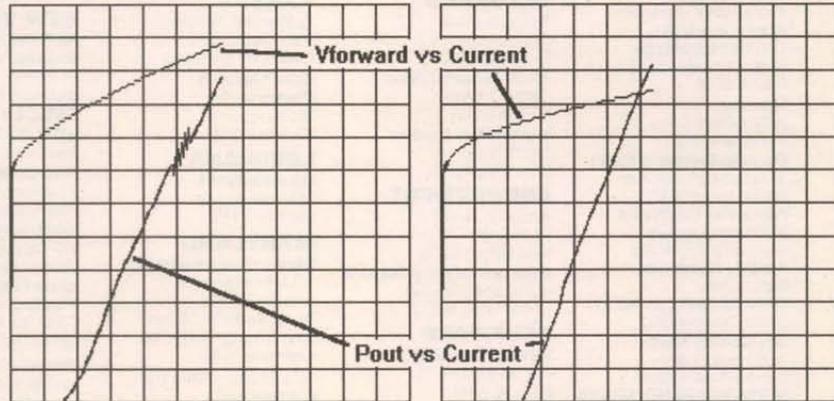



Figure 7

Mitel 1A440 VCSEL  
Laser has interesting kink @ 10 ma  
Horizontal: 2.0 ma/div.


Honeywell SV5637-001 VCSEL #2  
Vertical: 0.2 volts/div, 200 uw/div.

Figure 6

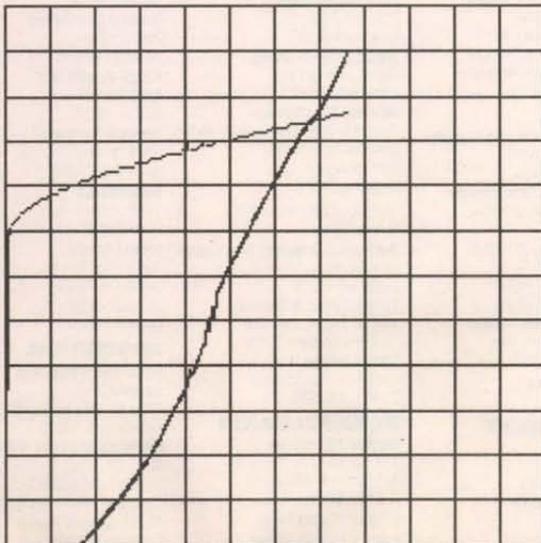Filename: honey01.bmp  
Honeywell SV5637-001 VCSEL  
850 nm wavelength  
Measured with 60% QE BP104 PIN  
Horizontal: 2.0 ma/div  
Vertical: 0.2 volts/div, 200 uw/div  
Cathode @ Case  
Anode @ TAB (isolated)



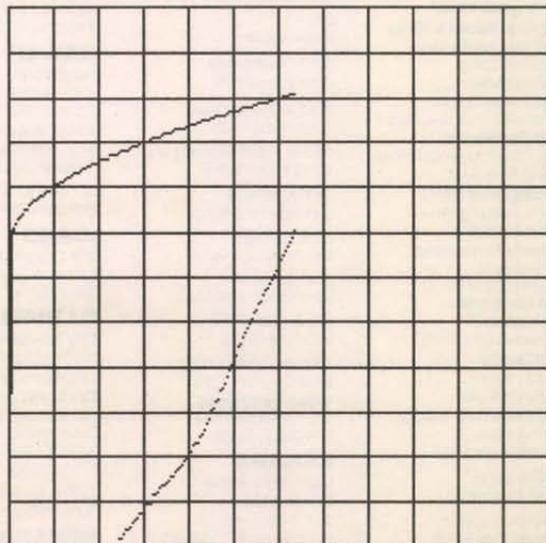Filename: 1a448a01.bmp  
Mitel 1A448A Eyesafe VCSEL  
0.84 um wavelength  
Measurements made with BP104  
Detector, 60% QE @ 840nm  
Horizontal: 2.0 ma/div  
Vertical: 0.2 volts/div, 50 uw/div  
Cathode @ pin 3,  
Case @ pin 2, Center,  
Anode @ pin 1, TAB





# DEALER DIRECTORY

The dealers listed below carry the latest issue of Nuts & Volts, for your convenience.

dealer directory dealer directory dealer directory dealer directory dealer directory dealer directory dealer

**ALABAMA**  
**Little Professor Book Center**  
 2717 S. 18th St.  
 Birmingham 35209  
**RT Systems**  
**Amateur Radio Supply**  
 8207 Stephanie Dr.  
 Huntsville 35802

**ARIZONA**  
**Batteries, Batteries**  
 3415 W. Glendale Ave. #4  
 Phoenix 85051  
 1829 E. Southern Ave.  
 Tempe 85282  
 6245 E. Bell Rd.  
 Scottsdale 85254  
**Elliott Electronic Supply**  
 1251 S. Tyndall Ave.  
 Tucson 85713  
**The Electronic Thrift Store**  
 12329 N.W. Grand Ave. #F  
 El Mirage 85375  
**Tower Records**  
 3 E. 9th St.  
 Tempe 85281

**AUSTRALIA**  
**DonTronics**  
 P.O. Box 595  
 29 Ellesmere Cres.  
 Tullamarine 3043  
 www.dontronics.com

**CALIFORNIA**  
**Abletronics**  
 9155 Archibald Ave. Unit E  
 Cucamonga 91730  
**Advanced Computer Products, Inc.**  
 1310 "B" E. Edinger Ave.  
 Santa Ana 92705  
**All Electronics**  
 905 S. Vermont Ave.  
 Los Angeles 90006  
 14928 Oxnard St.  
 Van Nuys 91411  
**Allen's To Go**  
 13461 Hwy. 88  
 Lockeford 95237  
**Alltronics**  
 2300-D Zanker Rd.  
 San Jose 95131  
**Brand Newsstand**  
 234-1/2 N. Brand Blvd.  
 Glendale 91203  
**Centerfold International**  
 716 N. Fairfax Ave.  
 Los Angeles 90046  
**Del Amo Books & News**  
 3758 Sepulveda Blvd.  
 Torrance 90505  
**Electro Mavin**  
 2985 E. Harcourt St.  
 Rancho Dominguez 90221  
**Ford Electronics**  
 8431 Commonwealth Ave.  
 Buena Park 90621  
**Harding Way News**  
 113 W. Harding Way  
 Stockton 95204  
**Harold's Newsstand**  
 524 Geary St.  
 San Francisco 94102  
**HdB Electronics**  
 2860 Spring St.  
 Redwood City 94063  
**Hi-Fi Doctor**  
 1814 E. Ball Rd.  
 Anaheim 92805  
**HSC Electronic Supply**  
 4837 Amber Ln.  
 Sacramento 95841  
 3500 Ryder St.  
 Santa Clara 95051  
 5681 Redwood Dr.  
 Rohnert Park 94928

**JK Electronics**  
 6395 Westminster Ave.  
 Westminster 92683  
**Laurel Park News**  
 4346 Laurel Canyon Blvd.  
 Studio City 91604  
**Lion Electronic Labs**  
 4948 E. Townsend Ave.  
 Fresno 93727  
**Netseller**  
 7207 Arlington Ave. Ste. G  
 Riverside 92503  
**Op Amp Technical Books**  
 1033 N. Sycamore Ave.  
 Los Angeles 90038  
**Panorama Electronics**  
 8737 Van Nuys Blvd.  
 Panorama City 91402  
**Sandy's Electronics Supply, Inc.**  
 20555 Soledad Cyn. Rd. #15  
 Santa Clarita 91351  
**Sav-On Electronics**  
 13225 Harbor Blvd.  
 Garden Grove 92643  
**SIERRA MADRE NEWSSTAND**  
 55 N. Baldwin Ave.  
 Sierra Madre 91024  
**The Red Barn**  
 Hwy. 299  
 Bleber 96009  
**Tower Books**  
 211 Main St.  
 Chico 95928  
 7840 Macy Plaza Dr.  
 Citrus Heights 95610  
 1280 E. Willow Pass Rd.  
 Concord 94520  
 630 San Antonio Rd.  
 Mountain View 94040  
 1600 Broadway  
 Sacramento 95818  
 5950 Florin Rd.  
 Sacramento 95823  
 2538 Watt Ave.  
 Sacramento 95812  
 2727 El Camino Real  
 San Mateo 94403  
**Tower Magazines/News**  
 885 Riverside Pkwy.  
 West Sacramento 95605  
**Tower Records/Video**  
 220 N. Beach Blvd.  
 Anaheim 92801  
 2520 Durant  
 Berkeley 94704  
 212 F St.  
 Davis 95616  
 5703 Christie Ave.  
 Emeryville 94608  
 2052 Redwood Hwy.  
 Greenbrae 94904  
 6310 E. Pacific Coast Hwy.  
 Long Beach 90803  
 2280 Market St.  
 San Francisco 94114  
 3205 20th Ave.  
 San Francisco 94132  
 2525 Jones St.  
 San Francisco 94133  
 871 Blossom Hill Rd.  
 San Jose 95123  
 1205 W. Covina Pkwy.  
 West Covina 91790  
**Video Electronics**  
 3829 University Ave.  
 San Diego 92105

**CANADA**  
**Corn-West Radio Systems Ltd.**  
 48 E. 69th Ave.  
 Vancouver, BC V5X 4K6

**Muir Communications Ltd.**  
 3214 Douglas St.  
 Victoria, BC V8Z 3K6

**COLORADO**  
**TH Electronics**  
 216 Commerce Dr., Unit 2  
 Ft. Collins 80524  
**Tower Records/Video**  
 2500 E. 1st Ave.  
 Denver 80206  
**Western Test Systems**  
 530 Compton #C  
 Broomfield 80020

**CONNECTICUT**  
**Archway News**  
 64 Bank St.  
 New Milford 06776  
**Electronic Service Products**  
 437 Washington Ave.  
 North Haven 06473

**DELAWARE**  
**Newark Newsstand**  
 70 E. Main St.  
 Newark 19711

**DISTRICT OF COLUMBIA**  
**Tower Records**  
 2000 Pennsylvania Ave.  
 Washington 20006

**FLORIDA**  
**Alfa Electronic Supply**  
 1502 S. St. Rd. #7  
 Hollywood 33023  
**AI's News**  
 8219 S.W. 124th St.  
 Miami 33156  
**Bob's News & Books**  
 1515 S. Andrew Ave.  
 Fort Lauderdale 33316  
**Clarks Out of Town News**  
 303 S. Andrews Ave.  
 Fort Lauderdale 33301  
**Mike's Electronic Distributing Co.**  
 1001 N.W. 52nd St.  
 Fort Lauderdale 33309  
**Skycraft Parts & Surplus, Inc.**  
 2245 W. Fairbanks  
 Winter Park 32789  
**Sunny's At Sunset, Inc.**  
 8260 Sunset Strip  
 Sunrise 33322

**GEORGIA**  
**Tower Records**  
 3400 Around Lenox Dr.  
 Atlanta 30326

**HAWAII**  
**SolarWorks!**  
 525 Lotus Blossom Ln.  
 Ocean View 96737  
**Tower Records**  
 4211 Waiolae Ave.  
 Honolulu 96816  
 611 Keaamoku  
 Honolulu 96814

**IDAHO**  
**The Current Source**  
 5159 Glenwood  
 Boise 83714

**ILLINOIS**  
**City Newsstand**  
 4018 N. Cicero  
 Chicago 60641  
**Tower Records/Video/Books**  
 383 W. Army Trail Rd.  
 Bloomington 61008  
 2301 N. Clark St. #200  
 Chicago 60614  
 1209 E. Golf Rd.  
 Schaumburg 60173

**INDIANA**

**Harbourtown Sales**  
 108 Park 32 W. Dr.  
 Noblesville 46060

**KANSAS**  
**Hollywood At Home**  
 9063 Metcalf Ave.  
 Overland Park 66212  
**Lloyd's Radio & Electronic, Inc.**  
 220 W. Harry St.  
 Wichita 67213

**LOUISIANA**  
**Lakeside News**  
 3323 Severn Ave.  
 Metairie 70002

**MARYLAND**  
**Silicon Valley Electronics**  
 2014-A Industrial Dr.  
 Annapolis 21401  
**Tower Records/Video**  
 2566 Solomons Island Rd.  
 Annapolis 21401  
 1601 Rockville Pike #210  
 Rockville 20852

**MASSACHUSETTS**  
**Full Spectrum Communications**  
 244 Essex St.  
 Salem 01970  
**Newsbreak, Inc.**  
 579 G.A.R. Hwy. Rt. 6  
 Swansea 02777  
**Tower Records #172**  
 360 Newbury St.  
 Boston 02115

**MICHIGAN**  
**Little Professors Book Center**  
 22174 Michigan Ave.  
 Dearborn 48124  
**MW Electronics**  
 229 E. Michigan Ave.  
 Paw Paw 49079  
**Purchase Radio Supply, Inc.**  
 327 E. Hoover Ave.  
 Ann Arbor 48104  
**Tower Records**  
 1214 S. University Ave.  
 Ann Arbor 48104

**MINNESOTA**  
**Radio City, Inc.**  
 2633 County Road 1  
 Mounds View 55112

**MISSOURI**  
**Accurate Instruments**  
 11201 E. 24 Hwy.  
 Independence 64054  
**Electronics Exchange**  
 8544 St. Charles Rock Rd.  
 St. Louis 63114

**NEVADA**  
**Amateur Electronic Supply**  
 1072 N. Rancho Dr.  
 Las Vegas 89106  
**Less Buster's Electronics**  
 2930 N. Las Vegas Blvd.  
 VSTG-22  
 North Las Vegas 89030  
**Radid World**  
 1656 Nevada Hwy.  
 Boulder City 89005  
**Tower Records/Video**  
 4580 W. Sahara Ave.  
 Las Vegas 89102  
 6450 S. Virginia  
 Reno 89511

**NEW JERSEY**  
**Sys-Com**  
 707 22nd St.  
 Union City 07087  
**JR Tech Systems**  
 1309 Hwy. 71  
 Belmar 07719

**NEW MEXICO**  
**Newsland Bookstore**  
 2112 Central S.E.  
 Albuquerque 87106

**NEW YORK**  
**All Phase Video Security, Inc.**  
 70 Cain Dr.  
 Brentwood 11717  
**Goldcrest Electronics**  
 480 St. Paul St.  
 Rochester 14605  
**Ham Central**  
 3 Neptune Rd.  
 Poughkeepsie 12601  
**Hirsch Sales Corporation**  
 219 California Dr.  
 Williamsville 14221  
**Tower Records/Video**  
 105 Old Country Rd.  
 Carle Place 11514  
 350-370 Route 110  
 Huntington 11746  
 1961 Broadway  
 New York 10023  
 383 Lafayette St.  
 New York 10003

**OHIO**  
**Compusluff**  
 241 Great Oaks Trl.  
 Wadsworth 44281  
**Digital One**  
 7603 Mentor Ave.  
 Mentor 44060  
**Footsteps**  
 4925 Jackman Rd. Store #58  
 Toledo 43613  
**Hosfelt Electronics, Inc.**  
 2700 Sunset Blvd.  
 Steubenville 43952  
**Keyways, Inc.**  
 204 S. 3rd St.  
 Miamisburg 45342  
**Leo's Book Shop**  
 330 N. Superior St.  
 Toledo 43604  
**Powermaxx, Inc.**  
 1587 U.S. Route 68 N.  
 Xenia 45385

**OKLAHOMA**  
**Steve's Books & Magazines**  
 2612 S. Harvard  
 Tulsa 74114

**OREGON**  
**News & Smokes**  
 2295 W. Main St.  
 Medford 97501  
**News & Smokes #8**  
 259-C Barnett Rd.  
 Medford 97501  
**Norvac Electronics**  
 7940 S.W. Nimbus Ave. Bldg. 8  
 Beaverton 97005  
 960 Conger  
 Eugene, OR 97402  
 1545 N. Commercial N.E.  
 Salem 97303  
**Powell's Technical Bookstore**  
 33 N.W. Park  
 Portland 97209  
**Taylor News & Books**  
 133 W. Main, Ste. 102  
 Oklahoma City 73102  
**Tower Books**  
 1307 N.E. 102nd Ave.  
 Portland 97220

**PENNSYLVANIA**  
**Bedford St. News**  
 308 Bedford St.  
 Johnstown 15901  
**Genes Books, Inc.**  
 King of Prussia Plaza  
 King of Prussia 19406

**Lehman Scientific**  
 2997-F Cape Horn Rd.  
 Red Lion 17356  
**Monico Electronics & Computers**  
 2555 Industry Ln. Ste. D  
 Norristown 19403  
**Surplus AI**  
 RR 1 Box 337  
 Hunlock Creek 18621  
**Tower Books**  
 425 South St.  
 Philadelphia 19147  
**Tower Records**  
 340 W. Dekalb Pike  
 King of Prussia 19406

**SOUTH CAROLINA**  
**555 Electronics**  
 5646 Farrow Rd.  
 Columbia 29203

**TENNESSEE**  
**Tower Books**  
 204 W. End Ave.  
 Nashville 37203

**TEXAS**  
**BDL News, Inc.**  
 809 Pierce  
 Houston 77002  
**Electronic Parts Outlet**  
 3753-B Fondren Rd.  
 Houston 77063  
**Mouser Electronics**  
 958 N. Main St.  
 Mansfield 76063  
**Tanner Electronics**  
 1301 W. Bellline #105  
 Carrollton 75006  
**Tower Records**  
 2403 Guadalupe  
 Austin 78705

**VIRGINIA**  
**Satellite Headquarters**  
 7920 Timberlake Rd.  
 Lynchburg 24502  
**Tower Records/Video/Books**  
 4110 W. Ox Rd. #12124  
 Fairfax 22033  
 1601 Willow Lawn Dr.  
 Richmond 23230  
 8389 E. Leesburg Pike  
 Vienna 22182

**WASHINGTON**  
**A-B-C Communications, Inc.**  
 17541 15th Ave. N.E.  
 Seattle 98155  
**Bolico Concepts**  
 214 2nd St.  
 Morton 98356  
**Cody Books Ltd.**  
 1125 Fir Ave.  
 Blaine 98230  
**Service Request**  
 3304 W. Rowan Ave.  
 Spokane 99205  
**Supertronix**  
 18650 68th Ave. S.  
 Kent 98032  
**Tower Books**  
 10635 N.E. 8th St.  
 Bellevue 98004  
 20 Mercer St.  
 Seattle 98109

**WISCONSIN**  
**Amateur Electronic Supply, Inc.**  
 5710 W. Good Hope Rd.  
 Milwaukee 53223  
**Greenfield News & Hobby**  
 6815 W. Layton Ave.  
 Greenfield 53220  
**Cudahy News & Hobby Ctr.**  
 4758 Packard Ave.  
 Cudahy 53110

## Three More Ways to Use Graphic LCD Displays

by Ryan Sheldon, National Control Devices (404) 244-2432 <http://members.aol.com/ncdcat>

Three Convenient Sizes of LCD Displays Offer Complete Display Solutions for Most Embedded and PC Applications

I received lots of feedback and excellent suggestions from my previous graphic LCD display articles. I also heard from lots of curiosity seekers with good questions about LCD screens. I was very surprised to find that many of you wanted smaller graphic LCD screens, not larger. If anything, I would have thought you would have all wanted larger screens so you could display more information ... Instead, most of you preferred smaller screens to fit in your car, or as a discreet wall display in your house, or even in small-customized electronics project cases. And, after many phone conversations with several of my readers, I realized that the screens that I provided were simply too large for some applications.

So, I went back to the drawing board to see how I could adapt the LCD Animator 128 to use smaller screens. While this was theoretically possible, I had never really tried to do it until two days before this article was due for publication. So, I have not had time to change the LCD Animator 128 Setup program (included with the controller) to support these smaller screens. But, I went ahead and wrote a few Visual Basic 5 drivers that would get the job done.

This month, I will introduce two other displays for the LCD Animator 128. The smallest is 128x64, and the larger is 256x64. Both offer excellent image quality and one of these screens should fit your display requirements and budget.

So this month, I am going to show you how to use these different LCD screens from Visual Basic 5, and I am

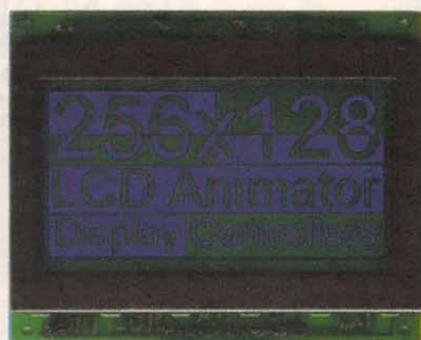


FIGURE 1

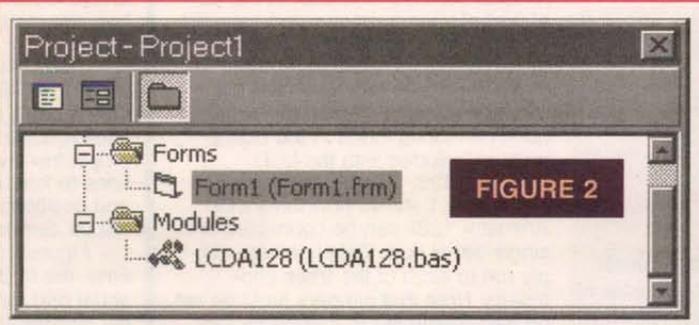
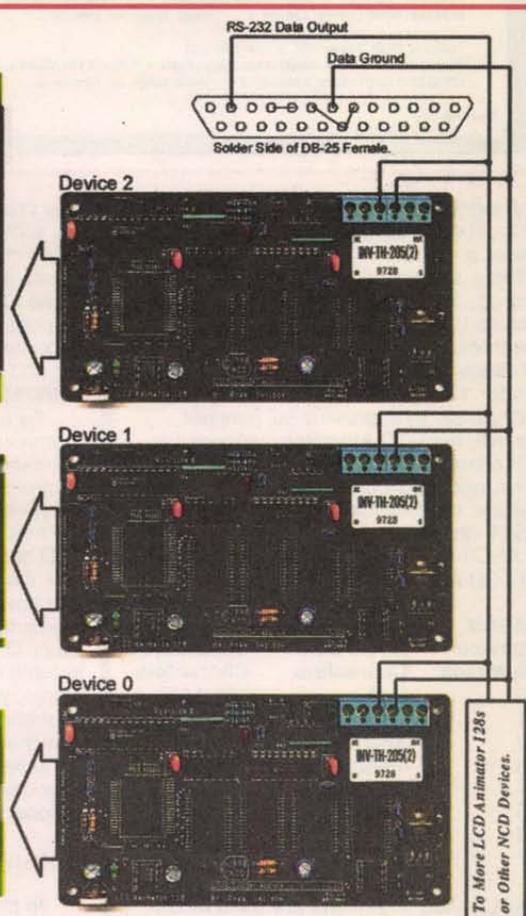


FIGURE 2

controller. This month's application will demonstrate how to drive three LCD Animator 128 controllers from a single serial port, each with a different size display attached, with each screen showing different images and text.

The RS-232 network typically allows you to control 16 NCD devices from a single RS-232 serial port on your computer. But since graphic LCD displays require more network resources, you can only have eight different (or same) graphic LCD displays attached to a single RS-232 serial port. You only need two wires to con-

```

Project1 - Form1 (Code)
Form Load
Private Sub Form_Load()
    Form1.Visible = True
    'Show Image on the PC's Screen
    MSCOMM1.Settings = "19200, n, 8, 1" 'Setup Serial Port
    MSCOMM1.CommPort = 2 'Select Comm2 of the Serial Port
    MSCOMM1.PortOpen = True 'Open the Serial Port

    'Initialize LCD Animator 128 with a 128x64 Screen Attached to Device 0
    LCDAI28.Setup_128x64 0
    'Initialize LCD Animator 128 with a 256x64 Screen Attached to Device 1
    LCDAI28.Setup_256x64 1
    'Initialize LCD Animator 128 with a 256x128 Screen Attached to Device 2
    LCDAI28.Setup_256x128_With_64_Frames_Graphics_Text 2

    LCDAI28.CLRTEXT_128x64 0 'Clear a 128x64 LCD Attached to Device 0
    LCDAI28.CLRTEXT_256x64 1 'Clear a 256x64 LCD Attached to Device 1
    LCDAI28.CLRTEXT_256x128 2 'Clear a 256x128 LCD Attached to Device 2

    'Load a Test Image for a 128x64 LCD
    Picture1.Picture = LoadPicture(App.Path + "/TestPics/EG2201.BMP")
    LCDAI28.SendPicture_128x64 0 'Send Image to Device 0

    'Load a Test Image for a 256x64 LCD
    Picture1.Picture = LoadPicture(App.Path + "/TestPics/EG2401.BMP")
    LCDAI28.SendPicture_256x64 1 'Send Image to Device 1

    'Load a Test Image for a 256x128 LCD
    Picture1.Picture = LoadPicture(App.Path + "/TestPics/EG4401.BMP")
    LCDAI28.SendPicture_256x128 2 'Send Image to Device 2
End Sub

```

FIGURE 3



FIGURE 4

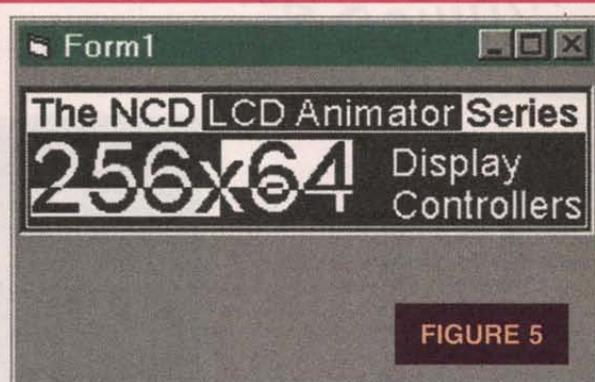


FIGURE 5



FIGURE 6

trol all eight LCD screens. One wire provides data to all eight devices, and the other wire provides a ground.

Three address jumpers identify each board: J1, J2, and J3. When the LCD Animator 128 boards are first powered up, these three jumpers are read to determine what range of ASCII characters the LCD Animator 128 will listen to.

When set to address 0 (all jumpers removed), the LCD Animator responds to ASCII characters 0 to 15 for data communications, and ASCII characters 128 to 143 for command communications. A complete table of ASCII characters (shown below) identifies how ASCII characters are used to control eight LCD Animator 128 boards.

ASCII Device Address	ASCII Data Characters	Command Characters
0	0-15	128-143
1	16-31	144-159
2	32-47	160-175
3	48-63	176-191
4	64-79	192-207
5	80-95	208-223
6	96-111	224-239
7	112-127	240-255

ASCII data characters are used to dis-

play images and text on the screen. ASCII command characters are used to turn on/off the backlight of the LCD display and are responsible for feeding important cursor positioning and setup commands to the LCD screen.

As a Visual Basic programmer, you can use my pre-canned routines to control these displays. You will never have to know too much about how the LCD screens work, just how the software works and how to use my programs to control these displays. Once you are comfortable with using my programs, you can dissect my control routines to find out how they work, and probably write better ones for your own custom applications.

### Getting Started

In previous months, I have shown how to connect the LCD Animator to the serial port of your computer and have discussed power requirements and all the technical information required to make the controller work. I will not repeat this information in this article, but it can all be found in the user's manual included with the LCD Animator 128.

Figure 1 shows how three LCD Animator 128s can be connected to a single serial port. Data lines are simply run to each of the three controllers. Note that jumpers must be set on each controller to identify its location on the network. The 14-pin LCD interface is standard, and can be used to connect to most Epson graphic dis-

plays up to 256x128.

Visual Basic 5 will again be used to control these LCD screens. Send me an E-Mail and I will provide the necessary files for this article in ZIP format. Ask for CCWJAN99.ZIP. You can start by loading my example program.

I want you to pay particular attention to the LCDA128 module shown in Figure 2. This module contains all of the basic subroutines required to drive all three displays from only a few lines of code. I have written routines to load images, clear graphics and text, and position text on the screen. All of which will be demonstrated in the coming sections.

Figure 3 is where all the magic happens. First, the MSComm control is used to set the serial port for RS-232 communications. On my system, Comm 2 is used for the RS-232 serial port. Once the port and baud rate are set, the port is opened.

The first three subroutine calls set each

of the three LCD Animator 128 controllers for graphics and text mode. Since a different size LCD screen is attached to each controller, a different setup subroutine is required to tell each controller what type of screen is attached.

Device numbers 0 to 2 are used to identify each of the three controllers. Device 0 has a 128x64 LCD screen attached, so anytime you want to talk to device 0, you should use a subroutine written specifically for this size of display. I haven't written too many subroutines for these different size screens just yet, but there are certainly enough to cover the lion's share of graphics and text manipulation.

Once the three LCD Animators are told what size display is attached to each controller, I send commands to clear the text screen on each of the three controllers. Keep in mind, this ONLY clears the text layers, it does NOT affect the graphic layers. Again, three separate clear text (CLRTXT) subroutines are called. Each is optimized for a different size LCD screen.

Now for the fun part. I used a Picture Box in my application so I could see what images are being loaded on my PC screen. I use a different "SendPicture" subroutine for each of three sizes of LCD screens. Once a test image is loaded, I simply call the appropriate subroutine to dump the image from the "PictureBox" to the LCD display. Figures 4, 5, and 6 show the source image that is to be loaded. Figure 1 shows how each of the three images looks once loaded onto the LCD screen.

### Graphics and Text Overlays

As I mentioned before, graphics and text can be overlaid independently on a single screen. You can change the image without affecting the text. Likewise, you can change the text without affecting the image. Figure 7 shows how to send text and graphics to

```
Project - Form (Code)
[General] GraphicTextOverlays

Public Sub GraphicTextOverlays()

LCD128.CLRTXT_128x64 0 'Clear the Text Screen on Device 0
'Write Text to Device 0 Beginning in Column 3
LCD128.Text_128x64 0, 3, 2, "Device 0 is a"
LCD128.Text_128x64 0, 3, 5, "LCD Display."
LCD128.Text_128x64 0, 3, 6, "Overlay Text and Graphics."
'Load Background Picture
Picture1.Picture = LoadPicture(App.Path + "/TestPics/EG2201b.BMP")
LCD128.SendPicture_128x64 0 'Send Background Picture to Device 0

LCD128.CLRTXT_256x64 1 'Clear the Text Screen on Device 1
'Write Text To Device 1 Beginning in Column 15
LCD128.Text_256x64 1, 15, 2, "Device 1 Also"
LCD128.Text_256x64 1, 15, 3, "Supports Graphics"
LCD128.Text_256x64 1, 15, 4, "and Text Overlays."
'Load Background Picture
Picture1.Picture = LoadPicture(App.Path + "/TestPics/EG2401b.BMP")
LCD128.SendPicture_256x64 1 'Send Background Picture to Device 1

End Sub
```

FIGURE 7



FIGURE 8

each of these layers on two of the LCD screens.

The 128x64 LCD is the first display to show an overlay. I begin the subroutine by clearing the text layer. I then use the Text\_128x64 subroutine to write text to the screen. The first parameter is 0, once again indicating we are speaking to device 0, which has a 128x64 LCD screen attached. I use 3, 2, "Device 0 is a" to move the cursor to column 3, line 2, and write the quoted text to the display. The 3, 2 set the cursor start position; as text is written to the screen, the cursor is automatically indexed. Once text is

written, I load a background image into the "PictureBox." I again use the "SendPicture" subroutine to send the picture to device 0.

Similar steps are taken to overlay text with graphics on the 256x64 LCD screen. Again, device 1 is used to identify the LCD Animator with a 256x64 LCD attached. The 256x128 screen also supports graphics and text overlays. Figures 8 and 9 demonstrate the appearance of two LCD screens used in graphics/text overlay mode.

### Technical Notes

The LCD Animator 128 set to Device 0 is shown controlling an Epson EG2201 128x64 Graphic LCD Display. The controller is configured for 16x8 text with graphics and can store 128 different text and graphic images. Model shown is a reflective display.

The LCD Animator 128 set to Device 1 is shown controlling an Epson EG2401 256x64 Graphic LCD Display. The controller is configured for 32x8 text with graphics and can store 128 different text and graphic images. Model shown has an emerald green EL backlight.


The LCD Animator 128 set to Device 2 is shown controlling an Epson EG4401 256x128 Graphic LCD Display. The controller is configured for 32x16 text with graphics and can store 64 different text and graphic images. Model shown has a white EL backlight.

Some displays made by other manufacturers will work with the LCD Animator 128. Additional information for interface will be available when the LCD Animator X is complete.

Thanks again for reading this month's "Computer-Controlled World." As usual, feel free to E-Mail, call, or write with your questions and comments. NV



FIGURE 9

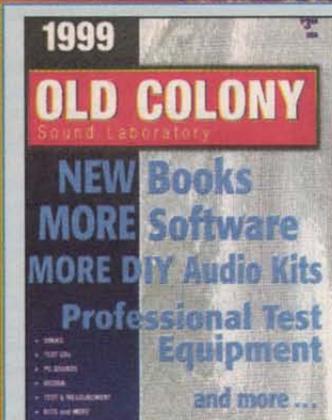

**1999 OLD COLONY SOUND LABORATORY CATALOG**

Audio Amateur Corp. announces the 1999 edition of the Old Colony Sound Laboratory has been printed and is ready to mail to over

40,000 DIY audio enthusiasts worldwide. This year's catalog features books on all aspects of audio, software, PC boards, test CDs, and equipment and vendor sources for all areas of audio construction and modification.

This year's catalog contains a number of new products including test equipment from TES Corporation, new books on a variety of subjects in audio and electronics and an updated software version of SoundEasy for loudspeaker design and placement.

The 1999 edition of the catalog also features a new index which includes authors, enhancing the catalog's use as a reference for audio books.

For more information, contact:

**AUDIO AMATEUR CORP.**  
**1-888-924-9465 or 603-924-9464**  
**E-MAIL: [custserv@audioxpress.com](mailto:custserv@audioxpress.com)**  
**WEB: [www.audioXpress.com](http://www.audioXpress.com)**

**NYE 330C KEY**

Morse Express announces a new straight key from Wm. M. Nye Company - it's Nye's first new product since the late 1970s.

The Model 330C is a deluxe version of Nye's classic Master Key, with a highly polished chrome base, nickel-plated hardware, and Navy Knob.

The hardware is selected by hand and each 330C is carefully inspected before packing to ensure a flawless finish.

Model 330C has gold-plated hard silver contacts which are electrically isolated from the rest of the

key, and is supplied complete with cord and 1/4" phone plug.

Unlike any other Nye or Speed-X key, each 330C has a serial number stamped in the base.

Nye's Model 330C is priced at \$139.95 and is covered by Nye's standard two-year warranty.

For more information, contact:

**MORSE EXPRESS**  
**3140 S. PEORIA ST., #K-156**  
**DEPT. NV**  
**AURORA, CO 80014-3155**  
**303-752-3382 FAX: 303-745-6792**  
**1-800-752-3382**  
**E-MAIL: [hq@MorseX.com](mailto:hq@MorseX.com)**  
**WEB: [www.MorseX.com](http://www.MorseX.com)**



**IIC LCD DISPLAY MODULES**

Advanced Graphic Systems announces the release of its two newest products, IIC LCD Display Modules.

The IIC inter-controller communication bus has long provided accurate, rapid communication between microcontrollers along with a variety of peripheral devices.

Now, added to that list of devices is the AGS ILCD1 and ILCD2 liquid crystal display modules. The ILCD1 is a single line by 16 supertwist LCD module with large display characters. The ILCD2 is a back-lit, two line by 16 supertwist LCD module with standard display characters.

Both units include all the necessary micro-controller support hardware on board. External connections require a nominal supply voltage of 5 VDC, and the interface to the IIC bus, the SDA and SCL signals (external pull-up resistors

are required).

They both utilize the standard seven-bit addressing scheme, can communicate at the 100Kbit/s transfer rate or the fast-mode rate of 400Kbit/s, and the internal module address can be programmed to reside at up to nine different locations making it possible to use several displays on one bus.

Both modules automatically clear the internal display memory queue after each write cycle so that the user need only send valid display data without the need for clearing previously displayed characters from the display, thus keeping programming overhead at a minimum.

Both devices measure approximately 1.5" x 3.25" so that use of standard 1x16 or 2x16 LCD mounting locations is still made possible.

Both modules are currently available and can be purchased for \$55.00 in single quantities to \$35.00 in 100+ quantities.

For more information, contact:

**ADVANCED GRAPHIC SYSTEMS**  
**4055 GRASS VALLEY HWY., #103, DEPT. NV**  
**AUBURN, CA 95602**  
**530-887-1619 FAX: 530-887-0107**  
**WEB: [www.ags-gv.com](http://www.ags-gv.com)**

**CAPANALYZER 88A**

The CapAnalyzer 88A has improved test probes for testing both radial and all types of surface-mounted caps with just one hand.

A higher DCR range set-alert now adjustable up to 500 ohms, allows checking both electrolytic and now tantalum caps.

A QuickESR test has been added for super-fast ESR-only testing, with the original discharge/DCR test/ESR test mode still available for super-accurate good-fair-bad testing.

Also new is one-to-five beep multitone that allows a technician to know the ESR reading without having to read the 20-segment LED display. Battery life is also improved.

All of the original CapAnalyzer 88's desirable features remain, such as the three-color chart on the front panel that allows comparison of ESR to capacity, the expanded scale display, and the portability of battery operation to repair big screens in the field in minutes. An adapter is also available for all-day power at the bench.



**LEAKSEEKER 82B**



Technicians looking for a better way to find that elusive shorted or leaky component now have a new improved LeakSeeker 82B that can turn hours of endless searching into seconds of satisfaction. Simply touch LeakSeeker's probe to pads along the trace that you suspect a short or leaky component is; the pad where the beep is highest is the lowest resistance and therefore is the bad component.

Touch pads in one direction then the other, and LeakSeeker will beep higher or lower, and light the LED scale to show you if you are getting closer or further from the leaky part.

LeakSeeker 82B will automatically recalibrate itself as you make progress, or switch to manual and probe a small dense area where a bad part only a quarter of an inch away from a good part can be found.

LeakSeeker 82B will locate not only shorted components, but even leaky components that can be as high as 150 ohms. It can even find active shorts that only show up when the unit is turned on!

There is also a three-wire test mode to locate high-resistance shorts and thermally defective components. This is one very special piece of test gear that no productive technician should be without. It comes with a very complete manual and gold-plated test leads.

For more information, contact:


**ELECTRONIC DESIGN SPECIALISTS, INC.**  
**4647 APPALACHIAN ST., DEPT. NV**  
**BOCA RATON, FL 33428**  
**561-487-6103**  
**WEB: <http://www.eds-inc.com/>**

**Showcase your New Products here! Send all press releases or information/photos to:**

**Nuts & Volts Magazine**  
**New Product News**

**430 Princland Court, Corona, CA 91719**  
**or E-Mail to [newproducts@nutsvolts.com](mailto:newproducts@nutsvolts.com)**

# New Product News

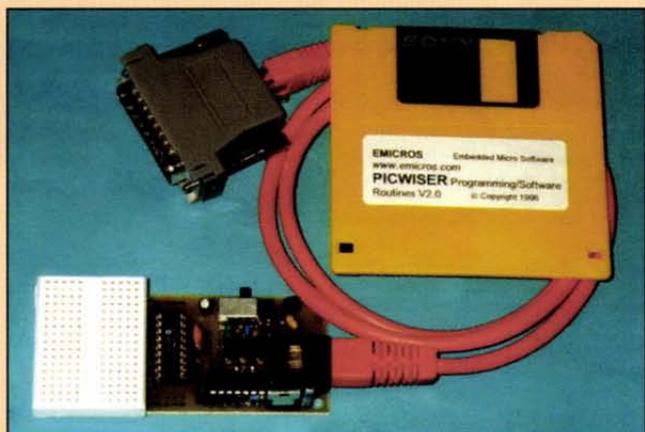

**PICWISER**

The PICWISER from Embedded Micro Software (EMICROS) is a low-cost development system for learning microcontrollers, rapid prototyping, or as a PIC programmer. The integrated programmer allows programs to be downloaded from the PC parallel port into the PIC16F84 flash microcontroller and executed with the flip of a switch.

The PICWISER comes assembled and tested, complete with interface cable, solderless breadboard, prototyping wire, programming software, power supply, and manual.

For more information, contact:

**EMICROS — EMBEDDED MICRO SOFTWARE**  
25759 RIDGEWOOD DR., DEPT. NV  
FARMINGTON HILLS, MI 48336  
248-477-6639

E-MAIL: [picwiser@emicros.com](mailto:picwiser@emicros.com) WEB: [www.emicros.com](http://www.emicros.com)

## ADONIS AM-7500E DESKTOP MICROPHONE



Adonis USA introduces the AM-7500E amplified desktop microphone with a four-band graphic equalizer and three-stage speech compressor for use with amateur, and other two-way radios.

The AM-7500E four-band graphic equalizer provides tone control over your transmitted voice — while the speech compressor and audio amplifier allow control over the strength and consistency of your transmitted audio.

Other features include: a highly-sensitive electret microphone element; an output level control; both momentary and locking push-to-talk switches; up and down frequency controls; a VU meter; a battery level tester; and an alarm that warns if the AM-7500E has accidentally been left in transmit

(this function can be turned off).

The AM-7500E is constructed of an anodized aluminum body and has a flexible metal gooseneck microphone. The microphone is powered by either four AA batteries, an optional DC power adapter (model PS-6A), or can be powered directly by some two-way radios.

The AM-7500E uses Adonis adapter cables (available separately) to connect to your transceiver, which makes switching between radios a 'solder-less' experience.

The AM-7500E retails for \$269.95 and has a full one-year warranty.

## OPERATE TWO TRANSCEIVERS WITH ONE DESKTOP MICROPHONE



Adonis USA introduces the AM-708E amplified desktop microphone with two transceiver outputs and a variable speech compressor for use with amateur, commercial, and other two-way radios.

The AM-708E has two microphone outputs for operating two different transceivers with one microphone. A two-position switch on the AM-708E allows the user to select and operate either transceiver. A speech compressor with a high, low, and a variable manual setting allows precise control over compression levels.

The AM-708E is constructed of an anodized aluminum body and has a flexible metal gooseneck microphone. The microphone is powered by either two AA batteries, an optional DC power adapter (model PS-3), or can be powered directly by some two-way radios.

The AM-708E uses Adonis adapter cables (available separately) to connect to your transceivers.

The AM-708E retails for \$219.95 and has a full one-year warranty.

For more information, contact:

**ADONIS USA**

P.O. BOX 1124

ISSAQUAH, WA 98027

425-558-9592 FAX: 425-558-9704

E-MAIL: [info@rflimited.com](mailto:info@rflimited.com) WEB: <http://www.rflimited.com>

Mail your New Products to: [newproducts@nutsvolts.com](mailto:newproducts@nutsvolts.com)

## MCM ELECTRONICS CATALOG 42A

MCM Electronics announces the introduction of their newest catalog — number 42!

This latest catalog features more than 3,000 new products including project accessories, semiconductors, connectors, test equipment, computer and home audio products, along with thousands of original OEM TV/VCR repair parts. Prices have been lowered on products throughout the catalog and customers will find special values in all sections.

For more information, contact:

**MCM ELECTRONICS**  
650 CONGRESS PARK DR., DEPT. NV  
CENTERVILLE, OH 45459-4072  
1-800-543-4330  
WEB: [www.mcmelectronics.com](http://www.mcmelectronics.com)

## VIBROPLEX® SQUARE RACERS

Vibroplex has New Square Racers! A departure from our traditional Brass Racer, these keys have a heavy solid-steel base which anchors the key in the operating position. The same unique Racer magnetic design is used on these New Racer models, NO springs!

Each key has the famous Vibroplex brass logo plate with a unique serial number pinned to the top of each base with stainless steel pins.

Available in two models: The deluxe version has a highly polished decorative chrome base with bright chrome top parts, with red finger pieces and retails for \$134.95. The standard version is a neat black textured base with decorative chrome top parts, with black finger pieces and retails for \$109.95.

## VIBROPLEX® 'BUG TAMER'

Anyone who owns a Vibroplex original 'Bug' knows that the speed range is

approximately 20 wpm on low side and 50+ wpm on high side. Given these high standards of speed, lots of hams struggle to use the traditional 'Bug.' Vibroplex has now introduced the 'Bug Tamer' just for that reason. Now, anyone can use a 'Bug.'

The 'Tamer' extends the pendulum and makes a dramatic reduction in the Bug's speed range with the use of your existing speed weight(s). Your Bug's speed can be adjusted down to 10-12 wpm or possibly slower.

Bug tamers include the extension arm, nylon, and stainless steel set screws with Allen wrench to attach it to the pendulum of your Bug.

Two versions are available: Chrome version (\$24.95) and Brass version (\$20.00).

For more information, contact:

**THE VIBROPLEX® CO., INC.**  
11 MIDTOWN PARK E., DEPT. NV  
MOBILE, AL 36606-4141  
334-478-8873 FAX: 334-476-0465  
1-800-840-8873

# Opto Hits The Spot



## SCOUT

- 10MHz - 1.4GHz
- Stores 400 frequencies in memory
- Reaction Tune the ICOM R7000, R7100, R8500, R9000, R10, AOR 8000, AOR 8200, and Opto R11
- 10 digit LCD with signal strength bar-graph
- Vibrator and beeper alert mode

**\$349** SAVE \$100

DB32 Antenna Sold Separately (\$29)



## R11

- 30MHz - 2GHz wide band receiver (Cellular Blocked)
- Built-in speaker for instant audio demodulation
- LED frequency range indication display
- Reaction Tune with Scout
- Capture 5 watt UHF signal from 500 feet
- 1000 frequency lockout

**\$299**

TA100S Antenna Included




## XPLORER

- 30MHz - 2GHz (Cellular Blocked)
- Two line LCD frequency display
- Decode CTCSS, DCS, and DTMF
- 500 memories
- 1000 frequency lockout
- Built-in PC interface
- Capture 5 watt UHF signal from 800 feet

**\$799** SAVE \$100

TA100S Antenna Included

## In The Spotlight

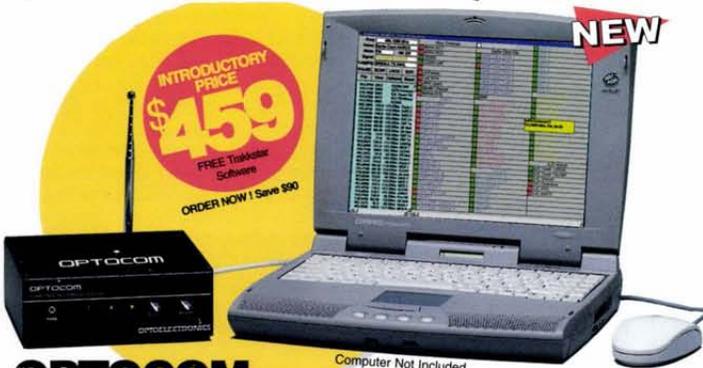

**INTRODUCTORY PRICE**  
**\$459**  
FREE Trakstar Software  
ORDER NOW! Save \$90

**NEW**

## OPTOCOM

Computer Not Included

- High speed triple conversion GRE receiver
- Track Motorola 400, 500, 800, and 900MHz systems
- Decode CTCSS, DCS, LTR, DTMF, and Motorola talk group IDs
- Scan trunked and conventional frequencies simultaneously
- Reaction Tune with Scout Frequency Recorder
- Software Controlled volume & squelch for remote control operation

- Store & Scan, download up to 28 different frequencies or one talk group ID for scanning without computer control
- Supplied with the all new Trakstar software
- Trunk Track LTR systems
- Scans conventional frequencies from 25-250, 760-823.995, 849.005-868.995, 894.005-1300MHz (Cellular frequencies blocked)

## Special Prices are for a Limited Time Only!!



## COUNTERS

Handheld frequency counters, all incorporating patented Digital Filter and Digital Auto Capture. All counters come with initial accuracy of +/- 1ppm. High impedance amplifiers standard on M1 and 3000APlus. Call for additional features on all three counters.

**CUB \$149**  
**M1 \$199**  
**3000A+ \$299**

SAVE \$50 on the M1 & 3000A+

Antennas Sold Separately


## OPTOTRAKKER



- Decodes CTCSS, DCS, LTR, Motorola Type I and II, and DTMF
- Scan multiple trunked systems at the same time under computer control
- All trunked frequency bands supported, including 400MHz, 500MHz, 800MHz and 900MHz
- Built-in Data Slicer Circuit
- Pass through technology requires only one com port

**\$299** Includes Software

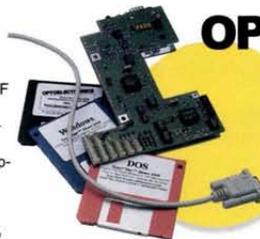Receivers supported under computer control: Icom R7000, R7100, R8500, R9000 and R10, AOR AR8000, AR3000A, AR5000, and Pro 2005/6 with OS456/OSLite, Pro 2035/42 with OS535



## OPTOSCAN

- Computer control scanning interface board for the popular RadioShack Pro 2005/6 (OSLite) and Pro 2035/42(OS535).
- Decode CTCSS, DCS, and DTMF with OS535 only
- Supported by popular third party software

**\$175** SAVE \$24  
OS456Lite: \$99



## TECHTOYZ

Micro Test equipment in pager style cases featuring a 2000 character DTMF decoder, a Frequency Counter with three memory hold, and an RF Detector with settable threshold alarm.

**Micro Counter \$99**  
**MicroDTMF \$99**  
**MicroRF Detector \$149**

TMC100 Antenna Sold Separately (\$9)

## FACTORY DIRECT ORDER LINE 800-327-5912

Made in the

**U.S.A**

www.optoelectronics.com

**OPTOELECTRONICS®**

5821 N.E. 14th Avenue • Ft. Lauderdale, FL • 33334

Telephone: (954)•771•2050 Fax: (954)•771•2052 EMail: sales@optoelectronics.com

Prices and Specifications are subject to change without notice or obligation

The OptoCom has not been approved by the Federal Communications Commission. This device may not be sold or offered for sale until the approval of FCC has been obtained. Contact Optoelectronics for information on availability. Optoelectronics, ScanStar, Motorola, EF Johnson LTR and Microsoft Windows are all registered trademarks. Scout, 3000A+, R11, Xplorer, MicroCounter, M1, Cub are covered by U.S. Patent No. 5,471,402.

**FIVE INDIVIDUAL  
CONTROLLERS  
FOR FULL PERFORMANCE.**

**HIGH PERFORMANCE  
INTEL EMBEDDED  
RISC PROCESSOR.**

**COPIES EVERYTHING:  
PARTITIONS, O/S,  
PROGRAMS - THE WORKS!**



**SURFACE ANALYZER FOR  
PERFECT COPIES.**

**COMPLETE SYSTEM - NO  
PC CONNECTION REQUIRED.**

# COPY HARD DRIVES INSTANTLY!

"THE FASTEST WAY WE'VE FOUND TO MASS PRODUCE SYSTEMS." ANDY HSU, GENESIS TECHNOLOGY

**BUY MANUFACTURER DIRECT: \$895**

**408 330-5543**

## **FOUR DRIVE DUPLICATOR**

Copy entire hard drives with ease. Drive duplicators are an essential tool for dealers and system builders. Why spend hours installing and formatting drives when you can clone four at once? This high speed, stand-alone IDE copier is easy to use and totally self-contained.

Set up any IDE or Ultra-DMA drive with all your original software. Connect blank drives and press "copy". You'll completely duplicate

four drives faster and more accurately than you can copy just one on a PC!

Notebook and desktop drives are supported. Five separate ports let you copy drives at full speed without changing jumpers. Other copiers slow down with two or more drives attached. This true parallel transfer duplicator runs at full speed regardless of the number of drives attached. The built-in surface

verification scans drives for perfect data integrity.

Call now and get the duplicator chosen and approved by Computer Sciences, IBM, and Maxtor.



**CORPORATE SYSTEMS CENTER**


3310 WOODWARD AVE., SANTA CLARA, CA 95054

[WWW.CORPSYS.COM](http://WWW.CORPSYS.COM)

This product is sold and intended for legitimate in-house duplication purposes only.  
Copyright laws must be observed.

New Year's Resolution #1


"I will run faster  
in 1999."

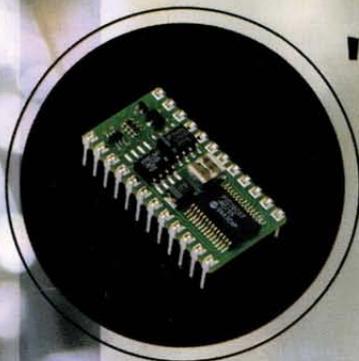

In fact, the BS2SX-IC runs 2.5 times faster than the BS2-IC! With a 16K Byte EEPROM storing up to 4,000 lines of PBASIC code, the BS2SX-IC is an ideal solution for BASIC Stamp customers who have been limited by speed, program size, and RAM. Documentation is available at our website.

Price is \$59 quantity one (1) and it's available today. Interpreter chip OEM format will be available early 1999.

INTRODUCING the  
BASIC Stamp II SX!

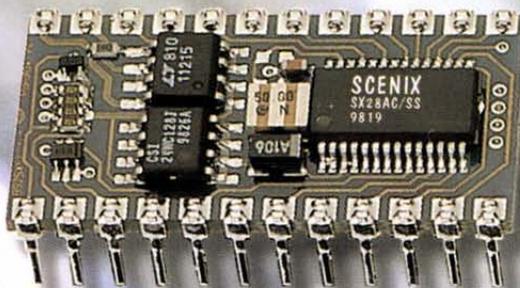

	BS2-IC	BS2SX-IC
Microcontroller	Microchip PIC 16C57	Scenix Semiconductor SX28AC/SS
Program Execution Speed	4,000 instructions/sec.	10,000 instructions/sec.
Processor Speed	20 Mhz	50 Mhz
Program Memory Size	2k Bytes	8 programs x 2k Bytes ea. (16K Bytes)
RAM Size	32 Bytes	32 Bytes
Scratch Pad RAM	N/A	63 Bytes
Current @5V	8ma Run/100µA Sleep	60ma Run/200µA Sleep
Source/Sink Current per I/O	20mA/25mA	30 mA/30mA

**PARALLAX** 

To order call **916.624.8333**  
For more information please visit our  
website at <http://www.parallaxinc.com>

BASIC Stamp and the Parallax, Inc. logo are registered trademarks of Parallax, Inc.  
Scenix is a registered trademark of Scenix Semiconductor, Inc.  
Microchip is a registered trademark of Microchip, Inc.

Write in 194 on Reader Service Card.

**NUTS & VOLTS MAGAZINE**  
430 PRINCELAND COURT  
CORONA, CA 91719

CHANGE SERVICE REQUESTED

BULK RATE  
U.S. POSTAGE  
**PAID**  
PERMIT No. 49  
LONG BEACH CA

