

Enter the ExpressPCB/Nuts & Volts **ELECTRONICS DESIGN CONTEST** and **WIN!!!**

Nuts & Volts

May 2000
Vol. 21 No. 5

Exploring Electronics And Technology For A New Millennium

**Build Your Own Printer
Port LED Array Sign**

**Tools and Techniques
For Robot Builders**

**Monitor 16 Video Cameras On
Your Computer And Control the
Position of Each**

www.nutsvolts.com

- AMATEUR ROBOTICS
- BASIC STAMP
- COMPUTER CONTROL
- IR DETECTOR

U.S. \$4.50 CANADA \$6.50



PROFESSIONAL DISK DUPLICATION

CLONE, TEST OR REPAIR ANY HARD DRIVE

\$995!



- SUPPORTS IDE, SCSI, SCA & NOTEBOOK DRIVES
- COPIES AND SERVICES HARD DRIVES
- PRINTS TEST REPORTS ON YOUR PRINTER
- DATA RECOVERY MODE BUILT-IN

Copy entire hard drives with this pro service station. Set up any SCSI or IDE drive with your original software. Attach a blank drive and press start. Make copies quickly and easily.

Use the built-in drive service system to make used drives run like new! Eliminate defective sectors, and restore hard drives to error-free condition with the factory re-mapping system. Test hard drives for top reliability using the built-in test feature. Print analysis reports on any standard parallel printer. Get the technology used by drive repair services. Call today!

25GB MP3 PLAYER

\$395!
after mail-in rebate



- PLAYS OVER 10,000 SONGS FROM HARD DISK!
- PLAYS STANDARD AUDIO AND MP3 CDs AND CD-R
- DOWNLOADS MP3 FROM CD-R TO HARD DRIVE
- POWER AMPLIFIER DRIVES SPEAKERS DIRECTLY

MP3 is here! Get high performance digital sound and store over 15,000 songs on hard disk. Download over 300 songs from a single CD!

Grab new music from the net. Use your PC to create custom MP3 CDs with just the songs you like. Load them to the internal hard drive for realistic, 3-D theater sound. Patented digital signal processing gives you crystal clear sound. No PC connection is required. Connect any stereo system, or directly power external speakers. Get digital sound and room-filling bass.

The hard drive organizes your music in folders. ID-3 tags display the title, album, and artist on a large LCD. Use the jukebox feature for an entire evening of great music. Play songs randomly or in sequence from the internal hard drive. Unlike CD changers, the A/V certified 25 GB hard drive won't wear out, even under continuous use. Call now and try your MP3 player tomorrow!

CORPORATE SYSTEMS CENTER

3310 WOODWARD AVE. • SANTA CLARA, CA 95054

WWW.DUPEIT.COM

408 330-5524



Over 80% of the Fortune 500 depend on CSC products. Shouldn't you? Call today. Most orders ship within 24 hours! Call now for more information and a free price comparison guide. Quantity discounts are available for dealers and system builders. Copyright laws must be observed when duplicating CDs and hard drives. © 2000 CSC.

COPY ANY CD NOW NO PC REQUIRED

from \$995!



- MULTI-FORMAT DUPLICATION - FAST AND EASY!
- DUAL 8X DRIVES MAKE TWO COPIES AT ONCE
- INTERNAL 25GB HARD DRIVE STORES IMAGES
- PRO AUDIO MODEL HAS SP/DIFF AND ANALOG I/O

Instantly copy music and CD-ROM compact discs. Make backup copies of your favorite music and software on rugged, permanent CDs. Produce discs quickly and economically. Make custom audio CDs with just the songs you like.

Use our dual drive units to copy two CDs simultaneously, or choose the Pro Audio model to make crystal clear music CDs from any analog or digital source. Dupe-It copiers are totally self-contained. No additional software or hardware is required. Call today for more information!

MULTI DRIVE IDE DUPLICATORS

from \$495!



- COPIES EVERYTHING, PARTITIONS, O/S, THE WORKS!
- BOTH STANDARD AND ULTRA, FOUR AND SEVEN DRIVE MODELS ARE AVAILABLE NOW!
- THE ULTIMATE HIGH SPEED PRODUCTION TOOL FOR SYSTEM BUILDERS AND CORPORATE MIS

Copy entire hard drives with ease. Multi-drive duplicators are an essential tool for dealers and system builders. Why spend hours installing and formatting drives when you can dupe them instantly? Work like the pros. Get your own multi-drive, stand-alone duplicators today. CSC offers a complete line of four and seven drive copiers in both standard and ultra versions. Ultra models transfer data faster than any hard drive! Rates of over 1GB per minute are supported.

Set up any IDE drive with all your original software. Attach blank target drives, and press "start". It's that easy! You can duplicate four drives in less time than it takes to copy one on a fast PC! Your duplicate drives will be identical, bit-for-bit perfect copies, with all the files, partitions, and information on the original drive. Building systems is tough enough. Why spend hours installing software? Save time. Save money. Call today and let us Fed-X your duplicator for a risk-free evaluation!

HSC Electronic Supply

Serving
Silicon Valley
since 1964!

...brings you a potpourri of high-tech goodies for the techno-tinkerer!
For thirty years we have been your source for Silicon Valley exotica!

License-Free Two-Way Radio!

- ◆ Fanon "Courier KF-310, factory-new in box!
- ◆ Stay in touch at the park, in the mall or on the road!
- ◆ Transmits up to two-mile range without a license
- ◆ Full-power (.5W) with extras not found on others!
- ◆ LCD backlit display for use day or night
- ◆ Uses new "Family Radio Service band" -- all 14 channels, plus 38-channel CTCSS encode-decode
- ◆ VOX or Push-to-talk, w/3-type call tone
- ◆ Auto "power save" mode, auto-squelch
- ◆ Monitor button, speaker/mic jack, wrist strap
- ◆ Uses four "AAA" batteries (not included)
- ◆ Perfect for camping, sports, road trips, work...more!



HSC#18198 \$49.95/ea
...or Get TWO for \$89.95

Lucent 56K Modem!


- ◆ Digitan Systems - Model DS560-548
- ◆ 56K, V.90, for Windows 95/98
- ◆ New, OEM pack
- ◆ 90-day warranty
- ◆ Lucent chip set, PCI bus
- ◆ Can modem prices get any lower?
- ◆ Drivers available at: <http://www.digitan.com>



HSC# 18179 \$19.95

Tiny Color CCD Camera!

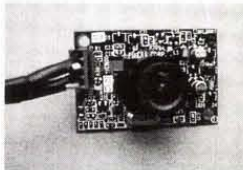
- ◆ Camera-on-a-board measures 1.87" x 1.3", 1" thick!
- ◆ Has glass micro-lens element, not pinhole lens
- ◆ DSP on board for auto white-balance, shutter
- ◆ Standard NTSC composite video output
- ◆ 350 lines horiz. resolution, good low-light sensitivity
- ◆ Uses 4 - 5 VDC, only 150 mA! Three AA batteries would power it for over six hours!
- ◆ New in OEM pkg. (no box), 90-day HSC warranty



HSC#18209 \$69.95

MMX Motherboard Special!

- ◆ High quality DFI brand motherboard, model P5BTX/L, AT form-factor
- ◆ Intel 82430TX "PciSet" chipset
- ◆ For Pentium MMX 166/200/233 MHz processors (Socket 7)
- ◆ Also supports a wide range of Cyrix, AMD & IDT CPUs, up to 300 MHz! (Note: CPU not included)
- ◆ 8MB to 256MB of memory capacity, two DIMM and four SIMM sockets
- ◆ DIMM sockets use x64 EDO (60/70ns), fast-page mode (60/70ns), or SDRAM (10/12/13ns), 3.3V
- ◆ 72-pin SIMM sockets use EDO or fast-page mode, 60/70ns, x32 DRAM
- ◆ Level 2 cache memory, 512KB pipeline burst, direct map write-back
- ◆ Four dedicated PCI slots, three dedicated 16-bit ISA slots
- ◆ 2-SIO, 1-PIO, Floppy controller, Dual IDE controller
- ◆ PS/2 mouse port, PS/2 or AT keyboard port
- ◆ IrDA interface, header for external USB, Award BIOS (Flash EPROM)
- ◆ AT power connector, port connectors/cable, manual, update disk
- ◆ New in box, with manual, 90-day warranty

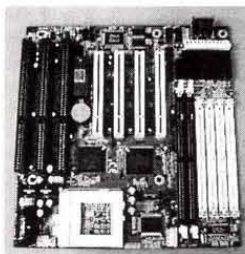

HSC# 18169

\$39.95

Keyboards for any hand!

- ◆ Stylish SEGA unit, features low profile shape
- ◆ Fashionable all-black housing & keys, white markings
- ◆ PS/2 type Mini-DIN connector on black coil-cord
- ◆ Foldout legs for inclining keyboard
- ◆ New with 90-day HSC warranty

HSC#18200 \$12.95

- ◆ 101-key bargain keyboard -- rock-bottom price!
- ◆ Perfect for that startup system...or as a backup, get several at this price!
- ◆ Beige color, AT-style 5-pin DIN connector
- ◆ New, in box, 90-day warranty

HSC#18205 \$7.95

- ◆ 104-key keyboard with AT-style 5-pin DIN connector
- ◆ Windows 95/98-ready, special-function menu keys
- ◆ Excellent starter or backup keyboard for those who want the extra keys
- ◆ Beige color, new in box, 90-day warranty
- ◆ Check the price/feature ratio!...another HSC Bargain!

HSC#18206 \$9.95

Price Breakthrough on Variable Transformers!

You say you've wanted one of these in the past, but the price kept you away? Now you can afford a brand-new variable AC supply for your workbench! All have enclosed cases, knob and dial.

- ◆ Model AICVR-500W, 120 VAC input
- ◆ 0 - 120 VAC output, 500 watts
- ◆ Measures 5" dia., 6" tall
- ◆ Features meter, binding post terminals for input, output
- ◆ New in box, made in China

HSC#80474 \$50.00

- ◆ Model AEEC-1090VR, 120 VAC 60 Hz input
- ◆ 0 - 120 VAC output, 1 KVA
- ◆ Measures 6.5" dia., 8" tall
- ◆ Features meter, illuminated switch, line cord, fuse
- ◆ New in box, made in China

HSC#80481 \$85.00

- ◆ Model AEEC-2090VR, 120 VAC 60 Hz input
- ◆ 0 - 120 VAC output, 2 KVA
- ◆ Measures 8" x 10" x 8" tall
- ◆ Features meter, illuminated switch, line cord, fuse
- ◆ New in box, made in China

HSC#80461 \$125.00

Multimeter Specials!

- ◆ Model #AEEC-1890 DMM with extras!
- ◆ 3 1/2 Digit LCD
- ◆ Adjustable Flip-Up display for the easiest viewing ever!
- ◆ 0.5% basic accuracy, dual-slope integration A/D converter
- ◆ Measures AC/DC volts, Ohms, Current, Capacitance & hFE
- ◆ Ranges: 1000VDC, 700VrmsAC, 200 ohm - 200 Megohm, 20 mA - 20A, 2nF - 20 uF, NPN/PNP hFE.
- ◆ Separate jacks for capacitors and transistors
- ◆ "HOLD" function to capture measured peaks
- ◆ Yellow soft rubber cradle protects meter and prevents spills
- ◆ Brand New! - With Test Leads
- ◆ Compare at prices of \$70, \$80 and up!



HSC#80504 \$39.95

- ◆ Inexpensive Digital Multimeter is packed with features!
- ◆ 0.5% Basic Accuracy, 19 scales, battery included!
- ◆ Ohms, Volts DC & AC, Milliamps DC & AC, 10 Amps DC
- ◆ Diode Tester, Transistor checker
- ◆ With test leads, instructions
- ◆ New, 30 day warranty



HSC#80370 \$14.95

Miscellaneous Goodies!

- ◆ Dexxa Game pad for PC -- rev up those games!
- ◆ HSC#17825 \$7.50
- ◆ Refurbished 4X SCSI CD-ROM drive, 90 day warranty
- ◆ HSC#80512 \$14.95
- ◆ Generic PS/2 mouse, fast tracking! New in box
- ◆ HSC#18146 \$2.95
- ◆ DX-4-100 486 motherboard, no CPU, new bulk-packed
- ◆ HSC#18166 \$9.95

Attention RF Hackers!

For those whose interest ranges into the area of microwave frequencies and beyond...a rare purchase allows us to present you with some high-tech high-frequency goodies!

- ◆ Two active IF mixers and circulators
- ◆ Circulators are Dorado, Part# 13402-001 & -002 feeding a large copper milled dual 6 place comb filter.
- ◆ IF in mixer marked CTR-60703 R
- ◆ IF out mixer marked CTR-960701R with SMA flex guide to a 7 place comb filter
- ◆ Units are new, unused with test spec. sheets



HSC# 80524 \$99.00

Notebook Disk Drive Deal!

- ◆ Seagate ST9655AG 2.5" hard disk drive
- ◆ 524.5 MB, 1016 cyl., 16 heads, 63 sectors
- ◆ Measures only 2.75" x 4" x .75"
- ◆ Standard 47-pin 2.5" IDE connector
- ◆ Factory refurbished, 90 day warranty




HSC# 18164 \$34.95

Unique Project Base for Video Hackers!

- ◆ Perfect for experimenters, tinkers and the just curious...Logitech Videoman videoconference camera system!
- ◆ These were sold with Hewlett Packard S-700 UNIX workstations for videoconference capability
- ◆ We have technical data sheets for the camera. A condensed information sheet is included with camera pinouts and basic specs. Full specification document (camera only) available for \$2.00 (cost of printing)
- ◆ The camera is on a weighted stand that extends from 13" tall to over 20" tall
- ◆ Color camera is digital output only (not NTSC as was previously believed)
- ◆ Note: HP and Logitech will provide no information on these items!
- ◆ Interface box has two SCSI-II ports on back, and a DC power input (we do not have the adapter), and on the front it has a mic, out jack, composite video input (BNC), and the connector for the camera cable.
- ◆ Units are new!

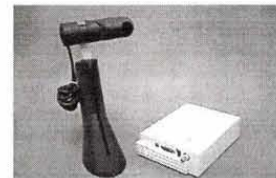HSC#17503 Lower Price for set! \$19.95
HSC#17503a Camera Only \$12.50
HSC#17503b Interface Only \$12.50



Halted specialties co. HSC Electronic Supply

Toll Free (Orders Only) 1-800-4 HALTED
Internet World Wide Web:
3500 Ryder St., Santa Clara, CA 95051
4837 Amber Ln., Sacramento, CA 95841
5681 Redwood Dr., Rohnert Park, CA 94928

(1-800-442-5833)
<http://www.halted.com>
(408) 732-1573
(916) 338-2545
(707) 585-7344

FAX your orders to:
(408) 732-6428



Visit HSC's Website!

- ◆ Pay us a virtual visit on the World Wide Web!
- ◆ Simply point your browser to <http://www.halted.com>
- ◆ Site is constantly being revised, please visit often!
- ◆ Or, you can email your order to hscmail@halted.com

HSC Catalog online!

- ◆ That's right, get HSC's catalog on the World Wide Web!
- ◆ Simply go to www.halted.com and follow the big red link.
- ◆ Adobe .PDF files are available for download and viewing.
- ◆ Or drop on by and pick one up...we'd love to see you!

Terms: Some quantities limited; all items subject to prior sale. Minimum order: \$10.00 plus shipping. Orders under \$20.00 subject to \$2.00 handling fee, in addition to shipping. All orders shipped FOB Santa Clara, CA (this means you pay freight!) by UPS Surface (no P.O. Boxes) unless otherwise specified, in which case prevailing carrier rate plus \$5.00 handling fee applies. Prepaid orders that do not include shipping charges will be shipped freight COD. There is a \$5.00 UPS charge added to shipping charges for COD shipments. If you have questions about your order, please call Customer Service at (408) 732-1854 M-F 9AM to 5PM PST.

THE ALL NEW MULTICOUNTER

\$399



TA100S Antenna Included
U.S. Pat. No. 5,471,402

Optoelectronics presents the **NEW Multicounter** CD100 Counter / Decoder.

The **Multicounter** combines a frequency counter and tone decoder in one handheld package. As the **Multicounter** locks onto a nearby RF signal, the frequency along with either **CTCSS**, **DCS**, **LTR**, or **DTMF** is instantly shown on the two-line LCD display.

Like the popular Optoelectronics Scout, the **Multicounter** also **Reaction Tunes** many radios for instant monitoring of the frequency captured.

ORDER NOW

The **Multicounter** is so easy to operate that it is ideal for quick radio checks by a two-way radio technician or the hobbyist looking for unknown frequencies and tones.

FEATURES

- 10MHz - 1GHz Frequency Range
- Measures frequency and tone in < 1 second
- Decodes CTCSS, DCS, LTR, and DTMF
- LTR displays Area code, Go to Repeater, Home Repeater, ID, and Free repeater
- Built-in .5ppm TCXO for accurate frequency measurement
- Reaction Tune the ICOM R10, R7000, R7100, R8500, R9000, AOR AR8000, AR8200, OS456/Lite, OS535, Optoelectronics R11, and Optocom.
- Two Line LCD Display with EL backlight
- Internal memory for frequency / tone measurement
- Download memory to PC with optional Optolinx PC interface
- Patented Digital Auto Filter



Reaction Tune
Scanner Not Included

OPTODIRECT 800-327-5912

OPTOELECTRONICS

5821 NE 14th Avenue • Ft. Lauderdale, FL 33334 • Visa • MasterCard • C.O.D. •

Prices and Specifications are subject to change without notice or obligation

Tel: 954-771-2050 Fax: 954-771-2052 Email: sales@optoelectronics.com Internet: www.optoelectronics.com

Contents

10. Ham Gear for Sale	37	120. Components	57
20. Ham Gear Wanted	0	125. Microcontrollers	58
30. CB/Scanners	37	130. Antique Electronics	58
40. Music & Accessories	0	135. Aviation Electronics	58
50. Computer Hardware	38	140. Publications	58
60. Computer Software	38	145. Robotics	59
70. Computer Equip. Wanted	38	150. Plans/Kits/Schematics	59
80. Test Equipment	39	155. Manuals/Schematics Wanted	0
85. Security	40	160. Misc. Electronics For Sale	59
90. Satellite Equipment	41	170. Misc. Electronics Wanted	60
95. Military Surplus Electronics	42	175. BBS & Online Services	61
100. Audio/Video/Laser	42	180. Education	0
110. Cable TV	56	190. Business Opportunities	61
115. Telephone/Fax	57	200. Repairs/Services	61

Advertiser's Index	81
Classified Ad Info	80
Dealer Directory	75
Events Calendar	30
New Product News	93
News Bytes	12
NV AdMart	68-70
NV Bookstore	46
Prize Drawing	47
Reader Feedback	7
Tech Forum	34

Call our subscription order only line at 1-800-783-4624

In this issue

TOOLS AND TECHNIQUES FOR ROBOT BUILDERS

8 Karl Lunt

You can blue-sky all kinds of ideas for a robot to build, but sooner or later, you have to start making a frame, dealing with electronics, and writing code. This article will describe some simple tools and techniques to help you get your robot going sooner.

FET PRINCIPLES AND CIRCUITS 14 Ray Marston

Part 1: Learn the basics of Field-Effect Transistors in this opening segment of a four-part series.

BUILD A WATCHDOG TIMER USING THE PC SPEAKER OUTPUT

43 Mike Keryan

How do you get a stand-alone system to automatically recover from a lock-up and continue running its programming? Check out this watchdog timer circuit you can build yourself. It monitors the PC speaker rather than an I/O address and only costs around \$10.00.

MAKE YOUR OWN PRINTER PORT LED ARRAY SIGN FOR AROUND \$50.00

48 Robert Davis

Got a message to flash? This article is about a programmable sign that connects to a computer's printer port. It is both useful and versatile.

BUILD AN INFRARED DETECTOR 71 Fred Blechman

They are everywhere!!! What? Infrared (IR) remote controls. Build this simple circuit to test infrared remote controls. It uses only 10 common electronic parts. No PCB is required and a common nine-volt battery will last "forever."

DIGITAL ALARM CLOCK 82 Brian Beard

Alarm clocks have become so common and cheap, that it's hard to find a construction project for a complete alarm clock. This article is just that — a complete alarm clock, from the power supply to the case.

MORE ON 121.5 MHz 87 Gordon West

Last month, the importance of the emergency locator beacon service at 121.5 MHz and the relatively new 406.025 MHz datastream was described. This month, learn how rescue personnel can get activated and on-scene faster when GPS coordinates are also carried in the signal.

NUTS & VOLTS (ISSN 1065-2035) IS PUBLISHED MONTHLY FOR \$19.00 PER YEAR BY T & L PUBLICATIONS, INC., 430 PRINCELAND COURT, CORONA, CA 92879. PERIODICALS POSTAGE PAID AT CORONA, CA AND AT ADDITIONAL MAILING OFFICES. POSTMASTER: SEND ADDRESS CHANGES TO NUTS & VOLTS, 430 PRINCELAND COURT, CORONA, CA 92879-1300.

AMATEUR ROBOTICS NOTEBOOK 63 Robert Nansel

Explore the topic of integrated H-bridges.

ELECTRONICS Q & A 52 TJ Byers

OPEN CHANNEL 76 Joe Carr

Dealing With AC Power Line EMI. AC power line harmonics and spark hash can create havoc with radio reception. But with the methods discussed this month, you will be able to overcome many of these problems.

STAMP APPLICATIONS 22 Jon Williams

Stamping Myself Into Better Shape. Build an exercise timer and review practical project development tips in the process.

THE COMPUTER-CONTROLLED WORLD 89 Ryan Sheldon


Video for Windows (Part 2). Watch 16 video cameras in a Windows 98 window and control the position of each camera.

Enter the Nuts & Volts and ExpressPCB Electronics Design Contest

**CONTEST ENTRY DEADLINE:
JULY 19, 2000**

1.


**Go
from
this:**

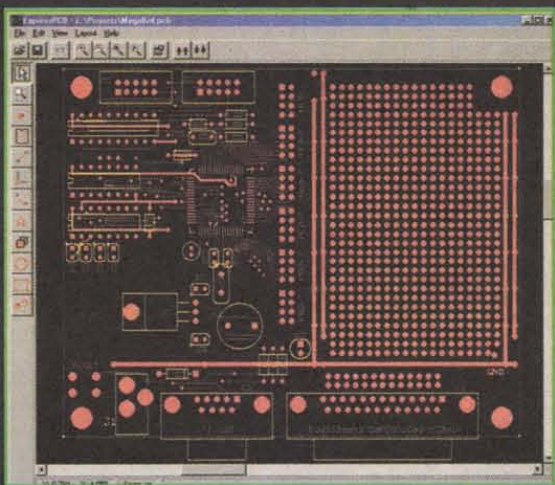

This is a sample project for our design contest. The first step is to lay out a circuit board using the ExpressPCB editor. Your project could be robotic like this one, or related to telecommunications, ham radios, PC computer devices, microcontrollers, scientific equipment, data logging, or almost anything else using an electronic circuit.

2.


**To
this:**

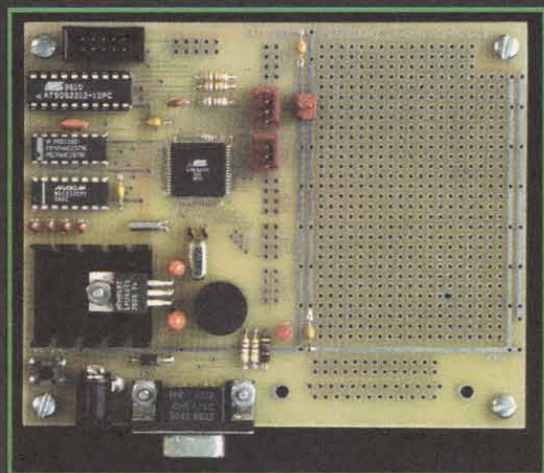

This circuit board controls three RC-servos. The heart of the electronics is a surface-mount Atmel ATmega microcontroller.

3.

**To
this:**

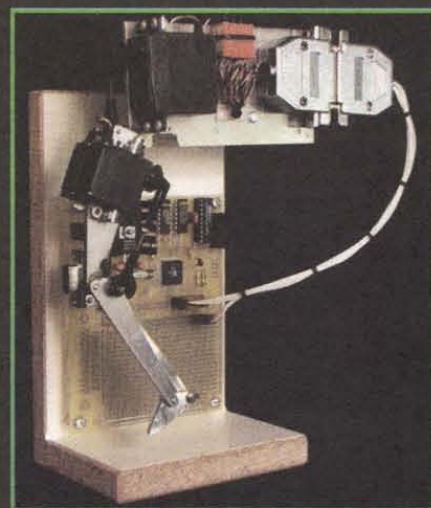

This robotic leg and foot was originally designed for movie special effects. It is a prototype mechanism used to animate small creatures.

1st Prize

**Tektronix TDS-210
Digital Oscilloscope**

2nd Prize

Palm Pilot V Organizer

3rd Prize

Palm Pilot V Organizer

Contest Rules:

- Enter the contest by submitting a written description and photographs of a working electronic project that you have designed.
- Each project must be built using an ExpressPCB circuit board.
- The circuit board must have been designed by you using the ExpressPCB layout program.
- One grand prize and two second prizes will be awarded to the most interesting projects.
- The winning projects will be announced in the September 2000 issue of *Nuts & Volts* and on the ExpressPCB website. Project photographs and descriptions will be published for each of the winners.
- All entries must be received on or before July 19th, 2000.
- Please note: The materials submitted with each contest entry will become the property of *Nuts & Volts Magazine* and will not be returned.

How to enter:

- Each contest entry must include:
- Your name, address, phone number, and E-Mail address.

- A written description of your project, about 250 to 500 words.
- A close-up photograph showing your assembled circuit board.
- One or two photographs of your completed project shown in use.
- The confirmation number given when your ExpressPCB circuit boards were ordered.

To enter by mail, send a hardcopy of your contest entry to:

Nuts & Volts Magazine
Design Contest
430 Princeland Court
Corona, CA 92879

To enter by E-Mail, send a single PKZip attachment to: designcontest@nutsvolts.com. PLEASE DIRECT ANY QUESTIONS TO: support@expresspcb.com.

Note: Project descriptions must be Microsoft Word documents or text files and photographs must be high resolution .TIF or .JPG files (.TIF preferred).

Reader Feedback

Dear Nuts & Volts:

Although most of the theory in *Nuts & Volts* remains way over my head, I do assimilate more and more information with each passing month. I attribute that to good and consistent writing. Yours is one of the few information sources that is virtually devoid of typographical errors. That alone makes it a pleasure to read!

I am in the midst of taking Heathkit's Master Course in Electronics. When combined with your quality magazine, it has really helped me understand ideas that I could not understand previously. Thank you for helping to make me feel more at home in the technological wilderness.

John Branco

On March 25th, JRL wrote to Steve Parkis:

I am having a problem with the second part of the "Building a better mouse trap" articles. Part one is working fine. But when I download the minmouse.bs2 file from the *Nuts & Volts* site, the file actually is not a BASIC Stamp file at all, but looks like the SX28 interface file. There is no SX28 interface file for the STAMP program on the *Nuts & Volts* site. I tried to change the name of the minmouse.bs2 file to a .src file, but it does not assemble with the SX28 key. Lots of undefined symbols.

Looks like two files are missing for part 2. The SX28.src interface file and the minmouse.bs2 file. Is this the case?

Thanks for the articles, we are hoping to get both a keyboard and a mouse connected to one stamp.

JRL

Looks like the files got mangled somehow. Am attaching zip'ed copies of MINMOUSE.BS2, MOUSESMNU.BS2 and bs2mouse.src for your convenience. Glad to hear somebody is looking at this closely enough to notice the problem, and I hope this helps!

As a former customer of clark.net (I've since escaped out west to Nevada), may I offer my condolences on your residing in the DC area.

Regards,
Steve

You can download these corrected files from the *Nuts & Volts* website at www.nutsvolts.com

Dear Nuts & Volts:

I have some new information on sources of used voltage dividers to update my article that appeared in your Jan. 2000 issue.

See below ...

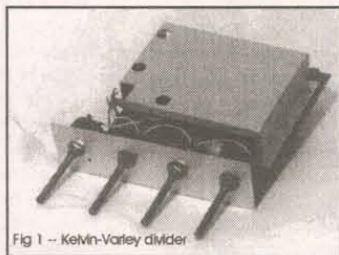


Fig 1 - Kelvin-Variety divider

Published Monthly By T & L Publications, Inc.
430 Princeland Court
Corona, CA 92879-1300
(909) 371-8497
FAX (909) 371-3052

E-Mail — editor@nutsvolts.com
URL — <http://www.nutsvolts.com>

Subscription
Order ONLY Line
1-800-783-4624

PUBLISHER
Jack Lemieux N6ZTD

EDITOR
Larry Lemieux KD6UWV

MANAGING EDITOR
Robin Lemieux KD6UWS

ON-THE-ROAD EXHIBIT
COORDINATOR
Audrey Lemieux N6VXW

SUBSCRIPTIONS
Abby Madain

CLASSIFIED ADS
Natalie Sigafus

DISPLAY ADS
Mary Gamar

Copyright 2000 by
T & L Publications, Inc.
All Rights Reserved

All advertising is subject to publisher's approval. We are not responsible for mistakes, misprints, or typographical errors. *Nuts & Volts* Magazine assumes no responsibility for the availability or condition of advertised items or for the honesty of the advertiser. The publisher makes no claims for the legality of any item advertised in *Nuts & Volts*. This is the sole responsibility of the advertiser. Advertisers and their agencies agree to indemnify and protect the publisher from any and all claims, action, or expense arising from advertising placed in *Nuts & Volts*. Please send all subscription orders, correspondence, UPS, overnight mail, and artwork to: 430 Princeland Court, Corona, CA 92879.

BUILD YOUR OWN BASIC STAMP 2

Build your own BASIC Stamp II and save \$15! This handy little module is a through-hole version of our popular BS2-IC. With this kit you'll learn how to embed a BASIC Stamp into your own production projects using our PBASIC interpreter chips. After a short soldering session you'll also have the power of a working BASIC Stamp. You supply the serial cable.

The OEM BASIC Stamp II package includes the module, documentation with component sources, and our CD. Measures 5.1 x 5.1 cm.




OEM BASIC Stamp II (#27290 - \$49)
OEM BASIC Stamp II - Kit Form (#27291 - \$34)

PARALLAX

order online www.parallaxinc.com
or call toll-free 888 512 1024 (in the U.S.)

Write in 211 on Reader Service Card.

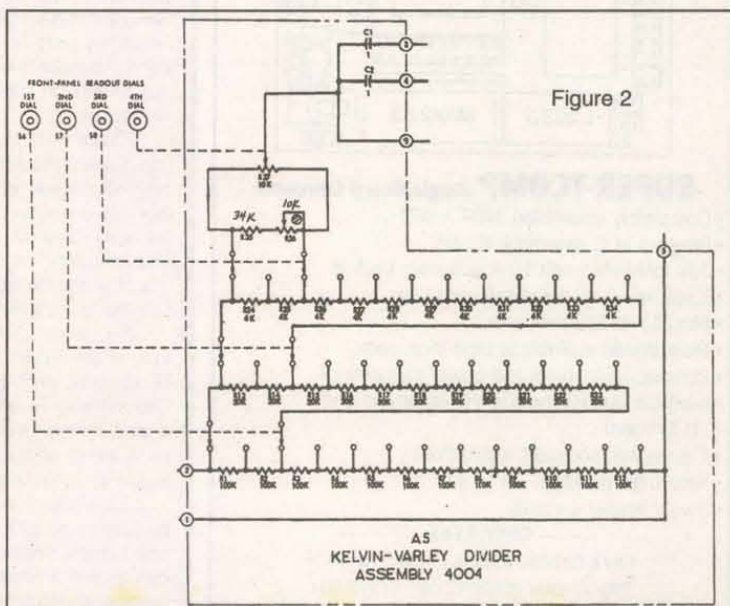


Continued on page 70

Tools and Techniques for Robot Builders

by Karl Lunt

You can blue-sky all kinds of ideas for a robot to build. It might be something simple, like a robopet, or a more challenging design, such as a six-legged walker. And it's great fun to daydream about all the different behaviors your robot will exhibit and the cool gadgets you can add to it.

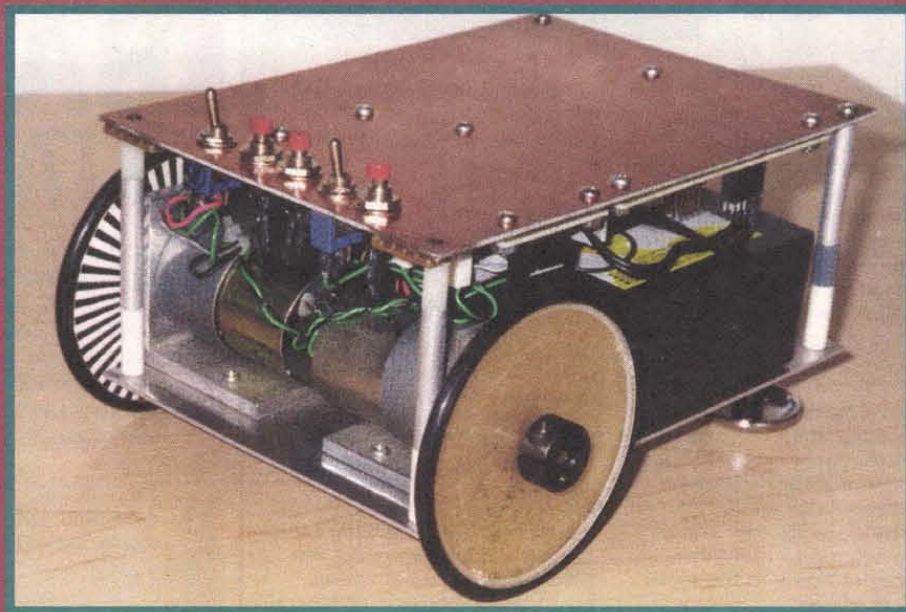But if you're truly serious about building your 'bot, you eventually have to start making a frame or electronics, or writing the code. Each of these elements has many pitfalls that can stall your progress, or make your robot more difficult to build than necessary. This article will describe some simple tools and techniques you can use to help get your robot going sooner.



Wheel mounts

The surplus outfits carry lots of DC gearhead or stepper motors that would be perfect for your next robot. Companies like Marlin P. Jones (www.mpja.com) or American Science and Surplus (www.sciplus.com) offer good deals on high-quality motors from makers such as Vexta, Pittman, Mabuchi, and others. It's pretty easy to find a gearhead motor with a rotation

speed of 100-200 RPM and suitable torque, ideal for that line-follower or maze-runner. Let's assume you've found the perfect 12 VDC gearhead, and the ad tells you it comes with a 6mm diameter shaft. How do you mount a wheel onto your new motor?

I went through this same drill not long ago, designing my latest machine, MBot. This robot measures 7-1/2 inches long by 5 inches wide by 4 inches high, a fairly typical size. I had some nifty 12 VDC gearhead motors laying around that I wanted to use, but I had to mount a wheel 3 inches in diameter by 1/4-inch wide to each 6mm shaft.

My first attempt involved drilling a 6mm hole down the center of a 1/2-inch bolt, then drilling and tapping a hole into the bolt's shoulder for a 4-40 set screw. I've used this technique before, and readers of my past Amateur Robotics column will remember how I used this method to put wheels on robots such as BYRD and Tacklebot.

These were big machines, sporting heavy lawn-mower wheels, and they needed a beefy wheel mounting system. But this mounting method is overkill for a robot as small as MBot. The large bolts and matching nuts looked inelegant and out of place on my little 'bot, and I didn't like the extra weight they added.

So I described what I was looking for in a wheel mount to the guys at a recent Seattle Robotics Society (SRS) meeting. Lance Keizer — a club stalwar — gave me a neat idea for such a mount, and I'll pass along what I did. Refer to the accompanying diagram (Figure 1).

This wheel mount consists of a steel or aluminum split-ring shaft collar of the appropriate diameter, modified so you can attach a wheel to the wall of the collar at one point. When you mount the

wheel/collar assembly onto the motor's shaft and tighten down the collar, you have a non-slip mechanical connection that is light, small, and inexpensive.


Since I needed a little help with the machining, I gathered up my parts and headed over to Dan Mauch's house. Dan — a long-time SRS member — has helped me many times with past projects; he is an experienced machinist with a garage full of tools and materials. As a rule, software people shouldn't operate heavy machinery, and I'm always grateful for Dan's help. (I know there are some software people who can use heavy machinery, but I'm not one of them.)

Dan had already told me which shaft collars to order from the extensive McMaster-Carr mail-order catalog, and at less than \$2.00 each, I consider my 6mm steel shaft collars a bargain. You can dig through the McMaster-Carr catalog by hitting their web site with a Java-enabled browser (www.mcmaster.com).

I had already stopped by the local TAP Plastics store and scooped up some machined three-inch Plexiglass discs, also for less than \$2.00 each. Each disc was made of 1/4-inch thick clear plastic, with protective peel-off paper, and with a smooth edge on the rim. If you have a TAP Plastics or similar store in your area, be sure to check them out. Besides stock items already machined for you, most such shops have a big bin of scraps, and you can find pieces of Sintra, ABS, Plexiglass, and other plastics at excellent prices.

My last stop took me to a local hardware store, where I picked up some 2-3/4 inch diameter by 1/4-inch thick black rubber O-rings. I had already decided to use these as the "tires" for my new wheels. They provide excellent traction, are fairly cheap and easy to get, and I figured they would look way cool on the new wheel design.

Dan began the wheel mount construction

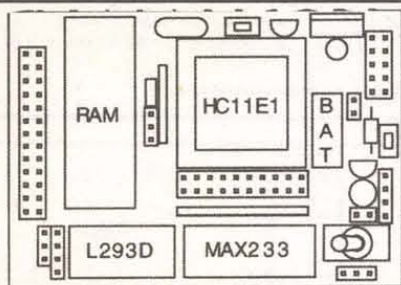

SUPER-TCOMP Single Board Computer

- Completely assembled. NOT A KIT!
- Program in C, assembly, IC, etc.
- 32K RAM chip with 10 year battery backup
- 5 volt low drop-out voltage regulator
- Max233 RS232 converter
- Most signals available at expansion ports
- External mode, reset and power connections
- Available options include I/O expansion and LCD board
- Comes with complete instructions
- Very small package: 2.1" x 3.0"
- 1 year limited warranty

----- ONLY \$145 -----

Ray's Robotic Racers (310) 515-6075
<http://www.teleport.com/~raybutts/>

by drilling a centered 6mm hole in each of the plastic discs. Then he locked a disc and a steel shaft collar together by stacking them on a 6mm bolt and running a nut down on them. He clamped this assembly into a vise on his drill stand, then locked the vise into position on the drill's table. He drilled a hole into each steel shaft collar all the way through the plastic disc, sized to tap for a 4-40 screw. Then, he removed the shaft collar and drilled a hole in the plastic disc, sized to clear a 4-40 screw. Note that he drilled this second hole by running the bit into the smaller hole previously drilled for the 4-40 tap.

To make sure the O-ring would stay on the wheel's rim, Dan next took each disc, minus the shaft collar, and mounted it onto a 6mm bolt, then ran a nut down on it. He clamped this assembly into his metal lathe and spun it up, then used a cutting tool to cut a 3/8-inch groove into the center of the wheel's rim.

All that remained now was to put the assemblies together. I used a 3/8-inch 4-40 bolt through the hole in each disc to clamp it to a shaft collar, keeping the bores of the two units aligned. Then, I carefully stretched an O-ring onto the rim of each disc, seating the O-ring into the rim's groove. Finally, I applied a small drop of Super-Glue to the joint between the disc and the O-ring at one-inch intervals around the rim. When the glue set, my wheel was finished. I slipped the wheel assembly onto a motor shaft, with the shaft collar away from the motor's body, and used a hex wrench on the collar's set screw to clamp the collar to the shaft.

I really like the final product. The wheels have no side-to-side play as they rotate, which means the inner surface stays a fixed distance away from the frame. This is important for robots that need an optical encoder disc mounted to the wheel, for measuring distance traveled. I peeled the protective paper off of the outer surface of each wheel, but left the paper on the inner surface. Now I have a good mounting surface for my encoder discs, but the outer surface is shiny and polished.

The above steps may seem complicated, but they really take just a few minutes when done by an experienced machinist. You end up with sleek, high-quality robot wheels for about \$5.00 each. If you don't own a garage full of machine tools, ask around at your next club meeting, or talk to people at the local vocational school or nearby machine shop. Wheels that look this good on your robot are worth a little trouble to make.

Cheap, efficient power

I use a pair of 12 VDC gel-cell batteries, wired in parallel, to power MBot. This gives me plenty of juice for the motors, but I have to convert this voltage to 5 VDC for the electronics. If you face a similar problem, resist the urge to grab a 7805 linear regulator. Sure, they work, but you will be losing a lot of operating time on your battery because the 7805 is so inefficient.

Linear regulators such as the 7805 generate 5 VDC from a higher voltage by wasting the difference between input and output voltages as heat; the more current you draw through the regulator, the hotter it gets. At 12 VDC input, it doesn't take a lot of current draw to get the reg-

To get details on Karl's book, including price and ordering information, contact the book's publisher, A. K. Peters, Ltd. Their web site is www.akpeters.com. You can also find it at other outlets, including Amazon.com.

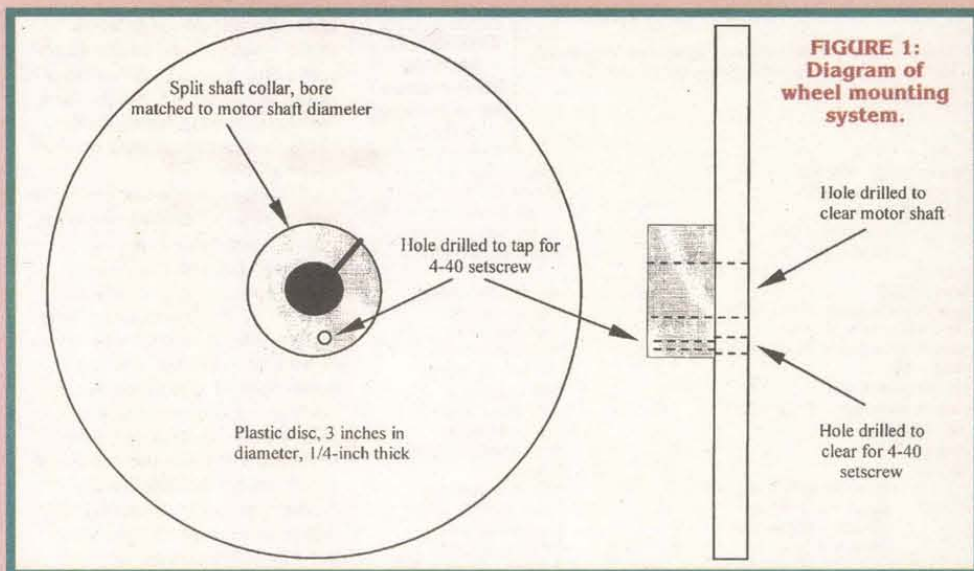


FIGURE 1: Diagram of wheel mounting system.

ulator so hot that it thermally shuts down. A more efficient regulator, such as a switching power supply, lets you use more of that excess voltage to run your robot, instead of heating the room.

National Semiconductor has been offering the SimpleSwitcher® power supply chips for a few years now. I still have one of their free demo boards that they handed out through the mail some time ago. The LM2595 regulator built into this board can supply up to one amp of current at 5 VDC out, with an efficiency of nearly 85%. And National offers a whole range of package designs and current ratings, if you want to try rolling your own board. For details, stop by the National website at www.national.com.

While you're there, check out their LM2675 SimpleSwitcher demo board, available by mail-order for just \$8.00 each for a one-amp switcher. This tiny board contains the full power supply, ready to hook up to your battery (8-40 VDC input). As of now, you can order this board only from the web site, and you must supply a credit card number to do so. Note that you will be giving your credit card info to a third party, contracted with National to handle web orders. I tried calling National's 800 phone number to place the order, and was told they aren't set up to handle this kind of business.

This little switcher board is the perfect addition to any robot design that uses a battery supply in the appropriate range. You can mount it on nearly any insulated surface using little more than double-sided foam tape or hot glue. And you'll really enjoy the longer running times that a switching supply gives you.

Line-following software

I built MBot as a multi-purpose robot. Among other tasks, MBot can carry a pod of phototransistors on its undercarriage, for use in a line-following contest. The line-following sensor array is pretty simple; just a set of five IR phototransistors and five bright red LEDs. Each LED is aimed so it illuminates the floor immediately underneath a matching, down-looking phototransistor. Each phototransistor's output is then fed into a separate analog input on my 68hc11 computer board.

I intentionally chose red LEDs,


rather than IR LEDs, to eliminate long-standing problems with IR emitters and detectors. We think of IR as "light you can't see," but IR behaves very differently from conventional light. For example, a sheet of white paper is translucent (at least) to IR, and a line-following pod that uses IR can get fooled by designs on the underlying floor. I have seen more than one robot veer off-course during a contest, following the design of a floor tile below the maze's paper.

By using red LEDs, I can be sure of where the light will appear, what pattern it makes on the maze surface, and what the photodetector will see. The phototransistors have plenty of sensitivity to the red light to give me a wide signal swing between a white surface and a black line.

But it isn't enough simply to turn on the robot and let it run. The signal returned by a phototransistor can vary, based on parameters such as the whiteness of the paper, the color of the line, and even the consistency of the line's width and darkness. And each phototransistor/

PIC'n Books

LEARN ABOUT PIC MICROCONTROLLERS

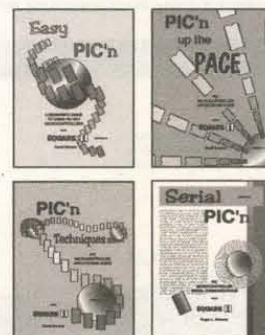

See Table of Contents: <http://www.sq-1.com>
Secure Online Ordering is Available

PIC is a trademark of Microchip Technology Inc.

SQUARE 1 ELECTRONICS

Voice (707) 279-8881 Fax (707) 279-8883

<http://www.sq-1.com>

' Scan routine for determining light/dark thresholds
' for an array of phototransistors in a line-following
' pod.

```
scan:
rpwm = RSCANSPD
lpwm = LSCANSPD
for n = 0 to 4
    vmin(n) = $fff
    vmax(n) = 0
next n
wait = 100
gosub setmotors, FWD, REV
do loop until wait = 0
gosub setmotors, STOP, STOP
wait = 60
do loop until wait = 0
gosub setmotors, REV, FWD
wait = 200
swait = 0
do
    do loop until swait = 0
    swait = LOOPDLY
    gosub read_sensor
    for n = 0 to 4
        if vmin(n) > eyes(n)
            vmin(n) = eyes(n)
        endif
        if vmax(n) < eyes(n)
            vmax(n) = eyes(n)
        endif
    next
loop until wait = 0

' compute the threshold for each eye as:
' threshold = (vmax - vmin) / 2 + vmin
'
for n = 0 to 4
    threshold(n) = rshft(vmax(n) + vmin(n))
next

gosub setmotors, STOP, STOP
return
```

FIGURE 2:
Sample
SBasic code
for scanning
a line.

LED pair will give a different value when looking at the exact same line, owing to differences in physical alignment, height from the floor, overlap from nearby LEDs, and ambient light on the maze surface.

You can take a few measurements in your lab and come up with a reasonable guess for a threshold between white and black, but your guess will only work in your lab and under conditions similar to your test set-up. Move that robot out into the harsh light of a club venue or auditorium, and your threshold values may be so far off that your 'bot can't see the line at all.

A simple solution to this problem involves sweeping all five sensors over the line when the robot first powers up. Software takes continuous samples of all five sensors, recording the highest and lowest readings for each. After the sweep is over, your code can compute a threshold for each sensor, based on these extremes.

Now your program will have a threshold that is tuned to the ambient conditions. Even if one of your sensors is jarred accidentally during handling, your robot will still correct for the new alignment and derive the proper threshold.

I've included a sample

SBasic routine that performs this scan operation, so you can see how the concept works (Figure 2). As usual, I've included a variable called WAIT, which acts as a down-counting timer. A piece of code, not shown here, services the computer's Real-Time Interrupt (RTI) every 4.1 msecs. In the service routine, code tests the value of WAIT and decrements it if WAIT is not zero. This means that anytime code writes a non-zero value to WAIT, WAIT "magically" begins counting down at the rate of about 250 counts per second, stopping when it hits zero. Thus, WAIT and a similar variable — SWAIT — act as timers for various operations in my program.

This isn't a complete program, but it contains enough detail so you should be able to modify it for your own use. I run it on a custom 68hc11 board, but it should work fine on nearly any 68hc11 computer, such as a BOTBoard. As long-time readers of my past columns already know, you can download the latest version of my 68hc11 SBasic compiler from my web site at www.seanet.com/~karllunt.

In closing ...

Speaking of my past columns, I have recently published a book containing some 50 articles from my past Amateur Robotics column for *Nuts & Volts* magazine. *Build Your Own Robot!* is nearly 600 pages long, has an extensive index, and features many of my favorites. I included material for beginner and intermediate hobbyists alike, and I left the column format unchanged. Personally, I think this makes the book good "grazing" material, and I hope you'll spend time browsing through the various articles for ideas for your next machine. **NV**

Have you Outgrown your Stamp?

Take the BasicX™-24 quiz-

Are you running out of RAM?
Are you running out of code space?
Do you need a lot more processor speed?
Do you need Built-in Floating point math?

If you answered yes to any of these questions then it's time you stepped up to the power of the BX-24.


With its 100% stamp compatible pin-out and powerful Basic command set you're just minutes away from breathing New life into your stamp projects!

Hardware Features:

32K EEPROM
400 bytes of RAM
65K+ Basic instructions per second
8 10-bit Analog to Digital Converters
6.5 times faster than the stamp SX1
2 on-chip LEDs
SPI Bus
And More!

Software Features:

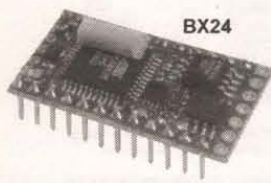Basic programmable
Real Multitasking OS
IEEE Floating Point Math
Serial in or out any pin
Dallas 1 wire support
I2C Support
And Much more!



BX-24 chip \$39.95*
in single quantities



BXK24 Development system \$99.95*

* Introductory price.

www.basicx.com

Order online or call us at 520.544.4567

Test Equipment Connection Corporation

Test Equipment Connection is looking to purchase your excess or underutilized electronic test and measurement equipment. We buy the largest variety of electronic test equipment in the industry.

WE BUY TEST EQUIPMENT



BUY

SELL

RENT

REPAIR

TRADE

Specialist in Hewlett-Packard, Tektronix, and many more manufacturers.

CALL: 800.615.TEST
FAX: 800.819.TEST

WWW.ATESTEQUIPMENT.COM


Upgrade Your Current Laptop Drive FREE Netcom #1 in Customer Service Since 1983

IBM ROAD WARRIOR
Professional Road Equipment
MAXIMUM ABUSE
strictly for professionals

4 Easy payments of
\$199.99
0% Financing!
On Credit Cards only

64% of our Customers call back &
BUY MORE!

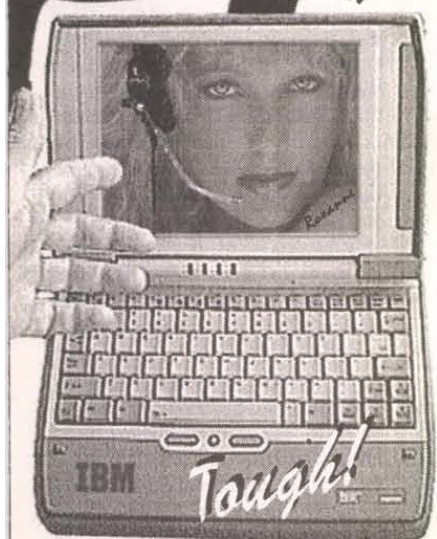GPS
Perfect for Satellite Navigation
Actual Selling Price From IBM **\$6912**



Rain: (4"/hr Rain w/ 40 MPH Winds)
Silicone Rubberized & Diecast Case!
Ultra Shock Mounted 1GIG EIDE Hard Drive!
ESD / EMF & RF Resistant, Works from -4 to 120 Deg F & Vacuum to 15,000 ft

- > 1- PCMCIA (type 1, 2 or 3), Serial & Parallel Ports in rear
- > 16m Ram / 1m Video / 32 Bit Local Bus 486-50 Mhz
- Runs 32 bit applications with Ease
- Math Co-processor, 28.8k Modem (Internet Ready)
- > Very Long Lasting Hydride Battery (\$150 Value)
- > Sound & Microphone,
- > 8.25" Display-64 Shade Monochrome REFLECTIVE
- > (Optional) Touch Screen with Handwriting Recognition
- Rough Service Handle with Loops for optional Shoulder Strap
- Roxanne's Voice Annotates Windows 95 Functions

OPTIONS

- > Floppy Drive \$89 > 12V Carcord \$29
- > Desktop 48X Cd Rom \$159
- > Touch Screen \$250
- > 33k Baud PCMCIA Fax- Modem Upgrade \$35

This was a unique (one shot) purchasing opportunity IT'S NOT OPEN STOCK WHEN THEY'RE GONE, THEY'RE GONE FOR GOOD
Sold till recently by IBM through their Local Area Network Div at \$4,699 & \$6,912 as shown here. (they were never discounted)

233 Low Price / High Performance
Mhz Pentium

4 Easy payments of
\$249!
credit cards only
\$976!
single payment



Our Customers Call back with
Rave Reviews!

233 mhz
3.2 Gig
32m ram
56k modem
CD 24x
USB (2)
W98

Easy Viewing High Resolution Razor Sharp & Bright SVGA 6.5" Display
16 Million Color Display Supports High Res modes up to 1024x768 (WOW)
Comfortable Keyboard with built-in wrist support, Includes CD & Floppy
Super Built-in Stereo Speakers & Mic / Excellent Touch Pad Mouse
3hr Long life Lithium battery / 2 USB ports, IR Port, 2 PCMCIA ports
Serial & Parallel Ports / Super Lightweight 3.3 lb 9.5 x 7 x 1.5
3 Year Warranty (best in the industry) FREE Lifetime Netcom Tech support
OPTIONAL CUSTOM Carrying Case \$24 SOYO Embossed LOGO, Tailored fit, Pockets, Handle & includes Shoulder Strap

SOYO is the leading maker of Computer Motherboards for FAMOUS BRAND NAME computers. The "Traveler" has every "State of the Art" feature you want at a Spectacular price. Runs ANY program with ease. Light weight & Ultra portable




The ONLY Model Laptop that ever Survived Accident in Outer Space

IBM Pentium 75

Huge 10.5" Active Matrix SVGA Color Display
33k FAX MODEM - 2 PCMCIA Expansion Slots
Dual Infrared Ports (Front & Rear)
Track Point Eraser Head Mouse (Very Responsive)
All Standard Ports (1S, 1P, 1V, 1K, 1Bd)
Pop out - Hard Drive, Ram, Battery & Floppy.
Ram & Hard Drive Expandable & Upgradable.
Includes Power Supply & Hydride Battery
Free Lifetime Tech Support Web Site Creator Software
Internet Ready, America On Line (Full install)
Fax Modem Software, Searchable Owners Manual shw, W95
2 Gig Hard Drive 24M Ram

\$792!
single payment
4 Easy payments of
\$215!
Credit Cards only

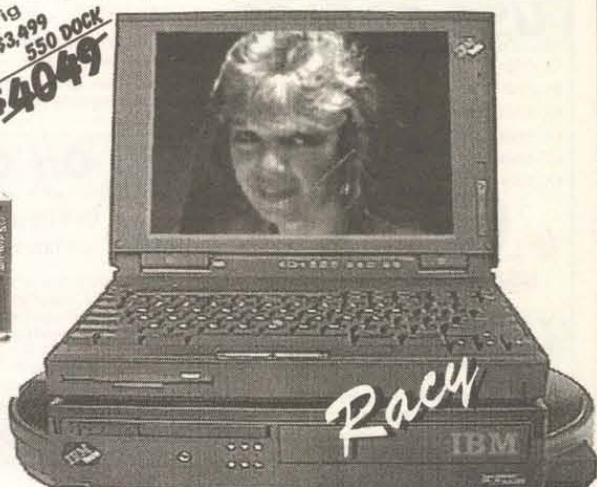Wow
This Model Survived the Russian Space Station Disaster of -200F to 280F in the Vacuum of Space!
Details in email



IBM Docking Station INCLUDED

This is not just a port expander it's a full blown docking station. You can add ANY desktop ISA card and it will work with your IBM laptop. Imagine the possibilities. Add a TV card and watch TV while you compute! ISA computer card hides in the base of the unit.

FREE Local Area Network (LAN) card (a \$79 value) Notebook Snaps onto the dock.
Expansion Port for optional CD Rom Built-in Speakers Built-in Power Supply & Fan
SCSI Expansion Port / Parallel / Serial / Keyboard / Mouse / Monitor / Stereo in & out
Front panel headphone Jack Hidden Carry handle LED Status Indicators
Color Black (matches notebook) ISA Port cover & Key optional (not required)

\$550



ICMaster Earlier Editions Perfect for Service or Lite Design. Later Editions Perfect for Advanced Design

ICM
95 3Book Set \$29 !!!!!!!!!
96 3Book Set \$49 !!!!!
97 3Book Set \$69 !! CD Rom \$ 99!!
98 3Book gone CD " \$129!
99 3Book gone CD gone

EEM Contains the Complete Catalogs of Most Electronic Component Manufacturers & Distributors

IBM
97 4 Book Set only on CD \$35
98 4 Book Set only on CD \$55
2000 4 Book gone

For: DOS, Win 3.1 & 95 & 98

1 Year Warranty - Satisfaction Guaranteed - The Friendliest People - The Best Customer Service

PAYMENT PLAN with Credit Card -or- Layaway ONLY **843-650-5700** For Questions-or-

COD's SINGLE PAYMENT ONLY **ORDERS ONLY 800-733-3733** **ORDERS ONLY** **FAX 843 650 5777 10-8 EST Mon-Fri**

EMAIL for Detailed Information **email: netcomd@aol.com**

Nuts & Volts Magazine/MAY 2000 11

CD Rom Works with ANY Computer

48X! \$159
Cheapest Anywhere

Desktop Parallel Port CD Drive
Built-in Printer Port,
Power Supply
& Audio Output

For: DOS, Win 3.1 & 95 & 98

Newsbytes

SEVEN STUDENTS ARE FIRST AND SECOND PLACE WINNERS IN 18TH ANNUAL DURACELL/NSTA CHALLENGE

100 Student Inventors receive
\$160,000 in Savings Bonds

US middle- school and high-school

students have demonstrated their innovative skills with an impressive array of practical and entertaining battery-operated devices addressing edu-

cational, health, sports, and safety needs in the 18th Annual Duracell/NSTA Invention Challenge.

The first and second place winners invented a portable communications tool, a device for hearing-impaired athletes, a useful home health aid, an important safety device for school buses, a handy home/office organizer, and a piano learning device.

Duracell and the National Science Teachers Association announced first through fifth place winners who are

recipients of \$160,000 in savings bonds in the 18th annual challenge — the nation's largest and oldest competition for middle school and high-school inventors.

Over 1,900 students submitted photos and plans for 1,436 prototype entries — in two categories, 6th through 9th grade and 10th through 12th grade.

In judging at Duracell headquarters, 100 finalist entries were awarded savings bonds ranging from \$20,000.00 to \$500.00. The seven first and second place winners, with their parents and sponsoring teachers, were honored in Orlando on April 5th during the annual convention of the National Science Teachers Association (NSTA).

First Place Winners

First place winners of \$20,000.00 savings bonds are a New Jersey High School senior, Stephen Cosenza, and a team of New York state sixth graders, Michael Marsal and Margaret Winter.

Cosenza invented the One-Hand Mobile Keyboard, an alternative communications system, which is a wearable keyboard. The invention is a new idea for data input or which Cosenza has developed both the hardware and software. A user can enter text while walking down the street and either immediately transmit it using radio waves or store it for processing later. Cosenza says, "practical uses for my invention are to equip soldiers in the military for secret communications, or for disabled persons who have limited mobility." The language is a new chording system which Cosenza calls Orderly Character Expansion, or OCE. Cosenza lives in Ocean, NJ and attends Ocean Township High School. His sponsor is Gilbert Lloyd, an electronics teacher.

Marsal and Winter, first place winners in the middle school category, invented the S3: Sports Signaling System designed to let hearing-impaired persons play hockey. The S3 attaches to a helmet and signals a green light when the coach wants a player's attention, such as for a line change, or a red light when the referee blows the whistle to stop play. The Hackley School students said, "We got the idea from ice hockey camp last summer where one of the campers was hearing-impaired." Marsal lives in Rye, NY and Winter lives in Purchase. Their sponsor is science and geology teacher, Ed Zapsen.

Second Place Winners

Four second place winners of \$10,000.00 savings bonds are Ana Lucia Ybarra Berry of The Woodlands, TX for the Asthmalyzer; Bari Spielfogel of Jericho, NY for Busguard; Gregory

Roger's Systems Specialist

24895 Avenue Rockefeller
Valencia California 91355

"We Have Great Connections"
Computer • Telecommunications
Network • Audio • Video

Call for
Quantity Price
breaks!!

(800)366-0579
(661)295-5577
fax(661)295-8777

www.rogerssystems.com

CAT. 5 CABLE



Grey		
TE-038-L5	3ft. Straight Patch	\$1.75
TE-068-L5	7 ft. Straight Patch	\$2.00
TE-128-L5	14ft. Straight Patch	\$4.00
TE-258-L5	25ft. Straight Patch	\$5.00
TE-358-L5	35ft. Straight Patch	\$7.00
TE-508-L5	50 ft. Straight Patch	\$8.00
TE-758-L5	75ft. Straight Patch	\$17.00
TE-108-L5	100 ft. Straight Patch	\$16.00

USB CABLES

CC-USB-6	6ft. USB "A"- "A" M/M	\$5.00
CC-USB-AB6	6ft. USB "A"- "B" M/M	\$5.00
CC-USB-AB10	10ft. USB "A"- "B" M/M	\$6.00
CC-USB-AB15	15ft. USB "A"- "B" M/M	\$8.00
CC-USB-X6	6ft. USB "A"- "A" M/F	\$6.00
CC-USB-X10	10ft. USB "A"- "A" M/F	\$6.00



cat.no. CC-USB-PP \$25.00

USB to Parallel Printer

USB to SCSI

USB-SCSI-25

USB to DB25 converter cable

USB-SCSI-HD50

USB to HD50 male converter cable



\$89.00

Preserve your investment in SCSI peripherals. Connect up to seven storage devices to your iMac, G3 (Blue&White), or USB equipped PC.

\$20.00 min. Order required
Add \$4.50 shipping for prepaid orders
Prices subject to change without notice
All major credit cards accepted
Special offers only valid on items in stock
Call for quantity discount
No out of state checks accepted

S-VGA Extensions

male/female



CC-VGA-4C	6FT	\$6.00
CC-VGA-5C	10FT	\$8.00
CC-VGA-25CX	25FT	\$16.00
CC-VGA-50CX	50FT	\$25.00
CC-VGA-100CX	100FT	\$44.00

S-VGA Switch Box Cable

male/male

CC-VGA-3C	6FT	\$6.00
CC-VGA-9C	10FT	\$8.00
CC-VGA-11C	25FT	\$16.00
CC-VGA50MM	50FT	\$25.00
CC-VGA100MM	100FT	\$44.00

These premium VGA cables are made with 75 ohm coaxial cables. They are triple shielded to support extremely high bandwidth and unsurpassed protection against interference. Furthermore, our premium cables are Plug-N-Play ready and are compatible with the latest technology.

ADD ON CARDS



Call for more information
on any of these cards!!

CA-PPGA-S1	PPGA Celeron CPU Slot 1 adaptor	\$10.00
IO-398	ISA 8bit Single Parallel IEEE Card	\$12.00
IO-400	PCI 32bit Single Parallel IEEE Card	\$33.00
SD-884	16bit ISA Sound Card ESS Chip	\$16.00
USB-PCI	USB x PCI Add on Card	\$22.00
VD-466	S-VGA SIS 4MB PCI Video Card	\$33.00
VD-488	Savage4 32MB AGP 12bit 3D Video Card	\$99.00

Multi-PC Controller

w/keyboard & mouse emulation

Easy to select by push button

HD15-S-VGA

PS/2 KEYBOARD

PS/2 MOUSE



cat.no.

DS-HD2-66EM	2-WAY	\$49.00
DS-HD4-66EM	4-WAY	\$69.00

USB HUB

4-port USB hub w/power & cable
Full compliance w/USB spec. Rev 1.0.
LED indicator for fault or dummy USB port.
Transmission for 5meter cable segment.
Plug & Play capability for outside peripherals.
Support UHCI and OHCI spec.
One year factory warranty!

\$39.00



cat.no. TM-USB-4HUB

Electronic CPU Switch

Includes: cat.no. DS-102-KMMP5

- One MiniView KVM switch
- 2 Sets of Premium Grade KVM Cables
- One PS/2 to AT keyboard adapter
- One PS/2 to Serial mouse adapter
- One User Guide

\$99.00

Features:

- Keyboard & mouse emulation for error free PC booting
- No external power required
- Works virtually with any operating system
- Fully hot pluggable



SLOT FAN

Extends your computer life.

BallBearing

Takes up only one of the PCI/ISA slots.

Special designed turbine fan gives you great performance and quietness.



\$12.00

Cat.no. TM-FAN-SLOT

CPU's-Motherboards-HardDrives
Memory-SCSI Adaptors-SCSI Cables
CD burners-CD's & Rewritable CD's
And Much Much More!!!!

Eden of Columbia, MD for SNAP — The Sight-Reading Notation Acceleration Program; and Advay Mengle of Carmel, IN for SmartRack — a CD Locator.

Berry's Asthmalyzer is a practical self-monitoring device for people with asthma. It measures and reports peak exhaled breath flow, the total volume of air exhaled, and the average air flow rate. "It's vital to monitor the breathing patterns of asthmatics," Berry says. "I've had asthma for seven years and I thought of making this device when I was monitoring a new medication and needed to know if it was working." Berry is a junior at the Academy of Science and Technology in Conroe, TX. Her sponsor is Scott Rippetoe, a physics and electronics teacher.

Spiefogel developed Busguard, an important safety device to monitor children as they enter and exit school buses which ensures that no child is left on a bus at the end of a route. "I got the idea because of hearing about the problems of children who fell asleep and were left on school buses after they were parked for the night," Spiefogel says. She is in 10th grade at Jericho High School, Jericho, NY and her sponsor is Allen Sachs who teaches independent research.

Eden created SNAP — Sight-Reading Notation Acceleration Program, an educational tool to help musicians increase their sight-reading skills. "It is useful for pianists with varying skills because it offers six learning speeds and from one to five notes per screen," says Eden. "My device is entertaining and makes sight-reading a SNAP!" Eden is in 7th grade at Burleigh Manor Middle School in Ellicott City, MD. His sponsor is science teacher, Kathleen McLaughlin.

Mengle invented SmartRack to help organize his computer CDs.

SmartRack is a time-saving locator system that quickly identifies with a light where an individual CD is in a large rack. "This prototype locates CD-ROMs or audio CDs, but could easily be extended to identify other jacketed items such as audiotapes, videocassettes, and DVDs," Mengle says. He attends Carmel Junior High School in Carmel, IN where he is in 7th grade. His sponsor is general science teacher, Beth Lehner.

Every Entry is a Winner

The Duracell/NSTA Invention Challenge is awarding 10 third place \$3,000.00 savings bonds, 24 fourth place \$1,000.00 bonds, and 60 fifth place \$500.00 bonds. All 1,953 students who entered the 2000 Challenge will receive a gift and a certificate of participation. Sponsoring teachers of the 100 finalists also receive gifts.

The Challenge

The Duracell/NSTA Invention Challenge rewards 6th through 12th grade students for designing and creating battery-powered devices which are educational, useful, and entertaining. Judging is based on creativity, practicality, and energy efficiency of each invention, and clarity of an explanatory essay.

Sponsored by Duracell and administered by the National Science Teachers Association, the Duracell/NSTA Invention Challenge has awarded over one million dollars in scholarships, savings bonds, and cash awards to more than 1,000 students since 1983. Student inventors retain all rights to their devices.

The National Science Teachers Association has 53,000 members and is the largest organization in the world

dedicated to promoting excellence in science teaching and learning.

The Internet Doesn't Do Security ... Building Linux and OpenBSD Firewalls

The Internet was originally designed to distribute research papers, getting information to as many people as possible, as quickly as possible. Preventing people from reading someone else's E-Mail, acquiring his or her credit card number, or altering a company's payroll information just wasn't the major consideration.

Clearly — say security experts Wes Sonenreich and Tom Yates — the design criteria of the past is inadequate for the modern Web. Security and IT professionals need to learn how to protect today's fastest growing, freely-distributed operating systems with simple, secure, and inexpensive firewalls.

Their new work, *Building Linux and OpenBSD Firewalls* (Wiley Computer Publishing; available now for \$44.99, paper; ISBN 0-471-35366-3) is the only book to focus exclusively on Linux and OpenBSD firewall security issues.

Highlighting the strengths of Linux and OpenBSD, the book shows: How to build both a Linux and OpenBSD solution; how to select the proper hardware; how to install and configure each system; how to deal with network services such as E-Mail: newsgroups, and Internet and Intranet access; and how to monitor and update the system. *Building Linux and OpenBSD Firewalls* also has a companion website that includes links to scripts, online resources, technical support, and installa-

JFETS

ULTRA LOW NOISE
LS843 - 3nV/Hz typ

TIGHT MATCHING
LS843 - 1 mV max

- ♦ N & P Channel
- ♦ Duals & Singles
- ♦ Custom Screening
- ♦ Die, SMT, Thru-Hole
- ♦ No. Order Minimum
- ♦ COD's Accepted

Second Source for Domestic & Foreign JFETs & Bipolars

Full Service U.S. Manufacturer of Specialty Linear Products

LINEAR SYSTEMS

4042 Copper Court
Fremont, CA 94538
510-490-9160/510-353-0261(Fax)
E-mail: 3623671@MCI.COM

Write in 107 on Reader Service Card.

tion information.

Wiley books are available at your local bookstore or by calling 1-800-225-5945. In Canada, call 1-800-567-4797.




(Left)
Winners
Grades
10-12

(Below)
Winners
Grades 6-9



The Pocket Programmer

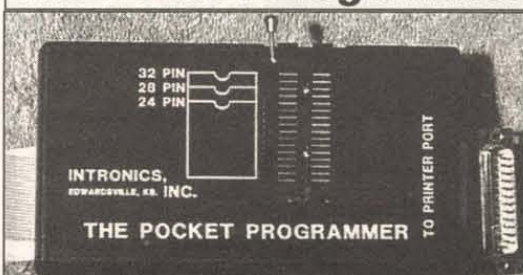

The portable programmer that uses the printer port of your PC instead of a internal card. Easy to use software that programs E(E)prom, Flash & Dallas Ram. 27(C)/28(C)/28F/29F/29CXXXX & 25XX series from 16K to 8 Megabit with a 32 pin socket. Adapters available for Pic, MCU's 874X, 875X, 40-Pin X 16 & Serial Eprom's, PLCC, 5-Gang, 82/74 Prom's and Eprom Emulator to 32K X 8.
Only \$129.95

Same Name, Address & Phone Number for 16 Years....
Now isn't that Amazing?

Intronics, Inc.

Box 13723 / 612 Newton St.
Edwardsville, KS 66113 Add \$5.00 COD
Tel. (913) 422-2094 Add \$4.00 Shipping
Fax (913) 441-1623 Visa / Master Charge / Amex

FET PRINCIPLES AND CIRCUITS

Part 1

Field-Effect Transistors

by Ray Marston

Ray Marston explains FET (Field-Effect Transistor) basics in this opening episode of this new four-part series.

Field-Effect Transistors (FETs) are unipolar devices, and have two big advantages over bipolar transistors: one is that they have a near-infinite input resistance and thus offer near-infinite current and power gain; the other is that their switching action is not marred

by charge-storage problems, and they thus outperform most bipolars in terms of digital switching speeds.

Several different basic types of FETs are available, and this opening episode looks at their basic operating principles. Parts 2 to 4 of the series will show practical ways

of using FETs.

FET BASICS

An FET is a three-terminal amplifying device. Its terminals are known as the source, gate, and drain, and correspond respectively to the emitter, base, and collector of a normal

transistor. Two distinct families of FETs are in general use. The first of these is known as 'junction-gate' types of FETs; this term generally being abbreviated to either JUFET or (more usually) JFET.

The second family is known as either 'insulated-gate' FETs or Metal Oxide Semiconductor FETs, and these terms are generally abbreviated to IG-FET or MOSFET, respectively. 'N-channel' and 'p-channel' versions of both types of FET are available, just as normal transistors are available in npn and pnp versions. Figure 1 shows the symbols and supply polarities of both types of bipolar transistor, and compares them with both JFET versions.

Figure 2 illustrates the basic construction and operating principles of a simple n-channel JFET. It consists of a bar of n-type semiconductor material with a drain terminal at one end and a source terminal at the other. A p-type control electrode or gate surrounds (and is joined to the surface of) the middle section of the n-type bar, thus forming a p-n junction.

In normal use, the drain terminal is connected to a positive supply and the gate is biased at a value that is negative (or equal) to the source voltage, thus reverse-biasing the JFET's internal p-n junction, and accounting for its very high input impedance.

With zero gate bias applied, a current flow from drain to source via a conductive 'channel' in the n-type bar is formed. When negative gate bias is applied, a high resistance region is formed within the junction, and reduces the width of the n-type conduction channel and thus reduces the magnitude of the drain-to-source current. As the gate bias is increased, the 'depletion' region spreads deeper into the n-type channel, until eventually, at some 'pinch-off' voltage value, the depletion layer becomes so deep that conduction ceases.

Thus, the basic JFET of Figure 2 passes maximum current when its gate bias is zero, and its current is reduced or 'depleted' when the gate bias is increased. It is thus known as a 'depletion-type' n-channel JFET. A p-channel version of the device can (in principle) be made by simply transposing the p and n materials.

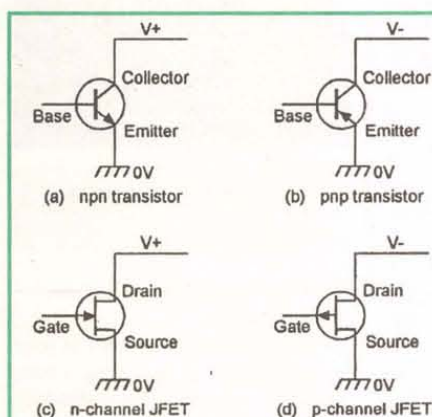


Figure 1. Comparison of transistor and JFET symbols, notations, and supply polarities.


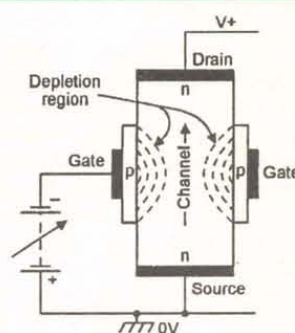


Figure 2. Basic structure of a simple n-channel JFET, showing how channel width is controlled via the gate bias.

EASILY ADD TEXT TO VIDEO WITH BOB-II

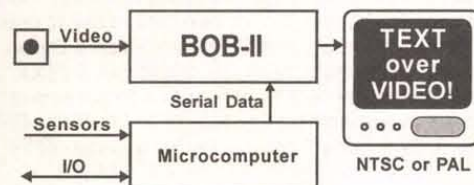- Auto-switching genlock overlay module
- Generates complete video signal on-board
- Up to 308 characters in 11 rows, 28 cols
- Fast 'RS-232' serial control (2400-19.2kbps)
- Small footprint; only 3.50" by 1.05"
- Developer board now available (BNAB)
- Compatible with Parallax[™] BASIC Stamp[™]



Only \$79.95 ea. (NTSC qty. 1-9)



DECADE ENGINEERING
Tel: 503.743.3194 ~ Fax: 503.743.2095
www.decadenet.com

PRINTED CIRCUIT BOARDS

Since 1969

Prototype to Production
Quick • Quality • Service • Price

- Single Sided
- Double Sided
- Multi-Layer
- Surface Mount
- Punch Press Capability
- LPI

QUICK TURN AROUND
COMPLETE IN-HOUSE CAPABILITY

CIRCUIT ETCHING TECHNICS

Since 1969
700 Lee Street Phone: 847-228-1722
Elk Grove Village Fax: 847-228-1816
Illinois 60007 Modem: 847-228-6549
Toll Free: 888-657-3827

E-MAIL — CET@MET-NET.COM
WEB ADDRESS —
WWW.MET-NET.COM/USERS/CET

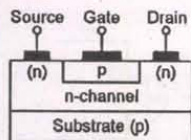


Figure 3.
Construction
of n-channel
JFET.

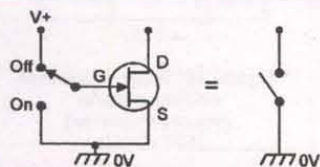


Figure 6. An n-channel
JFET can be used as a
voltage-controlled switch.

JFET DETAILS

Figure 3 shows the basic form of construction of a practical n-channel JFET; a p-channel JFET can be made by transposing the p and n materials. All JFETs operate in the depletion mode, as already described. Figure 4 shows the typical transfer characteristics of a low-power n-channel JFET, and illustrates some important features of this type of device. The most important characteristics of the JFET are as follows:

(1). When a JFET is connected to a supply with the polarity shown in Figure 1 (drain +ve for an n-channel FET, -ve for a p-channel FET), a drain current (I_D) flows and can be controlled via a gate-to-source bias voltage V_{GS} .

(2). I_D is greatest when $V_{GS} = 0$, and is reduced by applying a reverse bias to the gate (negative bias in an n-channel device, positive bias in a p-type). The magnitude of V_{GS} needed to reduce I_D to zero is called the 'pinch-off' voltage, V_P , and typically has a value between 2 and 10 volts. The magnitude of I_D when $V_{GS} = 0$ is denoted I_{DSS} , and typically has a value in the range 2 to 20mA.

(3). The JFET's gate-to-source junction has the characteristics of a silicon diode. When reverse-biased, gate leakage currents (I_{GSS}) are only a couple of nA ($1\text{nA} = .001\mu\text{A}$) at room temperature. Actual gate signal currents are only a fraction of an nA, and the input impedance of the gate is typically thousands of megohms at low frequencies. The gate junction is shunted by a few pF, so the input impedance falls as frequency rises.

If the JFET's gate-to-source junction is forward-biased, it conducts like a normal silicon diode. If it is excessively reverse-biased, it avalanches like a zener diode. In either case, the JFET suffers no damage if gate currents are limited to a few mA.

(4). Note in Figure 4 that, for each V_{GS} value, drain current I_D rises linearly from zero as the drain-to-source voltage (V_{DS}) is increased from zero up to some value at which

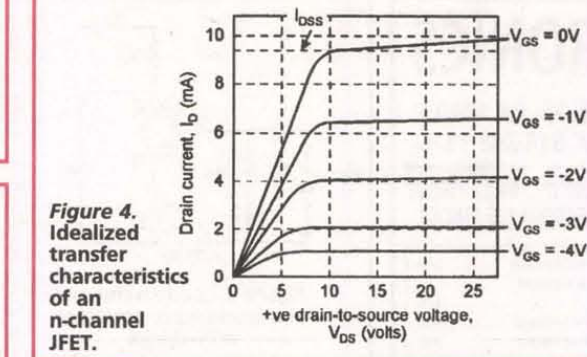


Figure 4.
Idealized
transfer
characteristics
of an
n-channel
JFET.

a 'knee' occurs on each curve, and that I_D then remains virtually constant as V_{DS} is increased beyond the knee value. Thus, when V_{DS} is below the JFET's knee value, the drain-to-source terminals act as a resistor, R_{DS} , with a value dictated by V_{GS} , and can thus be used as a voltage-variable resistor, as in Figure 5.

Typically, R_{DS} can be varied from a few hundred ohms (at $V_{GS} = 0$) to thousands of megohms (at $V_{GS} = V_P$), enabling the JFET to be used as a voltage-controlled switch (Figure 6) or as an efficient 'chopper' (Figure 7) that does not suffer from offset-voltage or saturation-voltage problems.

Also note in Figure 4 that when V_{DS} is above the knee value, the I_D value is controlled by the V_{GS} value and is almost independent of V_{DS} , i.e., the JFET acts as a voltage-controlled current generator. The JFET can be used as a fixed-value current generator by either tying the gate to the source as in Figure 8(a), or by applying a fixed negative bias to the gate as in Figure 8(b). Alternatively, it can (when suitably biased) be used as a voltage-to-current signal amplifier.

(5). FET 'gain' is specified as

transconductance, g_m , and denotes the magnitude of change of drain current with gate voltage, i.e., a g_m of 5mA/V signifies that a V_{GS} variation of one volt produces a 5mA change in I_D . Note that the form I/V is the inverse of the ohms formula, so g_m measurements are often expressed in 'mho' units. Usually, g_m is specified in FET data sheets in terms of mmhos (milli-mhos) or μmhos (micro-mhos). Thus, a g_m of $5\text{mA/V} = 5\text{-mmho}$ or $5000\text{-}\mu\text{mho}$.

In most practical applications, the JFET is biased into the linear region and used as a voltage amplifier. Looking at the n-channel JFET, it

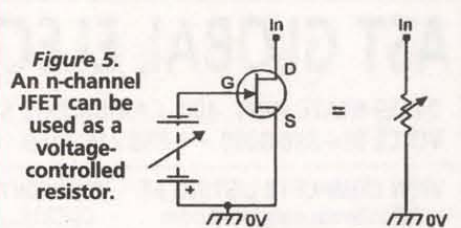


Figure 5.
An n-channel
JFET can be
used as a
voltage-
controlled
resistor.


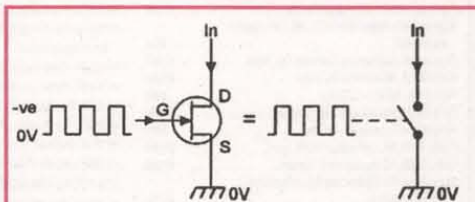


Figure 7. An n-channel JFET can be used as an electronic chopper.

can be used as a common source amplifier (corresponding to the bipolar npn common emitter amplifier) by using the basic connections in Figure 9.

Alternatively, the common drain or source follower (similar to the bipolar emitter follower) configuration can be obtained by using the connections in Figure 10, or the common gate (similar to common base) configuration can be obtained by using the basic Figure 11 circuit. In

Figure 8. An
n-channel JFET
can be used as a
constant-current
generator.

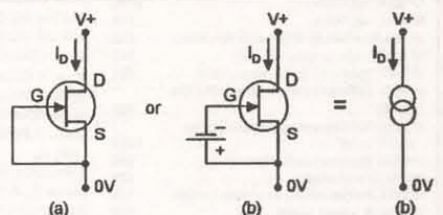

BIG POWER LOW COST



Dominoes are rugged, miniature encapsulated controllers that combine lots of analog and digital I/O with a fast control-oriented floating-point BASIC to provide a one-stop computation and control solution for cost-sensitive control tasks. Used stand alone or connected via RS-232/RS-485, Dominoes are true plug-and-go control.

Domino 1 features:

- Full floating-point ROMed BASIC
- 32-KB SRAM and 32-KB EEPROM
- 12 bits of parallel I/O
- 2 PWM outputs
- I²C bus
- 2-channel 12-bit ADC
- Serial port: 19.2-kbps RS-232A, RS-422, or RS-485
- +5V @ 15 mA

Domino 2 has:

- everything in Domino 1 plus
- 16 more bits of high-current parallel I/O
- Hardware dock/calendar
- Wide-range power operation
- Hardware PWM output

\$99 to \$139

Visit our Web site for complete datasheets

www.micromint.com

To Order Call: **1-800-635-3355**

Micromint, Inc.

740 Florida Central Pkwy, Longwood, FL 32750
(407) 262-0066

Write in 134 on Reader Service Card.

plug-ins
test sets
counters
generators
oscilloscopes
power supplies
spectrum analyzers
& much more!

www.levylatham.com
PRIVATE MARKETERS OF U.S. GOVERNMENT MILITARY SURPLUS ASSETS

Write in 130 on Reader Service Card.

AST GLOBAL ELECTRONICS

24529 STATE HWY. 408, CAMBRIDGE SPRINGS, PA 16403
VOICE 814-398-8080 • 1-888-216-7159 • FAX 814-398-1176

VIEW COMPLETE LISTING AT:
<http://www.astglobal.com>

IF WE DON'T CARRY IT ... WE'LL FIND IT
QUICKLY ... AT REASONABLE PRICES.

Advantest RS372P, Microwave Counter	\$1,700	HP 6289A, Power Supply, 0-40V @ 1.5A (metered)	\$175
Bionton 4200, Power Meter w/RE, 4E-S21, Sensor and Manual	\$750	HP 6294A, Power Supply, 0-60V @ 1A (metered)	\$225
Fuke 5100B, Multifunction Calibrator, Opt. 0305	\$2,800	New in box w/manual	\$275
Fuke 5100B, Multifunction Calibrator	\$2,400	HP 6299A, Power Supply, 0-100V @ 75A Metered	\$225
Fuke 515A, Portable Calibrator	\$750	HP 6428B, Power Supply, 0-20V @ 40-45A Metered	\$550
Fuke 5200A, Programmable AC Calibrator	\$1,000	HP 651B, Test Oscillator, 10Hz-10MHz	\$125
Fuke 5215A, Precision Power Amp	\$800	HP 652B, Test Oscillator, 10Hz-10MHz	\$125
Fuke 5440B, DC Calibrator, 0-1100V, 3ppm	\$2,900	HP 654A, Oscillator, 10Hz-10MHz, 90dB Attenuator	\$225
Fuke 5790A, AC Measurement Standard	\$9,500	HP 6626A, Bipolar Power Supply/Amp $\pm 50V \pm 1A$	\$475
Fuke 6060A/AN, Synthesized Signal Generator, 100KHz-105MHz	\$1,750	HP 8116A, Programmable Pulse/Function Generator, 50MHz	\$2,400
Fuke 6070A, Synthesized RF Signal Generator, 200KHz-620MHz	\$1,400	HP 8165A, Programmable Sig Source, 1mV-50MHz	\$950
Fuke 8050A, DMM 4-1/2 Digit w/Battery Pack	\$145	HP 8165A, Programmable Pulse Generator, 50MHz, Opt. 002	\$1,100
Fuke 8050A, DMM 4-1/2 Digit w/o Battery Pack	\$145	HP 8350A, Spectrum Analyzer Mainframe	\$900
Fuke 8840A, DMM 5-1/2 Digit w/GPIB	\$375	HP 8350B, Spectrum Analyzer Mainframe	\$1,100
Gigatronics 600, Frequency Synthesizer, 6-12GHz	\$950	HP 853A, Spectrum Analyzer Mainframe	\$750
Gigatronics 600, Frequency Synthesizer, 10-18GHz	\$950	HP 853A, Spectrum Analyzer, w/BS58B, 1-1500MHz	\$1,800
Gigatronics 6081A, Synthesized Signal Generator, 10KHz-105MHz	\$2,200	HP 853A, Spectrum Analyzer, w/BS59A, 0.1-21GHz	\$2,200
Gigatronics 6541, Power Meter	\$1,400	HP 8622A, RF Plug-In, 0.1-2.4GHz, NICE1	\$850
HP 105B, Quartz Oscillator	\$525	HP 8640B, Signal Generator, 5-1050MHz, Opt. 002/001 or 003	\$1,800
HP 141T, Spectrum Analyzer Mainframe	\$375	HP 8640B, Signal Generator, 5-512MHz, Opt. 001 or 003	\$700
HP 141T, Spectrum Analyzer w/BS52B/BS53B, 1KHz-110MHz	\$1,100	HP 8656A, Synthesized Signal Generator, 100KHz-990MHz	\$1,400
		HP 8657A, Synthesized Signal Generator, Opt. 002	

TURN IDLE TEST EQUIPMENT — INTO CASH — CALL OR FAX FOR QUOTATION

HP 141T, Spectrum Analyzer w/BS52B/BS53A, 20Hz-300KHz	\$1,000	HP 3336C, Synthesizer Level Generator	\$950
HP 141T, Spectrum Analyzer w/BS52B/BS54B, 10Hz-1.2GHz	\$1,600	HP 334A, Distortion Analyzer	\$275
HP 141T, Spectrum Analyzer w/BS52B/BS55A, 10MHz-18GHz	\$1,800	HP 3400A, True RMS Voltmeter, 10Hz-10MHz, 1mV-300V	\$125
HP 1630G, Logic Analyzer w/pods	\$575	HP 3406A, RF Voltmeter, 50V-3V, 1.2GHz	\$200
HP 1633A, Logic Analyzer	\$2,000	HP 3455A, DMM 5-1/2 Digit	\$250
HP 1651A, Logic Analyzer	\$875	HP 3456A, DMM 6-1/2 Digit	\$475
HP 214B, Pulse Generator, 200V Pulse/50 ohms, 10MHz	\$625	HP 3466A, DMM 4-1/2 Digit, AC/Battery, 5 Function	\$175
HP 3312A, Function Generator, 1Hz-13MHz	\$425	HP 3488A, Switch Control	\$325
HP 3325A, Synthesized Function Generator, 21MHz	\$650	HP 3575A, Digital Phase Gain Meter 1Hz-13MHz	\$500
HP 3325A, Synthesized Function Generator, HP1B, 21MHz, Opt. 002	\$825	HP 3580A, Spectrum Analyzer, 5Hz-50KHz, LED Readout	\$650
HP 3326A, DC-13MHz Synthesized Function Generator		HP 3730B, Down Converter Mainframe	\$625
40V P-P, Opt. 002	\$3,400	HP 400EL, AC Voltmeter, 10Hz-10MHz	\$150
HP 3336C, Synthesizer Level Generator	\$950	HP 400FL, RMS Voltmeter, 20Hz-4MHz, 100V-300V	\$175
HP 334A, Distortion Analyzer	\$275	HP 415E, SWR Meter	\$100
HP 3400A, True RMS Voltmeter, 10Hz-10MHz, 1mV-300V	\$125	HP 424A, Power Meter w/Cable/47dB, 0.1-18GHz Sensor	\$350
HP 3406A, RF Voltmeter, 50V-3V, 1.2GHz	\$200	HP 436A, Power Meter w/Opt. 022 HP1B	\$650
HP 3455A, DMM 5-1/2 Digit	\$250	HP 436A, Power Meter	\$450
HP 3456A, DMM 6-1/2 Digit	\$475	HP 4972A, LAN Protocol Analyzer	\$750
HP 3466A, DMM 4-1/2 Digit, AC/Battery, 5 Function	\$175	HP 4972A, LAN Protocol Analyzer w/software, Opt. 002/005	\$750
HP 3488A, Switch Control	\$325	HP 5315B, Counter, 10MHz, Opt. 001, w/manual, NICE1	\$275
HP 3575A, Digital Phase Gain Meter 1Hz-13MHz	\$500	HP 5315B, Counter, 1GHz, Opt. 001/003, w/manual	\$425
HP 3580A, Spectrum Analyzer, 5Hz-50KHz, LED Readout	\$650	HP 5316A, Counter, 100MHz, HP1B	\$350
HP 3730B, Down Converter Mainframe	\$625	HP 5328A, Counter, 100MHz w/DMM/Opt. 021	\$200
HP 400EL, AC Voltmeter, 10Hz-10MHz	\$150	HP 5328A, Counter, 500MHz	\$250
HP 400FL, RMS Voltmeter, 20Hz-4MHz, 100V-300V	\$175	HP 5334A, Counter, 100MHz, Opt. 010 Oven	\$500
HP 415E, SWR Meter	\$100	HP 5345A, Counter, 500MHz, HP1B	\$450
HP 424A, Power Meter w/Cable/47dB, 0.1-18GHz Sensor	\$350	HP 5803A, D/A Converter	\$125
HP 436A, Power Meter w/Opt. 022 HP1B	\$650	HP 6002A, Power Supply, 0-50V @ 10A Metered	\$450
HP 436A, Power Meter	\$450	HP 6034A, System Power Supply, 0-60V @ 10A-200W	\$525
HP 4972A, LAN Protocol Analyzer	\$750	HP 6101A, Power Supply, 0-20V @ 1A	\$125
HP 4972A, LAN Protocol Analyzer w/software, Opt. 002/005	\$750	HP 6104A, Power Supply, 0-20, 20-40V @ 2A, 1A	\$150
HP 5315B, Counter, 10MHz, Opt. 001, w/manual, NICE1	\$275	HP 6112A, Power Supply, 40V @ 5A (metered)	\$150
HP 5315B, Counter, 1GHz, Opt. 001/003, w/manual	\$425	HP 6177C, DC Current Source to 100V @ 500mA	\$275
HP 5316A, Counter, 100MHz, HP1B	\$350	HP 6202B, Power Supply, 40V @ 75A (metered)	\$150
HP 5328A, Counter, 100MHz w/DMM/Opt. 021	\$200	HP 6203B, Power Supply, 7.5V @ 3A (metered)	\$150
HP 5328A, Counter, 500MHz	\$250	HP 6205B, Power Supply (dual), 0-40V @ 3A, 0-20V @ 8A (metered)	\$175
HP 5334A, Counter, 100MHz, Opt. 010 Oven	\$500	HP 6206B, Power Supply, 0-60V @ 1A (metered)	\$200
HP 5345A, Counter, 500MHz, HP1B	\$450	HP 6227B, Dual Tracking PS 0-25V @ 2A	\$375
HP 5803A, D/A Converter	\$125	HP 6264B, Power Supply, 0-20V @ 20A	\$225
HP 6002A, Power Supply, 0-50V @ 10A Metered	\$450	HP 6265B, Power Supply, 40V @ 3A (metered)	\$200
HP 6034A, System Power Supply, 0-60V @ 10A-200W	\$525	HP 6266A, Power Supply, 40V @ 6A (metered)	\$200
HP 6101A, Power Supply, 0-20V @ 1A	\$125	HP 6266B, Power Supply, 0-40V @ 5A	\$275
HP 6104A, Power Supply, 0-20, 20-40V @ 2A, 1A	\$150	HP 6269, Power Supply, 0-40V @ 50A Metered	\$750
HP 6112A, Power Supply, 40V @ 5A (metered)	\$150		
HP 6177C, DC Current Source to 100V @ 500mA	\$275		
HP 6202B, Power Supply, 40V @ 75A (metered)	\$150		
HP 6203B, Power Supply, 7.5V @ 3A (metered)	\$150		
HP 6205B, Power Supply (dual), 0-40V @ 3A, 0-20V @ 8A (metered)	\$175		
HP 6206B, Power Supply, 0-60V @ 1A (metered)	\$200		
HP 6227B, Dual Tracking PS 0-25V @ 2A	\$375		
HP 6264B, Power Supply, 0-20V @ 20A	\$225		
HP 6265B, Power Supply, 40V @ 3A (metered)	\$200		
HP 6266A, Power Supply, 40V @ 6A (metered)	\$200		
HP 6266B, Power Supply, 0-40V @ 5A	\$275		
HP 6269, Power Supply, 0-40V @ 50A Metered	\$750		

• 60-DAY WARRANTY
• 10-DAY RIGHT OF RETURN
• SATISFACTION GUARANTEED

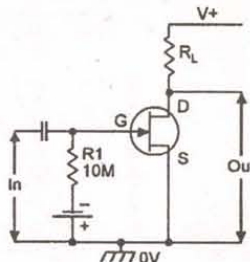


Figure 9. Basic n-channel common-source amplifier JFET circuit.

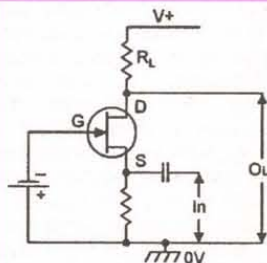


Figure 11. Basic n-channel common-gate JFET circuit.

practice, fairly accurate biasing techniques (discussed in Part 2 of this series) must be used in these circuits.

THE IGFET/MOSFET

The second (and most important) family of FETs are those known under the general title of IGFET or MOSFET. In these FETs, the gate terminal is insulated from the semiconductor body by a very thin layer of silicon dioxide, hence the title 'Insulated Gate Field Effect Transistor,' or IGFET. Also, the devices generally use a 'Metal-Oxide Silicon' semiconductor material in their construction, hence the alternative title of MOSFET.

Figure 12 shows the basic construction and the standard symbol of the n-channel depletion-mode FET. It resembles the JFET, except that its gate is fully insulated from the body of the FET (as indicated by the Figure 12(b) symbol) but, in fact, operates on a slightly different principle to the JFET.

It has a normally-open n-type channel between drain and source, but the channel width is controlled by the electrostatic field of the gate bias. The channel can be closed by applying

suitable negative bias, or can be increased by applying positive bias.

In practice, the FET substrate may be externally available, making a four-terminal device, or may be internally connected to the source, making a three-terminal device.

An important point about the IGFET/MOSFET is that it is also available as an enhancement-mode device, in which its conduction channel is normally closed but can be opened by applying forward bias to its gate.

Figure 13 shows the basic construction and the symbol of the n-channel version of such a device. Here, no n-channel drain-to-source conduction path exists through the p-type substrate, so with zero gate bias there is no conduction between drain and source; this feature is indicated in the symbol of Figure 13(b) by the gaps between source and drain.

To turn the device on, significant positive gate bias is needed, and when this is of sufficient magnitude, it starts to convert the p-type substrate material under the gate into an n-channel, enabling conduction to take place.

Figure 14 shows the typical transfer characteristics of an n-channel enhancement-mode IGFET/MOSFET,

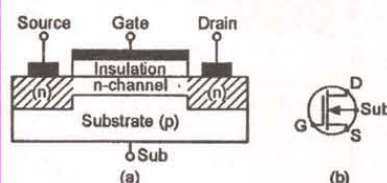


Figure 12. Construction (a) and symbol (b) of n-channel depletion-mode IGFET/MOSFET.

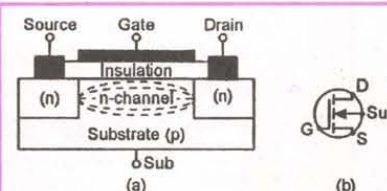


Figure 13. Construction (a) and symbol (b) of n-channel enhancement-mode IGFET/MOSFET.

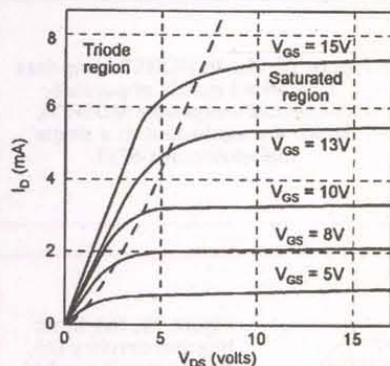


Figure 14.
Typical transfer
characteristics of
n-channel
enhancement-mode
IGFET/MOSFET.

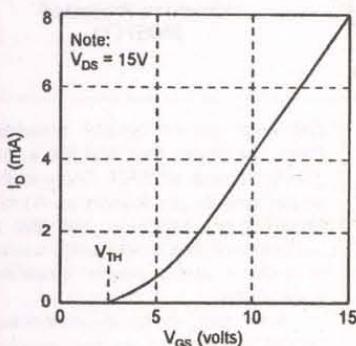


Figure 15.
Typical V_{GS}/I_D
characteristics of
n-channel
enhancement-mode
IGFET/MOSFET

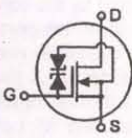


Figure 16.
Internally-
protected
n-channel
depletion-mode
IGFET/MOSFET.

and Figure 15 shows the V_{GS}/I_D curves of the same device when powered from a 15V supply. Note that no I_D current flows until the gate voltage reaches a 'threshold' (V_{TH}) value of a few volts, but that beyond this value, the drain current rises in a non-linear fashion.

Also note that the transfer graph is divided into two characteristic regions, as indicated (in Figure 14) by the dotted line, these being the 'triode' region and the 'saturated' region. In the triode region, the device acts like a voltage-controlled resistor; in the saturated region, it acts like a voltage-controlled constant-current generator.

The basic n-channel MOSFETs of Figures 12 and 13 can — in principle — be converted to p-channel devices by simply transposing their p and n materials, in which case their symbols must be changed by reversing the directions of their substrate arrows.

A number of sub-variants of the MOSFET are in common use. The type known as 'DMOS' uses a double-diffused manufacturing technique to provide it with a very short conduction channel and a consequent ability to operate at very high switching speeds. Several other MOSFET variants are described in the remainder of this opening episode.

Note that the very high gate

impedance of MOSFET devices makes them liable to damage from electrostatic discharges and, for this reason, they are often provided with internal protection via integral diodes or zeners, as shown in the example in Figure 16.

VFET DEVICES

In a normal small-signal JFET or MOSFET, the main signal current flows 'laterally' (see Figures 3, 12, and 13) through the device's conductive channel. This channel is very thin, and maximum operating currents are consequently very limited (typically to maximum values in the range 2 to 40mA).

In post-1970 times, many manufacturers have tried to produce viable high-power/high-current versions of the FET, and the most successful of these have relied on the use of a 'vertical' (rather than lateral) flow of current through the conductive channel of the device. One of the best known of these devices is the 'VFET,' an enhancement-mode power MOSFET which was first introduced by Siliconix way back in 1976.


Figure 17 shows the basic structure of the original Siliconix VFET. It has an essentially four-layer structure, with an n-type source layer at the top, followed by a p-type 'body' layer, an epitaxial n-type layer, and (at the bottom) an n-type drain layer. Note that a 'V' groove (hence the 'VFET' title) passes through the first two layers and into the third layer of the device, and is electrostatically connected (via an insulating silicon dioxide film) to the gate terminal.

If the gate is shorted to the source, and the drain is made posi-

FREE to all Electronics Addicts

\$199 To All Others!

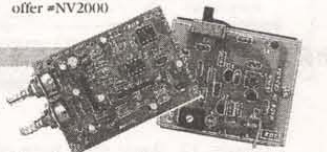when you mention this special offer #NV2000



For the first time ever we've decided to offer a proprietary software package titled, "Basic Electronics Concepts" to the general public. (Until now, the software hasn't been available to the public, at any price!).

Over 1500 Electronics teachers nationwide use this exact software package to teach Junior High through Graduate Students the basics of electronics, teaching them step by step. The total course of instruction is over 10 full hours and teaches all about resistors, potentiometers, photocells, capacitors, speakers, silicon diodes, SCRs, NPN transistors, PNP transistors, transistor oscillators, and IC timers!

We sell this package day in and day out for \$199 to teachers, parents, and hobbyists that want a detailed, complete method of teaching electronics to themselves, friends or children.

Here's our offer: As part of our "Grand Opening", for a limited time every first time order on the web will receive a copy of this incredible software absolutely free!

We have a limited quantity of the software program in stock, at last check, approximately 1136 units, so place your order today!

Here's a few of the 117 different kits that you can build that we offer ONLINE:

Color Organs • FM Transmitter Kits
Amplifier Kits • Strobe Light Kits
Alarm Kits • Radios Kits • Meter Kits
Keypad Lock Kits • Infrared Kits
and more!

We carry national brands and guarantee that your order will arrive promptly and be exactly what you expected! **ORDER NOW!**

Build a kit today!

24 Hour Ordering on the web:
www.HobbyTron.com

PHONE: 877-606-8766

FAX: 800-470-1606

TRON

HOBBY TRON.com

Write In 128 on Reader Service Card.


RF Data Modules



AM TRANSMITTER

- Small size: 17.78 x 11.43mm
- CMOS/TTL input
- No adjustable components
- Low Current: 4mA typical
- 418MHz or 433.92MHz OOK
- Simple to integrate—simply add antenna, data and power
- Range up to 250ft.
- Wide supply range, 2-14Vdc
- SAW controlled—stability
- Also available in DIL package

AM-RT5 \$12.10

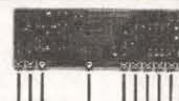

AM RECEIVER

- Compact size: 38.1 x 13.7mm
- On-board data recovery, CMOS
- Low current: 2.4mA typical
- 2kHz data rate, CMOS/TTL output
- 5Vdc operation
- On 418MHz or 433.92MHz (4xx)
- No adjustable components
- Patented Laser Trimmed component
- High stability
- Sensitivity: -105dBm
- Available also in 8mA version

AM-HRR3-4xx \$10.95



FM TRANSCIVER

- Only 23 x 33 x 11mm
- Up to 40k bps data rate
- 19200 baud with ASCII
- Up to 500ft. range
- 5v operation
- 0.25mW into 50
- 418 or 433MHz FM
- Fast 1ms enable
- Direct interface to 5V CMOS
- Auto TX/RX changeover

BIM-4xx-F \$87.36

RS232 TRANSCEIVER MODULES



- 4,800 to 38,400 bps half duplex
- 3-wire RS232 interface
- μ Controller with user EEPROM
- RS232 interface protected to ± 15 kV
- Data packetizing performed by user
- Auto TX/RX changeover
- 418 MHz and 433MHz versions
- Range up to 500ft. (0.25mW ver.)
- 0.25mW & 10mW versions
- Reset switch and status LED's
- 7.5-15V dc via DB9 connector, 20mA

BIM-4xx-RS232 \$139.30



Transceiver..... RTcom-4xx..... \$247.90
Transmitter..... RTcom-Tx-4xx..... \$ 87.15
Receiver..... RTcom-Rx-4xx..... \$105.52



ABACOM
TECHNOLOGIES



Tel: (416)236-3858
Fax: (416)236-8866
www.abacom-tech.com
abacomtech@compuserve.com

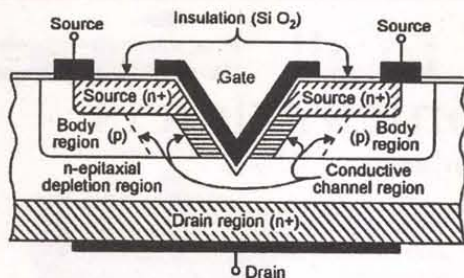


Figure 17. Basic structure of the VFET power device.

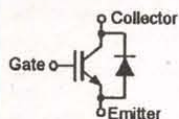


Figure 20. Normal circuit symbol of the IGBT (Insulated Gate Bipolar Transistor).

tive, no drain-to-source current flows, because the diode formed by the p and n materials is reverse-biased. But if the gate is made positive to the source, the resulting electrostatic field converts the area of p-type material adjacent to the gate into n-type material, thus creating a conduction channel in the position shown in Figure 17 and enabling current to flow vertically from the drain to the source.

As the gate becomes more positive, the channel width increases, enabling the drain-to-source current to increase as the drain-to-source resistance decreases. This basic VFET can thus pass reasonably high currents (typically up to 2A) without creating excessive current density within the channel regions.

The original Siliconix VFET design of Figure 17 was successful, but imperfect. The sharp bottom of its V-groove caused an excessive electric field at this point and restricted the device's operating voltage. Subsequent to the original VFET introduction, Intersil introduced their own

version of the 'VMOS' technique, with a U-shaped groove (plus other modifications) that improved device reliability and gave higher maximum operating currents and voltages. In 1980, Siliconix added these and other modifications to their own VFET devices, resulting in further improvements in performance.

OTHER POWER FETs

Several manufacturers have produced viable power FETs without using 'V'- or 'U'-groove techniques, but still relying on the vertical flow of current between drain and source. In the 1980s, Hitachi produced both p-channel and n-channel power MOSFET devices with ratings up to 8A and 200V; these devices were intended for use mainly in audio and low-RF applications.

Supertex of California and Farnant of England pioneered the development of a range of power MOSFETs with the general title of 'vertical DMOS.' These featured high operating voltages (up to 650V), high

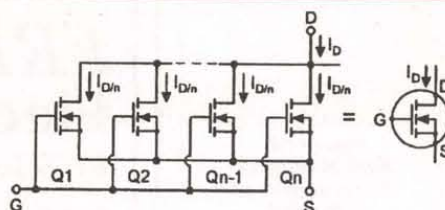


Figure 18. The IR HEXFET comprises a balanced matrix of parallel-connected low-power MOSFETs, which are equivalent to a single high-power MOSFET.

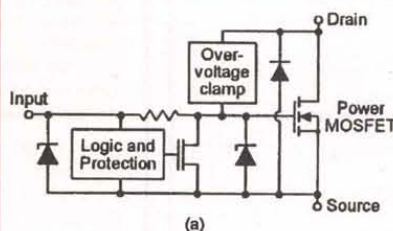


Figure 19. The basic internal circuitry (a) and the circuit symbol (b) of the TOPFET (Temperature and Overload Protected MOSFET).

current rating (up to 16A), low on resistance (down to 50 milliohms), and very fast operating speeds (up to 2GHz at 1A, 500MHz at 10A).

Siemens of West Germany used a modified version of DMOS, known as SIPMOS, to produce a range of n-channel devices with voltage ratings as high as 1kV and with current ratings as high as 30A.


One International Rectifier solution to the power MOSFET problem is a device which, in effect, houses a vast array of parallel-connected low-power vertical MOSFETs or 'cells' which share the total current equally between them, and thus act like a single high-power MOSFET, as indicated in Figure 18. These devices are named HEXFET, after the hexagonal structure of these cells, which have a density of about 100,000 per square centimeter of semiconductor material.

Several manufacturers produce power MOSFETs that each comprise a large array of parallel-connected low-power lateral (rather than horizontal) MOSFET cells that share the total

operating current equally between them; the device thus acts like a single high-power MOSFET. These high-power devices are known as lateral MOSFETs or L-MOSFETs, and give a performance that is particularly useful in super-fi audio power amplifier applications.

Note that, in parallel-connected MOSFETs (as used in the internal structure of the HEXFET and L-MOSFET devices described above), equal current sharing is ensured by the conduction channel's positive temperature coefficient; if the current in one MOSFET becomes excessive, the resultant heating of its channel raises its resistance, thus reducing its current flow and tending to equalize it with that of other parallel-connected MOSFETs. This feature makes such power MOSFETs almost immune to thermal runaway problems.

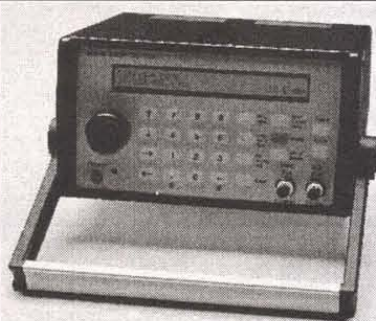Today, a vast range of power MOSFET types are manufactured. 'Low voltage' n-channel types are readily available with voltage/current ratings as high as 100V/75A, and 'high voltage' ones with ratings as



Telulex Inc. model SG-100A

New Features:
✓ 21.5 MHz
✓ .01 Hz steps
✓ multi-unit phaselock

Any waveform you want!

● Synthesized Signal Generator

Clean sinewaves DC-21.5 MHz with .001% accuracy!
.01 Hz steps. DC Offset. RS232 remote control.

● Arbitrary Waveform Generator


40 Megasamples/Second. 32,768 points. 12 bit DAC

● Function Generator


Ramps, Triangles, Exponentials, Noise & more.
0 to 2 MHz in 1 Hz steps. Continuous or Triggered.

● Pulse Generator

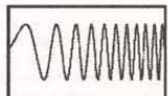
Digital waveforms with adjustable duty cycle




DC to 21.5 MHz linear and log sweeps

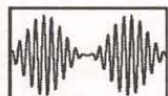


Int/Ext AM, SSB, Dualtone Gen.

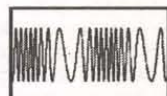


Int/Ext FM, PM, BPSK, Burst

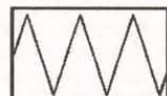


Ramps, Triangles,

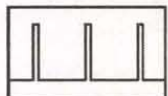


Pulse Generator

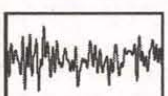

Noise

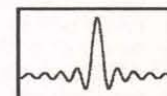

Arbitrary Waveforms

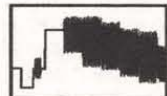

Unlimited Possibilities!

Telulex Inc.

2455 Old Middlefield Way S
Mountain View, CA 94043

Tel (650) 938-0240
Fax (650) 938-0241

<http://www.Telulex.com>
Email: sales@Telulex.com

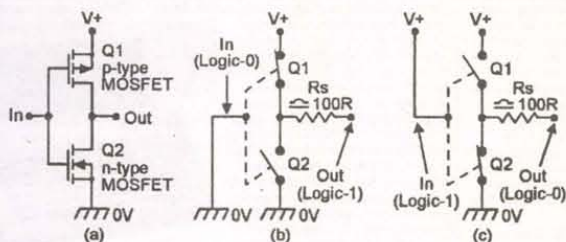


Figure 21. Basic CMOS circuit (a), and its equivalent with (b) a logic-0 input and (c) a logic-1 input.

high as 500V/25A.

One of the most important recent developments in the power-MOSFET field has been the introduction of a variety of so-called 'intelligent' or 'smart' MOSFETs with built-in overload protection circuitry; these MOSFETs usually carry a distinctive registered trade name. Philips devices of this type are known as TOPFETs (Temperature and Overload Protected MOSFETs); Figure 19 shows (in simplified form) the basic internal circuitry and the circuit symbol of the TOPFET.

The Siemens version of the smart MOSFET is known as the PROFET. PROFET devices incorporate protection against damage from short circuits, over temperature, overload, and electrostatic discharge (ESD). International Rectifier produce a range of smart n-channel MOSFET known as SMARTFETs; these incorporate protection against damage from short circuits, over temperature, overvoltage, and ESD.

Finally, yet another recent and important development in the n-channel power MOSFET field, has been the production — by various manufacturers — of a range of high power devices known as IGBTs (Insulated Gate Bipolar Transistors), which have a MOSFET-type input and an internally protected high-voltage high-current bipolar transistor output. Figure 20 shows the normal circuit symbol of the IGBT. Devices of this type usually have voltage/current/power ratings ranging from as low as 600V/6A/33W (in the device known as the HGTD3N603), to as

high as 1200V/520A/3000W (in the device known as the MG400Q1U551).

CMOS BASICS

One major FET application is in digital ICs. The best known range of such devices use the technology known as CMOS, and rely on the use of complementary pairs of MOSFETs. Figure 21 illustrates basic CMOS principles. The basic CMOS device comprises a p-type and n-type pair of enhancement-mode MOSFETs, wired in series, with their gates shorted together at the input, as shown in Figure 21(a). The pair are meant to use logic-0 or logic-1 digital input signals, and Figures 21(b) and 21(c), respectively, show the device's equivalent circuit under these conditions.

When the input is at logic-0, the upper (p-type) MOSFET is biased fully on and acts like a closed switch, and the lower (n-type) MOSFET is biased off and acts like an open switch; the output is thus effectively connected to the positive supply line (logic-1) via a series resistance of about 100R.


When the input is at logic-1, the MOSFET states are reversed, with Q1 acting like an open switch and Q2 acting like a closed switch, so the output is effectively connected to ground (logic-0) via 100R. Note in both cases that the entire signal current is fed to the load, and none is shunted off by the CMOS circuitry; this is a major feature of CMOS technology. NV

Digital Storage Oscilloscopes

From \$99.00

ATC modules turn your PC into a full-function DSC, spectrum analyzer, logger, & DVM. Units DC to 50MHz. O-Scope II now in Windows 3.1, 95/98, NT and DOS.

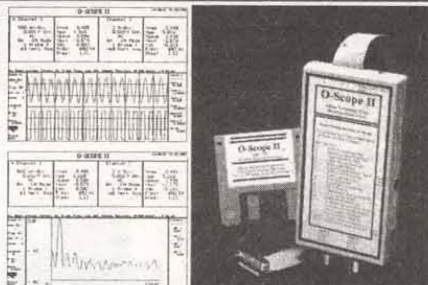O-Scope Ip \$189.
O-Scope II \$349.
Specialty probes call.



ATC is a stocking distributor for Pico Technology LTD which offers scope modules to 100MSPS, resolutions from 8 to 16 bit. Pico offers PC based data loggers from 1 to 22 channels, 8 to 16 bit and the Enviromon environmental monitoring system.

Pico products - call

The DFA-5, low cost differential amplifier, cuts through common mode noise problems to reveal low voltage signals. With gains from 1X to 1000X and band widths from 20KHz to 1.2MHz, DFA-5 is the test accessory to help you work with signals from 5 Volts to 5 microVolts. Only \$129.00.

Serial Port Problems ???
Check out Serial !! Our lowest cost serial channel analyzer only \$99.00.

Allison Technology Corporation
2006 Finney Villet Rd., TX. 77471 U.S.A.
800-980-9806 or 281-239-8500
<http://www.atcweb.com> atc@accesscomm.net

ALLTECH ELECTRONICS

WWW.COMPUTERCHOPPER.COM

WE CHOP
PRICE\$!

SCSI CD ROM Matsushita / Apple OEM PC or Mac SCSI 4x \$19	486 Mini System 486SX25 • Great for Linux DX266 Upgradable • 2 ISA Slots • VGA, LPT, 2COMs • FD \$29	250VA Isolation Transformer 115V Pri - 115V 250VA Sec Magnetek Triad 6" x 4" x 5" \$35
PC Game Accessories Steering Wheels • Flight Sticks • Joysticks Have a ball! Starting at: \$19	7 SCSI CD's in a Tower 7 CR-504-L Drives in a SCSI Tower case - 2 50 Pin Connectors \$179	Open Frame Industrial DC P/S +5/12-5/12 +24V \$29
24 Bit Flat Bed Scanner Win95/98 - ImageWave by Storm Technology. Parallel Port Interface Software Included! 5 Minute Installation \$39	Flat Bed Photo Scanner Win98/98 - Scan Photos, Slides, Negatives. Small foot- print. Great scanner! ISA Slot Req. \$45	8 Port Hub Refurbished Network Hardware - For PC and Mac. Why pay more? Get Networked Now! \$24

9.75" Mono, 8.6" and 10.4" Color LCDs



\$89 & up.

Great for Servers:
ISA Controller Included!!
All screens are 640x480. The
controller supports 256 Colors.
9.75" Mono Passive.....\$89.00
9.5" Color Passive.....\$199.00
10.4" Color Active.....\$319.00
P200 Motherboard with integrated
24 bit color available.
See our web site
for more details.

Cheaper Ethernet Stuff
Industrial Surplus
PC Parts • Mac Parts
For more information
on these products and
hundreds of other
products check out:

WWW.
ComputerChopper
.Com

760/724-2404
Fax 760/724-8808
Computer Circulation Center, Inc.
2618 Temple Heights Drive
Oceanside, CA 92056

Mon-Fri 9AM-5:30PM - Or see us on the internet.
VISA • Mastercard • Discover • American Express
Prices & Availability subject to change without notice • Government
& Educational PO's Accepted. • Not Responsible for Typographical Errors

M.E.M. ELECTRONICS CO.

DISTRIBUTOR FOR THE NEW

SIMS SVR-S825 8 HOUR DIGITAL VOICE RECORDER

- 8 HOUR RECORDING/PLAYBACK or 396 MESSAGES ON FLASH EPROM
- MINIATURE SIZE AND LIGHTWEIGHT, VOX, BACKLIT LCD DISPLAY
- GREAT- 4- JOURNALISTS, DOCTORS, LAWYERS, ENGINEERS, STUDENTS
- DOWNLOADING WIN '95 & '98 SOFTWARE ON CD INCLUDED ALSO EXT. MIC., EARPHONE, "AAA" BATTERIES, DUBBING CORD INCLUDED



GREAT FOR SSTV IMAGE STORAGE
THE SVR-S825 WILL HOLD OVER 800, COLOR
IMAGES AND THEN DOWNLOAD TO ANY SSTV,
PC SOFTWARE!

NEW - LOW COST. 2.5", 4" AND 6.8" COLOR TFT-LCD VIDEO
MODULES WITH NTSC DRIVER CARDS *** CALL 4 INFO!
FOR PRICING AND LITERATURE ON THESE AND OTHER GREAT PRODUCTS
CALL: 215 - 657 - 3119 E-MAIL: mocenter@erols.com
<http://www.memelectronics.com>

WOW! COMPUMOTOR, 4000 MOTION CONTROLLER PLUS, TWO, SERIES LE, STEPPER MOTOR DRIVERS.


Motion, 1 to 4 axes of step & direction control. Accepts encoder position feedback.
I/O, Optically isolated programmable inputs (24) and outputs (24) compatible with industry standard signal conditioning products.

Features, 4000 Programmer/Operator Panel. Detachable can be mounted remotely. Dedicated jog function for each axis. Four-line, backlit, Liquid Crystal Display (LCD). Six soft-function keys labeled by the LCD change definition as needed. Sealed membrane keypad.
Language, Simple BASIC-like motion control program language. (No software supplied.) Multiple programs may be entered and saved. Feedrate override allows operator interaction. Insert, edit, copy & delete functions. User-defined operator prompts. Linear interpolation on up to four axes. Teach mode uses analog joystick (not supplied) inputs or operator panel jog keys.

Interface Capability, Remote programming capability over RS-232C and IEEE-488, remote program downloading and uploading. Second RS-232C port for operator messages or control of other devices. **Special System.....COMP4000/LE.....\$1495 Ltd. Qty.**


DOVER AIR BEARING X/Y TABLE, is ULTRA PRECISE.

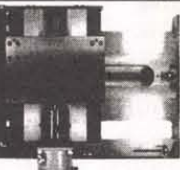Like New, The ultimate in precision motion control. Leadscrew operated air bearing tables with 1-20 Microns typical repeatability. Straightness, <1 micron each axis, angular error, <1 arc/sec. Squareness, <5 arc/sec. Unit has 4"x5" travel with two Compumotor LE57-S1-MTR steppers attached. Ready to play with our Compumotor 4000 series system above. **DOVER-B45.....\$949**



DAEDAL / COMPUMOTOR, MODEL 3002-P, X-Y INDEXER.

The 3000 is a programmable indexer capable of controlling up to four axes at one time. (Supplied with 2 axes installed). It can be programmed via the front panel or via a remote computer or terminal. RS-232 and IEEE488 ports are supplied as well as PIO. Specifications include: Step accy., $\pm 0.02\%$ of max. rate, Veloc. repeatability, $\pm 0.02\%$ of set rate. Veloc. range, 0.017 steps/sec to 1,092,000 steps/sec. System includes two MD2302-2020 stepper motor drivers as well. Very compact and rock mountable. Size: 8.5"H x 16"W x 6.5"D. 120VAC powered. Used, excellent condition. With operation manual. **Limited Qty.....COMP3002-P.....\$895**

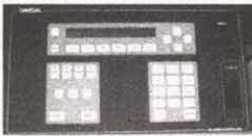

TREK- 678 or 676, HIGH VOLTAGE POWER SUPPLY / AMPLIFIERS

TREK-678, 0 to -30KVDC, high voltage, high speed "amplifier" provides high voltage output which follows a 0-10VDC control voltage with fast response and settling time. Rack size. Like new.
TREK-676, 0-20KVDC, high voltage, high speed "amplifier" provides high voltage output which follows a 0-10VDC control voltage with fast response and settling time. Rack size. Like new.

TREK-678, -30KV.....\$795ea. TREK- 676, -20KV.....\$695ea.

SUPER VACUUM PUMP, LEYBOLD, TRIVAC B, type D16, #91266-2

Dual stage, oil sealed, rotary vane pump with a 11.7cfm pumping capacity and an ultimate vacuum of 8×10^{-5} mbar.

This brand new pump is powered by a three phase, 1HP, AC motor with built in thermal protection. The motor can operate on 200 / 230 or 460 VAC. Completely modular construction for easy maintenance. Pump weighs 78lbs. **LEYBOLD D16.....\$1395**

GENERAL SCANNING, TYPE M3, CLOSED LOOP, GALVANOMETER, LASER SCANNER.

Innovative motor design coupled with an advanced capacitive position detector, provides high speed, wide angle and improved stability. Using moving magnet technology this scanner provides low inertia, rigidity and low inductance. Specs. include, $\pm 1.30^\circ$ excursion, wobble: 1.5urad, Repeatability: 2urad, Coil Res.: 4.8 Ohms, Peak current: 10Amps, Angular sensor sens.: 8.1uA/o. A high quality galvo for demanding laser displays. Galvos only, you provide the drivers. Very limited quantity.
M3 GALVO.....\$299ea. or \$549 for a pair.

\$5000 HI-TECH SURVEILLANCE SYSTEM, 90% OFF!

THIS SUPER SYSTEM INCLUDES:
• MOTORIZED, 6X ZOOM LENS
• MOTORIZED, 360° PAN
• MOTORIZED, TILT up to 90°
• PHILIPS HIGH RES. 1/2" CCD CAM.
• OPAQUE BLACK INNER DOME
• CLEAR ACRYLIC OUTER DOME
• ZOOM LENS CONTROLLER with A/I
• PAN and TILT CONTROLLER

Walk into any major department store and you will see these fully integrated systems. Manufactured by Sensormatic, the same company who supplied the Atlanta Olympics! These are late model, new in the box systems. Virtually ready to use. All you add is power and cable. A quality Philips, 1/2", B&W CCD camera provides 450 lines resolution and 0.5 Lux sensitivity. Anodized aluminum construction. Camera plus Pan & Tilt are powered by external 24VAC via the included Pan & Tilt controller. Super 6X, f/2 motorized, Zoom, Focus and Iris lenses provides the capability of "close up" inspections. Zoom lens controller with auto iris control included. Size of dome: 14" diam. Includes mounting kit for drop ceiling installation. Sensormatic price \$5000ea.

MAY SPECIAL, SENSORMATIC.....\$529ea.

GEAR MOTOR, METAL CONSTRUCTION, HIGH TORQUE,

BUEHLER PRODUCTS, type 127K01880

These are brand new, very rugged gearmotors. They offer a 5mm diameter x 9mm long, flatted output shaft, located off-center (approximately 10mm from the edge of the 35mm diameter gearbox). Overall size: 35mm d x 73 mm L (including the shaft) with 2" red and black leads. The motors are rated at 17VDC nominal and provide the following speeds:

@Vn	1 NOLOAD RPM
12V	60mA 360
15V	62mA 457
17V	64mA 523

MAY SPECIAL, BUEHLER 127K.....\$10ea. or 4 for \$35

NEW, LINEAR SLIDE, GOES to EXTREME LENGTHS, Very high quality, Techno-Isel, series one, German made.

This is the slide you have been looking for! Did we say it was LONG? How does 4 feet sound? Actually 49 and 1/4" to be precise and we know you are. Very sturdy, based on a heavy duty 1.5" wide, extruded aluminum and 1/2" diam. steel, dual rail. The slide carriage incorporates superior quality, recirculating ball bearings. Size of carriage is 3" x 3" with a solid 1/2" thick aluminum mounting plate. Limited quantity. The dual rails are new or have been carefully removed from precision optical equipment. The slider carriages are all brand new & unused. Each rail includes one slide carriage. Extras are available.

LONG-ISEL - 48".....\$149ea. or \$279 for pair. EXCAR-1, addl. carriage only.....\$69ea. or \$129 for pair.

VERY UNUSUAL, MULTI AXIS DRIVE SYSTEM, Includes just a few goodies!

This is a tough one to describe so try to follow. Lets start with TWO SLO-SYN steppers type: MO61-LF-504 mounted at one end on a 3/8" thick, black anodized aluminum plate. Each stepper has a 1/2" d. toothed belt drive pulley. Each belt rides over a spring loaded tensioner

and turns the end of its own, sealed ball bearing mounted, 14" L x 0.4" diam. stainless? polished lead screw with 8TPI. Each lead screw is mounted parallel to a polished steel rod of 0.375" diam. Each lead screw/rod combination support an anti-backlash carriage. One carriage (slide) can be considered an Z or Y axis with mini linear slide. Providing a stepper driven 3" of travel perpendicular to the long axis. Driven by a 1.5" cube sized, 4 wire stepper with 1.8deg/step and 80hm coils. Got that so far? The second long axis supports a stepper driven "3/4" travel "elevator" which is also oriented perpendicular to the long axis. Same cube size stepper as previous. Most axis have optical end of travel sensors as well. Overall size of assembly is: 6.5"W x 19.1" L x 10.5"H. Removed from equipment, very good condition. All of this can be reconfigured to suit many applications. Whew! That's a lot to think about. Don't think too long as we have, as usual, a limited quantity.

MAY SPECIAL, QUADRIVE.....\$69ea. or 2 for \$129

NEW, TYGON FLEXIBLE PLASTIC TUBING

Norton type B-44-4X, factory boxed, 50ft roll of 3/32 I.D. x 5/32 O.D. with 1/32 wall thickness. Very high grade, Tygon is recognized as the finest product of its kind. Unmatched rigid quality control.
TYGON-50.....\$10ea., or 3 for \$25

6V@12AH SEALED, RECHARGEABLE, GEL CEL. BATTERY,
New Panasonic, LCR6V12PI. Tough to get at a discount. Very compact. Two top mounted 1/4" faston connectors. Perfect for: high drain projects.
Size: 5.9"L x 3.7"H x 1.9"D 2 for \$20, or 10 for \$89

TWO MORE NEW ESOTERIC GOODIES? Do you think we have gone mad?

How about an 8313VAC @ 15KVA Pole Transformer. 120/240 VAC output. Of course you could use it as a step up couldn't you? It's new and its ships by truck. **Limited Qty. POLE-FMR.....\$350**

"For High Tension Relief"

how does a giant ceramic insulator sound? Now you can insulate yourself from anything you want... say your mother or father in law? This baby weighs 42lbs! and its size 18" x 8" diam with cast steel ends each with four 1/2" threaded mounting holes. We have only a few available. Would make a nice lamp. Hmmm... maybe coffee table legs? **Limited Quantity INSULATOR.....\$69ea., 4 \$239**

NEW, 3 POLE CONTACTOR, Fasco, type: 30E030 with 208/230VAC Coil,

NEW, Rated for:
240VAC 480VAC 600VAC
FLA/POLE 30A 30A 30A
RES/POLE 40A 40A 40A
LRA/POLE 180A 180A 180A
LRA 3PHASE 3 POLE 150A 120A
Size: 3.7"H x 2.5"W x 3.7"D and UL approved.
FASCO 30E030.....\$20ea. 3 for \$49

NEW, CURRENT TRANSFORMER, 500:5AMPS,

Instrument Transformer CAT 5, type, SFT-501

NEW, Rated for $\pm 1\%$ Accuracy, 600VOLT insulated Usable from 50 to 400HZ. Size: 4.2"H x 3.5"W x 1" Thick. UL approved too.
SFT-501 XFMR.....\$29ea.

NEW, 3M ELECTRICAL TAPE, Type, 471

Plastic tape, Two colors Blue and Yellow! You get five of each color, total 10 rolls each 3/4" x 108ft. Until we run out of one of the colors! **3M TAPE.....10 rolls for \$5**

HP OPTICAL ENCODER, HEDS-7500,

NEW, 1000 ppr quadrature, 256 ppr direct TTL compatible, A & B output for count and direction, 5VDC @20mA power. Shaft has a 1.1" diam., anodized aluminum, removable gear and mounting bracket. Perfect for do it yourself motion control. Size: 1.13" diam. x 87" d. Supplied with data. Removed from new equipment.
HEDS-7500.....\$15ea. or 2/\$25

WIRELESS MOBILE WORKSTATION is a Hackers Bonanza! Itronix T5000 mobile terminal with 2Meg. PCMCIA Mem card.

Well this is a device we would really like to know more about. Our people are working on it and this is what we know so far. This unit is built like a brick pizzeria. Polycarbonate case sealed from rain, dust and repeated drops. It has a 75 key QWERTY keyboard which curiously seems to be mapped one key off. These units were just replaced by a fortune 500 company that was using them in the daily operations. Therefore they must require some external input for the correct keyboard mapping. Probably a security measure? The flip up cover holds a transfective Samtron UG24D02 monochrome LCD display that we think is 640 x 240 pixels. Size: 7.3"W x 2.75"H and displays 16 shades of gray also has a white E/L backlight. The unit has an internal Motorola Type RPM4051 Radio Packet Modem with built in flip up antenna. We believe it operates on the ARDIS or similar network. There is also an RS-232 serial port / bar code wand port. Also there is a port for a hand held laser scanner. Power required: At the external connector, 10VDC @ up to 800mA. The unit only draws about 175ma after boot. The battery packs were 7.2V. They were originally powered by a NICAD pack which has been removed. The battery compartment is external and could easily hold an alternate power source. We believe there is an internal modem as the unit sports an RJ-11 style connector as well lip and ring connections. Upon the application of power the 80C552 processor boots MS DOS ROM Version 5.00 to an A: > prompt. The screen indicates an internal memory of 640K. A 2meg. PCMCIA memory card is also supplied. Operating temp from -4 to +140F. From there on your own. All units are tested for boot up otherwise sold as an experimenters package.
T5100.....\$49ea., or 3 for \$129

IT WILL MOVE YOU! PRECISION, XY TABLE.

Long travel, Really nice and like new. (Removed from a \$100K film scanner) Super X-Y table offers approximately 24"x 24" of travel. The system is stock mounted to a rugged tubular steel, wheeled base with a chrome colored powder coat finish. Dual, heavy duty, Berger RDM-566-50, 1.3A, 140hm stepper motors are attached. Heidenhain 500ppr encoder on one axis. Stepper drivers are not included. Perfect for laser system. Overall size is 55" x 44" x 39" Ships via truck.
Limited Qty.....\$1295

FABULOUS, NEW, YAG LASER SYSTEMS provide 100Watts, CW @1.064um, also a frequency doubled model with 40Watts @ .532um (green)

Laser Photonics Type YCO-1003M, adjustable output power from 100mW to 100Watts $\pm 2\%$. Modes include: CW, Single pulse adjustable from 0.1 to 9.9 seconds in 0.1 sec increments. Repeat pulse with adjustable duration as previous and adjustable rate from 0.1 to 9.9 seconds in 0.1 sec. increments. Beam delivery via a 4 meter length quartz fiber optic.

Internal fiber calibration system. LCD control panel for easy setup. Frequently used program settings can be saved to memory. Internal graphics printer. Pulsed laser diode aiming laser. Two stage microprocessor system monitoring. Key switch access with foot switch laser activation. Internal liquid to air cooling. Power required: 220VAC, single phase @40A, 60Hz. Mechanical: 38"H x 33"W x 22"D, weighs 325lbs. Wheel around cabinet. The Dual mode system in addition to the YAG specifications above includes frequency doubling on demand. The green output is Q-switched at 10KHz producing an output beam of 6mJ @ 200ns or 60W average with 2 to 40 watts delivered at the fiber. Pulse mode operation for the dual mode is different as well: Single pulse mode is adjustable from 0.1 to 600 seconds in 0.1 sec. increments. Repeat pulse mode has the same adj. pulse width and an adjustable pulse interval of 0.1 to 9.9 seconds in 0.1 sec. increments. These numbers apply to the 1.064 wavelength only. Cabinet size: 40"H x 33"W x 23"D weight 500lbs. Both models are NEW. Must ship via truck.
SINGLE YAG SYSTEM.....\$18K, DUAL FREQUENCY YAG SYSTEM.....\$25K

NEW, GEN III, INTENSIFIED GOOGLES, STATE OF THE ART, U.S. MADE.

The NQ5001, the world's most rugged and reliable, high performance night vision goggles for ground operations. Extensively used by the U.S. Army, it is the State-of-the-Art in mono-tone Night Vision Goggles. Utilizing the MX-10130 Gen III intensifier, it can be used in the darkest of conditions, headstrap mounted or handheld. Engineered for maximum comfort and simple to use. The system contains an IR illuminator, low battery indicator & high light sensor for automatic power off to image tube. Soft Case, headstrap, demist shields, sacrificial filter, eye cups, 2 AA batteries, and operators manual.

Specifications:
Photocathode Gallium Arsenide
Resolution 45 lp/mm
Objective Lens 25mm F/1.2
Field of View 40°
Tube Gain 35,000x
System Gain 3,200x
Signal to Noise 18:1
Battery Type 2 AA Life 20Hrs
Magnification 1x
Objective Lens 25mm F/1.2
Field of View 40°
Focus Distance 2.5m to Infinity
Size 14.9 x 14.9 x 9.1 cm
Weight 680 gm
MAY SPECIAL.....2495ea.

NEW WEB SITE NOW ON-LINE

WWW.RESUNLTD4U.COM

PLEASE VISIT TODAY

RESOURCES

UN-LTD.

VISA, MC, AMEX, DISCOVER, COD, ON-LINE

ORDER: 800-810-4070 TECH:LINE 603-668-2499

FAX: 603-644-7825 EMAIL sales@resunltd4u.com

300 BEDFORD STREET, MANCHESTER, NH 03101

CO₂ LASER SYSTEM is SELF CONTAINED and MOBILE!
Fabulous 20Watt Laser with flexible, hand held, beam delivery.
 True plug and play operation. Simple 120VAC @3amp power and "BAM, kick things up a notch". This unit is specifically designed for "cutting, coagulation and ablation". Laser functions are controlled by a user friendly control panel. Self contained & air cooled, CW or pulsed mode operation. Sealed CO₂ technology for long life & low maintenance. A simple foot switch energizes the laser, leaving you free to use the focusing hand piece. Selection of power & duration are made through the control panel with LED display. Accuracy of the delivered power is maintained through an internal calibration feature. A 1.5mW, 635nm, red aiming laser diode is visible at the precise focal plane of the CO₂ output. Maximum operating time at full out put is 10 minutes. CO₂ laser is class 4 with output at 10.6 microns. Output power is selectable from 1 to 20 watts. Spot size 0.3mm at tip. Super pulse mode offers 1 to 10 Watts, 600usec. pulse width up to 750Hz rate. Single pulse width of 0.1 to 1.0 sec. Pulse train of 0.1 to 1.0 sec. with 50% duty. Internal air purge system. Heavy duty industrial construction with integral wheels for one handed portability. Size: 38"H x 25"D x 12"W. Weight is 80lbs. Includes operation manual. Slightly used in mint condition. Don't miss this one. **SPECIAL Limited Qty., CO2-CS1.....\$3500ea.**

MINIMOTOR SA, SWISS GEARMOTOR, Sooooo TINY
 State of the art "ironless" type, mini motor.
 Model: 1219E-012G-400. Includes a 104:1 Planetary gearbox. Size: 12mm d x 44mm l with 2mm x 6mm l, flatted shaft, solder terminals.
 @VIN INL RPM
 6V 5mA 68
 12V 5mA 145
LIMITED QUANTITY
TYPE A: \$22ea. or 5 for \$99

NEW, TELECONFERENCING MIC, Super high quality construction, PictureTel, system mic 200.
 Was used on the "Venue 2000" video conferencing system. The handsome desk top unit includes 25ft. of cable. The internal includes a noise cancelling electret microphone with preamp and gain control. Operates on 12VDC @50mA.
MIC200.....\$12ea. or 3 for \$25

ULTRA MINI and WEATHERPROOF, "LIPSTICK"
 Sleek black anodized, alum. housing, O-Ring sealed & RAINPROOF. Adj. tilting mount. 1/3" CCD, 380 Lines, 0.3 Lux, AGC, Auto Shutter. 9-12VDC @100mA, 4mm, f1.8, 78° FOV real glass lens, NTSC video. <1ounce! IR SENSITIVE. 23mmx50mm, 36" cable with BNC video & DC barrel jack.
GM-200K, PINHOLE Model. So tiny you can install it directly into a door. Only a 0.9" diameter hole! Specs as above. 90° FOV Pinhole lens. 1/2 ounce! Size only 23mm x 35mm long. Think of the places you could put this little jewel.
LOOK! SPECIAL MAY PRICE, GM-200KSTD..\$69
LOOK! SPECIAL MAY PRICE, GM-200KPH.....\$69

NEW! LCD COLOR, TFT, ACTIVE MATRIX DISPLAY
Offers a super 5.6" VIEWABLE AREA.
Pro System Available with Custom Case, BUILT-IN 12V GEL CELL, all A/V cables and charger. Super Deal.
 You asked for it. Finally we found a unit with exceptional quality at an affordable price. Perfect as a portable, general purpose color monitor for standard NTSC color or B&W video systems. Fully compatible with all our cameras as well as Camcorder, VCR's etc. Perfect as a rear view system with any video camera by virtue of its built in, mirror image function. Completely enclosed unit has adjustments for color, contrast and brightness and volume, for it's internal stereo speakers! A std. 1/4 x 20 Tripod socket and a tilt down stand for table top viewing. Inputs include: audio (L&R) and video on std. 1/8" mini jacks. External 12VDC on std. barrel connector. Specifications: 5.6", TFT active matrix LCD with 76.8K Pixels, CCR, backlight with 270cd/m luminance, 500mW audio output available on std. 1/8" jack. 12V@600mA powered, 50mV min. or std. line level audio input. Overall size: 6.4"W x 5.25"H x 2.2"D. New first quality. An optional accessory kit is available which includes: A luggage quality, custom made, padded case with dual removable straps for shoulder and/or holding at waist level for portable, hands free viewing. Built into the case is a 12V Gel Cell, rechargeable battery. Also supplied is a complete set of A/V cables. AC power adapter, power switch and battery charger.
GM-TFT56, with AC power adapter.....\$299ea. GM-ACCYFT.....\$45

NEW, "COLOR STEALTH CAM", MICRO SIZE, with AUDIO!
 That's right! COLOR! In the same size package too! Sleek aluminum housing fits like a glove! Removable mtg. bracket & a 1.3m cable with BNC vid., RCA aud., internal mic & DC pwr. jack for no sweat hook up. Why fool around with an open P.C. board? Now you can have the "COLOR STEALTH CAM"
 • 1/3" • 350 Lines • 0.7 Lux • AGC
 • Auto Shutter • Pwr. 6-12V @30mA
 • 270K pixels • Std. 7mm, 56° FOV lens
 • Focus:10mm to inf. • NTSC video
 • 1-ounce! • Size: 31mm sq. x 28mm d.
GM-4000S-STD w/audio, SPECIAL..\$89ea.
B & W "STEALTH CAM", MICRO SIZE, with AUDIO!
 The sleek aluminum housing fits like a glove! Removable mtg. bracket & a 1.3m cable with BNC vid., RCA aud., internal mic & DC pwr. jack for no sweat hook up. Why fool around with an open P.C. board? Now you can have the "STEALTH CAM" • 1/3" CCD • 410 Lines • 0.3 Lux • AGC • Auto Shutter • Pwr. 12V @110mA • 250K pixels • Std. 4mm, 78° FOV lens • Pinhole, 90° FOV • Focus:10mm to inf. • NTSC video • 1-ounce! • SENSITIVE • Size: 30mm sq. x 29mm d. PH: 16mm d. Don't confuse with LOW RES. HIGH LUX C-MOS CAMERAS. **GM-2000S-STANDARD OR PINHOLE, SPECIAL..\$69ea.**

NOW YOU CAN SEE WHAT THE "FISHES ARE DOIN" (down 60 ft.) UNDERWATER B&W CAMERA with INTERNAL, INFRARED ILLUMINATOR!
 Sleek black anodized, BRASS, housing, O-Ring sealed & WATERPROOF. Adjustable mount incl. Specs: 1/3" CCD, 400 Lines res., 0.05 Lux sensitivity, AGC, Auto Shutter. 12VDC @225mA, 4mm, 78° FOV lens, A real glass lens. NTSC video out. Superior construction. SENSITIVE to IR.
 Ultra small Size only: 1.25" diam. X 2" long. With 60 ft. cable. Perfect as a remote area inspection camera. Great for general outdoor use as well. **GM-300KIR.....\$179**

SEIKO INTELLIGENT ROBOTS, D-TRAN RT-2000
Cylindrical Coordinate Servo Robot with Controller.
 The robot is based on a four axis, closed loop servo system. The provided teach terminal allows for programming and direct robot operation. Programs can also be downloaded from a PC. The included controller requires 220VAC @0.5KVA. Controller Size: 17"W x 10"H x 21"D. The robot offers high precision, repeatability and speed. Some specifications include: Max. Swing area: 20.6" radius. Base plate dim: 13" x 8.6". Repeatability: ±0.0006". Speed: 63"/sec. Payload @ max. speed: 5.5lbs. Overall dimensions: 11"W x 24.6"D x 21"H. Robot only weight: 110lbs. System also includes: 1" thick solid steel base plate, I/O interface module, Dual RS-232 comm. ports and printer port.
 Specs: Rotation Resolution Speed Reach Stroke Max. Torque.
 A AXIS 290° 0.005° 240°/s N/A N/A 30 Kg. cm
 R AXIS N/A 0.0003° 47"/s 20"/16" 9.84" 30 Kg. cm Vert.
 T AXIS 290° 0.0009° 110°/s N/A N/A 20 Kg. force on T
 Z AXIS N/A 0.0001° 15"/s N/A 3.94" 6kg. @250mm
 Only one chance to own this robot. Removed from working lab. Sold as is. Software available from Seiko. Original cost >\$36K
Ships via truck. D-TRAN, RT2000.....\$2895

A FLEXIBLE, ARTICULATED MANIPULATOR
what wild uses can you think of this?
 What we have here is a 40" long X 3/8" diameter remotely controlled and effector. The probe tube is protected by a steel sheath covered in a flexible plastic jacket. This particular model was intended to hold an ultrasonic transducer for inserted into the body for diagnostic purposes. (Not by aliens as far as we know!) The inside of the tube is hollow and about 1/4" in diameter. All minor wiring and sensor hookups could be manipulated through this channel. The last 2.5" of the device, the "business end" is linked to the hand piece via a system of four steel mini cables. Two knobs on the hand piece cause the tip to move ± 90 degrees in a 360 degree arc about the tip. It is quite amazing to see. It looks "alive" Operates on similar principal to those hand controlled anemimetric devices used in movies except on a smaller scale. So use your imagination, connect something interesting to the tip and start being an articulate manipulator. These were removed from evaluation lab and may not have cover for handpiece. Does not effect operation. **MANIPULATOR.....\$225ea.**

NEW! Q - SWITCH, CRYSTAL TECHNOLOGIES, MODEL 5100
 We were fortunate to obtain a small quantity of these first quality units. They were destined for use in a 100W YAG laser. See our "YAG DECKS" previous page. No specifications at press time. Water cooled. A limited number of matching RF drivers for these Q-switches are available.
Q-SWITCH.....Q5100.....\$225ea.
RF DRIVER.....RFMHZ-5100.....\$350ea.

PRECISION GEARMOTOR with GOVERNOR
TRW, GLOBE IND. Type, 25140
 VIN INL RPM
 6V 160mA 600
 9V 180mA 1180
 12V 210mA 1675
 New and very high quality MIL SPEC. mini motor with a planetary gearbox (ratio unknown) and governor output. Size: 18mm d x 72mm long not including the 2 mm diam. x 11mm long, flatted shaft, with attached 3" wire leads.
TRW-GOV.....\$22ea. or 2 for \$39

ZOOM RIFLE SCOPE, BUSHNELL 3-7X Custom .22
 We have a small quantity of these used zoom scopes removed from optical equipment in good condition. They have an 18mm objective and an eye relief of about 2.5". Basic cross hair reticle with windage and elevation adjustments. Standard Weaver type groove. Sorry we have no mounting bases. Size: 9.75"L x 1.1"D max.
BUSHNELL.....\$20ea.

CUBE BEAM SPLITTER w/FREE EG&G detector & signal conditioner board.
 EG&G, SCD 100A detector mounted at the approx. 7% split output of a 12mm cube beam splitter. Transmission is about 85% straight through. The signal conditioner board operates from ±15 VDC. All optical components are mounted on an anodized adjustable mount. Used in good condition.
EGG-B51...\$20ea. 2 for \$35

STEPPER MOTORS with Belt drive pulley, NEW, VEXTA type PH265M-31, Each 6 wire stepper has a removable 1.2"d. toothed belt drive pulley. The motor is rated for 6VDC @0.85A and 0.9sec/step with 5" long wire leads. Very high quality unit. Standard mounting size: 2.74" x 2.21" x 2.2" flat face, 0.25"D x 0.61" shaft, \$15ea. or 2 for \$25

10V @ 2.5 AH SEALED, LEAD ACID, PACK.
 Each pack has 5, 2 Volt cells. D'size cells are arranged in 1X5 cells. Enclosed in an ABS outer shell. (removed for photo) Perfect for high drain applications. Make custom packs of any rating. Size: 7.5" x 2.8"H x 1.5"D. **6-five packs for \$20, 40 for \$99**

WOW! THERMAL IMAGER from TEXAS INSTRUMENTS, NIGHTSIGHT 100.
 Detects a human sized image at up to 800ft., in complete darkness. Yes, it is tough to hide from a thermal imager. (You have seen them in action on "COPS") This like new unit generates a real time, black and white video output, compatible with any standard monitor or VCR. Unlike "Night Vision" systems which require some available light or added external illumination, the thermal imager will operate in TOTAL darkness. Also ambient lighting such as street lights or bright auto headlights have no blinding effect. Thermal imagers function by detecting the difference between the background ambient temperature and the temperature of the objects being observed. Completely self contained, apply 12VDC and it works. Specifications: Temperature stabilization via internal thermoelectric cooler. FOV 27H x 18V degrees. Power required: 12VDC @2Amps max. Video output standard NTSC/Composite, Auto brightness and contrast. Selectable image polarity. <30 seconds from turn on to operation. Operating temp. range -40 to +122°F. Waterproof package is only 8"H x 7.4"W x 8"D. Weight: 6.5 lbs. FANTASTIC don't miss out. **Regular Price \$8500, SPECIAL, NIGHTSIGHT 100.....\$5549ea.**

A VERY COOL COLOR CAMERA, "The ROVING EYE CAM" with Ultra Compact PAN and TILT AUTO IRIS and AUTO FOCUS to boot!
 Another super quality color conference camera designed as part of a high end system from PictureTel. The unit consists of a camera head attached to a base PC board. The attachment is via a moveable mount. There are two tiny stepper drives which create the pan and tilt motion. The tilt stepper is mounted to the PC board. The pan stepper is unmounted and attaches to the side on your base or enclosure. We assume the camera is controllable via serial commands however we have no info on how to do it. Anyone who can tell us can have some free cameras. The camera module specs: 400 lines @ 1lux, the power required is 12VDC @500mA. size of head is: 5.5" diam. x 3.2"H. The attached PCB is 3W x 4L x 1.3"H. Oh, and did we mention it's auto focus and auto iris too? Composite video output. We think it has Y/C also. Check our web site for further details as they become available. Order now, the price goes up when we get the serial commands. Removed and tested. **SPECIAL MAY PRICE MINI-R2D2 CAM.....\$149ea. or 2 /\$289, or 5/\$499**

CO₂, 120Watt CW, SEALED GLASS LASER HEADS
Integral Hard Sealed Mirrors, NEW!
 High quality water cooled heads. Were originally designed for medical application. All models are similar in construction. Size of the model 103: 6.01" x 3.2" diam. Model 160: 4.41" x 3.2" diam. Model 135: 3.51" x 3.2" diam. Power requirement, model 103, 40KV trigger with 25KV @ 10 to 30ma operating current. Model 160 and 135, 30KV trigger with 15-20KV @ 7 to 20ma operating current. They are not toys. They must conform to Class IV CDRH regulations when assembled into a functioning system. Perfect for engraving, cutting and drilling most materials. Only three available. Only one 200W system. We don't expect any more.
Special 200W dual tube head with metal housing & dual power supply.....\$4395.
Limited Quantity.....100+Watts.....\$1475., 35Watts.....\$895.

SUPER SPECIAL OFFER, ACCESSORIES to COMPLETE YOUR CO₂ SYSTEM!
CO₂ Power Supplies: for 100Watt+ Tube..\$495ea. Supply for 35Watt Tube..\$399ea. 100W, power supplies are used, tested and guaranteed. 35Watt, power supplies are NEW! Supplies are not sold without laser tube purchase. **Articulated beam delivery arm with focusing hand piece. Brand new. A fantastic item. Regular price >\$3500. ea!** With purchase of tube..\$895ea. Arm without laser tube..\$1295ea.
A NICE ASSORTMENT OF CO₂ and YAG OPTICS to MAKE YOUR LIFE EASIER!
All NEW and factory boxed first quality, BK-7 glass or ZnSe.

ITEM #	NAME	DESCRIPTION	MSC
RP10-02	RISLEY PRISM	1deg. AR @1064 & 540 to 650nm	Alignment/multi wavelength path.
RP10-03	RISLEY PRISM	1deg. AR @450 to 650nm	Alignment/multi wavelength path.
BS10-01	BEAM SPLITTER	AR @45deg for 1064nm	YAG or CO ₂ , High Power
BS10-02	BEAM SPLITTER	AR @45deg for 1064nm	YAG or CO ₂
DUAL-01	MIRROR/HT-HR	HT @45deg, for 532nm, HR for 1064nm	High Power
PLCV-01	DUAL FREQ LENS	HT for 1064 and 6328nm >98.5%, 113mm	Focus CO ₂ & HeNe ZnSe


Order by Item Number. All models priced at \$25ea. or 2 for \$45

ACOUSTO-OPTIC MODULATORS, ISOMET 1205C-2

Spectral Range	Active Aperture	Material	Typical Risettime	Information Bandwidth	Center Frequency
440-1.5µm	2.0mm	PbMoO ₄	25nsec	15MHz	80MHz

 Removed from equipment, excellent condition. **ISO-1205C..\$35ea. 2 for \$59**

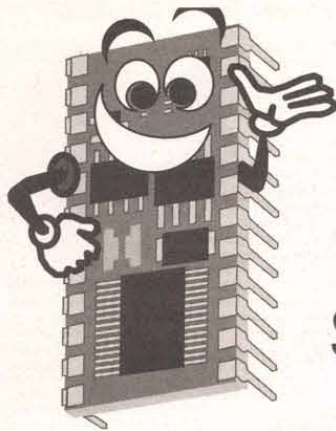SECURE ON-LINE ORDERING
WWW.RESUNLTD4U.COM
RESOURCES UN-LTD.
 VISA, MC, AMEX, DISCOVER, COD, ON-LINE
 ORDER: 800-810-4070 TECH:LINE 603-668-2499
 FAX: 603-644-7825 EMAIL sales@resunltd4u.com
 300 BEDFORD STREET, MANCHESTER, NH 03101



by Jon Williams

Stamp Applications

Stamping Myself Into Better Shape

Putting the Spotlight on BASIC Stamp Projects, Hints, and Tips

One of the best things about doing electronics as a hobby or profession is the ability to design something useful that doesn't currently exist. Case in point:

It's hard to believe, but the BASIC Stamp has been around for almost seven years now. While this column isn't quite that old, it's been around awhile too, and the three of us that have written it have delved into some reasonably sophisticated projects.

Parallax has made terrific efforts in the way of getting Stamps into the hands of youngsters through their "Stamps in Class" program. What this means is a whole new crop of young Stampers. This month, we're going to take a step back in sophistication and focus on the process of program development.

It's a simple project and yet, might even teach the "old dogs" a few new tricks.

Some of you know that I'm a part-time actor. Yes, really, an actor — I have an agent, go on auditions, and even get hired from time-to-time. I was recently lamenting to a friend about some great auditions I'd had that didn't result in bookings. It is the worst part of being an actor: the unexplained rejections. My friend reminded me that — especially in commercials — most of the time it's about appearance, and that almost everyone being called in to audition can act. It made me think long and hard. I've spent the last two and a half years training with the best acting coaches in Dallas and, sad to say, have not dealt much with my appearance. I guess I could blame my advancing age for my advancing waistline, but the fact is I really should make an effort to drop a few pounds. I just saw myself on tape from my last stage appearance and was not happy.

I study with an actor named Tim who is in great physical shape. On a class break, I approached Tim about his exercise regimen, expecting to hear about how he spends a couple hours a day in the gym and eats next to nothing. Not so. Tim told me how he entered a 12-week contest and dropped an amazing amount of weight and completely transformed his physique. He even showed me his driver's license photo to prove it. He had made an amazing transformation and had spent less than three hours

per week in the gym! Hey, I can live with that.

Well, I don't really want to enter a contest, I just want to drop 10 or 15 pounds and improve my physical appearance. As luck would have it, I found a book that detailed the diet and exercise regimen that Tim follows. To my very happy surprise, the diet and exercise plan is not difficult, yet it is regimented and needs to be followed with some discipline.

Specific to the exercise plan is the timing. While the aerobic part of the plan calls for only 20 minutes of exercise every other day, it must be done in a specific manner: four cycles of five minutes each, with each cycle divided into four stages (two minutes, one minute, one minute, then one minute).

I turned to my cool digital wristwatch. Darn! The timer has only three stages, and between the overhead TVs, the radio blaring, and the other treadmills, I can't hear the watch beeping in the noisy environment of the gym, anyway. Sounds like a good opportunity to build a custom circuit. Sounds like a great opportunity to use the BASIC Stamp!

So, I want a little exercise timer that will time four cycles of five stages and give me both visual indicators for use in the noisy gym and an audible indicator for those days that I'm on the jogging trail and the unit is strapped to my arm.

Before we jump in, let's talk a bit about the "process." What I mean by this are the steps that we will follow to develop our project. Don't make the mistake of thinking that you can just jump right into small projects without planning them — like dogs, small projects can bite you as badly as big ones.

Here's a good process to use for Stamp project development:

1. Define the project/product
2. Design the hardware
3. Write test code to verify hardware design
4. Write software
5. Test software to requirements
6. Field-test project
7. Refine software and re-test

Define the Project

The first step, "define the project," is the trickiest and causes the most amount of trouble because it is usually taken for granted. I'm sure you've heard the phrase "Plan your work, work your plan." That's what Step 1 is all about. You'll save a lot of time and — especially if you enter the professional ranks — a lot of development money if you commit

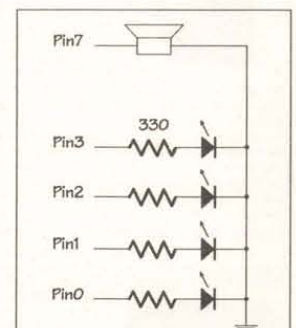


Figure 1: Exercise Timer schematic

STAMP APPLICATIONS

Stamping Myself Into Better Shape

to Step 1.

How do we do this? The answer is simple and yet, it's not always easy: We must fully understand our customer's wants and needs. So take the time to do this step well. Ask a lot of questions. Sometimes the customer will be you. That's okay and doesn't excuse you from the step. And if the customer is someone else — especially if that someone will be paying you for the product — you really need to be diligent. If you don't, you may find yourself delivering a product that is missing features or, worst of all, is nothing close to what your customer actually wants.

Okay, I've already described our little exercise timer, and we're just going to leave the definition as-is for the moment. Let's move on to the hardware (Step 2).

Hardware

Our timer needs four stages, so we'll use an LED for each. Since we have a little bit of Stamp experience, we'll connect the LEDs to the lower bits of the output and use positive logic (output high will light the LED). This will be fine since we're only going to turn on only one LED at a time. We can get a little more current out of the Stamp if we use inverted logic (output low turns on LED), but this makes the code a little more difficult to read. The last thing we need is something to make sound. A small piezo speaker will take care of that nicely. See Figure 1 for the schematic of the exercise timer.

Testing

With the hardware designed, we need to test it. This is especially important since there is a lot of hardware interacting with the Stamp. While that's not the case with this project, we still need to test it, and we'll use this opportunity to develop a little bit of the code for the final project.

Listing 1 is the test code. To some, this code may look a little more refined than what one would generally consider "test" code, but it's best to have neat code from the start. That way, we're not cleaning up our test code to put into production; it's usable as-is.

For you beginners, I can't stress enough the importance of using SYMBOLS. Using SYMBOLS will save you time by making your code somewhat self-documenting. This allows you to focus on the code instead of the comments. And don't forget that PBA-

SIC allows you to assign more than one SYMBOL to the same variable (this is called aliasing). You can do this when you're running out of variables and want to use the same one in different parts of the program. Just keep in mind that PBASIC variables are global and you'll want to make sure that using a variable in one part of a program under a given alias does not interfere with its operation in another part of the program. Here again, planning will keep you out of these sticky spots.

The test program is pretty basic. We want to make sure that the LEDs work and that the beeper sound is pleasing. To that end, we've decided to structure the code like a shortened exercise cycle. One thing that I know I'm going to need is some sort of delay routine. We can't get away with a simple PAUSE command because the first stage is two minutes long. Since the maximum PAUSE value is 65535 — just over a minute — it won't work.

We could choose to use PAUSE 60000 twice for the first stage, but this doesn't give me much flexibility or re-use in this project or others. A delay routine that works in seconds would be a little more flexible and easier to apply elsewhere. In the Subroutines section, you'll find "DlySec." This works by setting the variable "secs" to the value we want and calling the routine with GOSUB. By using byte-sized variables, this routine will give us a delay of four minutes, 15 seconds (255 seconds). If you want to modify this to run longer, you'll need to change both "secs" and "loops" to word-sized variables.

Software

Okay, the LEDs work and the beeper sounds great, so let's start the production code (Step 4). Listing 2 is our first attempt. You see that it's really not too much of a change from the test code. In fact, the only thing necessary to get us from the test code to meeting the basic specification was to create a loop in the main body of code so that the program will run four cycles.

The code works — great! Now we could stop here, but what we've noticed is that there's a big chunk of code that has redundant sections that we may be able to refine. If we look at the operation of each stage, it goes like this: Turn on the stage LED, sound the beeper, time the stage. Yeah, we can clean this up a bit.

Take a look at Listing 3. What we've done is added an inner loop to handle the four stages of each cycle. We're able to deal with the discrete differences between each stage by using

```
' Stamp Applications - May 2000
' Listing 1

' -----[ Title ]-----
'
' File..... XTIMER1.BAS
' Purpose... Exercise Timer - Hardware test code
' Author.... Jon Williams

' -----[ Program Description ]-----
'
' Hardware test code for exercise timer project

' -----[ I/O Pins ]-----
'
SYMBOL BprPin = 7

' -----[ Constants ]-----
'
SYMBOL BprTone = 75
SYMBOL BprLen = 16          ' 0.192 secs

' -----[ Variables ]-----
'
SYMBOL secs = B2
SYMBOL loops = B3

' -----[ Initialization ]-----
Init:  Pins = %00000000      ' LEDs off to start

Dirs = %10001111            ' LEDs and Piezo outs

' -----[ Main Code ]-----
Main:
  Pins = %0001
  SOUND BprPin, (BprTone, BprLen)      ' stage 1 LED on
  secs = 120                            ' sound start of stage
  GOSUB DlySec                          ' 2-minute stage

  Pins = %0010
  SOUND BprPin, (BprTone, BprLen)      ' stage 2
  secs = 60
  GOSUB DlySec

  Pins = %0100
  SOUND BprPin, (BprTone, BprLen)      ' stage 3
  GOSUB DlySec

  Pins = %1000
  SOUND BprPin, (BprTone, BprLen)      ' stage 4
  GOSUB DlySec

Done:  Pins = %0000
  SOUND BprPin, (0,12,50,12,75,12,110,12) ' LEDs off
                                           ' sound end

END ' of program

' -----[ Subroutines ]-----
DlySec: FOR loops = 1 TO secs
  PAUSE 1000                            ' pause 1 second
  PAUSE 10                              ' quick pause for testing
NEXT
RETURN
```


STAMP APPLICATIONS

Stamping Myself Into Better Shape

LOOKUP to get the values we need for the LED output and for the stage timing. Notice that our stage loop is zero-based (goes from zero-to-three instead of one-to-four). This is necessary to conform to the requirements of LOOKUP. The first element in the LOOKUP table corresponds to the control variable value of zero.

Software Testing

All right, time for testing. Everything seems to be working fine and we even used less code space by adding the stage loop. That's good, it means there's more room for future features. Then something happened. I got up to get a drink of water and, while walking away, the beeper sounded. Cool, the next stage. But what stage? While I'm out on the jogging trail I don't want to think about where I am — I just want to be told what to do next.

What we need to do is have a distinct audio indication for each stage, just as each stage has its own LED. Take a look at Listing 4. What we've done is replace the single SOUND command that's embedded in our loop with a call to a subroutine named — appropriately enough — "Beep." Beep takes advantage of another great PBASIC command: BRANCH. We use BRANCH to route the routine to the appropriate sound commands. Stage 1 uses one low-frequency beep, Stage 2 uses two low-frequency beeps, Stage 3 uses one high-frequency beep, and Stage 4 uses two high-frequency beeps.

That's much better. Now it's time to move from the breadboard to a device that can be "field tested" (Step 6). It's one thing to conform to specifications in the lab, but it's in actual use where we really find out how well we've done our job.

Field Testing

Okay, I put on some gym shorts, laced up my favorite jogging shoes, and hit the trail. So far, so good. I'm thinking, "Yeah, baby, I can feel the pounds melting away." Then, just as I was so proud of myself, I tripped over an untied shoelace. To make matters worse, the lace breaks as I'm re-tying it, and then the beeper indicates it's time for the next stage. Shoot! This isn't working out — I need a Hold switch on the timer.

To be fair, we can't always foresee these problems in the design stage — that's why we do field testing. That said, we would minimize the chances of major problems arising during field test by asking a lot of questions up front; especially questions on how the device will be used. Field testing, as we've just seen, will catch all the final "gotchas."

Refining

Adding the hardware for the Hold switch is the easy part (see Figure 2); the software to support it is going to require a little more work. The reason is that we've kept things very simplistic. I'm not criticizing what we've done so far because it does work. The simplicity, however, does not support much in the way of flexibility and now we have to take a step back and re-design our code. Now you see why it's so important to know — to the extent we can — all of your project requirements up front.

Our Hold switch will work by suspending the current stage until pressed again. The device will tell us it's on Hold by flashing the current stage LED. Finally, we'll start the program in Hold mode since it's just a bit easier to press the Hold button than to flip the power switch when we want to get started.

You may remember from last month that I suggested we could give our programs a lot of flexibility by breaking them up into small chunks and using a "task switcher" or "time slicing" approach. Since the concept as it applies to this project may not be immediately obvious, let's just jump into the final code and see how we got there. Once you understand the concept, you should find it reasonably easy to apply to your time-oriented programs.

What you'll immediately notice is that the delay routine is gone and we've added quite a few variables. The approach of this program takes advantage of the fact that most programs run in a loop. What we're going to do is keep the loop simple and somewhat constant, allowing us to use it as a time base.

Did you know that the first PCs didn't have real-time-clock

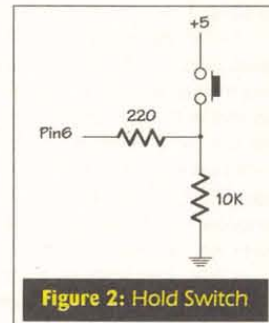


Figure 2: Hold Switch

```

Stamp Applications - May 2000
Listing 2

' -----[ Title ]-----
' File..... XTIMER2a.BAS
' Purpose... Exercise Timer - Version 2 (4 cycles, full time)
' Author.... Jon Williams

' -----[ Program Description ]-----
' This program serves as a multi-stage exercise timer. The program runs
' four cycles of four stages, with an LED and audio indication for each
' stage.

' -----[ I/O Pins ]-----
SYMBOL BprPin = 7

' -----[ Constants ]-----
SYMBOL BprTone = 75
SYMBOL BprLen = 16
' 0.192 secs

' -----[ Variables ]-----
SYMBOL cycle = B2
SYMBOL secs = B3
SYMBOL loops = B4
' stage timing (minutes)
' counter for long delay

' -----[ Initialization ]-----
Init: Pins = %00000000
' LEDs off to start

Dirs = %10001111
' LEDs and Piezo outs

' -----[ Main Code ]-----
Main: FOR cycle = 1 TO 4

    Pins = %0001
    SOUND BprPin,(BprTone, BprLen)
    secs = 120
    GOSUB DlySec
    ' stage 1 LED on
    ' sound start of stage
    ' 2-minute stage

    Pins = %0010
    SOUND BprPin,(BprTone, BprLen)
    secs = 60
    GOSUB DlySec
    ' stage 2

    Pins = %0100
    SOUND BprPin,(BprTone, BprLen)
    GOSUB DlySec
    ' stage 3

    Pins = %1000
    SOUND BprPin,(BprTone, BprLen)
    GOSUB DlySec
    ' stage 4

    NEXT ' cycle

Done: Pins = %0000
      SOUND BprPin,(0,12,50,12,75,12,110,12)
' LEDs off
' sound end

END ' of program

' -----[ Subroutines ]-----
DlySec: FOR loops = 1 TO secs
        PAUSE 1000
        ' pause 1 second
        PAUSE 10
        ' quick pause for testing
    NEXT
    RETURN
    
```


STAMP APPLICATIONS

Stamping Myself Into Better Shape

chips? They kept time, at their lowest level, by keeping a tic counter. Tics were then converted into the appropriate time format. That's what we're going to do. Our code will run in a continuous loop and each pass through the loop will cause the tic counter to be updated. Actual loop timing is a bit of a trade and some projects will require experimentation to get the best results. We have an additional requirement: to monitor and debounce the Hold switch. Yes, we could just use the PBASIC BUTTON command, but it's not my favorite and can be a little confusing. What we'll find is that loop-based architecture of our code will support monitoring and debouncing the switch with fairly simple code.

For the moment, we'll arbitrarily decide to run our loop at 20 times per second, or 50 milliseconds per loop iteration. Since our stage delay is in seconds, we'll want to count 20 tics (loops) and

then update a seconds counter. When the seconds counter reaches the stage timing value, we'll move on to the next stage.

Take a look at the main body of code. The beginning of each stage is noted with the stage LED lit and an audio indication. This will only occur when our seconds timer (timing the current stage) and the tic counter (time base for seconds) are zero. We also need to load the stage timing when we start a new stage.

At the heart of our loop is the PAUSE command that pads it to 50 milliseconds. We need this because even the Stamp 1 can zip through its code pretty quickly. Now you'll notice that the SYMBOL called "LoopTm" is not set at 50 (it's 46 in the final code). It did, indeed, start at 50 and was fine-tuned during testing. I'll explain how at the end.

Now we get to the switch monitoring and debouncing. The

```
' Stamp Applications - May 2000
' Listing 3

' -----[ Title ]-----
'
' File..... XTIMER2b.BAS
' Purpose... Exercise Timer - Version 2 (refined main loop)
' Author.... Jon Williams

' -----[ Program Description ]-----
'
' This program serves as a multi-stage exercise timer. The program runs
' four cycles of four stages, with an LED and audio indication for each
' stage.

' -----[ I/O Pins ]-----
'
SYMBOL BprPin = 7

' -----[ Constants ]-----
'
SYMBOL BprTone = 75
SYMBOL BprLen = 16          ' 0.192 secs

' -----[ Variables ]-----
'
SYMBOL cycle = B2           ' cycles counter
SYMBOL stage = B3           ' stage counter
SYMBOL secs= B4             ' stage timing (seconds)

SYMBOL loops = B5          ' counter for long delay

' -----[ Initialization ]-----
'
Init:  Pins = %00000000      ' LEDs off to start
      Dirs = %10001111      ' LEDs and Piezo outs

' -----[ Main Code ]-----
'
Main:  FOR cycle = 1 TO 4
      FOR stage = 0 TO 3
        LOOKUP stage, (%0001,%0010,%0100,%1000), Pins
        SOUND BprPin, (BprTone, BprLen)
        LOOKUP stage, (120,60,60,60), secs
        GOSUB DlySec
        NEXT ' stage
      NEXT ' cycle

Done:  Pins = %0000          ' LEDs off
      SOUND BprPin, (0,12,50,12,75,12,110,12) ' sound end

      END ' of program

' -----[ Subroutines ]-----
'
DlySec: FOR loops = 1 TO secs
      PAUSE 1000            ' pause 1 second
      PAUSE 10              ' quick pause for testing
    NEXT
  RETURN
```

```
' Stamp Applications - May 2000
' Listing 4

' -----[ Title ]-----
'
' File..... XTIMER2c.BAS
' Purpose... Exercise Timer - Version 2 - Final
' Author.... Jon Williams

' -----[ Program Description ]-----
'
' This program serves as a multi-stage exercise timer. The program runs
' four cycles of four stages, with an LED and audio indication for each
' stage.

' -----[ I/O Pins ]-----
'
SYMBOL BprPin = 7

' -----[ Constants ]-----
'
SYMBOL BprTone = 75
SYMBOL BprLen = 16          ' 0.192 secs

' -----[ Variables ]-----
'
SYMBOL cycle = B2           ' cycles counter
SYMBOL stage = B3           ' stage counter
SYMBOL secs= B4             ' stage timing (seconds)
SYMBOL loops = B5          ' counter for long delay

' -----[ Initialization ]-----
'
Init:  Pins = %00000000      ' LEDs off to start
      Dirs = %10001111      ' LEDs and Piezo outs

' -----[ Main Code ]-----
'
Main:  FOR cycle = 1 TO 4
      FOR stage = 0 TO 3
        LOOKUP stage, (%0001,%0010,%0100,%1000), Pins
        GOSUB Beep
        LOOKUP stage, (120,60,60,60), secs
        GOSUB DlySec
        NEXT ' stage
      NEXT ' cycle

Done:  Pins = %0000          ' LEDs off
      SOUND BprPin, (0,12,50,12,75,12,110,12) ' sound end

      END ' of program

' -----[ Subroutines ]-----
'
Beep:  BRANCH stage, (Beep1,Beep2,Beep3,Beep4)
Beep1: SOUND BprPin, (50,12)
      GOTO BeepX
Beep2: SOUND BprPin, (50,12,0,8,50,12)
      GOTO BeepX
Beep3: SOUND BprPin, (90,16)
      GOTO BeepX
Beep4: SOUND BprPin, (100,16,0,8,100,16)
BeepX: RETURN

DlySec: FOR loops = 1 TO secs
      PAUSE 1000            ' pause 1 second
      PAUSE 10              ' quick pause for testing
    NEXT
  RETURN
```


STAMP APPLICATIONS

Stamping Myself Into Better Shape

way this will work is by incrementing a counter whenever the switch is pressed. If the switch is released, the counter is cleared. When the counter reaches the threshold that indicates a valid switch press, some action will be taken.

By taking advantage of the Stamp's architecture and the fact that pins can be treated like variables, the switch variable updating or clearing can be done with one line of code. This works because a pin is a bit-sized variable and can have a value of zero

' Stamp Applications - May 2000
' Listing 5

```
' -----[ Title ]-----
'
' File..... XTIMER3.BAS
' Purpose... Exercise Timer - Version 3 - "Time Slicer"
' Author.... Jon Williams

' -----[ Program Description ]-----
'
' This program serves as a multi-stage exercise timer. The program runs
' four cycles of four stages, with an LED and audio indication for each
' stage.
'
' The timer includes a pause switch so that a stage can be interrupted and
' restarted. The timer begins in "Hold" mode. Pressing the Hold switch
' starts the timer

' -----[ I/O Pins ]-----
SYMBOL BprPin = 7          ' beeper pin
SYMBOL Swin = Pin6         ' Hold switch input

' -----[ Constants ]-----
SYMBOL LoopTm = 46         ' 1/20 second loop (tuned)
SYMBOL TixMax = 20         ' 20 x 50 ms = 1 second
SYMBOL SwMax = 5           ' switch debounce value

SYMBOL Up = 0              ' Hold switch released
SYMBOL Down = 1            ' Hold switch pressed

' -----[ Variables ]-----
SYMBOL cycle = B2          ' 4 cycles per workout
SYMBOL stage = B3          ' 4 stages per cycle
SYMBOL tix = B4            ' timing counter
SYMBOL secs = B5           ' stage seconds counter
SYMBOL sMax = B6           ' max time for stage
SYMBOL swch = B7           ' switch debounce

' -----[ Initialization ]-----
Init:  Pins = %00000001     ' light stage one at start
      Dirs = %10001111     ' LEDs and Piezo outs

      cycle = 0             ' first cycle
      stage = 0             ' first stage
      tix = 0               ' clear tix timer
      secs = 0              ' clear seconds

      GOTO OnHold          ' start in Hold mode
```

```
' -----[ Main Code ]-----
Main:  IF secs > 0 THEN Pad          ' beep only when secs and
      IF tix > 0 THEN Pad          ' tix are zero
      LOOKUP stage, (%0001,%0010,%0100,%1000), Pins ' stage LED
      GOSUB Beep
      LOOKUP stage, (120,60,60,60), sMax          ' get stage timing (secs)

Pad:    PAUSE LoopTm                ' pad the loop for timing

ChkSw:  switch = switch + Swin * Swin          ' check pause switch
      IF switch >= SwMax THEN OnHold          ' debounce; call Hold if
                                              ' held down

Test:   tix = tix + 1 // TixMax          ' increment with rollover
      IF tix > 0 THEN Main              ' still in same second
      secs = secs + 1 // sMax          ' increment seconds
      IF secs > 0 THEN Main              ' still in stage
      stage = stage + 1 // 4            ' increment stage
      IF stage > 0 THEN Main            ' still in cycle
      cycle = cycle + 1 // 4            ' increment cycle
      IF cycle > 0 THEN Main            ' still running

Done:   Pins = %0000                ' LEDs off
      SOUND BprPin, (0,12,50,12,75,12,110,12) ' sound end

      END ' of program

' -----[ Subroutines ]-----
Beep:   BRANCH stage, (Beep1,Beep2,Beep3,Beep4)
Beep1:  SOUND BprPin, (50,16)
      GOTO BeepX
Beep2:  SOUND BprPin, (50,16,0,8,50,16)
      GOTO BeepX
Beep3:  SOUND BprPin, (90,16)
      GOTO BeepX
Beep4:  SOUND BprPin, (90,16,0,8,90,16)
      GOTO BeepX
BeepX:  RETURN

OnHold: IF Swin = Down THEN OnHold          ' wait for release
      switch = 0                          ' clear switch check
      Dirs = %00000000                    ' turn off LED
      PAUSE 65
      Dirs = %10001111                    ' back on
      PAUSE 65
      switch = switch + Swin * Swin          ' check switch
      IF switch < 2 THEN Hold1              ' debounce
      switch = 0                          ' reset timers/counters
      tix = 0
      secs = 0
      GOTO Main
```



EPROM+

A device programming system for design, repair and field service

◆ EXCEPTIONAL POWER FOR THE PRO
◆ EASY-TO-USE FOR THE NOVICE

Here's what you get: A rugged, portable programming unit including the power pack and printer port cable both of which store inside the case. A real printed user and technical manual which includes schematic diagrams for the programming unit plus diagrams for all technology family adapters*. Comprehensive, easy-to-use software which is specifically designed to run under DOS, Windows 3.1, 95 and 98 on any speed machine. The software has features which let you READ, PROGRAM, COPY and COMPARE plus much more. You have full access to your system's disk including LOADING and SAVING chip data plus automatic processing of INTEL HEX, MOTOROLA S-RECORD and BINARY files. For detailed work the system software provides a full screen buffer editor including a comprehensive bit and byte tool kit with more than 20 functions.

Broad device support: Including FIRST GENERATION EPROMS (2708, TMS2716*, 25XX etc.) SECOND GENERATION EPROMS (2716-27C080)(8 MEG), 40 and 42 PIN EPROMS* (27C1024-27C160)(16 MEG) EEPROMS (2816-28C010) PLUS ER5901, FLASH EPROMS (28F, 29C, 29EE, 29F)(32 MEG), NVRAMS (12,20,X2210/12) 8 PIN SERIAL EEPROMS* (24, 25, 85, 93, 95, 80011A) PLUS ER1400/MS8657* BIPOLAR PROMS* (74S/82S), SERIAL FPGA CONFIGURATORS (17CXXX) MICROS* (874X, 875X, 87C5X, 87C75X, 89C) ATMEL MICROS*(89S, 90S(AVR)) PIC MICROS* 8, 18, 28, 40 PIN (12CXXX, 16C5X, 6X, 7X, 8X PLUS FLASH & 17C) MOTOROLA MICROS* (68705P3/U3/R3, 68HC705C8/C9/J2/P9, 68HC711E9/D3)

\$289

Includes step-by-step tutorial plus explanation of EPROM fundamentals
1 YEAR WARRANTY - 30 DAY MONEY BACK GUARANTEE
*REQUIRES SNAP-IN ADAPTER (ORDER FACTORY DIRECT OR BUILD YOURSELF)

\$5.00 SHIPPING = \$5.00 C.O.D.
VISA • MASTERCARD • AMEX

ANDROMEDA RESEARCH, P.O. BOX 222, MILFORD, OHIO 45150
(513) 831-9708 FAX (513) 831-7562
website - www.arlabs.com email - arlabs@worldnet.att.net MADE IN THE U.S.A.

Build Your Own Intelligent Robot, We Make It Easy!



At Lynxmotion we cater to the beginner. All of our kits are easy to assemble, requiring only common hand tools in the construction process. The detailed assembly manuals include 2D and 3D exploded view diagrams. The kits can be controlled or programmed in an easy to follow BASIC programming language. The technology is here, the costs are affordable, the support is available, join in and become a robot builder!

Lynxmotion, Inc.
104 Partridge Road
Pekin, IL 61554-1403
www.lynxmotion.com

Tel: 309-382-1816
Fax: 309-382-1254
sales@lynxmotion.com
tech@lynxmotion.com

Visit our website or ask for our free catalog!

STAMP APPLICATIONS

Stamping Myself Into Better Shape

or one. Our hardware design supports the code design by pulling the Hold pin low (value of zero) when the switch is released. Pressing the switch brings the pin up to five volts, which is read as one. So, when the switch is pressed, we will add one to our counter and then multiply by one (which has no effect on the counter). When the switch is released, we add zero (no change), but then multiply by zero, which immediately clears the counter. This trick saves a potentially tedious IF-THEN construct in the code.

The next line checks the switch value. If it reaches five (corresponding to 250-millisecond press; the reason our loop time is less than one second), the code will jump to the routine called "OnHold." This routine flashes the current stage LED by setting the Dirs register to inputs then back to outputs. The same switch monitoring and debouncing technique is used to release the timer from hold.

The final part of the loop is testing and updating the various timers and counters. Once again, we save code by taking advantage of Stamp math and by adopting zero-based counters. By using the Modulus (/) operator (remainder of a division) and counting from zero to our max value minus one, we considerably simplify the code. Any number MOD itself is zero. By using this technique, a value of zero indicates a rollover and the need to update our next level counter.

So you see that in the section called "Test," the counters are tested from the inside out. First, we check the tic counter. If it rolls over to zero, a second has elapsed; otherwise we go back to the main loop. The same process works for the seconds counter, the stage counter, and the cycles counter. When the cycle counter rolls over to zero, we've completed all four cycles and are done. I'm sure that you can see how easy it would be to synthesize a real-time clock using this technique to generate seconds, minutes, and

hours.

The last step is testing and fine-tuning. We'll find that with a "LoopTm" value of 50, the timer will run long. That shouldn't come as a surprise since we know that the code itself will take some time to run. Here's how to determine the final value for "LoopTm." Start a stopwatch and time the first stage. We get a value of about 129 seconds — nine seconds too long. If we take 120 (the desired time) and divide by 129 (tested time) we get 0.93. Now we multiply 0.93 by 50 (loop pad) and get 46.5. We'll round down to 46 for our "LoopTm" value. We run the stopwatch test again and find that it's dead on. Perfect — time to hit the jogging trail.

Even if this timer project is of no value to you, the technique used in the final program can be when you apply it to your projects. This timing technique, especially when combined with task-switching techniques, is terrific for Stamp-based robotics. Give it a try, because we will be using it more frequently in future articles. Until then, Happy Stamping. **NV**

Resources:

Jon Williams

3718 Valley View Lane, #3040
Irving, TX 75062
(972) 659-9090
jonwms@aol.com

Parallax

599 Menlo Drive, Suite 100
Rocklin, CA 95756
(888) 512-1024
www.parallaxinc.com

Scott Edwards Electronics, Inc.

1939 S. Frontage Rd. Ste. F
Sierra Vista, AZ 85635
phone 520-459-4802
fax 520-459-0623
www.seelron.com
info@seelron.com

Polaris can supply you with all of today's Hottest Video Technology, Micro Cameras to Professional Security Supplies

Color video camera
Power/Video cable
330 TV Lines
3.6mm Lens
LP-850c
\$179.95

Color & weatherproof
Power/Video cable
4.3mm Lens
WP-300c \$229.95

1" (Dia.) x 2.6" (L) w/o stand
Weather Proof
LP-850w
\$169.95

1.3" (Dia.) x 2.1" (L) w/o stand
Color 400 TV Lines
Power/Video cable
Lens: C-mount
Auto Iris
TC-300ux
\$229.95

1.3" (Dia.) x 1.8" (L) w/o stand
Built-In Infrared Illuminator, Camera can See in the Dark without Additional Light Source!
LP-850p \$119.95
LP-850l \$109.95

470 TV Lines Color "Micro-Zoom" Video Board Camera

470 TV Line Color Board Cameras, Technology has added high resolution to its smallest cameras. We've added a Vari-Focal lens to an already powerful board camera. The 4-8mm Vari-focal lens is a tool you won't be able to live without once you added this camera to your application.

MB-1250HRp \$149.95

• MB-1250HRVF \$199.95
470 Hi-Res Vari-Focal Color Camera
• MB-1250HRp \$149.95
470 Hi-Res Pinhole Color Camera
• MB-1250p \$99.95
350 Low-Res Pinhole Color Camera (not pictured)
MB-1250HRp & MB-1250p
Same physical look two resolution options to choose from: 470 or 350 TV lines.

Flat Screen TFT-LCD Monitors

TFT-4 \$209.95
Color 4" Screen.
(Size: 6"(W) x 4.5"(H) x 2"(D))
An excellent 4" monitor for one camera monitoring or for setting up cameras during installation or maintenance.

TFT-5.6 \$429.95
TFT-6.4 \$479.95
(Includes: patch cable & power supply)

Wireless Video

GW-2400S \$449.95
Includes: 2.4 Ghz. Color Wireless Camera, Receiver with Built-In Monitor.

GW-2400 \$229.95
• 1 - 4 Transmitting Channels.
• Can be integrated with other wireless applications.
• Up to 985 ft. Operating Distance.
• Dimensions: 2.5"(W) x 2.18"(H) x 3.28"(D)
Video/Stereo Audio

Free Polaris Video Catalog

CM-500CBC, A tough aluminum cased Color CMOS camera with mounting bracket, BNC video & barrel power connection for Plug & Play hook-up. View through standard VCR or Monitor!

- 1/3" Color CMOS
- 380 - TV Line
- 1 LUX
- Lens 3.6 mm
- Auto Iris

CM-500CBC \$129.95

CMOS C-Mount B/W & Color Cameras

CM-220
Color Camera: CM-220c
\$139.95


CM-220
B/W Camera: CM-220
\$69.95

The CM-220 & CM-220c are truly outstanding performance cameras with 380 Line Resolution & C-Mount options.

Polaris Industries
<http://www.polarisusa.com>

1-800-752-3571

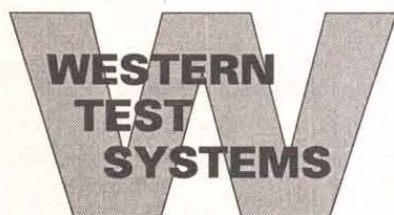470 Armour Drive NE • Atlanta GA 30324-3943 • Tech Info 404.872.0722 • FAX 404.872.1038



WE BUY AND SELL

Inquiries 307-635-2269 • Fax 307-635-2291

Orders 800-538-1493

2701 Westland Court, Unit B, Cheyenne, Wyoming 82001

OSCILLOSCOPES & ACCESSORIES

OSCILLOSCOPES

HP 54100D Dual Channel	\$875.00
1 GHz / 40 MS/s Digitizing Oscilloscope	
HP 54201D 300 MHz Logic Triggering Digitizing Oscilloscope	\$675.00
TEK 2445 150 MHz 4-channel Oscilloscope	\$950.00
TEK 2465 300 MHz 4-channel Oscilloscope	\$1,500.00
TEK 7104 1 GHz 2-Channel Oscilloscope	\$2,000.00

w/7A29,7A29-04,7B10,7B15	
TEK 7844 400 MHz Dual Beam Oscilloscope	\$750.00
with 7A24,7A26,7B80,7B85	
TEK 7904 500 MHz Oscilloscope	\$750.00
with 7A24, 7A26, 7B80, 7B85	

PROBES

HP 1122A Probe Power Supply	\$150.00
TEK 1101 Accessory Power Supply, for FET probes	\$175.00
TEK A6901 Ground Isolation Monitor	\$150.00
TEK A6902B Voltage Isolator, DC-20 MHz, 20 mV-500 V/div.	\$500.00
TEK P6046 100 MHz Differential Probe	\$400.00
TEK P6101A pair 1X 34 MHz Probe pair	\$50.00
10 Megohm/32pF, new in plastic	
TEK P6201 900 MHz 1X/10X/100X FET Probe	\$400.00
TEK P6202 500 MHz 10X FET Probe	\$150.00
TEK P6205 750 MHz 10X FET Probe, for TDS series	\$325.00
TEK P6701-opt.02 O/E Converter	\$175.00
450-1050 mV/0-1 mV: DC-700 MHz, ST conn.	

CALIBRATION

TEK 067-0587-02 Signal Standardizer Calibration Fixture	\$750.00
---	----------

WAVEFORM GENERATORS

FUNCTION

HP 3312A 13 MHz Function Generator	\$500.00
HP 3314A-001 Function Generator	\$1,200.00
0.001 Hz-19.99 MHz, 30 Vp-p, HP1B	
HP 3325A 21 MHz Synthesized Function Generator, HP1B	\$900.00
HP 3325A-002 21 MHz Synthesized Function Generator	\$1,200.00
HV output option	
TEK AWG5102 Arb. Waveform Gen.	\$650.00
20 MS/s, 12 bits, 50ppm synthesis <1MHz	
TEK AWG5105-opt.02 Arbitrary Waveform Generator	\$800.00
dual channel option	
TEK D0501 Digital Delay & Burst Gen.	\$200.00
for function & pulse gen's	
TEK FG5010 Programmable 20 MHz Function Generator	\$950.00
TM5000 series	
TEK FG502 11 MHz Function Generator, TM500 series	\$275.00
TEK FG503 3 MHz Function Generator, TM500 series	\$250.00
TEK RG501 Ramp Generator, TM500 series	\$175.00
WAVETEK 288 20 MHz Synthesized Function Generator, GPIB	\$650.00

PULSE

BERKELEY NUCLEONICS 7085B Digital Delay Generator	\$550.00
0-100 mS, 1 nS res., 5 Hz-5 MHz	
HP 8007B 100 MHz Pulse Generator	\$450.00
HP 8012B 50 MHz Pulse Generator, variable transition time	\$500.00
HP 8013B Dual Output 50 MHz Pulse Generator, 3.5 nS Tr	\$500.00
HP 8080A/81A/83A/84A 300 MHz Word Generator	\$850.00
HP 8080A/91A/92A/93A	\$800.00
1 GHz Single Channel Pulse Generator	
HP 8082A 250 MHz Pulse Generator	\$1,250.00
HP 8111A 20 MHz Pulse/Function Generator	\$1,100.00
TEK PG502 250 MHz Pulse Generator, Tr<1nS, TM500 series	\$600.00
TEK PG508 50 MHz Pulse Generator, TM500 series	\$350.00
WAVETEK 802 50 MHz Pulse Generator	\$250.00

VOLTAGE & CURRENT

VOLTMETERS

FLUKE 845AR High Impedance Voltmeter / Null Detector	\$400.00
HP 3456A 6-1/2 Digit Voltmeter, HP1B	\$450.00
HP 3457A 7-1/2 digit Voltmeter, HP1B	\$1,000.00
HP 3478A 1/2 digit Multimeter, HP1B	\$450.00
KEITHLEY 181 6-1/2 digit Nanovoltmeter	\$800.00
10 nV sensitivity, GPIB	
SOLARTRON 7081 8-1/2 digit Voltmeter	\$3,000.00
TEK DM5010 4-1/2 digit Multimeter, TM5000 series plug-in	\$300.00
TEK DM501A 4-1/2 digit Multimeter, TM500 series plug-in	\$225.00

CALIBRATION

FLUKE 510A AC Reference Standard, 10 VRMS, 0-10 mA	\$450.00
FLUKE 515A Portable Calibrator, DC/AC/Ohms	\$900.00
line & battery power	
FLUKE 5220A Transconductance Amplifier	\$2,500.00
DC-5 kHz, 0-20 A	

VOLTAGE SOURCES

HP 6115A Precision Dual Range Power Supply	\$750.00
50V 0.8A / 100V 0.4A	
KEITHLEY 228 Programmable Voltage/Current Source	\$1,900.00
TEK PSS00A Precision Programmable Power Supply	\$900.00
TM5000 series	

CURRENT METERS & SOURCES

HP 4114C Picoammeter / DC Voltage Source	\$1,500.00
without test fixture	
HP 6181C DC Current Source, to 100 V, 250 mA	\$500.00
HP 6186C DC Current Source, to 300 V, 100 mA	\$750.00

KEITHLEY 225 Current Source, 0.1 uA-100 mA	\$450.00
10-100 V compliance	
TEK CT-5 High Current Transformer for P6021/A6302	\$375.00
to 1000A	
TEK P6022 AC Current Probe w/termination	\$275.00
935 Hz-120 MHz, 6 A pk	

IMPEDANCE & COMPONENT TEST

L.C.R.

BOONTON 62AD 1 MHz Inductance Meter, 2-2000 uH	\$550.00
BOONTON 72BD 1 MHz Capacitance Meter, 3-1/2 digit display	\$650.00
BOONTON 72C 1 MHz Capacitance Meter, 1-3000 pF full scale	\$800.00
GR 1658 RLC DigiBridge, 120 Hz/ 1 kHz	\$1,000.00
GR 1659 RLC DigiBridge, 120 Hz/ 1 kHz	\$1,100.00
HP 4342A Q-Meter, 22 kHz-70 MHz	\$950.00

STANDARDS

E.S.I. SR-1 Standard Resistor, various values	\$125.00
E.S.I. SR1010 Resistance Transfer Standards	\$550.00
1 Ohm-100 K/step	
E.S.I. SR1050-1M Resistance Transfer Standard	\$2,000.00
1 Megohm/step	
GR 1404-A 1000 pF Reference Standard Capacitor	\$700.00
GR 1406 Standard Air Capacitors, GR900 connector	\$275.00
0.1% acc.	
GR 1432-U 4-Decade Resistor, 0-111.10 Ohms	\$100.00
0.01 Ohm resolution	
GR 1433-J 4-Decade Resistor, 0-11,110 Ohms	\$150.00
0.1 Ohm resolution	
GR 1433-K 4-Decade Resistor, 0-1,110 Ohms	\$150.00
0.1 Ohm resolution	
GR 1433-L 4-Decade Resistor, 0-111,100 Ohms	\$150.00
10 Ohms resolution	
GR 1433-X 6-Decade Resistor, to 111,111.0 Ohms	\$250.00
0.1 Ohm res.	
HP 4440B 4-Decade Capacitor, 40 pF-1.2 uF	\$750.00

T.D.R.

TEK 1503B-03.04 T.D.R., 0-50,000 ft.,	\$3,000.00
chart recorder & battery power	
TEK 1503-opt.04 Time Domain Reflectometer,	\$1,400.00
0-50,000 feet, chart recorder	

POWER SUPPLIES

SINGLE OUTPUT

HP 6110A 0-300V 0-6 mA CV/CL Power Supply	\$250.00
HP 6200B Dual Range Supply	\$200.00
0-20 V 0-1.5 A / 0-40 V 0-750 mA CVCC	
HP 6207B 0-160 V 0-200 mA CV/CC Power Supply	\$200.00
HP 6215A 0-25 V 0-400 mA CV/CL Power Supply	\$100.00
HP 6256B 0-10 V 0-20 A CV/CC Power Supply	\$200.00
HP 6263B 0-20 V 0-10 A CV/CC Power Supply	\$400.00
HP 6266B 0-40 V 0-5 A CV/CC Power Supply	\$550.00
HP 6267B 0-40 V 0-10 A CV/CC Power Supply	\$550.00
HP 6271B 0-60 V 0-3 A CV/CC Power Supply	\$375.00
HP 6274B 0-60 V 0-15 A CV/CC Power Supply	\$650.00
HP 6282A 0-10 V 0-10 A CV/CC Power Supply	\$200.00
HP 6289A 0-40 V 0-1.5 A CV/CC Power Supply	\$200.00
HP 6299A 0-100 V 0-750 mA CV/CC Power Supply	\$200.00
HP 6384A 4.0-5.5 V at 8 A CV/CL Power Supply	\$125.00
HP 6443B 0-120 V 0-2.5 A CV/CC Power Supply	\$450.00
HP 6632A System DC Power Supply	\$800.00
0-20 V, 0-5 A, 100 Watts, HP1B	
HP 6652A 0-20 V 0-25 A 500 Watt Programmable	\$1,875.00
Power Supply, HP1B	
KEPCO ATE 36-30M 0-36 V 0-30 A CV/CC Power Supply	\$900.00
KEPCO ATE 36-8M 0-36 V 0-8 A CV/CC Power Supply	\$375.00
LAMBDA LK-352-FM 0-60 V 0-15 A CV/CC Power Supply	\$600.00
SORENSEN DCR 150-3B 0-150 V 0-3 A CV/CC Power Supply	\$500.00
SORENSEN DCR 600-75B 0-600 V 0-750 mA	\$550.00
CV/CC Power Supply	
SORENSEN DCS 40-25 0-40 V 0-25 A CV/CC Power Supply	\$650.00
SORENSEN SRL 20-12 0-20 V 0-12 A CV/CC Power Supply	\$350.00
SORENSEN SRL 60-8 0-60 V 0-8 A CV/CC Power Supply	\$500.00
TEK PS501-1 Power Supply, 0-20 V, 2 mV res., 400 mA	\$175.00
TM500 series	

MULTIPLE OUTPUT

HP 6205C Dual Power Supply	\$300.00
0-40 V 300 mA & 0-20 V 600 mA, CV/CL	
HP 6228B Dual 0-50 V 0-1 A CV/CC Power Supply	\$375.00
HP 6236B Triple Output Power Supply, 0-20V 0.5A & 0-6V 2.5A	\$375.00
HP 6253A Dual 0-20 V 0-3 A CV/CC Power Supply	\$375.00
HP 6255A Dual 0-40 V 0-1.5 A CV/CC Power Supply	\$375.00
KEPCO MPS-620M Triple Output Supply	\$200.00
dual 0-20V 1A tracking & 0-6V 5A	
LAMBDA LPT-7202-FM Triple Output Power Supply	\$450.00
TEK PS5010 Programmable Triple Power Supply	\$450.00
TM5000 series	
TEK PS503A Dual Power Supply, TM500 series	\$200.00

MISCELLANEOUS

ACME PS2L-500 Programmable Load	\$350.00
0-75 V / 0-75 A / 500 Watts max.	
BEHLMAN 25-C-DIOSCD-1 AC Power Source	\$850.00
250 VA, 0-130 VAC, 45-2000 Hz	
HP 59501B HP1B Isolated DAC/Power Supply Programmer	\$175.00

HP 6060A 300 Watt Programmable Load	\$950.00
0-60 A / 3-60 V, HP1B	
KEPCO BOP 20-20M Bipolar Op Amp/Power Supply	\$675.00
to 20 V 20 A	
KEPCO BOP 50-2M Bipolar Op Amp/Power Supply	\$400.00
to 50 V 2 A	
TRANSISTOR DEVICES DAL-50-15-100 Programmable Load	\$200.00
0-50 V, 0-15 A, 100 Watts max.	

TIME & FREQUENCY

UNIVERSAL COUNTERS

HP 5314A-001 100 MHz/100 nS Universal Counter	\$250.00
TCXO reference option	
HP 5315A 100 MHz/100 nS Universal Counter	\$350.00
HP 5315A-001 100 MHz / 100 nS Universal Counter	\$400.00
TCXO reference	
HP 5315A-002,003 100 MHz/100 nS Univ. Counter	\$550.00
batt. power & 1 GHz C-ch.	
HP 5315A-003 100 MHz/100 nS Univ. Counter	\$450.00
1 GHz C-channel option	
HP 5315B 100 MHz/100 nS Universal Counter	\$375.00
HP 5316A 100 MHz/100 nS Universal Counter, HP1B	\$450.00
HP 5316A-001,003 100 MHz/100 nS Univ. Counter	\$600.00
HP1B, TCXO, 1 GHz C-ch.	
HP 5316B 100 MHz/100 nS Universal Counter, HP1B	\$550.00
HP 5335A-10,30,40 200 MHz/2 nS Universal Counter	\$950.00
OCXO ref., 1.3 GHz C-ch	
HP 5370B 100 MHz/20 pS Universal Counter, 11 digits	\$1,200.00
PHILIPS PM672/411 120 MHz/100 nS Universal Counter	\$375.00
C-channel 70-1000 MHz	
TEK DC5004 Programmable 100 MHz/100nS Counter/Timer	\$200.00
TM5000 series	
TEK DC5009 Programmable 135 MHz Univ. Counter/Timer	\$350.00
TM5000 series	
TEK DC5010 350 MHz / 3.125 nS Universal Counter	\$750.00
TM5000 series	
TEK DC503A 125 MHz/100 nS Universal Counter	\$275.00
TM500 series	
TEK DC509 135 MHz/10 nS Universal Counter, TM500 series	\$275.00

FREQUENCY COUNTERS

EIP 545A 18 GHz Frequency Counter	\$750.00
FLUKE 7220A-010,131,351 1.3 GHz Counter	\$500.00
battery power, OCXO, and res. mult.	
HP 5342A 18 GHz Frequency Counter	\$1,000.00
HP 5343A-opt.01 26.5 GHz Frequency Counter	\$3,000.00
OCXO reference	
HP 5343A-001,011 26.5 GHz Frequency Counter	\$3,500.00
OCXO reference, HP1B	
HP 5345A/5355A/5356B	\$3,500.00
26.5 GHz CW/Pulse Frequency Counter	
HP 5364A Microwave Mixer / Detector	\$2,000.00
for modulation domain an.	
MISCELLANEOUS	
HP 105B Quartz Oscillator, 0.1/ 1.0/ 5.0 MHz, battery power	\$1,100.00
HP 5087A-opt.032 Distribution Amplifier	\$1,750.00
12 outputs at 5 MHz	

AUDIO & BASEBAND

SPECTRUM ANALYSIS

HP 3586C Selective Level Meter	\$1,200.00
50 Hz-32.5 MHz, 50 & 75 ohms	

DISTORTION ANALYZERS

HP 8903A Audio Analyzer, 20 Hz-100 kHz	\$1,200.00
HP 8903B-001 Audio Analyzer	\$1,650.00
20 Hz-100 kHz; rear input option	

RMS VOLTMETERS

FLUKE 8922A True RMS Voltmeter	\$450.00
180 uV-700 V, 2 Hz-11 MHz	

OSCILLATORS

HP 3336C-004,005 21 MHz Synthesizer/ Level Gen.	\$1,400.00
OCXO & hi accuracy att.	
TEK SG502 Sine/Square Osc.	\$200.00
5 Hz-500 kHz, 70 dB step atten., TM500	

MISCELLANEOUS

HP 3575A Phase-Gain Meter, 1 Hz-13 MHz, single display	\$650.00
HP 3575A-001 Phase-Gain Meter, 1 Hz-13 MHz, dual display	\$850.00
HP 461A Amplifier, 20 dB or 40 dB gain, 1 kHz-150 MHz	\$125.00
HP 467A Power Amplifier	\$375.00
X1/X2/X5/X10, DC-1 MHz, 10 W output	
KROHN-HITE 3103 High/Low Pass Filter	\$350.00
10 Hz-3 MHz, 24 dB/octave	
KROHN-HITE 3200 High Pass / Low Pass Filter	\$275.00
20 Hz-2 MHz, 24 dB/octave	
KROHN-HITE 3202 Dual HP/LP/BR Filter	\$450.00
20 Hz-2 MHz, 24 dB/octave	
KROHN-HITE 3342R Dual HP/LP Filter	\$900.00
0.001 Hz-99.9 kHz, 48 dB/octave	
ROCKLAND 852 Dual Highpass/Lowpass Filter	\$650.00
0.1 Hz-111 kHz	
TEK AM502 Differential Amplifier	\$475.00
0.1 Hz-1 MHz, TM500 series	
WAVETEK 716 Brickwall Filter	\$1,500.00



90 DAY WARRANTY PARTS AND LABOR • 10 DAY INSPECTION TEST EQUIPMENT WANTED CALL OR FAX LIST • OPEN ACCOUNTS



RF & MICROWAVE

SPECTRUM ANALYZERS

HP 11517A/18A/19A/20A Mixer Set, 12.4-40.0 GHz, for HP 8555A/8569A	\$500.00
HP 11970A WR28 Harmonic Mixer, 26.5-40 GHz	\$1,100.00
HP 11970K WR42 Harmonic Mixer, 18.0-26.5 GHz	\$1,100.00
HP 11970Q WR22 Harmonic Mixer, 33-50 GHz	\$1,400.00
HP 11971A WR28 Harmonic Mixer, for HP 8569B	\$800.00
HP 11971K WR42 Harmonic Mixer, for HP 8569B	\$800.00
HP 70620B Preamp, 1.0-26.5 GHz, for 7000 series	\$3,900.00
HP 8559A/853A-001 Spectrum An., 0.01-21 GHz, 1 kHz res., w/rackmount frame	\$3,750.00
HP 85640A Tracking Generator, 300 kHz-2.9 GHz, for HP 8560 series	\$5,000.00
HP 8568B Spectrum Analyzer, 100 Hz-1.5 GHz, 10 Hz min. res.	\$8,500.00
HP 8569B Spectrum Analyzer, 10 MHz-22 GHz, 100 Hz min. res. bw.	\$5,500.00
TEK WM782V WR15 Harmonic Mixer, 50-75 GHz	\$1,500.00

NETWORK ANALYZERS

HP 11650A Network Analyzer Accessory Kit, APC7	\$600.00
HP 11665B Modulator, 0.15-18 GHz, for HP 8755/87	\$250.00
HP 85054A Type N Calibration Kit, for HP 8510 series	\$1,800.00
HP 85062A WR28 Detector, 26.5-40 GHz, for HP 8757 series	\$1,200.00

SIGNAL GENERATORS

FLUKE 6060A Synthesized Signal Gen., 0.1-1050 MHz, 10 Hz res., GPIB	\$1,650.00
FLUKE 6060A/AN Synthesized Signal Generator, 10 kHz-520 MHz, 10 Hz res.	\$950.00
FLUKE 6060B/AB Synthesized Signal Gen., 0.1-1050 MHz, 10 Hz res.	\$1,900.00
GIGATRONICS 600/6-12 Synthesized Source, 6-12 GHz, 1 kHz res., GPIB	\$2,500.00
GIGATRONICS 875/50 Levelled Multiplier, x4, 50.0-75.0 GHz output, -3 dBm	\$2,500.00
GIGATRONICS 900/2-8 Synthesized Signal/Sweep Gen., 2-8 GHz, 1 MHz res., GPIB	\$2,500.00
GIGATRONICS GT9000-opt.26A Synthesized Signal Gen., 0.01-20 GHz, 1 kHz res.	\$6,000.00
HP 11707A Test Plug-In for HP 8660 series	\$500.00
HP 11720A Pulse Modulator, 2-18 GHz, 80 dB on/off ratio	\$450.00
HP 3335A Synthesizer/Level Gen., 200 Hz-81 MHz, -87 to dBm	\$3,000.00
HP 85100V Frequency Mult., 10-15 GHz in / 50-75 GHz out >0 dBm	\$3,750.00
HP 8640B Signal Generator, 0.5-512 MHz, AM, FM, pulse modulation	\$950.00
HP 8656A-001 Signal Generator, 0.1-990 MHz, 100 Hz res., HP1B, OCXO	\$1,600.00
HP 8657A-002 Signal Generator, 0.1-1040 MHz, 10 Hz res., HP1B	\$2,750.00
HP 8660C/8660A/8663B Synth. Sig. Gen., 1-1300 MHz, AM / FM	\$2,500.00
HP 8660C/8660A/8663B Synthesizer, 1-2600 MHz, 1 Hz res., AM / FM	\$3,250.00
HP 8672A Synthesized Signal Generator, 2-18 GHz, dBm output	\$5,000.00
HP 8684B Signal Generator, 5.4-12.5 GHz, AM/ WBW/ Pulse	\$3,000.00

SWEEP GENERATORS

HP 8340B Synthesized Sweep Generator, 10 MHz-26.5 GHz, AM, FM	\$20,000.00
HP 8350A/8350A-002.004 Sweep Oscillator, 2.0-8.4 GHz, 70 dB step attenuator	\$4,000.00
HP 8350A/8350A-002 Sweep Oscillator, 5.9-12.4 GHz, 70 dB step attenuator	\$4,000.00
HP 8350B/83522A Sweep Oscillator, 10-2400 MHz, dBm levelled	\$4,000.00
HP 8601A Generator/Sweeper, 0.1-110 MHz, dBm levelled	\$400.00
HP 8620C Sweep Oscillator Frame	\$550.00
HP 86222A RF Plug-In, 10-2400 MHz, dBm levelled	\$1,200.00
HP 86222A-E69/8620C Sweep Oscillator w/RF Plug-In, 10-4000 MHz, dBm out	\$1,500.00
HP 86230B RF Plug-In, 1.8-4.2 GHz, dBm unlevelled	\$375.00
HP 86241A-001 RF Plug-In, 3.2-8.5 GHz, dBm levelled	\$300.00
HP 86260A-H04 RF Plug-In, 10.0-15.0 GHz, dBm unlevelled	\$500.00
HP 86290A-004 RF Plug-In, 2.0-18.0 GHz, dBm levelled output	\$1,250.00
WAVETEK 962 Sweep Generator, 1.0-4.0 GHz, markers, dBm unlvld.	\$1,250.00

POWER METERS

BOONTON 428/41-4E Analog Power Meter, with 1 MHz-18 GHz sensor	\$450.00
HP 432A/478A Power Meter, -30 to dBm, 10 MHz-10 GHz	\$300.00
HP 435B/481A Power Meter, -30 to dBm, 10 MHz-18 GHz	\$900.00
HP 435B/482B Power Meter, 0 to dBm, 100 kHz-4.2 GHz	\$1,500.00
HP 435B/482H Power Meter, -10 to dBm, 100 kHz-4.2 GHz	\$900.00
HP 436A-022/481A Power Meter, -30 to dBm, 10 MHz-18 GHz, HP1B	\$1,200.00
HP 436A-022/484A Power Meter, -70 to -20 dBm, 10 MHz-18 GHz, HP1B	\$1,200.00
HP 8477A Power Meter Calibrator, for HP 432 series	\$500.00
HP Q8486A Power Sensor, 33.0-50.0 GHz, WR22, for 435/67/8	\$1,500.00
HP R8486A WR28 Power Sensor, 26.5-40 GHz, for HP 435/67/8	\$1,500.00

RF MILLIVOLTMETERS

RACAL-DANA 9303 RF Millivoltmeter, 10 kHz-2 GHz, -70 to dBm	\$750.00
---	----------

AMPLIFIERS, MISCELLANEOUS

AMPLIFIER RESEARCH 4W1000 Amplifier, 40 dB gain, 4 Watts, 1-1000 MHz	\$950.00
HP 11729B-003 Carrier Noise Test Set, 5 MHz-3.2 GHz	\$2,250.00
HP 415E SWR Meter	\$200.00
HP 8406A Comb Generator, 1/10/100 MHz increments, to 5 GHz	\$500.00
HP 8447A Amplifier, 20 dB, 0.1-400 MHz, 5 dB NF, dBm output	\$375.00
HP 8447E Amplifier, 22 dB, 0.1-1300 MHz, dBm output	\$750.00
HP 8901A Modulation Analyzer, 150 kHz-1300 MHz	\$1,750.00
HP 8901B-1.2.3 Modulation An., 0.15-1300 MHz, rear input, OCXO, ext. LO	\$2,250.00
HP 8970A Noise Figure Meter	\$4,000.00
HUGHES 1177H10F000 TWT Amplifier, >30 dB gain, 1.4-2.4 GHz, 20 Watts	\$2,500.00
HUGHES 8010H13F000 TWT Amplifier, >30 dB gain, 3-8 GHz, 10 Watts	\$2,500.00
HUGHES 8020H10F000 TWT Amplifier, >30 dB gain, 2-4 GHz, 20 Watts	\$4,250.00
RF POWER LABS ML50 Amplifier, 2-30 MHz, 47 dB gain, 50 Watts, metered, 28V	\$350.00
ROHDE & SCHWARTZ ESH2 Test Receiver, 9 kHz-30 MHz	\$3,750.00

COAXIAL & WAVEGUIDE

AEROWAVE 28-3000/10 WR28 Directional Coupler, 10 dB, 26.5-40 GHz	\$300.00
AMERICAN NUCLEONICS AM-432 Cavity Backed Spiral Antenna, LHC, 2-18 GHz, TNC(f) "NEW"	\$95.00
AVANTEK AMT-400X2 WR28 Active Doubler, dBm in/ dBm out 26-40 GHz	\$450.00
BIRD 6735-300 1 kW Load, 25-1000 MHz, LC(f), with wattmeter	\$650.00
BIRD 8201 500 Watt Oil Dielectric Load, DC-2.5 GHz, N(f)	\$350.00
BIRD 8251 1 kW Oil Dielectric Load, DC-2.4 GHz, N(f)	\$500.00
BIRD 8325-30 30 dB Attenuator, 500 Watts, DC-500 MHz	\$400.00
FXR/MICROLAB S3-02N Triple Stub Tuner, 200-1000 MHz, 100 Watts max., N(mf)	\$125.00
FXR/MICROLAB SL-03N Stub Tuner, 0.3-6.0 GHz, 100 Watts max., N(mf)	\$75.00
GR 874-LTL Constant Impedance Trombone Line, 0-44 cm, DC-2 GHz	\$400.00
HP 11590A-001 Bias Network, 1.0-18 GHz, APC7	\$450.00
HP 11636A 2-Way Power Divider, DC-18 GHz, N(mf)	\$300.00
HP 11692D Dual Directional Coupler, 22 dB, 2-18 GHz	\$800.00
HP 33321K Programmable Step Attenuator, 0-70 dB, DC-26.5 GHz, 3.5mm	\$475.00
HP 33327L-006 Programmable Step Attenuator, 0-70 dB, DC-40 GHz, 2.9mm	\$1,000.00
HP 7740 Dual Directional Coupler, 20 dB, 215-450 MHz	\$275.00
HP 7760 Dual Directional Coupler, 20 dB, 940-1900 MHz	\$275.00
HP 7770 Dual Directional Coupler, 20 dB, 1.9-4.1 GHz	\$275.00
HP 7780-011 Dual Dir. Coupler, 20 dB, 100-2000 MHz, APC7 test port	\$450.00
HP 83017A Amplifier, 25 dB gain, 0.5-26.5 GHz, > dBm	\$3,250.00
HP 8431A 2-4 GHz Band Pass Filter, N(mf)	\$150.00
HP 8472B Crystal Detector, 10 MHz-18 GHz, negative polarity, SMA	\$225.00
HP 8494G-002 Programmable Step Attenuator, 0-11 dB, DC-4 GHz, SMA	\$350.00
HP 8495H-001 Programmable Step Attenuator, 0-70 dB, DC-18 GHz, N	\$400.00
HP 8496A-002 Step Attenuator, 0-110 dB, DC-4 GHz, SMA	\$375.00
HP 8497K-004 Programmable Step Attenuator, 0-90 dB, DC-26.5 GHz	\$750.00
HP K382A WR42 Direct Reading Attenuator, 0-50 dB, 18.0-26.5 GHz	\$2,750.00
HP K422A WR42 Flat Broadband Detector, 18.0-26.5 GHz	\$350.00
HP K532A WR42 Frequency Meter, 18.0-26.5 GHz	\$450.00
HP K752C WR42 Directional Coupler, 10 dB, 18.0-26.5 GHz	\$450.00
HP K752D WR42 Directional Coupler, 20 dB, 18.0-26.5 GHz	\$450.00
HP K870A WR42 Slide Screw Tuner, 18.0-26.5 GHz	\$275.00
HP K914B WR42 Moving Load, 18.0-26.5 GHz	\$300.00
HP Q752D WR22 Directional Coupler, 20 dB, 33-50 GHz	\$650.00
HP R382A WR28 Direct Reading Attenuator, 0-50 dB, 26.5-40 GHz	\$2,250.00
HP R422A WR28 Crystal Detector, 26.5-40 GHz	\$400.00
HP R752D WR28 Directional Coupler, 20 dB, 26.5-40 GHz	\$450.00
HP R914B WR28 Moving Load, 26.5-40 GHz	\$250.00
HP V365A WR15 Isolator, 25 dB, 50-75 GHz	\$750.00
HP V752D WR15 Directional Coupler, 20 dB, 50-75 GHz	\$650.00
HP X870A WR90 Slide Screw Tuner	\$150.00
HUGHES 45712H-1000 WR22 Frequency Meter, 33-50 GHz	\$900.00
HUGHES 45714H-1000 WR15 Frequency Meter, 50-75 GHz	\$900.00
HUGHES 45721H-2000 WR28 Direct Reading Attenuator, 0-50 dB, 26.5-40 GHz	\$1,000.00
HUGHES 45722H-1000 WR22 Direct Reading Attenuator, 0-50 dB, 33-50 GHz	\$1,000.00
HUGHES 45724H-1000 WR15 Direct Reading Attenuator, 0-50 dB, 50-75 GHz	\$1,000.00
HUGHES 45732H-1200 WR22 Level Set Attenuator, 0-25 dB, 33-50 GHz	\$250.00
HUGHES 45727H-1100 WR22 Thermistor Mount, -20 to dBm, 33-50 GHz	\$400.00
HUGHES 45773H-1100 WR19 Thermistor Mount, -20 to dBm, 40-60 GHz	\$650.00
HUGHES 45774H-1100 WR15 Thermistor Mount, -20 to dBm, 50-75 GHz	\$750.00
HUGHES 45776H-1100 WR10 Thermistor Mount, -20 to dBm, 89-99 GHz	\$700.00
HUGHES 47316H-1111 WR10 Tuneable Detector, 75-110 GHz, positive polarity	\$600.00

HUGHES 47741H-2310 WR28 Phase Locked Gunn Osc., 32.000 GHz, dBm	\$2,000.00
HUGHES 47742H-1210 WR22 Phase Locked Gunn Osc., 42.000 GHz, dBm	\$2,750.00
HUGHES 47974H-1000 WR15 SPST PIN Switch, 250 MHz speed, 60-82 GHz response	\$375.00
KRYTAR 201020010 Directional Detector, 1-20 GHz, SMA(f)/SMC	\$200.00
KRYTAR 2616S Directional Detector, 1.7-26.5 GHz, K(l/m)/SMC	\$200.00
M/A-COM 3-19-300/10 WR19 Directional Coupler, 10 dB, 40-60 GHz	\$450.00
MICA C-121S06 Circulator, 17.5-24.5 GHz, SMA(f)/m/m	\$75.00
MINI-CIRCUITS ZFDC-20-4 Directional Coupler, 19.5 dB, 1-1000 MHz, SMA(f)	\$25.00
NARDA 3000-SERIES Directional Couplers	\$150.00
NARDA 3020A Bi-Directional Coupler, 50-1000 MHz, N	\$475.00
NARDA 3024 Bi-Directional Coupler, 20 dB, 4-8 GHz	\$375.00
NARDA 3090-SERIES Precision High Directivity Couplers	\$225.00
NARDA 3688NM Coaxial High Power Load, 500 Watts, 2.0-18 GHz, N(m)	\$500.00
NARDA 3752 Coaxial Phase Shifter, 0-180 deg./GHz, 1-5 GHz	\$1,000.00
NARDA 3753B Coaxial Phase Shifter, 0-55 deg./GHz, 3.5-12.4 GHz	\$1,000.00
NARDA 4000-SERIES SMA Miniature Directional Couplers	\$75.00
NARDA 4226-10 Directional Coupler, 10 dB, 0.5-18.0 GHz, SMA(f)	\$275.00
NARDA 4227-16 Directional Coupler, 16 dB, 1.7-26.5 GHz, 3.5mm(f)	\$325.00
NARDA 4242-20 Directional Coupler, 20 dB, 0.5-2.0 GHz, SMA(f)	\$100.00
NARDA 4247-20 Directional Coupler, 20 dB, 6.0-26.5 GHz, 3.5mm(f)	\$200.00
NARDA 4247B-10 Directional Coupler, 10 dB, 0.6-26.5 GHz, 3.5mm(f)	\$200.00
NARDA 5070-SERIES Precision Reflectorometer Couplers	\$300.00
NARDA 562 DC Block, 10 MHz-12.4 GHz, 100 V max., N(mf)	\$65.00
NARDA 765-10 10 dB Attenuator, 50 Watts, DC-5 GHz, N(mf)	\$165.00
NARDA 7916F Variable Attenuator, 0-37 dB, 2.0-12.4 GHz	\$600.00
NARDA 792FF Variable Attenuator, 0-20 dB, 2.0-12.4 GHz	\$375.00
NARDA 794FM Direct Reading Variable Attenuator, 0-40 dB, 4-8 GHz	\$375.00
OMNI-SPECTRA 2085-6010-00 Crystal Detector, 1-18 GHz, negative polarity, SMA(mf)	\$50.00
PAMTECH KYG1014 WR42 Junction Circulator, 18.0-26.5 GHz	\$250.00
SONOMA SCIENTIFIC 21A3 WR42 Circulator, 20 dB, 20.6-24.8 GHz	\$75.00
TEKTRONIX 2701 Step Attenuator, 0-79 dB, DC-1 GHz, AC or DC coupled	\$175.00
TRG B510 WR22 Direct Reading Attenuator, 0-50 dB, 33-50 GHz	\$1,000.00
TRG V551 WR15 Frequency Meter, 50-75 GHz	\$600.00
TRG W551 WR10 Frequency Meter, 75-110 GHz	\$750.00
WAVELINE 100080 WR28 Terminated Crossguide Coupler, 30 dB	\$200.00
WEINSCHTEL 150-110 Programmable Step Attenuator, 0-110 dB, DC-18 GHz, SMA	\$450.00
WEINSCHTEL DS109 Double Stub Tuner, 1-13 GHz, N(mf)	\$150.00
WEINSCHTEL DS109LL Double Stub Tuner, 0.2-2.0 GHz, N(mf)	\$150.00

COMMUNICATIONS

HP 3780A-001 Pattern Generator / Error Detector, 1 kbit/s - 50 Mbit/s	\$1,000.00
HP 4935A Transmission Impairment Measuring Set	\$600.00
HP 59401A HP1B Bus Analyzer	\$375.00
MICRODYNE 1200MR 215-320 MHz Telemetry Receiver, PSK demodulation	\$600.00
TEK 1410R NTSC Gen., w/SPG2 sync. generator, TSG7 color bars	\$800.00
TEK 1411R PAL Gen., w/SPG12 sync./TSG11 color bars/TSG13 linearity	\$750.00
TEK 1411R PAL Test Gen., w/SPG12, TSG11, TSG13, TSG15, TSG16	\$1,000.00
TEK 1411R PAL Test Gen., w/SPG12, TSG11, TSG13, TSG15, TSG16	\$1,100.00
TEK 1411R-opt.04 PAL Test Gen., w/SPG12, TSG11, TSG13, TSG15, TSG16	\$1,400.00
TEK 147A NTSC Test Signal Generator, with noise test signal	\$800.00
TEK 148 PAL Insertion Test Signal Generator	\$700.00
TEK 520A NTSC Vectorscope	\$750.00
TEK 521A PAL Vectorscope	\$750.00

MISCELLANEOUS

FLUKE 2180A RTD Digital Thermometer	\$500.00
HP 7090A Measurement Plotting System	\$1,200.00
P.A.R. 5206-95 98 Two-Phase Lock-in Amp., 2 Hz-100 kHz, GPIB	\$1,500.00
TEK TM5003 5000-series 3-slot Programmable Power Module	\$450.00
TEK TM5006 5000-series 6-slot Programmable Power Module	\$500.00
TEK TM504 500-series 4-slot Power Module	\$175.00
TEK TM506 500-series 6-slot Power Module	\$250.00
TEK TM515 500-series 5-slot Traveller Power Module	\$250.00

Events

MAY 2000

MAY 5-6

LA - BATON ROUGE - State Convention. Baker Civic Auditorium, 3325 Groom Rd. VE Testing. Baton Rouge ARC, Herb Ramey W5LSU, 225-654-6087. E-Mail: W5GIX@AOL.COM
Web: <http://www.brarc.org>

MAY 6

AR - SILOAM SPRINGS - Hamfest. St. Mary's Catholic Church, 1996 Hwy. 412 E. 8am-3pm. Talk-in: 146.67. Siloam Springs ARC, Matt Hyde N5UYK, 501-524-4797. E-Mail: kengelke@cox-internet.com

AZ - SIERRA VISTA - Hamfest. Cochise ARA, Raymond Berger W1LYT, 520-378-4214

CANADA - OTTAWA - Hamfest. Ottawa Valley Mobile Radio Club, John J. Barnhardt VE3ZOV, 613-521-8910. E-Mail: ve3zov@rac.ca Web: <http://www.ovmrc.on.ca>

CO - MONUMENT - Hamfest. Lewis-Palmer High School, 1300 Higby Rd. 8am-2pm. Talk-in: 146.970 (100Hz) or 146.520 simplex. Pikes Peak RAA, Robert Ryals K10GF, 719-265-9950. E-Mail: rryals@pcisys.net

Web: <http://www.qsl.net/ppraa/swapfest.htm>

KY - LOUISA - Hamfest. Louisa Middle School. Talk-in: 147.390+ repeater. Big Sandy ARC, Fred Jones WA4SWF, 606-638-9049. E-Mail: wa4swf@arrl.net Web: <http://qsl.net/wa4swf/>

MD - GRASONVILLE - Hamfest. Kent Island & Anne Arundel ARCs, Ray Allen W2KBR, 410-969-8042. E-Mail: w2kbr@arrl.net

MI - CADILLAC - Hamfest. Wexauke ARC, Alton McConnell N08L, 231-862-3774. E-Mail: amcconnell3@hotmail.com

NY - OWEGO - Hamfest. Tioga County's Marvin Park Fairgrounds. Talk-in: 146.76. BARA, Bill Coleman N2BC, 607-748-5232. E-Mail: rmess@binghamton.edu

Web: <http://www.wtsn.binghamton.edu/bara>

OR - EUGENE - Hamfest. Up The Crick Radio Club, Karl Fuller K7ARL, 541-942-1624

WI - CEDARBURG - Hamfest. Ozaukee RC, Joe Holly AA9HR, 262-377-2137. E-Mail: aa9hr@excpc.com. Skip Douglas, 262-284-3271

WI - SUPERIOR - Hamfest. Arrowhead RAC, Jim Nielson KB9RQD, 715-392-3697. E-Mail: jnielson@bresnanlink.net

MAY 6-7

AL - BIRMINGHAM - Hamfest. Glenn Glass KE4YZK, 205-681-5019. E-Mail: ke4yzk@bellsouth.net Web: <http://www.bro.net/barc/fest.htm>

NJ - EDISON - Trenton Computer Festival. NJ Convention & Exposition Center, Raritan Center. KGP Productions, Inc., 1-800-631-0062. E-Mail: kgp@mail.com Web: <http://pcshow.com>

TX - ABILENE - Hamfest. Abilene Civic Center. Sat: 8am-5pm, Sun: 9am-2pm. VE Testing. Talk-in: 146.160/760. The Key City ARC, Peg Richard KA4UPA, 915-672-8889. E-Mail: ka4upa@arrl.net

MAY 7

FL - ST. PETERSBURG - Hamfest. St. Petersburg ARC, Gerald Dee Turner N2MNC, 727-548-7474. E-Mail: n2mnc@netzero.net

IL - SANDWICH - Hamfest. Sandwich Fairgrounds. 8am-2pm. Talk-in: 146.730 or 146.52 simplex. Kishwaukee ARC, Bob Yurs W9ICU, 815-895-3219. E-Mail: w9icu@tbcnet.com Web: <http://www.tbcnet.com/~jeonard/hamfest.htm>

MD - HAGERSTOWN - Hamfest. Hagerstown Community College Recreation Center. VE Testing. Talk-in: 146.94 & 147.09. Antietam RA, Inc., Tina Jones KB8ZQM, 304-728-7769. E-Mail: kb8zqm@intrepid.net

Web: <http://www.qsl.net/w3cwc>

NY - YONKERS - Flea Market. Lincoln High School, Kneeland Ave. 9am-3pm. VE Exams. Talk-in: 440.425 PL 156.7, 223.760 PL 67.0, 146.910, 443.350 PL 156.7. Metro 70cm Network, Otto Supliski WB2SLQ, 914-969-1053. E-Mail: wb2slq@juno.com

Web: <http://www.metro70cmnetwork.com>

PA - WRIGHTSTOWN - Hamfest. Middletown Grange Fairgrounds. Talk-in: 147.09 and 443.950. Warminster ARC, Roy Connors K3TEN, 215-974-9373. E-Mail: k3ten@arrl.net

Web: <http://www.voicenet.com/~k3dn>

MAY 12-13

NH - ROCHESTER - Hamfest. Fairgrounds. Hoss Traders, Joe, 207-469-3492

MAY 13

CA - FONTANA - Inland Empire ARC Amateur Radio & Electronics Swapmeet. A B Miller High School. Bill 909-822-4138 eves

WI - MANITOWOC - Hamfest. Mancorad RC, 30

CALENDAR

The Events Calendar is a free service for publicizing electronic events such as amateur radio hamfests, flea markets, etc. If your organization is sponsoring an event and would like a free listing, contact us at least 60 days in advance. Include your flyer, estimated attendance, name of the person to contact, and phone number.

Complimentary issues are available upon request for distribution to your attendees. A street address for UPS is required.

While we strive for accuracy in our calendar, we can not be responsible for errors or cancellations. The information contained in this column is for the use of the readers of *Nuts & Volts* and may not be republished in any form without the written permission of T & L Publications, Inc.

All listing information should be sent to:

Nuts & Volts Magazine

Events Calendar

430 Princland Court

Corona, CA 92879

Phone 909-371-8497

Fax 909-371-3052

E-mail events@nutsvolts.com

Dick Swanson N9QFY, 920-682-9264. E-Mail: rschwanson@lakefield.net

MAY 13-14

CA - FERNDALE - Hamfest. Humboldt ARC, Marcy Campbell KE6IAU, 707-442-3866. E-Mail: marcidon@quik.com

Web: <http://www.humboldt.com>

WA - YAKIMA - State Convention, Masonic Center, 510 N. Naches Ave. Sat: 9am-4pm, Sun: 9am-1pm. VE Testing. Yakima ARC, Jack Wrenn N7KNO, 509-249-0897. E-Mail: n7kno@arrl.net

Web: <http://eagle.ykcm.com/~w7aq/hamfest.html>

MAY 19-20-21

OH - DAYTON - ARRL National Convention. Dayton ARA, Dave Coons WT8W, 937-849-0604. E-Mail: wt8w@arrl.org

Web: <http://www.hamvention.org>

MAY 20

ID - CALDWELL - Hamfest. Snake River ARC, Don Ingram KK7VM, 208-459-2459. E-Mail: ingramde@cyberhighway.net

RI - FORESTDALE - Hamfest. RI Amateur FM Repeater Service, Rick Fairweather K1KYI, 401-725-7507. E-Mail: k1kyi@arrl.net

MAY 20-21

IL - ELGIN - CoCoFEST. Elgin Plaza Hotel, 345 W. River Rd. Tony Podraza 847-428-3576. E-Mail: tonypodraza@juno.com

MAY 21

CA - FAIR OAKS - Hamfest. Bella Vista High School, 8301 Madison Ave. 6am-12pm. North Hills RC, Earl Mead K6ESM, 916-331-1115. E-Mail: nhrc@k6is.org Web: <http://www.k6is.org>

MA - CAMBRIDGE - Flea at MIT. Albany and Main Sts. 9am-2pm. Talk-in: 146.52 & 449.725/444.725 W1XMR PL 114.8 (2A). Nick Altenbernd K1MQX, 617-253-3776 (9-5). Web: <http://web.mit.edu/w1mx/www/swapfest.html>

NY - FARMINGVILLE - Hamfest. Radio Central ARC, Neil Heft K2KY, 516-377-0019. E-Mail: nheft@ibm.net

MAY 26-27

MS - PASCAGOULA - Hamfest. Civic Center, Jackson County Fairgrounds. Fri: 5-9pm, Sat: 8am-2pm. VE testing. Talk-in: W5WA 145.110. Jackson County ARC, Charles F. Kimmerly N5XGI, 228-826-5811. E-Mail: montehat@datasync.com

MAY 27

CT - VERNON - Hamfest. Natchaug ARC, Wayne Rychling N1GUS, 860-487-1921. E-Mail: warych@neca.com

Web: <http://users.neca.com/warych/narfcest.htm>

KY - DAWSON SPRINGS - Pennyrite Area Tailgatefest 2000. Dawson Springs ARC, Princeton ARS, Hopkins County ARA, & Pennyroyal ARS, Curt Beshear KE4UZE, 270-797-9117. E-Mail: ke4uze@spis.net

NC - DURHAM - Hamfest. South Square Mall. 8am-3pm. FCC Exams. Talk-in: 147.225+. Durham FM Assn., Joseph Fields KF4QYV, 919-596-3738. Web: <http://www.vramp.net/~dfma/>

PA - WINFIELD - Hamfest. Milton ARC, Ray Grant K3COD, 570-568-1727. E-Mail: rgrant@csrlink.net

MAY 27-28

WY - CASPER - State Convention. Radisson Inn, Casper ARC, Warren (Rev) Morton W57W, 307-235-2799 or 307-237-9301. E-Mail: mortonwg@aol.com

Web: <http://w3.tnb.com/~carr/hamfest.html>

MAY 28

IL - CHICAGO - Hamfest. DeVry Institute of

COMPUTER SHOWS

AGI Shows, 317-299-8827.

E-Mail: info@agishows.com

Web: <http://www.agishows.com>

Blue Star Productions

612-788-1901.

Web: <http://www.supercomputersale.com>

Computers And You, 734-283-1754.

www.a1-supercomputersales.com

Computer Central Shows

847-412-1900 & 1-888-296-6066.

E-Mail: compcent@mcsinet.net

www.computercentralshows.com

Computer Country Expo

847-662-0811 Web: www.ccxpo.com

Five Star Productions

810-379-3333. E-Mail: jeff@fivestars.com

www.fivestars.com

Georgia Mountain Productions

706-838-4827.

E-Mail: gamtpro@blrg.tds.net

georgiamountain.com

Gibraltar Trade Center, Inc.

734-287-2000. Taylor, MI.

E-Mail: taylor@gibraltartrade.com

www.gibraltartrade.com

Technology, 3300 N. Campbell. 8am-2pm.

Chicago ARC, George 773-545-3622 or Dean 708-331-7764

MD - WEST FRIENDSHIP - Hamfest. Howard

County Fairgrounds. 8am-2:30pm. Talk-in:

146.76, 224.76, 444.00. Maryland FM Assn., Mike

WA3TID, 410-923-3829

JUNE 2000

JUNE 2-3

GA - MARIETTA - Convention. Jim Miller Park.

Fri: 3pm-6:30pm, Sat: 8:30am-3pm. VEC testing.

Talk-in: 148.82. Atlanta RC, Ben Dasher KE4YZX,

404-869-6959. E-Mail: bendasher@mindspring.com

Web: <http://www.saf.com/arc/>

NE - SOUTH SIOUX CITY - Midwest/Dakota

Convention, 3900 Club & Sooland ARA, Leroy

Baldwin WOOFY, 319-395-7183.

E-Mail: lgbw0fy@aol.com

JUNE 2-3-4

NY - ROCHESTER - Convention. Monroe County

Fairgrounds, Rt. 15A. Fri: 12pm-5:30pm, Sat:

8:30am-5:30pm, Sun: 8:30am-1:30pm. Harold

Smith K2HC, 716-424-7184.

E-Mail: rochfst@frontiernet.net

Web: <http://www.rochesterhamfest.org>

JUNE 3

IL - SPRINGFIELD - Hamfest. State Fairgrounds,

Gate 11. VE Testing. Talk-in: 146.685. Sangamon

Valley RC, Edmund Gaffney KA9ETP, 217-628-

3697. E-Mail: egaffney@family-net.net

Web: <http://www.w9dua.net>

ME - HERMON - Hamfest. Pine State ARC,

Edward Richardson K1DTW, 207-825-4417.

E-Mail: edandglo@earthlink.net

MI - GRAND RAPIDS - Hamfest. Hudsonville

Gibraltar Trade Center, Inc.

810-465-6440. Mt. Clemens, MI.

E-Mail: mtclemens@gibraltartrade.com

www.gibraltartrade.com

KGP Productions

1-800-631-0062, 732-297-2526.

E-Mail: kgp@mail.com

MarketPro, Inc., 201-825-2229.

<http://www.marketpro.com>

MarketPro, Inc., 301-984-0880.

E-Mail: md@marketpro.com

<http://marketpro.com>

Narisaam Computer Show

770-663-0983.

E-Mail: narisaam@aol.com

Web: <http://www.showsale.com>

Northern Computer Shows

978-744-8440.

E-Mail: inquiries@ncshows.com

Web: ncshows.com

Peter Trapp Computer Shows

603-272-5008.

Web: www.petertrapp.com

Fairgrounds. VE Testing. Talk-in: 147.16.

Independent Repeater Assn., Kathy KB8KZH, 616-

698-6627 between 4-7pm Eastern.

Web: <http://www.iserv.net/~w8hvg>

NJ - TEANECK - Hamfest. Fairleigh Dickinson

University. 8am-2pm. Talk-in: 146.19/79. Bergen

ARA, James Joyce K2ZO, 201-664-6725. E-Mail:

hamfest@bara.org Web: <http://www.bara.org>

JUNE 3-4

NE - CHADRON - Hamfest. Pine Ridge ARC, Phil

Cary WAOPZA, 308-432-3956. E-Mail:

philcary@bbc.net

OR - SEASIDE - Northwestern Division ARRL

Convention. Convention Center. VE testing. Talk-

in: 146.660 (-600). SEAPAC, Randy Stimson

K27T, 503-297-1175. Web: www.seapac.org

JUNE 4

CT - NEWINGTON - Hamfest. Newington High

School, Willard Ave. (Rt. 173). 9am-1pm. FCC

exams. Talk-in: 145.45, 146.52 simplex, 224.84,

443.05. Newington Amateur Radio League, Inc.,

Thomas Ponte WB1CZK, 860-666-4539.

E-Mail: wb1czz@arrl.net

IL - PRINCETON - Hamfest. Bureau County

Fairgrounds. Talk-in: 146.955

Events CALENDAR

412-826-8006. E-Mail: w3bis@breezeshooters.net
Web: <http://www.breezeshooters.net>
VA - MANASSAS - Hamfest. Prince William County Fairgrounds. Talk-in: 146.97, 224.660, 442.200. Ole Virginia Hams ARC, Jack McDermott N4YIC, 703-335-9139.
E-Mail: N4YIC@arri.net or patnjack@erols.com
Web: <http://www.qsl.net/olevahams/>

JUNE 9-10

TX - ARLINGTON - State Convention. HAM-COM, Maury Guzik W5BGP, 214-804-0680.
E-Mail: chairman@hamcom.org
Web: <http://www.hamcom.org>

JUNE 9-10-11

WA - DRYDEN - Hamfest. Apple City ARC, Roger Eckhardt WB7SHL, 509-782-4977. E-Mail: dmeckhardt@juno.com Web: <http://www.qsl.net/w7td>

JUNE 10

CA - FONTANA - Inland Empire ARC Amateur Radio & Electronics Swapmeet. A B Miller High School. Bill 909-822-4138 eves

MA - EAST FALMOUTH - Hamfest. Barnstable County Fairgrounds, Rt. 151, 9am-2pm. VE sessions. Falmouth ARA, Ralph K. Swenson 508-548-6405. E-Mail: DEPSHER911@AOL.COM

MO - MACON - Hamfest. Macon Vo-Tech School. 8am-12pm. FCC Exams. Talk-in: 146.805(-). Macon County ARC, Dale Bagley K0KY, 660-385-3629. E-Mail: n0pr@arri.net Web: <http://www.cyberusa.com/~kfoster/hamfest.htm>

NC - WINSTON-SALEM - Hamfest. Forsyth ARC, John Kippe N0KTY, 336-723-7388. Web: <http://members.xoom.com/w4nc/hamfest.htm>

NY - CORTLAND - Hamfest. Skyline ARC, Andrew Slauch KB2LIV, 607-753-0597. E-Mail: kb2liv@clarityconnect.com

PA - BLOOMSBURG - Eastern PA Section Convention. Bloomsburg Fairgrounds. 8am-3pm. VEC Testing. Talk-in: 147.225 (+600) and 146.52 simplex. Columbia-Montour ARC, George Law N3KYZ, 570-784-2299. E-Mail: n3kyz@epix.net Web: <http://www.bafn.org/~cmarc>

JUNE 11

IL - WHEATON - Hamfest. DuPage County Fairgrounds, 2015 Manchester Rd. VE testing. Six Meter Club of Chicago, Joseph Gutwein WA9RIJ, 630-963-4922 or 708-442-4961.

E-Mail: wa9rij@mc.net
Web: <http://cyberconnect.com/orion/smcc.html>

KY - INDEPENDENCE - Hamfest. Northern KY ARC, Robert Blocher N8JMW, 513-797-7252. E-Mail: n8jarc@juno.com

NY - BETHPAGE - Hamfest. Briarcliff College, 1055 Stewart Ave. 8:30am-1pm. VE testing. Talk-in: W2VL 146.85 repeater (136.5 PL). Long Island Mobile ARC, Ed Muro KC2AYC, 516-520-9311. E-Mail: hamfest@limarc.org Web: <http://www.limarc.org>

OH - CANFIELD - Hamfest. Twenty Over Nine ARC, Don Stoddard N8LNE. E-Mail: n8lne@juno.com

OH - SUFFIELD - Hamfest. Goodyear ARC, Fred Mealy KC8BQX, 330-665-4563. E-Mail: fmealy@earthlink.net

TN - KNOXVILLE - Convention. National Guard Armory, 3330 Sutherland Ave. 9am-4pm. VE Exams. Talk-in: 147.30+, 224.50, 444.575. RAC of Knoxville, David Bower K4PZT, 423-670-1503. E-Mail: rack@kornet.org Web: <http://www.kornet.org/rack>

JUNE 17

CT - GOSHEN - Hamfest. Southern Berkshire ARC, Lee Collins K1LEE, 860-435-0051. E-Mail: lee@leecollins.com

MI - MIDLAND - Hamfest. Midland County Fairgrounds, Gerstacker Fair Center. 8am-1pm. Talk-in: 147.000+. Midland ARC, Del Lafavor WB8FYR, 517-689-3477. E-Mail: lafavel@juno.com Web: <http://www.qsl.net/w8kea/MARCSWAP.htm>

MO - HOUSTON - Hamfest. Ozark Mountain Repeater Group, Blanche White NOFLR, 417-967-3000

NJ - DUNELLEN - Hamfest. Columbia Park. 7am-2pm. Talk-in: 146.025/625, 447.250/442.250, PL 141.3, 146.520 simplex. Raritan Valley Radio Association, Fred Werner KB2HZO, 732-968-7789 before 8pm. E-Mail: wb2zh@arri.net or Doug Benner W2NJJ, 732-469-9009. Web: <http://www.w2qw.org>

OH - MILFORD - Hamfest. Milford ARC, Chris Reinfelder KB8SNH, 513-753-5066

TN - NASHVILLE - Hamfest. Nashville ARC, Bob Malone WB5ZDS, 615-865-6225. E-Mail: bmalone5@juno.com

JUNE 18

IN - CROWN POINT - Hamfest. Lake County Fairgrounds. VE testing. Talk-in: 147.00 repeater, 146.520 simplex. Lake County ARC, Jim Harney KF9EX, E-Mail: kf9ex@arri.net

MA - CAMBRIDGE - Flea at MIT. Albany and

Main Sts. 9am-2pm. Talk-in: 146.52 & 449.725/444.725 W1XM/R PL 114.8 (2A). Nick Altenbernd KA1MQX, 617-253-3776 (9-5). Web: <http://web.mit.edu/w1xm/www/swapfest.html>
MI - MONROE - Hamfest. Monroe County Radio Communications Assn., Fred VanDaele KA8EBI, 734-587-2250 or 734-242-9487. E-Mail: ka8ebi@arri.net Web: <http://www.mcrca.org>
OH - MACEDONIA - Hamfest. Nordinia High School. 8am-1pm. Talk-in: 146.82(-) repeater. Cuyahoga ARS, Rich James N8FIL, 1-800-404-2282. E-Mail: n8fil@aol.com Web: <http://www.cars.org>

JUNE 24-25

CA - FERNDALE - Hamfest. Humboldt ARC,

Marcy Campbell KE6IAI, 707-442-3866. E-Mail: marcidon@quik.com Web: <http://www.humboldt.com>

JULY 2000

JULY 2

PA - WILKES-BARRE - Hamfest. Murgas ARC, Bob Michael N3FA, 570-288-3532. E-Mail: wb3fa@aol.com

JULY 7-8-9

UT - BRYCE CANYON - State Convention. UT Hamfest Committee, Kathy Rudnicki N7JSH, 801-547-9218. Web: <http://www.utahhamfest.org>

JULY 8

CA - FONTANA - Inland Empire ARC Amateur Radio & Electronics Swapmeet. A B Miller High School. Bill 909-822-4138 eves

GA - GAINESVILLE - State Convention. Georgia Mountains Center. 8:30am-3pm. VE Testing. Talk-in: 146.67(-). Lanierland ARC, Ken Johnson N2AQ, 706-335-9658. E-Mail: n2aq@aol.com Web: <http://www.mindspring.com/~w4tl/hamfest.htm>

IN - INDIANAPOLIS - Central Division Convention. Indianapolis Hamfest Assn., Rick Ogan N9LRR, 317-257-4050. E-Mail: oganr@in.net Web: <http://www.indyhamfest.com>

MI - PETOSKEY - Hamfest. 4-H Bldg. Emmet County Fairgrounds. 8am-12pm. VE testing. Talk-

AMAZING DEVICES

Laser Window Bounce Listening System

Powerful listening system, yet simple in operation. You shine a LASER at a window and intercept the reflected beam with our ultra-sensitive filtered OPTICAL RECEIVER. Vibrations on the window from internal sounds and voices are now clearly heard. Range can be up to several hundred meters depending on the output power of the laser and optics used.

LBWS Plans and all Data for 3 Laser Window Bounce Systems.....	\$20.00
LBWSK Kit of Complete 100' System with Visible Laser for Demo/Science Project.....	\$129.95
LLR30 Optical RECEIVER with voice filter.....	\$99.95
LLR30K Kit of Optical Receiver.....	\$69.95
LLR40 Higher performance with low noise preamp, basic optics and deluxe headset.....	\$199.95
CWL10 10 mw ClassIIA Invisible IR LASER for 500'.....	\$149.95
CWL1K Kit of LASER.....	\$99.95
LM650P5 5 mw ClassIIA Visible Red Laser Module for up to 100'.....	\$19.95
LM650P10 10 mw ClassIIA Visible Red Laser Module for up to 200'.....	\$69.95

Gravity Motor

Electrical charge reactions produce the effect of "anti gravity." You build a model craft from simple parts and levitate it with our ion power source. Battery or 115vac operation. Great science or fascinating research project includes our gravity handbook.

GRA3 Plans/Book.....	\$20.00
GRA3K Power Source Kit.....	\$99.95
GRA30 Assembled Above.....	\$149.95

TAKE CONTROL Using Electronic Hypnosis

Electronic circuitry induces hypnotic as well as ALPHA relaxed mind states. Place subjects under your control.

HYP2 Plans.....	\$10.00
HYP2K Kit/Plans.....	\$49.95
HYP20 Ready to Use.....	\$69.95

MIND2 Plans for Mind Control.....	\$15.00
MIND2K Kit/Plans.....	\$49.95
MIND20 Ready to Use.....	\$79.95

Therapeutic Pulsar

Complex Magnetic waves are claimed to produce many health benefits. Board level experimental device is sold for research purposes only.

THMAG10 Lab Assembled.....	\$24.95
----------------------------	---------

Cybernetic Ear!

Provides that "extra edge" for many listening applications. Enhances 3 to 4x of normal.

CYBEREAR.....	\$19.95
---------------	---------

Mini TESLA Coil

Lights up a 4' fluorescent tube-all without any contact! Yet only 3" tall!

MTCK1 Kit/Plans.....	\$19.95
MTCK10 Assembled.....	\$34.95

Telephone Line Grabber

Room Listener Controller and Call Diverter. Listen to your premises. Break in to calls. Control household appliances. Remote dial long distance calls from anywhere!

TELCN4 Plans.....	\$10.00
TELCN4K Kit/Plans.....	\$99.95
TELCN40 Ready to Use.....	\$149.95

Tesla Coil

Produces 30" Sparks. Create a spectacular display of nature own lightning. Many amazing experiments possible. See in action on our web site!

BTC4 Plans.....	\$20.00
BTC4K Kit.....	\$799.95
BTC40 Ready to use.....	\$999.95
Smaller Version (8-10" Sparks).....	
BTC3 Plans.....	\$15.00
BTC3K Kit.....	\$349.95
BTC30 Ready to Use.....	\$449.95

Pain Field Pistol

Blast out rodents with high power ultrasounds. Handheld and battery operated with all controls. Rental units available.

PP1 Plans.....	\$8.00
PP1K Kit/Plans.....	\$49.95
PP10 Ready to Use.....	\$79.95

Amazing Gravitron

Remarkable true levitation without any tethering or external sources of energy. Winning science project. Includes self starter.

GRV10 - Anti Gravity Top.....	\$39.95
GRV30 - Super Levitator.....	\$49.95

Hover Board

28 pages of data related to the most revolutionary advance in transportation. Cutting edge R&D.

HOVER Plans and Data.....	\$25.00
---------------------------	---------

Transistorized TESLA Coil

Amazing and bizarre effects turn a normal light bulb into a spectacular plasma display! With adjustable frequency control. Safe 12vdc input.

TCLS Plans.....	\$8.00
TCLS5K Kit/Plans.....	\$59.95
TCLS10 Assembled and Tested.....	\$99.95

Attention! High Voltage Modules

Battery powered for hovercraft, plasma guns, anti gravity, force fields, pyrotech.

MINIMAX4 4KV.....	\$19.95
MINIMAX3 3KV.....	\$17.95
MINIMAX2 2KV.....	\$14.95

Ion Ray Guns

Star Wars Technology Directs Energy. Star Wars Technology Demonstrates Weapons Potential, Force Fields, IonMotors, Antigravity etc. Projects electric shocks without contact! Conduct many weird and bizarre experiments. Handheld battery operated and easy to operate.

IOG7/9 Plans.....	\$10.00
IOG7K Kit/Plans.....	\$99.95
IOG70 Assembled/Tested.....	\$149.95

Higher Powered Device

IOG9K Kit/Plans.....	\$129.95
IOG90 Assembled/Tested.....	\$199.95

Semi-Cond Burning Lasers

10mw to 2 Watts of continuous output! Use for directed beam of heat, illumination source for night vision, laser window bounce IR driver for ultra-bright green lasers.

CWL5K Kit/Plans minus diode.....	\$199.95
CWL50 Assembled minus diode.....	\$299.95
LD34 CW 3/4 W 980nm diode.....	\$199.95

Nightstar Night Viewer

Sees in total darkness

• 3500x Light Gain	
• Over 100 yds Recognition	
• Built in IR Illuminator	
• 20 degree Field of View	
• 20 Hours Battery Life	
• Spectral Response 810-840 nm.	
NSTAR10 - Ready to Use.....	\$239.95

Jacobs Ladder

Pyrotechnical traveling fiery plasma expands over 3' before evaporating into space. Solid state circuitry with adjustable arc control. 115/230 volt operation. Uses safe high frequency energy.

JACK1 Plans.....	\$8.00
JACK1K Supply, Mtg Blks, Ladders.....	\$149.95
JACK10 Ready to Use.....	\$249.95

3 Mi FM Voice Transmitter

Crisp clear performance. Many applications. Easy to assemble

FMV1K Kit and Plans.....	\$39.95
--------------------------	---------

See Our "Action" Web Site at www.amazing1.com

Experiment with and Construct Lasers, Phasers, Hypnosis, Mind Control, TESLA COILS, Time Travel, Rail Guns, Magnetic Cannons, Coil and Sleeve Guns, Super High Gravity Pulses, Explode Wires and Water, Antigravity, Levitation, Mass Warping, Magnetic Can Crushing, Plasma Propulsion, High Energy Radio Frequency Guns (Herf), EMP, Lattice Snapping, Force Fields, Ion Ray Guns and all Types of Electrical Pyrotechnics, Plasma and Neon Displays, Sound Blasters, Ultrasonics, Super Hearing, Long Range Transmitters, Jammers, Personal and Property Protection, Surveillance Plus More!!

Ultra Bright Green Laser visible over a mile!!

30 to 50x brighter than the red pointers. Shirt pocket sized pen .55" x 6.3" Full 5mw. Operates for hours from two "AAA" batteries. Call for pricing as we will not be undersold!!!!!!

6 FM Xmtr Kits!

- 1 Super Sensitive Ultra Clear 1 Mile+ Voice Transmitter.
- 2 1 Mile+ Telephone Transmitter.
- 3 Line Powered Phone Transmitter. Never Needs Batteries!!
- 4 Tracking/Homing Beacon Bleeping Transmitter
- 5 Video/Audio Rebroadcast 1 Mi.
- 6 TV/FM Radio Disrupter. Neat Prank! Discretion Required

Includes Hints Using Wireless Devices

COMBOX Above 6 Kits/Plans.....	\$59.95
COMBOX Above 6 Plans Only.....	\$10.00

Shock Force Field Vehicle Object Electrifier

Hand shock balls, wands. Mini circuit is easily hidden. Great payback for those wise guys. SHK1K Kit/Plan.....

.....	\$19.95
-------	---------

Mind&Brain Controllers

Incredible device Turbo charges memory. Boost mental powers, Controls stress, Speeds up healing processes and Uncover hidden potentials. High quality unit with many features.

BWPLUS-APOLLO Ready to use.....	\$179.95
BWII- EINSTEIN Lower cost unit.....	\$129.95

Burning Cutting Lasers

Current and Future Weapons Systems. We Stock Parts!

LC3 Plans Poor Mans CO ₂ System.....	\$15.00
LC7 Plans Lab CO ₂ System 30W.....	\$20.00
LAGUN2 Plans Nd, Yag, Ruby 6Kw.....	\$20.00
All Three Plans for only.....	\$25.00!!

PLASMA FIRE SABER

Patented Moving Light Concept Defies all Logic as it Appears to Evaporate into Space!! Replaceable Blades, Overide Switch Interactive Sound Module Available on Request

Available colors: "C" photon blue, starfire red phaser green, neon red

PFS15K-"C" Kit of 15' Active Length.....	\$24.95
SAB34K-"C" Kit of 24' Active Length.....	\$39.95
*SAB46K-"C" Kit of 36' Active Length.....	\$99.95

*Please add \$10.00 for special handling

Information Unlimited PO Box 716 Amherst N.H. U.S.A. 03031
1 800 221 1705 Orders/Catalogs Only! Fax 1 603 672 5406 Information 1 603 673 4730 Free Catalog on Request
Pay by MC,VISA,Cash, Check, MO, COD. Add \$5.00 S&H plus \$5.00 if COD. Overseas Contact for Proforma

Events CALENDAR

in: 146.68-. Straits Area ARC, Tom W8IZS, 231-539-8459 or Dirk KG8JK, 231-348-5043, E-Mail: kg8jk@qsl.net

MO - KANSAS CITY - Hamfest. PHD ARA, Bob Roske WA0CLR, 816-436-0069. E-Mail: wa0clr@worldnet.att.net

Web: <http://members.tripod.com/~PHDARA/>
NC - SALISBURY - Hamfest. Salisbury Civic Center. VE Testing. Talk-in: 146.73 tone 94.8 and 146.52 simplex. Rowan ARS, Jim Morris KA4MPP, 704-278-4960 or Carol Maher W4CLM, 704-633-6603. E-Mail: rbrown@salisbury.net

WI - OAK CREEK - Hamfest. The American Legion Post 434, 9327 S. Shepard Ave. 6:30am-4pm. Talk-in: 146.52 simplex. South Milwaukee ARC, Bob Kastelic WB9TIK, 414-762-3235 days & early eves.

JULY 9

IL - PEOTONE - Hamfest. Will County Fairgrounds. Talk-in: 146.94 (-600). Kankakee Area Radio Society, Don Kerouac K9NR, 815-939-7548. E-Mail: k9nr@juno.com
Web: <http://www.w9az.com>

PA - PITTSBURGH - Hamfest. North Hills ARC, Keith Ostrom KB3ANK, 412-821-4135. E-Mail: kb3ank@harc.pa.us
Web: <http://www.nharc.pa.us>

JULY 14-15-16

MT - EAST GLACIER - State Convention. Glacier/Waterton Int'l Hamfest Committee, Frank Phillips AC7AY, 406-273-2894. E-Mail: ac7ay@bigsky.net
Web: <http://www.tlatche.com/hamfest/>

JULY 15

CO - LOVELAND - Hamfest. Larimer County Fairgrounds, 700 Railroad Ave. 9am-4pm. VE exams. Talk-in: 145.115 (-offset) or 146.52 simplex. NCARC, 970-352-5304

MD - BRUNSWICK - Hamfest. Mid-Atlantic DX & Repeater Assn., Roy Bates N2CSQ, 301-834-9351. E-Mail: 74163.200@compuserve.com

OH - WELLINGTON - Hamfest. Lorain County Fairgrounds. 8am-2pm. VE Exams. Talk-in: 146.10/70. Northern Ohio ARS, John Shaaf KC8AOX, 216-696-5709. E-Mail: kc8aox@qsl.net
TX - SHERMAN/DENISON - Hamfest, Wilmer O. Kinsey WB5DCU, 903-893-5872. E-Mail: wb5dcu@gte.net

TX - TEXAS CITY - Hamfest. Tidelands ARS, Joe

Wileman AA5OP, 409-945-6794. E-Mail: aa5op@aol.com

JULY 16

MA - CAMBRIDGE - Flea at MIT. Albany and Main Sts. 9am-2pm. Talk-in: 146.52 & 449.725/444.725 W1XMR/PL 114.8 (2A). Nick Altenbernd KA1MQX, 617-253-3776 (9-5). Web: <http://web.mit.edu/w1xm/swapfest.html>

MO - WASHINGTON - Hamfest. Zero Beaters ARC, Keith Wilson K0ZH, 636-629-2264. E-Mail: jwpubl@fidnet.com Web: <http://zbarc.usmo.com/>
NJ - AUGUSTA - Hamfest. Sussex County Fairgrounds, Plains Rd. Talk-in: 147.90/30. Sussex County ARC, Dan Carter N2ERH, 973-948-6999. E-Mail: n2erh@email.com
Web: <http://www.scarcnj.org>

PA - KIMBERTON - Hamfest. Mid-Atlantic ARC, Bill Owen W3KRB, 610-325-3995. E-Mail: gem@op.net
Web: <http://www.marc.org/hamfest.html>

JULY 21-22

FL - MILTON - Hamfest. Santa Rosa County Auditorium. Fri: 5pm-9pm, Sat: 8am-2pm. FCC Exams. Talk-in: 146.70. Milton ARC, Bill Couch W4VYV, 850-623-0592. E-Mail: billcouch@sprintmail.com
Web: <http://home.att.net/~k4ozl/marc.htm>

JULY 22

NH - NASHUA - Hamfest. Res Ctr Church. NE Antique RC 617-923-2665
NY - FRANKFORT - Hamfest. Utica ARC, Bob Decker AA2CQ, 315-797-6614. E-Mail: ktmd@borg.com

OH - CINCINNATI - Hamfest. Diamond Oaks Development Campus, 6375 Harrison Ave. 7am-2pm. VE Exams. Talk-in: 146.67 and 146.925. OH-KY-IN ARS, Gene McCoy N8KOJ, 513-541-6935. E-Mail: n8koj@arrl.net
Web: <http://www.qsl.net/k8sch>

JULY 23

IL - SUGAR GROVE - Hamfest. Waubesa Community College, Rt. 47 Harter Rd. VEC Exams. Talk-in: 147.210 (+600) PL 103.5/107.2. Fox River Radio League, Maurice Schietecatte W9CEO, 815-786-2860. E-Mail: w9ceo@arrl.net
Web: <http://www.frrl.org/hamfest.html>

JULY 28-29

OK - OKLAHOMA CITY - State Convention. OK State Fair Park (Hobbies, Arts & Craft Bldg.). Fri: 5-8pm, Sat: 8am-5pm. Talk-in: 146.82. Central OK Radio Amateurs, Harold Miller KB1ZQ, 405-672-7735 or 405-650-9963. E-Mail: n1lpn@swbell.net
Web: <http://www.geocities.com/heartland/7332>
TX - AUSTIN - Convention. Austin ARC, Austin Repeater Group, Texas VHF-FM Society, Joe Makeever W5HS, 512-345-0800

JULY 28-29-30

AZ - FLAGSTAFF - State Convention. Ft. Tuthill. Fri: 12pm-5pm, Sat: 9am-5pm, Sun: 9am-2pm. VE Testing. Talk-in: 146.980 MHz with 100.0 Hz PL Tone. ARCA, Norm Martin K7OLD, 520-297-9562. E-Mail: norm@hamsrus.com
Web: <http://www.hamsrus.com/tuthill.html>
CANADA - BC - VANCOUVER - Pacific Northwest DX Convention. BC DX Club & Fraser DX Club, Dave Johnson VE7VR, 604-438-8715. E-Mail: ve7vr@rac.ca Web: <http://www.bcdxc.org>

JULY 29

OR - BANDON - Hamfest. Coos County RC, Brian Howard W7MLT, 541-572-5623. E-Mail: w7mlt@usa.net

JULY 30

MD - TIMONIUM - Hamfest. Timonium Fairgrounds. Talk-in: 147.03+ and 224.96. BRATS, Mayer Zimmerman W3GXK, 410-461-0086. E-Mail: w3gsk@arrl.net
Web: <http://www.smart.net/~brats>
OH - RANDOLPH - Hamfest. Portage ARC, Joanne Solak KJ30, 330-274-8240. E-Mail: jsolak@apk.net Web: <http://parc.portage.oh.us>

AUGUST 2000

AUGUST 5

MI - TAWAS - Hamfest. Iosco County AR Enthusiasts, John Hanley KA8AIP, 517-756-2845. E-Mail: ka8aip@centurytel.net
Web: <http://www.oscoda.net/~icare/>
NM - ROSWELL - Hamfest. Pecos Valley ARC, Vernetta Verasso KC5WKA, 505-627-7777. E-Mail: kc5wka@dfn.com Web: <http://www.pvarc.com>
NY - ITHACA - Hamfest. Tompkins County ARC, Richard Spingarn AA2UP, 607-387-5251. E-Mail: richard@eagleprint.com
Web: <http://www.compcenter.com/~tcarc>
OH - COLUMBUS - Hamfest. Voice of Aladdin ARC, James Morton KB8KPJ, 614-846-7790. E-Mail: kb8kpj@cs.com


AUGUST 6

IN - ANGOLA - Hamfest. Land of Lakes, Bill

PIC Real-time 'Emulator' and Programmer for

\$159

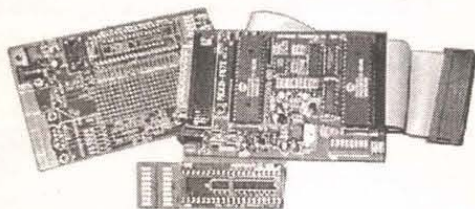Introducing **PIC-ICD** = Debugger + Programmer + Demo Board = \$159





PB-87X probe for RICE17A now shipping

supports 16F87x, 16C66/67/677

Featuring on-the fly data capture break with 2-level trigger and pass count support, stop watch function and real-time data bus capture - complete system for \$775

- For PIC16F87X and emulates most PIC16C6X/7X
- In-circuit run-time debugging
- Real-time code execution
- High speed parallel port interface
- Built-in device programmer
- 2.5V to 6.0V operating range
- One level real-time breakpoint
- Two external break inputs
- Conditional animation break
- Run, step, run to Cursor, etc.
- Operating frequencies from 32khz to 20mhz
- Runs under PICICD IDE (Win 95/98/2000NT) or MPLAB™ (Win 95/98)
- Source level and symbolic debugging
- Software animation trace captures 3 user-defined variables in addition to opcode, W, STATUS, FSR registers and corresponding instructions
- Comes with ICD Debug module, demo board, 40-pin and 28-pin emulator headers, cable, power adapter, IDE software and printed user's guide

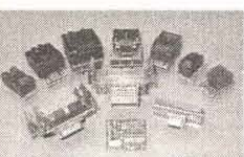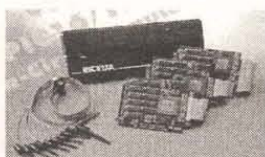

Full-feature, real-time RICE17A Emulator System, from \$595

- 64K program memory, 32K trace
- 12-clip external probe - break input, break output, trigger output, 8 logic traces and ground
- Source level debugging
- Unlimited software breakpoints and trigger points
- New PB-87x probe provides on-the-fly data break with 2-level trigger and pass count, stopwatch and databus capture
- Supports PIC12/16/17
- Low voltage emulation
- Self-diagnostic test board
- Optional PIC Time Stamp for \$59

Single Socket PIC Programmers and Adapters

- PGM16N supports all PIC12/14/16
- PGM17 supports all PIC17
- One 40-pin ZIF socket for all DIP parts
- Optional surface mount sockets for all package types which are compatible with all PIC programmers
- Emulation headers in SOIC, PLCC and QFP packages
- Win 95/98/NT hosting software
- DOS software for PGM17

Advanced TransData

14330 Midway, #128, Dallas, Texas
Tel 972.980.2667 Fax 972.980.2937
Email: atc1@ix.netcom.com

Stand Alone Gang Programmer from \$900

- New flash based firmware makes new device support a snap
- Production quality 8-gang programmer for PIC, SX, ST6 and more
- Approved by IC manufacturers
- Stand-alone chip duplication
- LCD and LEDs display program functions and results
- Codes reside securely in EEPROM of control module
- Custom all programming voltages in 0.1v increments

Visit the Ultimate Source for PIC Tools at

www.adv-transdata.com

AMAZING MICROVIDEO!

SUPERCIRCUITS.COM

America's #1 Microvideo Source

LIPSTICK VIDEO CAMERAS

MICRO COLOR CAMERA
1" X 1"
350 TVL
\$89.95!!



STEALTHY SUPER PINHOLE
\$69.95

FREE CATALOG! CALL US TODAY AND GET YOURS!

COLOR \$189.95

1 YEAR WARRANTY

WOW!

FREE PLUG & PLAY CABLES
1 YEAR WARRANTY

AMAZING!

STEALTHY SEE-IN-THE-DARK
WEATHERPROOF WITH 56
IR LED'S \$139.95

WIRELESS VIDEO

\$89.95

2.4 GHz AUDIO/VIDEO
TRANSMITTER, RECEIVER
W/ 700 FOOT RANGE
PART 15 FCC APPROVED

STEALTHY PINHOLE VIDEO CAMERA \$34.95
410 TVL, 0.5 LUX, 1.2"

1 YEAR WARRANTY

1-800-335-9777 ext NV

Or fax us at 512-260-0444

www.supercircuits.com

Free Catalog- Call Us Today And Get Yours

1-800-335-9777

Write in 56 on Reader Service Card.

Buy your microvideo equipment where NASA, The Air Force, JPL, Lawrence Livermore Labs and the FBI does. Call us today.

For the best in high performance microvideo equipment, call the experts at Supercircuits. We've grown to be America's microvideo leader by consistently offering the best equipment at the lowest prices, with unbeatable service...compare our plug 'n play ease of use, warranties and return policies. Of course, Supercircuits microvideo is used by some of the biggest names in science, industry and national defense. But with prices starting at under \$35 for tiny high resolution video cameras, it is truly technology that is as affordable as it is amazing. Call us today at 1-800-335-9777 for a free 80 page microvideo catalog, loaded with photos, specs and more. Or log onto our website at www.supercircuits.com. You'll be amazed!

WORLD'S SMALLEST! LISTED IN 1999 GUINNESS BOOK OF RECORDS

CCTV VIDEO CAMERA \$79.95!

SONY CHIPSET

1 YEAR WARRANTY

WIRELESS VIDEO

AMAZING!

MICRO VIDEO CAMERA \$59.95!

NIGHTVISION VIDEO CAM

.04 LUX
460 TVL
2 YEAR WARRANTY

ULTRA PINHOLE VIDEO CAMERA-EASY CONCEALMENT \$109.95

AMAZING NEW UNDERCOVER VIDEO

CAP CAM \$149.95
GLASSES CAM
TIE CAM
BAG CAM
PAGER CAM

WORLD'S SMALLEST VIDEO CAMERA & TRANSMITTER-700 FOOT RANGE \$299.95
1 YEAR WARRANTY

UNBEATABLE DEAL!

350 Lines of Resolution
TINY 1.25" COLOR CAMERA-PLUG & PLAY-ONLY \$69.95!!

SONY GV-A500HI-8 VCR WITH 4" TFT MONITOR \$979.95

www.supercircuits.com

Events CALENDAR

Brown WD9DSN, 219-475-5897.

E-Mail: sharon.l.brown@gte.net

VA - BERRYVILLE - Hamfest. Clarke County Ruritan Fairgrounds. VE Exams. Talk-in: 146.82-. Shenandoah Valley ARC, Irvin Barb W4DHU, 540-955-1745. E-Mail: ibarb@visualink.com
Web: <http://www.vvalley.com/svarc/hamfest>

AUGUST 12

CA - FONTANA - Inland Empire ARC Amateur Radio & Electronics Swapmeet. A B Miller High School. Bill 909-822-4138 eves

IL - QUINCY - Hamfest. Eagles Alps Grounds, 3737 N. 5th St. 8am-2pm. VEC Testing. Talk-in: 147.63/147.03. Western IL ARC, Jim Funk N9JF, 217-336-4191. E-Mail: jfunk@adams.net
Web: <http://www.qsl.net/w9awe>

NY - ROME - Hamfest. Rome RC, Russell Schorer KB2MAS, 315-853-8739.

E-Mail: w4bny@juno.com

WV - HUNTINGTON - Hamfest. Tri-State ARA, Dwight D. Smith, Sr. WB8JPJ, 304-522-7865. E-Mail: wb8jpj@home.com

AUGUST 13

IA - AMANA - Hamfest. Amana Outdoor Convention Center. VE Exams. Talk-in: 146.745/145 and 146.520. Cedar Valley ARC, Chuck Bassett N0UTS, 319-378-0448.

E-Mail: n0uts@rf.org Web: <http://cvarc.rf.org>

IN - GREENTOWN - Hamfest. Greentown Lions Club Fairgrounds. Kokomo & Grant County ARCs, L.B. (Nick) Nickerson KA6NQW, 765-668-4814. E-Mail: ka6nqwnick@netusa1.net Web: <http://www.netusa1.net/~ka6nqwnick/hamfest.html>

MA - ORANGE - Hamfest. Mohawk ARC, John Doud AE1B, 978-249-5905. E-Mail: ae1b@gis.net

MI - JACKSON - Hamfest. Cascade ARS, Dennis Byrne KC8JZ, 517-522-4058 or 517-796-6966. E-Mail: byrmeda@voyager.net

MN - ST. JOSEPH - Hamfest. St. Cloud ARC, Linden Scott KA0DAQ, 320-252-4498. E-Mail: lscott@aol.com

Web: <http://www.w0sv.org/hamfest.html>

NJ - BAYVILLE - Hamfest. Bayville Fire House, Rt. 9. VE Testing. Talk-in: 146.910 out, 146.310 in, PL 127.3. Jersey Shore ARS, Bob Murdock WX2NJ, 732-269-6379. E-Mail: jsarsfest@aol.com

Web: <http://members.aol.com/jsarsfest/jsarsfest.html>

NY - DEPEW - Hamfest. Hearthstone Manor, 333

Dick Rd. VE Testing. Lancaster ARC, Luke

Callianno N2GDQ, 716-634-4667 or 716-683-8880.

E-Mail: lcallianno@freeweb.com

Web: <http://hamgate1.sunyerie.edu/~larc>

PA - YORK - Hamfest. VE testing. Talk-in: 146.700. York ARC, Southern PA Comm. Group, & Hilltop Transmitting Assn., Cecil Mundorff K3DCU, 717-927-6662

AUGUST 18-19-20

CANADA - BC - PRINCE GEORGE - Hamfest.

Prince George ARC, Brent Lyons

E-Mail: lyonsden@saintmail.net

Web: <http://www.pghamfest.dhs.org/>

AUGUST 19

KS - CHANUTE - Hamfest. Chanut Area ARC,

Charlie Ward WD0AKU, 316-431-6402

WA - LONGVIEW - Hamfest. Cowlitz County

Expo Center. 9am-1pm. Talk-in: 147.26+. Lower

Columbia ARA, Bob Morehouse KB7ADO, 360-

425-6076. E-Mail: kb7ado@aol.com

Web: <http://www.qsl.net/nc7p/swapmeet.htm>

AUGUST 20

IN - LAFAYETTE - Hamfest. Tippecanoe ARA,

Bob Martin W9YE, 765-423-1035

KY - LEXINGTON - Hamfest. National Guard

Armory, adjacent to Lexington airport. 8am-4pm.

VE sessions. Talk-in 146.760. Bluegrass ARS,

John Barnes KS4GL, 606-253-1178. E-Mail:

KS4GL@juno.com Web: <http://www.qsl.net/k4kqj>

MA - CAMBRIDGE - Flea at MIT. Albany and

Main Sts. 9am-2pm. Talk-in: 146.52 &

449.725/444.725 W1XMR PL 114.8 (2A). Nick

Altenbernd KA1MQX, 617-253-3776 (9-5). Web:

<http://web.mit.edu/w1mx/www/swapfest.html>

AUGUST 25-26-27

MA - BOXBOROUGH - Convention. Holiday Inn

Conference Center. Tony Penta W1ABC, 617-248-

6996 or 978-887-8887. E-Mail: w1abc@arrl.net

Web: <http://www.boxboro.org>

AUGUST 27

IL - DANVILLE - Hamfest. Vermilion County

ARA, Gary Denison KA9SKS, 217-759-7389.

E-Mail: gdenison@danville.net

KS - SALINA - State Convention. Central KS

ARC, Ron Tremblay WA0PSF, 785-827-8149.

E-Mail: tremblay@midusa.net

Web: <http://www.qsl.net/w0cy>

Serial in, graphics out.

Almost too easy.

These serial displays take RS-232 at 2400 or 9600 baud and produce stunning text and graphics on a supertwist LCD screen. See our complete line at www.seetron.com. All models are in stock for immediate delivery.

G12032

120x32-pixel LCD

SGX-120L \$99.00

Same size as 2x16 text LCD


Editable font(s) in 4 sizes

Up to 6 screens in EEPROM

Easy terminal protocol



(3.2 x 1.4 in.)

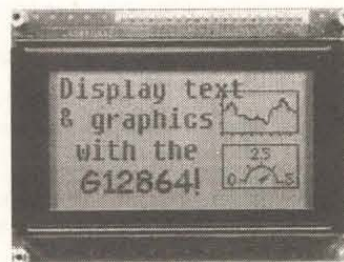

(3.7 x 2.8 in.)

G12864

128x64-pixel LCD

\$199.00 BGX-128L-1

Large, sharp LCD

Editable font(s)

Up to 14 screens in flash

Separate text, graphics layers

DB9 connector built in

AC adapter jack built in

Easy terminal protocol

www.seetron.com

Scott Edwards Electronics, Inc. ph 520-459-4802 fx 520-459-0623 nnv@seetron.com

Write in 57 on Reader Service Card.

Nuts & Volts Magazine/May 2000 33

TECH FORUM

This is a READER TO READER Column. All questions AND answers will be provided by *Nuts & Volts* readers and are intended to promote the exchange of ideas and provide assistance for solving problems of a technical nature. All questions submitted are subject to editing and will be published on a space available basis if deemed suitable to the publisher. All answers are submitted by readers and **NO GUARANTEES WHATSOEVER** are made by the publisher. The implementation of any answer printed in this column may require varying degrees of technical experience and should only be attempted by qualified individuals. Always use common sense and good judgement!

QUESTIONS

Send all material to **Nuts & Volts Magazine**, 430 Princland Court, Corona, CA 92879, OR fax to (909) 371-3052, OR E-Mail to forum@nutsvolts.com

ANSWER INFO

- Include the question number that appears directly below the question you are responding to.
- Payment of \$25.00 will be sent if your answer is printed. Be sure to include your mailing address if responding by E-Mail.
- In most cases, only one answer per question will be printed.
- Your name, city, state, and E-Mail address, (if submitted by E-Mail), will be printed in the magazine, unless you notify us otherwise with your submission.
- The question number and a short summary of the original question will be printed above the answer.
- Unanswered questions from a past issue may still be responded to.
- Comments regarding answers printed in this column may be printed in the Reader Feedback section if space allows.

QUESTION INFO

TO BE CONSIDERED FOR PUBLICATION

All questions should relate to one or more of the following:

- 1) Circuit Design
- 2) Electronic Theory
- 3) Problem Solving
- 4) Other Similar Topics

INFORMATION/RESTRICTIONS

- No questions will be accepted that offer equipment for sale or equipment wanted to buy.
- Selected questions will be printed one time on a space available basis.
- Questions may be subject to editing.

HELPFUL HINTS

- Be brief but include all pertinent information. If no one knows what you're asking, you won't get any response (and we probably won't print it either).
- Write legibly (or type). If we can't read it, we'll throw it away.
- Include your Name, Address and Phone Number. Only your name will be published with the question, but we may need to contact you.

choice would be to have the antenna relocated about 10 feet vertically to a floor above.

50014 Don Fuller
West Chester, PA

There are several companies pushing 900 MHz and 2.4 GHz video/audio transmitter and receiver units commercially.

Isn't there a simple and legal transmitter circuit that can be purchased or constructed that would use an unoccupied UHF channel that

I am looking for a schematic for a Motorola GP300 radio interface box.

5001 E. Herudl
Germany

I am looking for the "Common Core" series of books on electricity, electronics, servos, and radar. I believe these were around the 1970s and were geared towards the military (Navy).

I immigrated to the US from the UK two years ago, having retired from the Royal Navy (we used those books for some of our electronics theory).

5002 Michael Irving
Pendleton, OR

I've been trying to locate a very simple circuit for a pulse train transmitter where I can vary the pulses and that will operate at 230 MHz.

5003 A. J. Anzevino
Wappingers Falls, NY

I need to find information on the Internet or how to do my own circuit to display scrolling electronics messages on 4 x 12 characters. It has two different colors on 5 x 7 matrix display. I am using a PIC 12C74A controller for the project.

5004 Student
EM5G@aol.com

I need to add a time delay circuit on my RF power amplifier so the 110-volt AC cooling fan will continue to blow air on the final amplifier tubes for about three minutes after the amplifier is turned off. I would like to avoid using an expensive thermal time delay relay, if possible.

5005 Allan
via Internet

I need to know the serial number and stats for the laser in the Sony CD player CDP-C20.

5006 Ian Bruce
via Internet

I recently bought a pair of 900 MHz wireless headphones which are meant to connect to an audio device through an RCA jack.

The manual indicates that the unit could be damaged if connected to a speaker output, presumably

because of level.

Has anyone got a simple design for an AGC amplifier with 1V P-P output, so that I may use this with a speaker output?

5007 Jack Rebman
Fairfax Station, VA

A friend of mine is a shoe maker that wants to test electrical safety shoes. He needs an 18KV, 1mA AC power supply with a voltmeter and ammeter on the output.

The ability to manually ramp up the voltage at about 1KV/sec and maintain at full voltage for one minute is required.

How can I make this, or is there a product like this already available?

5008 Anthony Tekatch
Ontario, Canada

I want to use my Motorola TalkAbout walkie-talkies for motorcycle-to-motorcycle communications. The TalkAbout 250 has a VOX (voice activated transmission) feature, and so, one would think this would be ideal for my hands-free application.

The optional Motorola Earbud with Inline Mic, which is supposed to work with the VOX feature, doesn't. I either have to shout at the top of my lungs, or have to hold the Mic to my lips, in order to trip the VOX.

No, there is no Mic gain or VOX trip adjustment.

I am looking therefore, for a better Earbud-type microphone/speaker (that will fit under a helmet) that is or can be made to be compatible with the TalkAbout.

I think I saw Clint Eastwood with what I'm looking for in "In the Line of Fire" and I'm pretty sure Mulder and Scully used them in the episode where the veteran was able to sort of become invisible.

The stuff Jabra makes is close to what I'm looking for, but they don't offer anything that is compatible with the TalkAbout. Any Suggestions?

5009 Tom Tillander
via Internet

How would I go about retrieving an HTML document from the Internet on a DOS-based computer?

I want my DOS-based home-automation controller to be able to access the National Weather

Service forecast for my area, and automatically parse this report to schedule lawn watering.

I plan to get cable modem service to my house. I'm a programmer, but have limited experience with TCP/IP other than surfing. I have seen DOS-based TCP/IP stacks for sale, but don't know how to proceed. Any suggestions?

50010 Jeff Bowles
Columbus, OH

Does anyone know how to easily and inexpensively make your own PC boards? I have tried transferring laser printed layouts to copper, but can't get the whole circuit to stick. The sensitized copper clad available from Digi-Key requires a negative, but my layout program only prints black on white.

50011 Russell Kincaid
via Internet

I would like to set up a small network of one-five computers using a KVM (Keyboard Video Mouse) switch. I purchased an inexpensive two-way switch but often as not it loses the mouse and rebooting is necessary. I'm guessing that better switches involve some circuitry that maintains communication between the devices and the motherboard. Can anyone explain how this works? A design would be great.

50012 Carl Camper
Colstrip, MT

I need a schematic for a broadband UHF (50 MC to 500 MC approximately), one transistor, battery-operated impedance matching circuit that will match the high impedance of a random long-wire antenna to the low impedance whip antennas used on small radios, using an alligator clip to connect to the short whip on portable radios.

50013 Donald R. Smith
Palm Springs, CA

Is there a simple way to relocate or extend a 2.4 GHz antenna? It's the tiny antenna mounted on a digital, spread spectrum telephone base unit.

The best operating location of my base unit is the one that is terrible for communicating. The good

TECH FORUM

could be tuned by any TV or VCR without adding another box to the audio/video clutter.

50015 Dan Scheffner
via Internet

I'm a radio serviceman and I need manuals and service parts for two-way CB, ham, military aircraft, FM, public service, civilian avionics.

I am also looking for a OEM distributor that has OEM obsolete parts, such as coils, tubes, transistors, capacitors, inductors, etc.

50016 David N. Duerksen
Hesston, KS

I have several LED scrolling signs that were made by Innovative Signs (Color Cells). They use a nine-pin serial interface to program and what looks like a small IC board to control.

I am looking for any info on how to obtain a keypad or a schematic in order to program these signs.

50017 Jay Hughes
Hampden, MA

I am looking for a service manual for a LINK communications unit. The unit was made in the early 1940s. It is a type 250-UFS. The receiver is a type 12-UF (Ed.6) and the transmitter is a (250-UFS (Ed.6) covering the 30-50 MHz.

Any help with a person or place for this information would be great. By the way, this is a restoration project.

50018 Charlie Tipton
Ellicott City, MD

I'm trying to find a seven-segment LED display driver chip that shows hexadecimal, that is 0-F.

50019 Mark Phillips
via Internet

ANSWERS

ANSWER TO #1001 - JAN. 2000

I need any information available (hardware, software, programming) on HP 75D vintage laptop. Also accessories, printer, and mini-cassette.

I have the HP 75 manual including virtual FD/modem. Also HP 75s, HP printer for same, and other information. I can be contacted at: hilltop@webtv.com or call 760-726-6291.

Don Waters
via Internet

ANSWER TO #4007 - APRIL 2000

I need help with an Ultrasonic cleaner. Mostly, the oscillator to produce 40 to 60 KHz 1,000V sinewave to the piezoelectric transducers. I have a 1,000V transformer (1,500mA) with 110 VAC input.

Ultrasonic cleaners utilize circuits that look more like RF devices

than audio. Most commercial circuits utilize either an oscillator with an output stage, or a multi-vibrator type power oscillator.

The 1000V 60 Hz transformer you have will be of no help to you, as it will not pass much of the 40-60 KHz signal you will be generating.

The output transformers of most cleaners are like RF transformers, usually air core, with litz wire. Most often, the commercial designs using the standard (about 1/8" thick) transducers develop 35-45 watts per transducer.

The trick will be to match the output impedance of your circuit to the impedance of your transducers when mounted to the tank.

By the way, the transducers do generate a bit of heat, which must be transferred to the tank or they will crack in use. Regular epoxy is not very heat conductive. I recommend Loctite 383, which is a heat-conductive bonding agent usually used for permanent mounting of heatsinks to semiconductor devices.

Phil Shewmaker
Louisville, KY

ANSWER TO #4008 - APRIL 2000

I want to build a simple RF power amp. The approximate specs would be 12 VDC, a few hundred micro watts in, 3-5 watts out.

For years, I have looked for a simple schematic for a simple single or maybe two transistor amps that will amplify up to about five watts in the 30 MHz to 100 MHz range.

Is there a schematic that's simple to build, using only a transistor or two, a few caps and coils, no baluns or transformers?

Please provide values and transistor number.

A simple two transistor circuit without baluns and transformers probably does not exist. Minicircuits sells a ZHL-5W-1 amplifier with 40 dB of gain and 5W out, but it uses 24V power, consumes 75 watts (4% efficiency), and doesn't have enough gain. It also costs \$1,000.00.

All these numbers reflect on the difficulty of the design. Here's a closer look.

Your specifications are too demanding. One hundred microwatts in (-10 dBm) and five watts out (37 dBm) implies a gain of 47 dB. A single transistor stage will provide about 10 dB of gain, so you will need four or five stages.

Even low power MMICs only have about 13 dB of gain. If you want linear gain, then the power stages should use push-pull designs — but they require two transistors and a couple of transformers.

The alternative for linear gain is to burn lots of power. Power stages also require close attention to impedance matching. Narrowband designs can use reactive networks for the

impedance match, but broadband designs (your specifications are for almost two octaves) use transformers and baluns.

There may be other things to fix. You may not be driving the LPA1 to its full output power (what is the input power and what is the gain of the LPA1?). Adding a MMIC in front of the LPA1 would help that problem.

Increasing a transmitter from 1W to 4W only doubles its range. A directional antenna can supply the same benefit with no power increase.

Gerald Roylance
Mountain View, CA

ANSWER TO #4009 - APRIL 2000

I want to run the feed from my satellite dish about 150 feet under the lawn, but I have been unable to identify the types of coax that are suitable for burial. Is there some marking (like the UF for power cables)?

None of the references I have on coax mention burying the cable. Why?

I'm not sure there is a requirement for direct burial coaxial cable. The satellite feed is less than 24V, so it does not have the stringent requirements for (lethal) 120V cables — for example 18 inch burial depth and rigid anchors at the ends. If you don't have rodents with perverse appetites, then you should be able to bury any low voltage plastic cable.

I would stay away from all aluminum shields because of galvanic corrosion. RG-6 usually has a foil shield, so you cannot get away from that aluminum, but some cables have an aluminum braid. Get a cable with a copper braid.

In spite of the above, I would put the cable in plastic electrical conduit. The big expense is digging the trench, and you only want to do that once.

Plastic conduit is less than 10 cents/foot. The primer and cement are a few dollars more. That cost is a small part of the installation. Thread the conduit with twine as you lay it — 150 foot fish tapes are uncommon. You may want to run two coax cables while you're at it. You should also check if you will need an inline amplifier somewhere in the run.

Gerald Roylance
Mountain View, CA

ANSWER TO #4001 - APRIL 2000

I'm designing a device to provide some data while I'm bike riding. I think I've figured out speed, acceleration, and distance.

I'm looking for a way to measure grade — how steep a hill I'm going up. Is anyone aware of a sensor, or other way to measure this?

The simplest way to measure pitch is a pendulum bob. A weight on



DEDICATED TO BRINGING YOU THE MAGIC OF RADIO

THE MAGIC AND MYSTERY OF RADIO WAVES AND ANTENNAS UNRAVELLED IN TWO MONUMENTAL NEW BOOKS.

WRITTEN FOR YOU, THE INQUISITIVE AMATEUR OR SERIOUS EXPERIMENTER.

THE SCIENCE OF ANTENNAS: FIELDS, INDUCTION, RADIATION, WAVES, RECEPTION.....14.95 PPD.

ANTENNA SYSTEM OPTIMIZATION: RECEPTION, ANTENNA FACTORS, LINES, GROUNDS, LONG, MEDIUM AND SHORT WAVES.....14.95 PPD.

NOT YOUR TYPICAL ANTENNA BOOKS

FOR ORDERING OR INQUIRIES:
MAX RESEARCH
PO BOX 1306, GROUP AT
EAST NORTHPORT, NY 11731

Write in 52 on Reader Service Card.

Question: Who Uses .45 Shells

- The Lone Ranger
- GI Joe
- Metrologic

Answer: All the Above

Metrologic manufactures and sells low voltage (3Vdc), stable output (3mW)

DIODE LASERS housed in rugged "Bullet Packs"

For information on our laser diodes, laser and optics kits as well as a FREE catalog including over 100 laser experiments contact us at:

1-800-667-8400
www.metrologic.com

"Innovative Leaders in Laser Technology for over 30 Years"

Metrologic



NJ Phone: 856.228.5544
90 Coles Road
Blackwood, NJ 08012
laser@metrologic.com

Write in 53 on Reader Service Card. 35

the end of a rod provides a vertical reference, and an angle sensor [such as a potentiometer or rotary encoder] measures the angle between that vertical and the bike.

Unfortunately, the sensor is also sensitive to acceleration, but you can compensate for that. An interesting variation of this sensor uses a high dielectric constant fluid between two 90-degree sector electrodes. At 0 degrees, the electrode capacitance match; a tilt increases one capacitance and decreases the other by the same amount.

The combination makes a linear capacitive divider. The fluid also dampens the measurement.

A more involved technique would measure difference in height between the front of the bike and the back. You can do this with water and plastic tube. Imagine a U-tube almost filled with water with one end attached at the front, and the other end at the back. Put a ruler next to one end to measure the slope. You can measure the water heights optically or with pressure sensors. There is [or was] a commercial electronic level based on this idea.

Airplanes use gyroscopes, but that is probably too involved.

Gerald Roylance
Mountain View, CA

ANSWER TO #4002 - APRIL 2000

How is the current held reasonably constant in MIG welders?

I've got everything I need to put one together, but I can't figure out what is needed to achieve the constant current requirement. Transistors, SCRs, or what? And with what circuitry?

There are several ways to control the current in a welder. Older welders that were made in the 50s used the carbon block method which was nothing more than a very large variable resistor, in line with the transformer. According to Ohm's

Law, when you vary the voltage of any circuit, the current must follow, and vice versa.

Some welders use the "variac" method of a variable transformer where the current remains constant while the voltage output varies within the transformer, as you adjust the knob. A third method is the chopper method using a SCR circuit [or three] similar to a light dimmer circuit commonly used in household lighting.

The cost factor of a control circuit will vary greatly based upon several factors.

The most expensive method will probably be the variac transformer, then the carbon block method followed by the solid-state system which is by far the cheapest method. But there is a drawback to this order of cost and that is duty cycle, ripple, and starting current or surge.

If you chop the circuit using the SCR method, you then need to get out the ripple caused by the chopping action of the circuit, and that requires very large caps and chokes which can, in some instances, raise the price significantly back up.

Shopping around at a surplus store should control this added expense and still make the project a reasonable alternative.

You can also manufacture your own choke because they are crude and large consisting of nothing more than 10 or 20 feet of 1/2" copper bar stock formed around a 3" or 4" form. Testing them, however, requires some experimenting on your part and you can even place a variable tap on the choke for adjustable performance.

The next greatest cost of the control circuit depends upon your input or primary transformer. Is it single phase or three? If it's three phase, then triple all of your costs because you have to control each of the phase windings to a matched and balanced tolerance of 5% or less.

When you get into three-phase

control, the circuit has to be precisely balanced at each output level because of overheating problems. If the adjacent phase windings are out of balance with each other, they tend to fight each other and produce excess heat instead of usable current.

Creating or purchasing a control circuit that keeps this balance through-out the power range can add significantly to the cost of any design. Because not only do you have to have the balance, each of the 10 steps also have to be balanced to the 5% requirement which requires setting up, testing, and calibrating each of the 10 stages for each of the three-phase windings.

This requires one fixed resistor and two potentiometers at each stage, times 10.

You have to calibrate each step not only to the tolerance, but also to the preset voltage which translates into the amperage steps that you require. Depending on the size of your welder, the steps will control anywhere from 10 to 20 amps per stage but, if your welder is a large one, you may need a 15- or 20-step switch in order to cover a wider usable range.

Most 150 amp [or less] welders have at least a 10-step controller which gives you a 30 amp minimum, followed by a 10 or 12 amp increase between settings. However, you can add as many steps as you like.

On the single-phase welder, this multiple switch is replaced by a potentiometer which gives you a [almost] linear sweep which means that the current is infinitely adjustable between the low and highs. Overrate your SCRs by at least 50% of the maximum amperage used by the welder, and use "more than adequate" heatsinks and fans for a performance that won't vary in time, as things start to heat up.

You can purchase a full sweep three-phase controller [non-step] which consists of matched pairs of SCRs with complimentary matched and balanced potentiometers. These give you a linear and infinite variable, but these units usually cost upwards of several hundred dollars.

You can also purchase multiple variacs in pairs, triples, and quad configurations and they are matched and balanced to each other via a single shaft, but with the amperage requirements that you need to run a welder, this can easily exceed \$500.00.

The third method of the variable carbon block has been phased out mostly and I'm not even sure where to purchase such a large element of the size and wattage that you would need.

However, a single large element is all that is required because it is placed on the output lead going to the wire feeder cable [spool] and thus only one controller is required.

I'm sure they still make them, but with their usage being mostly replaced by solid-state devices these days, the number of manufacturers have diminished over the years and so the price accordingly has gone up. Last time I saw one in a catalog was many years ago, and it was around \$200.00 for a 200 amp unit.

Chris Bieber, CA

ANSWER TO #4005 - APRIL 2000

I need information on cable TV cable connectors. I am not sure how to tell the difference between various types of CATV cables and their connectors.

I have a 15 ft. cable [not sure what kind] running from a wall jack. I attempted to install a RadioShack CF-56 connector to one end so I could hook it up to my VCR. After crimping and screwing the cable to the back of my VCR, the signal was dirty.

There are only two common CATV cables used in homes, and they are RG-6 and RG-59.

The cable connectors are called 'F' connectors, and there is a different 'F' connector for each cable. You should find the cable type printed on the side of the cable. You can also tell from the cable dimensions, but the dimensions vary with manufacturers and materials.

RG-6 has an outside diameter of 0.266 inches and the inner dielectric diameter is about 0.180. RG-59 has an outside diameter of 0.242 and a dielectric diameter of 0.146.

The dielectric thickness is the quick way to tell. If you compare them side by side, the RG-6 dielectric looks much bigger.

The F connectors for the different cables must accommodate the different dielectric sizes, so the RG-6 connector has a bigger through-hole than the RG-59 connector. The inner dielectric should fit snugly. If it is loose or does not go in, then you have the wrong cable/connector.

RadioShack is good about providing assembly instructions on the blister pack, many vendors don't. The inner dielectric should be flush with the seating face of the connector.

The connector may or may not be responsible for your poor reception. If you can jiggle cable close to the connector and get good reception, then it is probably the cable and the connector — especially if the cable has been flexed a lot or has a sharp bend.

You might also notice a bubble on the cable jacket close to the connector. In that case, cut a few inches off the end of the cable and put a new connector on. If jiggling the connector does not improve reception, then there is a problem further up the cable.

Gerald Roylance
Mountain View, CA

Easy To Use!

Microcontroller Power!

Want to add advanced features like floating point math or PWM to your next **Basic Stamp, PIC, SX, HC11**, or other project? Supercharge your design today with PAK coprocessors from AWC.

Let PAKs energize your next microcontroller project:

- ▶ PAK-II—Floating Point Math
- ▶ PAK-V—PWM
- ▶ PAK-VI—PS/2 Keyboard Interface

Features

- ▶ 32-bit floating point math (PAK-II)
- ▶ 8 channels of PWM (PAK-V)
- ▶ Read PS/2 keyboards or mice (PAK-VI)
- ▶ Connects with as few as 1 or 2 wires
- ▶ Data sheets online

AWC
310 Ivy Glen
League City, TX 77573
(281) 334-4341
(281) 754-4462 (fax)


Perfect for data logging, averaging, engineering unit conversion, lamp or motor control, D/A and more.

Visit our Web site now for free tools and projects!

www.al-williams.com/awce

HAM GEAR FOR SALE

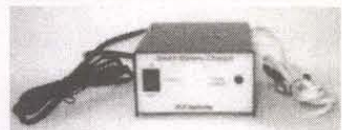WANTED: MILITARY capacitors, resistors, transistors, diodes, ICs, semi's, etc. Please fax/E-Mail excess lists & RFQs 818-769-1002 fax 818-769-1084. electrains@earthlink.net & <http://www.militarycomponents.com>




THE SMART BATTERY CHARGER for lead acid or gel cell batteries. Can be left connected to the battery **INDEFINITELY**, will not overcharge! Standard kit is 12V @ 1 amp. This kit is 100% complete. For the kit order #150-KIT at \$59.95. For an assembled and tested unit, order #150-ASY at \$79.95. CA residents add 7.75% sales tax. Add \$6.50 per unit shipping. MC/VISA accepted. A&A Engineering, 2521 W. La Palma #K, Anaheim, CA 92801. 714-952-2114, FAX 714-952-3280.

PRACTICAL ANTENNA HANDBOOK, by Joseph Carr. The most popular book on antennas ever written, widely known as "the antenna builder's bible." This *Third Edition* is a work for anyone with an interest in antennas, from the newest of novices to the most experienced engineer. This empowering book gives you all kinds of projects and material that explains why what you did works. Only \$49.95! **10% discount to Nuts & Volts subscribers.** Call 1-800-783-4624 to order using Visa or MasterCard.

SECRETS OF RF CIRCUIT DESIGN From Joseph Carr, one of today's most respected electronics authors, comes this pragmatic, intermediate-level guide to designing, building, and testing all types of radio frequency circuits. Filled with functional projects that demonstrate the principles of RF circuits. Only \$29.95! **10% discount to Nuts & Volts subscribers.** Call 1-800-783-4624 to order using Visa or MasterCard.

A GPS-based frequency standard. This highly accurate frequency standard is something you can build, thanks to the efforts of Brooks Shera W5OJM. Using the once-per-second timing pulse available from the GPS system to control a VCXO, you can achieve an accuracy of a few parts in 10-cya -2;cp3>11<va2:cp7>, about 10,000 times better than the WWV zero beat method. See July 1998 QST for details. Circuit board available. Order #217-PCB, \$19.95 plus \$1.50 S/H. CA residents must add 7.75% sales tax. A&A Engineering, 2521 W. La Palma, Unit K, Anaheim, CA 92801; 714-952-2114. mr2

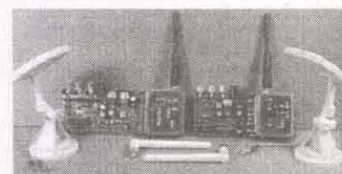

ATV-2400 and ATV-1200 2.4/1.2 GHz; 35/75 mW, 8 channels for legal ham use. **\$159 per pair**, 1,000 watts maximum allowed by FCC. Power amplifiers, compact size, 1 watt output with SMAs, **\$149.** Contact dealers through **EzATV** www.4atv.com

HAM GEAR WANTED

CB — SCANNERS

HALCON COMMUNICATIONS
Wholesale only: Cobra, Uniden, Midland, Galaxy, CTE, Super Star, Kenwood, Yaesu, Icom. Free catalog. Free call 1-800-683-6999.

SALES & SERVICE: CB equipment, modification kits, meters, antennas, mics, radios, transistors, repairs & hard-to-find items. Complete list \$4. D&R Electronics, 10 Park St., Thomaston, CT 06787. 860-283-9492 or RTed821836@aol.com

CB MODIFICATIONS! Frequencies, books, kits, high-performance accessories, plans, repairs, amplifiers, 10-meter conversions. The best since 1976! Catalog \$3. CBCI, Box 1898NV, Monterey, CA 93942. www.cbciintl.com

240+ CHANNEL CB/HAM/COMMERCIAL radios: AM/FM/SSB/CW export/domestic: RCI, Motorola, Uniden, Cobra, Alinco, Kenwood. Mics, antennas, linears, meters, books, night scopes, and tons more stuff! Catalog \$3. MAXTECH, Box 8086, New York, NY 10150. 718-547-8244.

CB MODIFICATIONS, repairs, new products, CB radios, exports, scanners, power supplies, microphones, amps, antennas, more! 15 yrs. same location, 6 page picture price sheets \$1 (refundable). Galaxy, Box 1202, Akron, OH 44309. <http://members.aol.com/galaxyelc>

Sell Nuts & Volts in your store! Contact us for complete details.




phone 909-371-8497
fax 909-371-3052
E-Mail distributors@nutsvolts.com

Electronics made easy & affordable **velleman**

NEW

PERSONALSCOPE™ HPS5

The Velleman **PERSONAL SCOPE™** is a portable fully-functional **oscilloscope**. At the cost of a good multimeter it gives you the best possible **value for the money**. The **PERSONAL SCOPE™** provides you with the **high sensitivity** (down to 5mV/div) often missing in higher or similarly priced units. Together with the other scope functions it makes this the ideal tool for students, hobbyists and professionals.

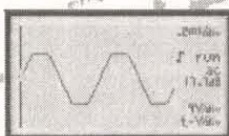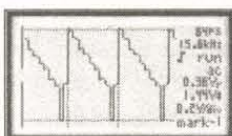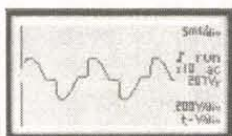

SPECIFICATIONS:

- Maximum sample rate: 5MHz
- Input amplifier bandwidth: 1MHz (-3dB at 1V/div setting) 11Mohm //20pF (standard probe)
- Vertical resolution: 8 bit (6 bit on LCD)
- LCD Graphics: 64 x 128 pixels
- dBm measurements: From -73dB tot +40dB (up to 60dB with X10 probe) ±0.5dB
- True rms AC measurement: 0.1mV to 80V (400Vrms with X10 probe) 2.5% accuracy
- Time base: 20s. to 2ns/div in 22 steps
- Input sensitivity range: 5mV to 20V/div in 12 steps (up to 200V/div with X10 probe)
- Supply voltage: 9VDC / min 300mA adapter
- Batteries (in option): Alkaline type AA (5 pcs required) NiCd/NiMH rechargeable
- Battery life: Up to 20 hours with Alkaline batteries
- Safety: Meets IEC1010-1 600V CATII, pollution degree 1
- Dimensions: 105 x 220 x 35mm (4.13 x 8.66 x 1.38")
- Weight: 395g (14oz) (excl. batteries)



OPTIONS:

- Insulated measurement probe x1 / x10: PROBE605
- Adapter for 110VAC: P5905USA

\$199.95

Probe not included



SERVICE & DEVELOPMENT



CAR DIAGNOSTICS



AUDIO TROUBLE SHOOTING

velleman

7415 Whitehall Street Suite 117
Fort Worth, TX 76118
(817) 284-7785 F: (817) 284-7712
www.velleman-kit.com email: velleman@earthlink.net

Questions ? Contact us for a list of US distributors or to get your **FREE** catalogue

MUSIC & ACCESSORIES

COMPUTER HARDWARE

COMPUTER CASES \$22, 450MHz bare-bone systems from \$250. 486 computers \$99. Pentiums from \$199. Motherboards \$20, 1.44/1.2 floppies, speakers \$10. 714-778-0450.


PC CABLES: <http://www.cablesusa.com> 100s of hard-to-find new cables and parts, pictures, free technical information. Low prices, RS232, SCSI, keyboard, network, VGA, Cat-5, USB, Firewire, fast secure online ordering & browsing. 954-418-0817.

DEC EQUIPMENT WANTED!!! We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), DSD, Datability, Dilog, other DEC compatibles, and Computer Output Microfilm (COM) units. Please call for a quote or fax us your equipment list. We buy, sell, and trade. **KEYWAYS, INC.**, 937-847-2300 OR fax 937-847-2350.

LOOKING FOR cheap clone PC parts that actually work? Call UTWE for CD-ROMs, hard drives, disk controllers, video cards, mainboards CPUs, etc. We also have network stuff like cables, cards, adapters, hubs, etc. NEW tape drives 1.4G \$30 ea. 1 (or 2) meg PCI video cards \$10 (or \$15). Don't forget to check our auctions on Ebay! Seller name JohnUTWE. Remember, today we have it, tomorrow we don't! So E-Mail or call now. Case of 7 nearly new Epson keyboards, \$21 (\$3 ea.). There are other deals too! For the latest dealsheets send an E-Mail to dealsheets@utwe.com or call 626-930-1121 (10am-5pm Pacific) or fax 626-930-1123. E-Mail: sales@utwe.com

ISO7816 PROGRAMMER built \$150. Kit \$125. No software. Blank smart cards \$20.00 or 8/\$100. Tony 419-385-3100.

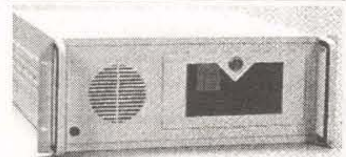WE CARRY a variety of cables, switch boxes, accessories, and adapters to connect PCs, printers, Mac's, networks, telecommunications, and audio/video equipment. We offer: custom cables, free catalogs, and same day shipping on most orders. Visit our web-site at www.rogerssystems.com or call 1-800-366-0579.



19" RACKMOUNT ATX PC chassis, \$169 (with ad). 972-242-8087, www.cti-tx.com



LOW-COST 12-BIT A/D KITS. \$59 LPT: Analog! PC printer-port interface acquires 8 analog signals. Also features two 12-bit D/As, current sources for sensor excitation and digital I/O lines. QuickBasic and VB software included. 1-channel A/D only \$39. <http://www.rgn.net/~adnav/> or E-Mail: adnav@rgn.net

EVERYTHING NEW w/warranty! Motherboards with CPU 500MHz \$195, monitors 15" \$125, Pentium systems from \$195. Modems, multimedia kits, scanners, hard drives 420/850/1280 megabyte \$25, 15 gigabytes \$120. Color printers \$65. Call 714-778-0450. E-Mail: ccl@surfside.net

COMPUTER SOFTWARE

FREE IBM DISK CATALOG of quality Shareware and CD-ROMs. **MOM 'N' POP'S SOFTWARE** <ASP>, PO Box 15003-N, Springhill, FL 34609-0111. 352-688-9108. momnpop@webcombo.net

FMSTUDY32 FM, LPTM allocation studies. Manage FCC database on your PC! Manual included, \$39.95. Demo, info, special Web pricing at <http://members.xoom.com/fmstudy>

CAM & MOTION SW/HW: Z-trace, PCB toolpath. Plotcam motion control, step drivers. www.megabits.net/ddt FAX 321-452-7197, 321-459-2729. heater@megabits.net

TIME SAVING utilities! Creative Win98 software. Visit: <http://www.rascom1.com> today for free downloads. Questions? E-Mail: rascom@mediaone.net

UNDERGROUND CDs: Hacking, phreaking, free energy, health, anti-gravity, time travel, way-cool electronics projects, music & books. <http://www.hi-techstuff.com>

LIQUIDATION WINDOWS 95/98, Office suites \$10-69. 1,000 games 10 pack \$25. How to Windows 95 \$5, Windows 98 book \$10. 714-778-0450.

COMPUTER EQUIPMENT WANTED

WANTED: FOR historical museum, pre-1980 microcomputers, magazines, and sales literature. Floyd, VA 24091-0341 (540-763-3311/540-382-2935).

Tired of Expensive Inkjet Cartridges ? Save 90% on Inkjet Inks !

Printer (Call for Others Not Listed!)	# of Refills		Cost/Refill		Kit Price	
	Black	Color	Black	Color	Black	Color
HP 500 Series, 400, Officejet 300, 350, Fax	7	14	4.71	2.85	32.95	39.95
HP 600 Series, Officejet 500, 570, 600	7	14	4.71	3.21	32.95	44.95
HP 820C, 855C, 870C, 1000C, 1150C, Copier 120, 210	6	12	6.67	3.33	39.95	39.95
HP 720C, 722C, 712C, 880C, 890C, 895C 1120C, 1170C	6	12	6.67	3.75	39.95	44.95
Canon BJC-100, 200, 210, 240, 250 Apple SWriter 1200, 1500	14	20	2.15	2.00	29.95	39.95
Canon BJC-4000 Series, C2500, C3000, C3500, C5000	60	60	0.50	0.67	29.95	39.95
Canon BJC-6000	14	8	2.85	1.67	39.95	39.95
Canon BJC-600, 610, 620 Apple SWriter Pro	20	13	1.50	3.07	29.95	39.95
Epson Stylus Color, Color Pro, Pro XL	12	12	2.50	3.33	29.95	39.95
Epson Stylus Color II, IIs, 1500 (Black)	15	15	2.00	2.66	29.95	39.95
Epson Stylus Color 500, 200	20	17	1.50	2.35	29.95	39.95
Epson Stylus Color 400, 600, 800, 850, Photo / 440, 640	20	17	1.50	2.65	29.95	44.95
Lexmark JP 1000, 1020, 1100, ExecJet II, IIC, Medley 4C	10	17	3.00	2.35	29.95	39.95
Lexmark JetPrinter 3200, 5700, 5000, 7000, 7200,	15	17	2.67	2.35	39.95	39.95
Compaq IJ700, IJ900, Xerox XJ8C, XJ9C	15	17	2.67	2.35	39.95	39.95
Xerox Home Center 450C, XJ6C Inkjet	22	12	1.36	3.33	29.95	39.95

SAVE 30 - 50% on New Compatible Cartridges!

Printer	BLACK CARTRIDGE	COLOR CARTRIDGE
(CALL FOR OTHERS NOT LISTED !!)		
Canon BJC-4000 Series, C2500, C3000, C3500, C5000	\$5.50	\$12.95
Apple StyleWriter 2400, 2500	\$5.50	\$12.95
Canon BJC-600, 610, 620 Apple StyleWriter Pro	\$4.95 (9cc)	\$4.95 @ (9cc)
Hi-Capacity Canon BJC-600, 610, 620	\$5.95 (15cc)	\$5.95 @ (12cc)
Canon BJC-70, BJC-80	\$9.95 (3-pak)	\$14.95 (3-pak)
Epson Stylus Color, Color Pro, Pro XL	\$10.95	\$16.95
Epson Stylus Color II, IIs, 200	\$11.95	\$16.95
Epson Stylus Color 400, 500, 600, 800, 850, 1520, Photo	\$11.95	\$16.95
Epson Stylus Color 440, 640, 660, 740, 900	\$11.95	\$16.95
Epson Stylus Color Photo 750, 1200	\$11.95	\$17.95

- BULK Inks, Refill Accessories
- Glossy card stock & Coated Paper
- School & Government PO's Welcome
- 2 - 3 Day Shipping

Quality Inks for:

HP • Epson • Lexmark
Canon • Apple • DEC

Call or see us online!

Monday - Friday

7:30 - 4:30 PST 10:30 - 7:30 EST

Inkjet

Southwest



www.inkjetsw.com

(480) 668-1069 Fax

1-800-447-3469

(480) 668-0959



SURVEILLANCE

Room Transmitters from \$30.00
Telephone Transmitters . from \$29.00
UHF Pen Transmitters \$299.00
Crystal-Controlled
Transmitters from \$75.00
UHF Telephone Transmitter
& Receiver & Recorder . . \$299.00

Catalogues \$5.00

And much more — too much to list here!

E-Mail: BitzTechnology@Compuserve.com

WANTED: HEATHKIT resistor substitution box. Will pay. Hugh M. Adams hugh@emcst.com or 850-864-2414. 1011D Hondo Ave., Ft. Walton Beach, FL 32547-3823.

DEC EQUIPMENT WANTED!!! We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), DSD, Datability, Dialog, other DEC compatibles, and Computer Output Microfilm (COM) units. Please call for a quote or fax us your equipment list. We buy, sell, and trade. **KEYWAYS, INC.**, 937-847-2300 OR fax 937-847-2350.

WANTED: MILITARY capacitors, resistors, transistors, diodes, ICs, semi's, etc. Please fax/E-Mail excess lists & RFQs 818-769-1002 fax 818-769-1084. electmatind@earthlink.net & <http://www.militarycomponents.com>

TEST EQUIPMENT

FEITEK PROVIDES repair, calibration and traceable certifications of test equipment. Free estimates. We buy, sell and trade all makes of test equipment. Visa and MasterCard accepted. Check out our inventory and specials at WWW.FEITEK.COM 2752 Walton Road, St. Louis, MO 63114, 314-423-1770.

KENTRONIX TEST EQUIPMENT SPECIALS. Check our WEB site at <http://www.kentronix.com> for monthly specials. We are also looking to buy test equipment, coaxial and waveguide components, manuals, etc. Contact Brian at 732-681-3229 or FAX 732-681-3312. E-Mail: brian@kentronix.com

DEC EQUIPMENT WANTED!!! We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), DSD, Datability, Dialog, other DEC compatibles, and Computer Output Microfilm (COM) units. Please call for a quote or fax us your equipment list. We buy, sell, and trade. **KEYWAYS, INC.**, 937-847-2300 OR fax 937-847-2350.

POOR MAN'S Spectrum Analyzer/Monitor Receiver Kit. 2 to 1,700 MHz. Basic kit only \$98. Now available with switched resolution filters, tracking generator and direct digital frequency readout. Works with ANY scope or IBM compatible computer. Send stamped envelope for details. Science Workshop, Box 310B, Bethpage, NY 11714. <http://www.science-workshop.com>

WANTED: MILITARY capacitors, resistors, transistors, diodes, ICs, semi's, etc. Please fax/E-Mail excess lists & RFQs 818-769-1002 fax 818-769-1084. electmatind@earthlink.net & <http://www.militarycomponents.com>

BROWSE OUR Web site and check out the "monthly special." TDL Technology, Inc., www.zianet.com/tld

AFFORDABLE HP power sensor repair! Most 8481As repaired for \$305 or less. We also handle 478As and many others. Call or fax for more information. Willamette RF, Inc., 541-754-7226, FAX 541-753-4629.

NEW, FASTER, POCKET TEST-BENCH, tiny, inexpensive, RS-232 instrument, with scope, logic analyzer, counter, generator, infrared modes. Oricom Technologies, 303-449-6428. www.sni.net/~oricom

MOTOROLA SYNTOR PROGRAMMER. Regular, XX and tone adapters for sale. From \$350 plus S&H. 212-544-8970. digicomkit@aol.com

TEKTRONIX 475A, 250 MHz dual channel/dual time base oscilloscope with piggyback DMA digital multimeter. Looks & works great. Original owner's manual. Advertised elsewhere for \$999. Buy it for \$700. 423-877-9406.

KROHN-HITE 3700 variable multi-function electronic filter .02Hz to 20KHz. Excellent \$500. Al Ross, 425-775-8853.

VISIT US ON THE WEB AT:
<http://www.candhsales.com>
email: candhsales@earthlink.net
C and H SALES COMPANY
2176 E. Colorado Blvd. • Pasadena, CA 91107
TOLL FREE:
1-800-325-9465

FREE
148 PAGE
CATALOG!

C & H SALES COMPANY HAS BEEN IN BUSINESS FOR OVER FIFTY YEARS.
WE'RE THE BEST SOURCE FOR GREAT BUYS ON ITEMS LIKE THESE - AND MORE!

ELECTRONIC COUNTER

HEWLETT PACKARD, Model 5328A. Universal counter. Usable to 100 MHz, 100 ns single shot resolution. Has frequency, period, period average, ratio, totalize, scale functions. Two input channels provide individual slope, polarity and level settings. Has 9 digit LED readout. Input power 100-240 VAC 48-66 Hz 100 VA max. Dimensions: 17" wide x 17-1/4" deep x 3-1/2" high.

Stock #TE9808

\$250.00



SOLA CONSTANT VOLTAGE TRANSFORMER

SOLA ELECTRIC, #93-13-150. Harmonically neutralized constant voltage transformer. Rated at 500 watts. Input voltage 95 to 130 VAC 60 Hz. Output voltage 120 VAC. This unit is designed for rack or bench mounting. The meters on the front panel indicate output current and input/output voltage. A toggle switch is provided for selection of input or output voltage. The input voltage is connected at the rear of the unit via a covered electrical panel. Two standard 3-wire grounded electrical outputs are supplied on the front and rear panels. Dimensions: 19" wide x 14-1/4" high x 10-1/4" deep. Weight 59 lbs.

Stock #STR9900

\$225.00

MILLIOMETER

HEWLETT PACKARD, Model 4328A. Designed to measure very low resistances. Measurement range 1m ohm to 100 ohms. Resolution 20 u ohms. Analog meter readout. Ideal for measuring contact resistance of switches or relays. This unit is also useful for measuring the resistivity of semiconductor devices. (Requires special 4 terminal probes which are not supplied, but probably are available from Hewlett Packard.) Power input: 115-230 VAC 48-66 Hz, 5 VA max. Dimensions: 5-1/8" wide x 11-1/2" deep x 6-1/2" high.

Stock #TE9812

\$200.00



PRECISION LINEAR WAY BEARING

This assembly consists of a linear ball bearing track rail and two ball bearing slider elements. 280mm long with 14 countersunk holes for rail mounting. Stainless steel.

Stock #BR2002

\$57.50

DIAPHRAGM PUMP

THOMAS INDUSTRIES Single diaphragm oil-less pump. Motor rated 115 VAC 60 Hz. Pump output is 0.69 cfm free air. Max. continuous operating pressure 20 psi.

Stock #PC9904

\$49.50



☒ Master Charge ☒ Visa ☒ American Express ☒ Discover

Call us first if you have surplus inventories of electronic, optical, or mechanical items for disposal

WE BUY & SELL!

Write in 34 on Reader Service Card.

Miniature Transmitters and Receivers

2 Button / 3 Channel Transmitter



RF300T

1....\$22.95
5....\$19.95 ea
10....\$16.95 ea

RF300XT

1....\$25.95
5....\$22.95 ea
10....\$19.95 ea

- 300' (XT), 150' (T) Range
- Frequency: 318 MHz
- 59,049 Settable Security Codes
- 12 Volt Battery and Keychain Included
- Current Draw: 4.8 ma
- Fully Assembled in Case
- Dimensions: 1.25" x 2.0" x .5"
- Push both buttons for the 3rd Channel
- Slide Button Cover Included

4 Button / 15 Channel Transmitter



RF304XT

1....\$27.95
5....\$24.95 ea
10....\$21.95 ea

- 250' Range
- Frequency: 318 MHz
- 6,561 Settable Security Codes
- 12 Volt Battery and Keychain Included
- Current Draw: 4.6 ma
- Fully Assembled in Case
- Dimensions: 1.35" x 2.25" x .5"
- Push combination of buttons to achieve up to 15 channels

2-4 Data / 3-15 Channel Receivers



RF300RL

RF300RM

RF304RL

RF304RM

1....\$27.95
5....\$24.95 ea
10....\$22.95 ea

- Compatible with 300/4 Transmitters
- 11-24 volts DC Operating Voltage
- 13 ma. Current Draw
- Latching (L) or Momentary (M) Output
- Kits Available (subtract \$5.00 ea.)
- Dimensions: 1.25" x 3.75" x .5"
- 2 (300) / 4 (304) Output Data Lines
- Binary to Dec / Hex Converter can achieve up to 15 channels

- Alarm Systems
- Garage / Gate Openers
- Lighting Control

- Magic Props
- Medical Alert
- Monitoring Systems

- Industrial Controls
- Surveillance Control
- Motor Control

- Schematics Available
- Receiver Board Layout Available
- Custom Design Consulting Available

Visitect Inc.

(510) 651-1425 Fax: (510) 651-8454
P.O. Box 14156, Fremont, CA 94539

Email: Support@Visitect.Com
Visa / Mastercard, COD

Write in 35 on Reader Service Card.

Nuts & Volts Magazine/May 2000 39

IFR 1500 COMMUNICATIONS SERVICE MONITOR WITH SPECTRUM. This unit is BRAND NEW from the factory. I just purchased this two months ago from IFR. It was in their display case and never used! It has been calibrated by IFR. This unit came standard with everything. Spectrum analyzer, modulation meter, frequency error meter, watt meter, sinad meter, DCS, CTCSS, all tones encode and decode, oscilloscope, and on and on. The CRT is perfect. All manuals included. Price \$6,500. Call 949-443-9322 all hours.

MOTOROLA R2001B monitor. Excellent working condition. \$2,200. 210-859-0881 or 210-699-9360.

TEST EQUIPMENT technicians needed: calibration and repair techs. Three full-time openings. We are located in Broomfield, Colorado, between Boulder and Denver. We perform electronic and physical/dimensional calibrations. Please send resume to irl@calibration.com

TEK 454A \$275, Wavetek 114 \$145, B&K 3030 LN \$195, Logical Devices Gangpro 8+ \$295, Spectronics 2000 Lg. PROM eraser \$145, HP 428B \$175, HP 400H \$45. Pikul & Associates 636-937-0335.

Subscribe to Nuts & Volts Today!
Call 1-800-783-4624
and Use Your Visa or MasterCard.

SECURITY

CONSUMERTRONICS 120+ exciting manuals: Electronics, computers, Internet, phones, energy, radionics, financial (including stocks), crime-fighting, security, survival, phenomena, **SPECIAL PROJECTS.** Catalog \$3. PO Box 23097, Albuquerque, NM 87192. www.tsc-global.com

SURVEILLANCE-COUNTERSURVEILLANCE: I buy and sell used equipment. Steve 410-879-4035.

STOP THEM from listening in or recording your telephone conversations with the **TELEPRIVACY-PLUS.** Send \$49 to Vakis, 1402 Pine Ave., Niagara Falls, NY 14301.



COUNTER-SURVEILLANCE=\$250 HR! Electronic eavesdropping is unbelievably widespread! Are you sure you're safe? Learn how others (without prior experience) earn **\$250 HR** in the fascinating field of COUNTER-SURVEILLANCE! For FREE catalog call: **1-800-732-5000.**

CCD Camera Cookbook

The CCD Camera Cookbook \$29.95

Here's a great book that tells you how to build your own astronomical CCD camera! It includes several designs, a computer disk with special programs and test routines. Cameras are designed to work with PC-compatible computers. "With a CCD camera on your telescope, a bigger universe is yours."

LEVITRON

"The Amazing Anti-Gravity Top"

This spinning top floats in mid air, supported by opposing magnetic forces. Includes floating top, levitron magnetic base, assortment of adjustment weights, lifter plate, levelling shims, and instructions. It takes some practice and a lot of patience to keep the top afloat, but the results are truly amazing!

Levitron Floating Top \$39.95

ANIMAL SOUNDS PIANO KIT

\$29.00

This project kit has ten keys for playing notes of the scale and eight buttons to select the sounds associated with each note. Select the piano mode and the kit will synthesize piano sounds for each key. OR select one of seven different animal voices including cat, dog, pig, bird, chicken, duck, and sheep. Old MacDonald never had a choir like this! The circuit features an auto power-off function, a demo mode, and easy step-by-step instructions. Requires 2 AA batteries not included.

Lightwave 2000 Flashlight

\$29.95

Four super-bright white LEDs replace the bulb you'd find in a traditional flashlight, providing a long-lasting high-intensity light. LED lights mean your flashlight will last about 14 times longer than a regular flashlight, and these flashlights are waterproof and shockproof. Ideal for short-range use in cars, planes, etc. Flashlight requires 3 AA batteries (included). Manufacturer's limited lifetime warranty even includes the LED lights!

Geophone

vibration sensing kit

Detect a fly stomping across the desk! Well maybe not that sensitive, but almost.

These vibration sensors made by Geosource® were used in oil exploration to determine geological statistics. They are made with a magnet suspended in a coil and are very sensitive to vibration. Compact size, the unit measures approx. 1.6" high and 1.2" dia. The kit includes a geophone vibration sensor along with parts to build a basic detector that will light an LED. In addition we include a schematic that will show you how to operate a relay. The sensitivity is adjustable, so you can set it to detect elephants and other small creatures. Similar units were used by our armed forces to detect enemy troop movements...the perfect device to alert you to the pitter patter of little Leroy's feet! Unit sensitivity can be set high enough to detect a business card dropped on a table, and we've made it work with vibrations up to 40 feet away! Earthquake or Aunt Agatha...you decide! It's a fun gadget with many uses.

COMPLETE GEOSOURCE KIT...\$9.95
GEOSOURCE UNIT ONLY...\$7.95

LIGHTED HEADSET MAGNIFIER \$34.95

You asked for it!!! Now we have our popular lighted headset magnifier with 4 changeable magnifying LENSES! This is a HANDS-FREE way to see little tiny parts as you work on them without having to be a contortion artist with a soldering iron! The headband style magnifier features a SEMI-ADJUSTABLE CENTER LIGHT (4 AAA BATTERIES NOT INCLUDED) so you can add a little light to the area without clutching a flashlight under your chin! The adjustable headband fits comfortably around your head, and the "goggles" pull down over your eyes for easy visibility. FEATURING 1.2X, 1.8X, 2.5X, and 3.5X magnifying LENSES plus a flip-down MAGNIFIER LENS slot allowing you to load two lenses into the headset for added magnification. (ONE REMAINS IN PLACE, the OTHER can be flipped up OR DOWN AS NEEDED.)

AMAZING MINI MICRO FM RADIO! \$7.50

Much lighter than a heavy jam box with really good sound! This tiny radio (1.5"x1.06"x0.38") has a seek button, reset control, and an on/off switch.

Personal listening has never sounded better! Ideal for ballgames, studyhall, and workouts. Battery and nugget style earphones included.

Lighted Screwdriver Supertool! \$9.95

At first glance, this appears to be an ordinary screwdriver, but press a button on the base and two lights illuminate the area you are working on. Nifty, huh? But wait, there's more! The seven interchangeable bits are stored right there at the base of the screwdriver (6 storage slots) for easy access. No handles to unscrew or tool boxes to dig through. Hey, you ain't seen nothin' yet...remove the bit and the magnetic retrieval tool telescopes from the screwdriver shaft! Incredible!!! Of course, the comfort grip handle and rugged construction are icing on the cake! Definitely a "gotta have it" tool!

B/W 430 LINE CCD CAMERA with optional black low-profile swivel adjustable enclosure. Pin hole or Std. lens type. 6, 8, and 12mm lens are available. 1/3" CCD, 3.6mm/F2.0 lens included; 9-14 VDC, 0.08 lux, IR sensitive; 1.27" x 1.27" x 0.5" D pin-hole or 1" deep standard. Price @ 10 pcs., \$44 each. Enclosure: \$8; optional lens: \$18. Dealers welcome. MATCO, Inc. 1-800-719-9605. Fax 847-619-0852. E-Mail: sales@mat-co.com Website: www.mat-co.com

USE PC MONITOR AS SECURITY MONITOR. The VGA-801 accepts standard NTSC or PAL inputs for display on any existing VGA/SVGA computer monitor. Small compact size. Over 600 lines of resolution, twice that of standard TV monitor! \$69 each. Dealers welcome. MATCO, Inc. 1-800-719-9605; Fax 847-619-0852; E-Mail: sales@mat-co.com Website: www.mat-co.com

SALE! PS 102 SMOKE DETECTOR: Built-in pin hole CCD, lens size: 3.6mm. \$89. Matco, Inc., 1-800-719-9605 Fax: 630-350-9546. E-Mail: nsales@matco.com Web site www.mat-co.com

COLOR — LOW LIGHT CCD pin hole and standard lens available, only 1.27" x 1.27". \$129, enclosure \$10 extra. Sony sensor. Matco, Inc., 1-800-719-9605 Fax: 630-350-9546. E-Mail: nsales@matco.com Web site www.mat-co.com

SEEKING DISTRIBUTORS FOR SECURITY PRODUCTS. Matco, Inc., Schaumburg, IL 630-350-0299. www.mat-co.com


www.gatewayelec.com




8123 PAGE BLVD * ST. LOUIS, MO 63130 * (314)427-6116
9222 CHESAPEAKE DR. * SAN DIEGO, CA 92123 * (619)279-6802
2525 FEDERAL BLVD. * DENVER, CO 80211 * (303)458-5444
MAIL ORDERS CALL TOLL-FREE 1-800-669-5810
FAX ORDERS (314)427-3147

nr0400


THE FINE PRINT: PRICES SUBJECT TO CHANGE WITHOUT NOTICE * GATEWAY IS NOT RESPONSIBLE FOR PRINTING ERRORS * MASTERCARD, VISA AND DISCOVER ACCEPTED * YES, WE'LL TAKE YOUR CHECK -- SORRY, NO C.O.D.'s * \$10 MERCHANDISE MINIMUM ON MAIL ORDERS * SUPPLY OF SOME ITEMS IS LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * ALWAYS REMEMBER SOME ITEMS ARE LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/H

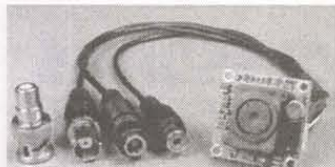

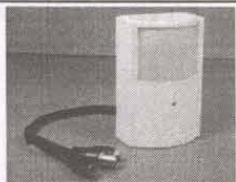B/W BOARD camera w/audio, \$49 @ qty 10, 1.27" x 1.27". Enclosure available for \$10. Matco, Inc., 1-800-719-9605 Fax: 630-350-9546. E-Mail: nsales@matco.com Web site www.matco.com



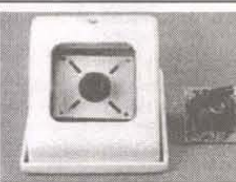SPECIAL! IC 113: PIR motion detector with audio! \$89 @ 5 pcs. Matco, Inc. 1-800-719-9605 Fax: 630-350-9546. E-Mail: nsales@matco.com Web site www.matco.com




UNIVERSAL WEATHERPROOF ENCLOSURE for board cameras, fits all 30-42mm color/back & white cameras, \$39 qty 1-4. Matco, Inc., Schaumburg, IL 1-800-719-9605 Fax: 630-350-9546. E-Mail: nsales@matco.com Web site www.matco.com



WIRELESS OBSERVATION SYSTEM w/built-in 5-1/2" monitor \$239. Matco, Inc., Schaumburg, IL 1-800-719-9605. E-Mail: nsales@matco.com Web site www.matco.com



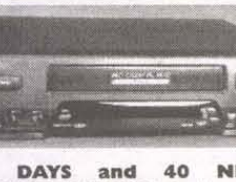QUAD SYSTEM displays 4 cameras simultaneously. Special price \$119. Matco, Inc., Schaumburg, IL 1-800-719-9605. E-Mail: nsales@matco.com Web site www.matco.com



40 DAYS and 40 NIGHTS RECORDER. TLR-6960 time lapse. Special price \$519. Matco, Inc., Schaumburg, IL 1-800-719-9605. E-Mail: nsales@matco.com Web site www.matco.com

Looking for a great value? Subscriptions to *Nuts & Volts* are only \$19 for a full year. Call Toll Free 1-800-783-4624 and use your Visa or MasterCard to order! OR visit our web site and take advantage of our special offer! www.nutsvolts.com



AS-1004, FCC approved. 2.4GHz transmitter & receiver with audio! Capable handling total of 4 wireless cameras, range: >300'. Built-in camera, 400 TV line. \$219 per system. Additional camera \$119 @ 10 pcs. Matco, Inc. 1-800-719-9605 Fax: 630-350-9546. E-Mail: nsales@matco.com Web site www.matco.com

SATELLITE EQUIPMENT

WANTED: MILITARY capacitors, resistors, transistors, diodes, ICs, semi's, etc. Please fax/E-Mail excess lists & RFQs 818-769-1002 fax 818-769-1084. electmatind@earthlink.net & <http://www.militarycomponents.com>

DTV INFORMATIONAL PACKAGE. LEARN ALL THE SECRETS. 1-888-447-7807.

FREE FLYER on DBS files, hacking, hardware info. Smart card socket \$5 ea. New Atmel 89C52 \$10 ea. Bill 1-800-879-9657.



FREE BIG dish catalog. Low prices! Systems, upgrades, parts, and "4DTV". Skyvision, 1010 Frontier Dr., Fergus Falls, MN 56537. www.skyvision.com Call 1-800-543-3025.



Doppler Direction Finder

Track down jammers and hidden transmitters with ease! This is the famous WAZEBY DF'er featured in April 99 QST. Shows direct bearing to transmitter on compass style LED display, easy to hook up to any FM receiver. The transmitter - the object of your DF'ing - need not be FM, it can be AM, FM or CW. Easily connects to receiver's speaker jack and antenna, unit runs on 12 VDC. We even include 4 handy home-brew "mag mount" antennas and cable for quick set up and operation! Whips can be cut and optimized for any frequency from 130-1000 MHz. Track down that jammer, with that fox hunt, zero in on that downed Cessna - this is an easy to build, reliable kit that compares most favorably to commercial units costing upwards of \$1000.00! This is a neat kit!!
DDF-1, Doppler Direction Finder Kit \$149.95

Wireless RF Data Link Modules

RF link boards are perfect for any wireless control application; alarms, data transmission, electronic monitoring...you name it! Very stable SAW resonator transmitter, crystal controlled receiver - no frequency drift! Range up to 600 feet, license free 433 MHz band. Encoder/decoder units have 12 bit Holtek HT-12 series chips allowing multiple units all individually addressable, see web site for full details. Super small size - that's a quarter in the picture! Run on 3-12 VDC. Fully wired and tested, ready to go and easy to use!
RX-433 Data Receiver..... \$16.95 TX-433 Data Transmitter..... \$14.95
RXD-433 Receiver/Decoder..... \$21.95 TXE-433 Transmitter/Encoder..... \$19.95

World's Smallest TV Transmitters

We call them the 'Cubes'.... Perfect video transmission from a transmitter you can hide under a quarter and only as thick as a stack of four pennies - that's a nickel in the picture! Transmits color or B&W with fantastic quality - almost like a direct wired connection to any TV tuned to cable channel 59. Crystal controlled for no frequency drift with performance that equals models that cost hundreds more! Basic 20 mW model transmits up to 300' while the high power 100 mW unit goes up to 1/4 mile. Their very light weight and size make them ideal for balloon and rocket launches, RC models, robots - you name it! Units run on 9 volts and hook-up to most any CCD camera or standard video source. In fact, all of our cameras have been tested to mate perfectly with our Cubes and work great. Fully assembled - just hook-up power and you're on the air! One customer even put one on his dog!
C-2000, Basic Video Transmitter..... \$89.95 C-2001, High Power Video Transmitter..... \$179.95

CCD Video Cameras

Top quality Japanese Class 'A' CCD array, over 440 line resolution, not the off-spec arrays that are found on many other cameras. Don't be fooled by the cheap CMOS single chip cameras which have 1/2 the resolution, 1/4 the light sensitivity and draw over twice the current! The black & white models are also super IR (Infrared) sensitive. Add our invisible to the eye, IR-1 illuminator kit to see in the dark! Color camera has Auto gain, white balance, Back Light Compensation and DSP! Available with Wide-angle (80°) or super slim Pin-hole style lens. Run on 9 VDC, standard 1 volt p-p video. Use our transmitters for wireless transmission to TV set, or add our IB-1 Interface board kit for super easy direct wire hook-up to any Video monitor, VCR or TV with A/V input. Fully assembled, with pre-wired connector.
CCDWA-2, B&W CCD Camera, wide-angle lens \$69.95
CCDHP-2, B&W CCD Camera, slim fit pin-hole lens \$69.95
CCDCC-1, Color CCD Camera, wide-angle lens \$129.95
IR-1, IR Illuminator Kit for B&W cameras \$24.95
IB-1, Interface Board Kit \$14.95

Imagine the fun of tuning into aircraft a hundred miles away, the local police/fire department, ham operators, or how about Radio Moscow or the BBC in London? Now imagine doing this on a little radio you built yourself - in just an evening! These popular little receivers are the nuts for catching all the action on the local ham, aircraft, standard FM broadcast radio, shortwave or WWV National Time Standard radio bands. Pick the receiver of your choice, each easy to build, sensitive receiver has plenty of crystal clear audio to drive any speaker or earphone. Easy one evening assembly, run on 9 volt battery, all have squelch except for shortwave and FM broadcast receiver which has subcarrier output for hook-up to our SCA adapter. The SCA-1 will tune in commercial-free music and other 'hidden' special services when connected to FM receiver. Add our snazzy matching case and knob set for that smart finished look!
AR-1, Airband 108-136 MHz Kit \$29.95
HFRC-1, WWV 10 MHz (crystal controlled) Kit \$34.95
FR-1, FM Broadcast Band 88-108 MHz Kit \$24.95
SR-1, Shortwave 4-11 MHz Band Kit \$29.95
SCA-1 SCA Subcarrier Adapter kit for FM radio..... \$27.95

AM Radio Transmitter

Operates in standard AM broadcast band. Pro AM-25, is synthesized for stable, no-drift frequency and is settable for high power output where regulations allow, typical range of 1-2 miles. Entry-level AM-1 is tunable, runs FCC maximum 100 mW, range 1/4 mile. Both accept line-level inputs from tape decks, CD players or mike mixers, run on 12 volts DC. Pro AM-25 includes AC power adapter, matching case and bottom loaded wire antenna. Entry-level AM-1 has an available matching case and knob set that dresses up the unit. Great sound, easy to build - you can be on the air in an evening!
AM-25, Professional AM Transmitter Kit \$129.95
AM-1, Entry level AM Radio Transmitter Kit \$29.95
CAM, Matching Case for AM-1..... \$14.95

Mini Radio Receivers

FR-6, 6 Meter FM Ham Band Kit \$34.95
FR-10, 10 Meter FM Ham Band Kit \$34.95
FR-146, 2 Meter FM Ham Band Kit \$34.95
FR-220, 220 MHz FM Ham Band Kit \$34.95
Matching Case Set (specify for which kit) \$14.95

PIC-Pro Pic Chip Programmer

Easy to use programmer for the PIC16C84, 16F84, 16F83 microcontrollers by Microchip. All software - editor, assembler, run and program - as well as free updates available on Ramsey download site! This is the popular unit designed by Michael Covington and featured in Electronics Now, September 1998. Connects to your parallel port and includes the great looking matching case, knob set and AC power supply. Start programming those really neat microcontrollers now...order your PICPRO today!
PIC-1, PICPRO PIC Chip Programmer Kit \$59.95

Order Toll-free: 800-446-2295
Sorry, no tech info, or order status at 800 number
For Technical Info, Order Status
Call Factory direct: 716-924-4560

RAMSEY ELECTRONICS, INC.
793 Canning Parkway Victor, NY 14564
See our complete catalog and order on-line with our secure server at:
www.ramseyelectronics.com

1 GHz RF Signal Generator

A super price on a full featured RF signal generator! Covers 100 KHz to 999.9999 MHz in 10 Hz steps. Tons of features; calibrated AM and FM modulation, 30 front panel memories, built-in RS-232 interface, +10 to -130 dBm output and more! Fast and easy to use, its big bright vacuum fluorescent display can be read from anywhere on the bench and the handy 'smart-knob' has great analog feel and is intelligently enabled when entering or changing parameters in any field - a real time saver! All functions can be continuously varied without the need for a shift or second function key. In short, this is the generator you'll want on your bench, you won't find a harder working RF signal generator - and you'll save almost \$3,000 over competitive units!
RSG-1000B RF Signal Generator \$1995.00

Super Pro FM Stereo Transmitter

Professional synthesized FM Stereo station in easy to use, handsome cabinet. Most radio stations require a whole equipment rack to hold all the features we've packed into the FM-100. Set free with Up/Down buttons, big LED display, input low pass filter gives great sound (no more squeals or swishing from cheap CD inputs!) Limiters for loud 'punch' in audio - without over mod, LED meters to easily set audio levels, built-in mixer with mike, line level inputs. Churches, drive-ins, schools, colleges find the FM-100 the answer to their transmitting needs, you will too. Great features, great price! Kit includes cabinet, whip antenna, 120 VAC supply. We also offer a high power export version of the FM-100 fully assembled with one watt of RF power, for miles of program coverage. The export version can only be shipped if accompanied by a signed statement that the unit will be exported.
FM-100, Pro FM Stereo Transmitter Kit \$249.95
FM-100WT, Fully Wired High Power FM-100 \$399.95

FM Stereo Radio Transmitters

No drift, microprocessor synthesized! Great audio quality, connect to CD player, tape deck or mike mixer and you're on-the-air. Strappable for high or low power! Runs on 12 VDC or 120 VAC. Kit includes snazzy case, whip antenna, 120 VAC power adapter - easy one evening assembly.
FM-25, Synthesized Stereo Transmitter Kit \$129.95
Lower cost alternative to our high performance transmitters. Great value, easily tunable, fun to build. Manual goes into great detail about antennas, range and FCC rules. Handy for sending music thru house and yard, ideal for school projects too - you'll be amazed at the exceptional audio quality! Runs on 9V battery or 5 to 15 VDC. Add matching case and whip antenna set for nice 'pro' look.
FM-10A, Tunable FM Stereo Transmitter Kit \$34.95
CFM, Matching Case and Antenna Set \$14.95
FMAC, 12 Volt DC Wall Plug Adapter \$9.95


RF Power Booster

Add muscle to your signal, boost power up to 1 watt over a frequency range of 100 KHz to over 1000 MHz! Use as a lab amp for signal generators, plus many foreign users employ the LPA-1 to boost the power of their FM transmitters, providing radio service through an entire town. Runs on 12 VDC. For a neat finished look, add the nice matching case set. Outdoor unit attaches right to the antenna for best signal - receiving or transmitting, weatherproof, too!
LPA-1, Power Booster Amplifier Kit \$39.95
CLPA, Matching Case Set for LPA-1 Kit \$14.95
LPA-1WT, Fully Wired LPA-1 with Case \$99.95
FMBA-1, Outdoor Mast Mount Version of LPA-1 \$59.95

FM Station Antennas

For maximum performance, a good antenna is needed. Choose our very popular dipole kit or the Comet, a factory made 5/8 wave coilinear model with 3.4 dB gain. Both work great with any FM receiver or transmitter.
TM-100, FM Antenna Kit \$39.95
FMA-200, Vertical Antenna \$114.95

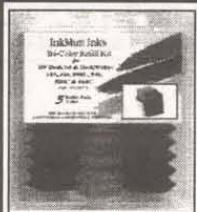ORDERING INFO: Satisfaction Guaranteed. Examine for 10 days, if not pleased, return in original form for refund. Add \$6.95 for shipping, handling and insurance. Orders under \$20, add \$3.00. NY residents add 7% sales tax. Sorry, no CODs. Foreign orders, add 20% for surface mail or use credit card and specify shipping method.



REFILL INKS FOR INKJET PRINTERS

Refill your old cartridge and save. All refill kits come with instructions and needed materials for refilling inkjet cartridges. Success guaranteed. Available for the following:

CANON BC-01, BC-02 CANON BJ10e, APPLE STYLEWRITER, BJ-200 Single, Black, \$8.00. **CANON BJC-600** (BC-201) Single Black or Single Colors (3 refills) \$8.00. **CANON BJ-130/300/330 & IBM Exec Jet** (Cart #BJ1-481 & BJ1-642) Black - 3-bottle kit \$22.00. **CANON BJC-210/240** (BC-05 Cart) 3-color kit (3 refills each color for BC-05) \$24.00. **CANON BJC-4000** and Apple Stylewriter 2400 Black 3-bottle kit (3 refills BC-20, 9 refills BC-21 black, 30 refills BC-11 black, 10 refills BC-10) \$19.00. **CANON BJC-4000/BJC70** and Apple Stylewriter 2400 Tri-color kit - 6 refills each color for BC-21 or 15 refills each color for BC-11 \$24.00. **CANON BJC-800/820/880** 3-bottle kit (for BJ1-643B) \$19.00. **CANON BJC-800/820/880** 3-bottle tri-color kit (Cart #BJ1-643CMY) \$24.00. **EPSON STYLUS COLOR PRINTER** - (Cart S020034) Single Triple black \$19.00; Tri-color kit (Cart S020036) 2 refills each color \$24.00. **EPSON STYLUS COLOR II** - (S020047) Triple Black \$19.00 (S020049). Tri-color (2 refills each color) \$24.00. **EPSON STYLUS COLOR 400, 500, & 600** (S020093) Triple black (7 refills total) \$19.00. **EPSON STYLUS COLOR 200, 500** (S020097) Tri-color 3 refills each color \$24.00. **EPSON STYLUS COLOR 400, 600, 800, 1520** Tri-color (S020089) 3 refills each color \$24.00. **EPSON STYLUS 800/1000** (S020025) 3-refill kit, black, \$19.00. **EPSON STYLUS COLOR 440 AND 640** Black refill kit, (S020187) 4 refills plus free vacuum bottle \$19.00. **EPSON STYLUS COLOR 440, 640, AND 740** (S020191) Color refill kit, 4 refills of each color \$24.00. **HP DESKJET 500/550/560** (51608A, 51633A, 51626A) Black single refills \$8.00. **HP DESKJET 500/550/560**, Black 3-bottle kit \$19.00. **HP DESKJET 500C/550C/560C** - Tri-color kit (5 refills each color) \$24.00. **HP DESKJET 1200C, DESIGNJET 650** (Cart #HP 51640B) Black Three pack (3 refills) \$19.00. **HP DESKJET 1200C/1600C, DESIGNJET 650** (Cart #HP 51640 C,M,Y). Tri-color kit (one refill each color) \$24.00. **HP DESKJET 600/660** (HP 51629A) Black three pack \$19.00. **HP DESKJET 600C/660C**, (HP 51649A) Tri-color (5 refills each color) \$24.00. **HP DESKJET 855C/1600C** (HP 51645A) Black three pack \$19.00. **HP DESKJET 855C** (HP 51641A) Tri-color kit (2 refills each color) \$24.00. **HP PAINTJET and PAINTJET XL** (51606A) Black 3-bottle kit \$19.00. **HP PAINTJET and PAINTJET XL** (51606C) Tri-color kit \$24.00. **HP PAINTJET XL300** (C1645A & C1656A) Black 3-refill kit \$19.00. **HP PAINTJET XL300** Tri-color kit (1 refill each color) HP 51639C,M,Y \$24.00. **HP THINKJET, QUIETJET, KODAK DICONIX 150** (51604A or 92261A) black 5 refills \$9.00. **IBM/Lexmark/Execjet/4076** (1380620) black 3-refill kit \$19.00. **IBM/Lexmark Execjet IIC, WinWriter 150 C** (Cart #1380619) 4 refills each color \$24.00. **Lexmark 3200, 5000, 5700, 7000, 7200, Optra 45 and Z51** (12A1970) 3 refills Black \$19.00. **Lexmark 3200, 6000, 5700, 7000, Optra 45 and Z51** (12A1980) 4 refills each color \$24.00. **SNAP AND FILL SYSTEM** - Permits refilling HP 51626A (black for HP 500-series) and HP 51629A (black for HP 600-series) cartridges without making a hole in the cartridge. Consists of special cartridge holder, syringe, plastic tubing, and directions. **STARTER KIT** - with ink for 3 refills \$28.00. **EXTRA INK FOR SNAP & FILL SYSTEM** (black only) 4-oz. bottle \$18.00; 8-oz. bottle \$34.00. Specify whether for HP 51626A or HP 51629A.

HARD-TO-GET PRINTER RIBBONS

Gorilla Banana, Commodore 1525 \$8.00; Adam Coleco \$12.00; TI-850/855 \$6.00; Centronics 700 Zip Pack \$5.00; C. Itoh Prowriter Jr., Riteman C/F \$6.00; Riteman Infomrunner \$8.00; Commodore MPS-801 \$5.00; MPS 803 \$5.00; Decuriter LA30/36 \$4.00; Apple Scribe \$4.00; Mannsman Tally Spirit 80, Commodore 1526 \$5.00; Epson JX-80 4-Color \$14.00; Printonix P-1013 \$11.00; Star SJ144 color 3-pack \$29.00. ALSO HEAT & TRANSFER RIBBONS AND PAPER FOR PRINTING T-SHIRTS.

Over 300 different ribbons in stock. All ribbons new, not re-inked. Fully guaranteed. Order directly or send SASE for complete list.

Add \$4 per order shipping. CA residents add 7.75% sales tax. On ribbon orders over \$50 deduct 10% discount.

H.T. ORR Computer Supplies

249 Juanita Way, Placentia, CA 92870-2216

714-528-9822 • 800-377-2023 • FAX 714-993-6216

<http://www.extremeplay.com/occomp/orr.htm>

Write in 37 on Reader Service Card.

TIMELESS PRODUCTS

The Best Prices and Service • In Business over 15 years!

Phone 218-346-6660 Fax 218-346-6664

CABLE TV CONVERTERS

WILL NOT DECODE

New! "TP 125 V"
128 Channel Converter with Volume

Special Prices for
TP150PC
Call for Details

Panasonic still available!

- REFURBISHED CONVERTERS ALSO AVAILABLE •
- QUALITY REPAIR DEPARTMENT FOR ALL YOUR TUNER REPAIRS •
- REMOTES AVAILABLE FOR MOST CABLE BOXES •

DEALERS ONLY • GREAT QUANTITY PRICES • NO DECODER SALES


LASERS & ACCESSORIES

HELIUM NEON LASERS

- ✓ Complete Systems
- ✓ Plasma Tubes
- ✓ Power Supplies

ACCESSORIES

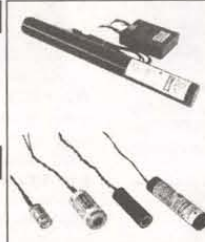- ✓ Optics
- ✓ Electro-Optics
- ✓ IR Viewers
- ✓ Books & More



MEREDITH INSTRUMENTS

DIODE LASERS

- ✓ Visible / IR
- ✓ Complete Modules
- ✓ Collimating Optics
- ✓ Drive Circuits

FREE CATALOG

WEB SITE:

WWW.

mi-lasers.com

Phone: 623-934-9387 • Fax: 623-934-9482

Write in 38 on Reader Service Card.



2000 DSS SOFTWARE COOK-BOOK 700+ CD-ROM COLLECTION: CLONING, REVERSE-ENGINEERING, PPV, ADULT, EMULATORS, DIAGRAMS, SCHEMATICS, PATCHES, PLANS, MUCH MORE. (SPECIALS 1ST 700 ORDERS GET 700+ ADDITIONAL PROGRAMS!) WHOLESALE ONLY \$22 (BUY 2, GET 1 FREE). DSS TEST-CARD INFO SOURCE MANUAL \$10. YEAR 2000 DSS HACKER SECRETS. Includes: CD-ROM, book/manual, ALL software, ALL plans, sources for hardware (cables, ports, circuit board cards, PICs, MUCH, MUCH MORE!) WHOLESALE \$20. VISA/MC/AMEX/COD/CHECKS/MO. BRINKER ENGINEERING LABS. USA. CALL NOW 352-326-3720. MAIL TO: 614 E. HWY 50 #404, CLERMONT, FL 34711. E-MAIL: brinker@maliccity.com



BEST PRICING on 18" satellite TV systems for home and RV. DISH Network DirecTV, multi-room viewing options, accessories, more. www.skyvision.com Call 1-800-543-3025.

FREE SATELLITE TV SYSTEM. USE THIS CERTIFICATE #S-18231100 AND CALL 626-568-0903.

DSS, SATELLITE equipment. Large website. Auctions, forums, files, codes. Call now 1-888-451-0083.

MILITARY SURPLUS ELECTRONICS

WANTED: MILITARY capacitors, resistors, transistors, diodes, ICs, semi's, etc. Please fax/E-Mail excess lists & RFQs 818-769-1002 fax 818-769-1084. electmatind@earthlink.net & <http://www.militarycomponents.com>

AUDIO — VIDEO — LASERS



ANTIQUE VIDEO TRANSFER SERVICE: transfer any 2" QUADRUPLIX tape. Affordable fast! Phone/fax 415-821-7500 or 415-821-3359. 5001 Diamond Heights Blvd., San Francisco, CA 94131-1621.

FREE LASER CATALOG. Helium-Neon, Argon, ruby, visible laser diode modules, lightshows, holography, laser pointers. Lowest prices. Midwest Laser Products, PO Box 262, Frankfort, IL 60423. 815-464-0085 www.midwest-laser.com

BROADCAST VIDEO equipment wanted: all types, new or old. Please call, Jon with info. 1-800-539-2859.

WANTED: PRO video equipment, VCRs, switchers, cameras, etc. Advanced Media 702-874-1911.

DSS, SATELLITE equipment. Large website. Auctions, forums, files, codes. Call now 1-888-451-0083.

Continued on page 56

Build a Watchdog Timer Using the PC Speaker Output



by Mike Keryan

I am in the process of configuring a stand-alone, dedicated PC that will monitor environmental conditions in various rooms in my house and control the heating/air-conditioning system.

The PC consists of a mixture of bargain-basement new parts, like a \$10.00 keyboard, \$14.00 ethernet board, and \$25.00 case/power supply, and some old, outdated parts that were replaced during upgrades (motherboard/CPU, 170 MB hard drive, a bunch of 4 MB SIMMs) that were either free or nearly free.

While this PC will never be able to run the new Windows 2000 OS, it will function fine as a dedicated controller. I have seen other people throwing together similar junk-part PCs for other purposes, such as firewalls between their cable modem and PCs, or as print servers on their home PC networks.

One requirement of a stand-alone system like this is that it should always be up and running, at least when the house has power. It is easy to have the PC automatically boot up and autostart a control program in case of a power failure.

For most uses, it really isn't necessary to have a battery-backup (UPS system) on the PC because it is controlling something that needs power anyway, like the HVAC system or the PC network. But it is important that when power is restored, the PC always

starts up and continues to do whatever it was doing.

Momentary glitches in the power-line can cause your PC program to crash, even when the power doesn't drop out enough to cause a PC reboot. As a PC user, you know that many other things can cause your PC to crash.

When a crash happens, the PC just sits there, doing nothing until someone reboots it. For your desktop PC, this is merely an annoyance, and may cause some data loss, but it gets rebooted quickly because staring at a screen on a locked-up PC isn't a whole lot of fun.

However, you won't be sitting at the dedicated control PC. There must be some way for the PC to recover from a locked-up condition all by itself.

To automatically recover from lock-up, the PC must first know that it is locked-up, and then it must do something about it. There exists software-only watchdog programs that attempt to do this, but many times when a PC locks up, the entire system is dead, and the only way to recover is by external

means, by pushing the reset switch.

The only foolproof way to reboot the PC is by way of some external system that is not dependent on the PC itself detecting the lockup and triggering the reboot.

You can buy watchdog timer PC cards that do just that. They continuously monitor a certain I/O address, usually set by jumpers, and trigger a reboot if nothing has written to that address within a preset time, also set by jumpers.

However, these cards cost about \$100.00 — more than any other single part in my stand-alone PC — and I just couldn't justify one. So I decided to build one using some inexpensive parts. In addition to low-cost, an additional design goal was being easy to program. I didn't want to mess around with I/O addresses.

What I came up with was a watchdog timer circuit that costs about \$10.00 to build. It monitors the PC speaker output, rather than an I/O address. If no output to the speaker has been made in five minutes, it generates a reset signal, which reboots the

computer.

Programming is easy. Your program merely has to output a beep every couple minutes so that the watchdog circuit knows everything is okay and the PC isn't locked up. If the PC does happen to lock up, no beeps will be output, and five minutes later, the PC will reboot.

What I came up with was a watchdog timer circuit that costs about \$10.00 to build. It monitors the PC speaker output, rather than an I/O address.

The circuit is shown in Figure 1. It consists of two inexpensive CMOS ICs, four diodes, and a few resistors and capacitors. IC1-E and IC1-D, C4, R4, and R5 function as a squarewave oscillator whose period is about five seconds (actually about 4.7 sec for the prototype).

This 0.21-Hz squarewave is fed to



www.cctvco.com
E-MAIL: SALES@CCTVCO.COM
1-800-323-8746

MONITOR  \$93.00 BLACK & WHITE 12" 1000 LINES ECL - 1202 MANY SIZES AVAILABLE	BLACK & WHITE BULLET CAMERA  \$79.00 WATERPROOF 420 LINES 1 LUX ECL - 377	4 CHANNEL RECIEVER  \$135.00 2.4 GHZ WITH POWER SUPPLY ECL - 2400BR	SAMSUNG  \$580.00 STR960 960 HOUR TIME LAPSE RECORDER DIAMOND-HEAD SYSTEM ON SCREEN DISPLAY TIME DATE ALARM AUDIO INPUT (ICA) POWER SOURCE 110 VAC (FREE VOLT)	
DIGITAL COLOR CAMERA  \$99.00 DIGITAL COLOR (DSP) 350 LINES 2 LUX ECL - 552	MINI DIGITAL COLOR CAMERA  \$78.00 350 LINES ECL - 554 2 LUX METAL HOUSING	2.4 GHZ VIDEO TRANSMITTER  \$89.00 500' 4 CHANNELS ECL - 2400MT 2.5' L x 1.5' W x 5' H	OUTDOOR ALUMINUM HOUSING & BRACKET  \$45.00 WITH HEAT SHIELD ECL - 601B 13" ADJUSTABLE P/T ECL - 205	
BLACK & WHITE CAMERA  \$69.00 420 LINES 1 LUX ECL - 375	BLACK & WHITE MICRO BOARD CAMERA  \$34.00 420 LINES 32MMX32MM 1 LUX ECL - 11P PINHOLE LENS	COLOR MICRO BOARD CAMERA  \$87.00 DIGITAL (WITH DSP) 350 LINES 32 MM X 32 MM 2 LUX * PINHOLE LENS ECL - 454P	PIR CAMERA  \$96.00 HIDDEN (COVERT) 420 LINES 1 LUX WORKING PIR	
<div style="text-align: center;"> <p>CLIPSE</p> <p>PIR CAMERA</p> <p>\$96.00</p> <p>MONTHLY SPECIALS!</p> </div>				BLACK & WHITE MINE DOME  \$59.00 3.5" x 420 LINES 1 LUX ECL - 372
		PLASTIC WALL BRACKET  \$4.50 7" ADJUSTABLE P/T ECL - 206	QUAD SEQUENTIAL OR FULL SCREEN  \$125.00 FREEZE FRAME MODE 15V ADAPTER INCLUDED REAL TIME B/W QUAD ECL - 4000	
		MINI METAL BRACKET  \$5.00 SWIVEL HEAD CAMERA MOUNT ECL - 203AL		

Phone or Fax us to be placed on our mailing list
1-800-323-8746
 Fax (305)635-3175

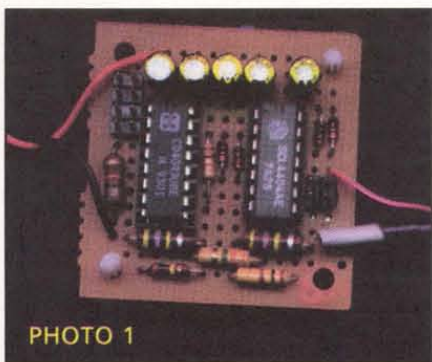


PHOTO 1

the clock input of IC2, a seven-stage binary counter. The output (Q7) of this IC is thus 0.21 Hz divided by two to the seventh power (128), for a 0.00166-Hz squarewave. The period of this squarewave signal is about 600 sec.

For the first half (300 sec), this signal is at zero volts, while the last half is at five volts. The change in state from low to high is detected by C5 and R6, which produce a five-sec positive pulse, which is inverted by IC1-F producing a five-sec negative pulse. This causes the reset pin of the PC to be set to near ground through D4, which reboots

the PC.

IC1-C, R2, and C2 form a power-on reset. When power to the PC is initially turned on, the voltage across C2 is zero volts, so the output of the inverter is high, five volts. The time constant of R2/C2 is such that it takes about five seconds to charge C2 to the point that the inverter will switch so that the output is at zero volts.

This five-sec reset pulse is passed to the reset pin of IC2 through D2. The power-on

reset ensures that all the counter states in IC2 are initially set to zero, so a full five minutes is required to trigger a reboot.

The speaker output pins on the PC motherboard consist of two pins: one of these is always at the +5-volt level, while the other pin outputs a negative-going pulse at a few hundred Hz when a beep signal is sent to the speaker. This negative-going pulse train is inverted by IC1-B to form positive pulses.

The positive pulses pass through diode D1 and are smoothed somewhat by R3/C3. These pulses reset IC2 sim-

ilarly to the power-on reset, so that any signal sent to the speaker resets the timer. As long as the speaker output is not dead for as long as five minutes, this circuit will never send a reboot signal to the PC.

The pulses from the speaker output are inverted once more by IC1-A, producing negative pulses again. These are passed through R7 and then to the real speaker in the PC. R7 is used to reduce the volume of the PC speaker so that you can just barely hear it. Since it will be beeping every minute or so, full volume could get very annoying. Of course, you could just not connect the speaker, but I wanted to be able to hear the beeps to make sure it was working okay.

The reset switch to the front panel is fed through D3 to the reset pin on the motherboard. This allows the real switch to function normally. The +5 volt and ground signals to power the watchdog timer circuit are stolen from the motherboard pins, so there was no need to connect a four-pin power cable like you do with your fan and drives. The +5-volt signal is taken from the motherboard output to the speaker; the ground is taken from the motherboard pins that normally connect to the reset

switch.

Something I added recently to the circuit is SW1, an SPST switch that is normally 'on,' but allows you to disable the watchdog circuit from resetting the PC. When would you switch this 'off'? When you are doing some work on the PC, such as installing software or hardware, or at any other time when your program generating the beep/minute output is not running.

I built the prototype on a 1.75x1.75 inch RadioShack PC board, as shown in Photo 1. I used IC sockets for both ICs. I wired everything using point-to-point wiring with wire-wrapping wire cut to 1.5-inch lengths. I soldered all connections. J1 and J2 are 1x4 pin and 1x2 pin, 0.1 inch male headers. However, I used 2x4 and 2x2 headers on the prototype because I didn't have the smaller ones.

I used a spare CD-ROM audio cable for both P1 and P2 and their cables. I cut the audio cable in two. One end has a four-pin connector, which goes to the speaker connector on the motherboard. The other end may be four-pin also, but depending on the CD-ROM drive, it may be two or three pins. If it has more than two pins, only use the two adjacent pins.

Quality Used Test Equipment

90 DAY WARRANTY Parts & Labor - 10 DAY TRIAL PERIOD

HEWLETT PACKARD

105B, Quartz Oscillator, aging < 5 x 10 ⁻¹⁰ per day	\$700
11720A, Pulse Modulator, 2-18 GHz, >80dB on/off ratio	\$300
11975A, 2.8GHz Amplifier (use w/ 11970 series mixers)	\$1500
214B, 10 MHz Pulse Generator, 200W Pulse/50 ohms	\$700
2225A, Thinkjet Printer, HP/IB	\$150
3314A, Arbitrary/Function Generator	\$1100
3325A-1-2, 21MHz Synth Func Gen, 40Vp-p, HP/IB	\$850
33322H, Prog Attenuator, DC-18GHz, 0-110dB	\$200
3403C, Digital RMS Voltmeter, 2 Hz-100 MHz	\$150
3456A, 6.5 digit Multimeter, HP/IB, cal'd with cert	\$450
3468B, 5.5 digit Multimeter, HP-IL	\$300
3497A, Data Acquisition/Control Unit	\$150
3498A, Data Acquisition Extender	\$300
3852A, Data Acq/Control Unit	\$800
436A, Power Meter w/ sensor cable, HP/IB	\$550
44462A/63A, 8 Chan MUX/2 Chan Actuator (3421A)	\$135
5004A, Signature Analyzer	\$200
5087A-033, Distribution Amp, 10MHz in/out, 12-chan	\$1000
5180A, Waveform Digitizing Recorder, 20MHz	\$500
5314A, 100 MHz Counter	\$150
5315B-04, 100 MHz Counter	\$200
5316B, 100 MHz Counter, HP/IB	\$250
5328A-011-020-030, 512 MHz Counter w/DVM, HP/IB	\$225
5334A-060, 100 MHz Counter, front & rear input, HP/IB	\$300
5335A, 200 MHz Counter, HP/IB	\$525
5335A-10-40, 200 MHz Counter, Oven Oscillator, HP/IB	\$675
5335A-10-20-30-40, 1.3GHz Counter, Oven/DVM/HP/IB	\$900
5342A-01-011, 18GHz Counter w/ Oven Osc & HP/IB	\$900
54501A, 100MHz 4-chan Digitizing OScope w/HP/IB	\$1100
6034A, Dig Autoranging Pwr Sup, 60V/10A/200W, HP/IB	\$650
6034L, Dig Autoranging Pwr Sup, 60V/10A/200W, HP/IB	\$575
6110A (Harrison), Pwr Sup, 3KV @ 6mA	\$150
6253A, Dual Pwr Sup, 0-20V @ 3A	\$250
6255A, Dual Pwr Sup, 0-40V @ 1.5A	\$300
6267B, Pwr Sup, 0-40V @ 10A	\$450
6268B, Pwr Sup, 0-40V @ 30A	\$600
6271B, Pwr Sup, 0-60V @ 3A	\$175
6274B, Pwr Sup, 0-60V @ 15A	\$675
6284A, Pwr Sup, 0-20V @ 3A	\$100
6289A, Pwr Sup, 0-40V @ 1.5A	\$100
6294A, Pwr Sup, 0-60V @ 1A	\$100
6515A, Pwr Sup, 0-1.6KV @ 5mA	\$175
7550A, Graphics Plotter, HP/IB	\$200
8447A, RF Amp, 0.1-400MHz, 20dB gain, +6dBm out	\$300
8496H, Prog Attenuator, DC-18GHz, 0-110dB, SMA type	\$300
8498A, High Pwr Atten, 25W, DC-18GHz, 30dB	\$500
8501A, Storage Normalizer w/cable (use w/8505A)	\$750
85041A, Transistor Test Fixture Kit	\$500
8566A, Spectrum Analyzer, 100Hz-22GHz, HP/IB	\$9000
8569B, Spectrum Analyzer, 0.01-22GHz, HP/IB	\$4500
8640B, Signal Generator, 0.5-512 MHz, AM/FM/Pulse	\$700
8660C/8663B/86603A, 2.6GHz Synth Sig Gen	\$1800
8903B-001, Audio Analyzer, 20 Hz-100 KHz, rear input	\$1500

9411B, Switch Controller, HP/IB	\$450
9413A, VHF Multi-Port Switch	\$450
E1406A, VXI Command Module	\$525
E1407A, VXI A/B-C-Size Active Adapter	\$200
E1499A, VXI V/382 Controller	\$550

TEKTRONIX

1241, Color Logic Analyzer w/ (4) P6460 probes	\$850
1502-04, TDR w/chart recorder	\$1000
AM503, Current Probe Amplifier	\$250
CFG280, 11MHz Function Gen/100MHz Counter (new)	\$600
P6452, Data Acquisition Probe (use w/ DAS9100)	\$150
P6460, Data Acquisition Probe (for 1240/1241 Analyzer)	\$125
PS503A, Triple Pwr Sup, 0 to +20V @ 1A, 5V @ 1A	\$150
SG504, Leveled Sine Wave Generator	\$1850
TDS460-1M, 350 MHz Digital O'Scope, 4-Channel, extra memory, includes 2 new P6138A probes & manuals	\$3500
TM501, 500-series Power Module	\$100
TM503, 500-series Power Module	\$125

MISCELLANEOUS

AstroMed ASC902, Medium Gain Amplifier Plug-in	\$100
Cablescan 256, Programmable Cable Assembly Tester	\$475
Cablescan 512, Programmable Cable Assembly Tester	\$750
EIP 548A, Microwave Counter, 10 Hz-26.5 GHz	\$1800
EMI TCR160T30, Pwr Sup, 0-160V @ 30A	\$650
Fluke 5200A, AC Voltage Calibrator	\$1000
Fluke 5440B, DC Calibrator, calibration verified	\$2800
Fluke 6080A/AN, Synth Signal Gen, 0.5-1024MHz, AM, FM, Phase-, and Pulse-Mod, High Spectral Purity	\$3200
Fluke 845AB, High Impedance Null Detector	\$300
Fluke 87, 4.5-digit RMS Handheld DMM	\$225
Fluke 8922A, Digital RMS Voltmeter, 2 Hz-11 MHz	\$400
GenRad 1404-B, 100pF Standard Capacitor, 20ppm/yr	\$400
Heise 711B, Digital Pressure Gauge, 0 to 30 PSI, 0.5%	\$250
Heise CC (18inch), Pressure Gauge, 0.1%, 0-1500psi	\$250
Heise CC (18inch), Pressure Gauge, 0.1%, 0-2000psi	\$250
Hughes 1177H04F000, TWT Amp, 12.4-18GHz, 10W	\$1500
Interface 553, Mil-Std-1553 Analyzer	\$850
Krohn-Hite 3550, Filter, Hi/Low Pass, Band Pass & Reject	\$275
Lambda LQ522, Digital Pwr Sup, 0-40V @ 1.8A	\$75
Lambda LQ530, Digital Pwr Sup, 0-10V @ 14A	\$125
Lambda LQ531, Digital Pwr Sup, 0-20V @ 8.6A	\$125
Lambda LQD421, Dual Dig Pwr Sup, 0-20V @ 1.7A	\$125
L&N 4385, Shunt Box, 8 ranges (0.75A to 15A), 0.02%	\$350
L&N 4398-M, 7-Decade Double Ratio Set, 20ppm ohms	\$275
PAR 128, Lock-in Amplifier, 0.5Hz-100KHz	\$500
RF Power Labs M102L, RF Amp, 30Hz-100MHz, 2W	\$400
Rockland 852, Dual Hi/Low Pass Filter	\$450
Spectral Dynamics SD131L, Tracking Filter	\$600
Wavelet 178, 50MHz Programmable Waveform Synth	\$900
Wavelet 2001, Sweep Generator, 1-1400MHz	\$375
Wavelet 271-02, 12MHz Pulse/Func Gen, GPIB	\$400
Wavelet 859, 50 MHz Prog Pulse Generator, GPIB	\$575

Visit our website at www.testequipmentplus.com


TEST EQUIPMENT PLUS

(800) 834-6068, FAX (520) 575-6936

3331 W. Bright Terrace, Tucson, AZ 85741



LOWEST COST LCD'S ON EARTH

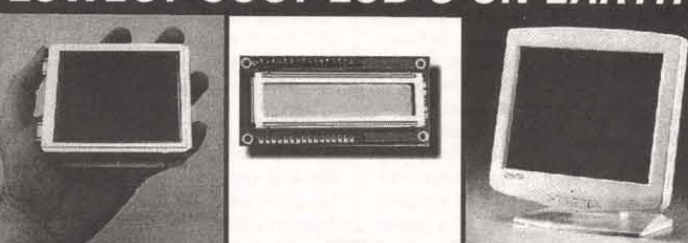

VIDEO LCD

4 Inch Video NTSC \$150
Sharp P/N 4LU4E
Composite NTSC & RGB Input
12:00 OR 6:00 Viewing Angle
Integrated Backlight & Inverter
Extended Temp: -10 to +60 C
Brightness: 260 nits
Power Consumption: 4.3 Watts
Contrast: 50 to 1

CHARACTER LCD

OPTREX DMF-5005N-EW
240 x 64 Graphic EL Backlit STN \$30
OPTREX DMF-5005N
240 x 64 Graphic Reflective STN \$30
SANYO DM2023-7G1
2 x 20 Character Reflective STN \$8
SHARP LM20A21
2 x 20 Character Reflective STN \$8
VIKAY 2035TND NOTW-D
2 X 16 Character LED Backlit STN \$8

LCD MONITOR

10.4" DSTN or 12.1" TFT
Analog SVGA Input
Autosync
Auto Sizing
Automatic Expansion of VGA
images to SVGA (On 12.1")
Very Aggressive Pricing
Starting under \$500!



TOUCH MONITOR

EarthVue 10.4
10.4" VGA TFT
Analog VGA Input
105 Nit Brightness
RS-232 Touch Screen Option
Only 9.9" W x 7.7" H x 1.5" D
Ideal For Factory Automation
Fully Articulating Ball Mount
Only \$1095 With Touch

LCD DISPLAYS

6.3" Mono STN \$60
9.4" Mono Reflective \$60
8.4" TFT \$250
9.4" DSTN \$150
10.4" TFT \$350
10.4" DSTN \$240

CONTROLLERS

ISA
PCI
PC/104
NTSC
Analog VGA
Complete LCD Kits with LCD,
Controller & Cable Starting
under \$200

NoteBook Screens
340 Models in Stock
Obsolete Screens Stocked
Hard To Find LCD? Call!



EARTH


Computer Technologies

"The World Leader In LCD Recycling"

Ph: (949) 361-2333 Fax: (949) 361-2121

<http://www.flat-panel.com>

FIGURE 1

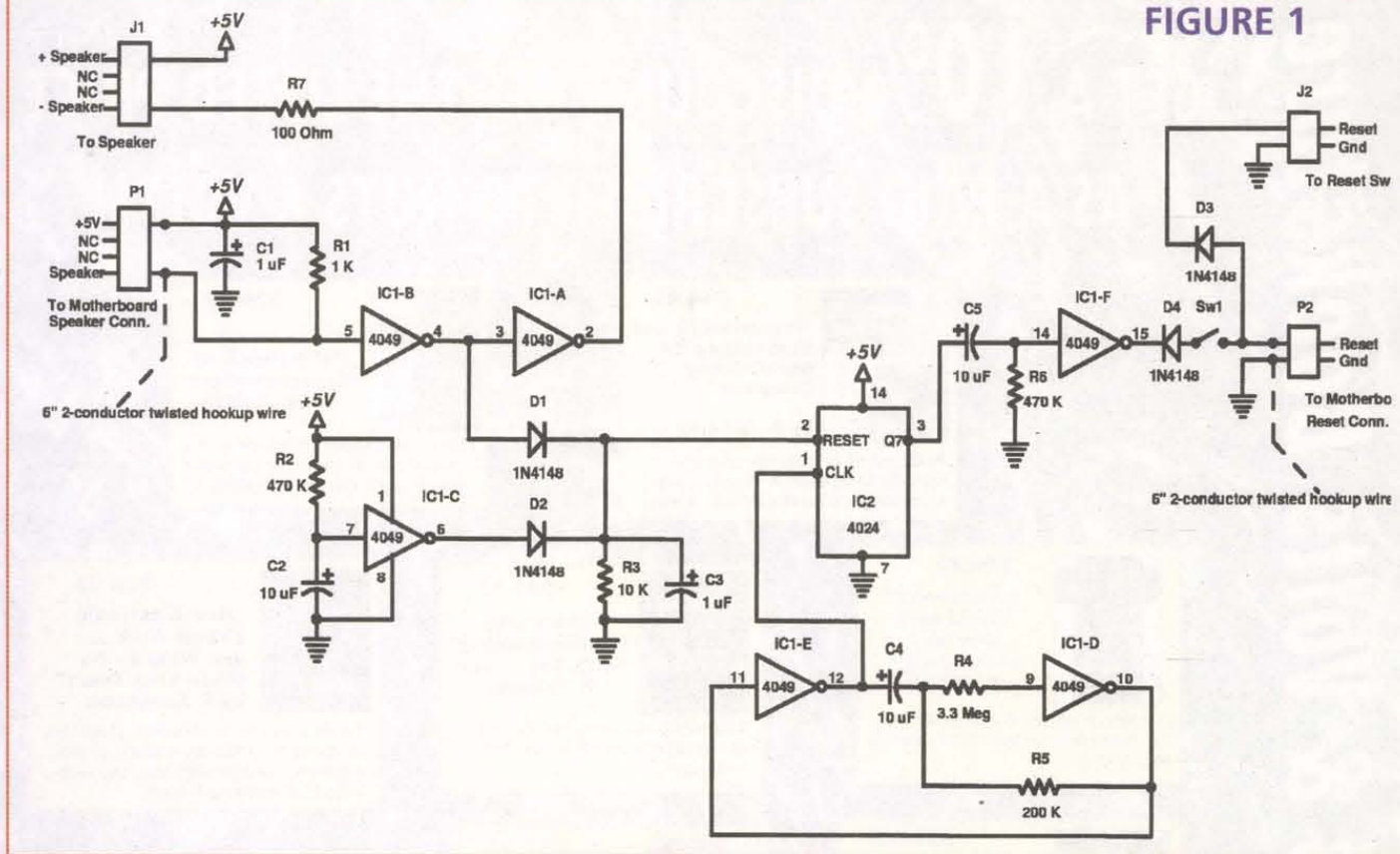

After you build the board, it is wise to test it first before hooking it up to the PC. Connect a nine-volt battery (+ to +5V pin on P1, - to the Gnd pin on P2). With a voltmeter, monitor pin 1 (Clk) of IC2. It should go from 0V to 5V with each state lasting about two to three seconds. Then monitor pin 3 (Q7) of IC2. It should stay at 0V for about five minutes, then jump to 5V for five minutes. When Q7 is high,

momentarily grounding the 'Speaker' pin of P1 should result in Q7 jumping back to 0V as a result of the reset.

When installing it in the PC, mount it somewhere midway between the speaker, the reset switch, and the motherboard headers. Unplug the PC from the powerline. Use the motherboard manual to make sure you fiddle with the correct wires. Unplug the two-conductor plug that comes from the

front-panel reset switch. Note where this cable was plugged in.

Plug the cable onto J2 (orient it either way). Then determine which of the two pins on the motherboard is really the ground. If you don't have the manual, use an ohmmeter to see which pin has very low resistance to the metal chassis. Then plug your P2 onto these two pins so that your ground wire connects to the ground pin.

Unplug the four-pin speaker connector from the motherboard. Again, note the location from which you just unplugged the speaker cable. Plug the speaker cable onto J1, the red wire to +5V end. Then plug P1 onto the same four pins that the speaker was plugged into.

Make sure the +5V end of the cable is connected to the pin that really has +5V. If you are unsure, use the voltmeter to find the correct pin (you must power up the PC and turn it on) prior to plugging in P1.

Mount SW1 somewhere on the front panel. The most convenient place is on one of the plastic covers that are removed when installing disk drives. Pop off one of these panels and drill a hole to hold the switch. It is probably a good idea to stick on labels (made with a labelmaker) that indicate something like 'Watchdog off,' 'Watchdog on.' Then push the plastic panel back on.

That's it for the hardware. For the software end, your programs must generate a beep every minute or so to keep it from rebooting. Details of how to do this vary for each OS and language. Most of the time, your program can send a control-G character to the console to get it to beep.

If you are running Linux, you can easily set up a cron job that generates

the beep. As root, create a file called crontab as below:

```
SHELL=/bin/sh
PATH=/home/root
MAILTO=""
# beep every minute
* * * * * echo -e "\a"
>/dev/console
```

The MAILTO line as above is required to keep cron from sending you mail every minute. Then, install the file by entering this line:

crontab crontab

Of course, it is preferred to have your custom program generate the beep rather than the operating system itself generate the beep. However, the PC may possibly be used as some sort of server or firewall and it may be running no custom software, whatsoever. In this case, the crontab method is just as effective as custom software.

I have found this watchdog circuit to function reliably. I have it working on two PCs that are left on 24 hours a day, seven days a week. Both of these have AT-style motherboards with AT-style power supplies.

It is possible that this circuit is incompatible with some of the newer ATX-style systems. However, I've reviewed the manuals of a number of AT systems and am convinced that the circuit should work on most, if not all of them.

You can test it in your PC by killing the software that generates the beep and waiting five minutes. The only potential failure would be if the PC would fail and lock up when sending out a continuous 'beep.' This is rather unlikely. **NV**

PARTS LIST FOR PC-SPEAKER WATCHDOG TIMER

SEMICONDUCTORS

IC1 - CD4049 hex inverter CMOS integrated circuit
IC2 - CD4024 (or CD4404) seven-stage binary counter CMOS integrated circuit
D1, D2, D3, D4 - 1N4148 (or 1N914) silicon switching diode 75-PRV 10 mA

RESISTORS

(All resistors are 1/4 watt, 5% units)
R1 - 1000 ohm
R2, R6 - 470,000 ohm
R3 - 10,000 ohm
R4 - 3.3 megohm
R5 - 200,000 ohm
R7 - 100 ohm

CAPACITORS

C1, C3 - 1.0 uF, 25 WVDC, electrolytic
C2, C4, C5 - 10 uF, 25 WVDC, electrolytic

ADDITIONAL PARTS AND MATERIALS

J1 - 0.100" male header four conductor (1x4) or (2x4)
J2 - 0.100" male header two conductor (1x2) or (2x2)
P1 - 0.100" female socket four conductor (1x4) with 6" two-conductor twisted hook-up wire (red/black)
P2 - 0.100" female socket two conductor (1x2) with 6" two-conductor twisted hook-up wire (red/black)
SW1 - SPST switch

IC sockets (1 14-pin, 1 16-pin), 1.75" square PC board: one-half of RadioShack 276-148A, wire, mounting hardware.

Note: The two plugs (P1 and P2) with their connecting wires that plug onto the motherboard can be made by cutting in half a general-purpose CD-ROM audio cable. One end will have the four-pin plug for the speaker connector. The other end may be two-pin, three-pin, or four-pin, of which only the first two are used.

GET A 10% DISCOUNT OFF THE LISTED PRICE AS A PAID SUBSCRIBER TO NUTS & VOLTS!



\$34.95

"Programming and Customizing the BASIC Stamp Computer"

by S. Edwards

Build smart electronics projects with the inexpensive, simple-to-use, surprisingly powerful BASIC Stamp.



\$54.95

"Handbook of Microcontrollers"
by M. Predko

This much-needed reference is the first to cover all the most common types of eight-bit microcontrollers.



\$44.95

"Handbook of Radio and Wireless Technology"
by S. Gibilisco

A comprehensive compendium on the entire field of radio and wireless technology.



\$34.95

"Electronic Troubleshooting"
by D. Tomal and N. Widmer

Troubleshoot and repair any type of electronics with this comprehensive guide.



\$24.95

"How Electronic Things Work ... and What to Do When They Don't"
by R. Goodman

Never again be flummoxed, flustered, or taken for a ride by a piece of electronic equipment with this fully illustrated, simple-to-use guide.



\$39.95

"Encyclopedia of Electronic Circuits"
Vol. 7
by R. Graff

An extensive library of 1,000 circuits from the bestselling, seven-volume "Encyclopedia of Electronic Circuits."



\$39.95

"Programming and Customizing the 8051 Microcontroller"
by M. Predko

This tutorial/disk package details the features of the 8051 and demonstrates how to use these embedded chips to access and control many different devices.



\$39.95

"Circuit Troubleshooting Handbook"
by J. Lenk

This handbook gives full descriptions of the operation of important circuits, and how each circuit's characteristics may figure in its failure or poor performance.

by Joseph J. Carr



SECRETS OF RF CIRCUIT DESIGN
\$29.95

From one of today's most respected electronics authors comes this pragmatic, intermediate-level guide to designing, building, and testing all types of radio frequency circuits. Filled with functional projects that demonstrate the principles of RF circuits, this revision of a bestseller also provides a handy parts list and sources of components.



PRACTICAL ANTENNA HANDBOOK
\$49.95

The most popular book on antennas ever written, widely known as "the antenna builder's bible." This *Third Edition* is a work for anyone with an interest in antennas, from the newest of novices to the most experienced engineer. This empowering book gives you all kinds of projects and material that explains why what you did works.

BOOKS
PUBLISHED
BY
MCGRAW HILL

Call 1-800-783-4624 today!
WE ACCEPT VISA AND MASTERCARD

Send check or money order to Nuts & Volts, 430 Princeland Court, Corona, CA 92879. Include a complete shipping address (no P.O. Boxes, please). Shipping & handling \$4.50. CA residents add 7.75% sales tax. Or, call our toll-free order-only line at 1-800-783-4624 and use your MasterCard or Visa. ALL ORDERS MUST BE PREPAID.

"The Illustrated Dictionary of Electronics"
by S. Gibilisco **\$39.95**

"The Robot Builder's Bonanza"
by G. McComb **\$18.95**

"Programming and Customizing the PIC Microcontroller"
by M. Predko **\$39.95**

"How Radio Signals Work"
by J. Sinclair **\$24.95**

"Making Printed Circuit Boards"
by J.L. Axelson **\$22.95**

OTHER AVAILABLE TITLES ::

"TAB Encyclopedia of Electronics for Technicians and Hobbyists"
by S. Gibilisco **\$69.50 (Hard Cover)**

"How to Read Electronic Circuit Diagrams"
by R.M. & Lawrence Brown **\$19.95**

"Build Your Own Test Equipment"
by H.L. Davidson **\$22.95**

"Radio Receiver Projects You Can Build"
by H.L. Davidson **\$21.95**

"Basic Electronics Theory"
by D.T. Horn **\$26.95**

OTHER AVAILABLE TITLES ::

"Troubleshooting and Repairing Consumer Electronics Without a Schematic"
by H.L. Davidson **\$24.95**

"Amateur Radio Encyclopedia"
by S. Gibilisco **\$50.00 (Hardcover Only)**

"Ready-to-Build Telephone Enhancements"
by D.T. Horn **\$17.95**

"The Benchtop Electronics Handbook: 260 Most Common Popular Electronics"
by V. Veley **\$65.00 (Cloth Cover)**


Win Win Win

As a paid subscriber to *Nuts & Volts*, you will be automatically entered each month in our prize drawing!

Win "great stuff" like this month's prize from
LEMOS INTERNATIONAL
(Page 65)

A \$50.00 Gift Certificate towards purchases

Past Prizes have included ...

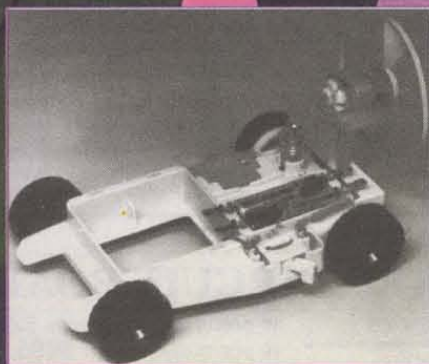

NETCOM will continue to provide prizes monthly!

To Subscribe — Just fill in and mail the card supplied in the magazine or call our toll free order line at **(800) 783-4624** with a Visa or MasterCard.

If you do not wish to order a subscription, but would like to be entered in our drawing, simply send or E-Mail your name, address, and telephone number to *Nuts & Volts*, 430 Princeland Ct., Corona, CA 92879 or drawing@nutsvolts.com. No phone entries accepted. All orders/entries must be received by the last day of the month to be included in that particular month's drawing.

Join

DANIEL CHURCHILL of Cavendish, VT
and **RAYMOND MOORE** of Anderson, IN

Make Your Own Printer Port

LED ARRAY SIGN

**For Around
\$50.00**

by Robert Davis

I have always wanted to play with some LED arrays. So, when Electronics Goldmine advertised them at 10 for only \$18.00, I quickly bought some. Their part number G7295 gets you 40 bright red LEDs arranged as five columns by eight rows. These displays are over two inches tall by 1-1/2 inches wide. They can be used for all kinds of fun

projects and fun devices.

There were two things that I planned to make using the LED arrays. One was an "ON THE AIR" sign, and the other a multiple channel LED VU meter. The VU meter had already been made using a computer as the Printer Port

VU meter. The problems with it were that the monitor was taking up too much room in the sound control booth and that the computer seemed like overkill for a 16-channel VU meter.

Somehow the sign idea grew into two versions: a fixed one and a programmable one using a computer. The VU meter also grew into two versions: one that uses four of the five columns in each display and the other uses all five columns.

This article is about the programmable sign that connects to a computer's printer port. It is the neatest, most versatile, and most useful of the LED array projects.

Initially, the easiest method of lighting up the arrays that comes to mind would be to arrange them as one giant matrix and pass a rather large current through them. To see the problems that would arise, con-

This article is about a programmable sign that connects to a computer's printer port. It is one of the neatest, most versatile, and most useful LED array projects you'll come across.


sider 10 of the eight by five arrays arranged as an eight row by 50 column matrix. A counter and decoder could rapidly select the 50 columns to make it appear like they are all lit. Since each is only lit 1/50 of the time, it would need 50 times the normal current during that time to reach normal brightness. Considering 10 mA per LED as sufficient, then we would need eight (LEDs in the column) times 10 milliamp times 50 or a total of four amps!

The current-limiting resistors would need to be large and, if the counter stopped, any lit LED would likely smoke. If it was instead broken down into 10 separate LED arrays, the same current would be 1/5 of four amps or a much more manageable 8/10 of an amp.

Even 8/10 of an amp exceeds the maximum rating of ordinary transistors like the 2N2222. I have tried using 2N2222s, but they get very hot. For the columns, my preference is to use a more powerful driver like the TIP120 or TIP125. These Darlington power transistors can easily drive 10 or more LED array columns with all LEDs lit and only get warm to the touch. If they do get too hot, a small heatsink can easily be attached, but none proved necessary in any of my designs.

Some designers will use individual drivers for

**LED ARRAY
LTP2058AHR-01**

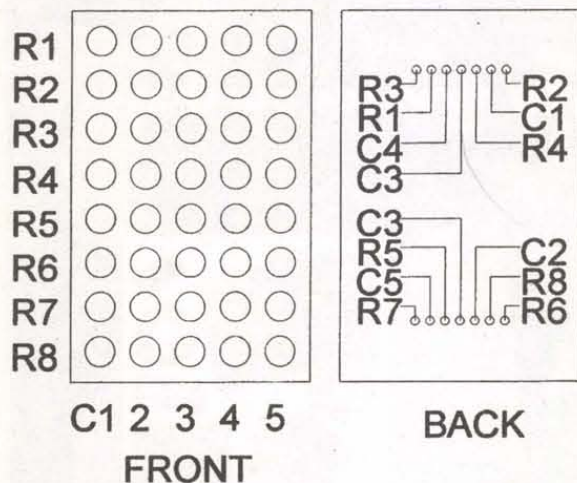

**Enter the Nuts & Volts
and ExpressPCB**

**ELECTRONICS
DESIGN CONTEST**

**WIN GREAT
PRIZES!!**

**SEE PAGE 6
FOR DETAILS!!**

PRINTED CIRCUIT BOARDS

QUALITY PRODUCT

FAST DELIVERY

COMPETITIVE PRICING

*We will beat any
competitor's prices!!!*

- * UL approved
- * Single & Double sided
- * Multilayers to 8 layer
- * SMOBC, LPI mask
- * Reverse Engineering
- * Through hole or SMT
- * Nickel & Gold Plating
- * Routing or scoring
- * Electrical Testing
- * Artwork or CAD data
- * Fast quotes

10 pcs (3 days) 1 or 2 layers \$249

10 pcs (5 days) 4 layers \$695

(up to 30 sq. in. ea.) includes tooling, artwork, LPI mask & legend

**PROTOTYPE THROUGH
PRODUCTION**

PULSAR, INC

9901 W. Pacific Ave.
Franklin Park, IL 60131
Phone 847.233.0012
Fax 847.233.0013
Modem 847.233.0014
yogii@flash.net • flash.net/~yogii

both the rows and columns for every LED array. Neither is required. On the rows, something like the ULN2803 driver would be used. But is that powerful of a driver really necessary? For instance, a 74LS373 can easily deliver 30 mA per output. If that is divided between five LEDs in the row, it gives 6 mA of current per LED. This will generally provide sufficient brightness with no high current driver.

My conclusion is that it is practical to share column drivers between multiple arrays, but not practical to share row drivers between multiple arrays. That means that a separate 74LS373 will be required for each LED array that is used. These drivers only deliver 30 mA, so there is little chance of damage to the LEDs if something goes wrong. The column drivers can be controlled by a counter that counts to 10 and then resets. A 4017 will work fine for this purpose. The 4017 delivers only about 1 mA, so a TIP120 driver transistor will be used to supply the needed current. The Darlington transistor reduces the load on the 4017 to where it can easily handle it.

Another problem is finding a circuit board big enough to hold 10 of the LED arrays.

Jameco has one that is 4-1/2 inches by 17 inches. That is enough room to fit 10 displays with about 2/10 of an inch between each of them. If you are into graphics, the space between them can be omitted, but the software to produce the graphics would be much more complicated than what I have provided.

The printer port sign is relatively simple to make. Most designs that I have seen use a latch to hold the next byte to display, then a latch for the currently displayed byte, and a current driver for each LED array. With some simple tricks, I was able to do all three of these things with just one IC — a 74LS373. I have tested 74F373, 74S373, 74HCT373, and the 74LS373, and did not notice any difference in brightness or performance. The 74XX374 eight-bit latches do create a timing difference that can be corrected in software.

The trick to doing all of these things with one

latch is to turn the display off while the latches are being loaded. This prevents a dim echo of the next or previous byte from appearing. A 4017 is used, but only every other output is connected to turn on the columns. This way the 10 latches can be loaded, then the columns turned on, then turned back off, and then load the latches with the next 10 bytes.

The current-limiting resistors for the printer port sign need to be smaller because there is only five volts to light up the LEDs instead of 10 or 12. This will prevent frying the 74LS373's output transistors. A value of 47 ohms works best,

Qty	Part	Number/Price	Total	Source
10	LED arrays	G7295 10/\$18	\$18.00	Electronic Goldmine 1-800-445-0697
1	Board 4x17	37604 10.95	10.95	Jameco 1-800-831-4242
10	74LS373	47600 .39	3.90	Jameco
2	CD4017	12749 .35	.70	Jameco
1	LM7805	51262 .29	.29	Jameco
5	TIP120	32993 .65	3.25	Jameco
1	1.5A bridge	145429 .59	.59	Jameco
1	1000uF/16V	30015 .19	.19	Jameco
1	470uF/16V	93817 .19	.19	Jameco
1	9 VAC	119204 4.95	4.95	Jameco
80	47 ohm 1/4W	29946 100/.89	.89	Jameco
3	2.2K 1/4W	29946 100/.89	.89	Jameco
10	20 pin sockets	112248 .12	1.20	Jameco
2	16 pin sockets	112221 .12	.24	Jameco
1	26 pin header	53495 .35	.35	Jameco
1	25 pin Male to header socket cable (from parts pile)			
Total cost of parts purchased			\$46.58	

Parts List For the Printer Port Sign

This is the software listing for a sign that will display four lines of text.

CLS : PRINT "Printer port sign, Copyright 1999 BY Robert J Davis"

'INPUT "Use Printer Port Number: ", lpt

'Hardcoded to lpt2 for higher speed - needed for a 486.

'Make these changes for using other printer ports;

IF lpt = 2 THEN dout = &H378: cout = &H37A: cin = &H379

IF lpt = 1 THEN dout = &H3BC: cout = &H3BE: cin = &H3BD

IF lpt = 3 THEN dout = &H278: cout = &H27A: cin = &H279

PRINT "Press q to quit displaying sign ———"; ""

INPUT "What do you want line 1 to say? ", line1\$

INPUT "What do you want line 2 to say? ", line2\$

INPUT "What do you want line 3 to say? ", line3\$

INPUT "What do you want line 4 to say? ", line4\$

new = 1

getline:

IF new > 300 THEN new = 1

IF new = 1 THEN message\$ = line1\$

IF new = 100 THEN message\$ = line2\$

IF new = 200 THEN message\$ = line3\$

IF new = 300 THEN message\$ = line4\$

DJM array, byte(50)

FOR i = 1 TO 10

letter\$ = MID\$(message\$, i, 1)

letter\$ = UCASE\$(letter\$)

SELECT CASE letter\$

CASE IS = "A": RESTORE a

CASE IS = "B": RESTORE b

CASE IS = "C": RESTORE c

CASE IS = "D": RESTORE d

CASE IS = "E": RESTORE e

CASE IS = "F": RESTORE f

CASE IS = "G": RESTORE g

CASE IS = "H": RESTORE h

CASE IS = "I": RESTORE i

CASE IS = "J": RESTORE j

CASE IS = "K": RESTORE k

CASE IS = "L": RESTORE l

CASE IS = "M": RESTORE m

CASE IS = "N": RESTORE n

CASE IS = "O": RESTORE o

CASE IS = "P": RESTORE p

CASE IS = "Q": RESTORE q

CASE IS = "R": RESTORE r

CASE IS = "S": RESTORE s

CASE IS = "T": RESTORE t

CASE IS = "U": RESTORE u

CASE IS = "V": RESTORE v

CASE IS = "W": RESTORE w

CASE IS = "X": RESTORE x

CASE IS = "Y": RESTORE y

CASE IS = "Z": RESTORE z

CASE IS = "1": RESTORE 1

CASE IS = "2": RESTORE 2

CASE IS = "3": RESTORE 3

CASE IS = "4": RESTORE 4

CASE IS = "5": RESTORE 5

CASE IS = "6": RESTORE 6

CASE IS = "7": RESTORE 7

CASE IS = "8": RESTORE 8

CASE IS = "9": RESTORE 9

CASE IS = "0": RESTORE 0

CASE IS = "-": RESTORE minus

CASE IS = "+": RESTORE plus

CASE IS = "=": RESTORE equal

CASE IS = "<": RESTORE less

CASE IS = ">": RESTORE great

CASE IS = "#": RESTORE num

CASE IS = "^": RESTORE up

CASE IS = "_": RESTORE down

CASE IS = "?": RESTORE ques

CASE IS = "*": RESTORE star

CASE IS = "!": RESTORE excl

CASE IS = " ": RESTORE blank

CASE ELSE: RESTORE blank

END SELECT

READ byte(0 + i)

READ byte(10 + i)

READ byte(20 + i)

READ byte(30 + i)

READ byte(40 + i)

NEXT i

start:

IF INKEY\$ = "q" THEN END

OUT &H37A, 7: OUT &H37A, 3 'reset

FOR a = 1 TO 50

OUT &H378, byte(a)

IF a MOD 10 = 0 THEN

OUT &H37A, 2: OUT &H37A, 0 'next column

FOR t = 1 TO 50: NEXT t 'delay to display (50 = 486)

OUT &H37A, 2: OUT &H37A, 0 'next column

END IF

OUT &H37A, 3: OUT &H37A, 2 'next byte

NEXT a

new = new + 1

IF new MOD 100 = 0 THEN GOTO getline

GOTO start

END

a: DATA 003,237,238,237,003

b: DATA 000,118,118,118,137

c: DATA 129,126,126,126,189

d: DATA 000,126,126,126,129

e: DATA 000,118,118,118,126

f: DATA 000,246,246,246,254

g: DATA 129,126,126,094,157

h: DATA 000,247,247,247,000

i: DATA 255,126,000,126,255

j: DATA 159,127,127,127,128

k: DATA 000,231,219,189,126

l: DATA 000,127,127,127,127

m: DATA 000,253,251,253,000

Continued


```

n: DATA 000,249,231,159,000
O: DATA 129,126,126,126,129
p: DATA 000,246,246,246,249
q: DATA 129,126,126,062,001
r: DATA 000,230,214,182,121
s: DATA 121,118,118,118,142
t: DATA 254,254,000,254,254
u: DATA 128,127,127,127,128
v: DATA 240,207,063,207,240
w: DATA 192,063,207,063,192
x: DATA 126,145,231,145,126
y: DATA 252,243,015,243,252
z: DATA 030,078,102,114,120
1 : DATA 255,125,000,127,255
2 : DATA 030,110,110,110,113
3 : DATA 118,118,118,118,137
4 : DATA 240,247,247,000,247
5 : DATA 112,118,118,118,142
6 : DATA 129,118,118,118,142
7 : DATA 254,254,254,014,240
8 : DATA 137,118,118,118,137
9 : DATA 249,246,246,054,193
star: DATA 213,227,128,227,213
excl: DATA 255,064,064,255,255
blank: DATA 255,255,255,255,255
great: DATA 255,190,221,235,247
less: DATA 255,247,235,221,190
equal: DATA 255,235,235,235,255
up: DATA 247,251,253,251,247
down: DATA 247,239,223,239,247
minus: DATA 247,247,247,247,247
plus: DATA 247,247,193,247,247
num: DATA 235,193,235,193,235
ques: DATA 254,078,238,238,241
colon: DATA 255,153,153,255,255

```

This is the software listing for a sign that displays a countdown to midnight. This version was written for and tested on New Years eve December 31 1999. Note that much of the code is the same as the previous version.

```

CLS : PRINT "Printer port sign, Copyright 1999 BY Robert J Davis"
PRINT "press q to quit"
INPUT "Use Printer Port Number: ", lpt
'Hardcoded to lpt2 for higher speed - needed for a 486.
'Make these changes for using other printer ports;
IF lpt = 2 THEN dout = &H378: cout = &H37A: cin = &H379
IF lpt = 1 THEN dout = &H3BC: cout = &H3BE: cin = &H3BD
IF lpt = 3 THEN dout = &H278: cout = &H27A: cin = &H279
newtime:
new = 1
hours$ = STR$(23 - VAL(MID$(TIME$, 1, 2)))
hours$ = MID$(hours$, 2, 2)
IF VAL(hours$) < 10 THEN hours$ = "0" + hours$
minutes$ = STR$(59 - VAL(MID$(TIME$, 4, 2)))
minutes$ = MID$(minutes$, 2, 2)
IF VAL(minutes$) < 10 THEN minutes$ = "0" + minutes$
seconds$ = STR$(59 - VAL(MID$(TIME$, 7, 2)))
seconds$ = MID$(seconds$, 2, 2)
IF VAL(seconds$) < 10 THEN seconds$ = "0" + seconds$
message$ = " " + hours$ + ":" + minutes$ + ":" + seconds$
IF hours$ = "00" AND minutes$ = "00" THEN
    IF seconds$ = "59" OR seconds$ = "58" THEN message$ = "** HAPPY *"
    IF seconds$ = "57" OR seconds$ = "56" THEN message$ = " NEW YEAR"
END IF
LOCATE 3, 2: PRINT "TIME: " + TIME$
PRINT "COUNT: " + message$

```

```

seconds$ = MID$(TIME$, 7, 2)
DIM array, byte(50)
FOR i = 1 TO 10
    letter$ = MID$(message$, i, 1)
    letter$ = UCASE$(letter$)
    SELECT CASE letter$
    CASE IS = "A": RESTORE a
    CASE IS = "B": RESTORE b
    CASE IS = "C": RESTORE c
    CASE IS = "D": RESTORE d
    CASE IS = "E": RESTORE e
    CASE IS = "F": RESTORE f
    CASE IS = "G": RESTORE g
    CASE IS = "H": RESTORE h
    CASE IS = "I": RESTORE i
    CASE IS = "J": RESTORE j
    CASE IS = "K": RESTORE k
    CASE IS = "L": RESTORE l
    CASE IS = "M": RESTORE m
    CASE IS = "N": RESTORE n
    CASE IS = "O": RESTORE o
    CASE IS = "P": RESTORE p
    CASE IS = "Q": RESTORE q
    CASE IS = "R": RESTORE r
    CASE IS = "S": RESTORE s
    CASE IS = "T": RESTORE t
    CASE IS = "U": RESTORE u
    CASE IS = "V": RESTORE v
    CASE IS = "W": RESTORE w
    CASE IS = "X": RESTORE x

```

```

CASE IS = "Y": RESTORE y
CASE IS = "Z": RESTORE z
CASE IS = "1": RESTORE 1
CASE IS = "2": RESTORE 2
CASE IS = "3": RESTORE 3
CASE IS = "4": RESTORE 4
CASE IS = "5": RESTORE 5
CASE IS = "6": RESTORE 6
CASE IS = "7": RESTORE 7
CASE IS = "8": RESTORE 8
CASE IS = "9": RESTORE 9
CASE IS = "0": RESTORE 0
CASE IS = "-": RESTORE minus
CASE IS = "+": RESTORE plus
CASE IS = "=": RESTORE equal
CASE IS = "<": RESTORE less
CASE IS = ">": RESTORE great
CASE IS = "#": RESTORE num
CASE IS = "^": RESTORE up
CASE IS = "_": RESTORE down
CASE IS = "?": RESTORE ques
CASE IS = "*": RESTORE star
CASE IS = "!": RESTORE excl
CASE IS = " ": RESTORE blank
CASE IS = ":" RESTORE colon
CASE ELSE: RESTORE blank
END SELECT
READ byte(0 + i)
READ byte(10 + i)
READ byte(20 + i)
READ byte(30 + i)
READ byte(40 + i)
NEXT i
start:
IF INKEY$ = "q" THEN END
OUT &H37A, 7: OUT &H37A, 3 'reset
FOR a = 1 TO 50
    OUT &H378, byte(a)
    IF a MOD 10 = 0 THEN
        OUT &H37A, 2: OUT &H37A, 0 'next column
        FOR t = 1 TO 300: NEXT t 'delay to display (50 = 486)
        OUT &H37A, 2: OUT &H37A, 0 'next column
    END IF
    OUT &H37A, 3: OUT &H37A, 2 'next byte
NEXT a
IF seconds$ <> MID$(TIME$, 7, 2) THEN GOTO newtime
GOTO start
END

```

```

a: DATA 003,237,238,237,003
b: DATA 000,118,118,118,137
c: DATA 129,126,126,126,189
d: DATA 000,126,126,126,129
e: DATA 000,118,118,118,126
f: DATA 000,246,246,246,254
g: DATA 129,126,126,094,157
h: DATA 000,247,247,247,000
i: DATA 255,126,000,126,255
j: DATA 159,127,127,127,128
k: DATA 000,231,219,189,126
l: DATA 000,127,127,127,127
m: DATA 000,253,251,253,000
n: DATA 000,249,231,159,000
O: DATA 129,126,126,126,129
p: DATA 000,246,246,246,249
q: DATA 129,126,126,062,001
r: DATA 000,230,214,182,121
s: DATA 121,118,118,118,142
t: DATA 254,254,000,254,254
u: DATA 128,127,127,127,128
v: DATA 240,207,063,207,240
w: DATA 192,063,207,063,192
x: DATA 126,145,231,145,126
y: DATA 252,243,015,243,252
z: DATA 030,078,102,114,120
1 : DATA 255,125,000,127,255
2 : DATA 030,110,110,110,113
3 : DATA 118,118,118,118,137
4 : DATA 240,247,247,000,247
5 : DATA 112,118,118,118,142
6 : DATA 129,118,118,118,142
7 : DATA 254,254,254,014,240
8 : DATA 137,118,118,118,137
9 : DATA 249,246,246,054,193
star: DATA 213,227,128,227,213
excl: DATA 255,064,064,255,255
blank: DATA 255,255,255,255,255
great: DATA 255,190,221,235,247
less: DATA 255,247,235,221,190
equal: DATA 255,235,235,235,255
up: DATA 247,251,253,251,247
down: DATA 247,239,223,239,247
minus: DATA 247,247,247,247,247
plus: DATA 247,247,193,247,247
num: DATA 235,193,235,193,235
ques: DATA 254,078,238,238,241
colon: DATA 255,153,153,255,255

```


but a smaller value might be used for more brightness. That is a limitation resulting from using the 74LS373; a higher voltage would damage the ICs. The 10-volt source does get connected to the TIP120s because the base of the transistors only rises to five volts and the transistor will not deliver any higher voltage in the emitter follower configuration. If the five-volt source is used instead, then the voltage regulator will get very hot due to the current that will be needed.

Assembly Hints

1. Mount electrolytic capacitors under the board laying flat against it.
2. Mount the TIP120's flat on the board and fasten them down with a copper wire or screws and nuts through their tabs.
3. The 47-ohm resistors fit best under the board soldered directly to LED arrays.
4. Pull-up resistors on the printer port control lines are not critical, they can be 1k to 10k.


The frame for the sign is made out of a one by three inch board with a 3/8-inch groove cut into it. I did not miter the corners, but that might have helped the appearance. I had to chisel a notch into the back side of the frame for the header that is used to connect to a ribbon cable that has a 25-pin male connector on its other end. A 25-pin printer type extension cord then goes to the computer's printer port.

The software was used on an old 486 laptop at first. The problem is that the 486 takes too long to load the 10 latches and lacks display time afterwards. This results in a dimmer display or one that blinks in a well-lit room. The software works best on a 100 MHz or faster Pentium computer. On such a computer, the delay for display setting can be set to 500 or even 1,000 on a faster computer.

The program has many "case" statements that seem like they could be replaced with a loop. The problem is that line titles must be identified for the restore statements. It is all right to use letters of the alphabet for line titles, but you cannot use punctuation for line titles. Hence, the punctuation lines have to be spelled out to work properly.

Another long part of the code is the data statements. They define what LEDs to light in order to produce the desired character. The confusing thing about the bytes used is that they are actually inverted. To light an LED, you need a zero or a low on the row drivers. Hence, a zero is a lit LED and a one does not light the LED.

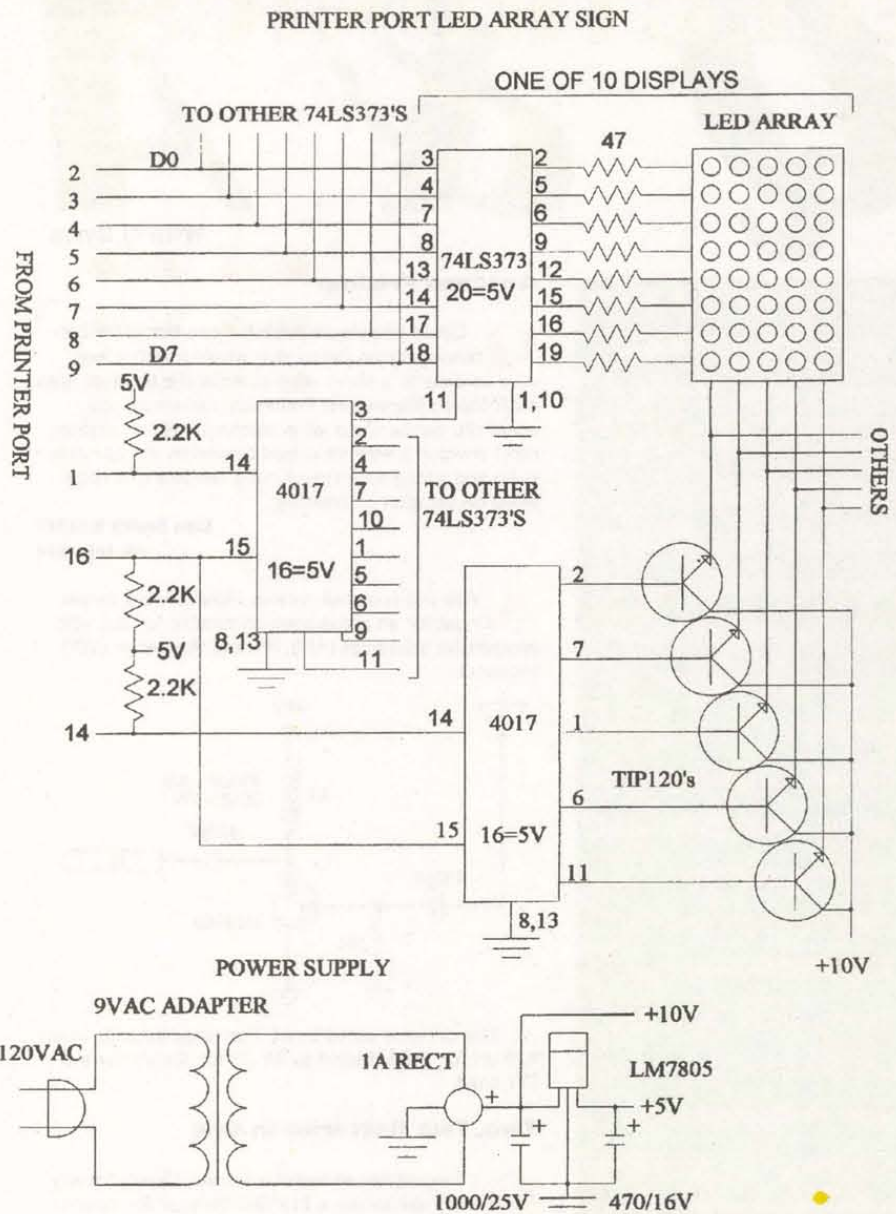To create the data statements, I drew out the pattern on graph paper then converted the lit



LEDs to binary, then octal, and subtracted the value from 255.

After a while, you might be able to do it in your head, or remember that the same bit pattern is used elsewhere and just copy it. NV

If you would like to download the software listing, go to www.nutsvolts.com.

Model PTS-10

\$55



LIFETIME WIRE STRIPPER, a breakthrough in wire stripping technology. Extremely fast tool will strip PVC insulation #14 to #30 AWG from solid, stranded or shielded wires. High quality strip is achieved by patented stripping element (.008" thick) which thermally cuts the insulation all the way to the conductor without nicks. Five year test, with over 2 million stripped wires, using the same element, speaks for itself. The stripper has won a —

"FIVE STAR PRODUCT OF THE MONTH"

award in DESIGNFAX magazine. Strippers for TFE, KAPTON, KYNAR, SILICONE RUBBER, etc. and rechargeable, battery powered strippers also available.

PATCO Service, Inc., 2515 Glencoe Rd., Baltimore, MD 21234
(410) 444-4010 Fax (410) 254-9566

Write in 161 on Reader Service Card.

SATELLITE TV — HACKERS 'BIBLE'!

The SECRETS are REVEALED!

- The principles of security
- Descrambler building blocks
- Smart cards, information wars & stupid mistakes
- Cracking codes (includes DirecTV source code)
- Installing and hooking up descramblers
- Video manipulative systems...and much more...

www.baylin.com
or... call 800-483-2423

ORDER via Internet or Send \$60 plus \$5 s/h to:
Baylin Publications, 1905 Mariposa, Boulder, CO 80302
MASTER, VISA & AMEX /COD orders accepted

FREE CATALOG — Satellite TV books, videos and software

European Scrambling Systems
John McCormack



576 pages, 6" x 8-1/2"

NEW!
5th Edition

Telephone: 303-449-4551
FAX: 303-939-8720

Write in 163 on Reader Service Card.

Nuts & Volts Magazine/May 2000 51

ELECTRONICS Q & A

With TJ Byers

In this column, I answer questions about all aspects of electronics, including computer hardware, software, circuits, electronic theory, troubleshooting, and anything else of interest to the hobbyist. Feel free to participate with your questions, as well as comments and suggestions.

You can reach me at:

TJBYERS@aol.com

or by snail mail at

Nuts & Volts Magazine,
430 Princeland Ct.,
Corona, CA 92879.

What's Up:


Two really useful preamps for your turntable and receiver, adding a utility battery to RV, and more on the magnetotach. Recycling old power transformer cores, PC software questions, some cool Web sites, and reader feedback on 70-volt audio.

Antenna Preamp

Q - Could you please publish a one-transistor, battery-operated circuit that would match a long wire antenna to a short whip antenna like the kind used on FM/aircraft/scanners? Preferably, something you could clip on the short whip antennas with an alligator clip. I envision a very small box clipped to the portable radio and a long wire strung out a window of a room while on vacation or traveling.

Don Smith K6CHS
via Internet

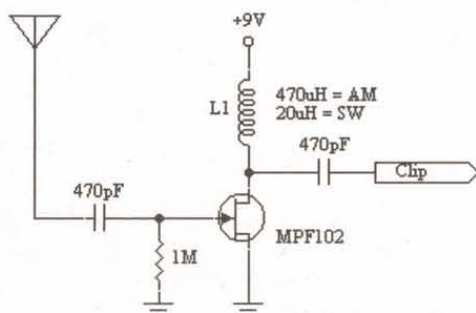A - Ask and you shall receive. Here's a very simple circuit for an active antenna suitable for use with inexpensive broadcast (AM), FM, and shortwave (SW) receivers.



The circuit is tuned by L1. The range extends from 470 uH for the AM band to 20 uH for the shortwave SW band.


Two, Two Batteries In One

Q - I would like to install a second 12-volt battery in my van to run a 115 VAC inverter for operating communications equipment, computer, printer, and maybe a cell phone with fax.

It should be able to operate independently of the van's battery — even to the point of running it to death, but not the starter battery. The circuit I am interested in is how to charge this second battery without burning out the alternator or interfering with the normal operation of the van. I'm surprised nobody wants an item like this.

Tom Reel
Milan, OH

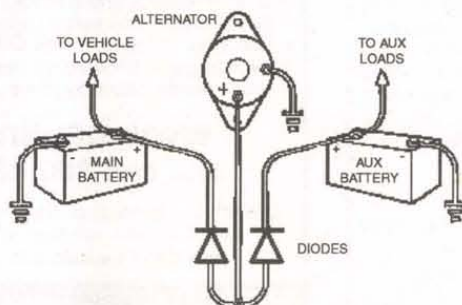A - Actually, this is a popular request. Isolation of the batteries is fairly straightforward using just two diodes. The hook-up looks like this



This places the diodes back-to-back, which prevents current from flowing from one battery to the other. When the batteries are being charged, both diodes conduct in a forward manner, and both receive a charge proportional to their needs. The appliance, on the other hand, can only draw power from the utility battery, not the van's battery — and the van can only draw current from the starter battery, not the utility battery. For this application, the diodes have to be heavy-duty alternator diodes that can handle the charging current of the battery, like the 8AF2R from International Rectifier, which is available from **Arrow Electronics (1-800-524-4735; www.arrow.com)** for a couple of bucks. Be aware that these diodes have to be mounted on a heavy-duty extrusion heatsink made by Avvid and Wakefield, among others (also available from Arrow Electronics). If this sounds like more than you want to tackle, you can buy battery isolators from most RV supply houses, like **Camping World (www.camping-world.com)**, and all marine supply outlets.




Sure Power Multi-Battery Isolator

Phono Preamp

Q - I have over 600 vinyl discs and would like to record them to CD. However, the sound card in my computer requires line input and the turntable output will not drive the sound card. What I require is a stereo phono preamp, like the kind RadioShack used to stock but no longer sells. I was wondering if you could supply a nifty circuit, or perhaps know of a dealer that may have such a device ready-assembled?

Marshall D. Landers
via Internet

A - Velleman Kits (817-284-7785; www.velleman.be/) sells an RIAA stereo phono preamp K2572 kit for \$13.82. Velleman Kits are stocked by many electronic supply stores, including **Jameco (1-800-831-4242; www.jameco.com)** and **Tech America (www.radioshack.com)**, and several hobby shops. Unlike a universal microphone preamp, the kind often used for karaoke mikes, the K2572 has frequency compensation to match the frequency response of a phono pick-up cartridge, which needs the lower frequencies attenuated and the upper frequencies emphasized, as shown below.

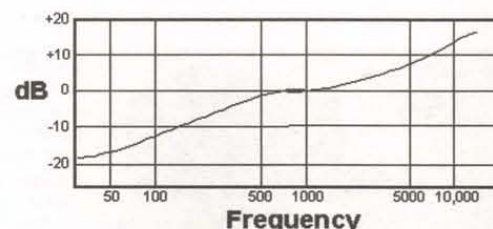


RIAA Phono Equalization Curve

The technical specifications of the RIAA curve are specified at the following conditions.

- Amplification (1 kHz): 0 dB
- Input impedance: 47k
- RIAA curve
- Input signal: 5 mV to 10 mV

You can also build your own RIAA equalized phono

preamplifier using this circuit.

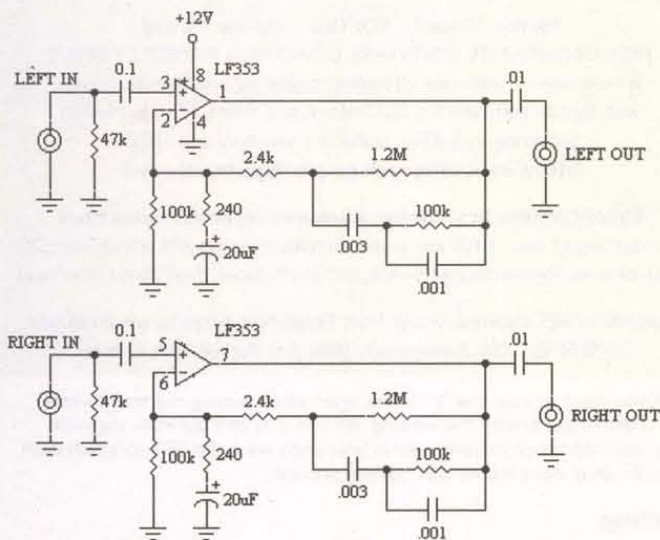

Basically, it's an active filter with a ladder-T feedback loop. While any op-amp should work in this circuit, I chose an FET op-amp over a BiCMOS or bipolar op-amp because it has characteristics similar to those found in vacuum tube amplifiers — traits that many audiophiles find desirable. The gain of the amplifier is about 35 dB, which is plenty enough to drive your sound card. For best operation, the 12-volt power source should be stabilized using an LM7812 voltage regulator.

Notebook Contacts

Q I have a GRiD Model 2050 GridPad SLI that has a 17.5 VDC, 1.5 A charger with a four-pin connector. Do you have any information or can you lead me to a Web site that can give me the information to the pinout of this product? I'd like to build a power supply capable of recharging its battery. I've put a surface charge on the battery, installed it, and then used my DDM to probe the four-pin connector for the presence of voltage. What I found were two pins that had some DC presence, but I wasn't sure if it would be safe to just hit them with a charging current without knowing what the other two pins did.

Larry Fostano
via Internet

A Two pins connect to the battery terminals (plus and minus) and the other two connect to a thermistor that's in physical contact with the battery. To make a long story short, you can determine the charge in a battery simply by monitoring the battery's temperature. Call it a battery thermometer. When the battery's temperature is low, it's safe to apply full charge to it — typically C/2 or C/4, depending on the battery's chemistry. As the charge accumulates in the battery, its temperature rises and the charge current has to be reduced to C/10 or less. Unfortunately, I can't find a pinout for this connector, but I can tell you that it has a twin — the Tandy 2050, and you may be able to wrangle a pinout from their RadioShack repair services. A good Web site for notebook repairs and parts is **National Computer Support (281-734-1348; <http://www.laptop-notebook.com/index.html>)**.

Motorbike Tachometer Revisited

Q I have two questions regarding the Motorbike Tachometer article in the Jan. 2000 issue.

1) What kind of transformer (ratings, part number, etc.) would you use to pre-test the tach circuit before hooking up the sensor coil? The article doesn't say.

2) Instead of an analog (i.e., needle) current meter for the RPM display, can a digital voltage or current meter be connected to the circuit to get a digital RPM display instead?

Bruce Morgenstern
via Internet


Q I haven't been able to find this SMD. Any thoughts as to a source?

Tony Serra
via Internet

A The Jan. 2000 answer wasn't intended to be a full-blown tachometer solution, but it seems to have gone that direction. So let me fledge it out the best I can in this limited space. For those readers who missed that installment, here's a brief recap of the question.

Q I have a motorized bicycle powered by a small two-stroke gasoline engine that I'm having a problem with. It keeps cutting in and out. Is there a circuit (or a commercial product) to tell whether or not the spark is still there when the engine cuts out, thereby indicating a fuel problem?

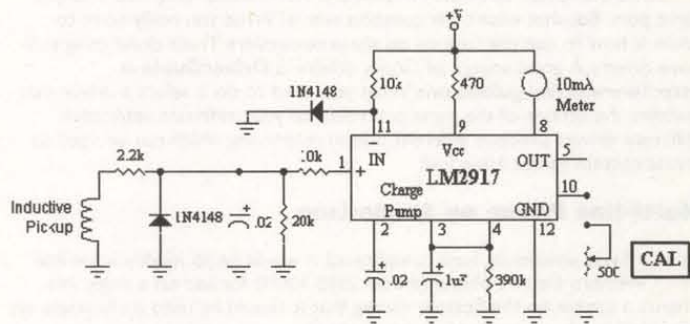
A How about a tachometer? Not only will it tell you if there's a spark or not, but it'll display the RPM speed of the engine. Here's a simple 12-volt (actually, 8 to 16 volts) circuit built around an LM2917 frequency-to-voltage converter chip.



Okay, now that we're up-to-date, let me fill in the blanks. The transformer used to test and calibrate the circuit is nothing more than a small 12-volt transformer, like the RadioShack 273-1385 (12.6 volts at 300 mA). For this test, you simply rectify the output of the transformer using a 1N4001 diode and input the signal to the tachometer. The output frequency is equal to 60 (Hz) x 60 sec = 3600 RPM (revolutions per minute).



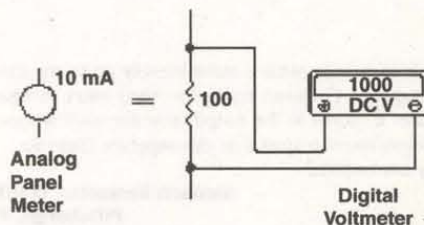The original design specifically called for an analog meter, but you're welcome to substitute a DMM or DVM as you like using the following modification.



As for the inductor, it's a J.V. Miller PM40-101K, which is stocked by **Digi-Key (1-800-344-4539; www.digikey.com)** and **Mouser Electronics (1-800-346-6873; www.mouser.com)**.

When 16MB RAM was King

Q I have an AT Memory Expansion card that plugs into the computer expansion slots.

On the board, I read "8 meg AT RAM." There are 36 memory chips on the board with 18-pin chip sockets to add 18 more chips. Most chips are numbered AAA1M200P-08H, but two are numbered KM41C1000AP-8. I find no FCC ID number and no manufacturer ID on the board, but there's an IC labeled

"M60030-1009J"
BOCA RESEARCH
PN 1945
038100

I installed the board in my NEC PowerMate Portable SX, but my computer doesn't recognize the board. I suspect that I need a driver or other software to implement this expansion. I called BOCA, but they weren't able to tell me anything. Can you tell me what I need and where to find it?

Oliver Curtis Powell
wb4waa@coastalnet.com

A Boy, this question takes me back to the days of old when 16 MB of RAM was the absolute limit. Fortunately, I now have 128 MB of RAM and yearn for more, but back to your problem. Yes, you're right; you need a soft-

were driver. Specifically, it's an extended memory manager (EMM) from Boca Research to access the BIOS chip on this card. Unfortunately, I don't have a copy of that driver anymore, but maybe one of our readers has one they'd like to share. It can be found bundled with most Zeos systems sporting an 80286 CPU.

No Joy without Pinout

Q Do you know the pinouts for the Gravis GamePad, Gravis Phoenix, and the Gravis XTerminator?

**Cory
via Internet**

A Sure, the GamePad pinout is either a 15-pin game plug or a four-pin USB connector. Both the Phoenix and Xterminator plug into a 15-pin game port. But that wasn't the question, was it? What you really want to know is how to use the buttons on these controllers. That's done using software drivers. A good source of Gravis drivers is **DriverGuide** at <http://www.driverguide.com>. What you need to do is select a driver that matches the actions of the game controller to your software application. Different drivers produce different button responses, which can be used to create custom games. Have fun!

Multi-line Phone on Single Line

Q I was wondering how complicated it would be to modify a five-line Western Electric phone (model 2565 HKM) for use on a single line. There's a sticker on the bottom stating that it should be used on business systems only, or there is risk of electrical shock.

**Peter Stratigos
via Internet**

A The Western Electric 2565 and its kin, the ITT 2568M, are high-quality desk telephones that plug into a standard 50-pin "telephone" connector or are hard-wired into a phone wire closet. Phone cable generally contains two wire pairs, which are color-coded. The first pair is green and red, and the second is black and yellow. A way to remember this is by the holidays Christmas and Halloween. After that, the wires are generally color-striped. What does this have to do with you? Everything, in that your 50-pin connector has more than just phone signals — there's power there, too, which is why Western Electric posts the warning. As for the modification, I'd sell the phone to someone who can use it (current market price is \$49.00).

Magnetic "E"

Q I'm an electronic repair technician who is quite literally up to my ears in old switching power supplies. I've been trying for many years to figure out how to separate the double "E" cores in the output transformers without success. Is there any magic potion/Voodoo spell that can separate them so that I can rewind them for my own needs?

**Stephen Varnecky W310D
Pittsburgh, PA**

A They are held together with varnish, which you can dissolve using any of the acute solvents. Back in the days of old, I would use MEK (methyl-ethyl ketone), but I doubt you can buy it over the counter today. Try a paint or varnish stripper. Simply soak the "E"s overnight and they will slip apart.

Cool Web Sites

Movies! Movies! SOFTIPS Movies! Movies!
FREE ONE-MINUTE SOFTWARE COACHING MOVIES BY EMAIL
A revolution in software e-learning: streaming one-minute movies with tips on software like IE, Outlook, and Word. (Vive le Movie!)
Subscribe to SofTips today! It's way cool and FREE!
<http://www.softcoach.com/softips.html?wow7>

CyberCircuits, <http://www.uslink.net/~cybercir/index.html>
A collection of over 1,100 electronic circuits, including AM transmitter, DC lamp dimmer, voice-activated switch, and much more. Free demo download.
Get 100% FREE Internet Access from **Freei.Net** <http://www.freei.net>.
100% FREE, 100% Anonymous, 100% Jam Packed with features.

BTW, you need to coat the "E" leaves again when putting the transformer back together, otherwise the winding will see it as one big iron-ring with about zero efficiency. In other words, you don't want the "E"s to touch each other, which is what the varnish coating prevents.

Mailbag

Thanks for the response to my question ("Two, Two Batteries in One," above). I purchased the isolator from Camping World, and I'm in the process of installing the second battery system. However, I now find that since I have a 1998 Ford Van, the alternator needs an isolator with "excitation" to operate, which I should obtain shortly. There are other considerations that I discovered while doing this conversion that I'd like to share with the readers. Such as vapors from the battery, battery tie downs (it would be no fun having battery acid flying around inside the van), proper wire size, and circuit breakers in case the wires become frayed or exposed. See www.surepower.com/pdfs/180012.pdf for more details on various installation options.

**Tom Reel
Milan, OH**

Dear TJ:

I read your Q & A response to 70-volt line audio today and need to point out a potentially serious error. At the end of the answer, you suggest that reversing a 70-volt speaker transformer will make a suitable "output" transformer for converting a conventional amp to 70 volts. The problem is that the eight-ohm winding's impedance is actually lower than eight ohms — more on the order of one ohm. This is because it "sources" the eight-ohm speaker. I have seen amps "burn up" from doing just this.

If you add a series eight- or four-ohm resistor (depending on the amp) with the secondary winding of the 70-volt transformer, it will protect the amp from overload. Yes, it is inefficient, but it's a lot cheaper than a new amp.

On occasion, I have driven both 25- and 70-volt lines with a standard eight-ohm output amp (of sufficient power) with no transformer. A 100-watt, 70-volt load is only a 50-ohm load in the eyes of the amp, while a 75-watt, 25-volt load is six ohms.

I've been installing and servicing sound systems for over 20 years, and other than this one issue, you gave a very good explanation of the subject.

**Chris Snyder KD40GD
Cosby, TN**

Dear TJ:

I suppose I'm not the first to point out the glaring mis-calculation on page 25 of the Mar. 2000 issue concerning the 70-volt audio question. In the example cited, you said that a 100-watt amplifier would only deliver 50 watts to an eight-ohm speaker through eight ohms of cable. But, if you do the math, you'll find that a 100-watt amplifier will only deliver 25 watts to an eight-ohm speaker through eight ohms of cable. While it's true that the voltage in the scenario is halved, the current is also halved, thus 1/2 the voltage times 1/2 the current equals 1/4 the power. I caught this immediately because I design and work with these systems on a daily basis.

**Dan Lash
Expanets of IN**

Response:

Obviously, the result of another long session of burning the midnight oil. Yes, you're absolutely right. Power is the product of both current and voltage ($P = EI$), so the correct answer is 25 watts, not 50 watts. Thanks for setting the record straight.

**TJ Byers
Q & A Editor**



**Motron
ELECTRONICS**

<http://www.motron.com/>

PO Box 2748
Eugene OR 97402-0280
(541) 687-2118

DTMF Controller
Only \$149.00 Plus SH



The **Auto-Kall® AK-16** DTMF Controller Board features 16 relay driver outputs and DTMF to X-10 house control capability! Control the relay driver outputs, X-10 modules, or both with your radio keypad! X-10 operation requires the PL-513 Power Line Interface (\$20). The **AK-16** mates readily with our **RB-8/10** (\$99) or **RB-16/10** (\$149) relay boards. The 0-12 digit security code is user programmable using your DTMF keypad. Additional features include re-programmable CW ID and several modes of operation, including two with CW response. The **AK-16** is a fully assembled and tested printed circuit board.

Price and Specifications are subject to change without notice.

Visa, MasterCard, American Express, Discover
And Government Purchase Orders accepted.
Sht. \$8 USA; \$11 Canada; \$16 Foreign
Se Habla Español. Pida Por Don Moser.





Info: (541) 687-2118

Orders: (800) 338-9058

Fax: (541) 687-2492

We accept Visa,
Mastercard, AmEx,
and Discover

Attention: Nerds-Geeks

Fax: 318-424-9771

To Order Call 1-800-227-3971

www.shrevesystems.com

MONITOR BLOWOUT!

19"-21" fixed res 1024 X 768

ONLY....\$49 as is



H.P. 17" fixed res 832 X 724

ONLY....\$99 30 Day

Warranty



13"-14" fixed res 640 X 480

ONLY....\$25 as is



H.P. 17" fixed res 640 X 480

ONLY....\$99 30 Day

Warranty



15" Radius Pivot


ONLY....\$25 as is



16" Rasterops fixed 832 X 624

ONLY....\$99 30 Day

Warranty

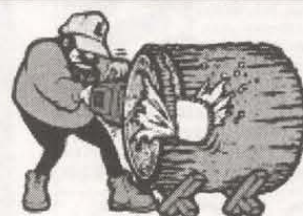

Build your own Mac!



PowerMac 7200
75 Mhz PPC 601
4 168 pin DIMM slots
**\$49 Brand
New!**



ClarisWorks 3.0

PC/Mac hybrid disk

ONLY \$29



Centris 650

Logic Board

ONLY \$29



LC Power Supply

+5V, -5V, +12V Output
\$5 New



Newton Message Pad

120

\$99 refurbished

While Supplies Last!



Peltier Junction

with heat sink, works on 5V & 12V
1 3/16x 1 3/16

\$10 each or 3 for \$25

MacAllly ADB Keyboard



\$19

PAS16 Audio Spectrum

16 Bit Sound Editing Card

Multi-track editing for LC or LCII



**ONLY
\$19**

CMS Tower SCSI Case

Holds 4 5.25 full height drives



\$79



Apple Color
Composite Display
Great for Surveillance
Refurbished \$69

Global Village Bronze

External Modem
2400 Bps/9600 Fax

\$1 Each



RAM

1 MB 30 Pin 4 For \$1
4 MB 72 Pin 2 For \$5

Apple II 256K Memory Expansion Kit

HM51256P-10 **ONLY \$1**



Apple IIE Logic Board
\$19



Curtis ADB Track Ball

\$19



Apple
Remote
Control

\$5 EACH

Drive Lock Security System for
Portable Computers-protects your
data if lost or stolen!

ONLY.....\$5



\$5

PDA Genuine
Leather Carry
Case
Let your palm
pilot lead the life
of luxury!



Membrane
Track Pad for
laptop **\$2**

Miscellaneous

Apple 8 bit Video Card	\$19
LaserWriter IINT	\$199
Apple ADB Keyboard	\$19
1.44 Super Drive	\$49
Clone ADB Mousell	\$19
Quicktake 100 Camera	\$99
Bernoulli 90 MB EXT	\$10
44MB SyQuest Ext	\$10
88MB SyQuest Ext	\$19

**\$25 minimum
order**

Shreve Systems

1200 Marshall st
Shreveport, La 71101

Returns subject to a 15% restocking fee.

Prices are subject to change without notice. We accept Visa,
Mastercard, AmEx, Discover

SINGLE CHIP COMPUTER!

Zero External Components
Built-in BASIC / Assembly
RS232 Program Download
1K flash, 64ee, 3irq, 2timers
15 I/O bits, A/D comparator
20mips, faster than pic8051
20 pin DIP part #MV1200

\$1.99 OEM (1K)
EVAL KIT
(1) \$7.00



NEW! 8K SUPER CHIP

Improved BTERP with 40 times the BASIC program capacity
40 pin DIP part #MV8515 - 32 I/O, 12 irq, 3 timers, bus
8K flash, 512 ee, 512 nram - Watchdog with internal osc.
\$5.40 OEM (1k), Eval Kit \$19.00

PC SOLID STATE DISK



\$21 OEM (1k), EVAL \$75
FLASH, NVRAM, ROM
256K-16M DIP/PCMCIA

\$95 UNIVERSAL PROGRAMMER



FLASH, EPROM, NVRAM, EEPROM
to 8meg (27080). Adapters for micros,
PLCC, etc.. Parallel port version for
notebooks. FAST and EASY TO USE.

PC WATCHDOG!

NO MORE HANGUPS..
Reboots PC on hardware
or software hangup..
oem \$21, eval \$75



LCD VGA \$27



OEM (1k), eval \$95
640x480 controller
use with PC or SBC

\$27 MINI PC

\$27 OEM, Eval \$95, Includes:
DOS, 3 ser, 2 par, rtc, NVmem,
Built-in LED display, ISA bus,
Keyboard and LCD interfaces.
COMPLETE !!!
Not a "core" or "engine". All
utilities and tutorial included.
Use Turbo C, BASIC, MASM.
386 version: \$42 oem, \$195 eval



WWW.STAR.NET/PEOPLE/~MVS
MVS Box 850
Merr., NH 03054
(508) 792 9507



Write in 40 on Reader Service Card.

DesignNotes.com

Your Design Resource on the Web

Improve Your Design
Skills, Find Project
Advice and More

Win up to \$1200

Free Circuits

Online Tutorials

Design S/W

Eqpmt Specials

Design Help

Online Forum

Free Literature

Cool Links

Internet Distributor for
**Mental Automation
Inc.**

Schematic capture, PCB layout &
Simulation Software

Easiest & Most Complete CAD
Package for the Price!

Try Out Our Free On-Line Demo


Share What You Know and
Learn What You Don't

Visit Us at
www.designnotes.com

Write in 41 on Reader Service Card.

Continued from page 42

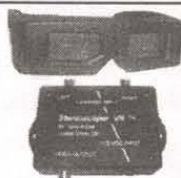SYNC-A-LINK UNIVERSAL video sync generators. For more details phone 918-479-6451, E-Mail: rlc@sstelco.com or write to **Sync-A-Link**, PO Box 4, Locust Grove, OK 74352.



STEREOSCOPER VR is a stereo multiplexer that creates 3D stereoscopic video from two genlock cameras. Stereoscopers VR comes with LCS glasses and driver. 90 day warranty \$247 or write to **Sync-A-Link**, PO Box 4, Locust Grove, OK 74352. Phone 918-479-6451, E-Mail: rlc@sstelco.com

CABLE TV

GENUINE UNMODIFIED JERROLD DPBB 7312. 410-485-7772. E-MAIL: CLEWIS7298@AOL.COM

NEW IN BOX 860MHz analog converters. Enjoy the newest technology CATV equipment can offer along with superior quality all in one unit. Channel output 3 or 4. HRC, IRC, standard switchable. Includes 1 set of audio/video cables, 1 RF quick connect cable and remote control. Parental control, sleep timer, last channel recall, memory 1 thru 4, and volume control are all available on remote. Minimum order taken for 10 pcs. at \$59.95 each. \$49.95 for 50 pc. order. Significant savings on larger quantities. Call 706-657-4445.

DISCOUNT CABLE converters, bullet snoopers, all makes and models: Genuine unmodified General Instrument, Jerrold, Tocom, Scientific Atlanta, Zenith, Pioneer, Panasonic and more. Best warranty. Free catalog 1-800-243-0962.

SONY PLAYSTATION MODCHIPS. Allows playing of CDR backups & imports. \$10 + \$3 shipping. 619-590-9320.

UNMODIFIED JERROLD DPV-5 CONVERTERS, \$25 ea. 10 lot min. Call 651-426-4435.

NEW! CABLE converter electronic service equipment and supplies for most cable converter boxes. Highest service, lowest prices. Call Ken Emry Electronics. 24 hr. order and information hot line 516-389-3536.



NOTCH FILTERS 110, 108.5, 106.5, 97.5 75dB deep notch. \$19.95 ea., 1-5 qty. \$15.95 ea., 6-10 qty. \$11.95 ea., 11-20 qty. \$9.95 ea., 21 or more qty. Call 24 hr. order and information hot line 516-389-3536.

CABLE PARTS & EVERYTHING. Best prices & quantity discounts. WE DON'T SELL BOXES. 1-800-MODULE-0.

CABLE CONVERTERS. Original equipment with remote. Like new. Lowest prices. Guaranteed, ready to go. Limited models. Call for flyer 412-833-0773.

CABLE BOX remotes, \$3 to \$4 each. Zenith tuners like new \$5. Zenith power supplies \$4 each. Prepaid shipping on Zenith parts only. Repair work on ST 1000 to ST 1086 available. 702-737-4727.

CABLE TV. Unmodified converters DP5 \$35; DPBB7 \$80; 8500 series \$15, etc., good prices over 100 pcs. Minimum 10 pcs. any qty., plus all major brands available. Lowest price new/refurbished/field pulls. Phone: 1-800-929-1549.

UNMODIFIED CABLE CONVERTERS. Zenith ST1600, ST1086, ST300, Panasonic 175, 145 vol. & non-vol. Regal RR-92 & RC 83, DP5, DP7, DRZ, 5503 VIP, SA 8580. Guaranteed low prices. Please call for more converters 405-631-1856.

POSITIVE NOTCH FILTERS. All channels available. Starting at \$16 each. Order by single channel #. Top quality non-tunable metal cylinder type. 75dB deep on the notch. Need to block the video on a cable channel? Order a negative notch filter. We carry a large stock on all channels for dealers and vendors. VISA, MASTERCARD, DISCOVER, and UPS COD for established customers. Quantity pricing on 5 or more. 100 pcs. \$7 each. Open 8am to 5pm CST, Monday-Friday. All sales must comply with FCC 1996 Cable Act. On the web go to WWW.GOFILTERS.COM "THE FILTER COMPANY." Call for all orders 1-800-235-8080.

Electro Mavin

Great Buys - Great Products - Great Gadgets
Check Out Our Great WebSite at

<http://mavin.com>

For Computer Items, Hobbies Projects,
Microwave Goodies and Some of the
Greatest Prices on the Web....

800-421-2442 or FAX 310-632-3557

E-Mail

john@mavin.com or mark@mavin.com

Weeder Technologies



RS-232 Stackable

www.weedtech.com

Data Book Available

850-863-5723

Digital I/O Module - 14 I/O pins individually configured for input or output. Turn on/off relays. Sense switch transitions, button presses, 4x4 matrix decoding using auto-debounce and repeat. One-shot pulse output with user programmable length. \$49

Analogue Input Module - 8 input pins. 12-bit plus sign self-calibrating ADC reads voltages from 0 to 4095 mV using 1 mV resolution. Supports single-ended, differential, or pseudo-differential modes. Software programmable alarm trip-points for each input. \$59

Stepper Motor Driver - Drives a unipolar stepper motor rated up to 25VDC @ 2A. Uses automatic self-generated parabolic acceleration/deceleration curves for smooth start and stop motion. Software programmable ramp-rate and speed. 24-bit absolute motor position counter. Limit-switch input. \$59

Pulse Counter/Timer - Read frequency from 0.50000 to 1,500.00 Hz using floating decimal point and 5-digit resolution throughout range. Measure period, RPM, duty cycle, pulse length, velocity of a projectile using a pair of trip wires. Accumulate pulse count. \$69

Multi-Drop Peripheral Interface Plug a third-party RS-232 peripheral into the multi-drop bus. Appended header character allows PC to exclusively communicate with each of up to 32 devices. Supports peripheral baud rates of 75, 150, 300, 600, 1200, 1800, 2400 and 9600. Built-in 122-byte FIFO RAM buffer. \$59

Plug
end-to-end.

Stack 32 modules on
the same RS-232 cable.

ATTN. DEALERS: Plo BA-6110 (raw) \$59; Zenith ST-1600 (600MHz, 99 true, ch.) only \$39; Zenith ST-1601 \$59, minimum 10-lot. Call for free catalog, 1-800-354-7719.


DSS, SATELLITE equipment. Large website. Auctions, forums, files, codes. Call now 1-888-451-0083.

CABLE PARTS! Computer parts. Call for great prices or visit us on the Web: [HTTP://WWW.CB-Electronics.com](http://WWW.CB-Electronics.com) or call 1-800-436-8630.

THE WIZARD SAYS check out our prices. Cable parts and huge sale on raw boxes. 1-888-79-CHIPS. www.chipwizards.com

NEW IN BOX 860MHz analog converters. Enjoy the newest technology CATV equipment can offer along with superior quality all in one unit. Channel output 3 or 4. HRC, IRC, standard switchable. Includes 1 set of audio/video cables, 1 RF quick connect cable and remote control. Parental control, sleep timer, last channel recall, memory 1 thru 4, and volume control are all available on remote. Minimum order taken for 10 pcs. at \$59.95 each. \$49.95 for 50 pc. order. Significant savings on larger quantities. Call 706-657-4445.

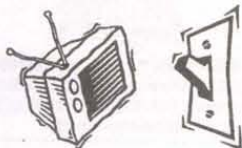ONE STOP for all your cable needs. New plain converters, parts, remotes, tools, bits, PICs, MC68HC705, EPROM-2764, toggle switches, push buttons, double sided foam tape (2" x 35 yds.) even 3M packing tape (2" x 110 yds.). Call us last, guaranteed low prices and best service. 405-634-1535.



EXPLOSIVE CABLE TV GRAB! BRINKER ZAPPER/SNOOPER STOPPER combo module all in one! Buy wholesale factory direct, no middleman. Let others get fined + zapped instead. 100% COMPATIBLE. Your order shipped NATIONWIDE immediately! LIFE-TIME GUARANTEE! VISA/MC/AMEX/COD/MO/CHECKS. ONLY \$10 (SPECIAL: 3/\$20 plus FREE DESCRAMBLER PLANS!). SUPER ZAPPER MODULES ONLY \$16! (3/\$33)! Use SUPER ZAPPERS if you have COX, TCI, WARNER, DESCRAMBLER PLANS (4=\$5, 20=\$15). 130+ DESCRAMBLER SOURCES (\$5). YEAR 2000 CABLE TV HACKER SECRETS BIBLE. Includes: 15 TEST device plans, installation instructions, master source code, CD-ROM, book/manual, what works, what doesn't. MUCH, MUCH MORE! WHOLESALE \$29. FREE SHIPPING. OPEN 24 HOURS! 352-326-3720. BRINKER ENGINEERING LABS, USA. 614 E. HWY 50 #404, CLERMONT, FL 34711. E-MAIL: brinker@mailcity.com

TELEPHONE/FAX

DSS, SATELLITE equipment. Large website. Auctions, forums, files, codes. Call now 1-888-451-0083.

PHONE SYSTEMS WANTED!!! We buy AT&T MERLIN, SYSTEM 25/75/85 and other AT&T phone systems. Please call for a quote or fax us your equipment list. **KEYWAYS, INC.**, 937-847-2300 or FAX 937-847-2350.



CELLULAR CLONING COLLECTION. 2000 CELLULAR CLONING INFO BIBLE \$22, 2000 CELLULAR CLONING SOFTWARE COLLECTION \$33, 2000 CELLULAR SECRETS & PROGRAMMING MANUAL \$11. ALL 3 FOR \$44, WOW!! (SAVE \$22). FOR EDUCATIONAL/TECHNICIAN TESTING USE ONLY. (VISA/MC/AMEX/

COD). OPEN 24 HOURS! 352-326-3720. BRINKER ENGINEERING LABS, USA. 614 E. HWY 50 #404, CLERMONT, FL 34711. E-MAIL: brinker@mailcity.com

COMPONENTS

WANTED: MILITARY capacitors, resistors, transistors, diodes, ICs, semi's, etc. Please fax/E-Mail excess lists & RFQs 818-769-1002 fax 818-769-1084. electmatind@earthlink.net & <http://www.militarycomponents.com>

RF TRANSISTORS, TUBES, SD1446, MRF455, MRF454, 2SC2290, 2SC1969, 2SC2166, 2SB754, TA7222AP, 2SC1947, TIP42C, KIA7217, MRF422, MRF448, MRF247, MRF317, SAV7, SAV17, 3-500ZG, 4CX250B, 572B, 3CX400A7/8874, 3CX3000A7, 4CX400A, silver mica caps, resistors, electrolytics, etc. Westgate 1-800-213-4563.

WANT TO Buy: ICs, military & aircraft relays, diodes, transistors, Cannon, TRW, Amp, Burndy, Deutsch, Bendix connectors, electronic test equipment & most components. Hoffer Electronic Ent., 818-718-1165, FAX 818-341-5506. E-Mail: Hoffel165@aol.com



SCSI HARD DRIVE KIT

Ideal for older system upgrade or newer system expansion. Great second drive for added storage or backup.

• 2.13GB Quantum Fireball 3 1/2" Disk Drive, with proven, reliable design, fast access and data rate. Prepared FAT32 for Win 95/98.

• NCR 53C00 based ISA half card SCSI controller is easy to install and has onboard terminator. Ballard firmware runs on XT, 286, 386, 486 or Pentium. Internal (50 pin) and external (25 pin Apple type) connectors. Interfaces 7 internal and/or external (Apple type cable) SCSI devices.

• Manual, software and two-drive flat ribbon internal cable included.

20C003 \$69.95 each



PENTIUM PRO COOLING FAN

12VDC, 0.08A, with heatsink. Sanyo Denki #109P6612H2036.

98F003 \$15.00 each

250 WATT TRANSISTOR PAIR

Complementary pair MJ15024 (NPN) and MJ15025 (PNP), used for high power audio and other linear applications. Over 100W RMS power output. 250 PD Watts @ 25°C. 250 VCEO. 15/60 °FE @ Min/Max. 8 IC Amps. 8 FT MHz typical. 80 V @ 2.2A ISB. Application notes included. Sold as pair only.

96S001 \$9.95/Pr.

22 GAUGE WIRE

100' Spools Solid Wire. New Lower Pricing. Shipping Weight 7 oz.

Order # Price

JW100BE - Blue \$3.95

JW100BK - Black 3.95

JW100BR - Brown 3.95

JW100GR - Green 3.95

JW100GY - Grey 3.95

JW100RD - Red 3.95

JW100RG - Orange 3.95

JW100WT - White 3.95

JW100YL - Yellow 3.95

TINY B/W CAMERA

This black and white camera with 3.6mm lens has 430 lines of resolution at 0.03 Lux minimum illumination. Metal housing, 25mm sq. x 16mm. 8-12VDC (9V standard) @ 80mA. Includes 9V AC adapter.

20V001 \$89.95 each

"SOLAR BABY"

Open circuit: 18.5V. Peak power: 15VDC at 333mA (5W). Ideal for recharging lead acid batteries. Sturdy aluminum frame on fiberglass-backed panel measures slightly less than 11" square. Wires included for easy hookup.

98E024 \$58.00 each

H-P MICROWAVE TRANSISTOR

Stripline 35828E. 10-13 dB gain at 2 GHz, usable to 6 GHz. Noise figure 2 dB typical at 2 GHz. 25V, 35mA, 600 mW maximum ratings. 17.5 dB (-50 mW) at 1dB compression.

10 for \$45.00

93S008 \$4.99 each

AMIDON SPLIT CORES

• 2-1/2" L x 1-1/8" W x 1/2" D assembled.
2X43-951 \$7.73/set
• 3-1/4" L x 1-1/4" W x 5/8" D with plastic case.
2X43-051 \$9.95/set

ION PROPULSION MOTOR

This amazing device demonstrates the basic propulsion principles used in NASA's Deep Space 1 ion engine! The Ion Motor creates a high voltage potential that generates four streams of "ION WIND". The ion streams exert a reactive force that spins the rotor like a top. This item makes a great science fair project or an interesting desktop toy. The Ion Motor also generates negative ions which can reduce pollen and pollution in the air to produce a healthier environment.

99K001 \$29.00 each

GENUINE 14X JEWELER'S LOUPE

High-quality glass Hastings Triplet flat field loupe made in the USA by Bausch & Lomb. If you're in the field searching part numbers on components or serial numbers on equipment, this little gem could pay for itself the first time you use it.

99Z003 \$29.95 each

HIGH VOLTAGE CERAMIC DISC CAPACITOR

2500pF @ 10KV high current. 60 Amp maximum. Dimensions: 5.25"D x 2"H.

99P004 \$80.00

BLACK (UV) LIGHT

Avon "Derma-Spec" imager designed for skin evaluation, but ideal for many other applications. Plastic case contains a UV-B bulb and reflector. Auto turn-off after 50 seconds. Powered by 12VDC @ 500mA wallwart (not included).

98L009 \$7.95

50-LB. CARE PACKAGE

Surplus goodies from Silicon Valley. This is not junk, just material we've acquired in quantities too small to catalog - electronic and mechanical subassemblies for everything from robots to rockets. Assortments may include ICs, caps, connectors, bearings, diodes, hardware, circuit boards, cables. Weird and wonderful stuff. Most folks are happy with the assortments we send and we often get re-orders. Try one.

92U034 50 Lbs/\$49.95

HEXA-DECIMAL DISPLAY WITH LOGIC

TIL311, with docs! Red, high-brightness, 0.3" tall LED with 4x7 alphanumeric display and left and right decimals. Internal integrated TTL MSI chip with latch, decoder and drivers. Visible from a wide viewing angle. Good for direct bus connections.

93S033 \$9.95 each



ULTRASONIC TRANSDUCER

Polaroid transducer is used for measuring distance and object detection. Operating frequency 50-60KHz. Nom. bias 150VDC, Nom. AC drive 150VAC peak, max. combined 400V. Nom. capacitance @ 1KHz 400-500pF. Documentation included.

99U001 \$19.95



MINI HEAT GUN II® and HEAT SHRINK TUBING

• Small, compact, lightweight heat gun with nozzle temperature to 1000°F. Uses standard 110VAC outlet. 6-foot electrical cord with workbench storage loop. U/L recognized.

• 60 pieces of heat shrink tubing from 1/8" to 1/2". Tubing shrinks to half original diameter.

20Z003 \$39.95 each

UNIPOLAR STEPPER MOTOR DRIVER IC

UCN5804. Drives a unipolar stepper in one of three operating modes: single phase, two phase or half step. Up to 1.25 Amps per phase. Step and direction input. Drive with a 555 timer, parallel port, etc. Build your own robot, anything that requires precision positioning.

93I002 \$4.50 each

PULSE MOTOR

42mm dia., 22mm thick. Shaft: 3mm dia. x 12mm long, with 13-tooth gear approx 16.6mm dia x 5mm thick. 7.5°/step, 48s/rev., 12VDC, 50Ω, 6-wire. With spec sheet.

92M010 \$3.95

COMBO PACK!

One 93I002 IC and 92M010 motor (both shown above) with schematics.

93I003 \$7.95/set



ALLTRONICS
2300-D Zanker Road - San Jose, CA 95131-1114
(408) 943-9773 - Fax (408) 943-9776

Send \$3.00 (US, \$4.50 foreign) for our Millennium Catalog!

Store Hours: 9-6 M-F & 10-3 Sat. - Pacific Visa, MC, AmEx Accepted All Sales Final. California Residents Add Sales Tax. Shipping Additional on All Orders. Prices Subject to Change Without Notice. Prices Good 90 Days from Date of Publication.

Download our New Catalog!
<http://www.alltronics.com>



The RF Connection
213 North Frederick Ave.
Suite 11N
Gaithersburg, MD USA
20877

<http://www.therfc.com/>

Complete Selection of MIL-Spec Coax, RF
Connectors and Relays

UG-21BU N Male for RG-213/214.....\$5.00
UG-21D/U N Male for RG-213/214.....\$3.25

N Connectors for 9913/Flexi4XL/9096

UG-21B/9913.....\$6.00 Pins Only.....\$1.50
UG-21D/9913.....\$4.00 Extra Gasket.....75

Amphenol 83-1SP-1050 PL-259.....\$0.90
UG-176/U Reducer RG-59/8X......25 or 5/1.00
UG-175/U Reducer RG-58/58A......25 or 5/1.00
Silver Teflon PL-259/Gold Pin.....
.....\$1.00 or 10/\$9.00

MIL-Spec Coax Available (Teflon, PVC IIA)

New Product: Belden 9913F. 9913 with
High Density PE Foam dielectric, stranded
center cond. and Duobond III Jacket.....
.....80/ft or \$76.00/100ft

Also New: 9092, RG8X with Type II Jacket
Intro Price.....\$23.00/100ft

Call for Specials of the Month

Full Line of Audio Connectors for Icom,
Kenwood, and Yaesu

8 Pin Mike Female.....\$2.50
8 Pin Mike Male Panel.....\$2.50
13 Pin DIN for Kenwood.....\$2.75
8 Pin DIN for Icom.....\$1.00
8 Pin DIN for Kenwood.....\$1.50

Prices Do Not Include Shipping

Orders 800/783-2666
Info 301/840-5477
FAX 301/859-3680

Write in 43 on Reader Service Card.

CASH PAID FOR ICs. Military or commercial integrated circuits, transistors, diodes, any semiconductors. **ELECTRONIC SURPLUS, INC.**, 5363 Broadway, Cleveland, OH 44127. 216-441-8500 or fax 216-441-8503, since 1946. www.electronic-surplus.com

ICs FOR EXPERIMENTERS: Elm offers a variety of ICs for home security, infrared, Control L, as well as basic timing, switch debouncing, etc. Secure purchasing on the web at www.elmelectronics.com

EXPERIMENTER'S PARTS kits, selection of new surplus components. Over 30 different types ranging from resistors to ICs plus! \$10 each plus \$4 shipping. Send check/MO to MCR, 1240 Auburn Rd., Locke, NY 13092. 607-533-3603.


SEE OUR ad on 4-channel 2.4GHz wireless systems in the AdMart section on page 68. Matco, Inc.

MATCO WILL design, engineer, and develop a 2.4GHz wireless 8 channel solution for your remote applications. FCC approved. Matco, Inc., Schaumburg, IL 1-800-719-9605. E-Mail: nsales@matco.com Web site www.matco.com

MICROCONTROLLERS

WANTED: MILITARY capacitors, resistors, transistors, diodes, ICs, semi's, etc. Please fax/E-Mail excess lists & RFQs 818-769-1002 fax 818-769-1084. electmatind@earthlink.net & <http://www.militarycomponents.com>

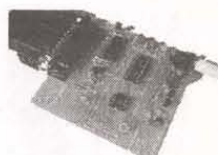ATMEL 89CXXX programmer, IBM parallel port, C++ source code, schematics, \$250 + S/H. E-Mail: cbanni3061@aol.com



PIC MICROCONTROLLER PROGRAMMER KIT. Super value at \$19.95 + \$4.95 shipping. See our web site for the complete range of PICs that can be programmed. Includes PCB, parts and instructions. P16PRO shareware must be downloaded from the web. Amazon Electronics, tel 1-888-549-3749. Lots of other products. www.electronic123.com

DALLAS DS80C320-MCG high-speed microprocessors 45 ICs plus data manual \$150 or best offer. 607-533-3603 NY.

EPROM PROGRAMMING system, with UV eraser, adapters and EPROMs \$100 or best offer. 607-533-3603 NY.

ANTIQUE ELECTRONICS

WESTERN ELECTRIC wanted: 1920s-1960s. Amplifiers, mixers, pre-amps, speakers, tubes, etc. FREE OFFER 1-800-251-5454.

WANTED: FOR historical museum, pre-1980 microcomputers, magazines, and sales literature. Floyd, VA 24091-0341 (540-763-3311/540-382-2935).

WANTED: MILITARY capacitors, resistors, transistors, diodes, ICs, semi's, etc. Please fax/E-Mail excess lists & RFQs 818-769-1002 fax 818-769-1084. electmatind@earthlink.net & <http://www.militarycomponents.com>

WANTED: EIAJ R/R 1/2" color VTR. Excellent operating condition only, please. 415-821-3359, fax 415-821-7500.

AVIATION ELECTRONICS

BUY, SELL, trade, avionics equipment, Collins, King, Sperry: test equipment, IFR, Litton LTN series INUs. 941-625-3222 P, 941-625-0494 F, E-Mail: avionics@afcon.net

WANTED: MILITARY capacitors, resistors, transistors, diodes, ICs, semi's, etc. Please fax/E-Mail excess lists & RFQs 818-769-1002 fax 818-769-1084. electmatind@earthlink.net & <http://www.militarycomponents.com>

PUBLICATIONS

NEW SURVIVAL COMMUNICATIONS BOOK. How to build complete home communications systems. Covers all needs: shortwave radio, amateur radio, citizens band, scanners, federal, weather, alternate news, satellite radio, equipment sources. How to build and use alternate emergency power sources, solar, generators, backup batteries. 200 pages. \$24 Fast delivery Priority Mail, MC or Visa. Call Universal Electronics 1-800-241-8171.



OUT-OF-PRINT TECHNICAL BOOKS. www.johnsontechbooks.com 805-525-8955. sales@johnsontechbooks.com

Turn Your Multimedia PC into a Powerful Real-Time Audio Spectrum Analyzer

Features


- 20 kHz real-time bandwidth
- Fast 32 bit executable
- Dual channel analysis
- High Resolution FFT
- Octave Analysis
- THD, THD+N, SNR measurements
- Signal Generation
- Triggering, Decimation
- Transfer Functions, Coherence
- Time Series, Spectrum Phase, and 3-D Surface plots
- Real-Time Recording and Post-Processing modes

Applications

- Distortion Analysis
- Frequency Response Testing
- Vibration Measurements
- Acoustic Research

System Requirements

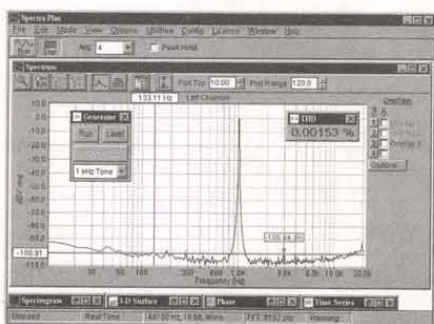- 486 CPU or greater
- 8 MB RAM minimum
- Win. 95, NT, or Win. 3.1 + Win.32s
- Mouse and Math coprocessor
- 16 bit sound card



Priced from \$299

(U.S. sales only - not for export/resale)

DOWNLOAD FREE 30 DAY TRIAL!

www.spectraplus.com

PHS Pioneer Hill Software
24460 Mason Rd.
Poulsbo, WA 98370
a subsidiary of Sound Technology, Inc.

Sales: (360) 697-3472

Fax: (360) 697-7717

e-mail: pioneer@telebyte.com



Spectra Plus
FFT Spectral Analysis System

Celebrating our 17th Year Of Service !!

COLLIMATING LENS

This economical collimating lens assembly consists of a black anodized aluminum barrel that acts as a heat sink, and a glass lens with a focal point of 7.5mm. Designed to fit standard 9mm laser diodes. Simply place diode in the lens assembly, adjust beam to desired focus, then set with adhesive.

STOCK	1-4	10-24	25+
2716	2.99	2.84	2.56
2732	4.49	4.27	3.84
2732A-20	5.49	5.22	4.70
2764-20	5.39	5.12	4.61
2764-25	4.49	4.27	3.84
2764A-20	3.49	3.32	2.99
2764A-25	2.99	2.84	2.56
27C64-15	2.99	2.84	2.56
27256-15	4.79	4.55	4.10
27C256-15	2.99	2.84	2.56
27512-25	3.09	2.94	2.65
27C512-25	2.99	2.84	2.56
27C010-15	2.79	2.65	2.39
27C020-15	3.49	3.32	2.99
27C040-12	5.49	5.22	4.70
27C080-12	10.99	10.44	9.40

DIODE/TRANSISTOR TESTER KIT

This dynamic tester allows checking of transistors & diodes in circuit. Identifies NPN or PNP transistors. Checks all types, small or large power. Identifies anode or cathode of diodes.

STOCK	1-4	10-24	25+
DT100K	24.99	23.74	21.37

ANTI-STATIC FOAM CLEANER

A thick, foaming cleaner for use in static sensitive applications. Safe for plastics and fiberglass. Use on computer cases and all office equipment. Also cleans soft fabrics. 5 oz. aerosol can.

STOCK	1-4	10-24	25+
S81102	1.99	1.89	1.70

EPROMS

STOCK	1-4	10-24	25+
2716	2.99	2.84	2.56
2732	4.49	4.27	3.84
2732A-20	5.49	5.22	4.70
2764-20	5.39	5.12	4.61
2764-25	4.49	4.27	3.84
2764A-20	3.49	3.32	2.99
2764A-25	2.99	2.84	2.56
27C64-15	2.99	2.84	2.56
27256-15	4.79	4.55	4.10
27C256-15	2.99	2.84	2.56
27512-25	3.09	2.94	2.65
27C512-25	2.99	2.84	2.56
27C010-15	2.79	2.65	2.39
27C020-15	3.49	3.32	2.99
27C040-12	5.49	5.22	4.70
27C080-12	10.99	10.44	9.40

Popular I.C.'s

STOCK	1-4	10-24	25+
7400	.39	.37	.33
74LS00	.19	.18	.16
4017	.29	.28	.25
7805T	.33	.31	.28
7812T	.33	.31	.28
LM317T	.49	.47	.42
LM3846N-1	.33	.31	.28
NE555N	.24	.23	.21
LM741N	.24	.23	.21
NE5532N	.55	.52	.47
68HC705CBP	8.99	8.54	7.69
8749	17.99	17.09	15.38
62254LP-10	2.79	2.65	2.39
2816	2.79	2.65	2.39

FM MICROPHONE KIT

Transmit your voice on any FM radio. Range up to 1000'. Case included.

STOCK	1-4	10-24	25+
K30	15.99	15.19	13.67

What Do We Have ?

- I.C.'s
- Oscillators
- Crystals
- Diodes
- Tools
- Laser Diodes
- Vises
- Resistors
- Capacitors
- Connectors
- Trim pots
- Kits
- Vises
- LED's
- Transistors
- And more!

GADGETEER'S GOLDmine

This exciting collection of electronic projects features experiments ranging from magnetic levitation and lasers to high-tech surveillance and digital communications.

• By Gordon McComb

STOCK	1-4	10-24	25+
TB3360	24.99	23.74	21.37

- Order Line — (800) 824-3432 • International — (724) 495-1230 • Fax Orders — (724) 495-7882
- Technical Support — (724) 495-1231 • No Minimum Order — (Orders under \$20 subject to \$5 charge) • UPS 3 day, Blue, Red, & Fed. Ex. Shipping Available (Call for charges) • PA Res. Add 7 % Sales Tax • Open Mon-Fri 9:00 AM - 5:00 PM (EST) • Corporate Accounts / Quantity Discounts Available • We accept M/C, VISA, Discover & American Express with no surcharge • Call For FREE Catalog (\$2.00 Outside U.S.)
- We Carry A Complete Line Of Electronic Components • Email - unielec@aol.com

Visit us on the web 1 www.uniconelectronics.com

FREE SHIPPING!! on pre-paid orders

Unicorn Electronics
1142 State Route 18
Aliquippa, PA 15001

WANTED: MILITARY capacitors, resistors, transistors, diodes, ICs, semi's, etc. Please fax/E-Mail excess lists & RFQs 818-769-1002 fax 818-769-1084. electmatind@earthlink.net & <http://www.militarycomponents.com>


HOW TO LOWER YOUR ELECTRIC BILL and SAVE MONEY. Learn proven methods of electricity reduction. Simply and **inexpensive**. Information \$2 to LWC, Dept. EN, 147 Halsey St., Brooklyn, NY 11216-2103.

ROBOTICS

ROBOT BOOKS.COM visit our web site for reviews of robotics books, plus robot kits, toys, movies, and magazines! www.robotbooks.com

ROBOTS WANTED: Dead or alive, whole or parts. Marvin (Iowa Precision), Gemini, RoPet, Hubot, RB5X, Newton SynPet, ComroTot, ELAMI, ITSABOX, HeathKit (HERO JR, I, 2000, or Arm Trainer), AndroBots (TOPO, BOB, Fred, and Andromed), Rhino, Maxx Steele, Omnibots, etc. Also looking for robot prototypes, options, and literature, will pay cash. Please E-Mail rdoerr@bizserve.com Call 810-777-1313 or write to: Robert Doerr, 26308 Cubberness, St. Clair Shores, MI 48081.

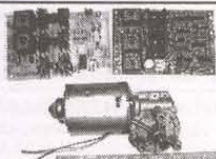
ARobot KIT from Arrick Robotics uses the BASIC Stamp II. Quality metal construction. Easy to assemble and very expandable. \$235. <http://www.robotics.com/robot>



ROBOT GUTS: Motor controls and motors. 35A motor controllers as low as \$35. 12V and 24V models available. Many features. Gearhead motors, manufacturer rated at 4000N (about 900 pound-force) \$10 each. Call 570-735-5053 or E-Mail: carlk3jml@bigfoot.com for shipping. Details: <http://div.elec.tripod.com>

STEPPER DRIVER: Bipolar constant current type, \$80 quantity of one, 3.5 amp 40V, current reduction when idle, step, direction and enable inputs. www.Brewingtons.com


PLANS — KITS — SCHEMATICS

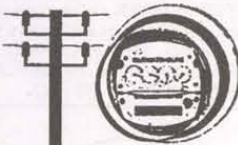

ELECTRIC POWER METER STOPPER MAKES METER RUN SLOWER, STOP, OR EVEN REVERSE! COMPLETE PLANS \$10, PARTS KIT \$20, BOTH \$23! SOLD FOR EDUCATIONAL PURPOSES ONLY. (VISA/MC/AMEX/COD) OPEN 24 HOURS! 352-326-3720 BRINKER ENGINEERING LABS, USA. 614 E. HWY 50 #404, CLERMONT, FL 34711. E-MAIL: brinker@mailcity.com

CONSUMERTRONICS 120+ exciting manuals: Electronics, computers, Internet, phones, energy, radionics, financial (including stocks), crime-fighting, security, survival, phenomena, **SPECIAL PROJECTS.** Catalog \$3. PO Box 23097, Albuquerque, NM 87192. www.tsc-global.com

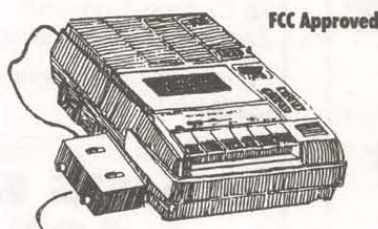TELEPHONE LISTENING DEVICE WITH 12 HR. RECORDER



Record telephone conversations in your office or home. Starts automatically when phone is answered, records both sides of phone conversation. Recorder stops when phone is hung up. \$99.95 + \$7 shipping. For telephone listening device separately \$19.95 + \$2 ship.

For comprehensive 50 page catalog of Micro Video, VHF transmitters, Surveillance, and Counter-surveillance and much more! Send \$3.00

Call 321-725-1000

USI CORP

P.O. Box N2052 Melbourne, FL 32902
COD'S OK

Write in 47 on Reader Service Card.



CIRCUIT BOARDS. Low-cost, precision-made PC boards from your CAD program files (no photoplots required). Single and double-sided with contour routing. Ideal for RF/analog/digital prototypes. Full details at <http://www.pcbmilling.com> E-Mail: feedback@pcbmilling.com FAX: 703-818-0071.

TEST EQUIPMENT kits. If you liked Heathkit, you will love Technology Systems, 4 Prospect Pl., Torrington, CT 06790.

200+ ELECTRONIC PROJECTS. Secure WEB ordering @ www.matcopublishing.com/plans1.htm or send \$1 (refundable) for catalog. MATCO-SA, POB 509, Roseville, MI 48066-0509.

CRYSTAL SETS. Parts, plans, books, kits. Largest source in the world. Catalog \$2. B. TURKE, PO Box 222288, Hollywood, FL 33022.

QUICKBUILD PROTOBOARDS. PIC instrumentation chips, new faster POCKET TESTBENCH (see ad in test equipment section). Oricom Technologies, 303-449-6428. www.sni.net/~oricom

SMART CARD applications CD-ROM \$50. Blank smart cards \$20 or 8/\$100. Tony 419-385-3100.

When Visiting Disney World And Sea World... Come To The World Of Electronic Surplus!

SKYCRAFT

PARTS & SURPLUS, INC.
ORLANDO, FLORIDA



Located At The Intersection Of I-4
And Fairbanks Avenue.

Self-Service Retail Outlet Featuring Commercial
And Government Electronic Surplus Including:

★ WIRE
★ SWITCHES
★ RESISTORS
★ TRANSISTORS
★ TRANSFORMERS
★ TEST EQUIPMENT
★ NI-CAD BATTERIES

★ COAX
★ RELAYS
★ HARDWARE
★ CAPACITORS
★ PANEL METERS
★ CIRCUIT BOARDS
★ INTEGRATED CIRCUITS

★ ★ ★ ★ ★ ★ ★ ★

We Buy Surplus
Electronic Parts —
FAX your list.
www.skycraftsurplus.com

FAX 407/647-4831

PH 407/628-5634

P.O. BOX 536186

ORLANDO, FLA. 32853-6186

HOURS:

Monday - Friday 8:30-6:00
Saturday 8:30-5:00



MANUALS — SCHEMATICS WANTED

MISCELLANEOUS ELECTRONICS FOR SALE

PC CABLES: <http://www.pccables.com> connectors, RS232, IDC, SVHS, ribbon cable, DB9, DB15, loopback, null modem, jumpers, SCSI, screws, rails. Secure online catalog, ordering, browsing. 954-418-0817.

PRIMECELL

IF YOU NEED NEW BATTERIES FOR YOUR ELECTRONIC EQUIPMENT
DON'T PITCH EM! - SEND THEM FOR REBUILDING! - SAVE \$ \$

CUNARD ASSOC. INC., 9343 US RT 220, Bedford, PA 15522

- WE INSTALL NEW NI-CAD OR NI-MH BATTERIES INTO YOUR ORIGINAL CASE.
- WE IMPROVE CAPACITY TO BETTER THAN ORIGINAL.
- WE FIX WHAT CAN'T BE FOUND. (OR AFFORDED)
- WE PROVIDE QUICK SERVICE. / EXTENDED LIFE FOR OLDER EQUIPMENT
- WE OFFER FREE QUOTES. / FREE RETURN IF QUOTE IS REFUSED.
- WE PROPERLY DISPOSE OF YOUR OLD CELLS BY RECYCLING.
- WE GIVE YOU A 12 MONTH WARRANTY.
- WE WILL BE HERE WHEN YOU NEED US / EST. 1986
- WE SAVE YOU \$\$\$ MONEY \$\$\$ \$ \$ \$



• NO JOB IS TOO LARGE OR TOO SMALL VOLUME DISCOUNTS AVAILABLE

GENERAL ELECTRIC	UNIDEN	RADIO SHACK
19A704850P (1200mAh) \$ 34.95	APX650 1050 \$ 29.95	HTX Packs \$ 29.95
19A704860P (1800mAh) \$ 39.95	1000 1010 1070 \$ 34.95	New 8.4V pack & chgr
PL19D429763 (777) G1/3 \$ 37.95	1100 1200 Series \$ 36.95	1500mAh nimh \$ 34.95
19A705293P 344A4506P \$ 34.95	BP205 650mAh \$ 19.95	
	BP205 1500mAh \$ 24.95	KENWOOD
	SC150 1500mAh \$ 22.95	PB2 / KNB3 \$ 29.95
MAXON SA-1155 1160 \$ 39.95		PB21/21H \$ 14.95
TAD 1450 1510 1520 \$ 21.95		PB25/H26 \$ 24.95
	ICOM	
MOTOROLA	BP2 / BP3 / BP22 \$ 18.95	CORDLESS DRILLS
P200 HT600 MT1000	BP5 / BP23 / 24 \$ 24.95	Any brand 7.2V \$ 18.95
NTN 4585 4824 5414 \$ 37.95	BP7 / CM7 / BP8 \$ 32.95	Any brand 9.6V \$ 29.95
NTN 5447 5521 5545 \$ 37.95	BP180 / CM79 \$ 34.95	Any brand 12.0V \$ 32.95
NLN 5860 NTN 4327 \$ 39.95		Any brand 14.4V \$ 37.95
	YAESU	Any Brand 18.0V \$ 45.95
	FNB 3 4 12 14 16 \$ 32.95	
MIDLAND	FNB19 21 26 27 38 \$ 32.95	COMPUTER PACKS
70-B10 B16 B19 B21 \$ 39.95	FNB10 1117 25 35 \$ 23.95	Send battery for quote.
B25 B26 B32 B36 B60 \$ 39.95		

FOR INFORMATION ABOUT YOUR REQUIREMENTS CONTACT US:
PHONE OR FAX : (814) 623-7000 E-MAIL TO: PRIMECELL@AOL.COM
SEND YOUR PACKS FOR FREE QUOTATION VIA UPS, RPS OR US MAIL
VISIT OUR WEB SITE <http://members.aol.com/primecell/primecell.htm>

BATTERY REBUILD SERVICE

MANY OTHERS AVAILABLE - WRITE OR CALL

FREE CATALOG

ADD \$ 4.50 SHIPPING & HANDLING PER ORDER




Write in 48 on Reader Service Card.

JUMP START YOUR USB DESIGNS

Take the pain out of designing for USB. Jan Axelsson's **USB Complete** has the answers to your questions:

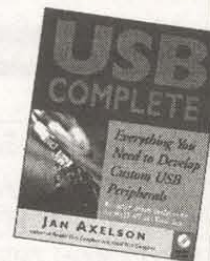- ✓ Can my project use a USB interface?
- ✓ Which peripheral controller chip should my design use?
- ✓ How do I access USB peripherals from Visual Basic applications?
- ✓ What embedded code does my peripheral need in order to communicate with PCs?
- ✓ Can my design use bus power or will it need its own supply?
- ✓ And much more!



USB Complete:
Everything You Need to Develop Custom USB Peripherals
by Jan Axelsson

"I tell all my students that they really need this book in their library." Paul Berg, Instructor, Annabooks USB Developers Workshop

Free! USB firmware, application code, & links to developer tools and info at

www.lvr.com

\$49.95. 496 pages
Includes CD-ROM

ISBN 0-9650819-3-1
Published by Lakeview Research

Available at bookstores everywhere

'SX-1SD' Debugger+Programmer


Qualified by and inhouse tool for
Scenix Semiconductor

- In-system debugger for SX18/20/28/48/52
- Built in programmer
- Full speed emulation
- Real-time in-system code execution and breakpoint
- Frequency synthesizer from 25khz to 75mhz / 120mhz*
- External oscillator support to 90 mhz / 100mhz*
- Source level debugging for SASM, SXC and more
- Selectable internal frequencies
- External break and clock inputs
- Conditional animation break and Software animation trace
- IDE runs under Win 95/98/2000/NT4 via parallel port
- Comes with SASM Assembler, SXDEMO board, SX28AC device and 18-pin, 28-pin SDIP headers


Now
supporting the
100 mhz SX

From
\$295*

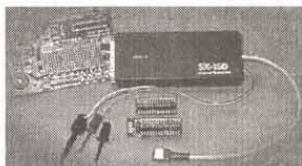- * SX-1SD \$295 (synthesize to 75mhz, external OSC support to 90-95mhz)
* SX-1SD100 ... \$350 (synthesize to 120mhz, external OSC support to above 100mhz)



Also Available...

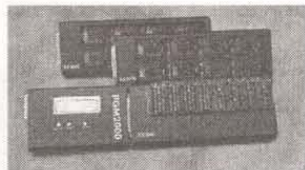

- PGM2000 Gang Programmer**
- Stand alone 8 gang programmer
 - Parallel Port Interface for on-line operation
 - Different 8-socket DIP, SOIC, SSOP, TQFP, PQFP adapters for all SX18/20/28/48/52
 - Adjustable programming voltages in 0.1V
 - Codes and fuse reside securely in EEPROM of Master Control Unit
 - Comes with Win 95/98/2000/NT4 software
 - Also supports other processors via different 8-socket adapter modules
 - Starts at \$900 with one 8-up DIP adapter



- PGM-SX Programmer**
- Parallel Port Interface
 - 40-pin ZIF socket to carry device to be programmed or program in-circuit
 - Win 95/98/2000/NT4 software
 - Comes with SASM assembler
 - Optional SOIC, SSOP, TQFP and PQFP programming sockets
 - PGM-SX \$149, SMT adapters \$120

Advanced Transdata
14330 Midway, #128, Dallas, Texas
Tel 972.980.2667 Fax 972.980.2937
Email: atc1@ix.netcom.com

www.adv-transdata.com

Write in 49 on Reader Service Card.

ABC ELECTRONICS 315 7TH AVE N. MPLS. MN. 55401
(612)332-2378 FAX (612)332-8481 E-MAILSURP1@VISI.COM
WE BUY TEST EQUIPMENT AND COMPONENTS.
VISIT US ON THE WEB AT WWW.ABCTEST.COM

HP 54501A 100MHZ DIGITIZING SCOPE	\$1300.00	HP 4935A TRANS IMPAIRMENT TEST SET	\$900.00
HP 54201D 300MHZ DIGITIZING SCOPE	\$1000.00	HP 5006A SIGNATURE ANALYZER	\$150.00
HP 54201A 300MHZ DIGITIZING SCOPE	\$1000.00	HP 8660C 1MHZ-1300MHZ RF PLUG	\$400.00
HP 54200A 500MHZ SCOPE/WAVEFORM ANALYZER	\$700.00	EIP 575 MICROWAVE COUNTER	\$1500.00
HP 3312A 13MHZ FUNCTION GENERATOR	\$250.00	FLUKE 95 50MHZ SCOPERMETER	\$550.00
HP 5370A 100MHZ U.T.I. COUNTER	\$400.00	LECROY 7200 400MHZ O-SCOPE	\$1000.00
HP 3386C LEVEL METER	\$750.00	TEK 475 200MHZ O-SCOPE	\$500.00
HP 436A POWER METER W/O SENSOR&CABLE	\$500.00	TEK 465 100MHZ O-SCOPE	\$400.00
HP 8350B SWEEP OSCILLATOR MAINFRAME	\$2000.00	TEK 496P 1KHZ-1.8GHZ SPEC ANALYZER	\$3500.00
HP 3437A 3.5DIGIT SYSTEM VOLT METER	\$250.00	TEK 1240 LOGIC ANALYZER	\$750.00
HP 3455A DIGITAL MULTIMETER	\$250.00	TEK TDS320 100MHZ DIGITAL O-SCOPE	\$1400.00
HP 3456A DIGITAL MULTIMETER	\$400.00	TEK 11401A 500MHZ SCOPE FRAME	\$750.00
HP 3336C SYNTHESIZER/LEVEL GENERATOR	\$800.00	TEK 7854 400MHZ OSCILLOSCOPE FRAME	\$500.00
HP 3325A SYNTHESIZER/FUNCTION GENERATOR	\$1000.00	TEK 7904 400MHZ OSCILLOSCOPE FRAME	\$250.00
HP 5335A 200MHZ COUNTER	\$600.00	TEK 7A26 200MHZ VERTICAL PLUG	\$75.00
HP 8165A PROGRAMMABLE SIGNAL SOURCE	\$1100.00	TEK 7A24 400MHZ VERTICAL PLUG	\$150.00
HP 8588B/181 100K-1.500MHZ SPECTRUM ANALYZER	\$1000.00	TEK 7880 400MHZ TIME BASE	\$75.00
HP 8559B/183 10MHZ-21GHZ SPECTRUM ANALYZER	\$3000.00	TEK 7892A 500MHZ DUAL TIME BASE	\$125.00
HP 1740A 100MHZ OSCILLOSCOPE	\$250.00	TEK 7812 SAMPLING PLUG	\$250.00
HP 6034A 60VDC-10A POWER SUPPLY	\$750.00	TEK 7L14 10KHZ-1.8GHZ SPEC. ANALYZER	\$1000.00
HP 6269B 40VDC-50A POWER SUPPLY	\$800.00	TEK AM503 CURRENT PROBE AMPLIFIER	\$250.00
HP 6553A 40VDC-17.5A POWER SUPPLY OPT.J01	\$1200.00	WAVETEK 145 20MHZ PULSE/FUNCTION GEN.	\$400.00
HP 6632A 20VDC-3A POWER SUPPLY	\$500.00	WAVETEK 182A 4MHZ FUNCTION GEN.	\$150.00
HP 6643A 45VDC-4.3A POWER SUPPLY OPT.J03	\$750.00	WAVETEK 955 7.5-12.4GHZ MICROSOURCE	\$1100.00

Lowest Dealer Price Available

	5+	10+	20+
Refurb. Panasonic 145	\$45	\$40	\$35
Regal w/Remote	\$38	\$35	\$30
BC4535 86 Channel	\$30	\$28	\$25
Oak Sigma 99 Channel	\$45	\$40	\$35
75 Channel Converter	\$18	\$18	\$18
Zenith ST1600 w/Remote	\$75	\$70	\$65

Panasonic Converters Model-175 \$65 \$55 \$45
(550MHz) Six month's warranty on this model only

Call us today to satisfy all your cable equipment needs!

SAM'S ELECTRONICS
1-405-631-1856

All Cable Equipment is unmodified.



SOLAR-POWERED FAN HAT.
Baseball type hat with solar powered fan. Great for sports fans, golfers, etc. Available in red or blue. \$19 plus \$2.00 shipping. CA residents add 7.75% sales tax. Visa/MC/Disc/Amex OK. H.T. Orr Computer Supplies, 249 Juanita Way, Placentia, CA 92670. 714-528-9822, 1-800-377-2023, FAX 714-993-6216.

HIGH QUALITY TOOLS AND STAINLESS STEEL HARDWARE.
European and American screwdrivers, nutdrivers, pliers, hex-keys, balldrivers, and more! Wiha, Bondhus, and Knipex. Stainless cap screws, machine screws, nuts, washers, U-bolts, and eyes. Free catalog. Robert Mink Import-Export, Box 6437V, Fair Haven, NJ 07704. Telephone or fax 732-758-8388. E-Mail: w2tv@compuserve.com



ANAHEIM WIRE PRODUCTS. DISTRIBUTOR OF ELECTRICAL WIRE AND CABLE since 1973. Items available from our stock: Hook up wire, Automotive primary wire, GXL, SXL, Plenum cable, Teflon wire, Multi-conductor cable, Irradiated PVC, SO-CORD, Mil-Spec wire, Building wire, Welding cable, Battery cable, Telephone wire, Shrink tubing, Cable ties, Connectors. Wire cut & strip to specs. If interested, please call **1-800-626-7540**, FAX: 714-563-8309. Visa/MC/Amex. SEE US ON THE INTERNET: <http://www.anaheimwire.com> OR E-Mail: info@anaheimwire.com

NUCLEAR ELECTRONICS (NIM, CAMAC), PMTs, optics, high vacuum, and high voltage components and equipment. Guaranteed quality at reasonable cost. OE Technologies, Box 703, La Madera, NM 87539. Ph: 505-583-2482, Fax: 505-583-9190. E-Mail: oetech@newmexico.com <http://www.oetech.com>

HARD-TO-find parts: for big screens and all TVs. TV, VCR, microwave diagrams and manuals. Phonograph needles. VCR RFs \$5. 912-272-6561. Scarborough, VT, 1422 Old River Road, East Dublin, GA 31027.

FREE FLYER on DBS, cable TV, phones, credit cards, schematics, health items. Bill 1-800-879-9657.

MISCELLANEOUS ELECTRONICS WANTED

HIGHEST PRICES PAID: I will pay the following prices for Western Electric tubes: 211A/D/E new \$300, used \$175; 212A/D/E new \$750, used \$275; 274A/B (engraved base) new \$250, used \$200; 300B (engraved base) used \$550; 422A new \$50, used \$25; 437A new \$50, used \$25; and many more. Also buying Western Electric, and other audio tube and equipment literature. Call or send us your list. Toll free tel/fax: 1-888-715-8823. Don Singerhouse/Singerhouse Sound, LLC, PO Box 321, New Richmond, WI 54017. E-Mail: singtube@frontiernet.net

ATTENTION: SINGERHOUSE Sound will be buying Western Electric, and many other audio tubes at Dayton Hamvention this year. We will be located in the outdoor flea market, space #3668. If you would like a complete want list, or have any questions, please call Don Singerhouse, toll free tel/fax: 1-888-715-8823 or E-Mail: singtube@frontiernet.net Singerhouse Sound, PO Box 321, New Richmond, WI 54017. See you there!

WESTERN ELECTRIC wanted: 1920s-1960s. Amplifiers, mixers, pre-amps, speakers, tubes, etc. FREE OFFER 1-800-251-5454.

DEC EQUIPMENT WANTED!!! We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), DSD, Datability, Dialog, other DEC compatibles, and Computer Output Microfilm (COM) units. Please call for a quote or fax us your equipment list. We buy, sell, and trade. **KEYWAYS, INC.**, 937-847-2300 OR fax 937-847-2350.

WANTED: TUBES, radios, transmitters, receivers, gyros, bearings, connectors, relays, lamps, synchros. Hyness Company, 709B Delair Road, Monroe Twp., NJ 08831. Phone: 609-395-1116, FAX 609-395-1117.



WANTED: EXCESS ELECTRONIC COMPONENTS, BOARD-LEVEL COMPONENTS; MILITARY COMPONENTS; ICs, MEMORY, TRANSISTORS, DIODES, CAPS, RELAYS, ETC. CALL LPS 562-439-2453 FAX 562-439-0453.

CASH PAID FOR ICs. Military or commercial integrated circuits, transistors, diodes, any semiconductors. **ELECTRONIC SURPLUS, INC.**, 5363 Broadway, Cleveland, OH 44127. 216-441-8500 or fax 216-441-8503, since 1946. www.electronic-surplus.com

WANTED: AVIONICS test equipment, IFR, 600A, 401L, others, Collins, King, Sperry, North Atlantic, Litton INUs LTN series, rate and tilt tables, air data test sets, 941-625-3222 P, 941-625-0494 F, E-Mail: avionics@afcon.net

WANTED: MILITARY capacitors, resistors, transistors, diodes, ICs, semi's, etc. Please fax/E-Mail excess lists & RFQs 818-769-1002 fax 818-769-1084. electmatind@earthlink.net & http://www.militarycomponents.com

WANTED: UNITEK WELDING EQUIPMENT. Buying power supplies, welding heads, etc. Call 608-831-3443.

WANTED: BALANCING machines & vibration analyzing equipment manufactured by the following: Spectral Dynamics, Hofmann, Bentley Nevada, Schenck, IRD Mechanalysis, Gishott. Contact Mike Park at E.T. Balancing, 12823 Athens Way, Los Angeles, CA 90061. 310-538-9738, FAX: 310-538-8273.

WANTED: 15,000+ 6-12 VDC dual shaft motors. 1280-2880 RPM. 1/8" dia. shafts. Size 1-3/8" dia. x 4-1/8" overall length or comparable motors. The Flashing Duck, c/o CH Sullivan III, PO Box 395, Covington, TN 38019. 901-476-2822.

OLD POCKET CALCULATORS WANTED: 1970s, LED, all makes, models. Cash paid! Erik 914-738-9422 or floete@aol.com

BBS & ONLINE SERVICES

WANTED: MILITARY capacitors, resistors, transistors, diodes, ICs, semi's, etc. Please fax/E-Mail excess lists & RFQs 818-769-1002 fax 818-769-1084. electmatind@earthlink.net & http://www.militarycomponents.com

BUSINESS OPPORTUNITIES

WANTED: MILITARY capacitors, resistors, transistors, diodes, ICs, semi's, etc. Please fax/E-Mail excess lists & RFQs 818-769-1002 fax 818-769-1084. electmatind@earthlink.net & http://www.militarycomponents.com



COUNTER-SURVEILLANCE=\$250 HR! Electronic eavesdropping is unbelievably widespread! Are you sure you're safe? Learn how others (without prior experience) earn \$250 HR in the fascinating field of COUNTER-SURVEILLANCE! For FREE catalog call: 1-800-732-5000.

REPAIRS — SERVICES

PC BOARD ASSEMBLY. Thru hole only. Small or large quantities OK. Call Network Sales. 616-683-0500.

PRINTED CIRCUIT design by professional with 30+ years: conventional, multilayer, downhole, fine line. Prototype and production fabrication. Reverse engineer existing 2-layer board. Toll free 877-236-3223. www.circuit-applied-tech.com

WE REPAIR and refurbish CBTV converters, all models, reasonable, 6-month warranty. Also sale converter parts and remote. 405-692-4982.

(E)EPROM PROGRAMMING done quickly and economically. One day turn around typical. Simple copy \$3 per device. Also prototyping, design, and consulting services available. Call or send SASE to: **Luzer Electronics, 4023 North Bayberry, Wichita, KS 67226. 316-687-2127, FAX 316-687-3103.**

WELD ALUMINUM WITH PROPANE! EZ, INEXPENSIVE, STRONG. DETAILS: WEEKS, 36 CAROLINA ST., TAYLORS, SC 29687. 1-800-547-WELD(9353) FAX 864-244-6349. http://www.durafix.com

CIRCUIT BOARDS for projects, prototypes, short runs. From your artwork. Low rates. Atlas Circuits 704-735-3943. www.pcbatlas.com

CABLE PARTS, COMPUTER CONNECTORS, CALL FOR LOW PRICES. WE NOW ACCEPT CONVERTER REPAIRS FROM ZENITH TO CFT. 1 FULL YEAR WARRANTY. 405-631-5153.

WANTED: MILITARY capacitors, resistors, transistors, diodes, ICs, semi's, etc. Please fax/E-Mail excess lists & RFQs 818-769-1002 fax 818-769-1084. electmatind@earthlink.net & http://www.militarycomponents.com

MAGICIAN IS available to solve your RF problem. Invest in your RF future, learn the practical side of RF circuit design in my laboratory. I will teach you how-to-do it with up-to-date components. Minaret Radio, John Horvath ph: 909-943-3676.

CABLE CONVERTER REPAIR: Quality repair service for all name brands. If you're tired of the runaround you're getting from the company you purchased it from, or they're out of business. Give us a call for fast and courteous service. Have model and problem ready. Sorry no box, chip, or IL repairs. **Highview Engineering 815-245-3735** or E-Mail: HIGHENG1@AOL.COM ask for George.

WE REPAIR AND REFURBISH ALL MAKES AND MODELS OF CONVERTER BOXES. CALL OUR OFFICE STAFF FOR DETAILED INFORMATION FOR SERVICES AND FOR "RAW" CONVERTERS, REMOTE HAND UNITS. CALL 405-634-1535.

ALL ELECTRONICS

C O R P O R A T I O N

QUALITY Parts
FAST Shipping
DISCOUNT Pricing

CALL, WRITE, FAX
or E-MAIL For A
Free 96 Page
CATALOG.
Outside the U.S.A.
send \$3.00 postage.

Tiny Vibrating Motor

Low voltage, low current miniature vibrating motor. Operates on 1.5 Vdc @ 62 mA. Tiny motor with offset weighted shaft is used in cell phones and pagers for vibrating alert signal. Remove the weight and they're great for many model and robotics applications. A removable black rubber boot surrounds the motor and provides a flat mounting surface. Without the rubber boot they are 0.24" dia. x 0.6" long. Shaft adds extra 0.21" to the overall length. 1.5" leads with miniature 2 pin connector.

CAT # DCM-154
\$2.00 each
10 for \$17.50
100 for \$125.00

Multi-Media Rack

Desktop flip rack keeps all of your important media in one place. CD's 3.5" floppies and ZIP discs all can be stored in the same rack. Outer rails hold 16 CD/CD ROMs. Inner rails hold 20 3.5" floppy discs, or 3 ZIP discs and two M.O. discs. Individually boxed.

CAT# CDB-18M
\$3.50 each
10 for \$30.00

Digital On-Timer

Digital timer from Mr. Coffee™ Small modular design, no brand name or logo. Ideal for use in any product that needs to be turned on automatically at a specific time. Operates on 120 Vac. Switch loads up to 10 amps. Can be switched manually. White plastic face. 2.48" X 1.77", with four digit LED clock. Overall size: 2.48" X 2.17" X 1.88" deep behind face. 0.25" qc terminals. Easy to connect and operate. Includes instruction sheet.

CAT# MCT-3
\$5.00 each

"Ear Bud" Stereo Earphones

Miniature "in-ear" earphones for use with most portable CD, radio and tape players. 3.5 mm stereo phone plug. 32 ohm impedance. Large Quantity Available

CAT # HP-6
85¢ each
10 for \$7.50
100 for \$50.00

Laser Level

Accurate and easy to use for short and long distance leveling. Center the bubble, and anything that intersects the beam is at exactly the same height. Use it to match heights in large rooms or across buildings. Set and align electrical and plumbing fixtures, cabinets and shelves. Rugged, black anodized aluminum housing with pocket clip. Looking push button switch to prevent unintended activation. Includes two AAA batteries.

CAT # LL-1
\$16.95 each

22 UF 450 Vdc

0.63" diameter X 1.6" long axial electrolytic capacitor.

CAT# 22/450VA
\$1.25 each
10 for \$10.00
100 for \$80.00

16 Character X 2 Line LCD with Backlight

Daewoo # 16216L-5-VSO 5 x 7 dot format. 2.56" x 0.54" viewing area. 3.15" x 1.41" module size. LED backlight. Includes hook-up/spec sheet.

CAT# LCD-53
\$7.50 each

Heatsink

4.53" X 2.3" X 1.44". High-capacity black anodized aluminum heatsink. 4.2" x 2" mounting centers. Weight: 0.54 lbs.

CAT # HS-65
\$3.75 each

Ionizer

Seawise Industrial Ltd. Model # SW750 Input: 120 Vac Output: 7.5 KV 60 Hz. The main component in a household ionization unit. 2.2" x 1" x 0.86" thick with a mounting tab that extends 0.75" from the unit. UL recognized.

CAT # SW-750
\$4.50 each

Blue & White Ultrabrights

BLUE / water clear 1200 mcd 45 degree viewing angle.

\$3.75 each
CAT # LED-58
10 for \$30.00

WHITE / water clear 1100 mcd

\$4.00 each
CAT # LED-48
10 for \$35.00

Motorized Potentiometer Dual 10K Linear Taper

Alps Electric # 726T-10KBX2 Dual 10K linear pot powered by a small reversible 6 Vdc gearhead motor. Pot and motor assembly are 1" square x 1.7" long excluding shaft and bushing. 6 mm flatted shaft is 0.5" long. 9mm threaded bushing. PC pins and mounting tabs for pc board mounting.

CAT # MPOT-10K
\$4.00 each
10 for \$35.00

ORDER TOLL FREE 1-800-826-5432
Shop ON-LINE www.allelectronics.com

MAIL ORDERS TO:
ALL ELECTRONICS CORP.
P.O. BOX 567 • VAN NUYS, CA 91408-0567

FAX (818) 781-2653 • INFO (818) 904-0524
E-MAIL allcorp@allcorp.com

NO MINIMUM ORDER • All Orders Can Be Charged to Visa, Mastercard, American Express or Discover • Checks and Money Orders Accepted by Mail • Orders Delivered in the State of California must include California State Sales Tax • NO C.O.D. • Shipping and Handling \$5.00 for the 48 Continental United States • ALL OTHERS including Alaska, Hawaii, P.R. and Canada Must Pay Full Shipping • Quantities Limited • Prices Subject to change without notice.

MANUFACTURERS - We Purchase EXCESS INVENTORIES... Call, Write, E-MAIL or Fax YOUR LIST.

CALL TOLL FREE

(800) 292-7711

Orders Only

Se Habla Español

C&S SALES

Secure On-line Ordering @ cs-sales.com

CALL OR WRITE

FOR OUR

FREE

64 PAGE CATALOG!

(800) 445-3201

Digital Multimeters

Elenco Model M-1740



\$39.95

- 11 Functions:**
- Freq. to 20MHz
 - Cap. to 20µF
 - AC/DC Voltage
 - AC/DC Current
 - Beeper
 - Diode Test
 - Transistor Test
 - Meets UL-1244 safety specs.
- Model M-2780 - \$24.95**
(9 functions)

Elenco Model LCR-1810



\$99.95

- Capacitance 1pF to 20µF
- Inductance 1µH to 20H
- Resistance 0.1Ω to 2000MΩ
- Temperature -20°C to 750°C
- DC Volts 0 - 20V
- Frequency up to 15MHz
- Diode/Audible Continuity Test
- Signal Output Function
- 3 1/2 Digit Display

Fluke 87III



\$319

Features high performance AC/DC voltage and current measurement, frequency, duty cycle, resistance, conductance, and capacitance measurement.

CCTV Cameras

Cameras have 420 lines (380 color) of resolution, 0.08 Lux, 3.6mm/F2 90° field of view. Power requirement is 12VDC @ 100mA (order SC-1).

MONOCHROME CAMERAS

COLOR CAMERAS



SC-12 - 35mm Lens (1.25"x1.25") \$69
SC-15 - Pin Lens (1.25"x1.25") \$69
Add \$10 for lens • Add \$10 for audio



SC-20 Pin Lens \$109
SC-21 3.6mm Lens \$109
360 Lines 1.25" x 1.25" Infrared Sensitive, Audio Included
Add \$10 for case
Call for complete catalog.

Accessories:
SC-1 - 12V 100mA adapter \$19.95
SC-2 - 50' cable with connectors \$19.95

Test Equipment

Elenco Sweep Function Generator with built-in frequency counter Model GF-8036

\$229.95



This sweep function generator with counter is an instrument capable of generating square, triangle, and sine waveforms, and TTL, CMOS pulse over a frequency range from 0.2Hz to 2MHz.

10 Function 1.3GHz Universal Counter Elenco Model F-1300

\$229.95

- Frequency .05Hz - 1.3GHz 3 Ranges
- Period - Can read 60Hz to 60,000,000 F=1/T
- Totalize - Counts to 999,999,999
- RPM - 3 to 2099994 RPM
- Duty Cycle
- Max/Min/AVG with Time
- Stop-watch set .2 sec. to 100 hrs.
- Math Functions
- Timer - 2 sec. to 99 days
- Pulse Width - 0.1ms to 66666.6ms



20MHz Sweep / Function Generator with Frequency Counter Model 4040

- 0.2Hz to 20MHz
- AM & FM modulation
- Burst Operation
- External Frequency counter to 30MHz
- Linear and Log sweep



21.5MHz Model 4070 \$1295
10MHz Model 4017 \$325
5MHz Model 4011 \$255

\$445

BK PRECISION

Elenco Handheld Universal Counter 1MHz - 2.8GHz Model F-2800

\$99



Sensitivity:
• <1.8mV @ 100MHz
• <6mV @ 250MHz
• <6mV @ 1GHz
• <10mV @ 2.4GHz

Features 10 digit display, 16 segment and RF signal strength bargraph. Includes antenna, NiCad battery, and AC adapter.

Elenco Quad Power Supply Model XP-581



4 Fully Regulated DC Power Supplies in One Unit

\$85

4 DC voltages:
3 fixed: +5V @ 3A
+12V @ 1A
-12V @ 1A
1 Variable: 2.5 - 20V @ 2A

B&K Frequency Counter Model BK-1875

50Hz - 2.8GHz 3 Channels



\$189

Sensitivity:
• <0.8mV @ 100MHz
• <6mV @ 300MHz
• <7mV @ 1GHz
• <100mV @ 3GHz

Ultra sensitive synchronous detector bargraph and RF strength.

B&K Video Monitor Tester Model 1275



\$169

Great handheld unit to test PC and Mac monitors. The model 1275 is ideal for the field or the service bench. Small, portable and very effective, the 1275 generates crosshatch, dots, color bars and raster patterns in green, blue, red, black and white.

Soldering Station

Weller Low Cost Soldering Iron Model WLC-100



- Variable power control produces 5-40 watts.
- Ideal for hobbyists, DIYers and students.
- Complete with 40W iron.

\$34.95

Elenco Oscilloscopes

Free Dust Cover and 2 Probes



S-1325	25MHz	Dual Trace	\$325
S-1330	25MHz	Delayed Sweep	\$439
S-1340	40MHz	Dual Trace	\$475
S-1345	40MHz	Delayed Sweep	\$569
S-1360	60MHz	Delayed Sweep	\$749
S-1390	100MHz	Delayed Sweep	\$995

DIGITAL SCOPE SUPER SPECIALS

DS-203	20MHz/10Ms/s Analog/Digital	\$695
DS-303	40MHz/20Ms/s Analog/Digital	\$995
DS-603	60MHz/20Ms/s Analog/Digital	\$1295

Tekk Radios

Pro-Sport FRS Two-Way Radio Model PRO-SPORT+

Talk up to 2 miles!

Available in Yellow, Blue & Black

No License Required

- 1/2 Watt Output, 14 Channels.
- TX & RX LED/LCD Indicators.
- Large LCD Display.
- 38 Privacy (CTCSS) Tones.
- Removeable Antenna.
- Water Resistant.
- 500mW Output.
- Palm Sized.



PRO SPORT Model \$109.95 set of 2
\$69 each or \$125 Set of 2

PC Repair

A+ Certification Self-Study Course™ Model XK-305

\$379

DOS/WIN Exam
DOS 6.2
Windows 3.1 Installation and Configuration
Windows 3.1 Application Support
Windows 3.1 Devices and Drivers
Windows 3.1 Networking and Troubleshooting
Windows 95 Installation and Deployment
Windows 95 Basic Configuration
Windows 95 Troubleshooting and Optimization
Includes all the technical material, knowledge and interactive exercises needed to pass the A+ exams and excel in the competitive PC repair marketplace.

Elenco Technician Tool Kit Model TK-1500

\$179

Introduction to PC Repair Self-Study Course™ Model XK-301
COURSE CONTENTS
Introduction to Computers
IBM PC's and Clones
PC Assembly/Disassembly
Introduction to MS-DOS
Introduction to Windows 3.1
Introduction to Windows 95
Introduction to Networks
Introduction to the Internet
Provides you with the easiest and most effective way to learn the fundamentals necessary for a profitable and successful career as a PC Repair Technician. Ideal for individuals new to the IT profession and as instruction prior to studying for A+ certification.

28 tools plus a DMM contained in a large flexible tool case with a handle ideal for everyone on the go.



Elenco Educational Kits

Model AR-2N6K



2 Meter / 6 Meter Amateur Radio Kit

\$34.95

Model AM-780K



Two IC Radio Kit

\$11.95



Model AK-700 Pulse/Tone Telephone Kit

\$15.95


Model AK-870 Radio Control Car Kit

\$24.95



Model M-1005K Digital Multimeter Kit

\$19.95

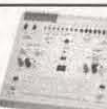

Model XK-150 Digital / Analog Trainer

\$89.95

Guaranteed Lowest Prices

UPS SHIPPING: 48 STATES 5%
OTHERS CALL FOR DETAILS
IL Residents add 8.25% Sales Tax

SEE US ON THE WEB

C&S SALES, INC.

150 W. CARPENTER AVENUE
WHEELING, IL 60090

FAX: (847) 541-9904 (847) 541-0710

<http://www.cs-sales.com>

15 DAY MONEY BACK GUARANTEE

2 YEAR FACTORY WARRANTY

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

AMATEUR ROBOTICS

by Robert Nansel

NOTEBOOK

I can't believe it's spring already and I still don't have my robotics shop unpacked here at the new Robot Ranch. I mean, good grief, man, there's robots to be built, transistors to be fried, and neighbors to be mystified.

I do have my tool boxes and office stuff unpacked (that you are reading this column is witness to that), but all my test gear and development tools — oscilloscope, signal generator, breadboards, power supplies, device programmers, I2C monitor — are still in boxes. These boxes are underneath other boxes which, in turn, can't be unpacked until we get shelves up, but the shelves can't be put up because the power tools are also still packed, and, guess what, there's no room to unpack those tools without swimming in packing peanuts.

Gradually, Shoshana and I are finding space to put the domestic necessities and, as we do, the boxes on top of boxes slowly disappear. It's remarkably like an archeological dig, except the artifacts get higher tech the lower we excavate, and we do have an inventory of what's in the lower layers — we just can't get to them, yet.

Then, too, there are mysteries we haven't solved yet, such as where the heck my stapler is and exactly where Igor (my 386 PC) has got to. The stapler I can live without for a while longer, but Igor has me worried. Maybe Igor accidentally got sold at our moving sale, or maybe he's stuck in a lower layer in an un-inventoried box ... I just don't know. The romantic in me fancies that maybe Igor just slipped away in the night once I undid his chains. Whatever has become of him, it just won't be the same using Shoshana's laptop to perform his duties.

As if to counterbalance the disappearance of Igor and my stapler, I can't seem to turn around without tripping over some component or another of Spanky, my Linux system. Spanky (the name comes from the way I refer to working with Linux: Spanking the Penguin) is the main exception to the high-

tech-on-the-bottom rule around here, though it does me no good because there's no room to set up another computer, not one with a 19-inch monitor. In fact, Spanky is actively impeding the unpacking process; the monitor is big enough, but the box it comes in is monstrous. Makes me entertain thoughts of selling all my worldly possessions and finding out if it really is possible to sail to Fiji and make everything you need with nothing but a Leatherman tool and the right attitude.

Left to My Own Devices

Shoshana brings me sharply back to reality, though, when she points out that we still need a few more years worth of Huggies diapers (try whittling some of those from a coconut husk some time).

I may still buy the Leatherman tool; I've been hoping for years to receive one as a Hannukah present, but for some reason all I ever get are things like socks and ties. The idea of a tool that can do practical-

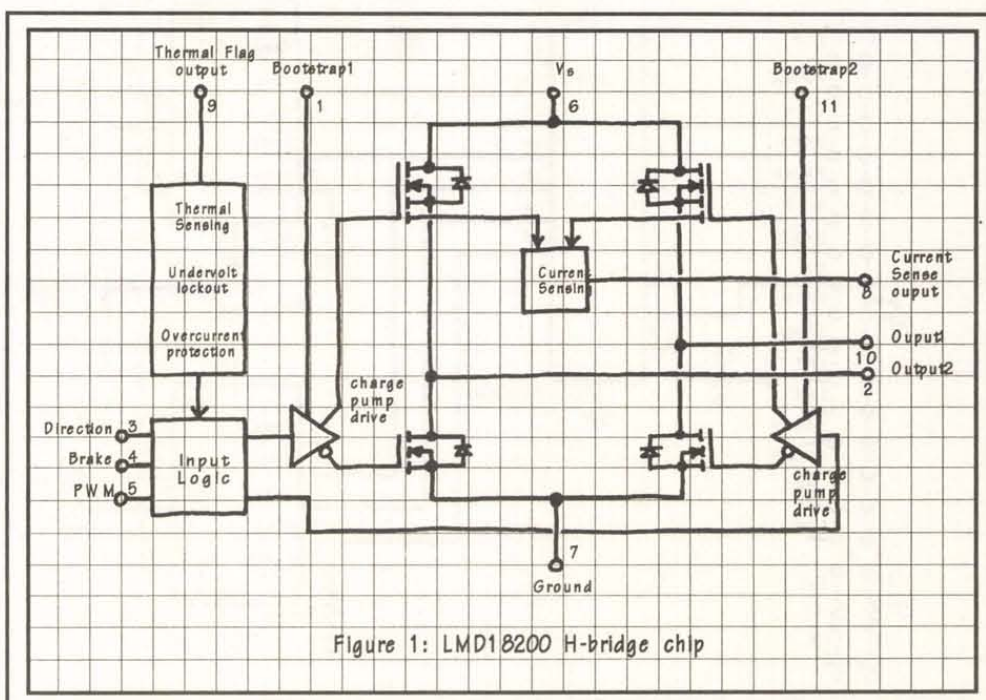


Figure 1: LMD18200 H-bridge chip



ZMI ENGINEERING

PAGER CODE RF GENERATOR: A PORTABLE Pager Tester that can test any POCSAG pager in the 930 MHz band, *FLEX upgrade pending*. Good for testing PDR receivers in the field or a quick test for customer pagers in small shops that are not ready to spend big bucks on more expensive test equipment. For more information please go to <http://www.zmieng.com>

Price: \$1,399.00

CODE SYNTHESIZER SPECIFICATION

1. Direct frequency entry, Starting at 929.0125 Ending at 931.9875, for 80 channels. 25 KHz channel spacing. Power out unleveled 2-5 mW into 50 ohms.
2. Direct CAP code entry of the 7 digit numeric address, send any numeric or alphanumeric message, up to 16 characters.
3. The POCSAG baud rate: 512, 1200, 2400 can be selected.
4. Single or continuous transmit select, this will send the message out once, or continuous for testing and troubleshooting receivers and Pagers or PDRs. Also send out Preamble only, once or continuous.
5. Battery operation, or wall adapter for in-house operation.

ZMI ENGINEERING

Phone (661) 254-1993 • E-mail zmi@zmieng.com
25023 Peachland Ave #150 • Newhall, CA 91321-2519
<http://www.zmieng.com>

PWM	DIR	BRK	Active Output Drivers
H	H	L	Source1 Sink2
H	L	L	Sink1 Source2
L	X	L	Source1 Source2
H	H	H	Source1 Source2
H	L	H	Sink1 Sink2
L	X	H	NONE

TABLE
1

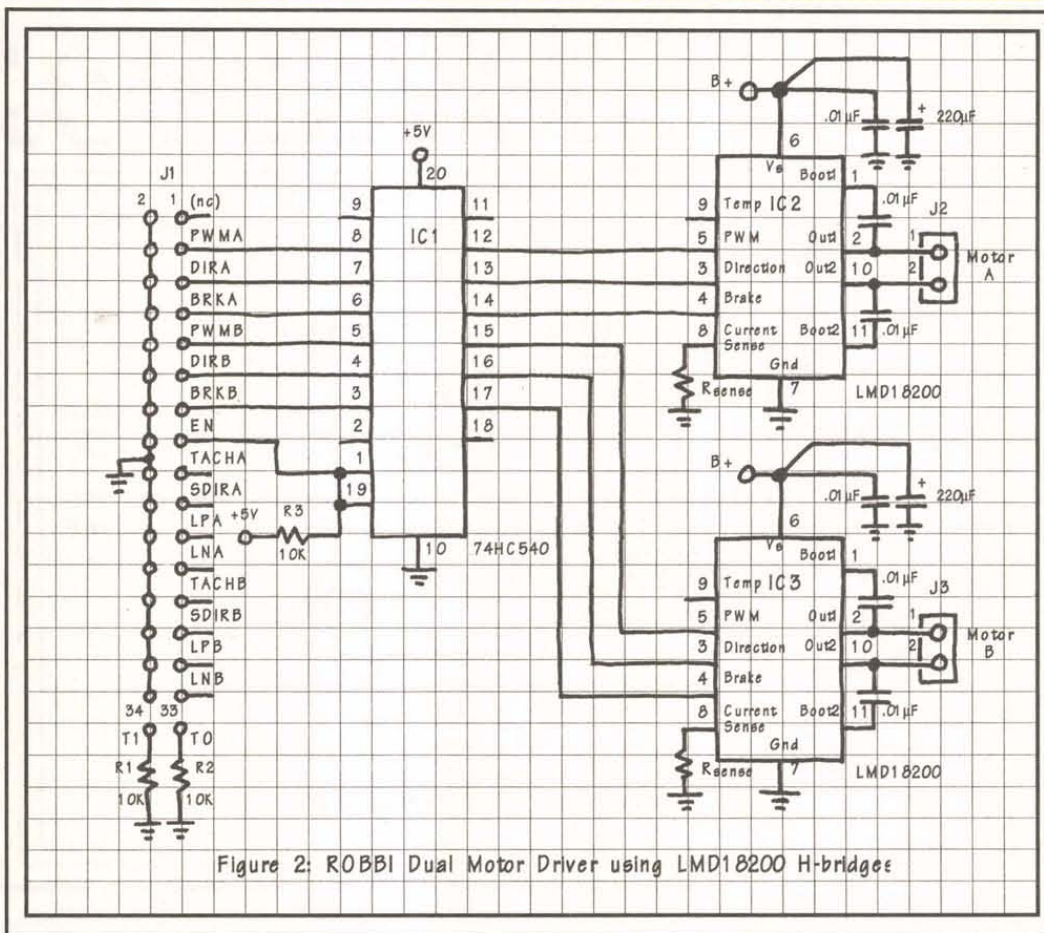


Figure 2: ROBBi Dual Motor Driver using LMD18200 H-bridges

ly everything intrigues me, and, to get back on the topic of robotics, I think it would be way cool to design a robot that could be built

with nothing but a Leatherman tool and, say, scrap floppy drives and tuna cans ...

Ah, spring is indeed a time for

daydreaming.

Fortunately, I have done more than daydream this month. I have in front of me some Robot Builder

Interface (ROBBi) Dual Motor Driver boards I built several years ago. These boards nicely illustrate the device independence of the ROBBi interface specification I talked about last month.

One board uses four SPDT relays and a couple power MOSFETs to make two H-bridges, and the other two both use decidedly more high-tech IC H-bridges — the LMD18200 from National Semiconductor and the L6203 from SGS Thompson. As it turns out, these two chips have quite similar capabilities, and they are a good place to begin exploring the topic of integrated H-bridges.

The LMD18200

Looking at Figures 1 and 2, National's chip seems tailor-made for the ROBBi motor interface. Actually, it's the other way around. Back eight years ago in the Seattle Robotics Society, when we were going through the exercise of defining what signals belonged in the ROBBi spec, I had just got my hands on some samples of the then-new IR8200, International Rectifier's version of the LMD18200. I kept its elegant interface in mind as we defined the motor driver signal set.

See, most H-bridge chips merely provide separate control pins for each half of the H-bridge, in effect treating it as two independent half H-bridges or so-called "push-pull" drivers.

This can be advantageous when you want to control separate single-ended devices (i.e., devices that have one terminal tied either to ground or B+ and the other terminal tied to the push-pull driver output). Each half H-bridge then acts as an independent current source or sink.

When you are driving a motor, though, it just adds complexity, since you need to be able to manipulate both control pins in order to optimally control a motor in all four quadrants (four-quadrant control is just a fancy way of saying your H-bridge can accelerate or decelerate the motor in either direction).

Moreover, Sign & Magnitude (S&M) control requires different manipulations of those control pins than Locked Anti-Phase (LAP) control requires.

All of the solid-state H-bridge circuits I've presented so far in this series have used simple two-pin control, not because that's the best way to build an H-bridge, but because it makes understanding the H-bridge circuitry easier. The LMD18200, however, provides the extra interface circuitry that makes controlling a motor easy.

Use your PC as a scope and datalogger!

Parallel Port Scope
spectrum analyzer, and digital multimeter



ADC Virtual Instruments turn your PC or laptop into a sophisticated storage scope AND spectrum analyzer AND multimeter. Display simultaneously on large screen! 100MS/s 8-bit or 1.2MS/s 12-bit or 333KS/s versions. Great for schools, test depts, etc. Input to Excel! LabView/NT drivers included.

Environmental Logging
record temperature, humidity, etc.



ENVIROMON - temperature (thermistor), humidity & light sensors, door position, etc. Record for 365/24 without a PC even if power fails. Monitor 30 sensors 400 yds away. With cables and easy software. Remote audio alarm. Use TC-08 for most thermocouples.

osziFOX
20MS/s handheld scope



osziFOX - handheld storage scope and DVM - stand-alone or plugs into your PC for display, store-to-disk, printing in color. Inputs to 100V, trigger, backlight LCD.

Download FREE demo software. Sales only: 1-888-7SAELIG

www.saelig.com 716-425-3753 • -3835 (fax) saelig@aol.com

pico
Technology Limited

Stocked in NY by Saelig Company: Virtual Instruments, I2C and embedded controllers, BITlink 2-wire networks, RS232/422/485, frame grabbers, etc. See www.saelig.com for Product of the Month!

PC-based Instruments!

Pumping Charge

The LMD18200 provides a great deal more, too, to make the robot-builder's life easier: it handles 6A peak current and 3A continuous and supply voltages up to 55V. Its switching elements have a low R_{ds} ON resistance of about 0.3 ohms per switch — not as low as the power MOSFET H-bridges I've already presented, but respectable.

It uses an internal 300kHz charge pump to provide a constant high-side drive voltage, but it can also use external bootstrap capacitors. These are needed when you switch the bridge at frequencies higher than 1kHz because the on-chip charge pump can provide only enough current to give a high-side drive voltage rise time of 20 microseconds.

External bootstrap capacitors use the H-bridge switches themselves to generate a high-side voltage boost in exactly the same manner as the bootstrapped H-bridge I presented in my Jan. 2000 column.

To review, the bootstrap principle is, in essence, a charge pump where a large value capacitance provides enough energy to quickly charge the gate capacitance of the high-side switches, making much higher H-bridge switching frequencies possible.

The charge-pump action is accomplished by the power switching elements themselves so that, with 10 nF bootstrap capacitors connected from the outputs to the bootstrap pins of each high-side switch, rise times less than 100 ns are possible, allowing switching frequencies up to 500kHz. Tired of your PWM circuit whining? You won't have that worry with these babies.

The chip provides such niceties as internal fast recovery protection diodes (shown in Figure 1) and

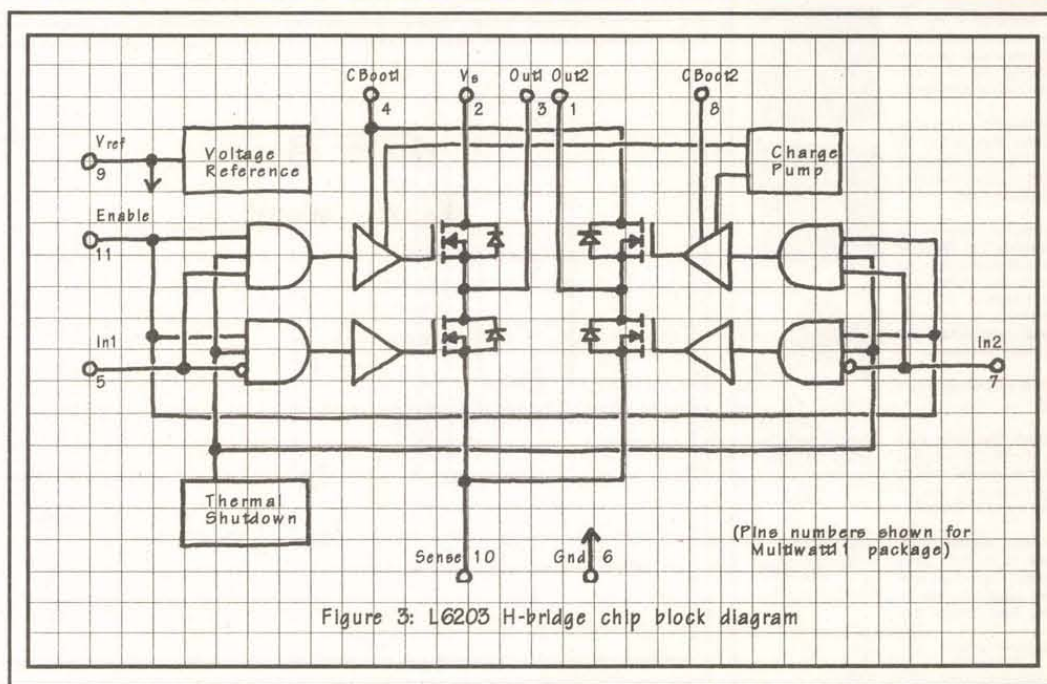


Figure 3: L6203 H-bridge chip block diagram

undervoltage lockout. Builders of robots powered by less than 12V won't like this nicety, but there it is. It also provides short circuit protection, a thermal warning output pin that trips at 145°C, and thermal shutdown at 170°C.

It also includes logic to produce a "deadband" delay between high-side and low-side switching transitions, thus eliminating shoot-through current — the current spike that would otherwise occur during the brief time when both upper and lower switches were conducting as one shut off and the other turned on.

One of the more intriguing features of the chip is its current sense output pin. The high-side switches dedicate a small number of their source gate cells to the current sense function. Rather than sense current by measuring the voltage across a precision low-resistance

current shunt that carries the whole H-bridge current, these current sense cells siphon off a minuscule amount of current directly from the high-side switches.

This current is directly proportional to the current flowing through the high-side switches, with a ratio of about 377μA:1A. All it takes is a resistor from the current sense output to ground to turn the sense current into a voltage proportional to the motor current.

The LMD18200 comes in an 11-pin package that looks something like a double-wide TO220. The mounting tab is common with the ground pin, so you can heatsink to a grounded chassis with no problem. The chip goes for less than \$20.00 through most distributors (\$23.55 from Digi-Key). Here's a hint: If you ever need to find price and availability for a chip and

who carries it, try this website: www.findchips.com.

The L6203

Figures 3 and 4 show what SGS-Thomson's L6203 is all about. The similarities with the LMD18200 are striking. The L6203 can handle similar currents (5A peak, 4A cruise), has an R_{ds} ON of 0.3 ohms, has thermal shutdown and shoot-through protection, and operates between 12V and 48V.


It also has an on-chip charge pump and pins for optional external bootstrap caps to improve high-side switching speed, and it comes in an 11-pin super-duper TO220 package (they call it the "Multiwatt11" package).

Its maximum operating frequency is 100kHz — 1/5 that possible with the LMD18200 — but this won't affect most motor drive

UNI-MICRO™

Super-Small-Low Power

The NEW UNI-MICRO series of modules provides a complete ready to use single board computer on a 1.75" X 1.5" module with large amount of non-volatile flash based memory. Expanded capabilities, multiple serial busses, in-circuit programming, including first time programming and a very low power consumption of 58 mA, makes this series of modules perfect for instrumentation, monitoring and control applications.

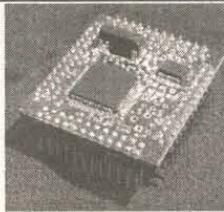

Microcontroller Design Made Simple

Small • 80C51 code compatible • 256 x 8 ram • 2K x 8 Battery backed sram with automatic power switching • 128K x 8 Flash memory • Parallel or serially programmable • 32K x 8 Flash memory • 3 16 bit timers • One 8 channel 10 bit A/D converter • Two 8 bit PWM outputs • One full duplex UART • 16 Mhz speed • 3000 gates flash CPLD • IIC serial bus • JTAG bus • 54 configurable I/O pins • RS232 driver on board • Voltage regulator on board • Power-on reset • Program security • Very low development costs • Assembly, C, Basic programmable.

\$59

OS Systems 678 731-0730 <http://www.ossystems.net>
205 Morgan's Landing, Dunwoody, GA 30350

Write in 117 on Reader Service Card.

ON SCREEN DISPLAY-CHARACTER OVERLAY BOARD


Need to display more text than your LCD module can handle? OSD-232 is the solution! From any RS-232 serial source like a PC or Basic Stamp, display 28 columns by 11 rows of information (308 characters total) directly onto any NTSC or optional PAL baseband (video in) television or VCR. OSD-232 can overlay monochrome text onto an incoming video source or display colored text on a self-generated colored background screen.

OSD-232 \$99.00
We accept Visa and Mastercard.

Intuitive Circuits, LLC
2275 Brinston • Troy, MI 48063
(248) 524-1918 • <http://www.icircuits.com>



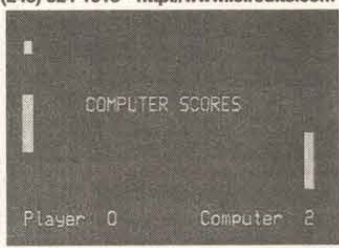OSD-232 on board a radio controlled airplane



An OSD-232 video game programmed in BASIC

Write in 112 on Reader Service Card.

Software for learning & designing

This new range of products, from Matrix Multimedia in the UK, includes resources and tools to help you learn about electronics and helping you to design electronic products and systems.

A complete course in electronics. Made up of 3 CD ROMs: Electronic Circuits & Components, Digital Electronics, and Analog Electronics.

A complete course in programming the PICmicro series of microcontrollers: the PICtutor CD ROM and development board. Comprehensive tutorials, assembler / send package, and flexible development board.

A course in Filter design: Filters CD ROM.

A complete Electronics CAD suite: CADPACK includes software for schematic capture, circuit simulation, circuit animation and even PCB layout.

A scalable digital logic simulator. Digital Works allows complex digital logic circuits to be built and tested on-screen for learning logic design and



	Student	Institution	10 user
each program / CD ROM	\$50	\$99	\$300
PICtutor CD + development board	\$149	\$300	-

CD ROMs now available from all Velleman distributors

Complete product descriptions available at:
www.matrixmultimedia.co.uk
or order immediately at:
Bright Future
6540 Cedarview Court,
Dayton Ohio 45459-1214
Tel: (937) 438 5373 Fax: (937) 438-3229

Write in 111 on Reader Service Card.

PICmicros & BASIC

PicBasic Compiler - \$99.95

PicBasic Pro Compiler - \$249.95

Now it's even easier to program the fast and powerful Microchip PICmicros. The PicBasic and PicBasic Pro Compilers convert your English-like BASIC programs to files that can be put directly into a PICmicro. True compilers for faster, longer programs. BASIC Stamp™ I/II* libraries. For mid-range PIC12C67x, 14Cxxx, 16C55x, 6xx, 7xx, 8x, 87x, 9xx and high-end 17Cxxx (PicBasic Pro only).

*BASIC Stamp is a registered trademark of Parallax Inc.

**New! PIC-X1
Experimenter/
Lab Board**

Assembled - \$199.95
Kit with parts - \$139.95
Bare PCB only - \$49.95



EPIC Plus PIC Programmer - \$59.95



Programs PIC12C5xx, 67x, 14Cxxx, 16C505, 55x, 6xx, 7xx, 8x, 87x and 9xx.
Optional ZIF adapters for DIP, SOIC, MQFP, PLCC.

Runs off two 9-volt batts or optional AC adapter. Includes programming software and assembler.

**PICProto
Prototyping Boards**

Get it wired quicker! High-quality blank prototyping boards for PICmicros. Holds PICmicro, 5V reg, caps, oscillator, DB9-25, large proto area. \$8.95 - \$19.95



microEngineering Labs, Inc.

Box 7532 Colorado Springs CO 80933
(719) 520-5323 (719) 520-1887 fax
<http://www.melabs.com>

NOTEBOOK

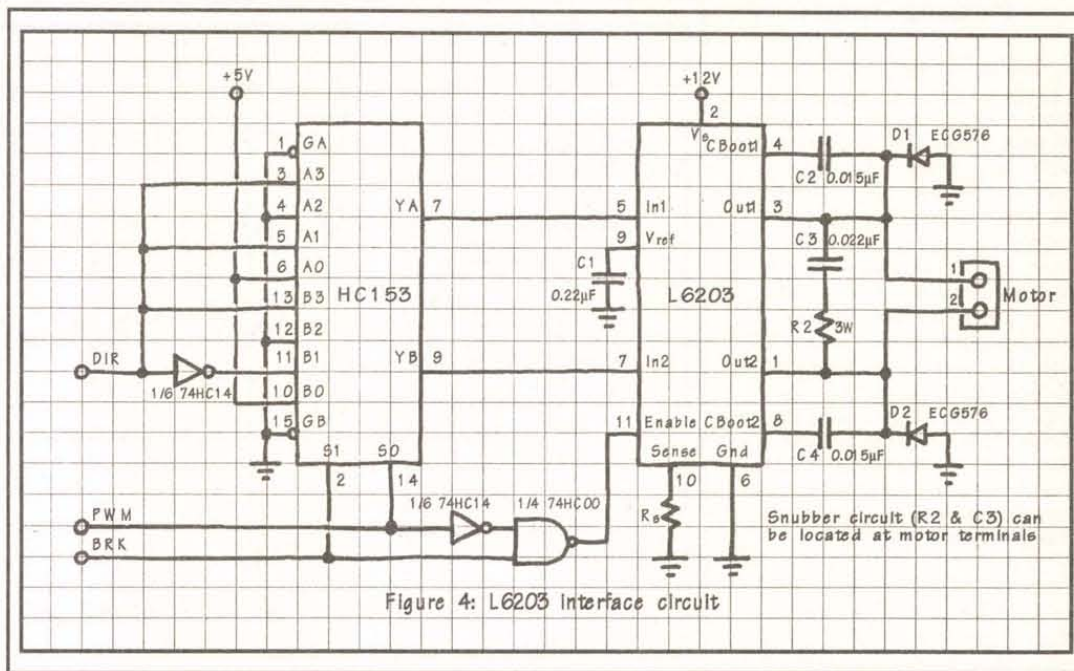


Figure 4: L6203 interface circuit

designs. The larger differences are that it uses the two-wire control approach and that current sensing must be done the old fashioned way. It's also about half the cost of the LMD18200.

The two-wire control causes the most headaches when it comes to interfacing to the ROBBi signals. Figure 4 shows a low-tech, but quite usable design using simple HC glue logic.

You could replace everything to the right of IC1 in figure two with two copies of the circuit in figure four to get a full ROBBi Dual Motor Driver (that schematic is left as an exercise for someone less sleep-deprived than me).

The HC logic implements the truth table shown in Table 1, which allows an L6203 to behave the same as an LMD18200 with full S&M and LAP modes.

The heart of the design is a dual 4-to-1 logic multiplexer. Multiplexer logic design is as easy as writing down a truth table. In this circuit, two logic inputs — PWM and BRK — drive the multiplexer select lines S0 and S1.

The logic level at the outputs then corresponds with the logic level present at the multiplexer input selected. Notice that some of the MUX inputs are permanently tied either high or low; the outputs are functions of PWM and BRK alone, corresponding to the "X" (don't-care) states of DIR.

For instance, when both PWM and BRK are low, you want to turn ON the high-side switches of both halves of the bridge, regardless of the state of DIR, so the A0 and the B0 MUX inputs are tied high. When PWM is low and BRK is high, on

the other hand, you want all switches — high-side and low-side — to be turned OFF, again regardless of the state of DIR. Tying B2 and A2 to ground accomplishes this.

The rest of the multiplexer logic uses either true or inverted versions of the DIR input to determine the states of the outputs. Inspecting the truth table reveals that the A1, A3, and B3 inputs all must use the non-inverted DIR signal because the required logic outputs YA and YB are the same level as DIR for those combinations of PWM and BRK. The B1 input, however, must use DIR inverted because YA and YB need to be the opposite logic level as DIR for that state.

The rest of the logic, the second inverter and the NAND, takes care of the last line in the truth table. When PWM is low and BRK is high, all of the H-bridge switches must be turned OFF, and a low level on the L6203's Enable pin does the trick.

If the above explanations about multiplexer logic have left your head spinning, take a look at Don Lancaster's *TTL Cookbook* or *CMOS Cookbook*; in these classic books, he gives the complete run-down on multiplexer logic design with lots of examples to help you reach the "Ah-hah!" stage.

And, for those of you who really do want to implement this interface as individual gates — maybe to program them into a PLD, say — here are the corresponding logic equations in C notation:

```
In1 = (!PWM && !BRK) ||
      (PWM && !BRK && DIR) ||
      (PWM && BRK && DIR)
```

```
In2 = (!PWM && !BRK) ||
      (PWM && !BRK && !DIR) ||
      (PWM && BRK && DIR)
Enable = !(PWM && BRK)
```

(I've made no attempt to tease out the common terms and minimize these equations; this is also left to the reader as an exercise.)

Build Your Own Robot!

Few books on Amateur Robotics have been as avidly anticipated as Karl Lunt's book, *Build Your Own Robot!* (paperback, published by A. K. Peters, 2000, ISBN 1-56881-102-0). I know I was looking forward to it, and I may well have been the first person in the country to receive a copy of it: a hefty sheaf of laser-printed galley sheets. For those of you who have only recently begun reading *Nuts & Volts*, Karl preceded me with his own column, "Amateur Robotics," before I began writing the Amateur Robotics Notebook column. Amateur Robotics ran 70 issues straight from October '92 to

Please note that my contact information is now different. If you have suggestions, questions, or comments about amateur robotics topics, you can now reach me at:

Robert Nansel
Box 228
Ambridge, PA 15003

The E-Mail address is the same:
E-Mail: bnansel@nauticom.net

NOTEBOOK

May '98. When I slipped into Karl's shoes (metaphorically speaking) in June '98, I knew I'd have a long way to go before I could claim 70 straight columns in a row, and an even longer way to go before I could say I'd come close to filling those shoes.

Now he's gone off and put together a book, a collection of his favorite *Nuts & Volts* columns — a big book, 574 pages — and I despair of ever even catching up to him, forget about the shoes.

I subscribed to *Nuts & Volts* during most of Karl's tenure specifically to read his column even though we saw each other at least once a month at Seattle Robotics Society meetings.

In those years, we talked endlessly about robots over the phone or at dinners at each other's homes, or on the beach during the SRS annual G.E.A.R. campouts.

I subscribed because, even with all this obsessive communication, I still couldn't otherwise keep up with everything Karl was up to in robotics. Reading his column helped me and many, many others get consistently good information, new ideas, and new projects.

When I first met Karl in 1990, the position of Joe Gearhead in the world of Amateur Robotics was pretty grim: amateur robotics was just starting to recover from the debacles of the 1980s, but even so, there was no BOTBoard, no TinyForth, and no SBasic.

Interactive C was barely a gleam in Randy Sargent's eye, and Flynn and Jones' *Mobile Robotics: From Inspiration to Implementation* had not even been written. A lot has changed in 10 years.

Leafing through this book, I'm struck by how much influence Karl has had. The ubiquitous BOTBoard, for instance, came about in part because Marvin Green was trying to find ways to beat Karl in the

Line Following contest.

There were several years there where Karl's 'bots would beat Marvin's by margins of just a fraction of a second. I remember escorting Marvin to a local hobby shop one Sunday morning an hour before one of these competitions so he could put larger wheels on his 'bot to gain a little more speed.

Anyway, Karl has arranged the best of his columns into related categories (Getting Started, Software, Electronics, Mechanics, Robotics Projects, Adventures in Hacking, Way Cool Robots, and Sidelights), adding background and historical where-are-they-now blurbs at the beginning of each. He's finished it off with three superb appendices: Contacts, Hobby Servo Mods, and Web Pages.

There are some slight negatives. Karl warns that some of the material in his book is dated, and it's true. In particular, certain surplus deals and toys he hacked over the years are no longer readily available.

Then, too, there is a certain Seattle-centrism that's hard to overcome (I know, I never could overcome it when I lived in Seattle). But his enthusiasm and expertise are infectious, and the way he approaches any project, new or old, is worth the \$34.00 price.

Next Time

Next time, I'll take a break from H-bridges and motors (mostly) and talk instead about the results of this year's Trinity Home Robot Fire Fighting Contest.

Going to Hartford for this, the largest Amateur Robotics competition in America, always gets me jazzed up. Also, I've got a whole new robot design in progress, the beginnings of which you'll see, too. NV

Go Wireless With Our Modules


SILRX/TXM

SILRX — \$26.00 ea.
TXM — \$15.50 ea.

The TXM and SILRX modules are a transmitter and receiver pair which can achieve a one-way radio data link-up to a distance of 200m over open ground.

Both units are supplied in space-saving single-in-line packages and offer SAW controlled, wide band FM transmission/reception.

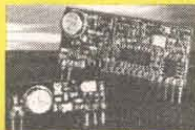The modules are particularly suited to battery-powered, portable applications where low power and small size are critical design criteria.



TX2/RX2

TX2 — \$19.50 ea.
RX2 — \$38.50 ea.

The TX2 and RX2 radio transmitter and receiver pair enable the simple implementation of a data link at up to 40kb/s at distances up to 75m in-building and 300m open ground. Both modules combine full screening with extensive internal filtering to ensure EMC compliance by minimizing spurious radiations and susceptibilities. The TX2 and RX2 modules will suit one-to-one and multinode wireless links in applications including car and building security, EPOS and inventory tracking, remote industrial process monitoring, and computer networking.

Because of their small size and low power requirements, both modules are ideal for use in portable, battery-powered applications such as hand-held terminals.



900 MHz
AVAILABLE NOW

RPC

RPC — \$99.00 ea.


The RPC module is an intelligent transceiver which enables a radio network link to be simply implemented between a number of digital devices. The module combines an RF circuit with processor-intensive low-level packet formatting and recovery functionality, requiring only a simple antenna and 5V supply to operate with a microcontroller or a PC.



BiM

BiM — \$69.00 ea.

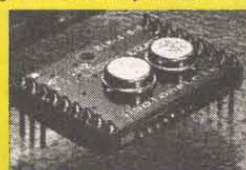The BiM module integrates a low-power UHF FM transmitter and matching superhet receiver together with data recovery and TX/RX change over circuits to provide a low-cost solution to implementing a bi-directional short-range radio data link.



Lemos International Co., Inc.

65 Southbridge Street, Auburn, MA 01501

Phone (508) 798-5004 ♦ Fax (508) 798-4782

www.lemosint.com ♦ sales@lemosint.com

All products available in either 418 or 433 MHz

Write in 113 on Reader Service Card.

SAME DAY PROTOS


Modem Gerber files before 9 AM EST.

We ship the boards same day.

Multilayers NEXT DAY.

Service:

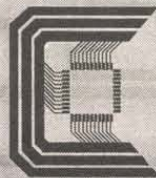- Instant Quotes
- Single / Double / Multi-Layers
- SMOBC and LPI
- Thru Hole or SMT
- Nickel and Gold Plating
- Routing / Scored Panels
- Blind and Buried Vias
- Electrical Testing
- Carbon Ink / Peelable Mask
- UL Approved



CHICAGO CIRCUITS CORPORATION

Manufacturer of Printed Circuit Boards

2685 UNITED LANE

ELK GROVE VILLAGE, IL 60007

E-MAIL: sales@chicagocircuits.com

TEL: (847) 238-1623 • FAX: (847) 238-9160

MODEM: (847) 238-1728


Write in 116 on Reader Service Card.

World's Smallest 68HC11 Microcontroller Module!

MicroStamp1™

NEW!

- tiny 1-inch x 1.4-inch module
- 5V regulator, 8MHz crystal
- choice of 8K or 32K EEPROM
- plugs into your breadboard like a DIP
- SCI, SPI, OC, IC, timer, interrupts, and more
- all I/O lines brought out to versatile 20-pin connector
- easy programming/code-loading with Docking Module
- 8K Starter Package #MS11SP8K.....\$49*
- 32K Starter Package #MS11SP32K.....\$60*
- additional modules from \$34 each

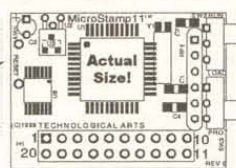

Possible Applications:

- remote telemetry
- micro robotics
- smart sensors
- many more!

Technological Arts

Visa/MasterCard
Discover/Amex


Phone: (416) 963-8996

Fax: (416) 963-9179

www.technologicalarts.com

Write in 118 on Reader Service Card.

2.4 GHz Wireless Transmitter & Receiver

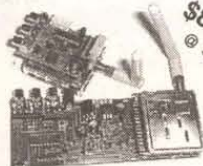

\$89/pair
@ 50 pcs

2.4 GHz - 2.48 GHz User Selectable
Over 700' Range and 4 Chl Auto-scan
NTSC, PAL, Composite video B/W or Color
2 Audio Inputs may be used for digital data
Customizations including battery packs
and Special Frequencies

Matco Inc.
(800)440-0299 or (800)719-9605
www.mat-co.com

MFM COMMUNICATIONS

NOW IN STOCK —

- Magnetic Strip Reader/Writers
- Mobile Mag-Strip Readers
- 7816 Programmers

PLUS


*A wide range of
cellular accessories*

24 HOUR DELIVERY

Tel/Fax: 011441342312403
<http://members.aol.com/mfmcom123/index.htm>

SBC2000-074

RS-232

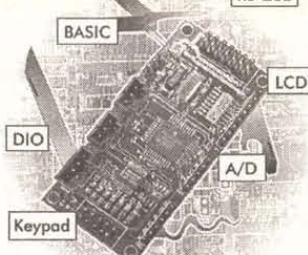

Versatility starting at \$64 each.

Voice: 303.422.8088 Fax: 303.422.9800
www.sbc2000.com

Vesta Technology, Inc.

SWITCHES — LEDs — MOTORS —
SPEAKERS — POWER SUPPLIES —
CONVERTERS — CHEMICALS — WIRE —
OTHER ELECTRONIC PARTS — All types —
All sizes — Commercial to Spec Grade

Full Size Toggle Switch, 1/2" Dia., as low as..... 364
Mini Toggle Switch, 1/4" Dia., as low as..... 304
Sub-Mini Toggle Switch, 1/8" Dia., as low as..... 324
Rocker Switches, as low as..... 204
Slide Switches, as low as..... 204
Push Button Switch, 1/4" Dia., as low as..... 294
Surplus Small and Mini Motors, as low as..... 504
Mini Speakers, as low as..... \$1.00
3mm LED — Red, Green, Yellow, as low as..... 154
5mm LED — Red, Green, Yellow, as low as..... 154

Let us quote on your specific LED needs

AC-DC Converters, 7 outputs, 1000 mA.....\$4.00

Chemicals, see catalog

WIRE: Hook-Up, Lead, Speaker & Telephone

CALL OR FAX FOR QUOTES

OR CATALOG

DEMAR ELECTRONICS

P.O. Box 7215, Algonquin, IL 60102

Toll Free 877-655-6433

Fax 847-854-4434

Got Dial Tone?

Telecom Hardware/Software Developers
STOP using your phone lines to test and demonstrate
your telecom devices. Our affordable telephone line
simulators offer authentic USA dial tone, busy signals
and ringing. Supports high speed analog modems too!



RING-IT! TELCO SIMULATOR
• Caller-ID
• LED display
• Audio Output Jack
• Real 20Hz Ring
• \$325 (\$169.95 kit avail)

PARTY-LINE TELCO SIMULATOR
• Six Extensions
• Caller-ID
• Distinctive Ringing
• CPC Disconnect
• \$425 (\$199.95 kit avail)

Digital Products
COMPANY

134 Windstar Circle
Folsom, CA 95630 USA
Tel: 916-985-7219
Fax: 916-985-8460

<http://www.digitalproductsco.com>

LCD Terminal \$99



Re-Programmable
LCD 240 x 64 EL Backlit
RS-232 Port
1200 Baud Modem
8051 Compatible Microcontroller
192k Low Power Static Memory
Infrared Transmitter
Nicad Battery Pack
QWERTY Keyboard
FM SCA Data Receiver

Junkware.com

<http://www.junkware.com>

PC BOARD SERVICES

PCB Design Layout

Thru Hole

SMT

Multilayer

PCB FABRICATION

In-house Prototypes

Single and Double Side

Plate Thru Hole

ASSEMBLY

Thru Hole

Small Project Specialists

Serving Engineers and Hobbyists
for 16 Years

MIDLAND TECHNOLOGIES

800-726-8871 Voice

406-586-0300 FAX

Press-n-Peel Transfer Film

PC Boards in Minutes

8.5" x 11" Shts.
1" Or Photocopy
**Use standard
household iron

1. LaserPrint*
2. Press On**
3. Peel Off
4. Etch



Use Standard Copper Clad Board
20 Shts \$30/ 40 Shts \$50/ 100 Shts \$100
Visa/MC/PO/CK/MO \$4 S&H/Foreign Add \$7

Techniks Inc.

P.O. Box 463, Ringoes NJ 08551

ph. 908.788.8249 fax 908.788.8837

www.techniks.com

Visit Our E-Store On-Line!

ATOMIC TIME

Automatic time synchronization
for applications where accurate
time is essential to data integrity

FEATURES

WWVB based
Serial and LCD outputs
Y2K compatible
0.1 second accuracy

APPLICATIONS

Network time servers
Embedded systems
Timers/sequencers

ULTRA LINK

775 782 9758 www.utio.com

New! ActiveWire™USB Simple USB Interface



- Internet Browser Script-able
- 24 MHz CPU core with USB
- Firmware downloadable via USB
- 16 bit parallel I/O
- Expandable add-on boards
- New firmware and scripts
available from website

\$59 plus shipping

ActiveWire, Inc.

www.activewireinc.com

ph(650) 493-8700 fx(650) 493-2200

QUALITY KITS

#1 Source for Electronic Kits

Great selection of Hi-Fi AUDIO Kits,
PSUs, Transmitters, Oscilloscopes,
PIC Programmers, and much more.

Toll Free Order Line:

1-888-464-5487

Secure On-Line Ordering

www.qkits.com

Call 613-544-6333 for free catalog

North American Kit Distributor

49 McMichael St., Kingston, ON

K7M 1M8, CANADA

Convert RS-232 to RS-485 or TTL/CMOS for Only \$49.00

Communicate up to
4,000 feet, at up to
1 MEGA-BPS, full
or half duplex, up to
32 units on one serial
link, with 31 jumper
options for flexible
configuration, LED
indicators.



COMMUNICATIONS CONVERTER

- FULL SCHEMATIC AND DOCUMENTATION
- FULL FAMILY OF MODULAR DESIGNS
- RS-485/RS-422 REMOTE I/O MODULE KITS
- NETWORK SOFTWARE AND SOURCE CODE
- AUTOMATIC OR RTS UNITS AVAILABLE
- RJ-11/12 CONNECTORS OR TERMINAL STRIP
- TURN YOUR PC INTO A DISTRIBUTED DATA
ACQUISITION AND CONTROL SYSTEM

R.E. SMITH

(513) 874-4796

4311 TYLERSVILLE RD. ■ HAMILTON, OHIO 45011

www.rs485.com

Fast / Economical / Easy CIRCUIT BOARDS

As-Low-As **\$80.00** Per-Lot



- Next Day Delivery
- 2-Sided, plated thru
- Order over the
Internet

For Complete Details and
Instructions Log on:

www.pcbexpress.com



13626 South Freeman Rd., Mullino, OR 97042
(503) 829-9108 Fax (503) 829-5482

ESP CONNECTOR FOR HIGH-TECH GARMENTS

Electrical
Contacts for
Clothing

ESP:
Electrical
Snap Patch
Connector easily
sews into clothing

Audio applications, sensors,
display panels or keypads

Molded cable assembly with
3.5mm phono plug snaps
into ESP

Gold plated for reliability

3" x 1.5" patch

EVALUATION KIT AVAILABLE
www.autotime.com 503-452-1455

GLOBALTECH DISTRIBUTORS

The Ultimate Electronic Saving Store

Call Today!—1-(800)582-5116

	25ps.	100ps.	500ps.
PIC12C508	1.30	1.20	1.15
PIC16C54	1.40	1.35	1.30
PIC16C56	1.65	1.50	1.45
PIC16C621	2.00	1.95	1.85
PIC16C622	2.25	2.15	1.95
68HC705C8A	5.50	5.00	4.85
ATF89C52	4.00	3.50	3.15
82S131	1.50	1.30	1.15
Gall16V8b	1.00	.95	.75
4mhz Res.	.45	.40	.32
20mhz Crystal	.50	.45	.40
CATV Remote	4.25	3.75	3.25
Universal Remote Controls			4.50

Order@globaltechdistributors.com



BEST MICROPROCESSOR STOCK DISTRIBUTOR WORLD WIDE.

ELECTRONIC KITS

Robotics ♦ Audio ♦ Science ♦ RF

The most extensive selection of
hobbyist and professional
Electronic kits available anywhere
in the world.

Toll Free Order Line

1-877-449-0739

Call 1-877-449-0743 for a free catalog

MODULAR CONCEPTS

P.O. Box 2250

Livermore, CA 94550

PCB EXPRESS, INC.

"PROTOTYPE TO PRODUCTION"

S/SIDED: 5-days, 10 Pcs.	\$275.00
D/SIDED: 5-days, 5 Pcs.	\$300.00
D/SIDED: 5-days, 10 Pcs.	\$350.00
4-LAYERS: 5-days, 5 Pcs.	\$750.00
4-LAYERS: 7-days, 10 Pcs.	\$850.00
6-LAYERS: 5-days, 5 Pcs.	\$950.00
6-LAYERS: 7-days, 10 Pcs.	\$1,175.00

(Up to 30 sq. inch each, includes Tooling)

"SERVICES" - UL Approved

SMOBC, LP1 mask & Legend
Photoplotting, Electrical Testing
Thru hole/SMT, Gold/Nickel Plating
Routing and Scored Panel, Instant Quotes

PH: (888) 427-2920, Fax (847) 427-1949

E-Mail: cir1920@aol.com

LOWEST COST & FAST DELIVERY

VIDEO PRODUCTS



CNL-100 \$49 BX-120-P \$59 SX-800 \$79

- 430 TV Lines Resolution
- 9-14 VDC Operation
- Infrared Sensitive
- SX-800 has Audio Output
- A-300 Camera Enclosure also available

MATCO, INC.

Schaumburg, IL
1-800-719-9605 • 1-847-619-0852 FAX
E-Mail - info@mat-co.com
Website - www.mat-co.com

10&14 Hour Telephone

Recorders Starting at \$69



Times based on a 180 tape
14 Hour \$89.50/H
120 Tape included!
Automatically starts recording when the phone is picked up and stops when you hang up. Records both sides of the conversation!
Printed catalog \$3 (free with order)

Visit our Online Catalog
www.mscelectronics.com

MSC Electronics

PO BOX 461 Jessup, MD 20794

(301) 497-1600

FAX (301) 497-1925

No Checks • US & Canada Only



EPS

EPROMS AS LOW AS 25¢

27C256	27C040	27C1024	87C51
27C512	27C400	28F010	8751
27C32A	27C4096	28F020	8755
27C32	27C4000	28F040	MC68HC70
27C128	27C4002	28F040H	5C8A
27C84	27C4020	28F040H	PIC16C56
27B16	27C020	8741	PIC16C54
27B08	27C210	8742	PIC16C22
27C512-90	27C010	8744	GAL16V8

STATIC RAM PROCESSOR

HM628128	8255
62256	8254
6264	80C31
6116	

- Many more parts in stock
- All major brands
- All guaranteed

E-Mail: eproms@aol.com

TEL: (818) 774-9444 • FAX: (818) 774-0822

WE BUY EXCESS INVENTORY

FREE SAMPLE COPY! ANTIQUE RADIO CLASSIFIED

Antique Radio's Leading Monthly Magazine

Articles - Classifieds - Ads for Parts & Services. Also: Ham Equip. - Books - Telegraph - 40's, 50's & 60's Radios - Early TV - Auction Reports & more...

1-Year: \$39.49 (\$57.95 by 1st Class)
6-Month Trial - \$19.95. Foreign - Write.

A.R.C., P.O. Box 802-G23
Carlisle, MA 01741
Call: 978-371-0512 — Fax: 978-371-7129
Web: www.antiqueradio.com

SINGLE SIDED PCBS

9¢

9¢ PER SQUIN, \$100 SET UP.
SMOBC, ONE OUNCE COPPER,
PC 75, 1/16", ONE SOLDER MASK
AND ONE SILK SCREEN.
PHOTOPLOT \$ 50.

DOUBLE SIDED PCBS

14¢

14¢ PER SQUIN, \$150 SET UP,
PTH, ONE OUNCE COPPER,
FR4 1/16", TWO SOLDER MASK
AND ONE SILK SCREEN.
PHOTOPLOT \$ 75.

PLEASE VISIT OUR WEB SITE FOR MORE INFORMATION AND
OTHER PRICE EXCEPTIONS WWW.VANDVMACHY.COM

• THESE PRICES APPLY ONLY
TO RECTANGULAR PCBS.

V&V MACHY & EQUIP. INC.

V&V MACHY AND EQUIP. INC. (HOUSTON TX. OFFICE)
PH. (281) 397 8101 FAX (281) 397 6220
MARKETING TECH. S.A. (MEXICO PLANT)
PH. 011 525 3613351, FAX 011 525 3615996

ASSEMBLY & ENGINEERING

Producible designs since 1970

Contract Engineering
Embedded Microprocessors
PCB Layout and Packaging Design
Analog Including RF to 1 GHz
Instrumentation
A/D and D/A

Contract Assembly

High-Speed Fujii Surface Mount
Through hole
Turn-key or Kit
Run sizes one through thousands
Test and burn-in available

Bilocon Corp.
800-736-5927
425-353-2276
www.bilocon.com



Ph 650/367-8320
Fx 650/365-5845
VISA MC

STEREO MICROSCOPE

Model ST 251A

10X and 30X

4 in. Throat

Top & Bottom light

Dust cover

Eyecups

5 year warranty

\$ 250.00



CONTROL • MEASURE • INPUT


MODEL 40-\$109

- RS-232 interface
- 28 lines digital I/O
- Eight analog inputs
- PWM output
- Three stepper ports



MODEL 100-\$279

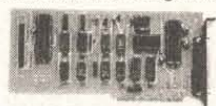- 12-bit 100KHz A/D • Four analog outputs
- Three timer counters • 24 digital I/O



PRAIRIE DIGITAL, INC.

920 SEVENTEENTH ST., INDUSTRIAL PARK
PRAIRIE DU SAC, WI 53578
TEL: (608) 643-8599 • FAX: (608) 643-6754

Specializing in hard-to-find, pre-owned, electronic parts, components and systems

- Monitors, 13" - 21"
- Computer Systems
- Disk Drives
- CPU's
- PC Peripherals
- RF/Microwave
- Specialty Equipment
- Test Equipment
- Measurement Equipment
- Too many items to list

Stock is continually changing.
Check our web site for current inventory and pricing.

www.dmdsystems.com

DMD Systems Recovery, Inc.
Fax 602.305.8485 info@dmdsystems.com

CABLE CONVERTS

TV86/3 86/CH TV86/3V/A
TRIVISON 550/3 \$37.95

VIEW MASTER 2600

125 CHANNEL UNITS

TRI 860/3 10 LOT \$49.95

TRI 860/3V/A 10 LOT \$59.95

V/MASTER 3800/3V/A

FOSS WAREHOUSE DIS

289 SCHENCK ST

N TONAWANDA NY 14120

800-473-0506

800-488-0525 FAX

716-694-6400 716-693-4322 FAX

E/M FOSS@BUFFNET.NET

WEB PAGE: WWW.FOSSW.COM

NO DISCRAMBERS ONLY CABLE CONVERTS

Price Reduction

- GPS Trimble SV6 w/ Mag Ant \$49.95
- Rockwell MicroTracker I I \$49.95

Just in - Siemens
Gigaset 2420 2 unit Cordless
System..... \$199.00

Communications Surplus

713-526-8000 or
1-877-878-6GPS(477)
commsurplus@ev1.net
Fax to 713-522-6309

SOLAR ENERGY!

SIEMENS SOLAR PANELS

MODEL	WATTS	SUGG. PRICE	OUR PRICE	SHIPPING
SP85	65	\$472	\$322	
SP75	75	\$500	\$359	
SM55	55	\$410	\$293	FREE SHIPPING!
SR50	50	\$360	\$259	
SR90	90	\$635	\$437	
SR100	100	\$640	\$464	

All Siemens' Solar Panels are Available!
Quantity Discounts Available!

RV SOLAR POWER KITS

WATTS	SUGG. PRICE	OUR PRICE	SHIPPING
36	\$499	\$350	
50	\$599	\$445	FREE SHIPPING!
75	\$799	\$595	
100	\$999	\$735	

74 page Renewable Energy catalog - \$5

GeneSys Resources, Inc.

P.O. Box 311, Newport, MI 48166-0311
734-552-2074

www.gr12000.com

SMARTCARD

DEVELOPMENT KIT

INCLUDES: UNIVERSAL
PROGRAMMER, POWER
SUPPLY, DB9 CABLE

DEVELOPMENT SOFTWARE,
4 BLANK BASIC SMARTCARDS.

KIT \$200.00 + SHIPPING

EXTRA CARDS \$20.00 EACH
OR 8/\$100.00

SOFTWARE INCLUDED.

POSSIBLE APPLICATIONS INCLUDE:

IDS, COMPUTER SECURITY, SECURE

DATA, MEDICAL RECORDS, ETC.

NOT FOR USE WITH DSS TV

Call TONY at

WIZARD ENGINEERING

1-419-385-3100

Power Quality Inc.
800-255-5545
Fax: 520-344-8847

Heavy Duty Surge Suppressor
Plug Strips, 6 outlet, circuit breaker,
Case of 25 in individual boxes...\$50/case

HP Power Supplies, HP6260B
current is 0-50A...\$100

UPS, 250va to 3 kva, functional and nonfunctional.....Please call

Power Conditioners, Oneac, T.L.C., Teal, Sola, various sizes.....Please call

BMI, Dranetz, and RPM
Power Quality Monitors.....Please call

www.powerqualityinc.com

SURPLUS SALE

1,000,000 WALL TRANSFORMERS



3VDC/100MA CX099 \$0.75
6VDC/100MA CS039 \$1.45
9VDC/100MA CR314 \$1.45
12VDC/200MA CS033 \$0.99
13.5VAC/400MA... CR574 \$1.29
24VDC/500MA... CR174 \$3.40

Min 1000/type -- Call for other types

SURPLUS TRADERS

PO Box 276,
Albany, VT 05440
Tel: (01) 514-739-9328
Fax: (01) 514-345-8303
<http://www.73.com/vt>

FREE CATALOG!

IC PROGRAMMERS

ADVANTECH EETOOLS NEEDHAM DATA IO BP MICRO
XELTEK SYSTEM GENERAL ICE TECHNOLOGY CHROMA

1295 Advantech Labtool-48
895 Needham EMP-30
869 EETool Topmax
650 Xeltek SuperPro III
629 ICE Tech Micromaster LV
469 Xeltek SuperPro F
419 Needham EMP-20
419 EETool Megamax
379 Xeltek SuperPro LX
299 EETool ChipMax
279 Xeltek Micromaster II
209 Needham EMP-10



Gang Programmers 4 TO 8 Sockets

CALL Advantech Labtool-848 8XGang
1085 EETool TopMax W/8XGang
689 Needham SA-20 8X Gang
529 EETool MegaMax4G 4XGang

General Device Instruments

Sales 916-393-1655 Fax 916-392-4949
Order Only Toll Free 800-760-3820

WWW.GENERALDEVICE.COM
WWW.LABTOOL.COM

COMPUTER

BAREBONES SYSTEM THAT INCLUDES:

44X CD-ROM Drive
1.44MB Floppy Drive
56K V.90 Fax/Modem
64 bit 3D AGP Video, 8MB shared
3D Sound with Wavetable
10/100Mbps Ethernet Network Port
UDMA/66 Hard Drive Controller
Removable Hard Drive Rack
Micro ATX Case with Power Supply
3 SDRAM slots for up to 768MB Ram
1 Serial, 1 Parallel, 2 USB Ports
Keyboard, Mouse, Speakers
Accepts ALL Slot 1/Socket 370 CPUs

Just add CPU,
memory, and
Hard Drive

\$245

Visit our website for more details and CPU, memory and hard drive options

www.lapazelectronics.com

La Paz Electronics International
PO Box 261095 San Diego, CA 92196
Order 1-(800) 586-4199 Fax (858) 586-1482

CUSTOM PLASTIC PARTS

• MODELS (WOOD AND RESIN). TO EVALUATE YOUR PARTS BEFORE YOU COMMIT TO MANUFACTURE A MOLD.
• MOLD DESIGN AND BUILDING.



• PRODUCTION OF INJECTION MOLDED PARTS. NO ORDER TOO SMALL OR TOO BIG.
• VERY COMPETITIVE ON HIGH LABOR PARTS.



We can also inject your parts on manual low pressure machines for very small runs or prototypes of parts up to 2 oz. At surprisingly low price.

USA Office: V&V Mech. And Equip. Inc.
Tel. (281) 397-8101, Fax. (281) 397-6220.

Please send blue prints or samples to:
Marketing Tech. S.A., Alamo 93, 4 Piso Sta. Monica,
Tlal. Edo. De Mexico 54040 Tel. 011 (525) 361-3351,
Fax. 011 (525) 361-5986. ATTN: VICTOR M. MENDOZA.

PLEASE VISIT OUR WEBSITE
WWW.VANDVMACHY.COM

SECURETEK
DIRECT FROM MANUFACTURER
"WE WILL BEAT ANY COMPETITORS PRICE"

WORLD SMALLEST
WIRELESS VIDEO CAMERA
(BLACK & WHITE OR COLOR)
TRANSMITS VIDEO UP TO 1000FT.

WE ALSO CARRY:
• CONVERT VIDEO CAMERAS
• COAXIAL SURVEILLANCE PRODUCTS
• CUSTOM MADE VIDEO SYSTEMS
• IN HOUSE ENGINEERING DEPT.

DISTRIBUTOR PROGRAM AVAILABLE

CALL FOR CATALOG:
SECURETEK
7152 S.W. 47TH ST.
MIAMI, FL 33155
TEL. 305.667.4345
FAX. 305.667.1744
www.securetek.net

alone use. The photo in Figure 1 shows the divider assembly as it looks when removed from the model 891A. The rotary switches and pot are easily removed from their aluminum mounting bracket. The resistors are all precision wire wound units mounted on the circuit board that is hidden by the removable shield.

This meter was designed to measure voltages up to 1,000 volts so the divider has a 1 megohm input resistance — see Figure 2. This isn't a problem except good shielding is necessary. I suggest

retaining the shield shown in the photograph and also putting the divider assembly into an aluminum enclosure. A SESCO model MC-14A* looks like a good choice. It measures 8.5 inches wide by 10 inches deep by 3.5 inches high. I've included a suggested circuit as Figure 3. The SESCO enclosure is deep enough to put the opamp power supply behind the divider assembly with a shield plate between them.

Since the input resistance is high, the output resistance is

also high so I suggest an output voltage follower using a low-noise chopper stabilized opamp. This could be built on a small circuit board mounted very near the output binding posts. Another suggestion is to replace the single-turn 10K pot (R37) with a 10-turn pot. This adds another digit to the resolution, but does require recalibration by adjusting R36 (in Figure 2).

Of course, you may not find a Fluke 891A, but ALL differential voltmeters contain a divider which is bound to be useful. Look around and see what you can find. It's helpful (but not essential) to get an Instruction Manual. A good source is Manuals Plus, 130 N. Cutler Dr., N. Salt Lake, UT 84054. 801-936-7000. www.manualsplus.com.

SESCOM, Inc., 2100 Ward Dr.,
Henderson, NV 89015-4249.
800-634-3457. www.sescom.com

Ron Tipton
TDL® Technology, Inc.
5260 Cochise Trail
Las Cruces, NM 88012-9736
Voice 505-382-3173,
FAX 505-382-8810
www.zianet.com/tld

reader Feedback

Continued from page 7

OTHER SOURCES OF KELVIN-VARLEY VOLTAGE DIVIDERS

A differential voltmeter nulls the voltage to be measured against an equal amplitude internal reference. This was a way to get multi-digit measurement resolution in the days before digital voltmeters (DVMs) became com-

mon. To achieve a null, the internal reference voltage must be adjustable in steps equal to the measurement resolution. This adjustment is done with a Kelvin-Varley divider.

Since DVMs are now so common and inexpensive, differential voltmeters are no longer in much demand so they can often be bought rather inexpensively. For example, I recently got a Fluke model 891A for \$40.00. It contains a lovely four-digit Kelvin-Varley divider. The divider assembly is easy to remove for stand-

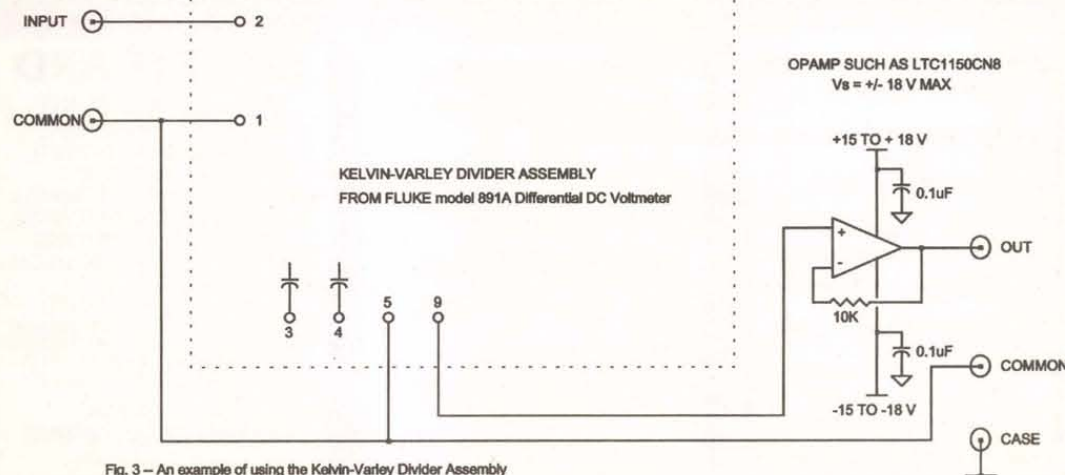


Fig. 3 — An example of using the Kelvin-Varley Divider Assembly

Dear Nuts & Volts:

On the earthquake prediction device article, here is an interesting note. According to my search of the Internet both, Japan and Russia are working on it.

In the Readers Digest book "How in the World" on page 204 it says that there are four possible indicators that may be methods of predicting earthquakes.

"And the fourth is any change in the electrical and magnetic behavior of rocks in the moments when they come close to their breaking point before an earthquake."

It goes on to say that that and other methods worked in 1974 to predict a magnitude 5 earthquake in Hollister, CA an entire day in advance! This is evidence that my invention will work!

Bob Davis

Build An Infrared Detector

by Fred Blechman

The entire IR Detector is smaller than the standard nine-volt battery that powers it.

Build this simple circuit to test infrared remote controls. It uses only 10 common electronic parts you can get at any RadioShack store or order on-line. No printed circuit board is required and a common nine-volt battery will last "forever."

They are everywhere!

You'll find them in living rooms, family rooms, breakfast rooms, dining rooms, and bedrooms. They may even be found in some bathrooms! What? Infrared (IR) remote controls.

IR remote controls are used to perform various functions for television sets, cable boxes, video cassette recorders, hi-fi audio sets, lights, ceiling fans, and a growing number of other electronic devices.

Increasingly, pressing various buttons on these remote controls are the ONLY way to perform some functions on these devices. Manufacturers, in order to save the cost and installation of switches and potentiometers, simply program a chip in the device to respond to infrared commands. For example, try to find a CONTRAST or BRIGHTNESS control on your modern TV set. Or clock controls on a VCR. These, and many other settings, have been relegated to the IR remote control designed for the specific device.

For the most common functions — ON/OFF, Channel, Volume, Play, Record, Fast Forward, Rewind, and others — a "universal" remote control can operate several different devices.

But what do you do when the control doesn't seem to work? Is there a battery problem? Is a button making contact when pressed? Is the control defective? Since you cannot see the infrared beam produced by these controls, how can you tell if it is working properly?

This dilemma is solved with the "IR Detector" which you can build

from only 10 common parts.

Older Remote Control Methods


Probably the first use for remote control in the home came with changing television channels. At first there were mechanical methods, using a cable connected to the TV tuner. You physically pushed a button or turned a knob to change channels. Various means were devised to turn off the sound ("commercial killers"), some as simple as a flashlight beam shining on a photocell in the speaker circuit. However, daylight and sunlight could also trigger the sound off.

Pretty soon ultrasound — sound waves above human hearing — were used. This drove some animals wild, and was subject to interference from other sound sources.

But some years ago, infrared signals came into use. To prevent interference with other light sources, the infrared light was pulsed at around 38,000 cycles per second (KHz), with different pulse codes for each function. Therefore, infrared receivers could be "tuned" to about 38 KHz and decode the specific pulse train for each function. Infrared emitters and detectors coupled with programmed integrated circuits made all this practical.


Infrared Energy

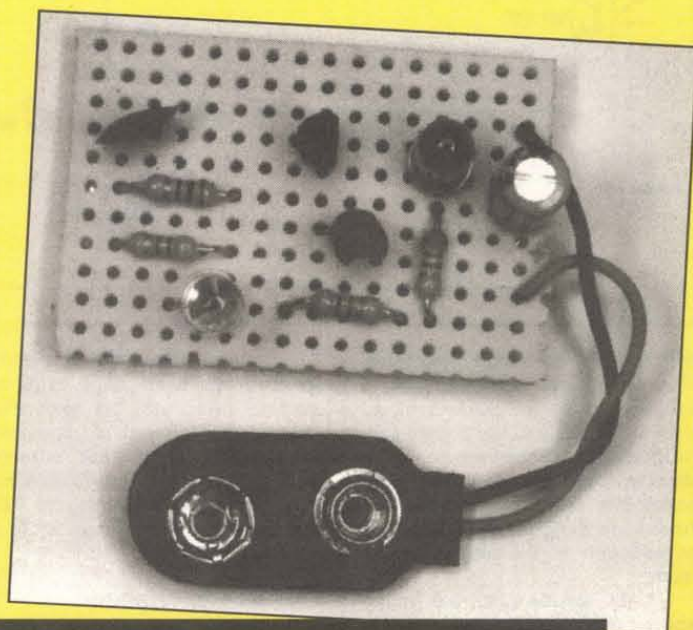Infrared energy consists of light rays that are below the



Only 10 electronic parts, a small piece of perforated board, and a battery snap connector are used to build the IR Detector.

All wiring is underneath the board, and is point-to-point, using component leads.

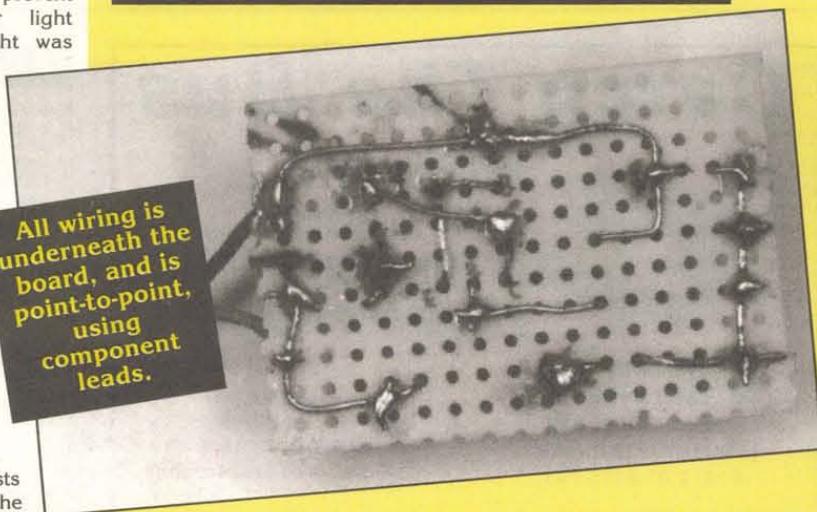

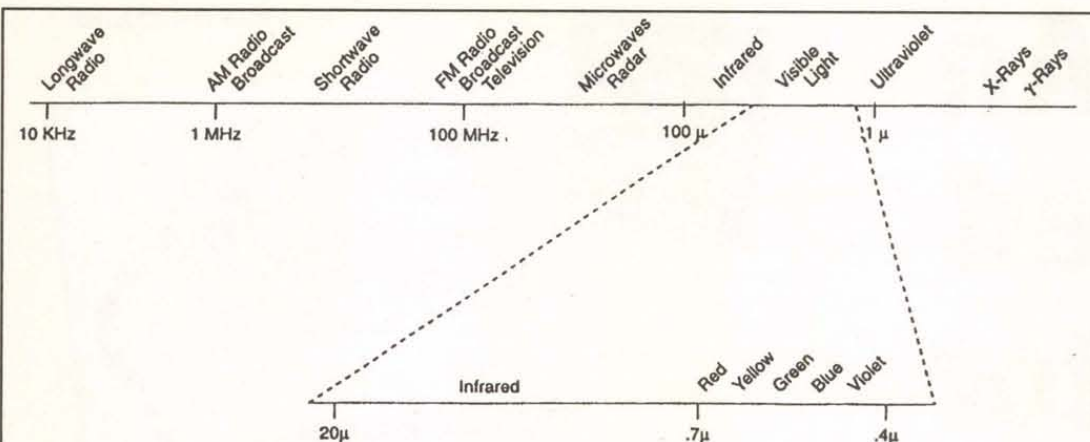


Figure 1 — Frequency spectrum from longwave radio to gamma rays, with expanded view of infrared to ultraviolet.

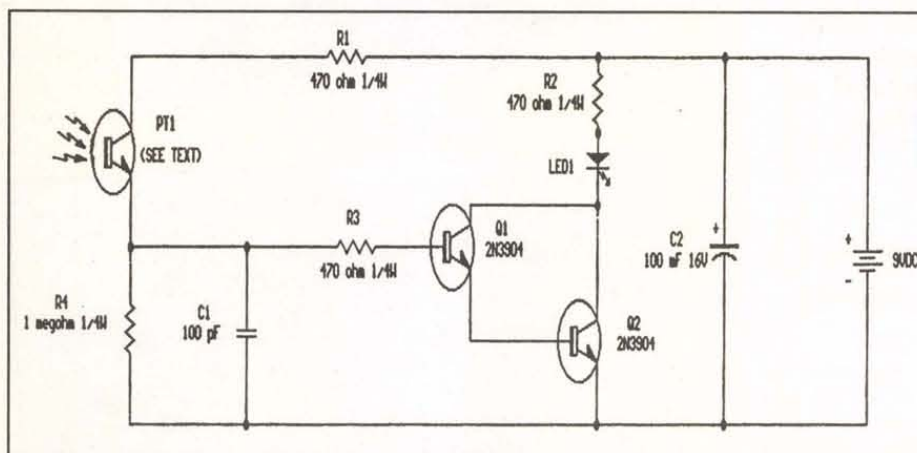


Figure 2 — IR Detector Schematic.

red end of the visible spectrum. The wavelength of these rays is longer than that of visible light, so they are invisible to the human eye. Infrared rays, however, can be detected by means of special photodetector semiconductors that have been designed to be sensitive to radiation in the infrared spectrum.

Light wavelengths are much shorter than typical broadcast and microwaves, and longer than x-rays. The higher the frequency, the shorter the wavelength.

Figure 1 shows the frequency spectrum from longwave radio to gamma rays, with an expanded view of the infrared to ultraviolet wavelengths. Note that infrared wavelengths are approximately from 0.7 micrometers to 20 micrometers. (A micrometer is a millionth of a meter.)

Circuit Description

The schematic of the IR Detector is shown in Figure 2. Powered by a simple, standard nine-

volt battery, essentially no current flows through this circuit unless PT1, an infrared phototransistor, "sees" light. Since visible light also contains invisible infrared light, daylight and even artificial light will cause some current to flow in the circuit.

Basically, the circuit consists of the phototransistor, when responding to light, biasing a pair of transistors in a Darlington amplifier circuit so that current can flow through the light-emitting diode, making it glow.

PT1 has no base lead, since infrared light is intended to provide base bias. When there is no infrared light, little or no current flows from the collector to the emitter (the arrowhead symbol) of PT1. This means there is no bias voltage to the base of transistor Q1, so it does not conduct, also depriving transistor Q2 of bias, so Q2 does not conduct. Therefore, essentially no current flows through resistor R2 or light-emitting diode LED1. The circuit is dormant.

However, as soon as any light — especially infrared light — is allowed to fall on the transparent shell of PT1, the current from collector to emitter increases; the brighter the light, the greater the current. Resistor R1 limits the current through PT1, as well as providing a voltage-divider with resistor R4.

As current flows through PT1, a positive voltage is created at the intersection of resistors R3, R4, and capacitor C1. This voltage biases Q1 into conduction, which allows Q2 to conduct, thus providing a path for current to flow through current-limiting resistor R2 and LED1, which then glows.


Since the infrared signals this detector is expected to receive are operating in a pulse mode with a basic signal frequency of about 38 KHz, capacitor C1 acts to filter out the signal and pulses, and electrolytic capacitor C2 stabilizes the power.

Construction

Before you can build the IR Detector you need to get the parts, some of which are so common you probably already have them. Nothing is critical in the layout or components of this circuit except for the infrared phototransistor, PT1.

Q1 and Q2 may be just about any NPN general-purpose silicon transistor, such as the 2N2222. The resistors, capacitors, and LED can be slightly different sizes or values. You might even find other phototransistors would work in this circuit.

Catch The Bus

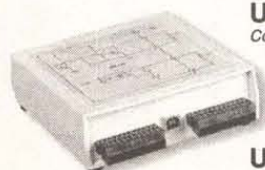

USB Relay Module
Control 8 to 16 "form C", 1 Amp relays

USB Opto Module
8 to 32 opto-isolated Inputs and Outputs

USB Digital Module
Industry standard 50 pin interface

USB Temperature Module
Measures temperature over multiple remote sensors

J-Works, Inc
12328 Gladstone St., Unit 4
Sylmar, CA 91342
(818) 361-0787 Voice
(818) 270-2413 Fax

Visit our Web site for free
information on all our products
<http://www.j-works.com>
E-mail sales@j-works.com

PROGRAMMABLE SOLENOID

- Low cost motion control
- Wide operating voltage (12 - 28)
- Onboard programming and parameter storage
- Self-contained electronics

Rotary (PPS-1)



\$95.00 + \$5 s/h

Linear (PPS-2)



\$145.00 + \$5 s/h

- Simple connection only 3 wires: Power, Ground, and CMD signal
- Long Life: Brushless ball bearing stepper
- Constant current Torque/Force

The Picard Programmable Solenoid (PPS) delivers the motion capability of a sophisticated stepper motor system with the simplicity of a solenoid. This eliminates the non-linear and erratic banging motion of a traditional solenoid. The electronics of the PPS allows the user to program and store the desired motion profile using the simple user interface. The innovative PPS gives programmability to the motion of a solenoid without the expense of a costly motion control system.

PICARD INDUSTRIES

Specializing in Miniature Smart Motors and Sensors

4960 Quaker Hill Road
Albion, New York 14411

Phone/Fax 716-589-0358

Email: jcamdep4@iinc.com
www.picard-industries.com

cuit, but I've found that RadioShack carries an acceptable unit, as well as all the other parts, as identified in the Parts List.

This simple circuit can be built on a perforated board, using point-to-point wiring. If a perforated board with holes spaced 0.1-inch apart is used, Figure 3 (enlarged view for readability) shows the perforated board holes and the parts layout I used for the IR Detector. Although the computer drawing program has distorted the shape of some of the components, the locations are accurate. Figure 3A shows the actual size.

Figure 4 (enlarged view for readability) shows the parts on the top of the board and the wiring paths UNDERNEATH the board. This wiring is accomplished by bending the component leads under the board and connecting them as shown. The only place it is necessary to jump one wire over another is, as shown, between the emitter of Q1 and the base of Q2.

Use care in soldering and orienting the parts properly. If you use the 2N3904 or 2N2222 transistors, when looking at the flat face of the transistor with the leads at the bottom, the leads are emitter, base, and collector (EBC) from left to right.

Note, however, that many types of general-purpose transistors will work in this circuit, and some have pinouts that are CBE. As a matter of fact, the unit shown in the photos — for you eagle-eyed readers — has such transistors, and they face in the OPPOSITE direction than the 2N3904 or 2N2222 would face. See Figure 3 for the correct orientation.

As for the phototransistor, the collector, which connects to R1, is the lead closest to the flat side of the clear plastic dome. The LED cathode, which connects to the collectors of both Q1 and Q2, is closest to the flat spot on the clear plastic dome. Most electrolytic capacitors identify the negative lead. The disc capacitor and resistors have no polarity.

Testing

Testing the unit is simple. All you really need is an infrared remote control and a nine-volt battery. It is not necessary to use an alkaline battery — zinc-carbon will do nicely. But only leave the battery connected when you will be using the IR Detector, since there is current flowing when any light (which usually contains some infrared) falls on the phototransistor.

It is necessary to test the unit in very dim light. This unit is VERY sensitive, and the LED will glow with any appreciable ambient light once the battery is connected. You can place a black tubular "hood"

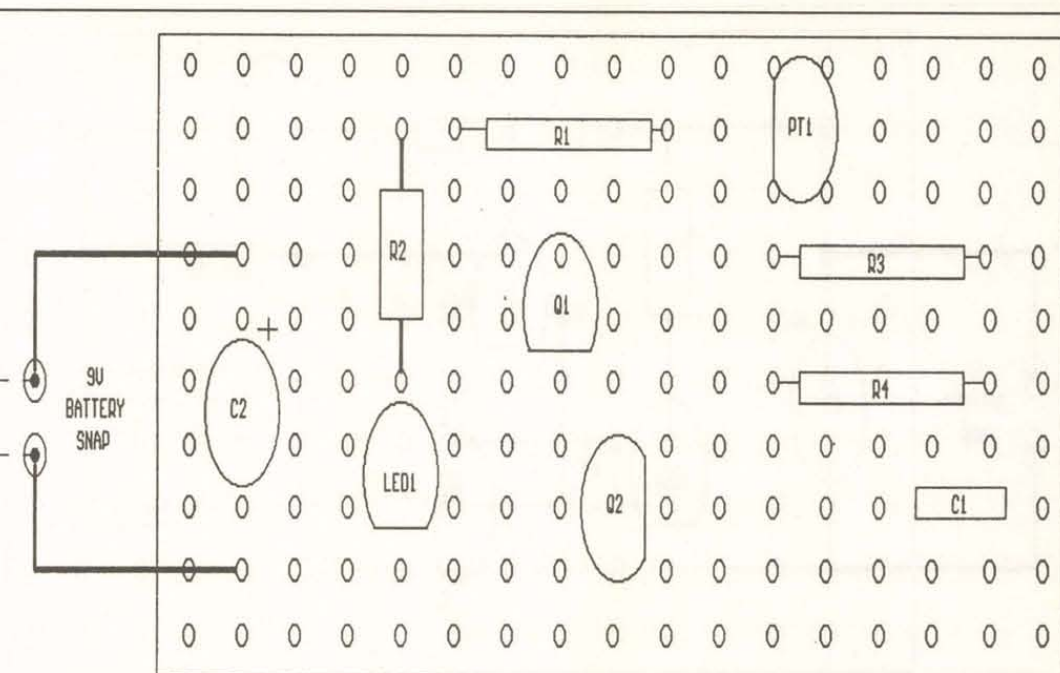


Figure 3 — Enlarged view of parts layout on 0.1-inch spaced perforated board.

(such as can be made from a large soda straw wrapped with black tape to make it opaque) over the phototransistor to block light from the sides of the Detector. Or, you could mount the entire unit in a black box with just a small hole for access to the phototransistor.

With the battery connected, and the IR Detector in dim light, LED1 should not be glowing — or glowing dimly. Now, from six inches to a foot away, point the active end of the IR remote control directly at

the photodetector, press ANY button, and LED1 should either flash once, or glow with a pulsing light. Some remote buttons only put out a single short burst, others continue to pulse.

Test all the buttons on the remote to see if the Detector picks up their signal. Some buttons, especially on older units, have developed high contact resistance internally, and some buttons may have to be

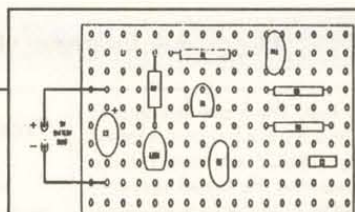



Figure 3A — Actual size parts layout.

pushed hard to make enough contact to emit a signal.

Also be aware that the selection of the device on universal

PCB LAYOUT Software For Windows - FREE

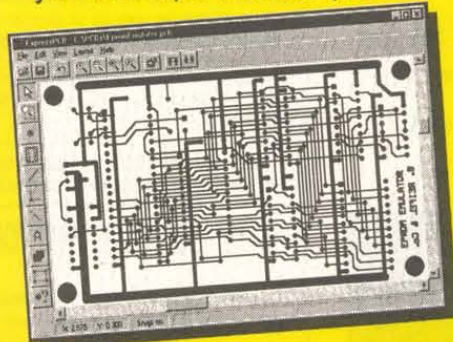- 1 Download our board layout software
- 2 Design your 2 sided plated-through PCB
- 3 Send us your layout over the Internet
- 4 In 2-3 business days, UPS delivers your boards, often under \$100



www.expresspcb.com

World Passing You By?

Are you interested in Microprocessors & Embedded Control Systems? If not you should be! Look around, just about everything these days has an embedded microprocessor in it. TVs, cars, radios, traffic lights & even toys have embedded computers controlling their actions. The PRIMER Trainer is the tool that can not only teach you how these devices operate but give you the opportunity to program these types of systems yourself. Examples & exercises in the Self Instruction manual take you from writing simple programs to controlling motors. Start out in Machine language, then move on to Assembly, & then continue on with optional C, Basic, or Forth Compilers. So don't be left behind; this is information you need to know!

Examples Include:

- Measuring Temperature
- Using a Photocell to Detect Light Levels
- Making a Waveform Generator
- Constructing a Capacitance Meter
- Motor Speed Control Using Back EMF
- Interfacing and Controlling Stepper Motors
- Scanning Keypads and Writing to LCD/LED Displays
- Bus Interfacing an 8255 PPI
- Using the PRIMER as an EPROM Programmer
- DTMF Autodialer & Remote Controller (New!)

The PRIMER is only \$119.95 in kit form. The PRIMER Assembled & Tested is \$169.95. This trainer can be used stand alone via the keypad and display or connected to a PC with the optional upgrade (\$49.95). The Upgrade includes: an RS232 serial port & cable, 32K of battery backed RAM, & Assembler/Editor software. Please add \$5.00 for shipping within the U.S. Picture shown with upgrade option and optional heavy-duty keypad (\$29.95) installed. Satisfaction guaranteed.

EMAC, inc.
11 EMAC WAY, CARBONDALE, IL 62901
618-529-4525 Fax 457-0110 BBS 529-5708
World Wide Web: <http://www.emacinc.com>

1985 - 1998
OVER
12
YEARS
OF SERVICE

Write In 180 on Reader Service Card.

MAY 2000 73



DEALER DIRECTORY

The dealers listed below carry the latest issue of Nuts & Volts, for your convenience.

ALABAMA

Little Professor Book Center
2717 S. 18th St.
Birmingham 35209
RT Systems
8207 Stephanie Dr.
Huntsville 35802

ARIZONA

Batteries Plus #330
3014 N. Dobson
Chandler 85224
Batteries Plus #334
1155 S. Power Rd. #108
Mesa 85206
Batteries Plus #331
2404 E. Bell Rd.
Phoenix 85032
Batteries Plus #332
3415 W. Glendale Ave. Ste. 4
Phoenix 85051
Batteries Plus #333
1829 E. Southern Ave.
Tempe 85282

Elliott Electronic Supply
1251 S. Tyndall Ave.
Tucson 85713

Power Quality, Inc.
642 E. 39th Pl. Ste. 5
Yuma 85365

Tower Records
3 E. 9th St.
Tempe 85281

AUSTRALIA

DonTronics
P.O. Box 595
29 Ellesmere Cres.
Tullamarine 3043
www.dontronics.com

CALIFORNIA

Abletronics
9155 Archibald Ave. Unit E
Cucamonga 91730
Advanced Computer Products, Inc.
1310 "B" E. Edinger Ave.
Santa Ana 92705
All Electronics
905 S. Vermont Ave.
Los Angeles 90006

14928 Oxnard St.
Van Nuys 91411

Alltronics
2300-D Zanker Rd.
San Jose 95131

Centerfold International
716 N. Fairfax Ave.
Los Angeles 90046

Del Amo Books & News
3758 Sepulveda Blvd.
Torrance 90505

Electro Mavin
2985 E. Harcourt St.
Rancho Dominguez 90221

Ford Electronics
8431 Commonwealth Ave.
Buena Park 90621

Harding Way News
113 W. Harding Way
Stockton 95204

Harold's Newsstand
524 Geary St.
San Francisco 94102

Hi-Fi Doctor
1814 E. Ball Rd.
Anaheim 92805

HSC Electronic Supply
4837 Amber Ln.
Sacramento 95841

3500 Ryder St.
Santa Clara 95051

5681 Redwood Dr.
Rohnert Park 94928

Hyatt Electronic Surplus
371 N. Johnson Ave.
El Cajon 92020

JK Electronics
6395 Westminster Ave.
Westminster 92683

Len's Electronic Parts
14410 E. Valley Blvd.
Industry 91746

Len's Electronic Parts
108 W. 25th St. #D
National City 91950

Lion Electronic Labs
4948 E. Townsend Ave.
Fresno 93727

Op Amp Technical Books
1033 N. Sycamore Ave.
Los Angeles 90038

Panorama Electronics
8761 Van Nuys Blvd.
Panorama City 91402

Sandy's Electronics Supply, Inc.
20655 Soledad Cyn. Rd. #15
Santa Clarita 91351

Sav-On Electronics
13225 Harbor Blvd.
Garden Grove 92643

Sierra Madre Newsstand
55 N. Baldwin Ave.
Sierra Madre 91024

The Red Barn
Hwy. 299
Bieber 96009

Tower Books
211 Main St.
Chico 95928

7840 Macy Plaza Dr.
Citrus Heights 95610

1280 E. Willow Pass Rd.
Concord 94520

630 San Antonio Rd.
Mountain View 94040

1600 Broadway
Sacramento 95818

2538 Watt Ave.
Sacramento 95821

Tower Records/Video
220 N. Beach Blvd.
Anaheim 92801

5703 Christie Ave.
Emeryville 94608

6310 E. Pacific Coast Hwy.
Long Beach 90803

3205 20th Ave.
San Francisco 94132

2525 Jones St.
San Francisco 94133

871 Blossom Hill Rd.
San Jose 95123

Video Electronics
3829 University Ave.
San Diego 92105

CANADA

Cody Books Ltd.
139-3000 Lougheed Hwy.
Westwood Mall
Port Coquitlam, BC V3B 1C5
Com-West Radio Systems Ltd.
8206 Ontario St. #100
Vancouver, BC V5X 3E3
Emma Marion Ltd.
2677 E. Hastings St.
Vancouver, BC V5K 1Z5
Muir Communications Ltd.
3214 Douglas St.
Victoria, BC V8Z 3K6

COLORADO

Centennial Electronics, Inc.
2324 E. Bijou
Colorado Springs 80909
Lloyd's Radio & Electronic, Inc.
220 W. Harry St.
Wichita 67213

CONNECTICUT

Archway News
64 Bank St.
New Milford 06776

DELAWARE

Newark Newsstand
70 E. Main St.
Newark 19711

DISTRICT OF COLUMBIA

Tower Records
2000 Pennsylvania Ave.
Washington 20006

FLORIDA

Alfa Electronic Supply
6444 Pembroke Rd.
Miramar 33023

Astro Too
6949 W. Nasa Blvd.
West Melbourne 32904
Clarks Out of Town News
303 S. Andrews Ave.
Fort Lauderdale 33301

Mike's Electronic Distributing Co.
1001 N.W. 52nd St.
Fort Lauderdale 33309

Skycraft Parts & Surplus, Inc.
2245 W. Fairbanks
Winter Park 32789

Sunny's At Sunset, Inc.
8260 Sunset Strip
Sunrise 33322

Tower Records
3400 Around Lenox Dr. N.E.
Atlanta 30326

GEORGIA

Tower Records
3400 Around Lenox Dr. N.E.
Atlanta 30326

HAWAII

SolarWorks!
525 Lotus Blossom Ln.
Ocean View 96737

Tower Records
4211 Waialae Ave.
Honolulu 96816
611 Keeaumoku
Honolulu 96814

IDAHO

The Current Source
5159 Glenwood
Boise 83714

ILLINOIS

Tower Records/Video/Books
383 W. Army Trail Rd.
Bloomington 61008
2301 N. Clark St. #200
Chicago 60614

1209 E. Golf Rd.
Schaumburg 60173

INDIANA

Harbortown Sales
108 Park 32 W. Dr.
Noblesville 46060

KANSAS

Hollywood At Home
9063 Metcalf Ave.
Overland Park 66212
Lloyd's Radio & Electronic, Inc.
220 W. Harry St.
Wichita 67213

LOUISIANA

Lakeside News
3323 Severn Ave.
Metairie 70002

MARYLAND

Tower Records/Video
2566 Solomons Island Rd.
Annapolis 21401

1601 Rockville Pike #210
Rockville 20852

MASSACHUSETTS

Newsbreak, Inc.
579 G.A.R. Hwy. Rt. 6
Swansea 02777

MICHIGAN

Little Professors Book Center
22174 Michigan Ave.
Dearborn 48124
Purchase Radio Supply, Inc.
327 E. Hoover Ave.
Ann Arbor 48104

MINNESOTA

Radio City, Inc.
2633 County Road 1
Mounds View 55112

MISSOURI

Accurate Instruments
11201 E. 24 Hwy.
Independence 64054
Electronics Exchange
8644 St. Charles Rock Rd.
St. Louis 63114

NEVADA

Amateur Electronic Supply
1072 N. Rancho Dr.
Las Vegas 89106

Less Buster's Electronics
2930 N. Las Vegas Blvd.
VSTG-22
North Las Vegas 89030

Radio World
1656 Nevada Hwy.
Boulder City 89005

Tower Records/Video
4580 W. Sahara Ave.
Las Vegas 89102

6450 S. Virginia
Reno 89511

NEW YORK

All Phase Video Security, Inc.
70 Cain Dr.
Brentwood 11717
Computer Warehouse
137 E. Bridge St.
Oswego 13126
Ham Central
3 Neptune Rd.
Poughkeepsie 12601
Hirsch Sales Corporation
219 California Dr.
Williamsport 14221
Tower Records/Video
105 Old Country Rd.
Carle Place 11514

350-370 Route 110
Huntington 11746

1961 Broadway
New York 10023

383 Lafayette St.
New York 10003

OHIO

Bank News
4025 Clark Ave.
Cleveland 44109

Compustuff
241 Great Oaks Trl.
Wadsworth 44281

Footsteps
4925 Jackson Rd. Store #58
Toledo 43613

Hosfelt Electronics, Inc.
2700 Sunset Blvd.
Steubenville 43952

Keyways, Inc.
204 S. 3rd St.
Miami 33134

Leo's Book Shop
333 N. Superior St.
Toledo 43604

Powermaxx, Inc.
1587 U.S. Route 68 N.
Xenia 45385

OKLAHOMA

Steve's Books & Magazines
2612 S. Harvard
Tulsa 74114

Taylor News & Books
133 W. Main, Ste. 102
Oklahoma City 73102

OREGON

News & Smokes
2295 W. Main St.
Medford 97501

Norvac Electronics
7940 S.W. Nimbus Ave. Bldg. 8
Beaverton 97005

960 Conger
Eugene 97402

1545 N. Commercial N.E.
Salem 97303

Tower Books
1307 N.E. 102nd Ave.
Portland 97220

PENNSYLVANIA

Bedford St. News
308 Bedford St.
Johnstown 15901

Tower Books
425 South St.
Philadelphia 19147
Tower Records
340 W. Dekalb Pike
King of Prussia 19406

TENNESSEE

Tower Books
2404 W. End Ave.
Nashville 37203
Tower Records
504 Opry Mills Dr.
Nashville 37214

TEXAS

BDI News, Inc.
809 Pierce
Houston 77002

Electronic Parts Outlet
3753-B Fondren Rd.
Houston 77063

Mouser Electronics
958 N. Main St.
Mansfield 76063

Tanner Electronics
1301 W. Bellline #105
Carrollton 75006

Tower Records
2403 Guadalupe St.
Austin 78705

Tower Records/Video/Books
4110 W. Ox Rd. #12124
Fairfax 22033

1601 Willow Lawn Dr.
Richmond 23230
8389 E. Leesburg Pike
Vienna 22182

WASHINGTON

A-B-C Communications, Inc.
17541 15th Ave. N.E.
Seattle 98155

Service Request
3304 W. Rowan Ave.
Spokane 99205

Supertronix
16550 W. Valley Hwy.
Seattle 98188

Tower Books
10635 N.E. 8th St.
Bellevue 98004

20 Mercer St.
Seattle 98109

WISCONSIN
Amateur Electronic Supply, Inc.
5710 W. Good Hope Rd.
Milwaukee 53223

Greenfield News & Hobby
6815 W. Layton Ave.
Greenfield 53220

Cudahy News & Hobby Ctr.
4758 Packard Ave.
Cudahy 53110

WYOMING
Western Test Systems
2701 Westland Ct. #B
Cheyenne 82001

by Joseph J. Carr

Open Channel

Dealing With AC Power Line EMI

Radio reception is many things to many people, but all forms of radio activity boil down to one thing: the signal-to-noise ratio (SNR) game.

There is always some basic noise level caused by a combination of natural and man-made sources.

Figure 1 shows the fundamental situation in all radio reception problems. There is always some basic noise level caused by a combination of natural and man-made sources.

As society becomes more and more electrical, the man-made component becomes huge. But the actual amplitude of the noise signal is not nearly as important as the SNR, i.e., the relative strengths of the desired signal and the noise.

You will find that listening to weak signals on some frequencies, especially in the AM band or the "tropical" MW/SW bands, is made difficult or impossible by hash from the AC power lines.

Figure 1 shows four situations. There is a basic RMS noise level, which is labeled 0 dB. Four signals are present (A, B, C, and D). Signal A is clearly below the average noise level, so will not be heard. Some very skilled operators might be able to hear signal B because it sticks up just above the 0 dB noise level, but for most people it will remain a "... was that a signal or my imagination?" situation.

When the signal gets a little higher, say 3 dB above the noise floor, it becomes readable with a bit of discomfort and

annoyance. For most situations, "comfortable" listening requires an SNR of 10 dB, i.e., a signal that is considerably above the 0 dB noise floor.

Keep in mind that the absolute amplitudes of the noise and signals are not as important as the signal-to-noise ratio. Of course, as you start digging for weaker and weaker signals, the amplitude of the noise signal must be suppressed in order to get a usable SNR.

AC Power Line Noise


Perhaps the most common form of man-made noise afflicting radio and televi-

sion reception is from the AC power lines. When I first moved into my present home, my HF shortwave receivers were all but useless because of the high "hash" level of noise present.

The problem turned out to be a collection of "dimmer" switches that replaced the ordinary light switches. Those devices use a duty-cycle SCR circuit to lower the power level of incandescent lights, and the truncated waveform they produce is rich in harmonics (well into the HF bands!).

I replaced all six dimmers with conventional switches, and the noise level dropped enough decibels to be really impressive.

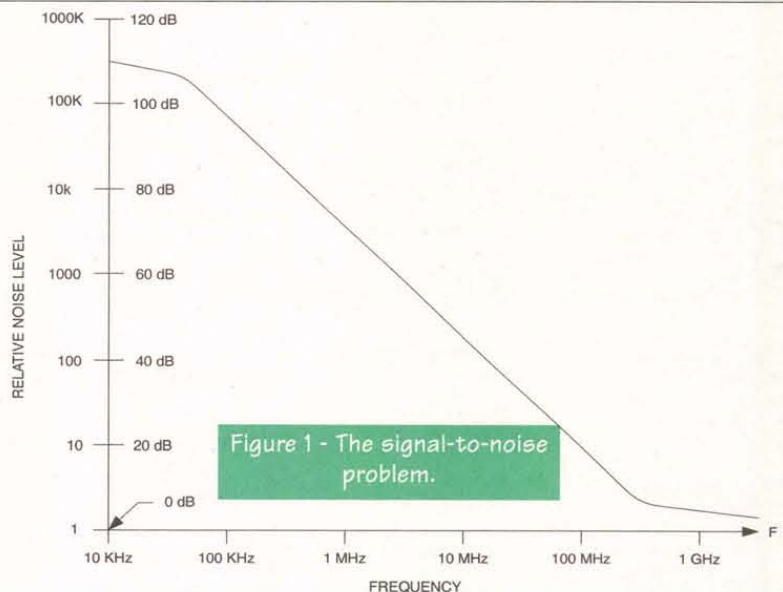Over the years, I have found a large number of non-radio sources of interference to AM broadcast band (BCB), FM BCB, high fidelity audio, and television equipment in addition to shortwave and scanner receivers.



BOB SAVED THE WORLD TODAY...



Bob, Super-Tech extraordinaire, has a secret weapon. This amazing device allowed him to locate and replace all 34 bad electrolytic capacitors in this TV in less than 30 minutes. So instead of throwing this TV into the local landfill and adding more pollution, Bob's secret weapon enabled him to give the World a brighter future. Impressed his manager and his customer too. Bob's secret weapon? The world's best in-circuit cap checker, the *CapAnalyzer 88A* by EDS.

Smart techs know that to be productive you need to find defective components quickly and accurately. That's why General Motors, Matsushita Industrial, Sears Service, Pioneer Electronics, Panasonic Authorized Service, NASA/Kennedy Space Center, Time/Warner Communications, NBC TV and thousands more independent service technicians have chosen the *CapAnalyzer 88A* over all of the other capacitor checkers. Check www.eds-inc.com/88users.html for actual *CapAnalyzer* users' comments as they compare their *CapAnalyzer* to the "wizards" and "z-meters" they already own. They all prefer the *CapAnalyzer* because it checks electrolytic capacitors, *in-circuit*, with 100% accuracy. No unsoldering to check out-of-circuit, no mistaking a shorted or leaky cap as good, as other "ESR" meters do, no guessing about whether a value is good or bad. With our exclusive three-color comparison chart right on the front panel, auto-discharge, multi-beep alert, and one-handed tweezer test probe, even your pet monkey could find defective caps in that problem PWM power supply, TV, monitor or VCR in a few seconds.

...NOW IT'S YOUR TURN.

So get your own *CapAnalyzer 88A*. It's only \$179. With our exclusive 60-day satisfaction-or-money-back guarantee, you risk nothing. Prepare to be amazed: your only problem will be running out of work as you take care of all of those "dogs" that you've been sitting on. We're **Electronic Design Specialists**. We make test equipment designed to make you money. Available at your distributor now, or call 561-487-6103. Check out www.eds-inc.com for the details.

Included are: electric motors, a microwave oven, loose tie-wires on AC mains transformers (on the pole outside the home), and electrical space heaters.

Many different forms of appliances were indicted, including (oddly enough) a dishwasher that has an SCR controller inside to turn it on and off, a garbage disposal unit under the complainant's sink, a garage door opener, and the most raucous door bell-chime I've ever heard.

Two forms of noise seem to be present. First, the harmonics of the 60 Hz power line waveform are present throughout the spectrum. If the power line produced a pure sine wave, then this would not occur. But the power line waveform is distorted, so has harmonics. Because the power levels are so high, the significant harmonics form a "comb" spectrum every 60 Hz high into the radio frequency spectrum. Second, any item that sparks (e.g., electric motors) will produce static signals much like lightning does.

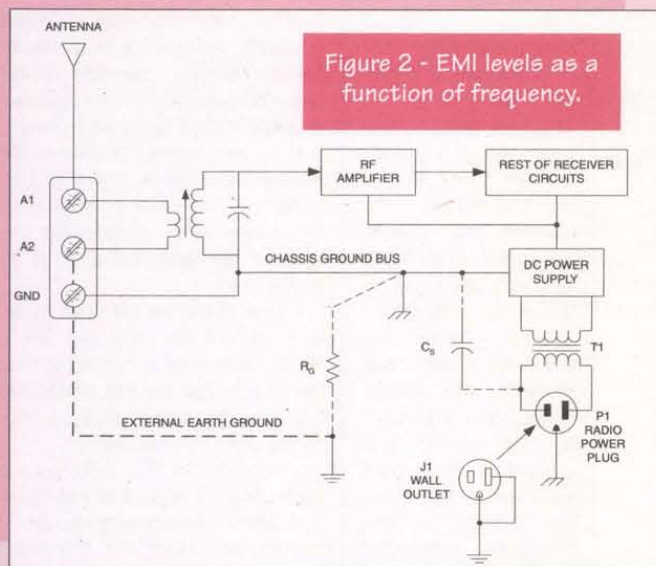


Figure 2 - EMI levels as a function of frequency.

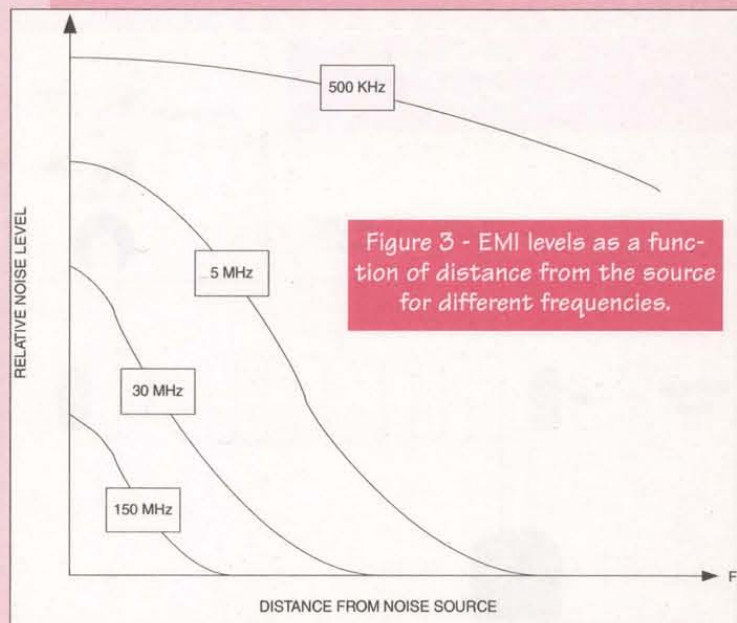


Figure 3 - EMI levels as a function of distance from the source for different frequencies.

Figures 2 and 3 characterize this noise emission in two different ways. Figure 2 shows the relative level in arbitrary units versus frequency. Typical intensity levels might run from a fraction of a microvolt per meter ($\mu\text{V}/\text{m}$) to nearly 500,000 $\mu\text{V}/\text{m}$, depending on the source (which is why Figure 2 is in "arbitrary voltage units").

Note in Figure 2 that the distribution of signal intensity is uneven throughout the spectrum. The levels will be extremely high in the VLF portion of the spectrum, and fall off almost evenly up into the UHF spectrum. If you tune into the AM BCB or medium wave bands (up to about 7 MHz or so), then you will note a high

hash level. It is more intense on the lower frequencies, but annoying well into the shortwave bands.

Figure 3 characterizes the 60 Hz power line EMI problem as a function of distance from the noise source. Again, because the actual values of the distance and signal strength vary with your particular situation, relative units are used in Figure 3. Note that the 500 KHz (bottom of AM BCB) strength does not fall off nearly as fast as the higher frequency components.

This fact leads us to a strategy for finding the source. Start at the lowest frequency, and tune to higher frequencies until the noise just begins to disappear. You want it

audible, but barely so. Walk, drive, or turn your antenna in first one direction and then the other to see in which direction an increase is noted. Go in that direction until the signal is again strong.

At that point, pick another higher frequency at which the noise is just barely audible and repeat the process. This process is repeated at successively higher frequencies until you are very, very close to the source. At that time, start looking for likely culprits.

Once the source is located, it can be dealt with by one or more methods. If it is the power line (loose connections raise hob with reception!), then contact the power company and ask them to fix it ... demand it if they balk. If it turns out to be an appliance, then either the appliance needs repair or some sort of filtering is needed.

Unless it is your appliance, I recommend having a professional technician actually do the work. If you do the necessary work on your neighbor's appliance, then you will be "married to it" if anything at all goes wrong even in the distant future (some people will use any excuse to get someone else to pick up their tab).

Things To Do At Your Receiver

You may or may not be able to do something about

the noise source (which is always the best solution!), but there are some things that you can do about the problem at your receiver. Let's take a look at some of those problems.

First, let's look at one of the sources of the problem. Let's assume

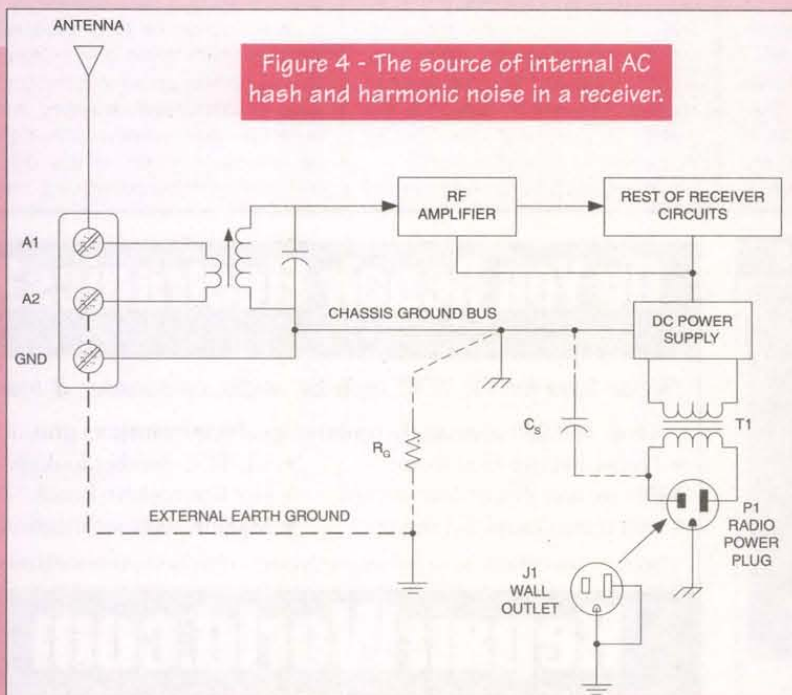


Figure 4 - The source of internal AC hash and harmonic noise in a receiver.

2 Great Books by Joseph Carr




\$29.95

SECRETS OF RF CIRCUIT DESIGN

From one of today's most respected electronics authors comes this pragmatic, intermediate-level guide to designing, building, and testing all types of radio frequency circuits. Filled with functional projects that demonstrate the principles of RF circuits, this revision of a bestseller also provides a handy parts list and sources of components.

PRACTICAL ANTENNA HANDBOOK

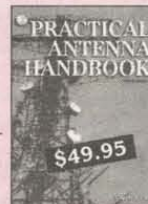The most popular book on antennas ever written, widely known as "the antenna builder's bible."




\$49.95

This Third Edition is a work for anyone with an interest in antennas, from the newest of novices to the most experienced engineer. This empowering book gives you all kinds of projects and material that explains why what you did works.

As a paid subscriber to *Nuts & Volts*, you'll receive **10% off** the list price!!
(See ad on page 46 for ordering details and other titles currently available.)

Dealing With AC Power Line EMI

Figure 5 - Simple power line EMI choke using a ferrite rod.

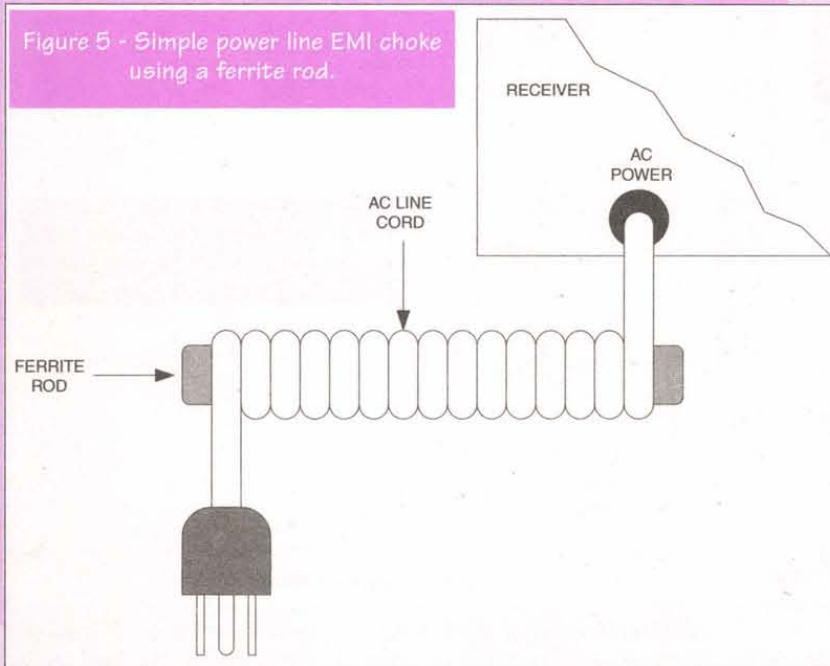

a generic shortwave or scanner receiver with a three terminal antenna connector (Figure 4).

The antenna terminals include A1 and A2, which lead to the antenna input circuitry, and GND which is the chassis ground (and zero-signal common). There is normally a coupling path between the AC power wiring and the chassis of the receiver.

The capacitance between the AC power wiring and the chassis forms a path, represented by capacitor CS in Figure 4. This means that noise-laden AC is passed onto the receiver chassis, where it can be coupled into the RF amplifier and the rest of the circuit due to

common ground impedances (RG).

Assume first that the external antenna is attached to A1, and that both A2 and GND are not connected. In this circumstance, the ground loop voltage developed across RG is seen as a valid signal by the receiver. The radio chassis is eventually grounded to earth, but through the power connectors (P1 and J1), to the power line ground at the service entrance to the building. Because of wire resistance, connector blade resistance, and the fact that your service entrance ground might be poor for RF, the value of RG can get quite high.

The solution: add an external ground connection to the receiver the way the instruction manual told you to do — strap A2 to GND, and then through a heavy conductor to a proper ground rod buried in the earth. That may eliminate a large part of the power line hash without further work.

AC Power Cord Chokes

Now let's assume that the receiver is properly grounded, but that a high noise level still exists. It may be that the RF components are riding into the receiver via the power lines, and then radiated into the sensitive circuitry. The way to deal with this problem is to eliminate them before they enter the receiver cabinet.

It is often hard to diagnose this

problem, but if the receiver is battery powered, the problem is easier. My favorite general coverage receiver has a DC connector on the rear panel to allow it to be operated from a 12-volt battery source. Disconnect the receiver from the AC power line and operate it from the battery. If the noise level drops appreciably, then suspect the entrance path is the power cord.

One of the easiest ways to deal with the problem is to use only as much power cord as needed to reach the outlet. Coil the rest of the cord into a six-inch diameter loop as close to the chassis as possible.

A species of "RF choke" can be built using the approaches of Figures 5, 6, and 7. The simplest approach is to wrap the receiver's AC power cord around a ferrite rod (Figure 5) as close as possible to the power entrance on the rear panel of the receiver.

Any of several ferrite rods can be used, but the Amidon Associates R61-050-750 is appropriate. Wrap as many turns as will fit onto the 7.5-inch rod, and then secure them with tape (they have a tendency to come unwrapped). There should be enough cord left to plug into the outlet, but even if you have to use an extension cord, wrap as many turns as will fit onto the rod.

A superior approach to the same idea is to use a toroid core as shown in Figure 6. Use one of the larger toroid cores (the kind used for making kilowatt and up BALUN transformers) so that the relatively thick coaxial cable can be accommodated. Wrap as many turns of the power cord as possible onto the toroid core. Note one thing well, however, with the power plug connected this might be impossible to do. If you don't want to modify the power cord, then

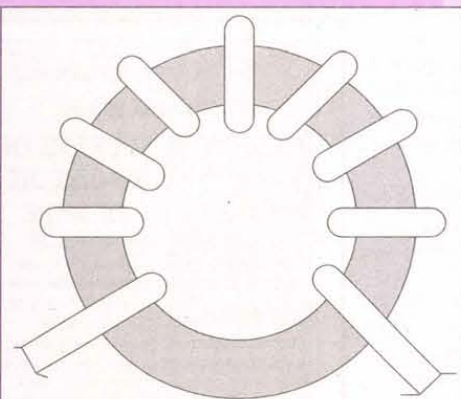


Figure 6 - EMI choke using toroid core.

EZ-EP DEVICE PROGRAMMER - \$169.95

Check Web!! -- www.m2l.com

Fast - Programs 27C010 in 23 seconds

Portable - Connects to PC Parallel Port

Versatile - Programs 2716-080 plus EE and flash (28, 29) to 32 pins

Inexpensive - Best for less than \$200

● Correct implementation of manufacturer specified algorithms for fast, reliable programming.

● Easy to use menu based software has binary editor, read, verify, copy, etc. Free updates via bbs or web.

● Full over current detection on all device power supplies protects against bad chips and reverse insertion.


● Broad support for additional devices using adapters listed below.

Available Adapters

EP-PIC1 (16C5x, 61, 62x, 71, 84)	\$49.95
EP-PIC64 (16C62, 5, 72-4)	\$39.95
EP-PIC12 (12C500)	\$39.95
EP-PIC17 (17C4x)	\$49.95
EP-51 (8751, C51)	\$39.95
EP-11E (88HC11 E/A)	\$59.95
EP-11D (88HC711D3)	\$39.95
EP-16 (16b1 EPROMs)	\$49.95
EP-Z8 (Z8E02, 3, 4, 6, 7, 8)	\$39.95
EP-SEE2 (93x, 24x, 25x, 85x)	\$39.95
EP-750 (750C750, 1.2)	\$59.95
EP-PEEL (IC22x10, 16x)	\$59.95
EP-1051 (89C1051, 2051)	\$39.95
EP-PLCC (PLCC EPROMs)	\$49.95
EP-SOIC (SOIC EPROMs)	\$49.95
EP-TSOP (TSOP EPROMs)	\$59.95

Many Other Adapters Available

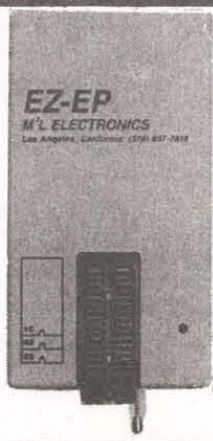M²L Electronics
970/259-0555
Fax: 970/259-0777
250 CR 218
Durango, CO 81301
CO orders please add 7% sales tax.
<http://www.m2l.com>



Do You Repair Electronics?

For only \$7.95 a month, you'll receive a wealth of information:

Repair data for TV, VCR, monitor, audio, camcorder, & more.

Over 100,000 constantly updated problem/solutions plus...

- TechsChat live chat room.
- UL/FCC number lookup.
- Private user discussion forums.
- Hot tips bulletin board.
- Automated email list server.
- Manufacturer information.


To access RepairWorld, direct your internet browser to <http://www.repairworld.com>

RepairWorld.com

Electronix Corp. 1 Herald Sq. Fairborn, OH 45324 (937) 878-9878

Dealing With AC Power Line EMI

Figure 7 - EMI choke fashioned by clamping ferrite blocks onto the AC power cord.

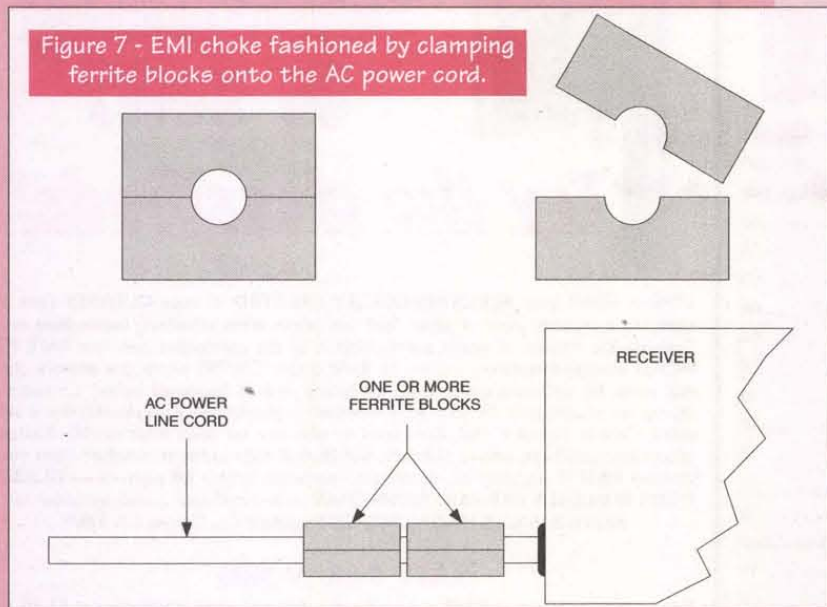

you might want to either use the ferrite rod approach, or a ferrite block as shown in Figure 7.

Two views of a ferrite split block are shown in Figure 7A. These blocks come in two halves, each of which is notched such that when put together they form a hole. The application of these blocks is shown in Figure 7B. The blocks are clamped onto the receiver's AC power cord as close as possible to the rear panel of the receiver. Once the blocks are clamped together, they can be secured with tape. In some cases, only a single split block is needed but, in severe cases, two or more split blocks may be added in series. These blocks act like RF chokes, so will snub the higher frequency components while not affecting the 60 Hz AC power.

Ferrite split blocks are available in a number of sizes and shapes to accommodate a number of different forms of cord. Some are flat to allow clamping onto computer ribbon cable, in case a digital device such as a computer is the noise culprit.

AC Power Line Filters

Another way to deal with the

problem of EMI carried into the receiver on the AC power line is shown in Figure 8. The idea here is to use a low-pass filter in series with the AC power line so that the RF components are snubbed out, leaving the 60 Hz to pass unimpeded.

Several filter designs are popular. Some of them use separate pi-section filters in both the hot and neutral lines, while the other uses a pair of coupled coils in a common mode arrangement such as Figure 8.

This design uses a ferrite rod such as the Amidon Associates R61-050-750 to form L1A and L1B. The turns are wrapped onto the cord with a size of AC power wire appropriate to the size. For the maximum power levels, use #12 AWG solid wire intended for AC power wiring applications. The turns for L1A and L1B are wound in the bifilar manner (Figure 9).

The capacitors used in the filter of Figures 8 and 9 should be rated for 125 volt AC service. Ordinary 600 volt or 1,000 volt capacitors are not suitable because they are not rated for constant application of 125 volts AC power line voltage. A typical rating for C1 through C4 is 0.0047 μ F to 0.05 μ F (0.01 μ F typical) at a volt-

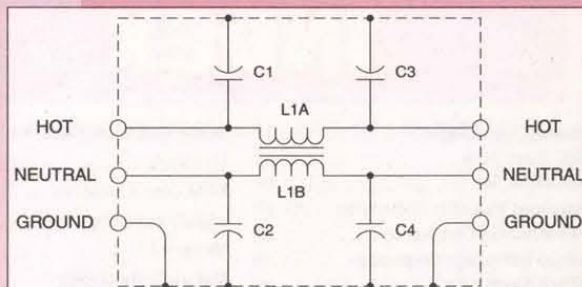


Figure 8 - AC power line EMI L-C low-pass filter (see warning in text).

age rating of 125 volts AC, and 1,400 volts DC (tested to at least 2,800 volts DC). Electronic parts catalogs are a good guide to suitable types of capacitor.

SAFETY NOTE:

Working with AC power lines is dangerous. Accidental contact with the line can kill you. Improper wiring or a bad selection of components, or improper construction methods can create both electric shock and fire hazards. It is highly recommended by the author, editor, and publisher that you select a commercially made, UL approved AC line RF filter made for this purpose rather than homebrew your own. If your receiver uses the same kind of square AC power receptacle that is found on computers, then you can find a replacement for the chassis receptacle that has an EMI filter built in.

Special Case

About five years ago, I had a problem at my house that created AC power line hash in great quantities, and also affected my AC power service. For several years, I listened to an evening shortwave broadcast in the 5-6 MHz band, and on Saturday night to WSM in Nashville (650 KHz AM) ... good country music is where you find it (There! I'm out of the closet ... a Carr's a hillbilly music fan!).

The hash started one summer, and continued into the fall, ruining many evenings of listening. It had an

average signal strength of S7 to S8 on my Drake R-8 receiver S-meter. I suspected that the problem was on the power pole,

but the local power company could not find any problem.

That winter, a strange thing started happening with the lights in my home. Whenever any heavy current drain (refrigerator, freezer, furnace) would turn on, the lights would nearly double in brightness. Notice anything odd? Lights should dim, not get brighter, when a heavy load is turned on.

This time, the power company did find a problem. The technician came to the Carr house about 10 o'clock one evening, when the effect was nearly constant, and found that the neutral line connection to my AC power line service was loose.

The fellow raised his "cherry picker" basket up to the power pole, at the point where my service tap was located, and used the largest crimping tool I've ever seen to repair the connection. The lights went back to normal, which was a blessing.

But the next evening, I noticed that the S-8 noise level was down somewhere near decimal dust ... the hash was gone. I suspect that the loose connection was causing the hash all along. Indeed, the power company could have fixed the service problem earlier if they had taken the EMI problem seriously. The hash was merely a prodromal symptom of the service problem!

Conclusion

AC power line harmonics and spark hash can create havoc with radio reception. But with the methods discussed in this article, you will be able to overcome many of these problems. **NV**

Connections ...

I can be reached by snail mail at P.O. Box 1099, Falls Church, VA 22041, or via E-Mail at CARRJJ@AOL.COM.


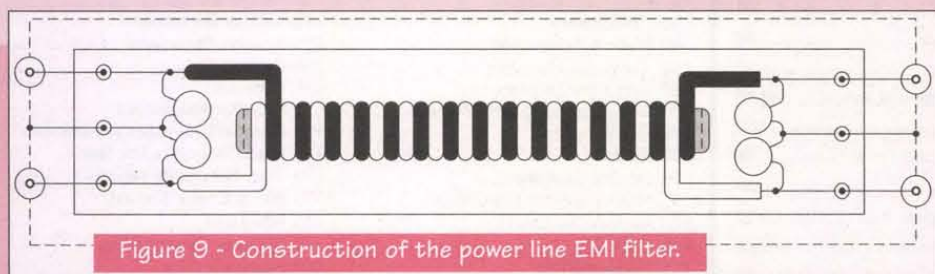


Figure 9 - Construction of the power line EMI filter.

ADVERTISER INDEX

Abacom Technologies	17	Metric Equipment Sales, Inc.	74
ABC Electronics	60	Metrologic	35
ActiveWire, Inc.	68	MFM Communications	68
Advanced Transdata Corporation	32, 60	microEngineering Labs	66
All Electronics Corporation	61	Micromint	15
Allison Technology Corporation	19	Midland Technologies	68
Alltech Electronics	19	Modular Concepts	68
Alltronics	57	Motron	54
Andromeda Research	26	Mr. Nicd	84
Antique Radio Classified	69	MSC Electronics	69
AST Global Electronics	16	MVS	56
Autotime Corp.	68	Netcom	11
AWC	36	Optoelectronics	4
Baylin Publications	51	OS Systems	65
Bilcoan Corp.	69	Parallax, Inc.	7, Back Cover
Blitz Technology	39	Patco Services	51
Bright Future	66	PCB Express, Inc.	69
C & S Sales, Inc.	62	Picard Industries	72
C and H Sales Company	39	Pioneer Hill Software	58
Carl's Electronics	82	Polaris Industries	27
Chicago Circuits Corporation	67	Power Quality, Inc.	70
Circuit Etching Technics	14	Prairie Digital, Inc.	69
Circuit Specialists, Inc.	94	Pulsar, Inc.	48
Communications Surplus	69	Quality Kits	68
Corporate Systems Center	2, 95	Ramsey Electronics, Inc.	41
Cunard Associates	59	Ray's Robotic Racers	8
Decade Engineering	14	R.E. Smith	68
Demar Electronics	68	Resources Un-Ltd.	20-21
DESIGN CONTEST	6	Roger's Systems Specialist	12
DesignNotes.com	56	Saelig Company	64
Digital Products Company	68	Sam's Electronics	60
DMD Systems Recovery, Inc.	69	Scott Edwards Electronics, Inc.	33
Earth Computer Technologies	44	Seabird Technical	69
ECD	68	Securetek	70
EDS	69, 76	Sheffield Electronics	69
E.H. Yost & Co.	84	Shreve Systems	55
Electro Mavin	56	Skycraft Parts & Surplus, Inc.	59
Electronix Corp.	78	Square 1 Electronics	9
EMAC, Inc.	73	SuperCircuits	33
ExpressPCB	73	Surplus Traders	70
Foss Warehouse Distributors	69	Techniks, Inc.	68
Fusion Electronic Security	43	Technological Arts	67
Gateway Electronics, Inc.	40	Telulex, Inc.	18
General Device Instruments	70	Test Equipment Connection	10
GeneSys Resources, Inc.	69	Test Equipment Plus	44
Globaltech Distributors	68	The End Connection	69
Halted Specialties Co.	3	The RF Connection	58
HobbyTron	17	Timeless Products	42
H.T. Orr Computer Supplies	42	Ultralink	68
Information Unlimited	31	Unicorn Electronics	58
Inkjet Southwest	38	USI Corp.	59
Intronics, Inc.	13	V&V Mach. & Equipment, Inc.	69-70
Intuitive Circuits LLC	65	Velleman	37
Junkware.com	68	Vesta Technology, Inc.	68
Jam RF	74	Visitect, Inc.	39
J-Works, Inc.	72	Weeder Technologies	56
Lakeview Research	59	Western Test Systems	28-29
La Paz Electronics International	70	ZMI Engineering	63
Lemos International Co., Inc.	67		
Levy Latham	15		
Linear Systems	13		
Lynxmotion, Inc.	26		
M2L Electronics	78		
Matco, Inc.	68-69		
Max Research	35		
MEM Electronics	19		
Meredith Instruments	42		

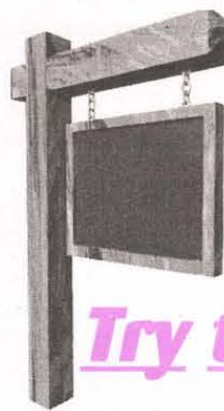

Got
something
to sell?

Try the classifieds!!

TYPE or PRINT your **ELECTRONICALLY RELATED** ad copy **CLEARLY** (not all caps) on a separate piece of paper. Spell out words when submitting handwritten copy. Calculate the number of words and multiply it by the appropriate rate (see **RATE PER WORD** section). Include any charges for bold and/or CAPPED words, any artwork costs that would be applicable, and/or costs for boxing your ad (explained below). Choose the appropriate classification for your ad(s) to appear in (see below). If no classification is indicated, it will be placed in Misc. Electronics or wherever we deem most suitable. **Enclose your name, address, phone number, and Nuts & Volts account number from your mailing label** (if available) for identification purposes. Include full payment — **CLASSIFIEDS RUN ON A PRE-PAID BASIS ONLY** — and mail your completed order to:
NUTS & VOLTS MAGAZINE, 430 Princeland Ct., Corona, CA 92879.

RATE PER WORD

The ad rate for **current PAID subscribers** is **60¢** per word. All others pay **\$1.20** per word. There is a **\$9.00** minimum charge per ad per insertion.

WORDS IN BOLD AND/OR ALL CAPS

Words to be set in **bold** or **CAPS** are each **10¢** extra **PER WORD**. **BOLD CAPS** are **20¢** extra per word. The first two words of each ad are bold capped at no charge. Indicate bold words by underlining. Words normally written in caps (e.g., IBM) and accepted abbreviations such as VAC or MHz are **NOT** charged as all cap words. Use a two-letter abbreviation for states.

PHOTOS, DRAWINGS, AND BOXES

A photo or drawing may be run at the top of your classified ad for an additional **\$10.00** (1" depth max.) for camera-ready art. No wording is allowed in this area. To **BOX** your ad, include an additional **\$50.00** for copy-only ads, or **\$75.00** for ads with art or photos.

FAXING IN AD COPY

You may fax in ad copy or changes before the closing date (5:00pm on the **5th**) at 909-371-3052 using MasterCard or Visa. Include credit card expiration date, the name that appears on the card, a daytime phone number, and your **Nuts & Volts** account number. Ads without credit card information will not be listed as received until payment is received in full. **WE DO NOT CALL OR FAX BACK VERIFICATION OR QUOTES OF FAXED-IN ADS.** For verification of faxed-in ads, please call 909-371-8497.

DEADLINE

Prepaid ads received by 5:00pm on the **closing date (5th of the month)** will appear in the following month's issue. Ads postmarked through the **5th**, but received after the closing date, will be placed in the next available issue. No cancellations or changes after the 5th. Cancellations and changes must be submitted in writing.

IMPORTANT INFORMATION

All classified ads are running copy only. No special positioning, centering, dot leaders, extra space, etc. is allowed. All advertising in **Nuts & Volts** is limited to **electronically related items ONLY**. All ads are subject to approval by the publisher. We reserve the right to reject or edit any ad submitted. We do not take ad copy or changes over the phone. We do not bill for classified ads. Repeat ads or ads run in multiple classifications within the same issue are allowed. Paid subscribers may run ads at the **60¢** rate only through their subscription expiration date. **NO REFUNDS.** Credit only. No credit for typesetting errors will be issued unless you clearly print or type your ad copy.

Choose a category for your ad from the classifications listed below.

10. Ham Gear For Sale	120. Components
20. Ham Gear Wanted	125. Microcontrollers
30. CB/Scanners	130. Antique Electronics
40. Music & Accessories	135. Aviation Electronics
50. Computer Hardware	140. Publications
60. Computer Software	145. Robotics
70. Computer Equipment Wanted	150. Plans/Kits/Schematics
80. Test Equipment	155. Manuals/Schematics Wanted
85. Security	160. Misc. Electronics For Sale
90. Satellite Equipment	170. Misc. Electronics Wanted
95. Military Surplus Electronics	175. BBS & Online Services
100. Audio/Video/Lasers	180. Education
110. Cable TV	190. Business Opportunities
115. Telephone/Fax	200. Repairs/Service

Product/Category INDEX

Find what
you need
FAST

AMATEUR RADIO & TV

Alltronics	57
Communications Surplus	69
Decade Engineering	14
Gateway Electronics, Inc.	40
HobbyTron	17
Lemos International Co., Inc.	67
Modular Concepts	68
Motron	54
Ramsey Electronics, Inc.	41
The RF Connection	58

ASSEMBLY SERVICES

Bilcon Corp.	69
--------------	----

BATTERIES/CHARGERS

Cunard Associates	59
E.H. Yost & Co.	84
Globaltech Distributors	68
Mr. NiCd	84
Power Quality, Inc.	70

BUSINESS OPPORTUNITIES

BUYING ELECTRONIC SURPLUS

ABC Electronics	60
Alltech Electronics	19
C and H Sales Company	39
Earth Computer Technologies	44
Metric Equipment Sales, Inc.	74
Roger's Systems Specialist	12
Skycraft Parts & Surplus, Inc.	59

CABLE TV

Foss Warehouse Distributors	69
Sam's Electronics	60
Timeless Products	42

CB/SCANNERS

USI Corp.	59
-----------	----

CCD CAMERAS/VIDEO

Circuit Specialists, Inc.	94
Decade Engineering	14
Fusion Electronic Security	43
Matco, Inc.	68-69
MSC Electronics	69
Polaris Industries	27
Ramsey Electronics, Inc.	41
Resources Un-Ltd.	20-21
Seabird Technical	69
Securetek	70
SuperCircuits	33
USI Corp.	59

CIRCUIT BOARDS

Chicago Circuits Corporations	67
Cunard Associates	59
ECD	68
ExpressPCB	73
PCB Express, Inc.	69
Pulsar, Inc.	48
V&V Mach. & Equipment, Inc.	69-70

COMPONENTS

Chicago Circuits Corporation	67
Circuit Etching Technics	14

Communications Surplus	69
ECD	68
La Paz Electronics International	70
Linear Systems	13
OS Systems	65
Pulsar, Inc.	48
Skycraft Parts & Surplus, Inc.	59
Unicom Electronics	58
Visitec, Inc.	39

COMPUTER

Hardware

ActiveWire, Inc.	68
Allison Technology Corp.	19
Alltech Electronics	19
Corporate Systems Center	2, 95
DMD Systems Recovery, Inc.	69
Earth Computer Technologies	44
Electro Mavin	56
General Device Instruments	70
Halted Specialties Co.	3
La Paz Electronics International	70
MEM Electronics	19
Roger's Systems Specialist	12
Shreve Systems	55
Techniks, Inc.	68
The End Connection	69
Ultralink	68

Software

Bright Future	66
Electronix Corp.	78
Globaltech Distributors	68
Pioneer Hill Software	58

Microcontrollers / I/O Boards

Autotime Corp.	68
AWC	36
EMAC, Inc.	73
Intuitive Circuits LLC	65
Junkware.com	68
La Paz Electronics International	70
Micromint	15
MVS	56
OS Systems	65
Parallax, Inc.	7, Back Cover
Prairie Digital, Inc.	69
Ray's Robotic Racers	8
R.E. Smith	68
Scott Edwards Electronics, Inc.	33
Square 1 Electronics	9
Technological Arts	67
Ultralink	68
Vesta Technology, Inc.	68

Printers/Printer Supplies

H.T. Orr Computer Supplies	42
Inkjet Southwest	38

DESIGN/ENGINEERING SERVICES

Chicago Circuits Corporation	67
DesignNotes.com	56
ExpressPCB	73
Midland Technologies	68
Prairie Digital, Inc.	69
Pulsar, Inc.	48
V&V Mach. & Equipment, Inc.	69-70

EDUCATION

Bright Future	66
EMAC, Inc.	73
HobbyTron	17
Metrologic	35

EVENTS/SHOWS

DESIGN CONTEST	6
----------------	---

KITS

Alltronics	57
------------	----

C & S Sales, Inc.	62
Digital Products Company	68
Earth Computer Technologies	44
EMAC, Inc.	73
Gateway Electronics, Inc.	40
HobbyTron	17
Information Unlimited	31
Inkjet Southwest	38
Modular Concepts	68
Quality Kits	68
Ramsey Electronics, Inc.	41
Scott Edwards Electronics, Inc.	33
USI Corp.	59
Velleman	37
Weeder Technologies	56

LASERS

Information Unlimited	31
Meredith Instruments	42
Metrologic	35
Resources Un-Ltd.	20-21
Unicom Electronics	58

MISC./SURPLUS

All Electronics Corporation	61
Alltech Electronics	19
C and H Sales Company	39
Communications Surplus	69
Demar Electronics	68
Halted Specialties Co.	3
Jam RF	74
Levy Latham	15
Linear Systems	13
MFM Communications	68
PCB Express, Inc.	69
Picard Industries	72
Power Quality, Inc.	70
Resources Un-Ltd.	20-21
Shreve Systems	55
Skycraft Parts & Surplus, Inc.	59
Surplus Traders	70
Unicom Electronics	58
Visitec, Inc.	39
Weeder Technologies	56

PROGRAMMERS

Advanced Transdata Corporation	32, 60
Andromeda Research	26
General Device Instruments	70
Intronics, Inc.	13
M2L Electronics	78
microEngineering Labs	66

PUBLICATIONS

Antique Radio Classified	69
Lakeview Research	59
Max Research	35
Netcom	11
Sheffield Electronics	69
Square 1 Electronics	9

RF TRANSMITTERS/ RECEIVERS

Abacom Technologies	17
Matco, Inc.	68-69
Securetek	70

ROBOTICS

Lemos International Co., Inc.	67
Lynxmotion, Inc.	26
Modular Concepts	68
OS Systems	65
SuperCircuits	33

SATELLITE

Baylin Publications	51
---------------------	----

SECURITY

Bitz Technology	39
Decade Engineering	14
Fusion Electronic Security	43
Information Unlimited	31
Lemos International Co., Inc.	67
Matco, Inc.	68-69
Motron	54
MSC Electronics	69
Polaris Industries	27
Securetek	70
SuperCircuits	33
Visitec, Inc.	39

SOLAR EQUIPMENT

GeneSys Resources, Inc.	69
-------------------------	----

STEPPER MOTORS

Alltronics	57
------------	----

TELEPHONE

Carl's Electronics	82
Digital Products Company	68
Globaltech Distributors	68
Telulex, Inc.	18
Weeder Technologies	56
ZMI Engineering	63

TEST EQUIPMENT

ABC Electronics	60
Allison Technology Corp.	19
AST Global Electronics	16
C & S Sales, Inc.	62
C and H Sales Company	39
Circuit Specialists, Inc.	94
DesignNotes.com	56
Digital Products Company	68
DMD Systems Recovery, Inc.	69
EDS	69, 76
Intronics, Inc.	13
J-Works, Inc.	72
Levy Latham	15
Metric Equipment Sales, Inc.	74
Optoelectronics	4
Pioneer Hill Software	58
Power Quality, Inc.	70
Prairie Digital, Inc.	69
Saelig Company	64
Seabird Technical	69
Telulex, Inc.	18
Test Equipment Connection	10
Test Equipment Plus	44
Western Test Systems	28-29
ZMI Engineering	63

TOOLS


Advanced Transdata Corporation	32, 60
C & S Sales, Inc.	62
Patco Services	51
The RF Connection	58

WIRE/CABLE & CONNECTORS

Roger's Systems Specialist	12
The RF Connection	58

DIGITAL ALARM CLOCK

by Brian Beard

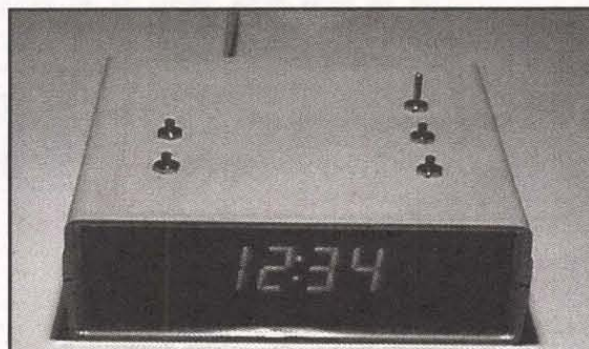

Alarm clocks have become so common and cheap that it's hard to find a construction project for a complete alarm clock. This article is just that, a complete alarm clock, from the power supply to the case. While it's probably no cheaper than one from K-Mart, unlike most construction projects, at least when it's built, your spouse won't need to ask, "What is it?"

Hardware

The alarm clock has all the basic features found in most commercial digital alarm clocks. The block diagram shown in Figure 1 breaks the alarm clock into four parts: power supply, alarm, microcontroller, and display. There are actually two circuit boards that make up the alarm clock: the DB1 display board and the CK2 circuit board which includes the power supply, alarm, and microcontroller.

Display Board

Display Controller

The DB1 is based on the MCI4489, U1 in Figure 2. Motorola calls this chip a "Multi-Character LED Display/Lamp Driver." It's quite a versatile device, capable of driving a five-

digit common-cathode display plus decimals, 25 discrete LEDs, or just about any combination in between. In the DB1 circuit, it drives four seven-segment digits plus colon while the fifth digit is used to drive four annunciator LEDs. It does this by multiplexing segments "a" through "h" among the five digits, or five banks as they are called on the IC's data sheet. The MCI4489's internal oscillator guarantees a minimum refresh rate of 700 Hz, more than fast enough to insure a flicker-free display. Other than the LED display, the only external component required is a single resistor (R1) to set the maximum segment drive current. Drive currents can go as high as 30 mA per segment, but thermal considerations become critical at high drive currents. The DB1 is designed for a peak segment drive current of approximately 12 mA.

LED is lit whenever the alarm is enabled. This will tell you at a glance whether you have the alarm turned on.

Main Circuit Board

Power Supply Circuitry

Now we return to the main circuit board, the CK2. Figure 4 shows the power supply. The alarm clock can be powered by a 9VDC wall transformer or a 9V backup battery. D1 and D2 isolate the 9VDC wall transformer and backup battery from each other. All the alarm clock circuitry runs on +5V, which is provided by U1, a 78S40 universal switching regulator subsystem. This high-efficiency step-down regulator keeps heat build-up at a minimum and extends the battery life when main power is off.

The regulator is designed to deliver +5V at up to 100mA of current. For normal operating conditions, the alarm clock draws between 30 and 50 mA, depending on the number of active segments in the display. When running off the battery in low power mode, the current drain drops to 5 mA. For an excellent tutorial on designing with the 78S40, see Motorola application note AN920.

Two comparators from the LM339 (U2) quad-comparator comprise the voltage monitoring portion of the power supply circuitry. U2A monitors the battery voltage and U2B monitors the 9VDC input at J2. Both comparators use a resistive divider to drop the monitored voltage close to the 1.2V reference from the 78S40. The total resistance of the divider for the battery (R4+R7) is high so the current drain on the battery is low.

In fact, as long as external voltage is applied at J2, reverse leakage current through D2 keeps the net drain on the battery near zero. Because the battery voltage drops slowly, hysteresis is required to prevent erratic switching. The output of U2A (BAT_OK) switches from high to low

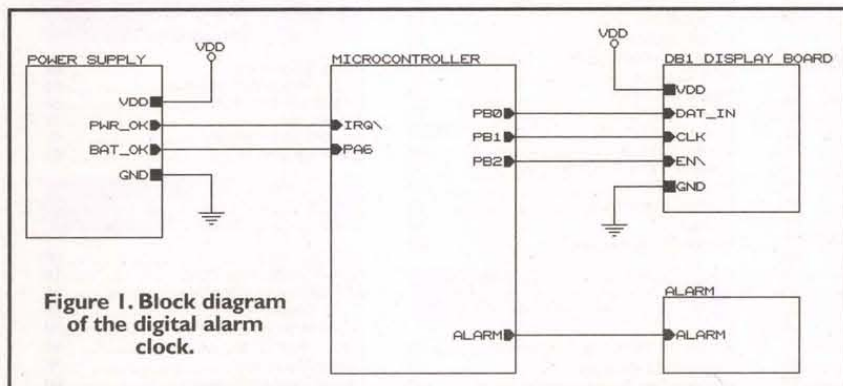


Figure 1. Block diagram of the digital alarm clock.

HOT NEW PRODUCTS!!!



Phone Manager - Reverse Caller ID. Now you can keep track of outgoing numbers. Records length, time and date of call. Keep track of the children, the wife, or the phone company. Easy hookup via phone jack.

New low price \$49.95

Phone and Internet Voice Changer - This device is new to the market and provides realistic sounding voices. It allows you to interface directly to your phone jack, or computer via patch cord and mic.

Intro price \$129.95



Order directly from our website at www.electronickits.com
We also have over 200 Electronic Plans, Kits and Spy Products
Carl's Electronics Inc. sales@electronickits.com

The MCI4489 has an eight-bit configuration register and a 24-bit data register. The configuration register controls blanking and how each digit's data is decoded.

Communication with the MCI4489 is via a synchronous serial interface. For details on the serial interface or programming the MCI4489, consult the part's data sheet which can be downloaded from the Motorola web site, <http://www.mot-sps.com/>.

LED Display

The actual display is a CC56-21EWA multiplexed LED module. This is a high efficiency red, four digit, common cathode, seven-segment display with 0.56" high digits.

The four discrete LEDs on the DB1 are annunciators. Their functions are shown in Figure 3. The upper-left

as the battery voltage falls below 6.5V, and back high as battery voltage rises above 7.4V. Hysteresis is also required on U2B because most DC wall transformers have large filter capacitors that cause the 9VDC to decay slowly when the main AC supply fails. The output of U2B (PWR_OK) switches from high to low as the voltage at J2 falls below 8.2V, and back high as the voltage rises above 8.6V.

Microcontroller

The MC68HC705J1A microcontroller, or J1A for short, is shown as U3 in Figure 5. The J1A has 1240 bytes of one-time-programmable (OTP) EPROM, 64 bytes of RAM, a 15-stage multifunction timer with prescaler, and 14 bidirectional I/O lines. For complete data on the MC68HC705J1A, see the technical data manual available from Motorola. The crystal frequency is 4.1943MHz which is 2^{22} . The J1A operates at half the crystal frequency or 2.097152MHz. Since the operating frequency is an exact binary number, the multifunction timer can produce real-time interrupts at integer Hertz rates. The alarm clock software sets the multifunction timer for 16 real-time interrupts per second.

The J1A's I/O lines are divided among two ports, port-A has eight lines (PA0-PA7) and port-B has six (PB0-PB5). On the CK2, PA0-PA5 are all used as inputs with pullup resistors. PA6 is an input for the BAT_OK signal. PA7 is an output and controls the alarm. PB0-PB2 are outputs to the display board.

Controls



PA5 connects to a jumper used to select a 12- or 24-hour display format. Grounding PA5 (closing jumper JP24) will give you the 24-hour display. The function is controlled by a jumper, because most people have a definite preference, but a switch can be con-

nected if you want to switch between display modes. If you hardwire the 24-hour display, the AM/PM indicators on the display board will never come on, so you need not even install them.

PA0-PA4 connect to user operated switches. Each switch connects to a pair of pads on the CK2 circuit board. The five pairs are marked SW1-SW5. The TIME_SET, ALARM_SET, HOURS_SET, and MINUTES_SET switches are all normally-open push buttons. The TIME_SET button allows you to set the time of day. Pressing it together with the HOURS_SET button will increment the hours digit until one of the buttons is released. Similarly, the TIME_SET and MINUTES_SET buttons will increment the minutes digit. When you press and hold the ALARM_SET button, the display will show the alarm time. While the alarm time is displayed, it can be changed with the HOURS_SET and MINUTES_SET buttons.

The ALARM_ENABLE switch can be an SPST toggle, or an SPST toggle in parallel with a normally-open push button. The ALARM_ENABLE switch connects to PA4 via SW5. When the switch is open, PA4 is high and the alarm enabled LED will be lit. At the first second when the time of day equals the alarm time, the J1A will turn on the alarm circuit if PA4 is high.

To turn off the alarm, PA4 only needs to be grounded for 1/16 of a second. A momentary push button works fine to turn the alarm off, but as soon as you release the button, the alarm is enabled for the next day. On the other hand, if the ALARM_ENABLE switch is a toggle, the alarm will turn off as soon as the switch is toggled closed, but you have to remember to toggle it back open to re-enable the alarm. However, the toggle will allow you to turn the alarm off for the weekend whereas the push button will not.

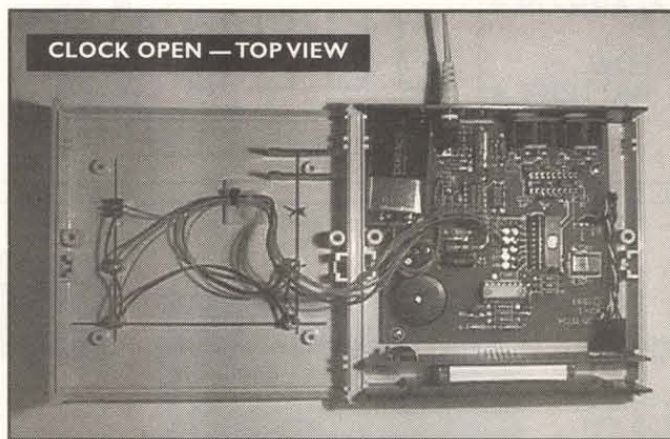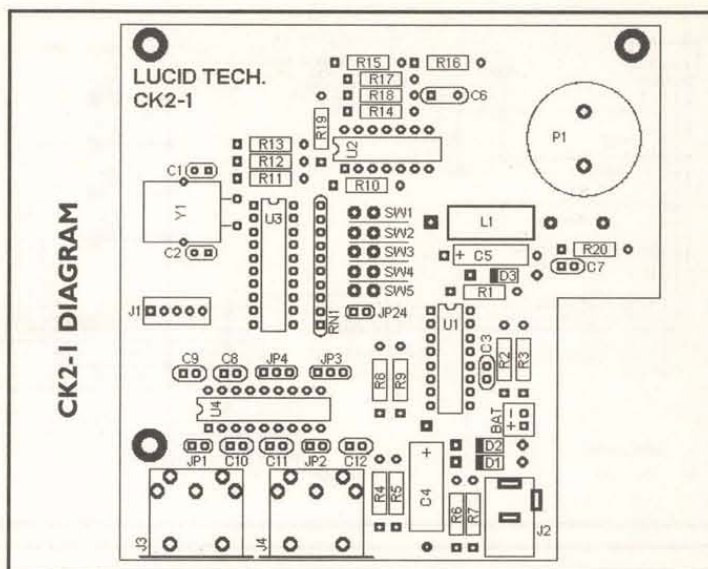

Alarm Circuitry

The alarm circuitry is shown in Figure 6. Comparator U2C is configured as a gated oscillator. The gate signal (ALARM) is the PA7 I/O line from the J1A. When PA7 is high, the output of U2C is a 1300 Hz squarewave.

When PA7 is low, the output of U2C is low. R18 and C6 set the oscillator's frequency according to the equation $F = 1/(1.388 \cdot R18 \cdot C6)$ where $R18 \geq 10 \cdot R19$. U2D functions as an inverting speaker driver. When U2C is low, U2D is high and both terminals of the

DB1 PARTS LIST

Qty.	Ref#	Part
Resistors		
1	R1	3.3K, 0.25W, 1% (orange-orange-black-brown)
3	R2-R4	10K, 0.25W, 5% (brown-black-orange-gold)
Capacitors		
1	C1	0.1uF
Semiconductors		
4	D1-D4	Red T-1 LED
1	DISP	CC56-21EWA, four-digit multiplexed display module
1	U1	MC14489P
Other components		
1	DB1	Circuit board

CK2 PARTS LIST

Qty.	Ref#	Part
Resistors		
1	R1	1.0 ohm, 0.25W, 5% (brown-black-gold-gold)
1	R2	30K, 0.25W, 5% (orange-black-orange-gold)
1	R3	10K, 0.25W, 5% (brown-black-orange-gold)
1	R4	2.2M, 0.25W, 5% (red-red-green-gold)
1	R5	6.8K, 0.25W, 5% (blue-gray-red-gold)
2	R6, R20	1.2K, 0.25W, 5% (brown-red-red-gold)
1	R7	470K, 0.25W, 5% (yellow-violet-yellow-gold)

7	R8, R11-R16	330K, 0.25W, 5% (orange-orange-yellow-gold)
1	R9	1K, 0.25W, 5% (brown-black-red-gold)
1	R10	10M, 0.25W, 5% (brown-black-blue-gold)
1	R17	150K, 0.25W, 5% (brown-green-yellow-gold)
1	R18	560K, 0.25W, 5% (green-blue-yellow-gold)
1	R19	15K, 0.25W, 5% (brown-green-orange-gold)
1	R20	1.2K, 0.25W, 5% (brown-red-red-gold)
1	R21	33K, 0.25W, 5% (orange-orange-orange-gold)
1	RN1	10-pin, 10K, pin-1 common

Capacitors		
2	C1, C2	20pF, 25V
1	C3	680pF, 10%
1	C4	47uF, 35V axial electrolytic
1	C5	22uF, 25V axial electrolytic
1	C6	0.001uF
3	C7, C8, C13	0.1uF

Semiconductors		
3	D1, D2, D3	1N5818, 30V Schottky rectifier
1	U1	78S40, switching regulator
1	U2	LM339, quad comparator
1	U3	MC68HC705J1A, microcontroller

Other components		
1	Y1	4.1943MHz crystal, HC-49
1	L1	100uH coil
1	J2	DC power jack, 2.1mm center pin
1	P1	Piezoelectric speaker, AT-20K or equal

1	JP24	Two pin header
1	BAT	Battery connector (red +, black -)
1	U1	16-pin low profile socket
1	U2	14-pin low profile socket
1	U3	20-pin low profile socket
1	CK2	Circuit board

The following are available from:

Lucid Technologies
12907 Crookston Lane, Unit 22
Rockville, MD 20851
<http://www.cs.net/lucid/>

- 1) The big kit for \$39.00. Everything needed to build the alarm clock described in the article except the case, switches, and wall transformer.
- 2) The small kit for \$31.00. This includes only the circuit boards, integrated circuits, four-digit LED display module, discrete LEDs, red Plexiglass window, and one capacitor.
- 3) ICs and display-only kit for \$20.00. This is the kit for you if you don't intend to use the case or circuit boards shown in the article. It includes only the following parts:

78S40 universal switching regulator
LM339 quad comparator
MC68HC705J1A programmed microcontroller
MC14489 multi-character LED display driver
CC56-21EWA four-digit LED display

NOTE: Schematics, source code, assembly instructions and users manual are supplied on disk. Include \$3.20 for shipping in the US and Canada, \$6.00 elsewhere. Maryland residents include 5% sales tax.

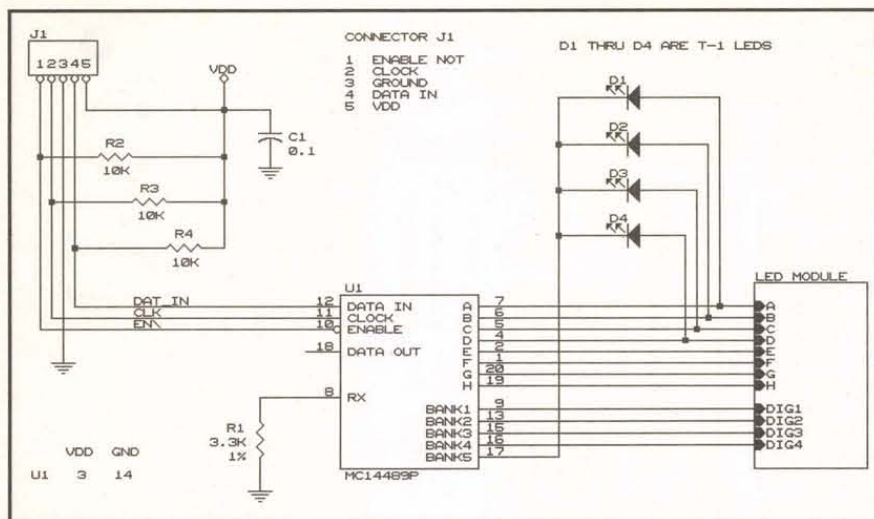


Figure 2.
Schematic of the
DB1 display circuit
board.

associated with it are not installed on the CK2.

Software

There isn't enough space to print the entire assembly language source code in this article. However, it is available on the Nuts & Volts website. The source code is well-commented and highly modular, so it should be easy to understand.

The code begins with several blocks of comments. These explain the memory map, functioning of all the ports, and the display interface. Mixed in with the comments are a large number of equate (EQU) statements. Equates associate understandable names with the numeric values used to reference various registers and memory locations. These equates make the difference between readable code and undecipherable hieroglyphics. The next section of code is the RAM definition area.

This section doesn't actually generate any code, but it does assign variable names to addresses in RAM. The subroutines come next in the program. One of the subroutines converts binary values to BCD, another converts 24-hour time to a 12-hour format, and another serializes the data before sending it to the display board. Internally, all times are kept in a 24-hour format, so the alarm will go off only once a day, even if you select the 12-hour display format.

Setting the time

Two other subroutines are responsible for setting the time of day and alarm time. Both of these subroutines call a delay subroutine that monitors how long you hold the "set" push buttons depressed. For example, if you press the TIME_SET and MINUTES_SET push buttons, the minutes will increase by one immediately.

If you keep both buttons depressed, the next increment will occur after 0.8 seconds; the interval between increments will then get smaller and smaller until it reaches a rate of five per second. This way, you can rapidly change a value by holding both buttons. Note that when the TIME_SET button is released, the seconds counter is cleared so that time-keeping resumes from the start of the displayed minute.

Program flow

At power-up, control is transferred to the address stored in the reset vector. In this case, it is the label "RESET." This portion of code config-

ures all the J1A I/O lines, and sets the multifunction timer for 16 real-time interrupts per second. All variables are initialized and the memory holding the current time is set to 0000, midnight in the 24-hour format. It then starts flashing the display on for one second, then off for one second until the TIME_SET button is depressed. Once the correct time is set, the program enters the main loop.

The main program loop (at the label LOOP) begins by putting the J1A in the WAIT-mode. The J1A must be brought out of WAIT-mode by an interrupt. When a real-time interrupt occurs, execution jumps to the real-time interrupt service routine, TICK. In the TICK routine, the memory locations holding the current time are incremented by 1/16 of a second. Execution then returns to the instruction following the WAIT instruction. After a real-time interrupt tick, the program checks the status of PWR_OK.

Assuming PWR_OK is true, the program branches to the normal power mode at label MLI00. The program checks the TIME_SET and ALARM_SET switches and calls the appropriate subroutines as required. The program clears the alarm condition flag if the ALARM_ENABLE input (PA4) is false.

Next, the program checks to see if it is the first tick of a new second. If it is, the display is updated. If it is the start of a new second and ALARM_ENABLE is true, the program compares the alarm time to the time of day.

If the times are equal, the alarm condition flag is set. While the alarm condition flag is true, the program will pulse the alarm on for one second, then off for one second for up to 30 minutes. Note that, in normal operation, switches are monitored every 1/16 of a second and the display is updated once a second. Finally, execution branches back to the LOOP label.

If PWR_OK is false, and has been for 32 consecutive real-time interrupt ticks, the program branches to low power (battery backup) mode at label LPI00. When first entering low power operation, the alarm clock will turn off all LED displays to conserve battery power. After the first real-time interrupt tick of every second, the program compares the alarm time to the time of day.

If the times are equal and ALARM_ENABLE is true, the alarm condition flag is set. While the alarm condition flag is true, the alarm will sound continuously for up to 59 seconds or until the ALARM_ENABLE input goes false.

Note that there is no visible indication of operation in low power mode and none of the SET switches will work. But as long as the battery lasts, the alarm will sound at the alarm time set before main power failed. This could keep you from missing work if a thunderstorm knocks the power out during the night. Finally, execution branches back to the LOOP label.


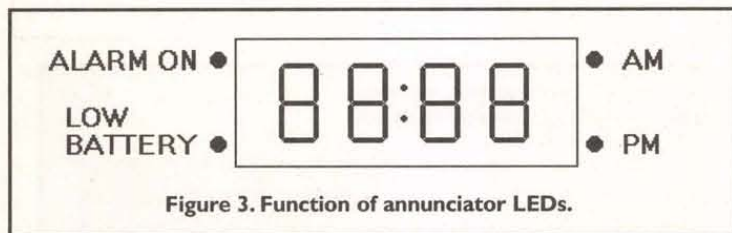


Figure 3. Function of annunciator LEDs.

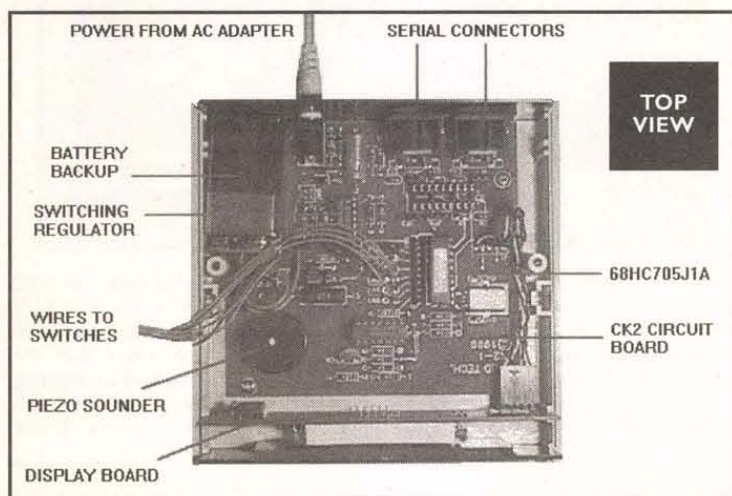

piezoelectric speaker are at the same potential so there is no audio output. When U2C oscillates, U2D applies a 5V squarewave to the piezoelectric speaker.

In addition to the circuitry mentioned above, the CK2 also includes an RS-232 serial communications link. Since this feature is not used with the digital alarm clock, the components

Mr. NiCd

May 2000 SUPER SPECIALS!

THE BEST BATTERIES IN AMERICA!

Packs & Charger for YAESU FT-50R / 40R / 10R:		For ICOM IC-2SAT / W2A / 3SAT / 4SAT etc:	
FNB-40xh 50m-NMH	7.2v 650mAh \$41.95	BP-83 pack	7.2v 600mAh \$23.95
FNB-47xh (NMH)	7.2v 1800mAh \$49.95	For ICOM 02AT etc & Radio Shack HTX-202 / 404:	
FNB-41xh (5w NMH)	9.6v 1000mAh \$49.95	BP-8h pack	8.4v 1400mAh \$32.95
For YAESU FT-51R / 41R / 11R:		BP-202S pack (HTX-202)	7.2v 1400mAh \$29.95
FNB-38 pack (5W)	9.6v 700mAh \$39.95	For KENWOOD TH-79A / 42A / 22A:	
For YAESU FT-530 / 416 / 816 / 76 / 26:		PB-32xh pack (NMH)	6.0v 1000mAh \$29.95
FNB-26 pack (NMH)	7.2v 1500mAh \$32.95	PB-34xh pack (5w NMH)	9.6v 1000mAh \$39.95
FNB-27S (5w NMH)	12.0v 1000mAh \$45.95	For KENWOOD TH-78 / 48 / 28 / 27:	
For YAESU FT-411 / 470 / 73 / 33 / 23:		PB-13 (original size)	7.2v 700mAh \$26.95
FNB-11 pack (5w)	12.0v 600mAh \$24.95	For KENWOOD TH-77, 75, 55, 46, 45, 26, 25:	
FBA-10 6-Cell AA case	\$14.95	PB-6X (NMH, w/cho plug)	7.2v 1200mAh \$34.95
Packs for ALINCO DJ-580 / 582 / 180 radios:		Mail, phone, & Fax orders welcome! Pay with Mastercard / VISA / DISCOVER / American Express	
EBP-20ns pack	7.2v 1500mAh \$29.95	Call 608-831-3443 / Fax 608-831-1082	
EBP-22nh pk (5w)	12.0v 1000mAh \$36.95	Mr. NiCd - E. H. Yost & Company	
EDH-11 6-Cell AA case	\$14.95	2211-D Parview Road, Middleton, WI 53562	
For ICOM IC-21A / T22-42A / W31- 32A / T7A:		CALL OR WRITE FOR OUR FREE CATALOG!	
BP-180xh pk (NMH)	7.2v 1000mAh \$39.95	Cellular / Laptop / Videocam / Commercial & Aviation packs too!	
BP-173 pack (5w)	9.6v 700mAh \$49.95	E-mail: ehyst@midplains.net	
For ICOM IC-W21A / 2GXAT / V21AT (Black or Gray):			
BP-132S (5w NMH)	12.0v 1500mAh \$49.95		

Interrupts

Following the main program loop, we come to the interrupt service routines. The first is TICK, the real-time interrupt service routine. TICK uses indexed addressing to access two tables: the time-of-day table (label TODAY) in RAM, and the rollover table (label RLOVR) in EPROM. Each time the real-time interrupt causes TICK to run, the TICKS variable is incremented. If TICKS is \geq its rollover value, it is cleared and the next higher variable in the time-of-day table is incremented. This process continues until there is no rollover or the entire time-of-day table is cleared, which happens every midnight. Finally, TICK clears the real-time interrupt flag, which enables the next real-time interrupt.

The second interrupt service routine is HICK, the external interrupt (IRQ) service routine. This routine consists of a single return from interrupt (RTI) instruction. The IRQ pin is tied to the PWR_OK signal monitoring the external 9V power supply. Thus, a falling edge on PWR_OK can trigger an IRQ interrupt. The IRQ input is monitored in the normal course of the program, so at first glance, it would seem that an interrupt service routine is not needed. Normally, one could simply disable the IRQ interrupt, but, to help keep power consumption low, the alarm clock program uses the WAIT instruction. WAIT automatically enables the IRQ interrupt so a minimal interrupt service routine must be provided.

Special registers

A special byte in EPROM — at address 07F1 — is called the mask option register (MOR). It controls several J1A hardware options. For the alarm clock, the MOR is programmed for: a 2M resistor across the oscillator pins, EPROM access allowed, no port-A interrupts, IRQ edge triggered, and watchdog timer disabled.

The J1A has four 16-bit interrupt vectors. Each vector contains the address for an interrupt service routine. When an interrupt occurs, the appropriate vector is fetched and execution branches to that address. The vectors are: 07F8/9 = Timer interrupt. This is the real-time-interrupt. The vector points to TICK. 07FA/B = External interrupt. This is the IRQ pin. The vector points to HICK. 07FC/D = Software interrupt. This is not used. The vector points to RESET. 07FE/F = Reset. The vector points to RESET.

Circuit Construction

The DB1 and CK2 circuit boards were designed to fit in a plastic case sold at RadioShack stores; you can, or course, put the clock in any case you like. If you don't purchase the circuit boards, you can put all the circuitry on one board instead of two. You can include a transformer and full-wave bridge in the clock case so you don't need a wall transformer. You can use a different LED display, but if you do, consult the MC14489 spec about set-

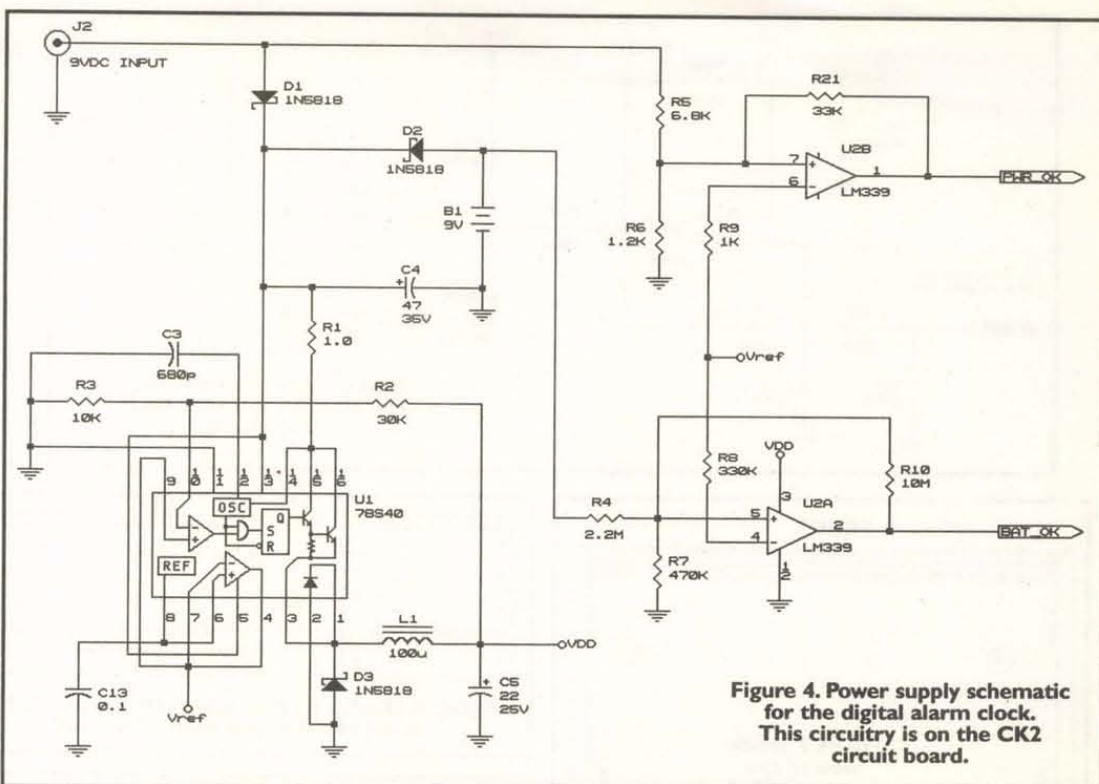


Figure 4. Power supply schematic for the digital alarm clock. This circuitry is on the CK2 circuit board.

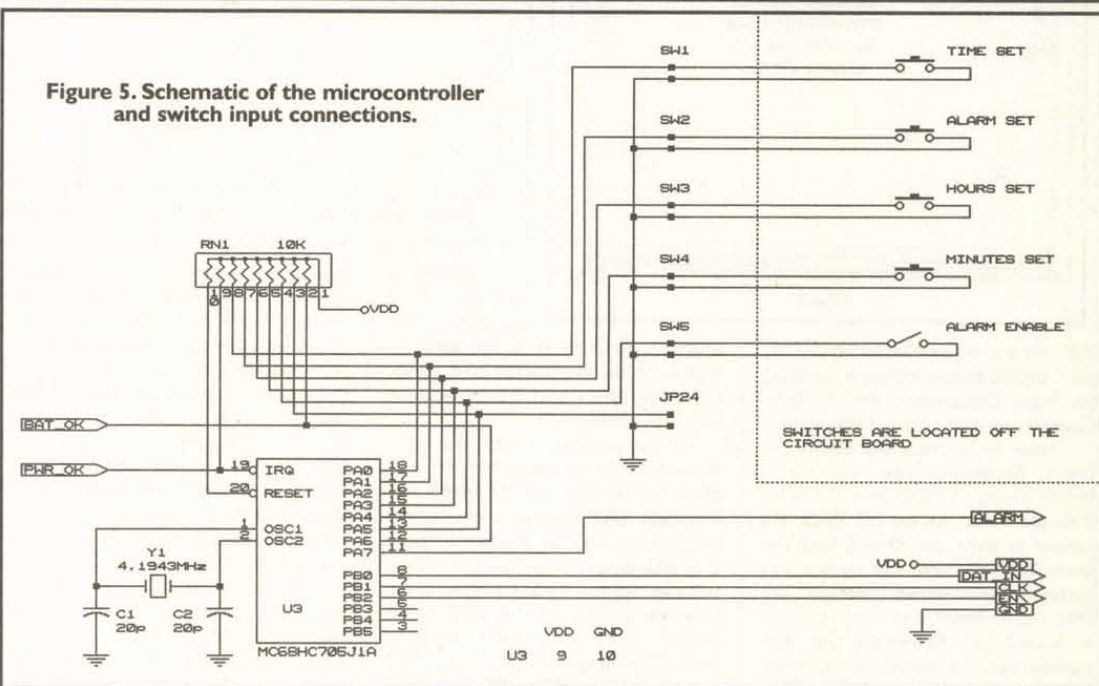


Figure 5. Schematic of the microcontroller and switch input connections.

ting the maximum segment drive current for your display.

For now, though, we'll assume you are building the alarm clock using the DB1, CK2, and RadioShack case. Detailed assembly instructions are included with the circuit boards. The only unusual thing about assembling the boards is that the DB1 has components on both sides. The LED module and discrete LEDs are on the front side, while all the other components are on the back or inside.

Circuit Board Checkout

Once the boards are assembled, you will need a multimeter or oscilloscope to check out the circuitry. You'll also need the wall transformer at this

time. You can use any wall transformer with a 9VDC output — 100 mA or more — and a coaxial power plug with 5.5mm O.D. and 2.1mm I.D.

Place the CK2 circuit board on an insulating surface. **DO NOT** install the ICs in their sockets or attach a battery yet. Attach the negative lead of your voltmeter to ground, such as the negative side of C4 or C5. Plug in the wall transformer and connect it to J2 on the CK2. The supply voltage should measure at least 9VDC at pins 5 and 13 of socket U1. Disconnect the wall transformer at J2, then insert the 78S40 in socket U1. Reconnect the wall transformer; then measure the voltage on the positive side of C5 (Vdd). The voltage should be between

4.8 and 5.1 volts.

Disconnect the wall transformer again, then insert the LM339 in socket U2. Reconnect the wall transformer, then measure the voltage at pin 4 of the 78S40. The voltage should be between 1.1 and 1.3 volts. This is the reference voltage (Vref) for the comparators. Next, we'll check the power monitoring comparators. With the wall transformer connected, measure the voltage at pin 1 of U2; it should be high. Measure the voltage at pin 2 of U2; it should be low. Now connect a fresh battery (Vbat >= 8V) to the CK2 battery connector. U2 pins 1 and 2 should both be high. Disconnect the wall transformer at J2 while leaving the battery connected. Confirm that

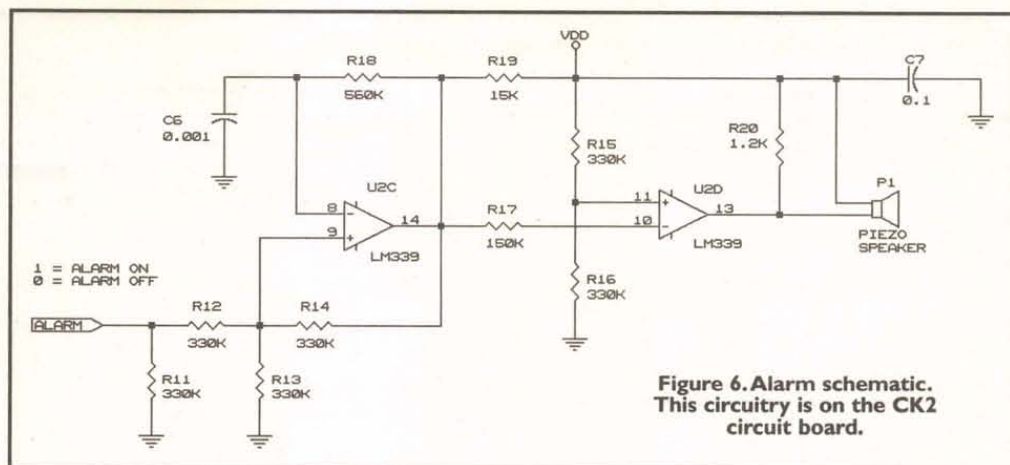


Figure 6. Alarm schematic. This circuitry is on the CK2 circuit board.

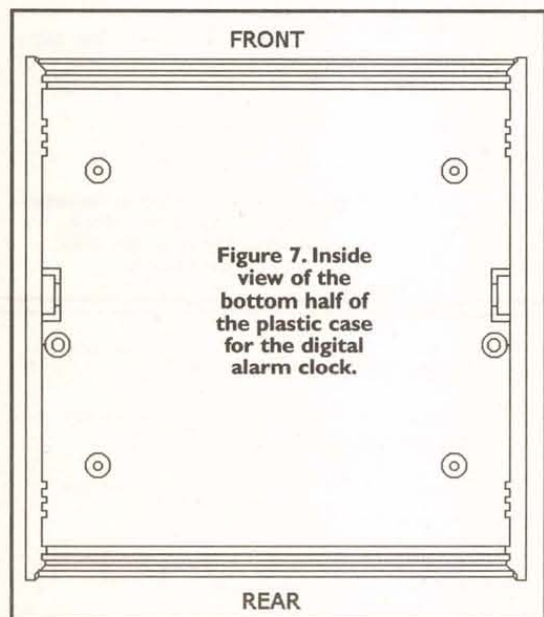


Figure 7. Inside view of the bottom half of the plastic case for the digital alarm clock.

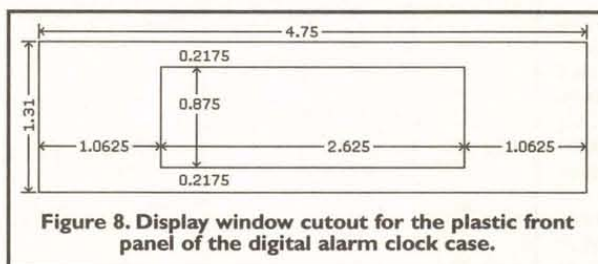


Figure 8. Display window cutout for the plastic front panel of the digital alarm clock case.

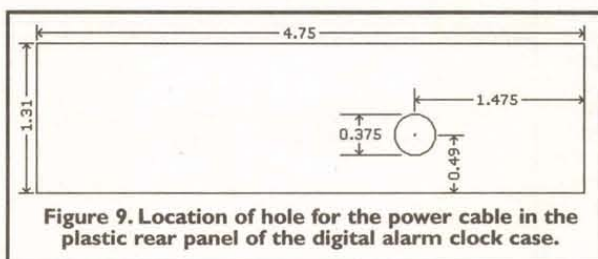


Figure 9. Location of hole for the power cable in the plastic rear panel of the digital alarm clock case.

Vdd remains at approximately 5V. U2 pin 1 should be low while pin 2 should be high. Disconnect the battery. Correct any errors and check again.

Now we'll check the alarm circuitry. Reconnect the wall transformer. Using a jumper wire, short pin 9 to pin 11 on socket U3. With this jumper in place, you should hear the alarm. With the wall transformer and battery disconnected, connect the DB1 display board and insert the J1A in socket U3. Reconnect the wall transformer. The display should begin flashing on for one second then off for one second. If this is not the case, the problem is either the J1A or the display board.

To see whether the J1A is functioning correctly, we'll look at the control lines going to the display. Observe pin 6 of the J1A with an oscilloscope or logic probe. This is the display select line which should pulse low, for about 360 microseconds, once a second. Next, look at pin 7 of the J1A. This is the synchronous data clock, which should exhibit a series of high pulses once a second. Finally, check pin 8 — the serial data to the display board. The serial data should exhibit a series of pulses once a second. If these three pins are functioning normally, we can be confident the J1A is good, and

any problem is with the DB1. If the J1A is the problem, be sure it is not installed backwards in the socket, and check the value of C1 and C2 to be sure they are correct.

If the problem is with the DB1, disconnect the wall transformer. First, check to be sure the MC14489 and four-digit LED module are oriented properly on the DB1. If either of these is upside-down, of course, the display will not work. Check for zero ohms between ground on the CK2 board and pin 14 of the MC14489. Check for zero ohms between Vdd on the CK2 and pin 3 of the MC14489. Check for zero ohms between pin 6 of the J1A and pin 10 of the MC14489. Check for zero ohms between pin 7 of the J1A and pin 11 of the MC14489. Finally, check for zero ohms between pin 8 of the J1A and pin 12 of the MC14489. Correct any errors and check again.

This completes the electrical checkout of the circuit boards. Final checkout can only be done after the clock is completely assembled and all the switches are connected.

Putting It All Together

Prepare the case

Now we turn our attention to the case (RadioShack 270-0214) and getting it ready to install the circuit

boards. Begin by identifying the bottom half of the case. The two screw holes, for holding the case together, go all the way through the bottom half.

The posts that these screws pass through are toward the rear of the case, as shown in Figure 7. There are four short posts for mounting a circuit board inside the case. The CK2 uses only three of these. The fourth post — located under the battery — must be removed so the battery will lie flat on the bottom of the case.

The next step is to add the red window to the front panel. Make a rectangular cutout 2-5/8 (2.625) by 7/8 (0.875) inches centered in the front panel; see Figure 8. Smooth the edges of the cutout and remove any plastic burrs. Place the front panel textured side down on a work surface. Position the red Plexiglass window (included with the circuit boards) on top of the panel, centered on the cutout. Place a drop of Super-Glue at the left and right edges of the window. This will bond the red Plexiglass window to the inside of the front panel. Don't touch the front panel until the glue has dried.

A hole must be drilled in the rear panel for the power plug that connects to J2. Figure 9 shows the position of the hole's center. Check your wall transformer's power plug to see how big a hole you must drill. Now we can start working on the top half of the case.

First, we'll drill the holes for the switches. There is no specific location for switches — you can put them wherever is best for you — but pay attention to two things. First, identify the front and rear of the top half. If you drill the holes in the wrong place, you can't just turn it around, the case only fits together one way! Second, watch the vertical clearance between the bottom of your switches and parts on the CK2 circuit board. I used submini momentary push buttons (RadioShack 275-1571) and a micro toggle switch (RadioShack 275-624). Temporarily place the CK2 and a battery in the bottom half of the case so you can measure clearances. After marking the switch locations on the top, drill the required mounting holes and securely mount the switches in the top half of the case.

Wire the switches

The switches must now be wired to the CK2 circuit board. Remove the J1A from its socket and store it in a safe place while soldering to the CK2. Figure 5 shows which switch goes to which SW connection on the CK2. One side of each switch is grounded and this ground can be daisy-chained around the switches, reducing the total number of wires going to the CK2. Allow enough slack in the wires so that the case can be opened and the battery replaced after the CK2 is attached to the bottom half of the case.

Finishing up

To keep the battery in place when the clock is moved, some sort of support is required. The simplest way to do this is to glue a piece of foam rubber to the inside top half of the case, just above the battery.

Attach the CK2 circuit board to the bottom half of the case using the three self-tapping screws that came with the CK2 circuit board. Insert the front panel into the most forward slot such that the red Plexiglass window is on the inside. Insert the DB1 circuit board into the slot behind the front panel. Insert the rear panel into the rear slot so that the hole lines up with connector J2. Put the J1A back in its socket. Plug in the wall transformer and connect it to the alarm clock via the hole in the rear panel. The display should now be flashing.

Try setting the time-of-day and alarm-time. Check that the alarm enabled LED follows the ALARM_ENABLE switch. If switches don't perform the anticipated function, you may have wired them to the wrong SW pad on the CK2.

Attach a 9V battery to the battery connector and place the battery in the case. Place the top on the case being sure not to pinch any wires in the seam. Use the long self-tapping screws that came with the case to securely close the case. Your alarm clock is now finished. Replace the battery whenever the low battery LED comes on. **NV**

MORE ON 121.5 MHz

In the April issue of *Nuts & Volts*, we described the importance of the emergency locator beacon service at 121.5 MHz and the relatively new 406.025 MHz datastream. When the 406.025 MHz signal also carries GPS coordinates, rescue personnel can get activated and on-scene much faster than conventional COSPAS-SARSAT Doppler shift positioning solely on 121.5 MHz.

But once rescuers arrive at the 406.025 MHz GPS-derived position, they won't necessarily be right on top of the activated emergency beacon. You may be assured that the GPS system is accurate within the radius of a 300-foot circle, but the uploaded 406.025 MHz GPS datastream may be rounded off. This occurs in order to minimize the frequency of updates of the position data.

The 406 MHz encoded position signal is encoded initially to be as close as possible to the actual position. The initial offset encoded is selected so that it may be summed with the course position to produce a finer position that is as close as possible to the actual position. Subsequent position updates (if applicable) are then encoded by retaining the course position and changing only the offset, provided that the required value is within the range of the offset. If the position update cannot be encoded by

changing the offset alone, there is a reset according to procedure for the initial position encoding.

Another problem might creep in where the position is in hours, minutes, and fractions of a minute, yet navigation to the EPIRB GPS-derived position is in hours, minutes, and seconds. The difference between fractions of a minute calculations and seconds within a minute calculations may affect how close rescue agencies are able to arrive on-scene to the indicated 406.025 MHz GPS-derived EPIRB position.

And what really happens out there with search and rescue agencies clearly illustrates the need for local homing in on the ever-present, half-watt, 121.5 MHz "localizer" signal. It is *this* signal that also transmits along with the now-and-then 406 MHz signal that allows rescuers to zero in on the activated ELT or EPIRB.

"We use the 406 MHz GPS position to get us in close, and then direction-find right down to the activated EPIRB on 121.5 MHz," comments William Alber, a reserve aero squadron sheriff. "Some of the equipment I own personally allows me to walk right up to an activated beacon, even though it might be totally hidden from the air," adds Alber.

Aboard the Coast Guard search and rescue boats and aircraft, direction finding to the 121.5 MHz signal employs an ADCOCK array antenna system which electronically spins the incoming signal heterodyned with an internal signal to calculate phase relationships among the multi-element antenna. These phase relationships are computed within the ADF to a visual readout of the signal source. As they fly in a direct path to the signal source, the ADF reads the bearing dead ahead. When they fly over the signal source, the ADF immediately shows the bearing behind the aircraft, and the signal strength begins to fall off, indicating the position has indeed been flown over.

But ADF systems are mighty expensive for rescue squad personnel who may only receive funding from donations. And this is where the ACR VECTA handheld direction-finder really pays off.

The ACR VECTA is a small, two-element beam antenna with an integral boom super-het-



erodyne receiver tuned to 121.5 MHz in Channel 1, and test frequency 121.775 MHz in Channel 2. The receiver outputs to a built-in weatherproof speaker, and the bright red LED signal strength indicator shows 255 step resolution of full scale in the zoom mode, and 16 steps of resolution on a full-scale mode. The LED signal meter will scroll in an upward fashion indicating an increase in signal strength as you approach the beacon and rotate the directional antenna in the direction of the beacon. During our trials on both the water, as well as in dense foliage, the LED bar becomes quite active showing our operators visually that they were getting closer to the rescue position as the LEDs began to climb up the signal meter. We would swing the beam back and forth, and easily see the general direction of the transmitting beacon.


In the macro mode, with the macro scale LED illuminated, the bottom light-emitting diode represents a value of zero, or no incoming signal. The next LED represents a value of 16, the third LED a value of 32, and so on. Each LED step represents a value jump of 16 units until you reach the top LED that has a value of 240 units in macro mode.

In the zoom mode, the bottom LED represents a value of 1, the second a value of 2, and so on. Each LED represents a value jump of 1 unit giving the top LED a value of 16, which is



ELT DEMO IN THE MALIBU HILLS ...

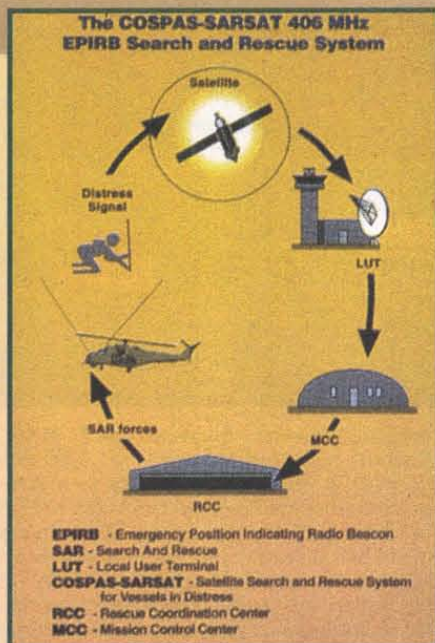(Above) Red Cross radio volunteers attend a briefing before an ELT transmitter hunt. (Right) Author West turning on the ACR test beacon during a search and rescue drill.



roughly equivalent to a 10 times increase of signal strength, 10 dB. The 16 LED units displayed in the zoom mode are equal to 1 LED unit of signal strength displayed in the macro mode, so it allowed us to switch between different modes as we began to get closer to the activated ELT.

It is important to slowly rotate the two-element beam antenna from horizontal to vertical when searching for the signal. This is because the activated transmitter could be in either the vertical or the horizontal plane, and you will receive best signal strength when the two planes are aligned.

When in the immediate vicinity of the beacon, signal reflections may cause you to receive numerous false direction indications. We wanted to reduce the sensitivity of the VECTA, so we closed the antennas and then wrapped our hands around the VECTA to detune the antennas. We next held the unit

close to our body, using the body as a shield by holding the base of the VECTA next to our belt line. By doing a couple of body twirls, we were finally able to figure out the general direction of the incoming signal in the direction of our belt buckle. The buckle actually has nothing to do with DFing, but the signal is dramatically less when coming in and needing to pass through our body back side.

Amateur radio operators who take part in VHF "fox hunting" are expert in tracking down hidden low-power transmitters, and anyone wishing to increase their fox hunting skills should buy the well-illustrated book by Joe Moell KOOV, at most ham radio dealers.

ACR is so committed to emergency locator beacon tracking, they offer a complete training package with the VECTA handheld portable direction-finder, along with a low-power test beacon operating on FCC-authorized EPIRB/ELT training frequency 121.775 MHz. The test beacon is an O-ring-sealed, battery-operated unit with an external antenna. It is submersible and carries a flotation collar for on-the-water training exercises. Although the unit only transmits 75 milliwatts, this is plenty of power at 121.775 MHz for open field or open water testing with the handheld VECTA direction finder.

Emergency groups working near an airport may also use the ACR emergency transmitter direction finder on the supplied external antenna as an initial alert device to an activated ELT that sometimes may occur with a hard landing. Many older aeronautical ELTs have no audible alert that the equipment is activated. The emergency group, or airport manager, or the airport Unicom station would have the VECTA running on AC power connected to the omnidirectional antenna. There is no mistaking the sound of an activated ELT. The emergency group would then respond by taking the VECTA off of the omnidirectional antenna and power supply, going outside and unfolding the directional antennas, and beginning the initial search of

the airport grounds to identify the source of the emergency signal.

If this can be done within a few minutes after activation, it very well could save a local Civil Air Patrol or United States Coast Guard unit from beginning an all-out search when notified by a mission control station that satellites are picking up an activated EPIRB somewhere in their area (as we described last month in *Nuts & Volts*).

"It is much easier to track down an activated EPIRB on the water than it is an activated ELT at an airport," claims Bill Alber. "On the water, there are little reflections of the signal, and the ACR handheld direction finder can easily spot the transmitting beacon. But at an airport, the VHF signals are easily reflected and scattered by metal hangars, and this is where the ACR equipment really pays off with its capability of attenuating the incoming signal," adds Alber. He points out that on-the-water signals can sometimes be traced in as little as 20 minutes, but down at the airport, it might take up to 40 minutes.

"Even though there is tremendous emphasis on boaters choosing a new 406 MHz EPIRB, this does not mean that 121.5 MHz is going away," comments Paul Hardin of ACR.

"121.5 MHz is still the frequency of choice for radio direction finding, or homing purposes — the 406 MHz side of the EPIRB is only on the air for less than a half a second duration at 50-second broadcast intervals — it is much easier to home in on 121.5 MHz, almost ignoring the 406 MHz signal when in close during direction-finding procedures," adds Hardin.

But when the 406 MHz signal is activated, along with the unique ACR interfaced GPS position datastream, rescue efforts start immediately, and ultimately end up with local rescue units homing in on the activated EPIRB with the 121.5 MHz local signal. If you have any type of VHF equipment that can listen in on 121.5 MHz, give it a try and see if you can pick up the sounds of an activated ELT or EPIRB. **NV**

The Computer Controlled World: RS-232 Network Control Methods and Applications

Video for Windows (Part 2)

by Ryan Sheldon, National Control Devices • (417) 646-5644 • www.controlanything.com

Watch 16 video cameras in a Windows 98 window and control the position of each camera.

Last year, I showed you how to watch 16 different video cameras in a Windows 95 window. This article serves as an update to the original article published in May '99. This article shows how the same job can be accomplished using a low-cost video control module. We also add the ability to control the position


of each camera using our new SCAM chip. And, for the first time, the video window can be adjusted to fit any size monitor.

To complete this project, you will need a few low-cost items. The capabilities of the system are simply a function of how much money you want to spend. Chances are, you already have some of these items. If not, Table 1

shows a simple list of items and sources I recommend.

Figure 1 shows the video window for all 16 cameras. The program tells the ASEL video switcher to go to camera 1, grab a frame, and display it in the video window. It then switches to camera 2, grabs a frame, and displays it next to the first image. It cycles through all 16 cameras, grabbing images, and updating the respective video window.

FIGURE 1

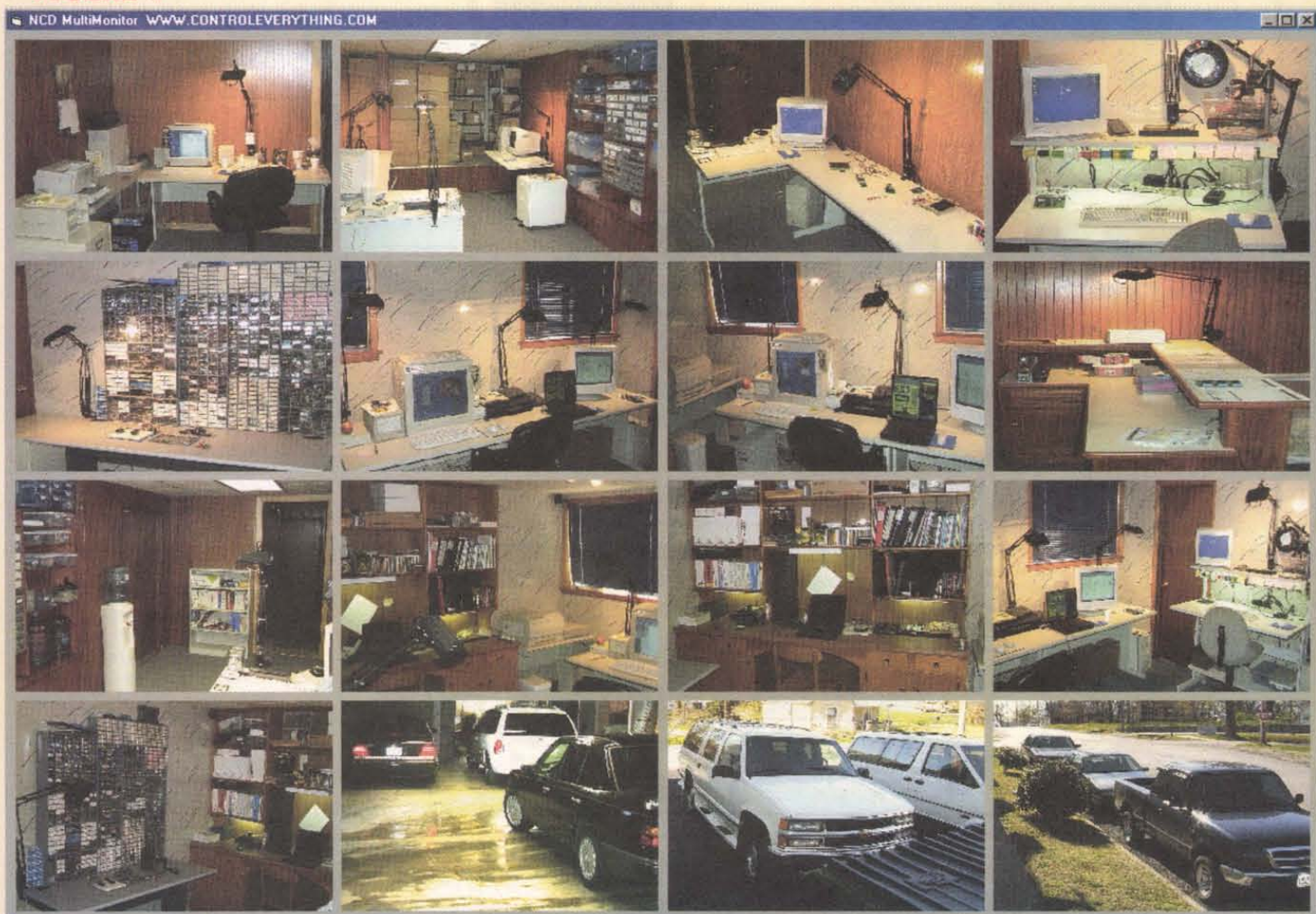

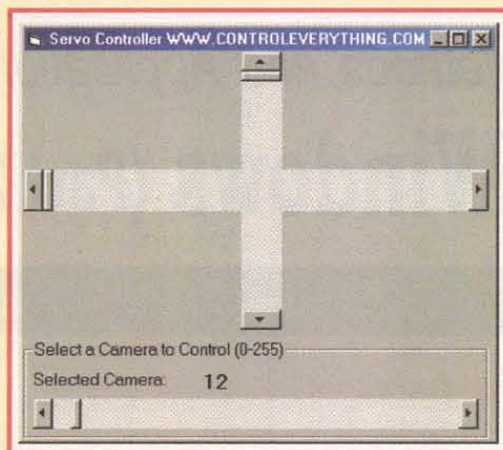


FIGURE 2

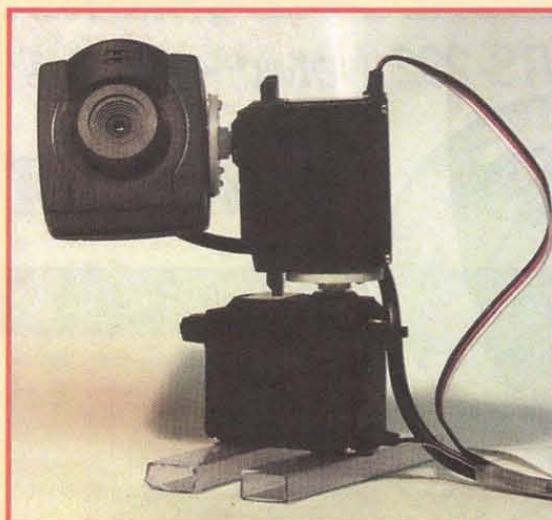


FIGURE 3A



FIGURE 3B

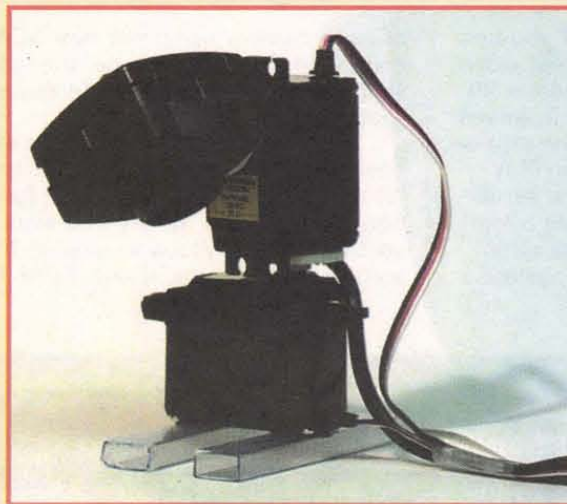


FIGURE 3C

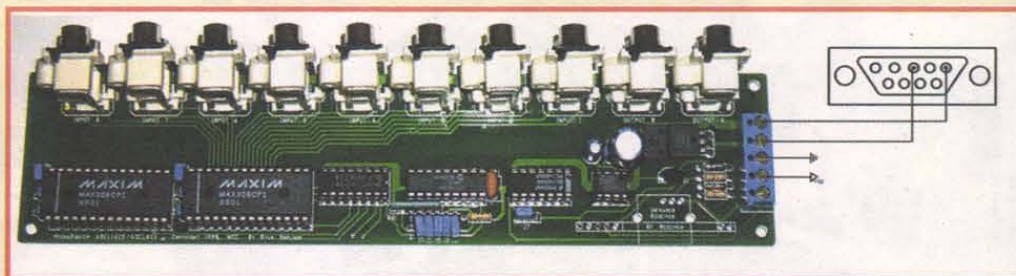


FIGURE 4



FIGURE 5

Performance

This program is capable of updating each video window every 2.14 seconds using a STB TV Tuner card on a Pentium II 400 system. If you have a faster computer, and an AGP All in Wonder Pro (with integrated TV Tuner), you will probably get faster frame rates.

Figure 2 shows sliders that can be used to position the video cameras. Use the slider on the bottom to select a camera to control, then use the horizontal and vertical sliders to move the camera.

Figures 3A, B, and C show how a small Panasonic CCD camera can be mounted to a couple of servos for pan and tilt. Use hot glue to attach the servos together. Make sure the servos are centered prior to gluing. The camera shown in this article is available from www.digikey.com, part number P9506-ND. The servos shown are System 2000 Standard Servo TS-51 from www.towerhobbies.com. These were purchased a few years ago and don't seem to be available. I believe the TS53J servo will work as a replacement, but have not tried it.

Hardware Installation

Figure 4 shows the ASEL video switcher connected to the solder side of a DB-9 female connector. Connect the DB-9 female to COM1 on your computer. A 12-volt DC power supply is required to power the video switcher board. Power can be tapped from the yellow and black wires used to power the hard drive inside your computer.

Figure 5 shows the video connections on the ASEL video switcher. Connect a camera to each of the video inputs. Connect Video Output 1 to the video input of your video capture card. Connect Video Output 2 to an external monitor.

Figure 6 shows a simple diagram for connecting your computer to several SCAM chips for camera positioning. The DB-9 female should be connected to COM3 on your computer. If COM3 is not available, it will be necessary to change the COM port in the software.

It is possible to connect the ASEL video switcher with version 2.0 firmware on

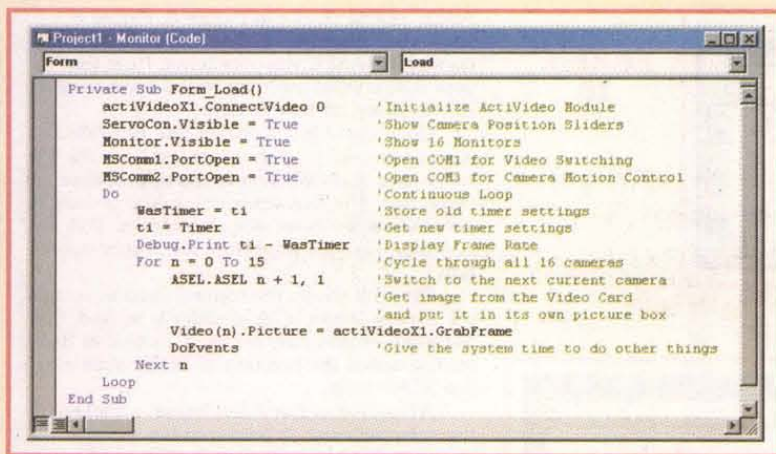


FIGURE 7

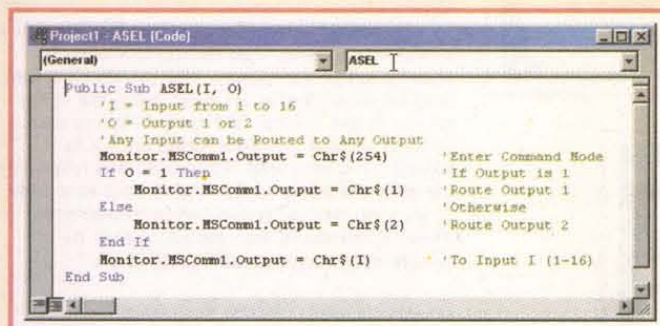


FIGURE 8

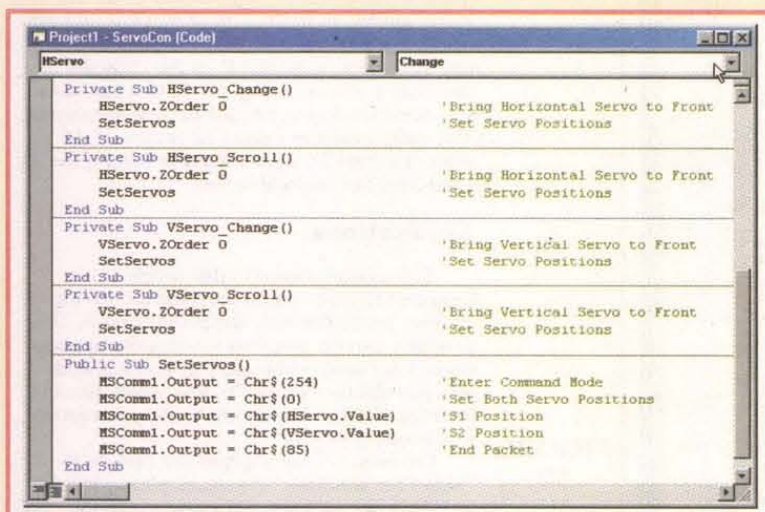


FIGURE 9

the same serial port as the SCAM chips. We chose not to do this in this application because of the high bandwidth requirements of this application. It is much better to devote COM1 to video switching and COM3 to motion control.

Software Installation

Step 1

Begin by installing Visual Basic 6 Professional or Enterprise on your computer.

Step 2

Go to www.contoleverything.com, select ASEL 16x2 RS-232 Controlled Video Switcher from the main page. From this page, select "Watch 16 Video Cameras in a Windows 98

Window." Now select "Download ActiVideo Control Module."

Step 3

Select "Download MultiMonitor Source Code" and unzip the contents into its own folder on the desktop.

Step 4

Install and register the ActiVideo control module with the manufacturer.

Step 5

Double click "MultiMonitor.vbp" to load the program in Visual Basic 6. Run the program. If you get any errors, they are probably related to the COM port. Remember, this program expects COM1 and COM3 to be available.

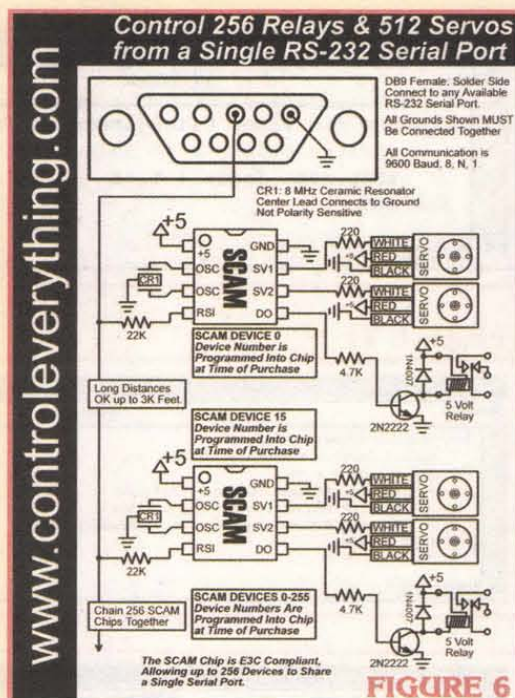


FIGURE 6

Using the Visual Basic Software

When the program is run, you will see 16 boxes, each with a video frame from each of the 16 cameras. Click on one of the video boxes to select a video source that will be displayed at full speed on the external monitor connected to Video Output 2 on the ASEL video switcher.

Next, use the sliders on the Servo Controller window to position a camera. You can control which camera is positioned by adjusting the slider on the bottom of this window.

Programming Details

When the program is run, the code shown in Figure 7 begins to execute. The program starts by connecting the ActiVideo control module to your video capture card. It then displays the MultiMonitor video window and opens COM1 and COM3. You can change which COM ports are in use by changing the "Properties" window for the MSComm1 and MSComm2 control modules. These modules are shown as telephone icons in the lower right corner of the program (when it is not running). These telephone icons represent COM1 (left) and COM3 (right).

Once the COM ports are open, the program goes into a continuous loop. The first three lines inside the loop are used to display the rate at which frames update. The number given in the immediate window represents the elapsed time between frame grabs.

The program then counts from 0 to 15, representing each of 16 video sources. The ASEL video switcher is routed to the first camera using the

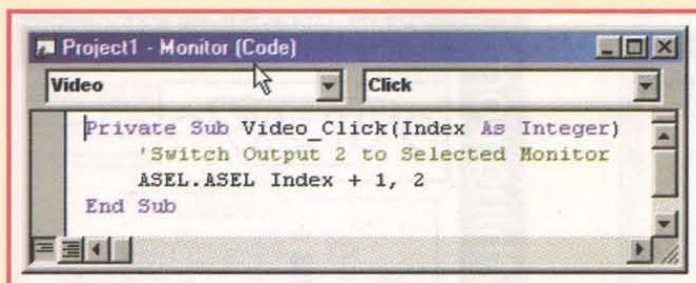


FIGURE 11

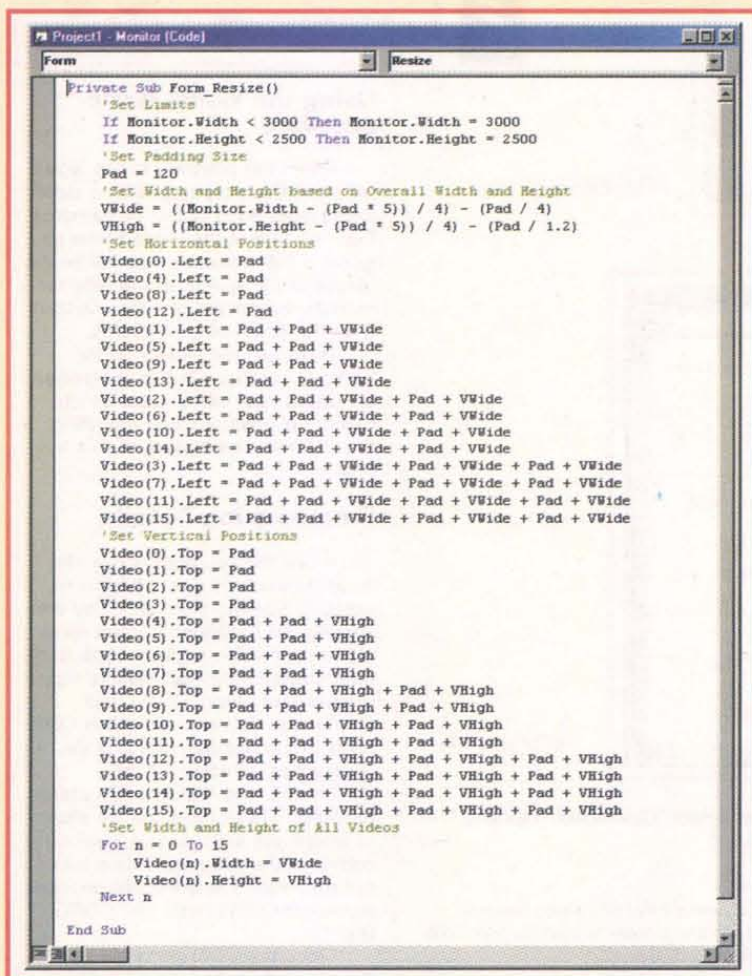
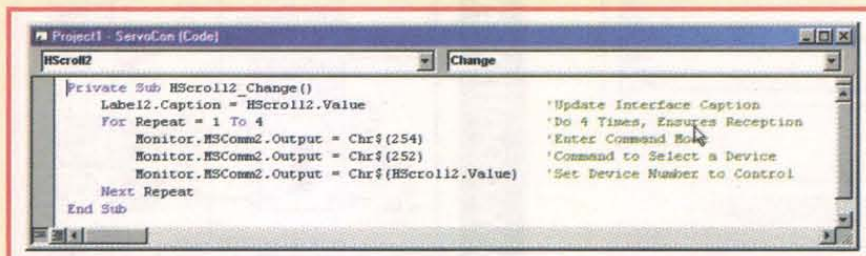


FIGURE 10

FIGURE 12

System Requirements

Visual Basic 6 Professional
 ActiVideo Control Module
 SCAM Servo Camera Controller Chips
 ASEL Video Switcher
 All in Wonder Pro with TV Tuner
 CCD Cameras P9506-ND
 Tower Hobbies LXJB61 TS53J Servo
 Television with Composite Video Input

Cost

varies
 \$100.00 Registration
 \$10.00/each
 \$149.00
 \$100.00 (approx.)
 \$125.00/each
 \$9.99/each
 varies

Sources

www.ebay.com
 www.controleverything.com
 www.controleverything.com
 www.controleverything.com
 www.buy.com
 www.digikey.com
 www.towerhobbies.com

TABLE 1

ASEL routine shown in Figure 8. Figure 8 shows the actual RS-232 commands used to control the ASEL video switcher. Note that your ASEL video switcher MUST have version 2.0 firmware for this to work.

Once the video is routed, the ActiVideo module is used to grab an image from the TV tuner card and display it in the appropriate video box. The DoEvents command is used to allow Windows to service other tasks. This command is very important for proper operation.

Figure 9 shows the routine used to control the servos. When a servo slider is moved, the SetServos subroutine is called. Note that this routine sends the position of BOTH sliders to the SCAM chip.

When one of the video boxes is clicked, the selected video is routed to the monitor connected to Video Output 2 of the ASEL video switcher. The routine that manages the "click" and "switch" operation is shown in Figure 10.

The SCAM chips support the E3C command set, allowing 256 different devices to share a single serial port. The SCAM chip that is to be controlled is selected using the slider shown at the bottom of Figure 2. When this slider is moved, the subroutine shown in Figure 11 is executed. This routine is responsible for controlling which SCAM chip responds to your horizontal/vertical slider movement. These commands are sent four times to ensure the receipt by all SCAM chips.

Scaling the Video Window

One of the big changes for the new program is the ability to dynamically scale the video window to fit the size of monitor you are using. For the first time, it is possible to use any size monitor, from 14" to 24". Thanks to the routine shown in Figure 12, you can resize the video window to fit your particular monitor. The code shown in Figure 12 resizes all 16 video windows by dynamically adjusting the horizontal and vertical scales.

Applications

The project shown in this article was designed to give you an introduction to the endless possibilities of computer control. This program can be modified for security applications, time lapse photography, and has endless possibilities for distributing video over the internet. Using a few simple tools, you can do just about anything.

I hope you have enjoyed my update to "Video for Windows." As usual, please feel free to E-Mail or call if you have any questions. **NV**

CONTACT INFO:

Ryan Sheldon
National Control Devices
P.O. Box 455
Osceola, MO 64776
Phone: (417) 646-5644
FAX: (417) 646-8302
ncdryan@aol.com
www.controlanything.com

New Product News



NIGHTVISION VIDEO CAMERAS

Applications such as drug interdiction and border security require the ability to operate in total darkness without the luxury of external infrared illuminators.

This new nightvision video camera is built around an enhanced generation-one intensifier tube.

The unit offers available ambient light operation, as well as total darkness technology via a built-in IR illuminator.

Lens is 90mm with a 14-degree field of view,

with 3X magnification.

Weight is only 1.5 pounds and a convenient tripod socket is located under the unit's center of gravity, and the unit is rugged and water resistant.

The image intensifier operates on an internal three-volt battery which provides 12 hours of continuous operations.

The video camera operates on 12-volts DC. The intensifier tube has automatic brightness control and light overload protection.

The video camera features auto exposure control and standard RCA video connectors for use with any standard VCR, monitor, or transmitter. Widely used for monitoring of illegal toxic waste dumping, drug interdiction, vandalism, and more.

Available for only \$1,299.95 from Supercircuits.

For additional information, contact:

SUPERCIRCUITS
1 SUPERCIRCUITS PLAZA, DEPT. NV
LEANDER, TX 78641
512-260-0333 FAX: 512-260-0444
WEB: www.supercircuits.com

AM-780 AM RADIO KIT

Elenco Electronics announces the AM-780 AM Radio Kit. The AM-780 is a tuned radio frequency receiver of the standard amplitude modulation (AM) frequencies (550 KHz 1660 KHz) that you assemble.

The AM-780's manual has easy-to-follow, step-by-step assembly instructions. The instructions include many drawings to clearly illustrate the assembly. All components are clearly identified.

The radio measures 5.3" x 3.5" and requires a nine-volt battery.

The AM-780 is designed to be a learning experience in electronics. It teaches proper soldering techniques using easy-to-understand pictures. It has a theory of operation section and block diagrams explaining how it works, along with schematics and other technical information. There is also an explanation of the resistor color code and a glossary.

The AM-780 is available at a list price of only \$13.25. For more information, contact:

ELENCO ELECTRONICS, INC.
150 W. CARPENTER AVE., DEPT. NV
WHEELING, IL 60090
847-541-3800 FAX: 847-520-0085
E-MAIL: elenco@elenco.com
WEB: <http://www.elenco.com>

RCC7K RADIO-CONTROLLED CAR KIT

Elenco Electronics announces the newest addition to its broad line of quality electronic kits: The RCC7K Radio-Controlled Car Kit. The RCC7K is a complete seven-function R/C car that you assemble.

The RCC7K is designed to be a learning experience in electronics. It teaches proper soldering techniques using easy-to-understand pictures. It has a theory of operation section and block diagrams explaining how it works, along with schematics and other technical information. It includes subjects like gears, radio transmitters and receivers.



The RCC7K is available at a list price of only \$33.25.

For more information, contact:

ELENCO ELECTRONICS, INC.
150 W. CARPENTER AVE., DEPT. NV
WHEELING, IL 60090
847-541-3800 FAX: 847-520-0085
E-MAIL: elenco@elenco.com
WEB: <http://www.elenco.com>

Showcase your New Products here! Send all press releases or information/photos to:

Nuts & Volts Magazine
New Product News
430 Princeland Court,
Corona, CA 92879
or E-Mail to
newproducts@nutsvolts.com

MULTIMEDIA SPEAKERS

Alltronic introduces a quality slimline 30-watt multimedia powered speakers with cables, power supply, and headphone jack.

Multimedia speakers may hang on your computer monitor or sit in small footprint on your desk. Size is 10.25"H x 2.5"W x 6"D.

Alltronic part 98V004 sells for \$19.95 a pair. For more information, contact:

ALLTRONICS
2300-D ZANKER RD., DEPT. NV
SAN JOSE, CA 95131-1114
408-943-9773 FAX: 408-943-9776
WEB: <http://www.alltronic.com>



TLR-6960 TIME LAPSE RECORDERS

Matco releases TLR-6960 Time Lapse Recorders. They are manufactured by JVC and distributed by Matco, Inc.

The TLR-6960 Time Lapse Recorders are the ideal solution for a variety of applications including consumer, industry, and business security systems.

The TLR-6960 Time Lapse Recorder has four heads and provides high-quality, clear pictures.

Some features of the TLR-6960 Time Lapse Recorders are: recording ranges

from 6-960 hours; built-in time and date generator with alarm inputs; easy time setting and tape recording; it integrates a battery backup up to three months that provides a special feature of automatic resumption of system operation after power failure; in addition, it has very easy on-screen programming.

For a special introductory offer, the sales price is only \$469.00 each (regular price is \$549.00).

For more information, contact:

MATCO, INC.
830 E. HIGGINS RD., #111-G, DEPT. NV
SCHAUMBURG, IL 60173
847-605-1020 FAX: 847-619-0852
1-800-719-9605
E-MAIL: press@mat-co.com
WEB: <http://www.mat-co.com>

High Performance Auto Ranging DMM

New to our DMM line-up and possibly (probably) the best DMM value anywhere! Includes: Analog Bar Graph! Auto-Ranging! Data Hold! Temperature Probe! Frequency Test! Continuity Test! AND MORE!

Features:
Data Hold: Freezes reading for easy checking
Auto Ranging: For easy precise range settings
Range Hold Control: allows for manual selection of test range
3-1/4 Digit LCD Display: Reads up to 3260.
Easy to read display
Function Dial: Easy to use to select measurement type or turn unit off.
4 Jack Plugs: Safety design with different capacities for different functions.
Diode, Continuity Check Push-Button: For toggling between diode check and continuity check.
Low Battery Indicator: Advises you when it's time to change battery.
Extra Long 44" Test Leads: Helps get to hard to reach places.
Screw-On Alligator Clips: Convert one or both probe tips to alligator clips.
Fuse-Protected Circuitry
Built-In Stand: Makes one hand operation easier.
Shock Absorbing Rubber Carrying Case: with convenient probe storage clips and hanging tab.
Helps protect the DMM from damage if accidentally dropped.

Measures:
DC Volts: up to 1000V
AC Volts: up to 750V
AMPS: up to 20 Amps (AC & DC)
Resistance: up to 30M ohm
Continuity Check: with audible signal (signal sounds if resistance is less than 20 ohms. Display reads actual resistance).
Frequency: (1KHz to 300KHz) displays both digital and bar graph reading
Transistor hfe Test: Display shows approximate hfe value based on test condition of 10uA base current and Vce of approx. 3V.
Temperature Test: Measures from 0° to 1832° F (probe supplied)
Diode Test: Tests if diodes are shorted or open
Specifications
Accuracy
Vdc: ±1.0% reading +5 digits
Vac: ±1.5% reading +8 digits
Aac: ±1.5% reading +5 digits
Aac: ±1.5% reading +5 digits
Resistance: ±1.5% reading +5 digits
Frequency: ±3.0% reading +5 digits
Temperature: ±1.0% reading +6 digits



#CS19903

Input Impedance: 10Mohm (Vdc/Vac); over 100Mohm on 300 mVdc range
Requires two AAA batteries sold separately.

NOW IN STOCK!**ONLY \$29.95****2GHz RF Field Strength Analyzer****ONLY \$1589**

• Frequency Range: 100KHz to 2.060GHz
• Narrow Band FM (NFM), Wide Band FM (WFM), AM and Single Side Band (SSB) Modulated Signals May Be Measured
• PLL Tuning System for Precise Frequency Measurement and Tuning
• LED Backlight LCD (192x192 dots)
• Built-In Frequency Counter
• Hand-Held and Battery Operated
• All Functions are Menu Selected
• RS232C for PC Interface and Printer

#3201

See the web site for details

Removable Hard Drive Rack

For IDE/Ultra DMA Hard Drives

We Sold Over 14,000 in 1998!

ONLY \$14.95 any qty.

This product can be used with any 3-1/2" IDE hard drive up to 1" high. It includes an electronic keylock for safe removal and insertion. Made of ABS 707 fireproof plastic. Use this product to protect sensitive hard drive data, take your hard drive between work and home or even set up different users with their own hard drives that they physically insert every time they use a PC. Other models available from C.S.I. include RH10 series and RH20 series, which are interchangeable within the same interface design (IDE or SCSI).
Other Models are Available. See www.web-tronics.com under "hard drive and accessories" for more details and pictures.



RH-10C-IDE

Removable Hard Drive Rack with Auto Door And Cooling Fan

• Auto door on the outer frame
• ABS material of outer frame, High efficiency cooling fan
• Worldwide patent pulling function handle
• CE Approved
• Coating iron bottom cover
• For IDE interface
• For 1" high 3.5" HDD
• Not compatible with our RH10 & RH20 series. Compatible with our RH17-IDE model.



#MR-27

ONLY \$18.95 any qty.Details at www.web-tronics.com**Auto-Temp Solder Station with Ceramic Element**

• With Ceramic Heating Element for More Accurate Temp Adjustment
• 3 Conductor Grounded Power Cord
• 250°C-480°C (470°F-900°F)
• Fast Heating Feature



SR-976

Extra Tip Options Available. See Web!

ONLY \$39

CTRL - D to bookmark this site

www.web-tronics.com

Don't forget the dash

Circuit Specialists Inc.

In Business Since 1971


• Easy to Navigate
• Includes a Search Engine That Really Works
• New Items Added Constantly

CCD B&W Board Cameras

• **ASIC CCD Area Image Sensor**
• **Extremely Low Power Consumption**
• **0.5 Lux Min Illumination**
• **Built-In Electronic Auto Iris for Auto Light Compensation**

Detailed Specs on the Web

VM1030PA-B 30mmx30mmx25mm, Pinhole lens, 12V \$39.00 any qty.
VM1030A 30mmx30mmx26mm, Standard lens, 12V \$39.00 any qty.
VM1035A 42mmx42mmx25mm, Standard lens, 12V with back light compensation \$49.00 any qty.
VMCB21 44mmx38.5mmx28mm, with 6 infra-red LEDs, 12V \$49.00 any qty.
VM1036A 32mmx32mmx25mm, Standard lens, 12V, reverse mirror image feature \$49.00 any qty.

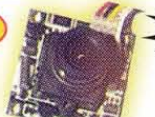**LOWER PRICES****Bullet CCD Cameras****B&W and Color**

• **Smart Rugged Metal Housing**
• **Extremely Low Power Consumption**
• **12 Volt**
• **CCD Area Image Sensor for Long Camera Life**
• **Built-In Electronic Auto Iris for Auto Light Compensation**
• **No Blooming, No Burning**
• **0.1 Min Lux Illumination (B&W) (1 Lux Min Lux Illumination (color))**

Detailed Specs on the Web

VMBLT1020 B&W, 21mm(D)x55mm(L) \$49.00 any qty.
VMBLT1020V B&W Weatherproof, 21mm(D)x58.5mm(L) \$79.00 any qty.
VMBLTJC19BW COLOR! Weatherproof, 17mm(D)x88mm(L) \$139.00 any qty.

**LOWER PRICES****COLOR CCD Mini Board Cameras**

• **Low Power Consumption**
• **1 Lux Illumination**
• **Built-In Electronic Auto Iris for Auto Light Compensation**
• **Internal Synchronization**
• **12Volts**
• **400 TV Lines**

Detailed Specs on the Web

VM3010PA 33mmx33mmx18mm, Pinhole lens \$99.00 any qty.
VM3011-A 45mmx40mmx24mm, Standard lens, single board \$89.00 any qty.
VM3010-A 33mmx33mmx32mm, Standard lens \$99.00 any qty.

**PRICE REDUCTION****new! 3-1/2 Digit JUMBO Digital Panel Meters**

Check these LOW PRICES!

• 21mm Figure Height
• 5 Volt Common Ground or 9V Independent Power Supply Versions Available
• Voltage Divider Resistors included and max. Measured Range Selectable by Soldering a Selection Joint
• Easy Bezel Snap-In Design (84mm x 41mm rectangular hole typical)
• "0" Reading for "0" Voltage Input
• High Quality SMD Production Method
• Dual Slope Integration A-D Converter System ±0.5% Accuracy

NOW IN STOCK!**AS LOW AS \$6.25**

PM-1028A LCD 9V Independent Power Supply Version 1/\$12.95 10/\$10.89 100/\$7.99 250/\$6.25
PM-1028B LCD 5V Common Ground Power Supply Version 1/\$13.95 10/\$11.84 100/\$8.89 250/\$7.15
PM-1029A LED 9V Independent Power Supply Version 1/\$14.95 10/\$12.50 100/\$9.95 250/\$7.89
PM-1029B LED 5V Common Ground Power Supply Version 1/\$15.95 10/\$13.40 100/\$10.79 250/\$8.65

Our Most Sophisticated DMM We Sold Over 700 Last Year!

with RS-232 Interface & Software, 3-3/4 Digit, 4000 Count, Auto-Ranging with Analog Bargraph

• True RMS Mode
• 10MHz Frequency Counter
• Time Mode with Alarm, Clock, and Stop Watch
• Dual Display
• 10 Location Memory
• Min, Max, Avg and Relative Mode
• Decibel Measurement
• Cap and Ind. Measurement
• Temperature Mode (C/F)
• K Type Temperature Probe Included
• Pulse Signal for Logic & Audible Test
• Continuity/Diode Test
• Logic Test
• Auto Power OFF/"Keep ON" Mode
• Fused 20A Input with Warning Buzzer
• Back Light
• Data Hold/Run Mode
• Safety Design IUL1244 & VDE-0411
• Protective Holster
• Silicon Test Leads

**NOW ONLY \$129 Reg. \$169**

More Details on our Web Site

PROTEK 506**3000 Series Digital R/O Bench Power Supplies**

♦ Low Cost Single Output ♦ 3 Amps

High stability digital read-out bench power supplies featuring constant voltage and current outputs. Short-circuit protection and current limiting protection is provided. Highly accurate LED accuracy and stable line regulation make the 3000 series the perfect choice for lab and educational use.



Line Regulation: $2 \times 10^{-4} + 1\text{ma}$
LED Accuracy: Voltage: $\pm 1\% + 2$ digits
Current: $\pm 1.5\% + 2$ digits
Wave Line Noise: $\pm 1\text{mVrms}$
Dimensions: 291mm x 158mm x 136mm



CSI3003: 0-30v/0-3amp
Digital R/O Bench PS,
1x10⁻⁴+5mv Load Regulation
\$99.00 5/\$89.00

AS LOW AS \$89**new! Hot Air SMD Rework Station**

WOW! ONLY \$489

Similar Systems Cost 100s More!

ONLY \$489

#SR-979



For technicians, service/repair depots and assembly rework. We also stock a selection of nozzles for QFP, SOP & PLCC devices (see our website for selection details). Hot Air temperature variable from 100°C to 400°C (212°F to 754°F) power consumption: 275w max. Auto cooling feature cools system after shut off to extend service life of heating elements and handle. One year limited warranty from C.S.I. Comes with QFP Nozzle (0.68" x 0.68")

new! O'Scope Offer

30MHz! ONLY \$299! ONLY \$299

Take Advantage of this low price!

• Dual Channel
• Dual Trace
• Vert Trigger
• 1 Year C.S.I. Warranty!



#OSC-1030

Manufactured for CSI by a leading O.E.M. manufacturer. See our website for detailed specifications!



CSIHTR2400 Includes One Transmitter & One Receiver with Power Supplies \$139.00 \$109.00
CSIHTR2400TX Extra Transmitter/Each Receiver will Monitor up to 4 Transmitters \$89.00

See more detailed specifications at www.web-tronics.com in the CCD camera section.



CLONE, TEST OR REPAIR ANY HARD DRIVE

"THE MOST COMPLETE HARD DRIVE WORKSTATION WE'VE SEEN!" BOB ROSENBLOOM, DIGITAL VIDEO, INC.

DRIVE SERVICE STATION

Copy entire hard drives with ease. Drive duplicators are essential tools for dealers and system builders. Don't spend hours installing and formatting drives. Do it instantly with the Pro. Set up any SCSI or IDE drive with your original software. Connect blank drives to the Pro and press start. You'll copy entire drives faster and more accurately than is possible on any PC. With our combination IDE and SCSI model, you can even copy data between different interfaces. All models include both 2.5" and 3.5" interface adapters. The Pro also supports SCA and Wide SCSI drives.

Choose the Pro, and you'll also have an entire factory drive test and repair system for under \$1000. The Pro gives

BUY MANUFACTURER DIRECT: \$995

408 330-5525

you the ability to copy, reformat, repair, translate, and test any hard drive. Use the Pro to put any hard drive through its paces. A full factory final test and performance analysis is performed. Complete test and repair reports are sent to any standard printer.

The Pro will also reassign and eliminate drive defects. Here's how it works: First, a precise media analysis system scans the disk for errors. Defects are mapped out, and effectively "erased." The error correcting system then "trains" the drive to permanently avoid defective areas. Data is stored only on the safe

areas of the disk. Capacity is reduced by an insignificant amount, and the drive works flawlessly once again. Get the technology used by major repair shops and data recovery centers. The Pro repairs all disk defects caused by normal wear. Drives with mechanical damage may not be repairable.




CORPORATE SYSTEMS CENTER

3310 WOODWARD AVE., SANTA CLARA, CA 95054
WWW.DRIVEDUPLICATORS.COM

Call today for high volume multi-drive copiers and CD Duplicators
Sold and intended for backup purposes only. Copyright laws must be observed.


WIRELESS COMMUNICATION

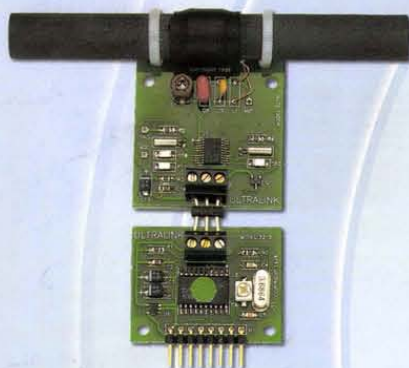

Sometimes a wire just won't do. These handy devices provide wireless solutions for data logging, control, and timekeeping. To demonstrate the operation of all of these products together, call our BASIC Stamp using a terminal emulation program at (916) 624-0160, with 2400 bps 8 N 1 settings. Press the "T" key to display the current time and temperature as transmitted via RF from our rooftop location in Rocklin, California. Details of this project are shown at www.parallaxinc.com.

Atomic Time Clock WWVB Receiver (#27971 - \$79.00)

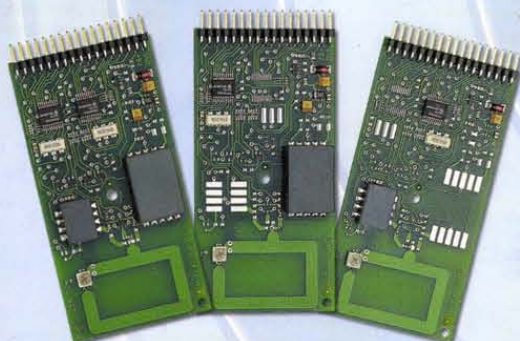Ultralink's WWVB receiver/decoder provides an accurate real time clock based on the National Institute of Standards and Technology radio station WWVB in Fort Collins, Colorado. Receiver and antenna may be separated for maximum signal reception. Operates in the 48 contiguous states and parts of Canada.



433 MHz Transmitter (#27986 - \$59.00)

433 MHz Receiver (#27987 - \$89.00)

433 MHz Transceiver (#27988) \$119.00)

These RF modules provide wireless single and bi-directional serial communication up to 250 between BASIC Stamps using simple SERIN and SEROUT commands. Each module has a built-in antenna, encoder, decoder, and RD data processors for sending serial strings or simple on/off controls.

Mode	Requires
Single-direction communication	(a) Transmitter and Receiver; (b) Transmitter and Transceiver; or (c) Transceiver and Receiver
Bi-directional communication	(a) Two Transceivers.



Cermetek Modem AppKit (#27947 - \$89.00)

Cermetek Modem (#603-00011 - \$69.00)

Okay, this modem isn't wireless, but sometimes only a wire will do! This AppKit consists of a Cermetek modem, components, and PBASIC source code required to let your BASIC Stamp dial a PC running a terminal program and transmit serial data. Includes a DS1620 Digital Thermometer as an example of monitoring remote temperature. Bi-directional communication between two BASIC Stamps requires two modems.

ORDER ONLINE AT
WWW.PARALLAXINC.COM

Or call toll-free 888 512 1024 (international 916 624 8333)

BASIC Stamp and the Parallax logo are registered trademarks of Parallax, Inc.

PARALLAX

Write in 194 on Reader Service Card.

NUTS & VOLTS MAGAZINE
430 PRINCELAND COURT
CORONA, CA 92879-1300

